

Q1) Using K-maps find the simplest form in sum of products of the function $H = f \cdot g$, where f and g are, respectively:

$$f(X,Y,Z,W) = XY + YZ' + Y'W' + X'Z'$$

AND $g(X,Y,Z,W) = (X + Y + W)(Y + Z)(X' + Y' + Z')$

f

| | | | | | |
|----------|----------|----------|---|---|---|
| | | <i>Z</i> | | | |
| | | 1 | 1 | 0 | 1 |
| | | 1 | 1 | 0 | 0 |
| | <i>Y</i> | 1 | 1 | 1 | 1 |
| <i>X</i> | | 1 | 0 | 0 | 1 |
| | | <i>W</i> | | | |

g

| | | | | | |
|----------|----------|----------|---|---|---|
| | | <i>Z</i> | | | |
| | | 0 | 0 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
| | <i>Y</i> | 1 | 1 | 0 | 0 |
| <i>X</i> | | 0 | 0 | 1 | 1 |
| | | <i>W</i> | | | |

f · g is the superset of all zero!

| | | | | | |
|----------|----------|----------|---|---|---|
| | | <i>Y</i> | | | |
| | | 0 | 0 | 0 | 0 |
| | | 1 | 1 | 0 | 0 |
| | <i>X</i> | 1 | 1 | 0 | 0 |
| <i>W</i> | | 0 | 0 | 0 | 1 |
| | | <i>Z</i> | | | |

$$f \cdot g = YZ' + XY'ZW' = (Y+Z)(X+Y)(Z'+W')(Y'+Z')$$

Q2) The Boolean function $F(A,B,C,D) = \sum m(0,2,3,4,8,10,14)$ has the following don't care conditions $d(A,B,C,D) = \sum m(9,11,12,15)$

Implement F using minimum number of gates as:

F in (SOP) = $C'D' + B'C + AC$

F in (POS) = $(C + D')(A + B' + C')$

F' in (SOP) = $C'D + A'BC$


F' in (POS) = $(C + D)(B + C')(A' + C')$

a) NAND-NAND

We use the SOP expression of F:


F

| | | | | | |
|----------|----------|----------|---|---|---|
| | | C | | | |
| | | 1 | 0 | 1 | 1 |
| | | 1 | 0 | 0 | 0 |
| | A | X | 0 | X | 1 |
| B | | 1 | X | X | 1 |
| | | D | | | |

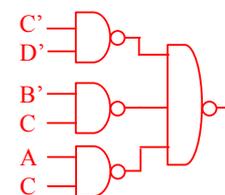

b) NOR-NOR

We use the SOP expression of F:

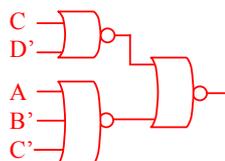


c) NAND-AND

Start with POS expression of F: $F = (C + D')(A + B' + C')$

Now double invert each SUM terms (won't change the function) $F = (C + D')''(A + B' + C')''$

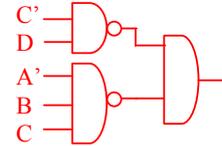Expand the 1st inversion $\rightarrow F = (C'D)')(A'BC)'$ (NAND-AND)




d) NOR-OR

Start with SOP expression of F: $F = C'D' + B'C + AC$

Now double invert each AND terms (won't change the function) $F = (C'D')'' + (B'C)'' + (AC)''$

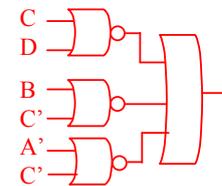
Expand the 1st inversion $\rightarrow F = (C+D)' + (B+C')' + (A'+C)'$



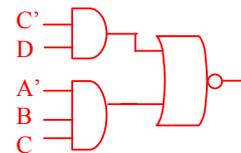e) AND-NOR

AND-OR-Invert \rightarrow We use F' SOP form for the AND-OR, then the Invert will get us F!


F' in (SOP) = $C'D + A'BC \rightarrow F = (C'D + A'BC)'$



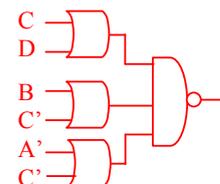f) OR-NAND

OR-AND-Invert \rightarrow We use F' POS form for the OR-AND, then the Invert will get us F!

F' in (POS) = $(C + D)(B + C')(A' + C) \rightarrow F = [(C + D)(B + C')(A' + C)]'$



g) Which of the above implementations are equivalent (i.e. logically the same)


Since we have not used any Don't Care condition as 0 and 1 to obtain all the above expressions, then all expressions are equivalent (logically identical)

If someone uses the same X as a 0 and then as a 1 to obtain two expressions, these expressions won't be equivalent.

Q.3. Implement the logic diagram below:

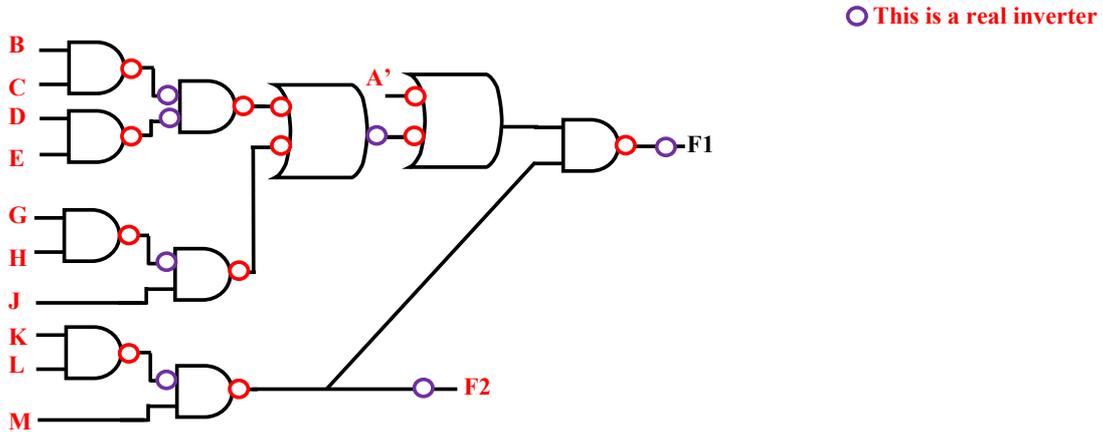a) Using 2-input NAND gates only

We need first to convert all gates (ANDs and ORs) to 2-input gates, then we do the logic transformations: AND-Invert is a NAND, and Invert-OR is also a NAND .. All bubbles are inserted in pairs not to alter the logic!



b) Using 2-input NOR gates only

We need first to convert all gates (ANDs and ORs) to 2-input gates, then we do the logic transformations: OR-Invert is a NOR, and Invert-AND is also a NOR .. All bubbles are inserted in pairs not to alter the logic!

