

Power Amplifiers Homework Solution

5.1-2 : $(P_{L,ac})_{\max} = 2W$, $R_L = 10\Omega$

$$(P_{L,ac})_{\max} = \frac{1}{2} I_{cm,\max}^2 R_L = 2W$$

$$\therefore I_{cm,\max} = 0.6324 A$$

$$\therefore I_{CQ} \geq 0.6324 A$$

$$\therefore \text{let } I_{CQ} = 0.6324 A \quad (\text{minimum rating})$$

$$P_{CC} = V_{CC} I_{CQ} = 9.5W$$

$$\eta_{\max} = \frac{(P_{L,ac})_{\max}}{P_{CC}} \times 100\% = 21\%$$

$$P_{C,\max} = P_{CC} = 9.5W$$

$$i_C(t)_{\max} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

$$R_{ac} = R_L = 10\Omega$$

$$\therefore i_C(t)_{\max} = 2.1324 A$$

$$V_{CE(t),\max} = V_{CEQ} + R_{ac} I_{CQ}$$

$$V_{CEQ} = V_{CC}$$

$$\therefore V_{CE(t),\max} = 21.324 V$$

5.2-1 $(P_{L,ac})_{\max} = 2W$, $V_{CC} = 20V$

$$\eta = \eta_{\max} = 50\%$$

$$\eta_{\max} = \frac{(P_{L,ac})_{\max} \times 100\%}{P_{CC}}$$

$$\therefore P_{CC} = 4W$$

$$P_{CC} = V_{CC} I_{CQ} = 4W$$

$$\therefore I_{CQ} = 0.2A$$

$$i_c(t)_{\max} = 2I_{CQ} = 0.4A$$

$$V_{CE(t),\max} = 2V_{CC} = 40V$$

$$P_{C,\max} = P_{CC} = 4W$$

$$I_{CQ} = \frac{V_{CC}}{R_L^-}$$

$$\therefore R_L^- = 100\Omega$$

$$R_L^- = N^2 10$$

$$\therefore N = 4$$

5.3-2 : $BV_{CE0} = 40V$, $(P_{L,ac})_{max} = 10W$
 $R_L = 10\Omega$

$$2V_{CC} = 40V = BV_{CE0}$$

$$\therefore V_{CC} = 20V$$

$$(P_{L,ac})_{max} = \frac{1}{2} \frac{V_{CC}^2}{R_L} = 10W$$

$$\therefore R_L = 20\Omega$$



$$R_L = N^2 10 , \therefore N = 1.414$$


$$P_{C,max} = \frac{1}{\pi^2} \frac{V_{CC}^2}{R_L} = 2.07W$$

5.4-2 : $V_{BE} = 0.65V$; $V_{CC} = 20V$

$$V_{BE} = 0.65 = \frac{10k}{10k + R_X} (20V) \Rightarrow$$

$$R_X = 298k\Omega$$

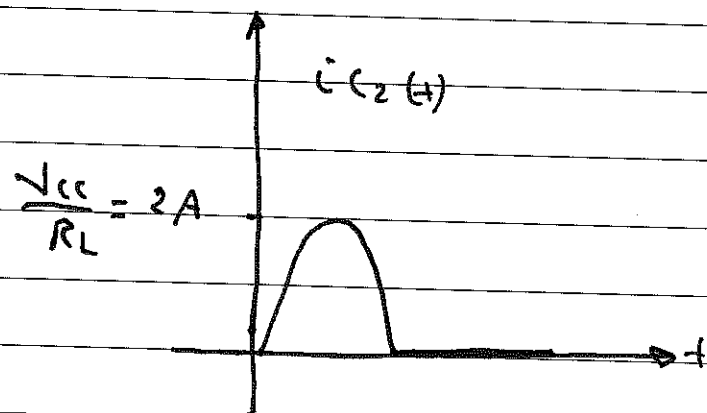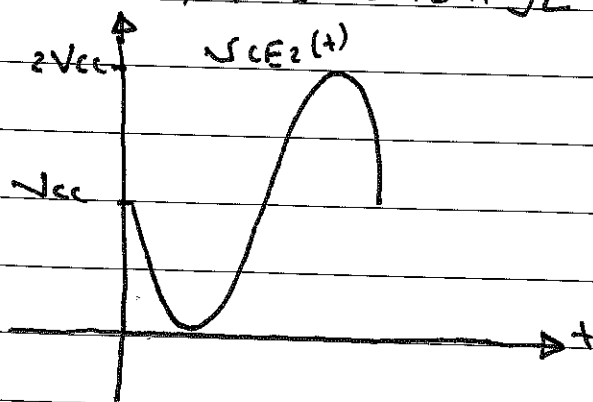

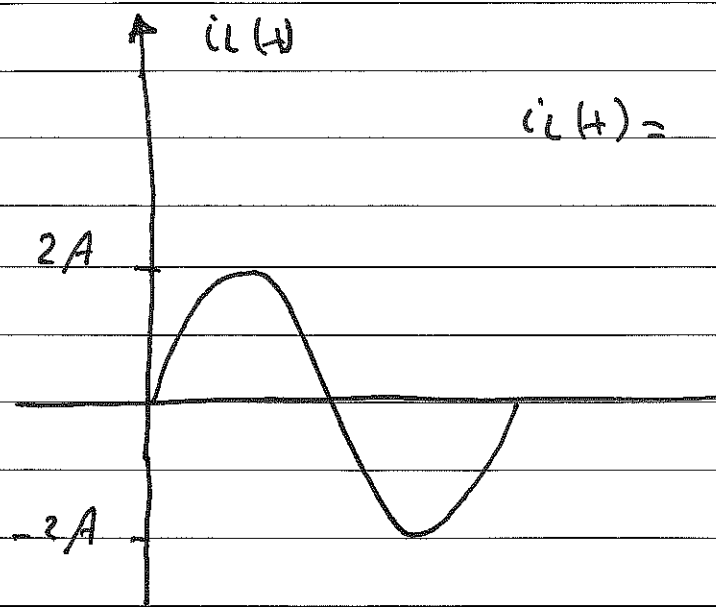

$$i_L(t) = i_{C2}(t) - i_{C1}(t)$$

$$c) (P_{L,ac})_{max} = \frac{1}{2} I_{cm,max}^2 R_L$$

$$I_{cm,max} = \frac{V_{cc}}{R_L} = 2A$$

$$\therefore (P_{L,ac})_{max} = 20W$$

$$P_{cc} = \frac{2}{\pi} I_{cm} V_{cc} = 25.5W$$

$$\eta_{max} = \frac{(P_{L,ac})_{max}}{P_{cc}} \times 100 \% = 78.5 \%$$

$$d) I_{cm} = \frac{2}{\pi} \frac{V_{cc}}{R_L} = 1.27A$$

$$P_{c,max} = \frac{1}{\pi^2} \frac{V_{cc}^2}{R_L} = 4W$$

14.1 :

$$V_o(t), \max = V_{CC} - V_{CE1, \text{sat}} = 5 - 0.3 = 4.7 \text{ V}$$

$$V_i(t) = V_{BE1}(t) + V_o(t) ; \therefore V_i(t) = 5.4 \text{ V}$$

$$I = \frac{V_{CC} - V_{BE2}}{R} = \frac{5 - 0.7}{1 \text{ k}} = 4.3 \text{ mA}$$

$$V_o(t), \min = -V_{CC} + V_{CE2, \text{sat}} = -4.7 \text{ V}$$

or

$$V_o(t), \min = -R_L I = -4.3 \text{ V}$$

$$\therefore V_o(t), \min = -4.3 \text{ V}$$

$$\therefore \text{The corresponding } V_i(t), \min = -4.3 + 0.7 = -3.6 \text{ V}$$

If the EB junction of Q_3 is made twice as big as that of Q_2

$$I = \frac{I_R}{2} = 2.15 \text{ mA}$$

$$V(t), \max = 4.7 \text{ V as before ; } V_i(t), \max = 5.4 \text{ V}$$

$$V_o(t), \min = -I R = -2.15 \text{ V}$$

$$V_i(t), \min = -2.15 + 0.7 = -1.45 \text{ V}$$

If the EB junction of Q_3 is made half as big as that of Q_2

$$I = 2 I_R = 8.6 \text{ mA}$$

$$V_o(t), \max = 4.7 \text{ V as before ; } V_i(t), \max = 5.4 \text{ V}$$

$$V_o(t), \min = -4.7 \text{ V ; } V_i(t), \min = -4 \text{ V}$$

14.

$$I_T = 1\text{mA} ; I_R = 0.5\text{mA} ; \therefore I_C = 0.5\text{mA}$$


$$\therefore V_{BE} = V_T \ln \frac{0.5\text{mA}}{1\text{mA}} = 0.683\text{V}$$

$$\beta = \infty \rightarrow I_B = 0$$

$$\therefore R_1 = R_2 = \frac{V_{BE}}{I_R} = \frac{0.683\text{V}}{0.5\text{mA}} = 1.366\text{k}\Omega$$

$$V_{BB} = 2V_{BE} = 1.366\text{V}$$

14.30 :

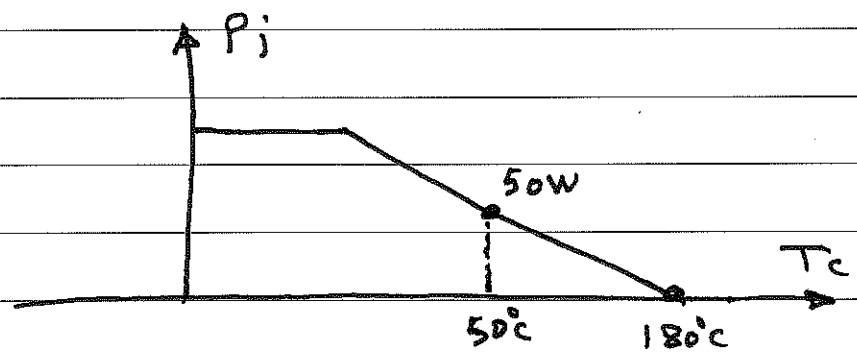

$$\Theta_{jc} = \frac{180 - 50}{50} = 2.6^\circ\text{C/W}$$

$$T_j - T_s = \Theta_{js} P_j$$

$$\Theta_{js} = \Theta_{jc} + \Theta_{cs} = (2.6 + 0.6) = 3.2^\circ\text{C/W}$$

Assume Case II : $T_j = T_{j,\text{max}}$

$$T_j - T_s = \Theta_{js} P_j$$

$$T_{j,\text{max}} - T_s = \Theta_{js} P_j ; P_j = 30\text{W}, \Theta_{js} = 3.2^\circ\text{C/W}$$

$$\therefore T_s = 84^\circ\text{C}$$

$$T_s - T_a = \theta_{sa} P;$$

$$84 - 39 = (\theta_{sa})(30)$$

$$\therefore \theta_{sa} = 1.5^\circ/\text{W}$$

$$\text{heat sink length} = \frac{4.5}{1.5} = 3 \text{ cm}$$