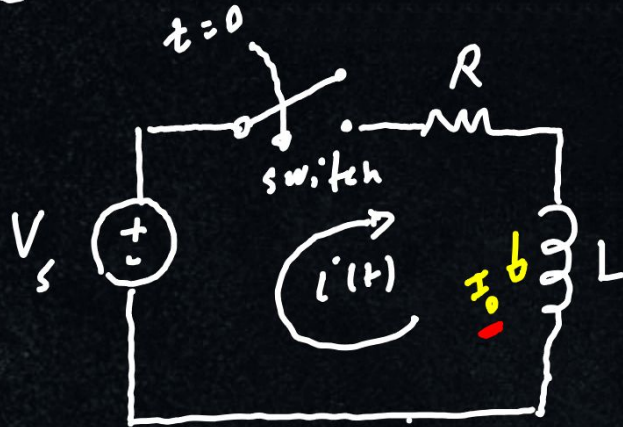


CH7: First Order RL & RC Circuits

(DC sources with RL & RC circuits)

① First order RL circuit



I_0 : initial inductive current.

KVL in the loop

$$V_s = Ri + L \frac{di}{dt} \Rightarrow \frac{V_s - Ri}{L} = \frac{di}{dt}$$

$$t = -\frac{L}{R} \ln \left| \frac{i - V_s/R}{I_0 - V_s/R} \right|$$

when $t \geq 0$



$$dt = \frac{L}{V_s - Ri} di$$
$$\int_0^t dt = \int_{I_0}^i \frac{-L}{R} \frac{1}{i - \frac{V_s}{R}} di$$
$$t \Big|_0^t = -\frac{L}{R} \ln \left| i - \frac{V_s}{R} \right| \Big|_{I_0}^i$$



Solve for i

$$-\frac{R}{L}t = \ln \left| \frac{i - V_s/R}{I_0 - V_s/R} \right|$$

$$i - \frac{V_s}{R} = \left(I_0 - \frac{V_s}{R} \right) e^{-Rt/L}$$

$$i = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau} ; \quad \tau = \frac{L}{R} \text{ time-constant}$$

$$i = I_f + (I_0 - I_f) e^{-t/\tau}$$

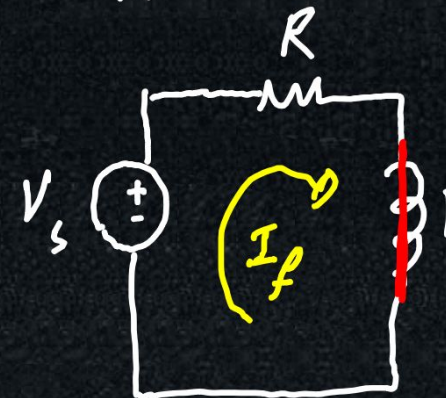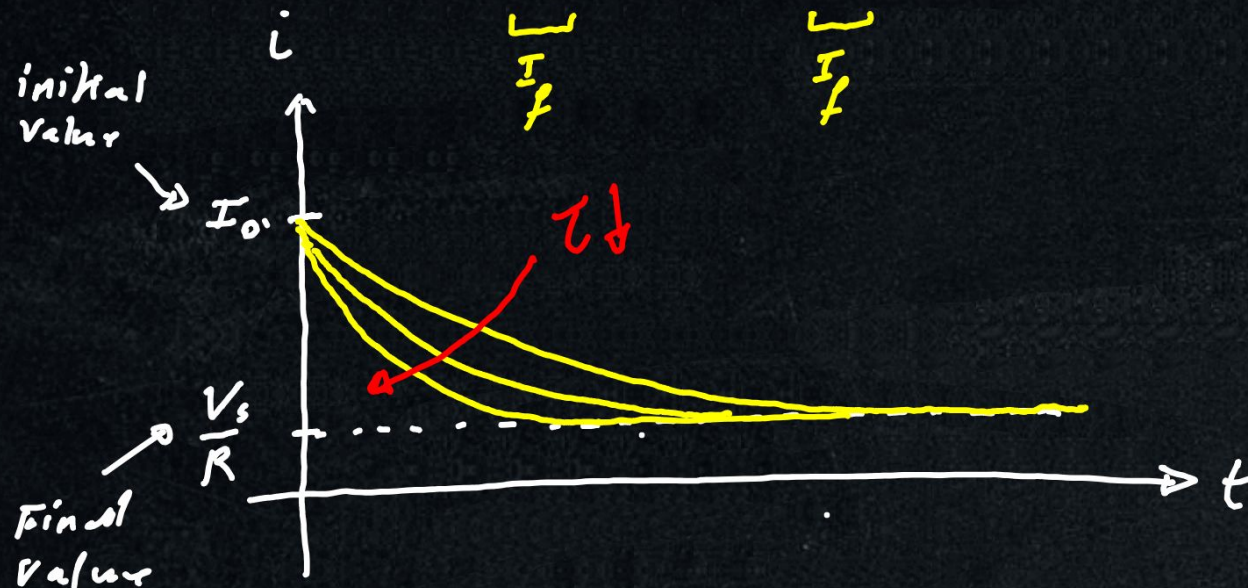

it appears
as a short
circuit at
 $t \rightarrow \infty$

$$I_f = \frac{V_s}{R} = \text{Final Value}$$


When $V_s \neq 0$ or $I_f \neq 0 \Rightarrow$ step response.



When $V_s = 0$ or $I_f = 0 \Rightarrow$ Natural response



First order RL circuit

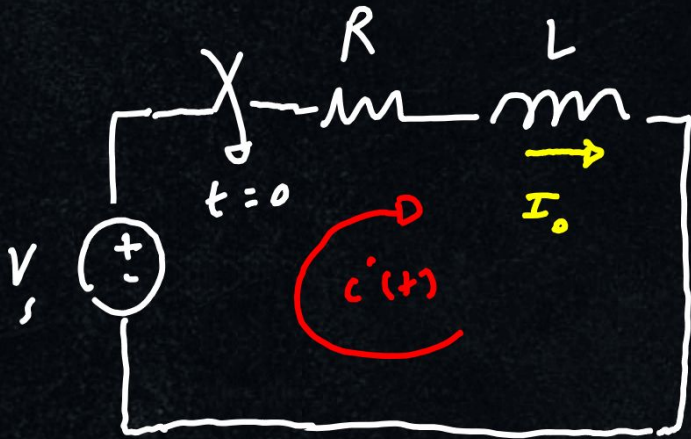

$$V_s = Ri + L \frac{di}{dt} \quad \text{1st order differential equation}$$

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}; \quad \tau = L/R$$


$$i(0) = I_0$$

$$i(\infty) = I_f = \frac{V_s}{R}$$

$$i(t) = I_f + (I_0 - I_f) e^{-t/\tau}$$

Note: At $t \rightarrow \infty \Rightarrow I_f = \frac{V_s}{R}$ L is short circuit

$$t \geq 0$$

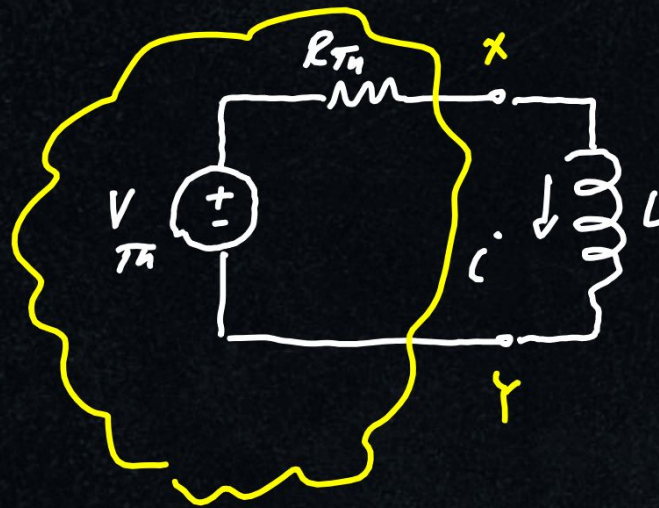


Thevenin
Equivalent


$$i = \frac{V_{Th}}{R_{Th}} + \left(I_0 - \frac{V_{Th}}{R_{Th}} \right) e^{-t/\tau};$$

$$\tau = \frac{L}{R_{Th}}.$$

EX :-

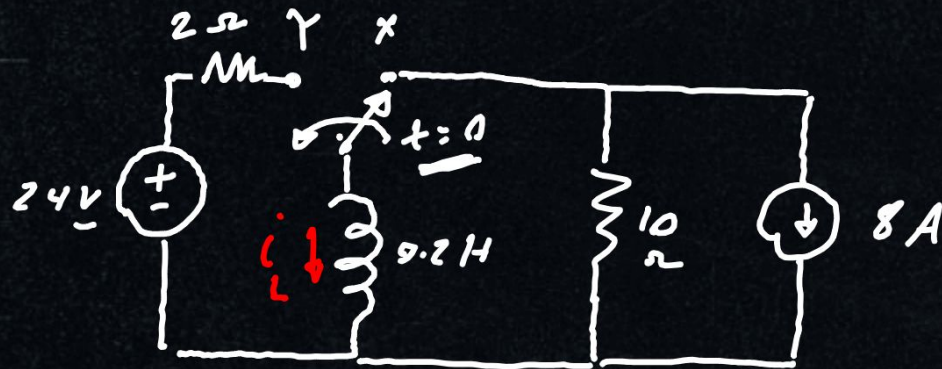

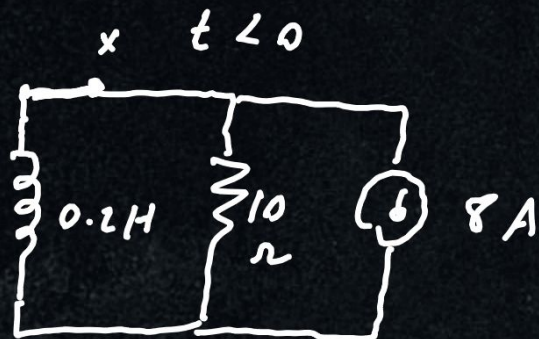The switch is set in position x for a long time. At $t=0$, the switch moves to position y . Calculate $i(t)$ $t \geq 0$?



$t = 0^-$ switch at position x
 $t = 0^+$ switch at position y

L is a current continuous device


$$V_L = L \frac{d(i_L)}{dt} \rightarrow \text{continuous}$$

$$i_L(t^-) = i_L(t^+)$$

$$i_L(0^-) = i_L(0^+) = i_L(0) = I_0$$

At $t=0$, i_L reaches its steady state value $\Rightarrow L$ appears as a short circuit


$$\underline{t = 0^-}$$

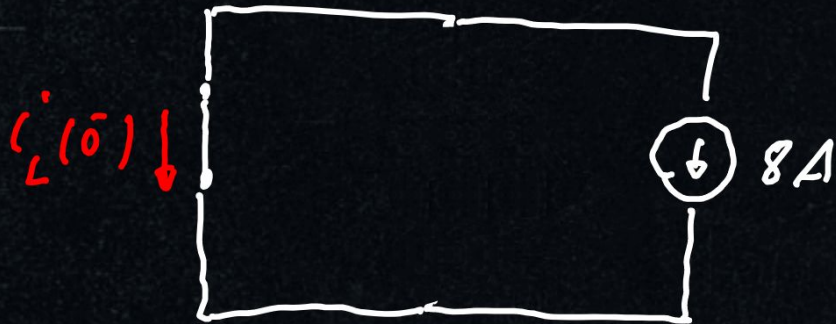

$$i_L'(0^-) = -8 \text{ A}$$

$$i_L'(0^-) = i_L'(0^+) = i_L'(0) = \underline{\underline{I_0 = -8 \text{ A}}}$$

$$\underline{t \geq 0}$$

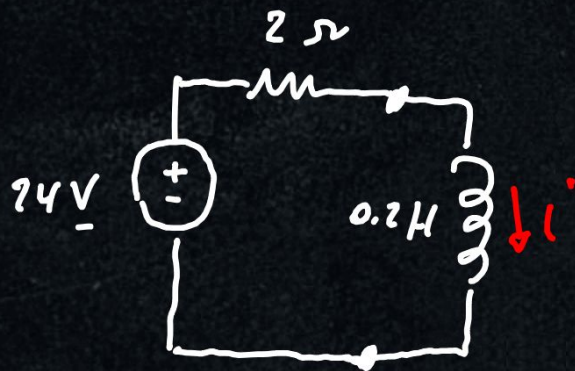

$$V_{Th} = 24 \text{ V}, R_{Th} = 2 \Omega$$


$$i = \frac{V_{Th}}{R_{Th}} + \left(I_0 - \frac{V_{Th}}{R_{Th}} \right) e^{-t/\tau}$$

$$\tau = \frac{L}{R_{Th}} = \frac{0.2}{2}$$

$$\tau = 0.1 \text{ s}$$

$$i = 12 - 20 e^{-10t} \text{ A}, t \geq 0$$


$$\underline{t = 0^-}$$

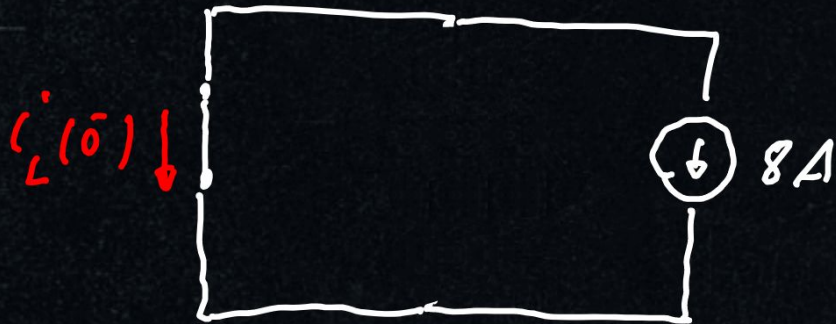

$$i_L'(0^-) = -8 \text{ A}$$

$$i_L'(0^-) = i_L'(0^+) = i_L'(0) = \underline{\underline{I_0 = -8 \text{ A}}}$$

$$\underline{t \geq 0}$$

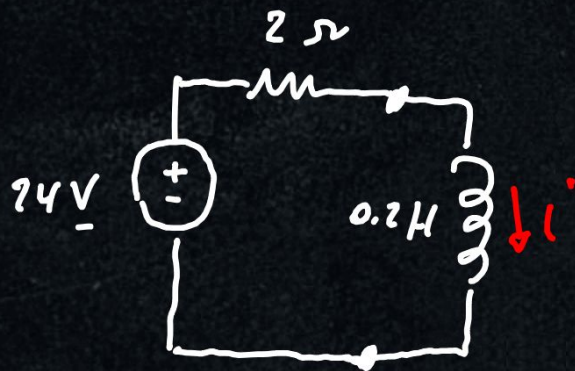

$$V_{Th} = 24 \text{ V}, R_{Th} = 2 \Omega$$

$$i = \frac{V_{Th}}{R_{Th}} + \left(I_0 - \frac{V_{Th}}{R_{Th}} \right) e^{-t/\tau}$$

$$\tau = \frac{L}{R_{Th}} = \frac{0.2}{2}$$


$$\tau = 0.1 \text{ s}$$

$$i = 12 - 20 e^{-10t} \text{ A}, t \geq 0$$

$$i_L = 12 - 20 e^{-10t}$$




EX:-

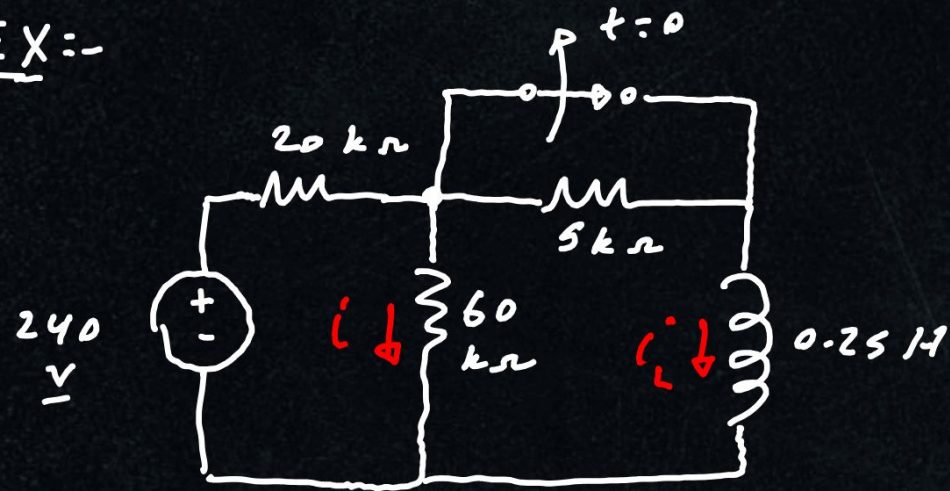


The switch has been closed for a long time. The switch opens at $t=0$. Find $i_L(t)$ & $i(t)$

$t=0^-$ L is a short circuit

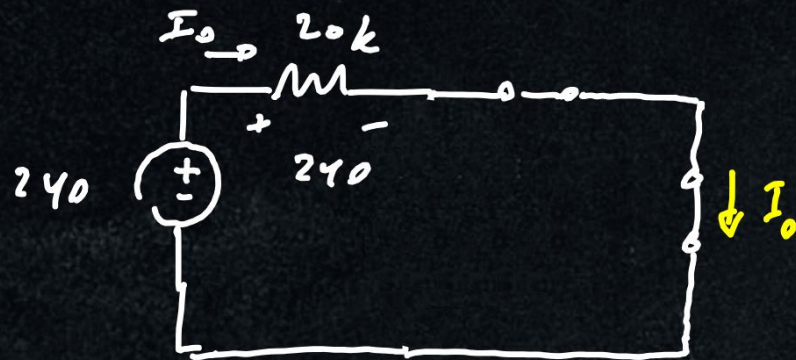


$$I_0 = \frac{240}{20} = 12\text{ mA}$$

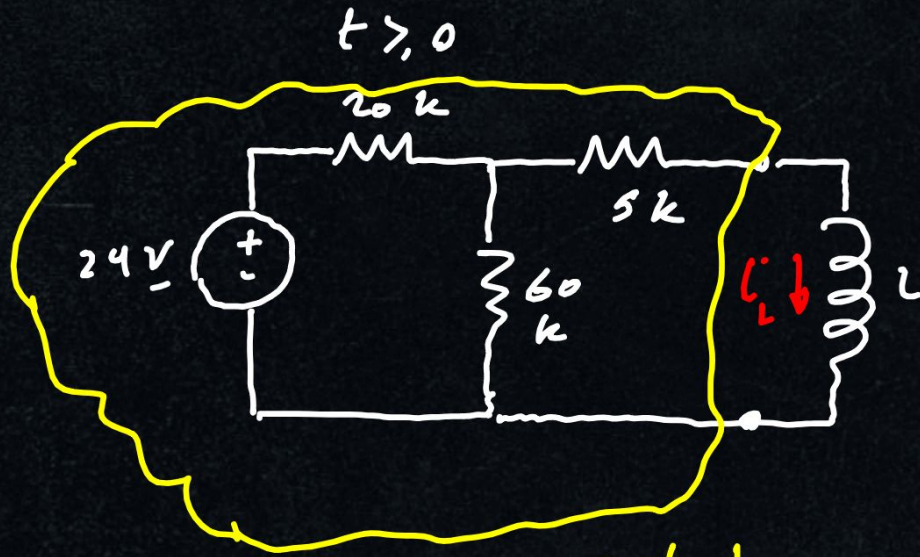


Thvenin Equivalent circuit
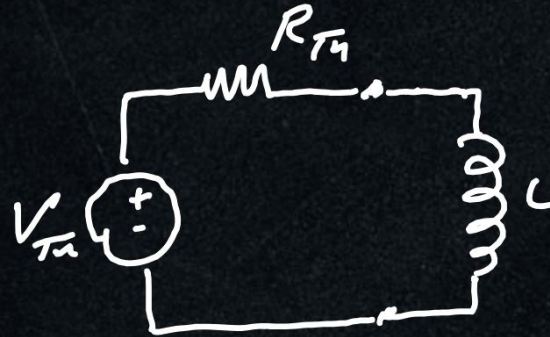
$$i_L = \frac{V_{Th}}{R_{Th}} + \left(I_0 - \frac{V_{Th}}{R_{Th}} \right) e^{-t/\tau} \quad t > 0.$$




$V_{Th} = V_{oc}$

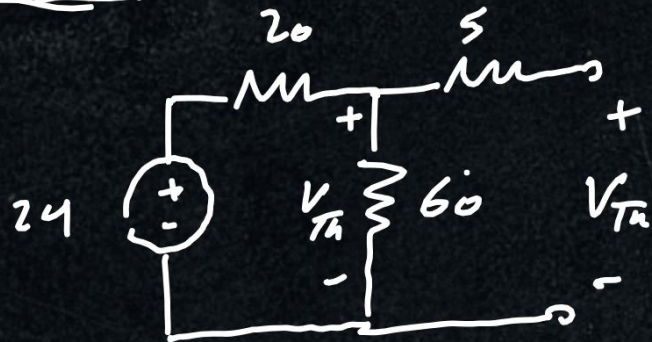

$$V_{Th} = \frac{60}{60 + 20} (24) = 18 \text{ V}$$

R_{Th} "Method II"

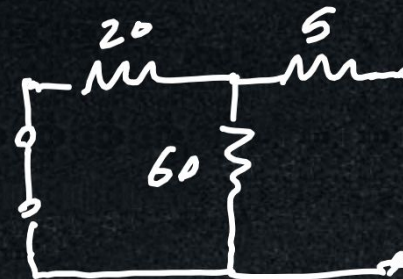

$$R_{Th} = (20 // 60) + 5$$

$$R_{Th} = 20 \text{ k}\Omega$$

$$\tau = \frac{L}{R_{Th}} = \frac{0.75}{20,000} = 12.5 \mu\text{sec}$$

$$i_L = \frac{V_{Th}}{R_{Th}} + \left(I_o - \frac{V_{Th}}{R_{Th}} \right) e^{-\frac{t}{\tau}}$$

$$V_{Th} = 180 \text{ V}$$


$$R_{Th} = 20 \text{ k}\Omega$$

$$\tau = 12.5 \mu\text{s}$$

$$I_o = 12 \text{ mA}$$

$$i_L = 90 + (12 - 90) e^{-80,000t} \text{ mA}, t \geq 0$$

$t > 0$

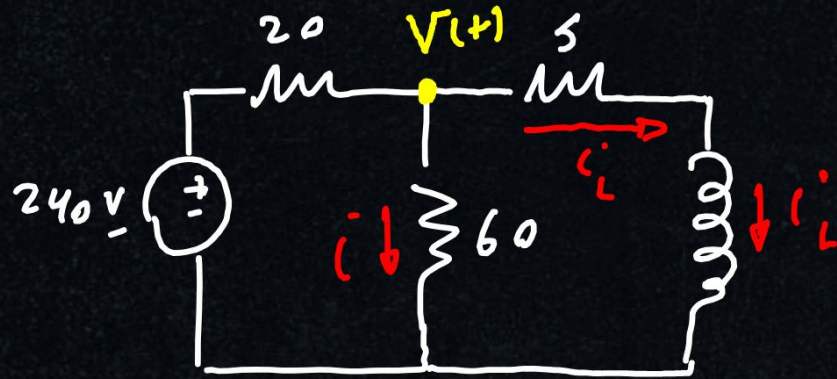

$$\frac{V - 240}{20} + \frac{V}{60} + i_L = 0$$

$$3V - 3(240) + V + 60i_L = 0$$

$$4V = 720 - 60i_L$$

$$V = 180 - 15i_L$$

$$i = \frac{V}{60} = 3 - 0.25i_L$$

$$i = 3 - 0.25i_L$$


$$i' = \frac{V_{Th}}{R_{Th}} + \left(I_0 - \frac{V_{Th}}{R_{Th}} \right) e^{-t/\tau}$$

180
20

$$i' = I_f + (I_0 - I_f) e^{-t/\tau}$$

To find I_f , draw the circuit at $t \rightarrow \infty$ with L is short circuit

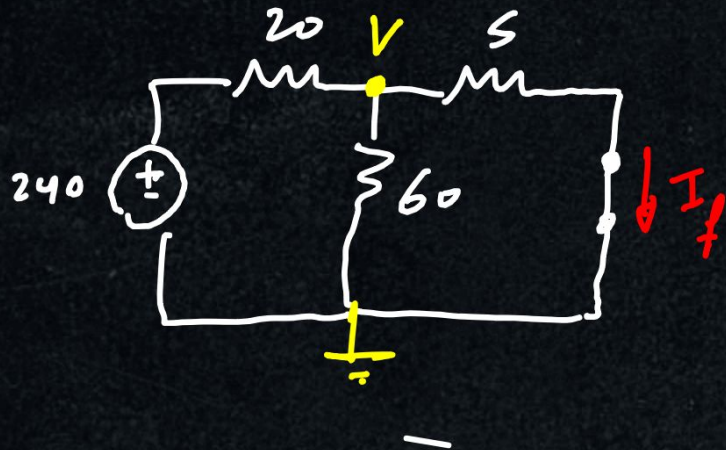$t \rightarrow \infty$ (L is short circuit)




$$\frac{V - 240}{20} + \frac{V}{60} + \frac{V}{5} = 0$$

$$3V - 720 + V + 12V = 0$$

$$16V = 720 \Rightarrow V = 45V$$


$$I_f = \frac{45}{5} = 9mA$$

EX :-

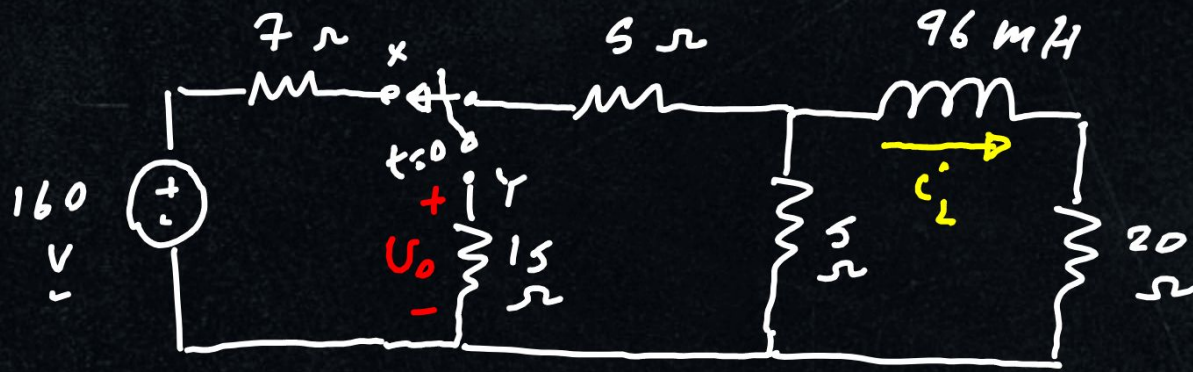

The switch has been in position X for a long time. At $t=0$, the switch moves to position Y. Find $U_0(t)$ $t \geq 0$.

$t=0^-$ (L is s/c)

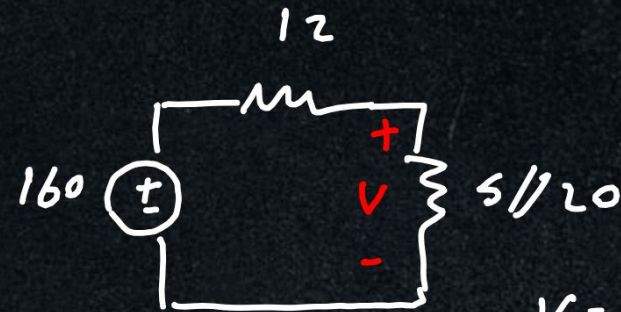

$$V = \frac{4}{16} 160 = 40\text{V}$$

$$I_0 = \frac{40}{20} = 2\text{A}$$

$$\underline{t > 0}$$



$$V_{Th} = 0$$

"Natural Response"

$$i_L' = I_0 e^{-t/\tau}, \quad t > 0, \quad A$$

$$I_0 = 2A$$

$$\tau = L/R_{Th}$$

R_{Th} "Method II"

$$R_{Th} = [(5 + 15) \parallel 5] + 20 = 24 \Omega$$

$$\tau = 96/24 = 4 \text{ ms}$$


$$i_L'(t) = 2 e^{-250t} \quad A, \quad t > 0$$

$$i_1' = \frac{5}{25} (-i_L')$$

$$i_1' = -0.4 e^{-250t}$$

$$V_o = 15 i_1' = -6 e^{-250t} \quad \underline{\underline{V}}$$

$$\underline{t > 0}$$

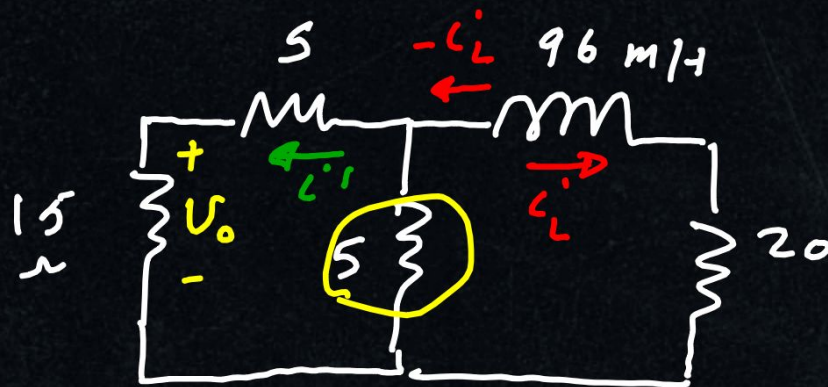

$$V_{Th} = 0$$

"Natural Response"

$$i_L' = I_0 e^{-t/\tau}, \quad t > 0, \quad A$$

$$I_0 = 2A$$

$$\tau = L/R_{Th}$$

R_{Th} "Method II"

$$R_{Th} = [(5 + 15) \parallel 5] + 20 = 24 \Omega$$

$$\tau = 96/24 = 4 \text{ ms}$$


$$i_L'(t) = 2 e^{-250t} \quad A, \quad t > 0$$

$$i_1' = \frac{5}{25} (-i_L')$$

$$i_1' = -0.4 e^{-250t}$$

$$V_o = 15 i_1' = -6 e^{-250t} \quad \underline{\underline{V}}$$

Natural + Step Response of RC circuit

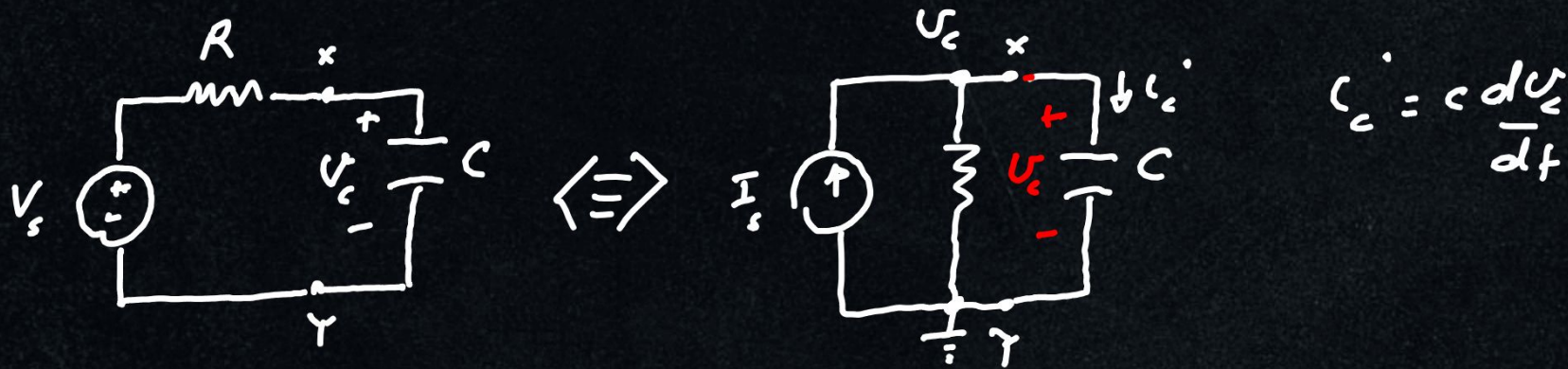

$$\text{KCL at } V_c :- -I_s + \frac{V_c}{R} + C \frac{dV_c}{dt} = 0$$

$$I_s = \frac{V_c}{R} + C \frac{dV_c}{dt} \quad \text{1st order diff. equation (Linear)}$$

$$\frac{1}{C} \left(I_s - \frac{V_c}{R} \right) = \frac{dV_c}{dt} \Rightarrow -\frac{1}{RC} V_c + \frac{1}{C} I_s = \frac{dV_c}{dt} \Rightarrow \frac{1}{RC} [V_c - RI_s] = \frac{dV_c}{dt}$$

$$\frac{-1}{RC} [V_c - RI_s] = \frac{dV_c}{dt} \Rightarrow \int_0^t \frac{-1}{RC} dt = \int_{V_0}^{V_c} \frac{dV_c}{V_c - RI_s}$$

where V_0 is the initial capacitive voltage

$$\frac{-1}{RC} t = \ln |V_c - RI_s| \Big|_{V_0}^{V_c} = \ln \left| \frac{V_c - RI_s}{V_0 - RI_s} \right|$$



$$(V_c - RI_s) = (V_0 - RI_s) e^{-t/RC}$$

$$V_c = RI_s + (V_0 - RI_s) e^{-t/\tau} ; \quad \tau = RC \quad +30$$

when $I_s \neq 0 \Rightarrow$ step response $\rightarrow V_c = RI_s + (V_0 - RI_s) e^{-t/\tau}$

when $I_s = 0 \Rightarrow$ Natural response $\rightarrow V_c = V_0 e^{-t/\tau}$

$$V_c = RI_s + (V_0 - RI_s) e^{-t/\tau} ; t \geq 0$$

$$V_c(0) = V_0 = V_c(0^-) = V_c(0^+) = V_c(0)$$



↓
initial


$V_c(\infty) = RI_s \Rightarrow$ The capacitor appears as an open circuit

↓
Final

$$V_c = V_{c,ff} + (V_{c,i} - V_{c,ff}) e^{-t/\tau}$$

↓ ↓
Final initial

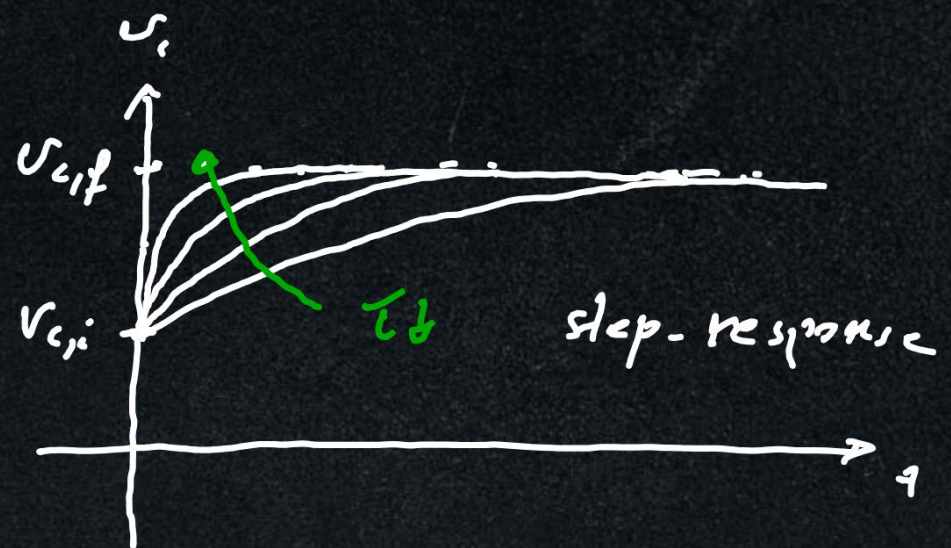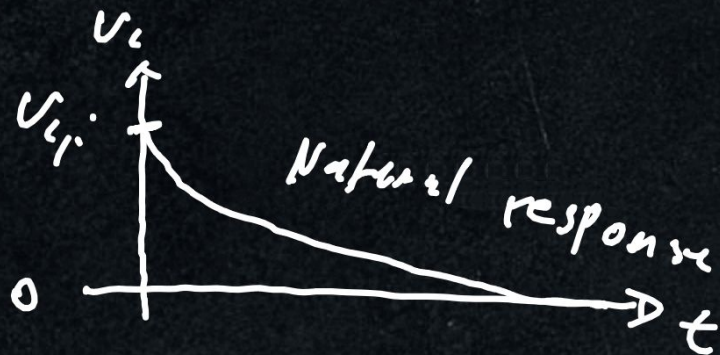

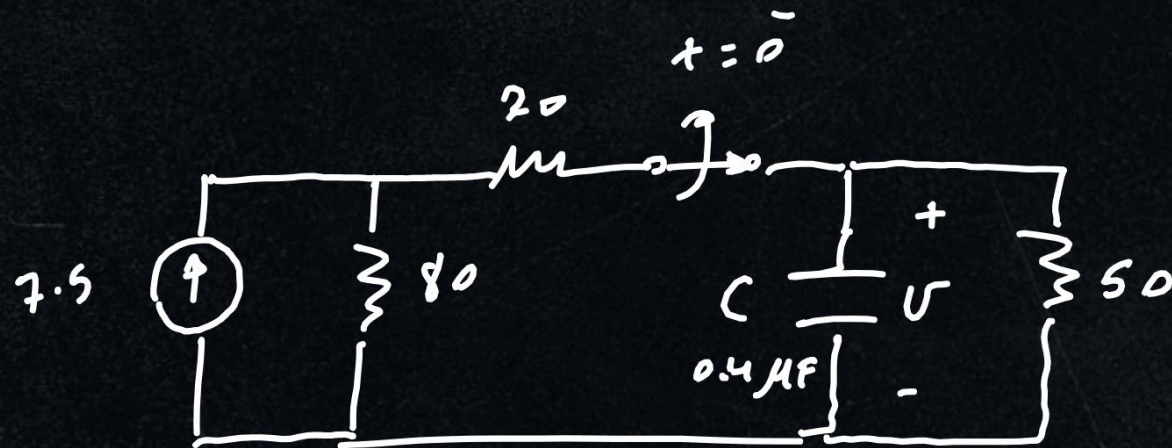


Find $v(t)$ $t \geq 0$

$t = 0^+$



$$V_o = \frac{50}{150} (600) = 200 \text{ V}$$

$$t \geq 0$$

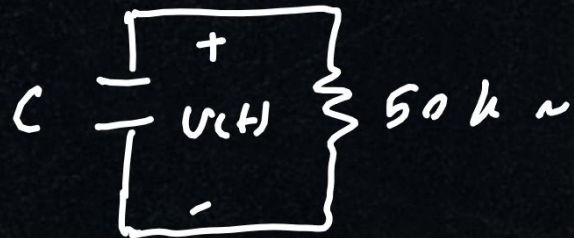

Natural Response


$$I_s = 0$$

$$V(t) = V_0 e^{-t/\tau}, \quad t \geq 0$$

$$\tau = RC = 50 \times 10^3 \times 0.4 \times 10^{-6} = 20 \text{ ms}$$

$$V(t) = 200 e^{-50t} \quad t \geq 0, \quad \checkmark$$

Ex :-

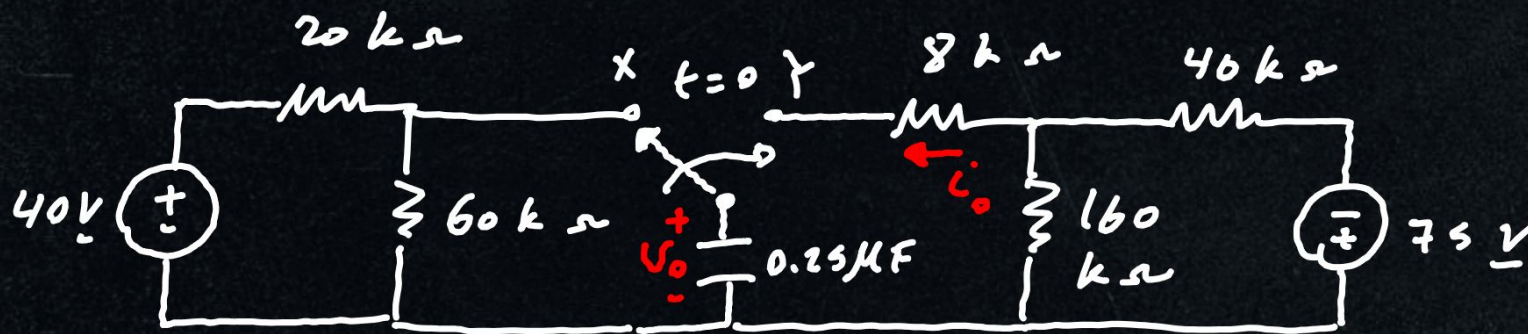


The switch has been in position X for a long time. At $t=0$, the switch moves to position Y. Find $V_0(t)$ + $i_0(t)$ $t > 0$ + $t > 0^+$.

$t=0^-$ (C is o/c)




$$V_0 = \frac{60}{60+20} (40) = 30 \text{ V}$$

$t > 0$

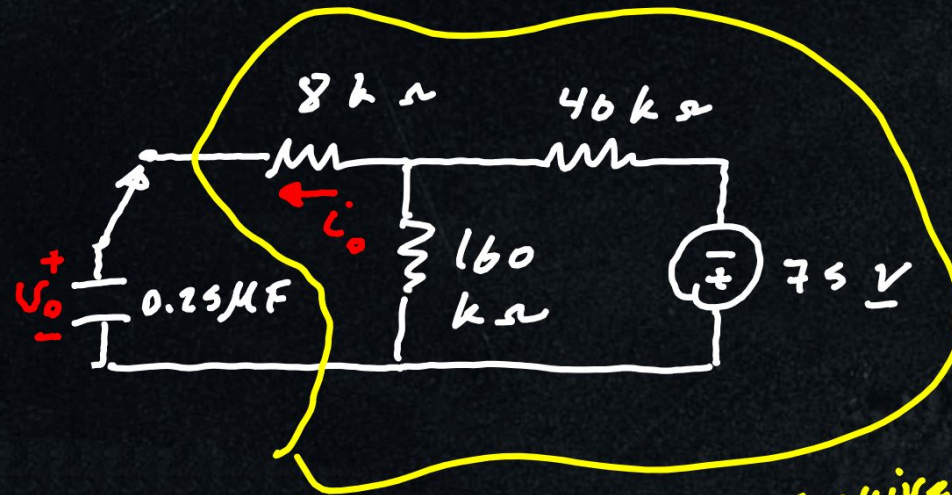


$V_{Th} ??$

Thevenin Equivalent circuit

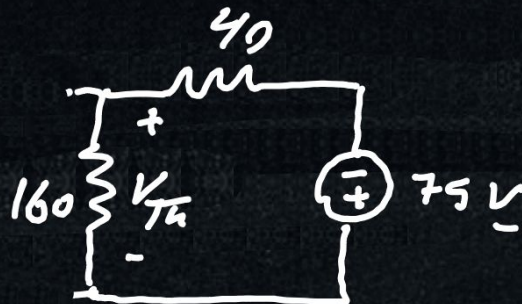

$$V_{Th} = \frac{160}{160 + 40} (-75) = -60 \text{ V}$$

$R_{Th} ??$ "Method II"

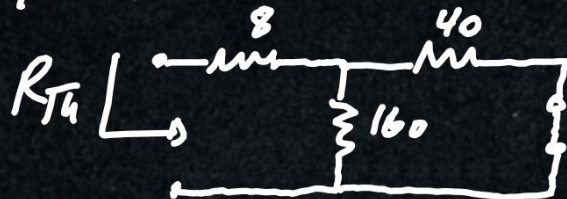


$$R_{Th} = (40 \parallel 160) + 8 = 40 \text{ k}\Omega$$

$$\tau = R_{Th} C = 40 \times 0.25 = 10 \mu\text{s}$$

$$V_{Th} = -60 \text{ V}$$

$$\tau = 10 \text{ msec}$$

$$R_{Th} = 40 \text{ k}\Omega$$

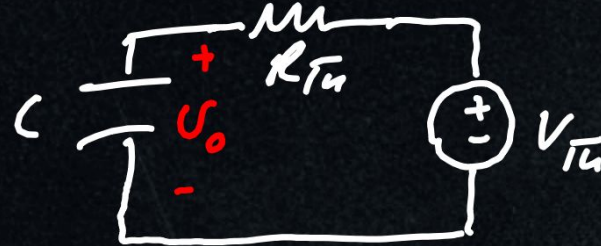

$$V_o = \underbrace{R_{Th} I_N}_{V_{Th}} + \underbrace{(V_o - R_{Th} I_N)}_{V_{Th}} e^{-t/\tau}$$

$$V_o = -60 + (30 - -60) e^{-100t}$$

$$V_o = -60 + 90 e^{-100t} \text{ V}, t \geq 0$$




$$i_o = C \frac{dV_o}{dt}$$

$$V_o = -60 + 90e^{-100t} \quad t > 0$$

$$i_o = (0.25 \times 10^{-6}) (-9000 e^{-100t})$$

$$i_o = -2.25 e^{-100t} \text{ mA}, \quad t > 0^+$$

EX :-

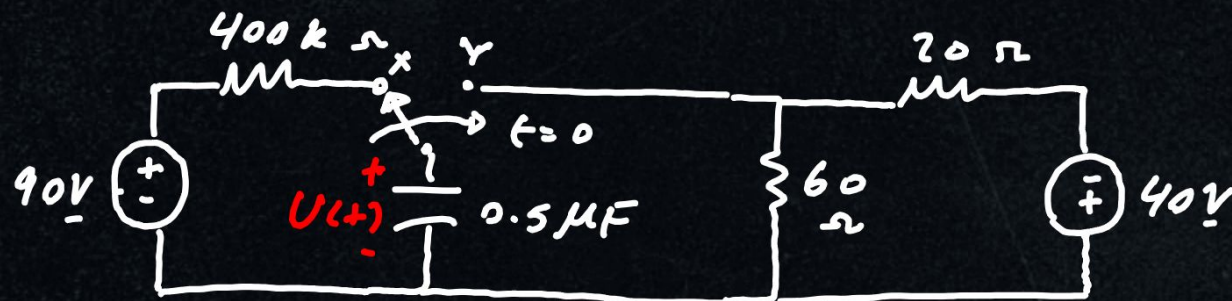

The switch has been in position X for a long time. At $t=0$, the switch moves to position Y. Calculate $V(t)$ $t > 0$?


$t = 0^-$ (C is o/c)



$$V_0 = 90 \text{ V}$$


Thévenin equivalent circuit

$t > 0$

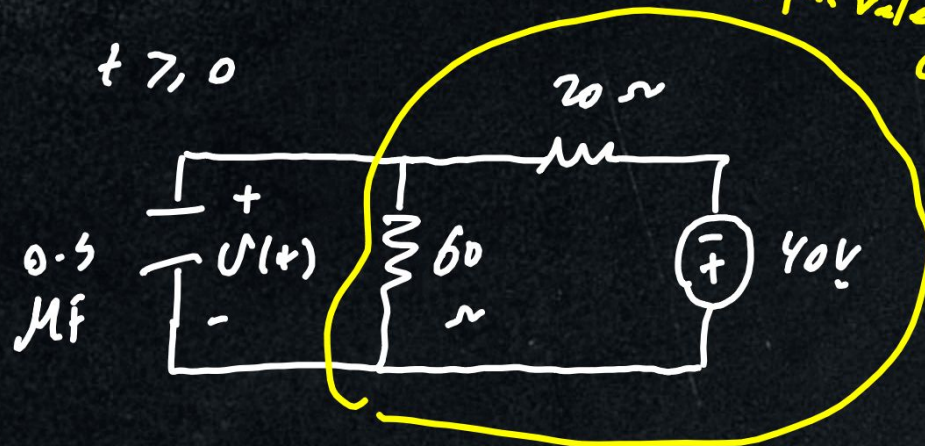


step response

$V_{Th} ??$

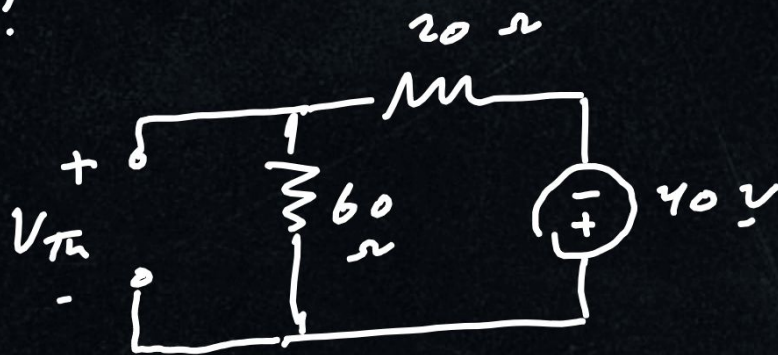

$$V_{Th} = \frac{60}{60+20} (-40) = -30\text{V}$$

R_{Th} "Method II"

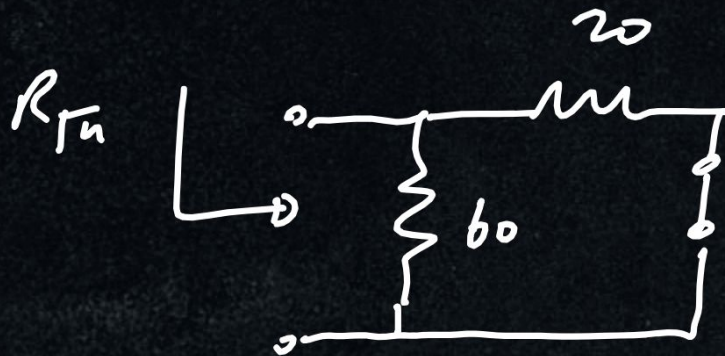

$$R_{Th} = 20 // 60 = 15\ \Omega$$

$$\tau = R_{Th} C = 15 (0.5 \times 10^{-6}) = 7.5\ \mu\text{s}$$

$$V(t) = V_{Th} + (V_0 - V_{Th}) e^{-t/\tau}$$

$$V(t) = -30 + (90 - -30) e^{-1.33 \times 10^5 t} \quad \text{V, } t \geq 0$$


EX:-



The two switches have been closed for a long time.
Find $i_L(t)$ $t > 0$?

$$i_L(t) = \begin{cases} i_{L1} & 0 \leq t \leq 35 \\ i_{L2} & t > 35 \end{cases}$$

$t = 0^-$ (L is s/c)

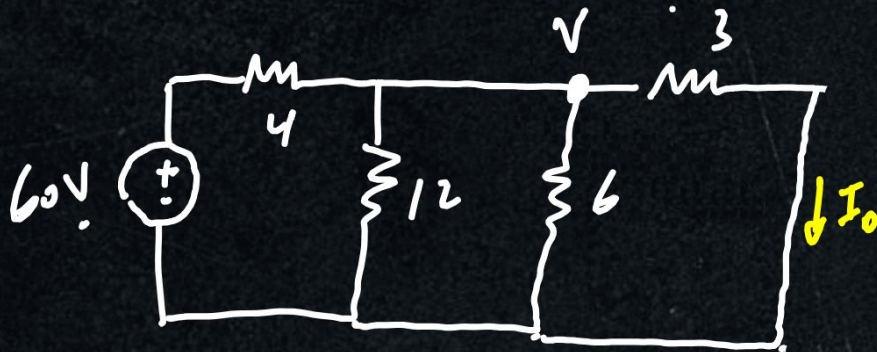

$$\frac{V}{6} + \frac{V}{12} + \frac{V}{6} + \frac{V - 60}{4} = 0$$

$$2V + V + 4V + 3V = 180$$

$$V = 18 \text{ V}$$

$$I_0 = \frac{18}{3} = 6 \text{ A}$$

$$i_L(0^-) = i_L(0^+) = i_L(0) = I_0 = 6 \text{ A}$$

$$0 \leq t \leq 35$$

$$i_{L_1} ??$$




$$i_{L_1} = I_0 e^{-t/\tau_1}$$

$$\tau_1 = L/R_{Th_1}$$

$$R_{Th_1} = (3+6) \parallel 18 = 6 \Omega$$

$$\tau_1 = \frac{150}{6} = 25 \text{ ms}$$

$$i_{L_1} = 6 e^{-40t} \text{ A}$$

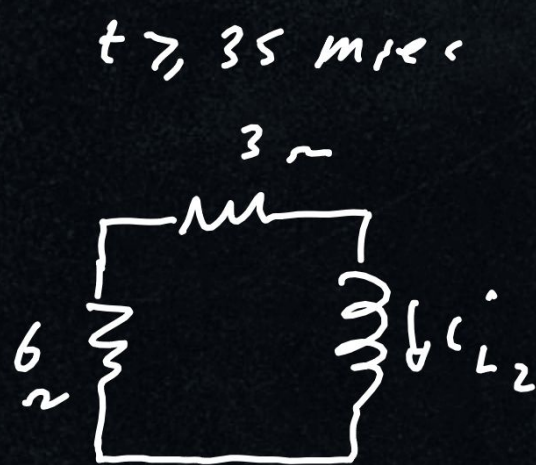

i_{L2}

Natural
response

$$i_{L2} = \underline{I_0'} e^{\frac{-(t-35\text{m})}{\tau_2}}$$

$$I_0' = i_{L2}(35\text{ms}) = i_{L1}(35\text{ms})$$

$$I_0' = 6 e^{-40 \times 0.035} = 1.48 \text{ A.}$$

$$\tau_2 = \frac{L}{R_{Th2}}, \quad R_{Th2} = 3 + 6 = 9 \Omega$$

$$\tau_2 = \frac{150}{9} = 16.667 \text{ msec}$$

$$i_{L2} = 1.48 e^{-60(t-0.035)} \quad t > 35 \text{ ms}$$

$$i_L = \begin{cases} i_{L1} & 0 \leq t \leq 35 \\ i_{L2} & t > 35 \end{cases}$$

$$i_L = \begin{cases} 6 e^{-40t} & 0 \leq t \leq 35 \text{ ms} \\ 1.48 e^{-60(t-0.035)} & t \geq 35 \text{ ms} \end{cases}$$

