


Chapter 10: Sinusoidal steady state Power Calculation:

* instantaneous power $P(t)$:

$$P(t) = v(t) \cdot i(t)$$

$$= V_m I_m \cos(\omega t + \phi_v) \cos(\omega t + \phi_i)$$
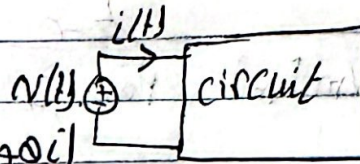
$$= \frac{1}{2} V_m I_m [\underbrace{\cos(2\omega t + \phi_v + \phi_i)}_{\text{Twice time frequency}} + \underbrace{\cos(\phi_v - \phi_i)}_{\text{Constant}}]$$



R_{eq}

$$\rightarrow i(t) = I_m \cos(\omega t + \phi_i)$$


$$\rightarrow v(t) = V_m \cos(\omega t + \phi_v)$$

$$\rightarrow \cos a \cos b = \frac{1}{2} (\cos(a+b) + \cos(a-b))$$

* Average power: Real Power

$$P_{av} = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) \text{ W.}$$

* if I have a pure:

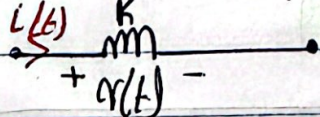


$$\phi_v - \phi_i = \text{Zero}$$

$$P_{av} = \frac{1}{2} V_m I_m$$


$$= \frac{1}{2} \frac{V_m^2}{R}$$

$$= \frac{1}{2} I_m^2 R$$

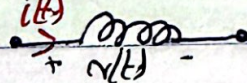


$$\phi_v - \phi_i = 90^\circ$$

$$P_{av} \text{ is Zero}$$

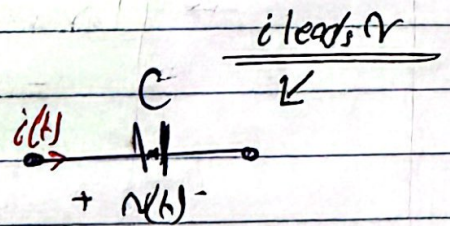

$$\phi_v - \phi_i = -90^\circ$$

$$P_{av} \text{ is Zero}$$

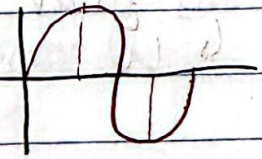


P_{avr}

$$P_{avr} = \frac{1}{2} V_m I_m$$

$$P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \text{ W.}$$

Power Factor

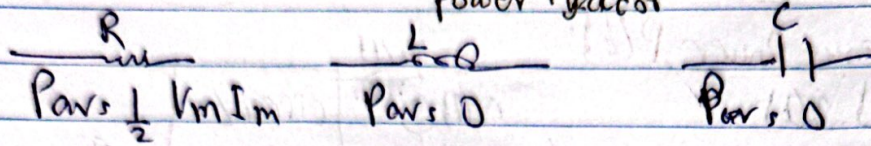

* RMS value:

$$P_{av} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$V_{rms} = \frac{V_m}{\sqrt{2}}$

$I_{rms} = \frac{I_m}{\sqrt{2}}$

$\left. \begin{array}{l} V_{rms}, V_{eff} \\ I_{rms}, I_{eff} \end{array} \right\}$


220V, 50 Hz

$$\Rightarrow P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

* Apparent Power & Power Factor:-

$$P_{av} = \underbrace{V_{rms} I_{rms}}_{\substack{\text{apparent} \\ \text{Power [VA]}}} \underbrace{\cos(\theta_v - \theta_i)}_{\substack{\text{Power Factor} \\ \text{[P.F.]}}}$$

R	L	C
$\theta_v - \theta_i = 0$	$\theta_v - \theta_i = 90^\circ$	$\theta_v - \theta_i = -90^\circ$
$\cos(\theta_v - \theta_i) = 1$	$\cos(\theta_v - \theta_i) = 0$	$\cos(\theta_v - \theta_i) = 0$
$\Rightarrow \text{P.F.} = 1$	$\text{P.F.} = 0$	$\text{P.F.} = 0$
unity P.F.		

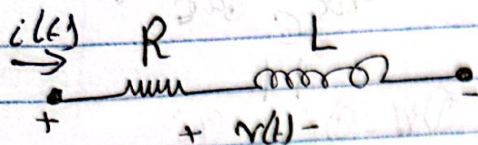


inductive load.

$$0 < \theta_v - \theta_i < 90$$

$$0 < \text{P.F.} < 1$$

lagging P.F

i lags v

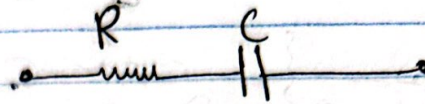

Capacitive load

$$-90 < \theta_v - \theta_i < 0$$

$$0 < \text{P.F.} < 1$$

leading P.F

i leads v

* Complex Power:-

$$\vec{S} = \vec{V}_{\text{rms}} \vec{I}_{\text{rms}}^* \quad \text{VA}$$

$$= (V_{\text{rms}} \angle \theta_v) (I_{\text{rms}} \angle -\theta_i)$$

$$= V_{\text{rms}} I_{\text{rms}} \angle (\theta_v - \theta_i)$$

$$= \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)}_{\substack{\text{P}_{\text{av}} \\ \text{P}}} + j \underbrace{V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)}_{\text{Q}}$$

P_{av}

P

Real Power

avg Power

W

Q

Reactive Power


VAR

$$\vec{S} = P_{\text{av}} + jQ$$

$$P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

$$\left\{ \begin{array}{l} |\vec{S}| = \sqrt{P_{\text{av}}^2 + Q^2} = V_{\text{rms}} I_{\text{rms}} \text{ (apparent Power)} \\ \angle \vec{S} = \tan^{-1} \frac{Q}{P_{\text{av}}} \end{array} \right.$$

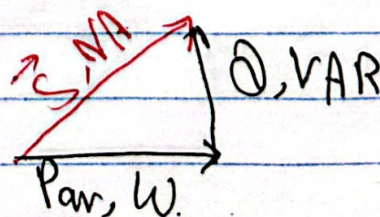

R

$$\phi_v - \phi_i = 0$$

$$\phi = \text{Zero}$$

ωL

$$\phi_v - \phi_i = 90^\circ$$

$$\sin 90^\circ = 1$$

$$\phi = V_{rms} I_{rms}$$

$$= V_{rms} \left(\frac{V_{rms}}{\omega L} \right)$$

$$\Rightarrow \frac{V_{rms}^2}{\omega L} = \frac{V_{rms}^2}{X_L}$$

$$= I_{rms}^2 (\omega L) = I_{rms}^2 (X_L)$$

$\frac{1}{\omega C}$

$$\phi_v - \phi_i = -90^\circ$$

$$\sin(-90^\circ) = -1$$


$$\phi = -V_{rms} I_{rms}$$

$$= -V_{rms} \left(\frac{V_{rms}}{\omega C} \right)$$

$$= -V_{rms}^2 \omega C = \frac{V_{rms}^2}{X_C}$$

$$= -I_{rms}^2 \omega C = -I_{rms}^2 X_C$$

* Power triangle.

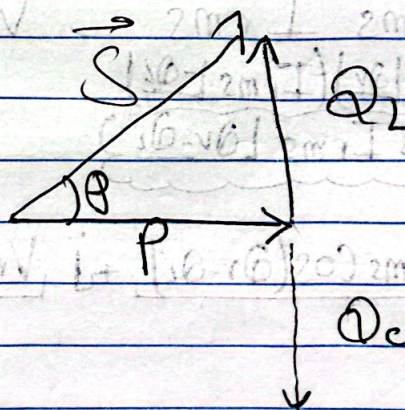

$$PF = \cos \theta$$

$$\theta = \cos^{-1}(PF)$$

+ve? -ve?

$$\Rightarrow \theta = \cos^{-1}(PF)$$

lagging PF

$$\Rightarrow \theta = -\cos^{-1}(PF)$$


leading PF

$$\therefore PF = \cos \theta = \frac{P_{av}}{|S|}$$

$$\theta = \tan^{-1} \frac{Q}{P}$$

* Conservation of AC Power
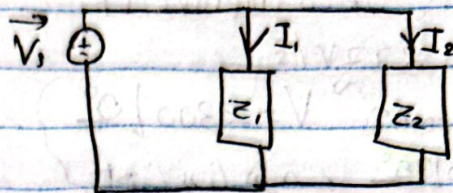
$$\begin{aligned}\vec{S}_{\text{source}} &= \vec{V}_s \vec{I}_s^* \\ &= \vec{V}_s (\vec{I}_1^* + \vec{I}_2^*) \\ &= \vec{V}_s \vec{I}_1^* + \vec{V}_s \vec{I}_2^* \\ &= \vec{S}_1 + \vec{S}_2\end{aligned}$$



$$* P_{av_T} = P_{av_1} + P_{av_2} + \dots + P_{av_n}$$



$$* Q_T = Q_1 + Q_2 + \dots + Q_n$$

$$* \vec{S}_T = \vec{S}_1 + \vec{S}_2 + \dots + \vec{S}_n$$

* Power Factor Correction:

$$0 < \phi_v - \phi_i < 90^\circ$$

PF $\neq 1$

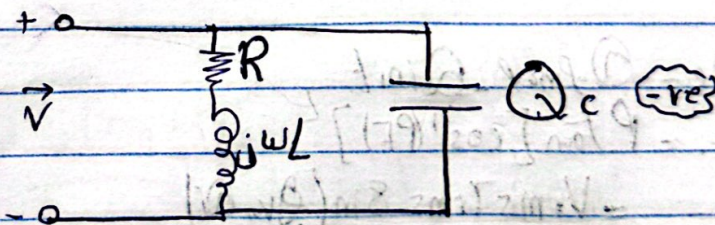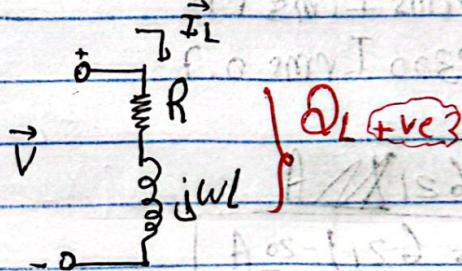

$$\rightarrow Q_C = Q_{\text{imp}} - Q_{\text{init.}}$$

$$Q_C = \frac{V_{\text{rms}}^2}{X_C} = -\omega C V_{\text{rms}}^2$$

$$\rightarrow C = \frac{-Q_C}{\omega V_{\text{rms}}^2}$$

Ex page 43:-

load 1 MW at 0.7 lagging. $V = 2300 V_{rms}$.

$C_{mn} = ?$ to improve PF = 0.9 lagging

$\omega = 377 \text{ rad/s}$

$$\vec{V} = 2300 \angle 0^\circ$$

$$\vec{V} = 2300 \angle 25^\circ$$

$$\cos(\theta_v - \theta_i) = 0.7$$

$$\theta_v - \theta_i = \cos^{-1} 0.7$$

$$\theta_v - \theta_i = 45^\circ$$

$$\theta_i = 25^\circ - 45^\circ$$


$$\theta_i = -20^\circ$$

$$P_{load} = V_{rms} I_{rms} \text{PF}$$

$$10^6 = 2300 I_{rms} 0.7$$

$$I_{rms} = 621 \text{ A}$$
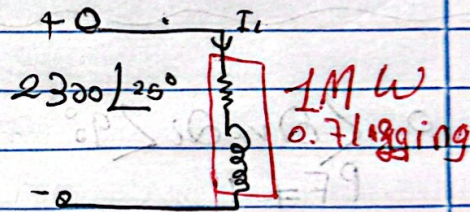
$$\rightarrow I_{rms} = 621 \angle -20^\circ \text{ A}$$




$$\Delta Q_c = Q_{final} - Q_{init}$$

$$Q_{init} = P \tan[\cos^{-1}(\text{PF})]$$

$$= V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$


$$= 2300 \times 621 \sin(25^\circ - 20^\circ)$$

$$= 1.02 \text{ MVAR}$$

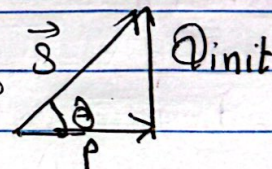

$$Q_{final} = P \tan[\cos^{-1}(\text{PF}_{new})]$$
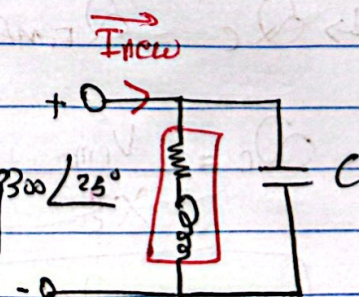
$$= 1 \text{ M} \times \tan[\cos^{-1} 0.9] = 0.484 \text{ MVAR}$$



$$\Delta Q_c = Q_{final} - Q_{init}$$

$$= 0.484 - 1.02$$

$$= -0.536 \text{ MVAR}$$



$$C = \frac{-Q_c}{\omega (V_{rms})^2} = \frac{-0.536}{377 (2300)^2} = \boxed{-269 \mu F}$$

$$I_{new} = \frac{P_{av}}{V_{rms} \text{PF}_{new}} = \frac{14}{2300 \times 0.9} = \boxed{483 \text{ A}_{rms}}$$

$$\begin{aligned} S_{load} &= \vec{V}_{rms} \vec{I}_{rms}^* \\ &= (2300 \angle 25^\circ) (483 \angle -\theta_i) \\ \rightarrow \cos(\theta_v - \theta_i) &= 0.9 \\ \theta_v - \theta_i &= 26^\circ \\ \theta_i &= 25^\circ - 26^\circ \\ &= -1^\circ \\ &= -P \end{aligned}$$


$$\rightarrow 2300 \times 483 \angle 25^\circ - 26^\circ$$

$$\rightarrow 1.104 \text{ MVA} \angle 26^\circ$$

$$= \boxed{1 + j0.484 \text{ MVA}}$$

* Max. avg. Power Transf. Lr.
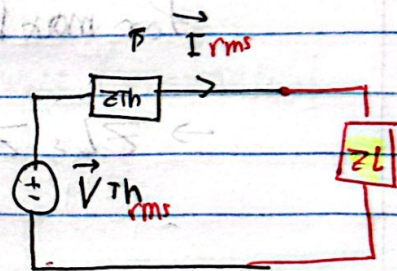
$$\begin{aligned} \rightarrow Z_{th} &= R_{th} + jX_{th} \\ Z_L &= R_L + jX_L \end{aligned}$$



$$\begin{aligned} \rightarrow \vec{I}_{rms} &= \frac{\vec{V}_{th}}{(R_{th} + R_L) + j(X_{th} + X_L)} \\ \rightarrow P_{av} &= |\vec{I}_{rms}|^2 R_L \\ &= \frac{V_{th}^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \end{aligned}$$

$$|\vec{I}_{rms}| = \frac{V_{th}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}}$$

$$\frac{\partial P_{av}}{\partial X_L} = \frac{0 - 2V_{th}^2 R_L (X_L + X_{th})}{[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2} = \text{Zero}$$

$$\frac{\partial P_{av}}{\partial R_L} = \frac{((R_{th} + R_L)^2 + (X_{th} + X_L)^2) V_{th}^2 - 2V_{th}^2 R_L (R_{th} + R_L)}{[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2} = \text{Zero}$$

~~$\frac{\partial P}{\partial X_L}$~~ \rightarrow


$$\frac{\partial P}{\partial X_L} = 0 \rightarrow \boxed{X_L = -X_{th}}$$

$$\frac{\partial P}{\partial R_L} = 0 \rightarrow (R_{th} + R_L)^2 + (X_{th} + X_L)^2 - 2R_L(R_{th} - R_L) = 0$$

$$\rightarrow (R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)$$

$$\rightarrow \boxed{R_L = R_{th}}$$

$$\rightarrow \boxed{Z_L = Z_{th}^*}$$

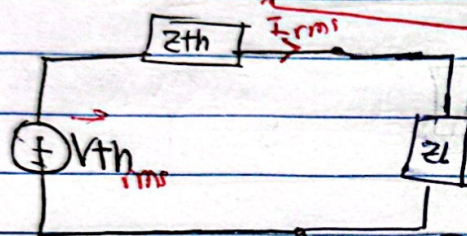

for max Power Transfer

$$\rightarrow Z_L = Z_{th}^*$$

$$\left. \begin{array}{l} R_L = R_{th} \\ X_L = -X_{th} \end{array} \right\}$$

$$P_{max} = |I|^2 R_L$$

$$= \left(\frac{|V_{th}|}{2 R_{th}} \right)^2 \times R_{th}$$

$$\because I = \frac{V_{th}}{Z_L + Z_{th}} = \frac{V_{th}}{R_{th} + R_{th} - jX_{th} + jX_{th}} = \frac{V_{th}}{2R_{th}}$$



$$\boxed{P_{max} = \frac{|V_{th}|^2}{4 R_{th}}}$$

$V_{th} \rightarrow \text{rms value!}$

$$\rightarrow P_{max} = \frac{|V_{rms}|^2}{8 R_{th}} \quad \text{max values}$$

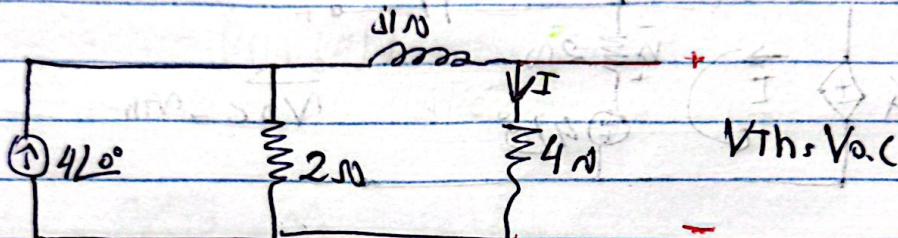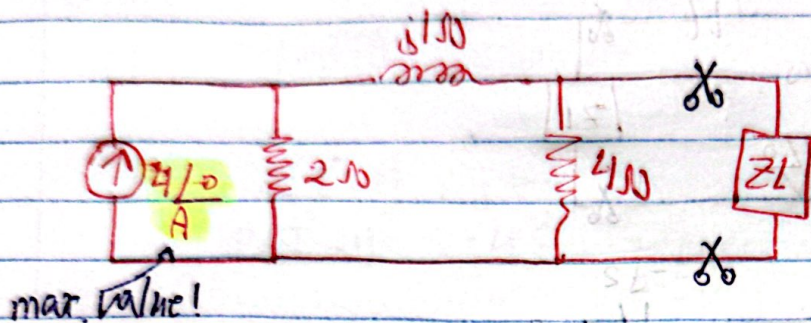
Example:

Find Z_L for maximum average power transfer.
Compute the maximum average power supplied to the load.



$$V_{Th} = R_4 \times I$$
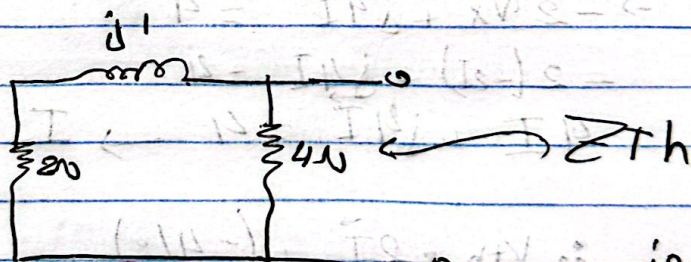
$$\vec{V}_{Th} = 4 \times \frac{2}{2+4+j1} \times 4 = 5.28 \angle -9.46^\circ \text{ Volt (max value)}$$




$$Z_{Th} = (2+j1) \parallel 4\Omega$$

$$= 1.4 + j0.43$$



$$\therefore Z_L = Z_{Th}^* = 1.4 - j0.43$$
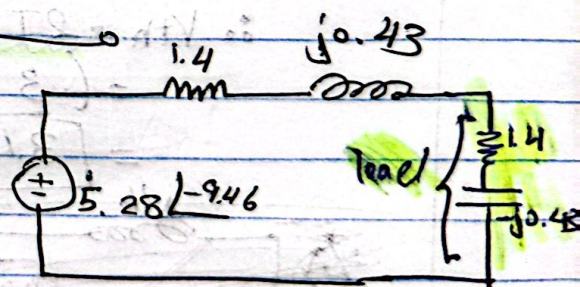
$$P_{max} = \frac{V_{Th, rms}^2}{4 R_{Th}} = \frac{\left(\frac{5.28}{\sqrt{2}}\right)^2}{4 \times 1.4} = 2.489 \text{ W}$$



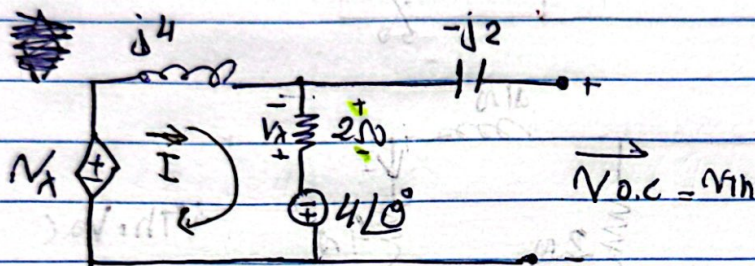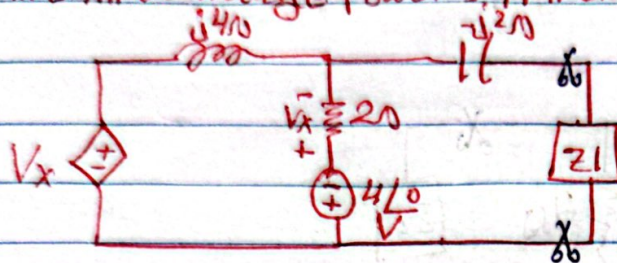Example:

Find Z_L for maximum average Power transfer compute the maximum average Power supplied to Z_L



$$-V_x + j4I - V_x - 4\angle 0 = 0 \quad I_x, N_x = -2I$$

$$\rightarrow -2V_x + j4I = 4$$


$$-2(-2I) + j4I = 4$$

$$4I + j4I = 4 \rightarrow I = \frac{4}{4 + j4} = 0.707 \angle -45^\circ \text{ A (max)}$$

$$\therefore V_{th} = 2I + (-4\angle 0)$$

$$= (-3 - j1) \text{ Volt}$$

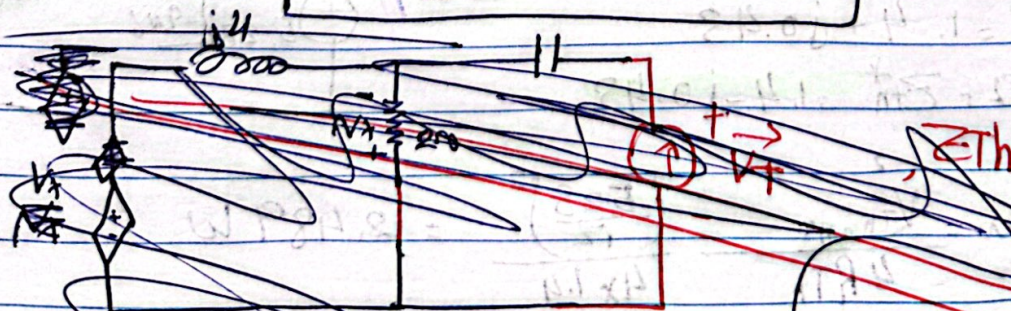
$$= 3.16 \angle 198.43^\circ \text{ Volt (max)}$$



$$Z_{Th} = \frac{V_T}{I_T}$$



let $I_T = 1 \angle 0^\circ$

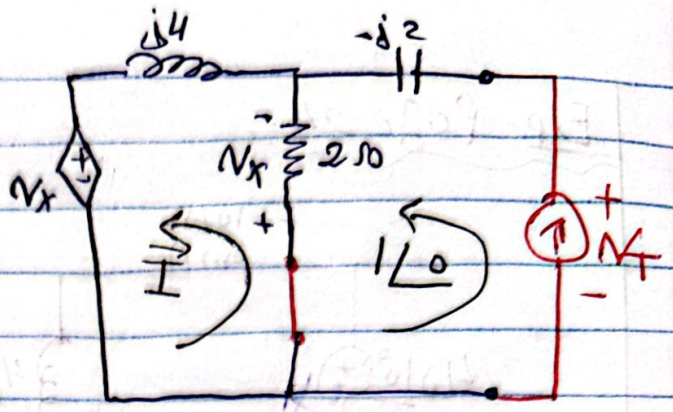

$$KVL \rightarrow 2(I-1) + j4I + V_x = 0, \text{ But } V_x = 2(I-1)$$

$$2(I-1) + j4I + 2(I-1) = 0$$

$$(4 + j4)I = 4$$

$$\rightarrow I = \frac{4}{4 + j4} = 0.707 \angle -45^\circ A$$

$$\therefore V_T = V_{-j2} + V_2 = -j2 + 1 + 2(1 - I) = 2 - j2 - 1.414 \angle -45^\circ$$

$$= 1 - j1$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{1 - j1}{1} = 1 - j1$$

$$Z_L = 1 + j1 \Omega$$

$$P_{max} = \frac{V_{Th}^2}{8 R_{Th}} = \frac{(3.16)^2}{8 \times 1} = 1.248 W$$

$$8 \times 5 + 0.1 \times 921.8 = 821$$


$$A_{25.1} = 1.71$$

$$88.11 \times 921.8 = 8121$$

$$W_{all} =$$

$$1.5111 \times 921.8 = 1393$$

Exp: Page 24.

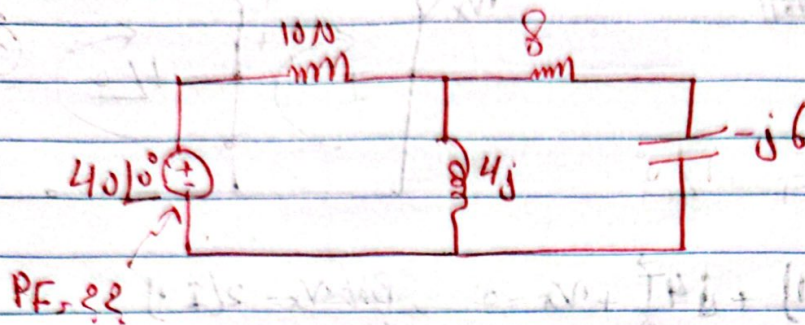

$$Z_{tot} = [8 - j6] // 4j + 10$$


$$= \left[\frac{32j + 24}{8 - j2} \right] + 10 = 12.69 \angle 20.62^\circ = 11.88 + j4.47$$

$$I = \frac{40 \angle 0^\circ}{12.64 \angle 20.62} = 3.152 \angle -20.62 \text{ A}$$

$$PF = \cos(\theta_v - \theta_i) = \cos(0 + 20.62) = 0.936 \text{ lagging}$$

OR
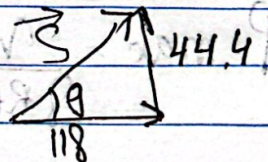
$$\begin{aligned} \vec{S} &= \vec{V}_{rms} \cdot \vec{I}_{rms}^* \\ &= (40 \angle 0^\circ) \cdot (3.152 \angle 20.62^\circ) \\ &= 126.08 \angle 20.62^\circ \\ &= \underbrace{118}_{P} + j \underbrace{44.4}_{VAR} \end{aligned}$$



$$PF = \cos \theta = \cos(\tan^{-1} \frac{44.4}{118}) = 0.935 \text{ lagging}$$

$$P = (3.152)^2 \times 11.88 = 118 \text{ W}$$

$$Q = (3.152)^2 \times (4.47) = 44.4 \text{ VAR}$$

$$118 = (3.152)^2 \times 10 + I_2^2 \times 8$$

$$|I_2| = 1.526 \text{ A}$$

$$\vec{I}_2 = \frac{4j}{8 - j2} = 3.152 \angle -20.62^\circ$$

$$= 1.526 \angle 83.41^\circ$$