

BIRZEIT UNIVERSITY

Faculty of Engineering and Technology

Electrical and Computer Systems Engineering

ENEE3102

“Prelab Exp#5”

The Field –Effect Transistor

Student's name: Tamara Amro

Major: Physics minor electronics

Student's number: 1172771

DR: Mohammad Jihad Al Ju'Beh

Eng: Amgad


11/11/2020

Table of Contents


CHARACTERISTICS OF AN N-CHANNEL JFET	1
A JFET AMPLIFIER	6
COMMON DRAIN AMPLIFIER	7
CONSTANT CURRENT SOURCE	8

➤ CHARACTERISTICS OF AN N-CHANNEL JFET :


A-

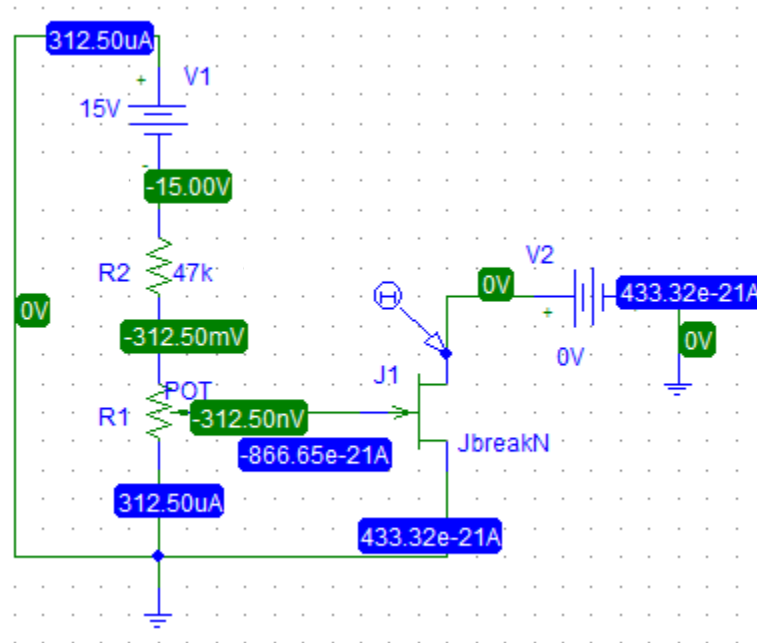


- When $V_{gs} = 0$:

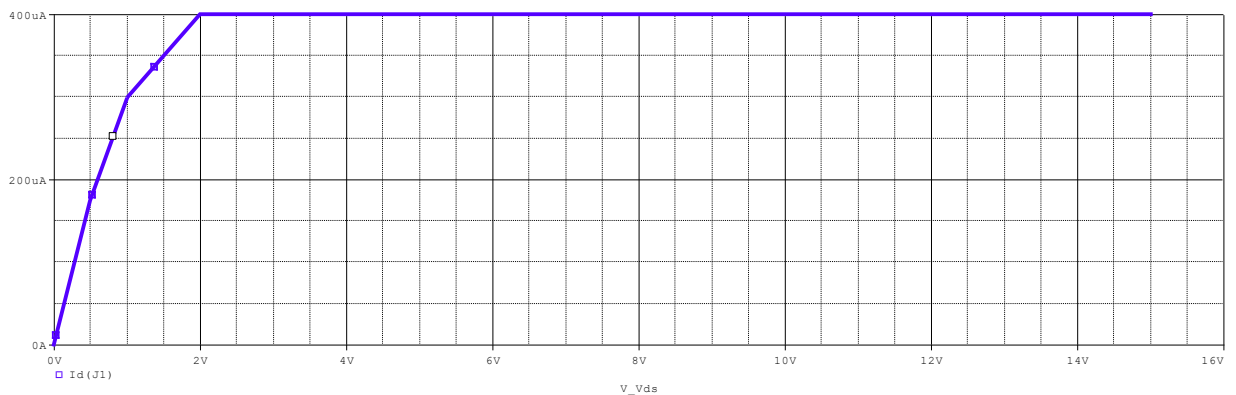


- When $V_{gs} = -0.5$ V :

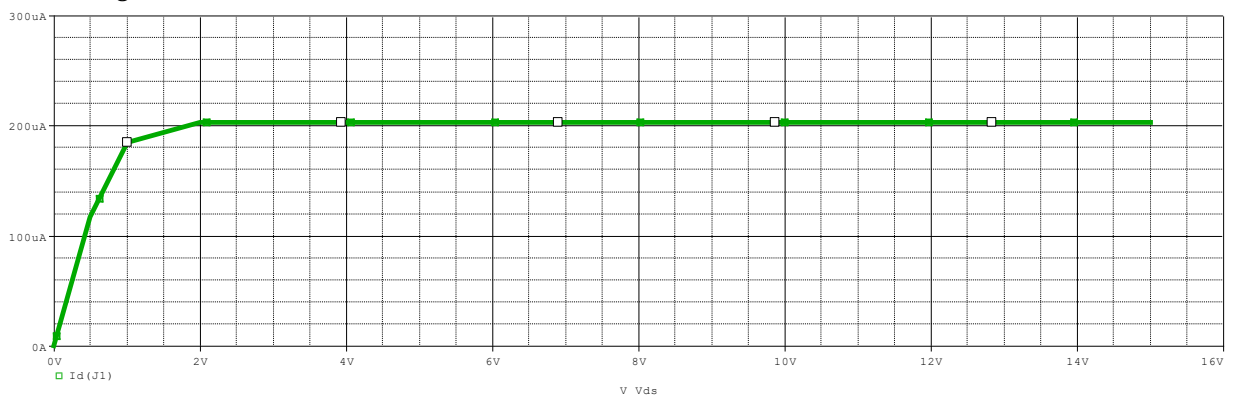


- When $V_{gs} = -1 \text{ V}$:

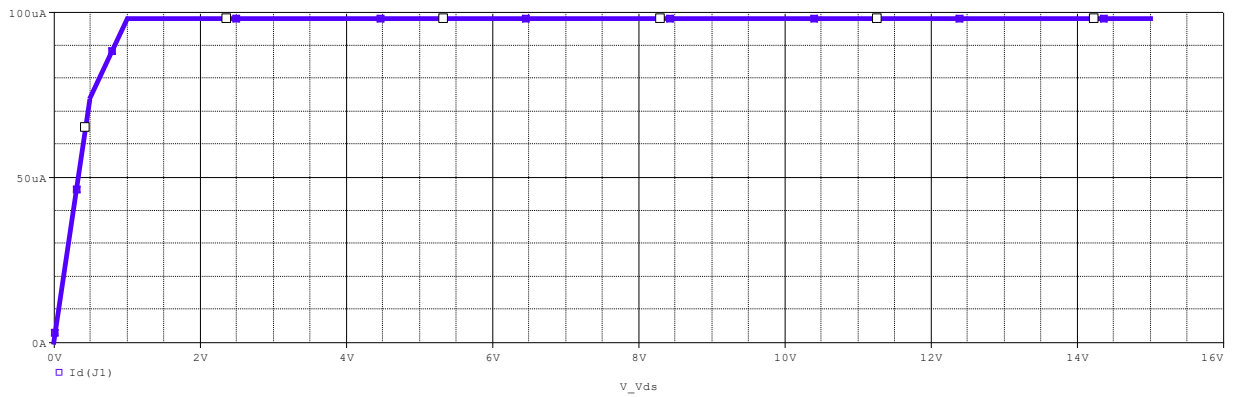


- When $V_{gs} = -1.5 \text{ V}$:

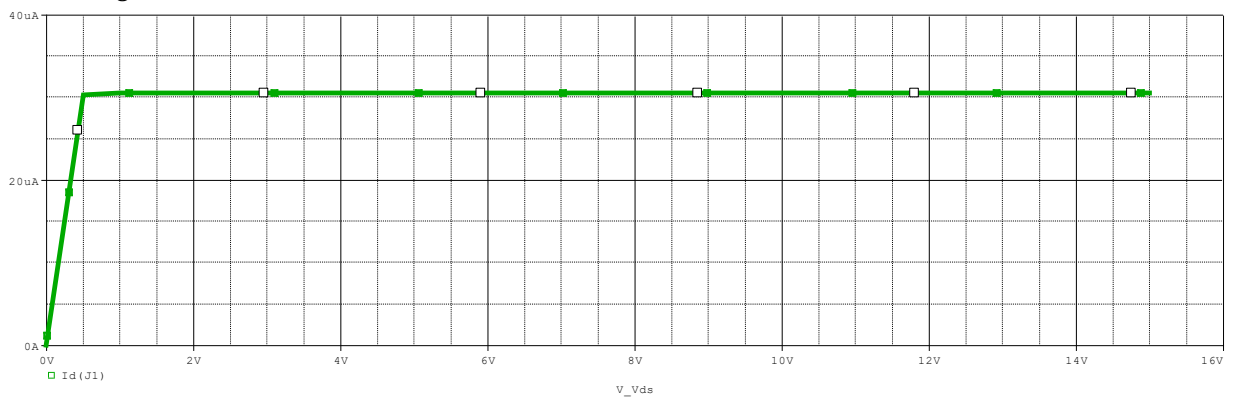


- When $V_{gs} = -2 \text{ V}$:

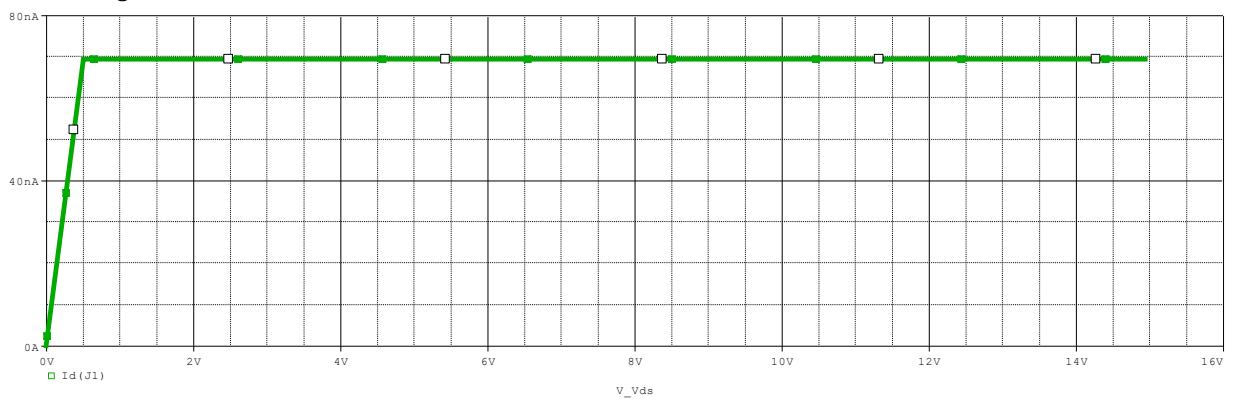

- When $V_{gs} = -2.5 \text{ V}$:


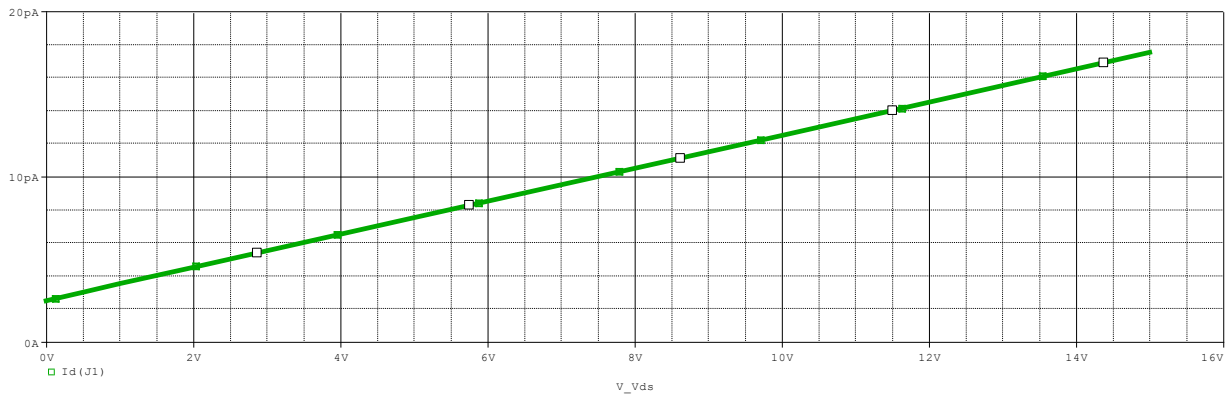


B-

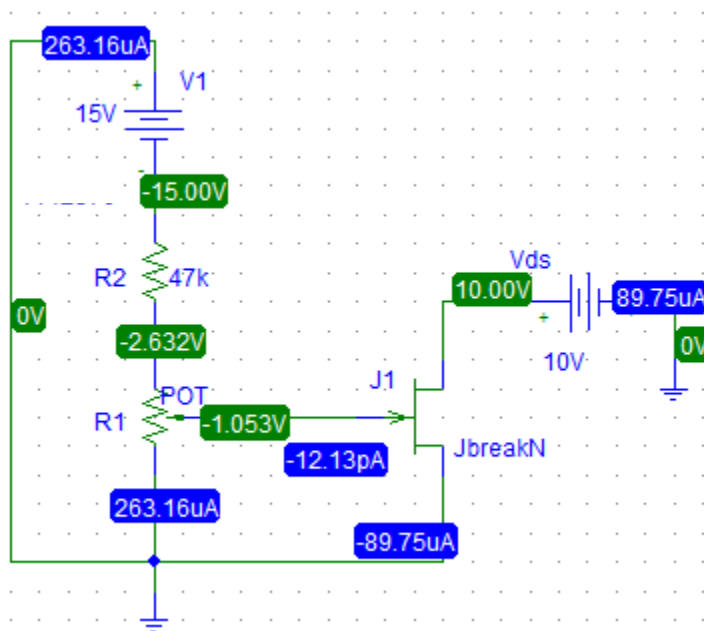



SO $I_G = -12.13 \text{ PA}$

A-

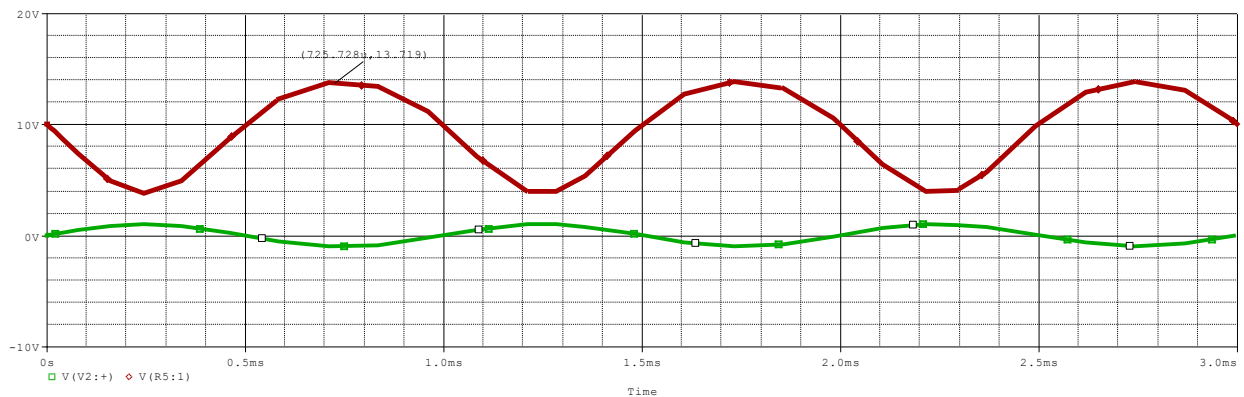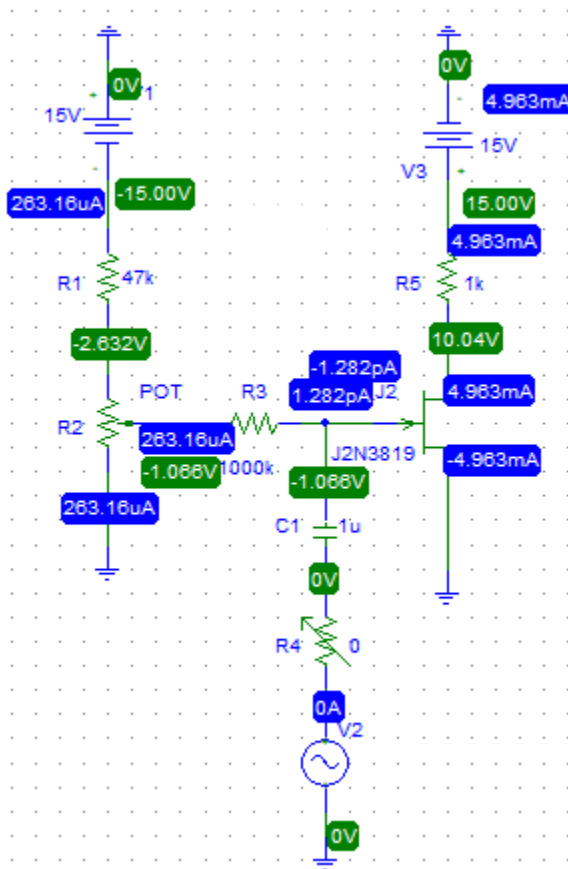


Voltage gain = 5 / 1 = 5.

➤ COMMON DRAIN AMPLIFIER :

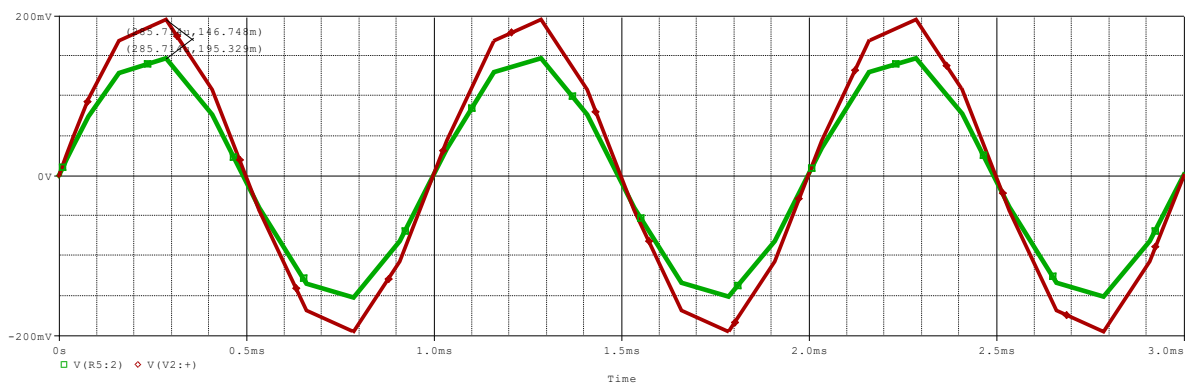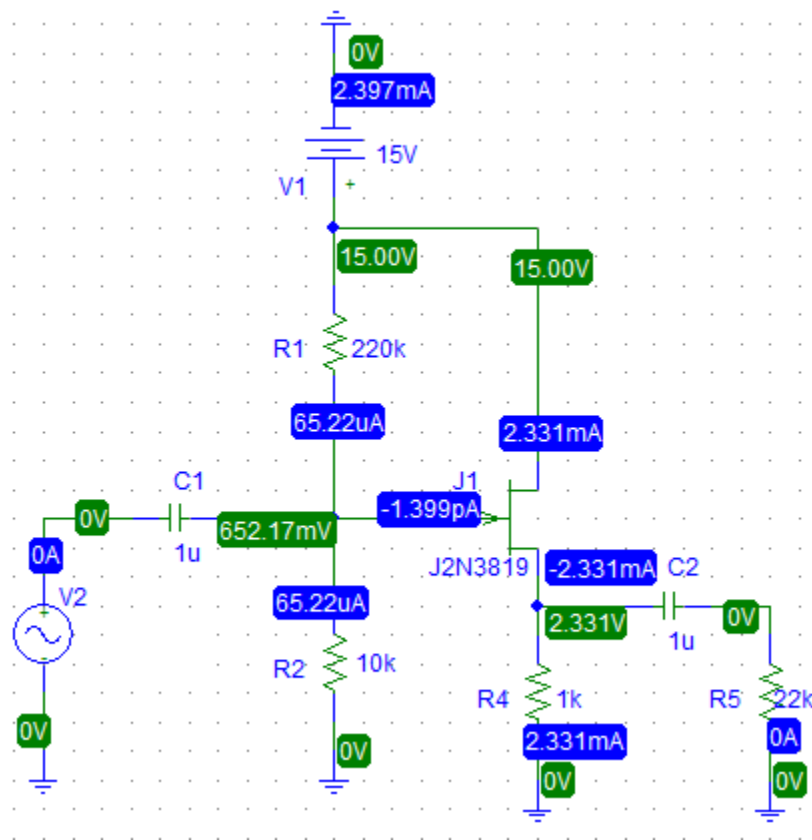

The gain voltage = $146.748/195.329 = 0.751$


The phase shift = 0

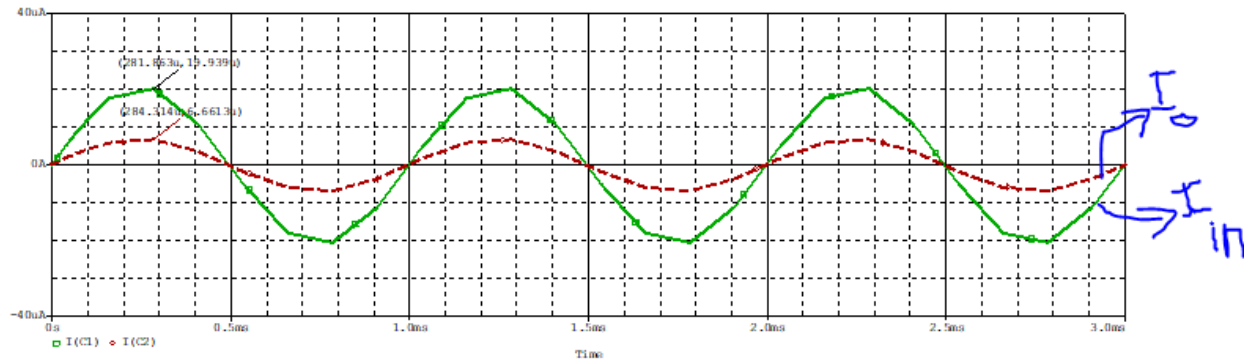


$$Z_{in} = V_{in} / I_{in} = 195.329\text{m} / 19.939\text{u} = 9.8\text{k ohm.}$$

$$Z_o = V_o / I_o = 146.748 / 6.661\text{u} = 22\text{k ohm.}$$


➤ .CONSTANT CURRENT SOURCE.

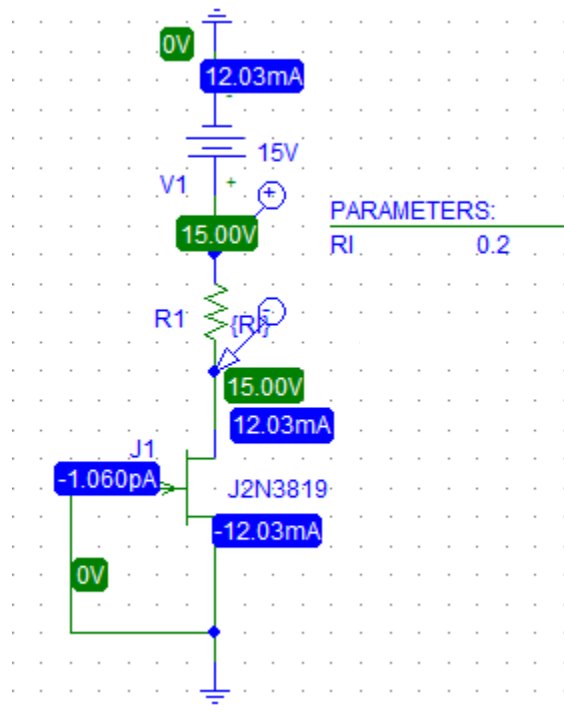

- **RL Vs VL :**

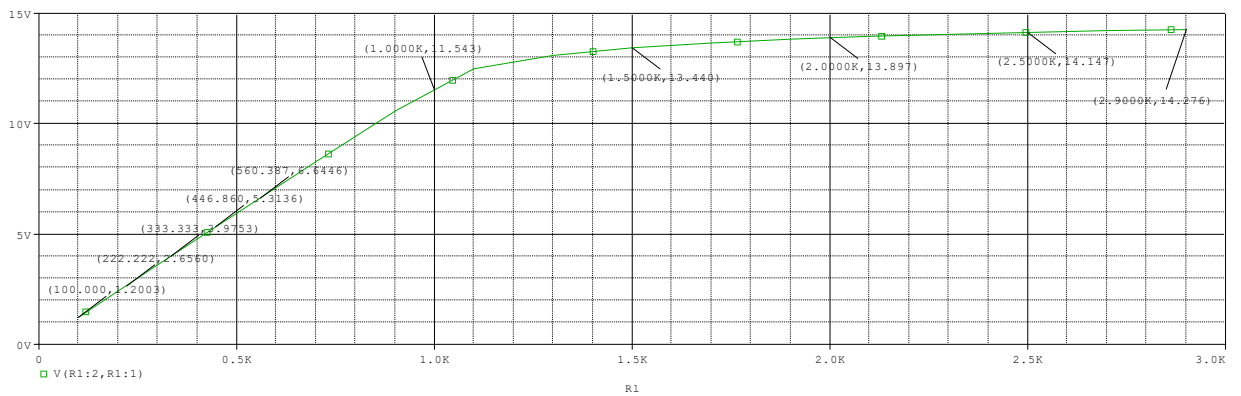

- **RL Vs IL :**

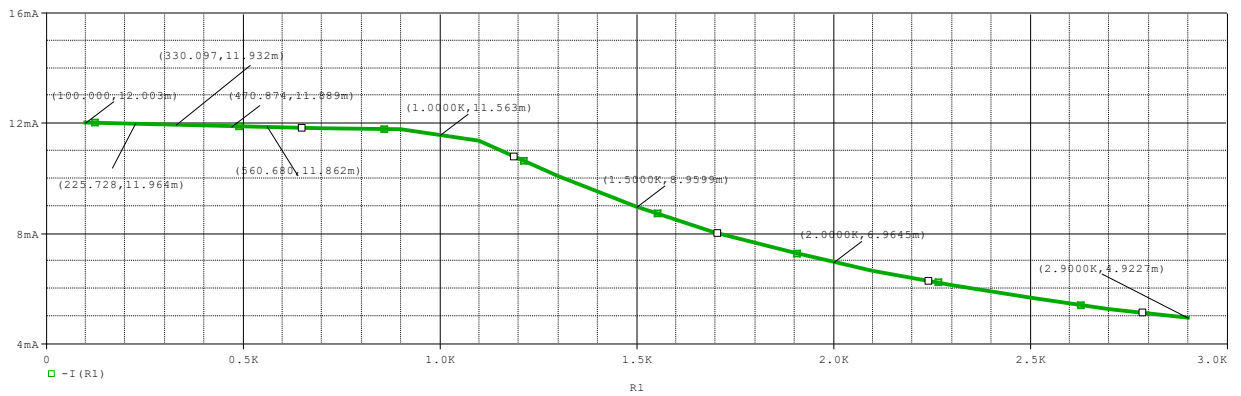

THE END

