
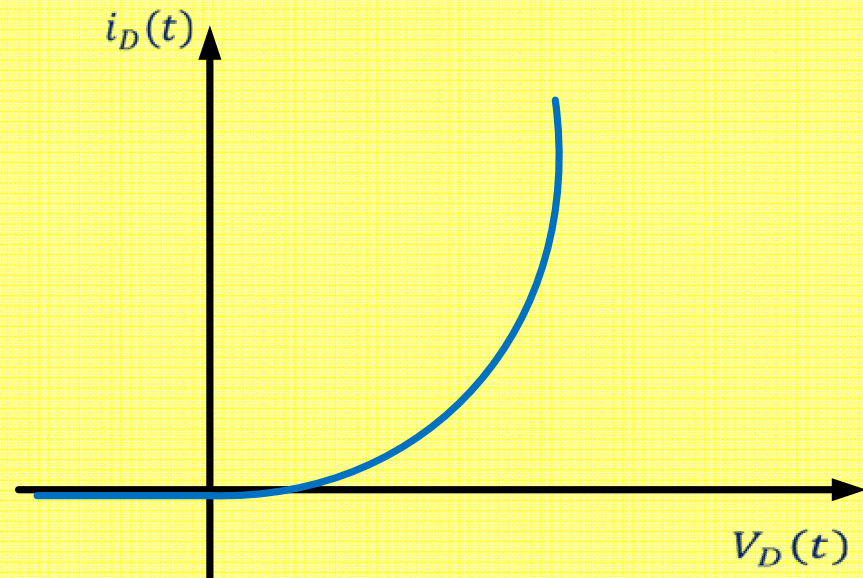


# The Use of Diode Model

### 3) The use of models


- ▶ A piece wise linear models is an electrical equivalent circuit of a nonlinear electronic device
- ▶ It is composed of linear circuit elements arranged to approximate the characteristics of the electronic device .

## a) ideal diode model

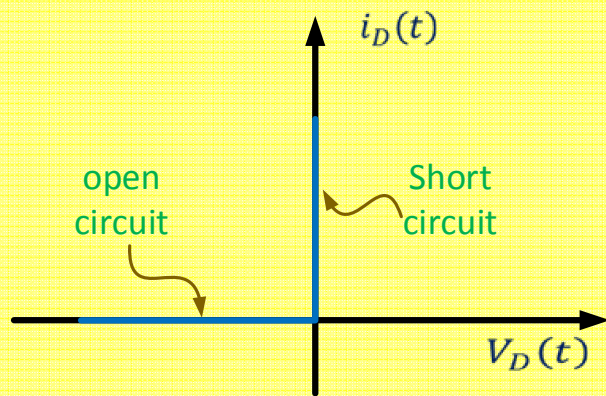


- ▶ When  $V_s \geq 0$  ; the Diode is on, and replaced with short circuit
- ▶ When  $V_s < 0$  ; the Diode is off, and replaced with open circuit

## b) Knee Voltage model


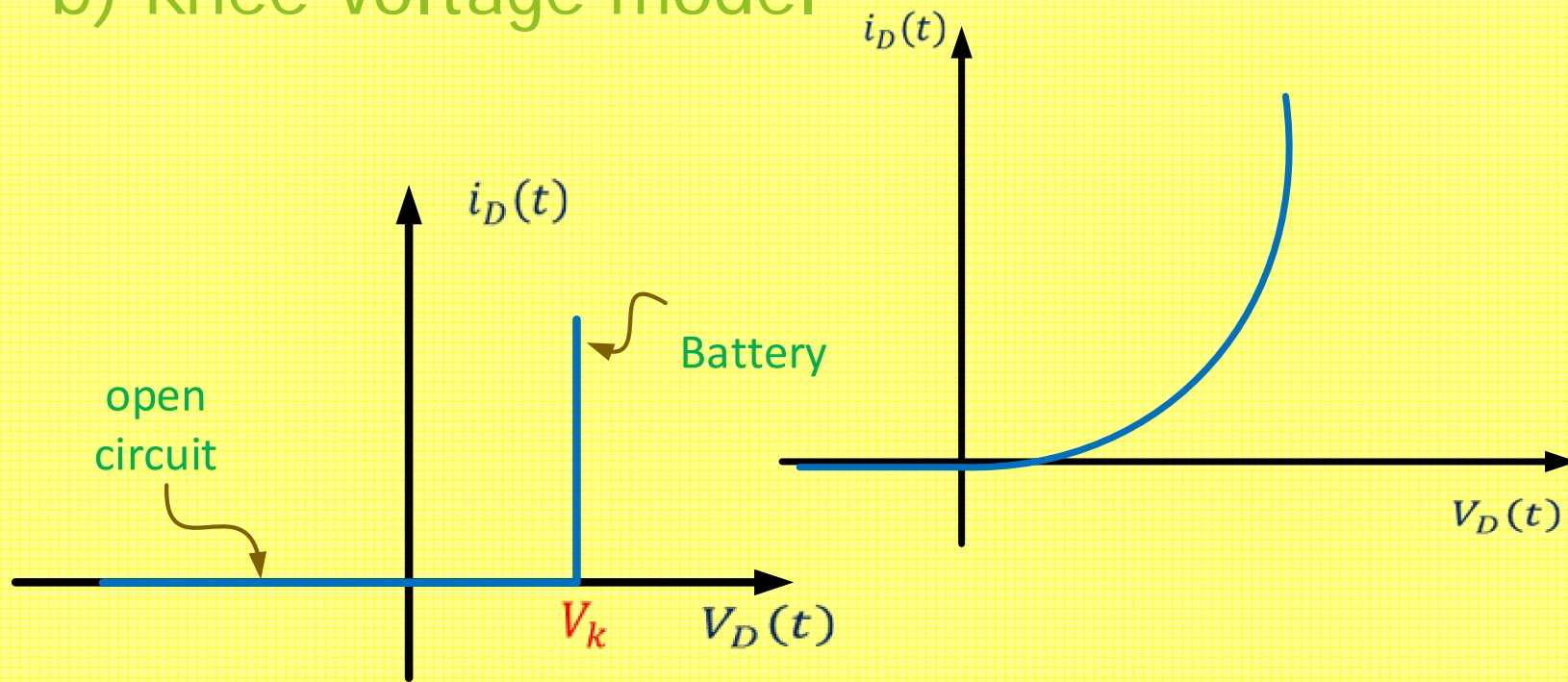

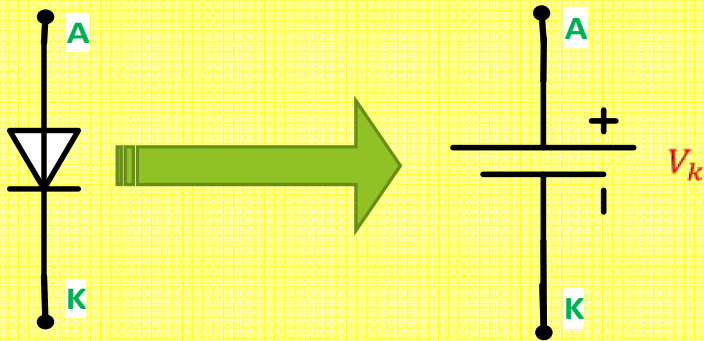
## b) Knee Voltage model


- ▶ When  $V_s \geq V_k$ ; the Diode is on, and replaced with a constant voltage source



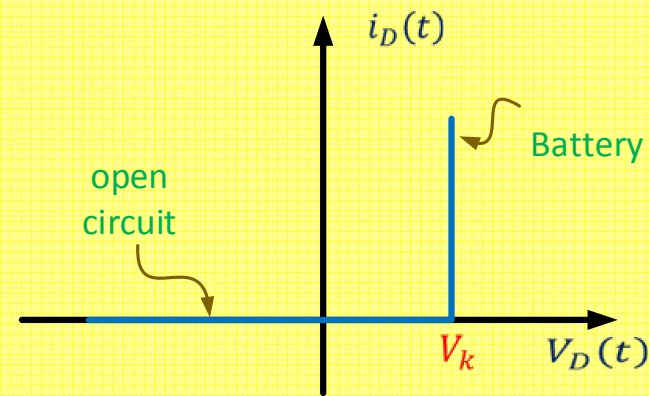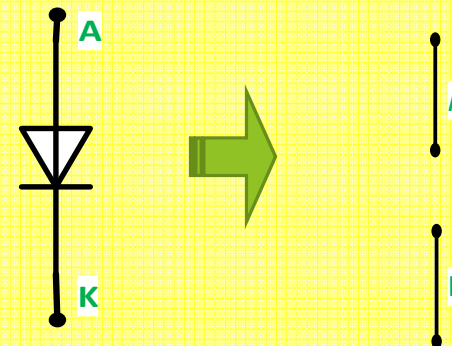- ▶ When  $V_s < V_k$ ; the Diode is off, and replaced with open circuit






### c) Dynamic resistance model

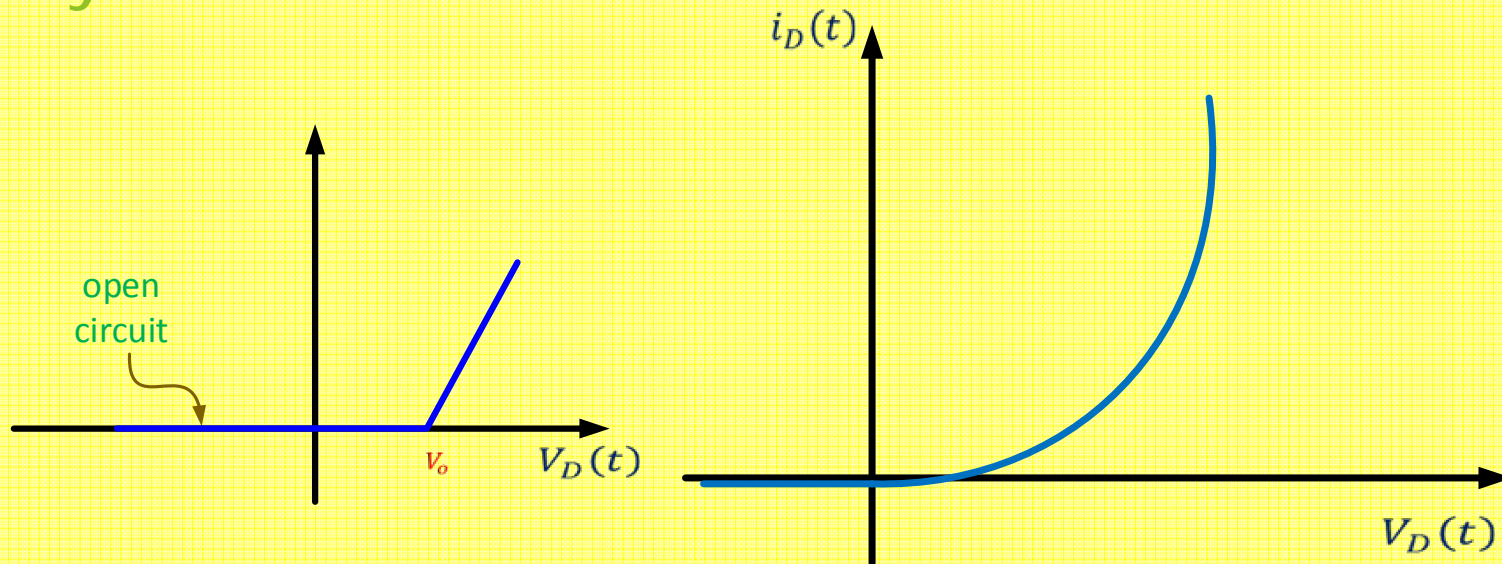

- ▶ When  $V_s \geq V_o$  ; the Diode is on, and replaced with a constant voltage source  $V_o$  and resistance  $R_o$
- ▶ // p 4
- ▶ When  $V_s < V_o$  ; the Diode is off, and replaced with open circuit
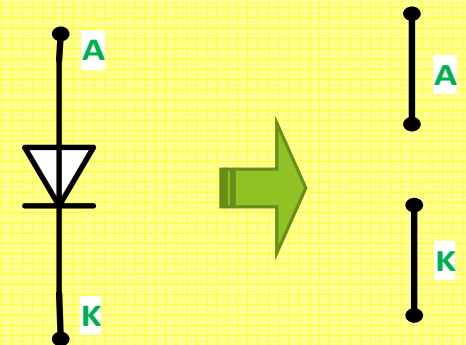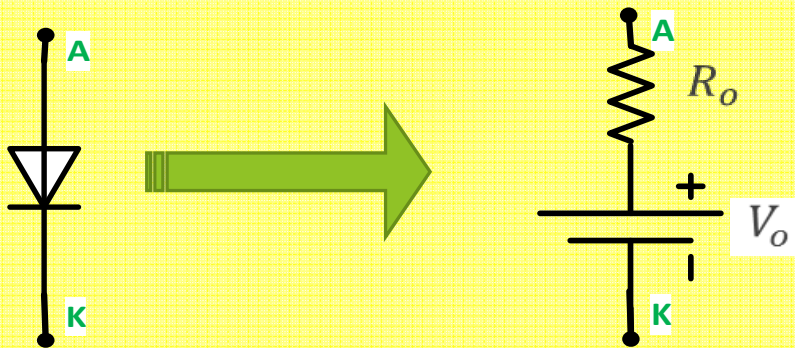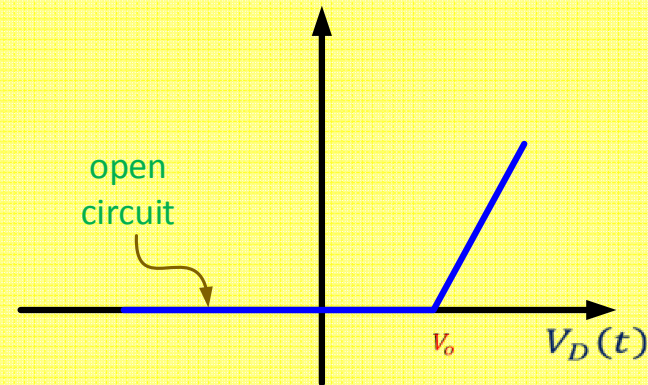
## c) Dynamic resistance model


- ▶ When  $V_s \geq V_o$ ; the Diode is on, and replaced with a constant voltage source  $V_o$  and resistance  $R_o$



- ▶ When  $V_s < V_o$ ; the Diode is off, and replaced with open circuit
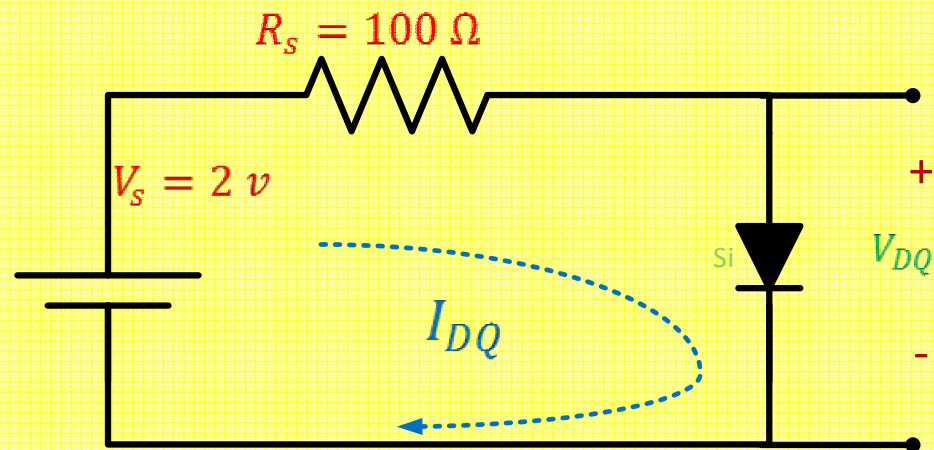
# Example

- Find the Q point ( $I_{DQ}$ ,  $V_{DQ}$ ) using
  - a) ideal diode model
  - b) knee voltage model




## a) using ideal diode model

since  $V_s \geq 0$  , the diode is on and replaced with short circuit .

$$\therefore I_{DQ} = \frac{2}{100} = 20 \text{ mA}$$

$$\therefore V_{DQ} = 0 \text{ V}$$


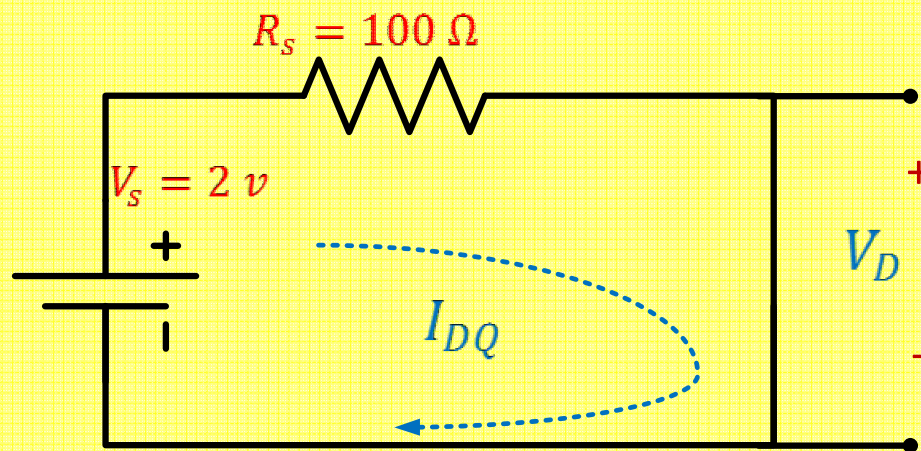


## b) Using knee voltage model

since  $V_s \geq 0.7$ , the diode is on and replaced with  $V_k = 0.7$ .

$$\therefore I_{DQ} = \frac{2 - 0.7}{100} = 13 \text{ mA}$$

$$\therefore V_{DQ} = 0.7 \text{ V}$$

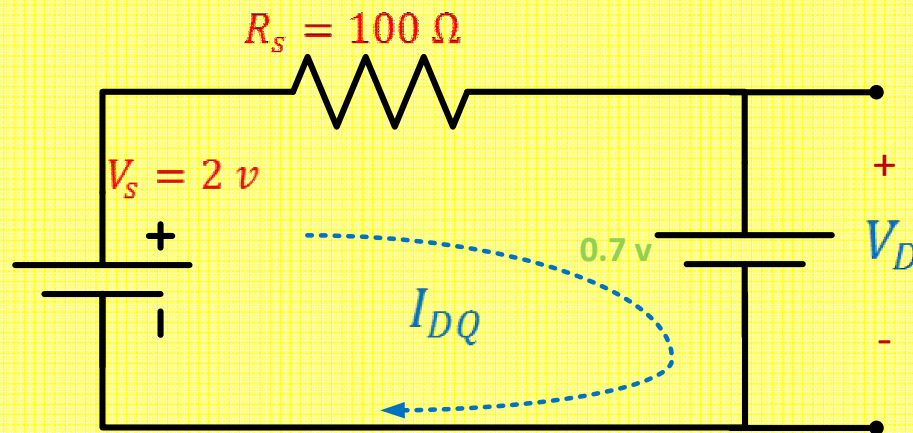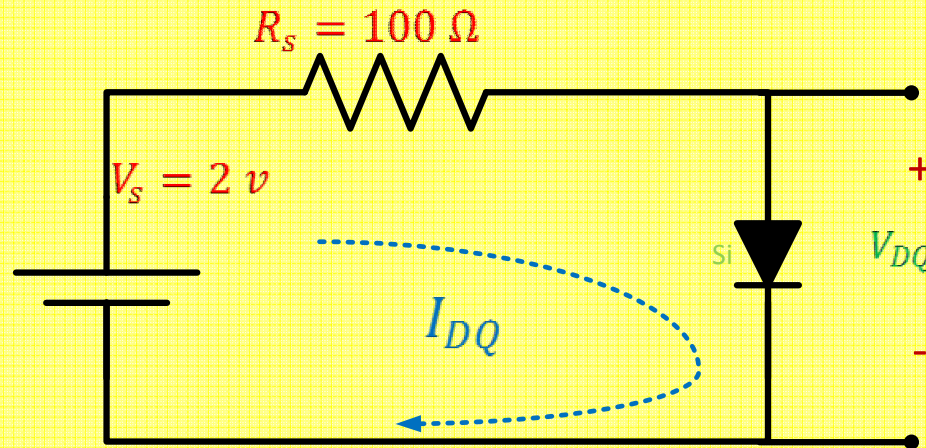

c) using nonlinear mathematic

$$I_{DQ} = 12.137 \text{ mA}$$

$$V_{DQ} = 0.7863 \text{ V}$$

## Taking the knee voltage into a count

- ▶ If  $V_S > 10 V_k$  , we could use ideal diode model .
- ▶ If  $V_S < 10V_k$  , we must use knee voltage model .