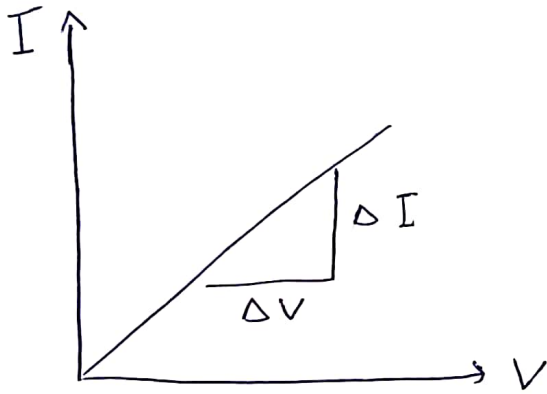


Exp 1 : Linear and non-linear Circuit components

Circuit components

Linear

- Components with straight line I-V characteristic (ohm's law)



$$\text{slope} = \frac{1}{R}$$

Example:

- * Carbon resistors.

Non-linear


- Components that don't possess straight line I-V characteristic.

Example:

(light bulb, diode)

* Light bulb

at low current has linear I-V

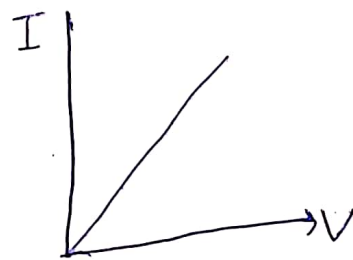

at high current



$$R = R_0 [1 + \alpha (T - T_0)]$$

R_0 = the resistance at temp = T_0

α = temp coefficient of resistivity

∴ So since the temp of the tungsten increases by increasing the current passing through it, one expects the light bulb to have a non-linear I-V characteristic and R that depends on the value of the current.

Light bulb



as $I \uparrow$ $T \uparrow$ ∴ R change

Diode

- A Semiconducting Diode: Consists of 2 pieces, P-type piece semiconducting material and n-type piece of the same material joined together.

Anode
P-type | n-type
Cathode

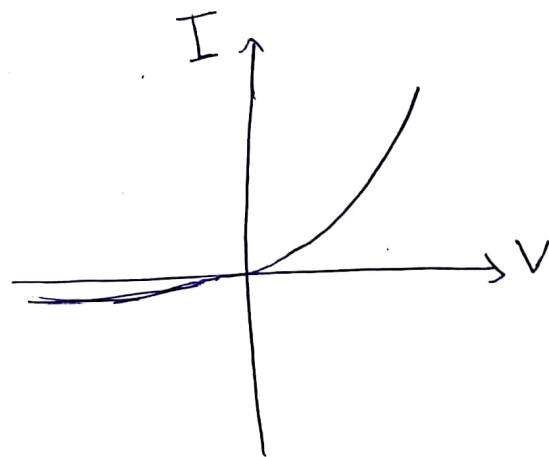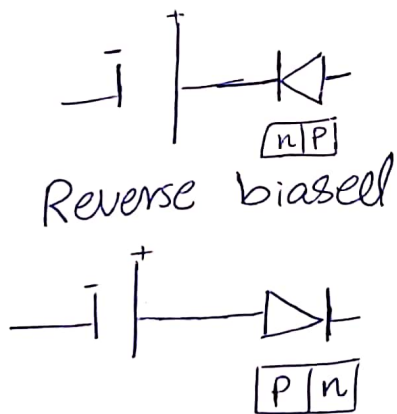* (P, n) components, one of them allow current to pass through in one direction only which is the P-type, while the n-type terminal connected to the battery, it blocks the current so that a very small current flow through the circuit.



Forward biased

$$I = I_0 (e^{V/K} - 1)$$




I_0 : Saturation Current

K : function of temp. only

$\therefore$ Then the diode has variable R that depends on the value of the current passes through it

procedure

1. Connect the circuit as shown:

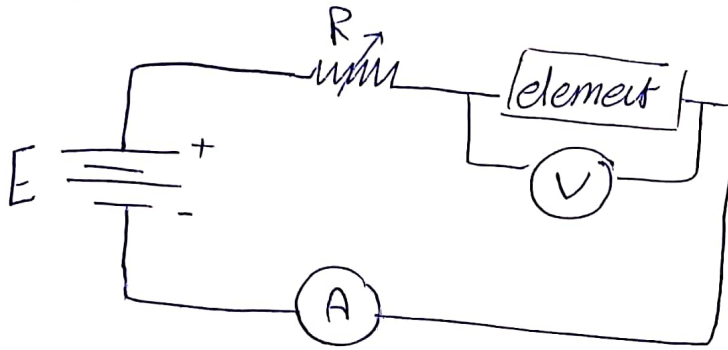

2. Change R , take eight different values for I , V according to the data sheet (for carbon resistor)

3. repeat (2) with forward-biased diode.
(Current shouldn't exceed 30mA)

4. Reverse bias your diode and check if it conducts or not, Register the current flowing, this is $\underline{I_0}$

5. repeat (2) using the light bulb

[high current needed to light the bulb $\sim 100\text{mA}$]

[Don't exceed $\sim 300\text{mA}$]

[start with high R , then decrease it gradually]

$\Rightarrow R_2, V = 10\text{V}$