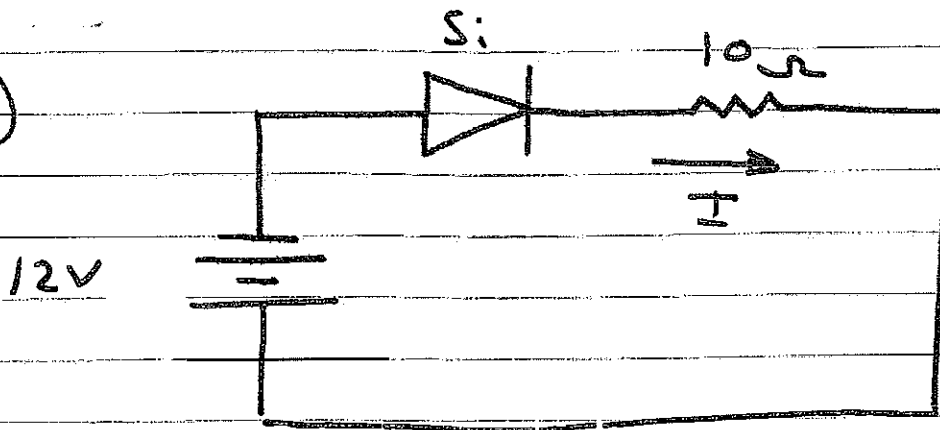


5:


a)




The diode is reversed bias

$$\therefore I = 0$$

b)

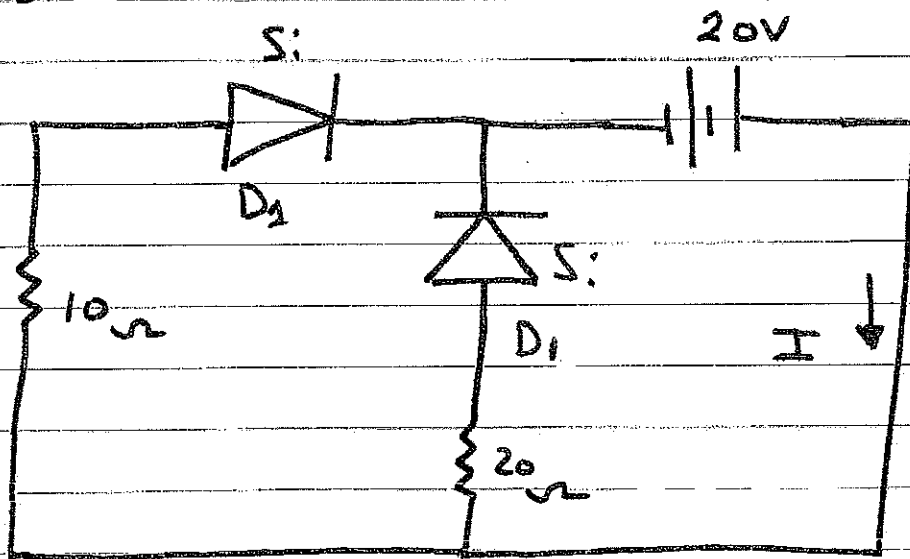

let assume D_1 and D_2 are on

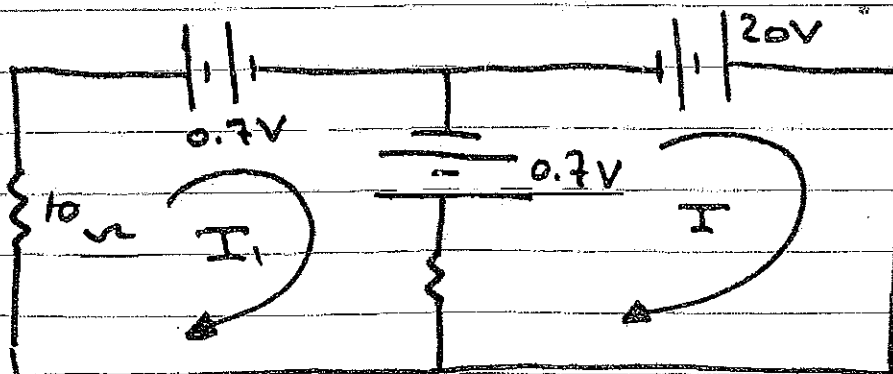

KVL in mesh ①

$$0 = 30 I_1 - 20 I$$

KVL in mesh ②

$$19.3 = 20 I - 20 I_1$$


Solving for I and I_1 , we get

$$I = 2.895 \text{ A}$$

$$I_1 = 1.93 \text{ A}$$

$$I_{D2} = I_1 = 1.93 \text{ A} > 0$$

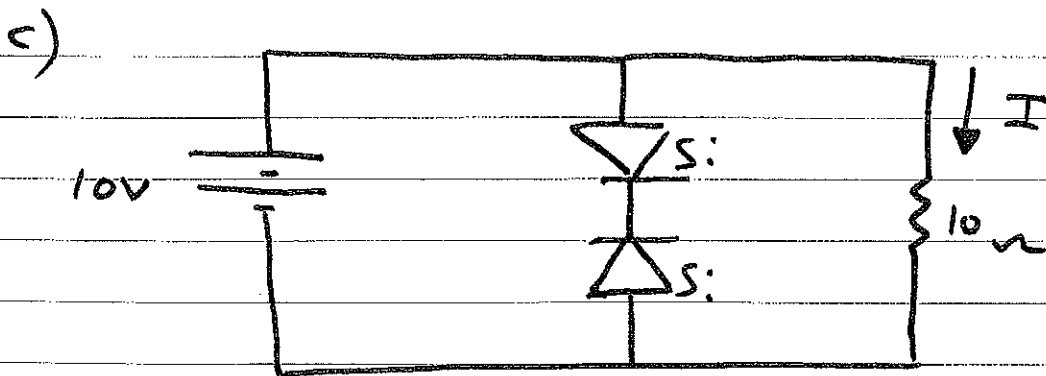
$$I_{D1} = I - I_1 = 0.965 \text{ A} > 0$$




Both diodes are OFF, replace them with open circuit

$$I = \frac{10\text{V}}{10\Omega} = 1\text{A}$$

26:

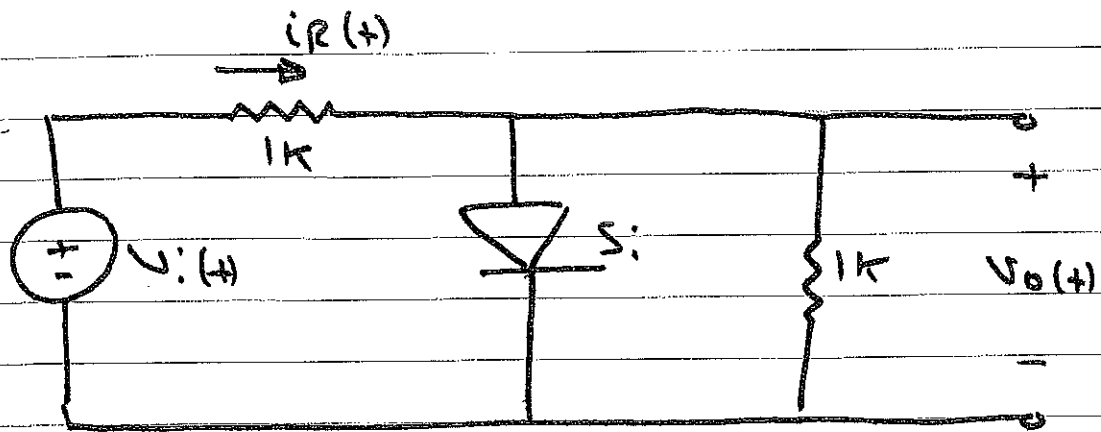

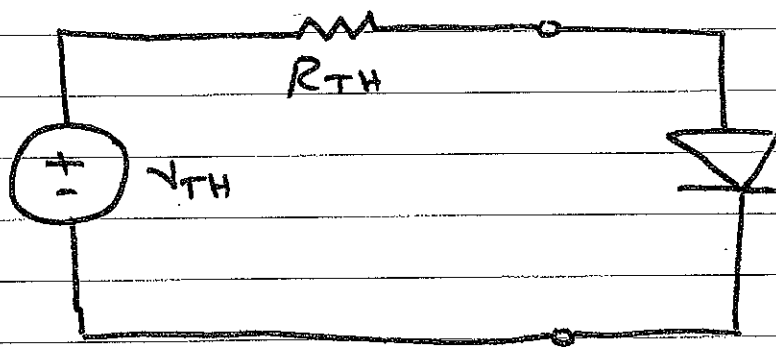
$V_i(t) = 10 \sin \omega t$
using thevenin's theorem



$$R_{TH} = 1k \parallel 1k = 0.5k$$

$$V_{TH} = \frac{1k}{1k+1k} V_i(t) = \frac{1}{2} V_i(t)$$

assume the diode is on

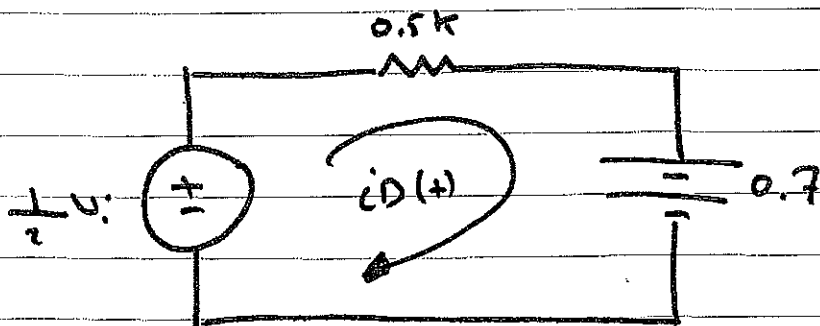


$$i_D(t) = \frac{\frac{1}{2} V_i(t) - 0.7}{0.5k} > 0$$

$$\therefore V_i(t) > 1.4V$$

-3-

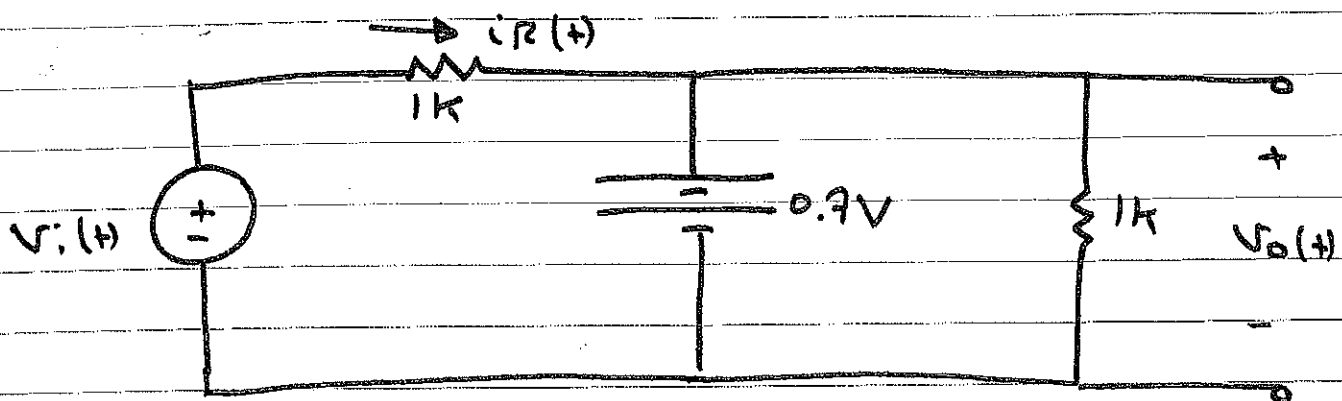
\therefore When $V_i(t) > 1.4\text{ V}$, Diode is on



$$V_o(t) = 0.7\text{ V}$$



$$i_R(t) = \frac{V_i(t) - 0.7\text{ V}}{1\text{k}}$$

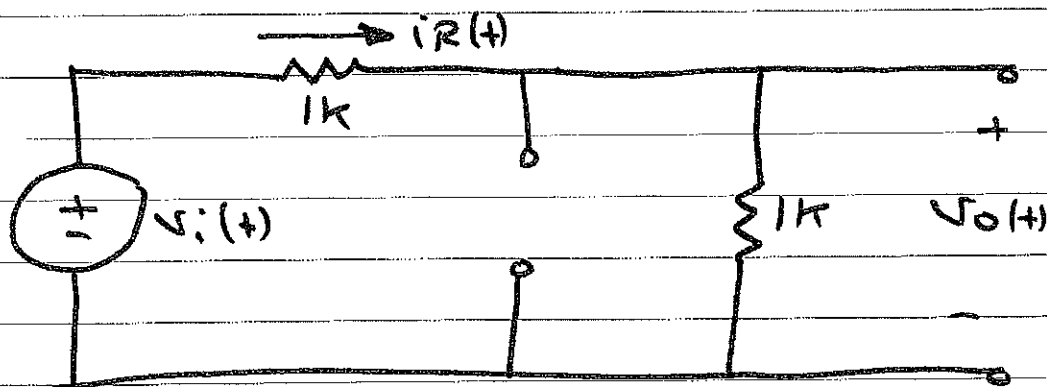When $V_i(t) < 1.4\text{ V}$, Diode is off




$$V_o(t) = \frac{1}{2} V_i(t)$$

$$i_R(t) = \frac{V_i(t)}{2\text{k}}$$

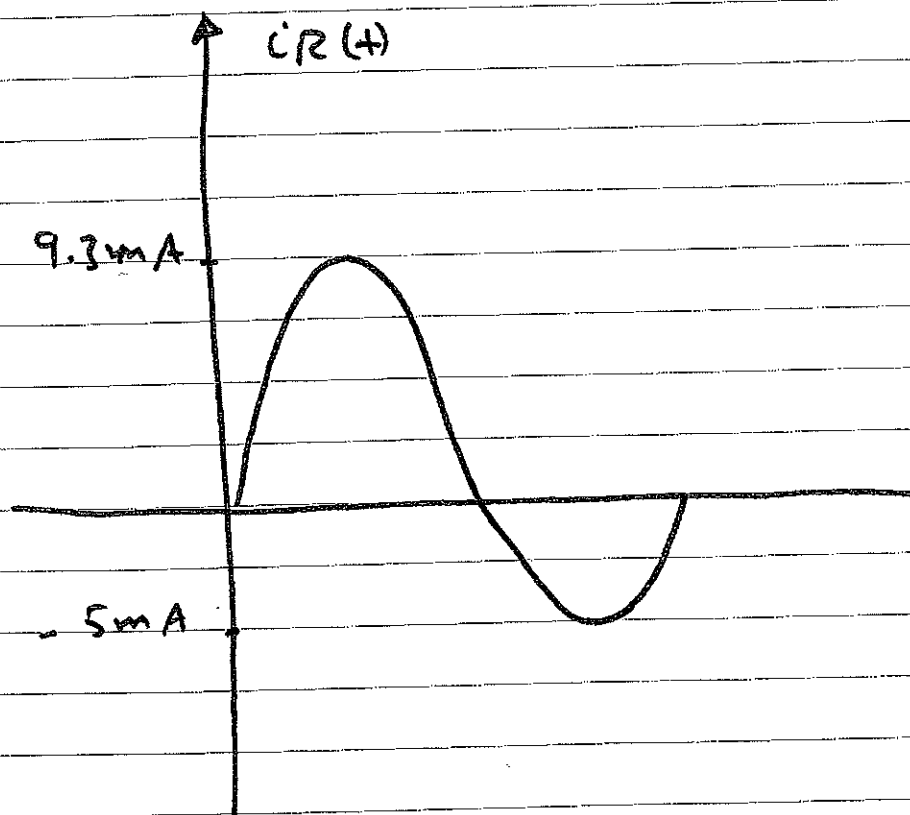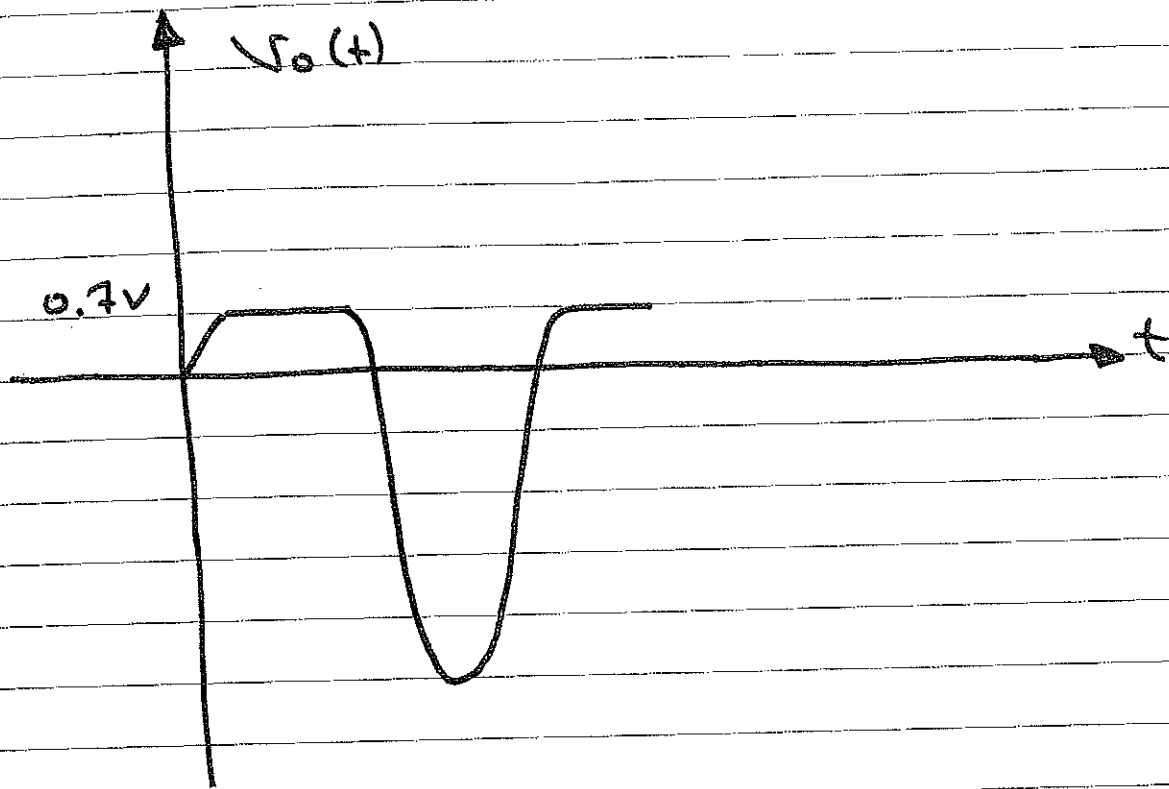

27:

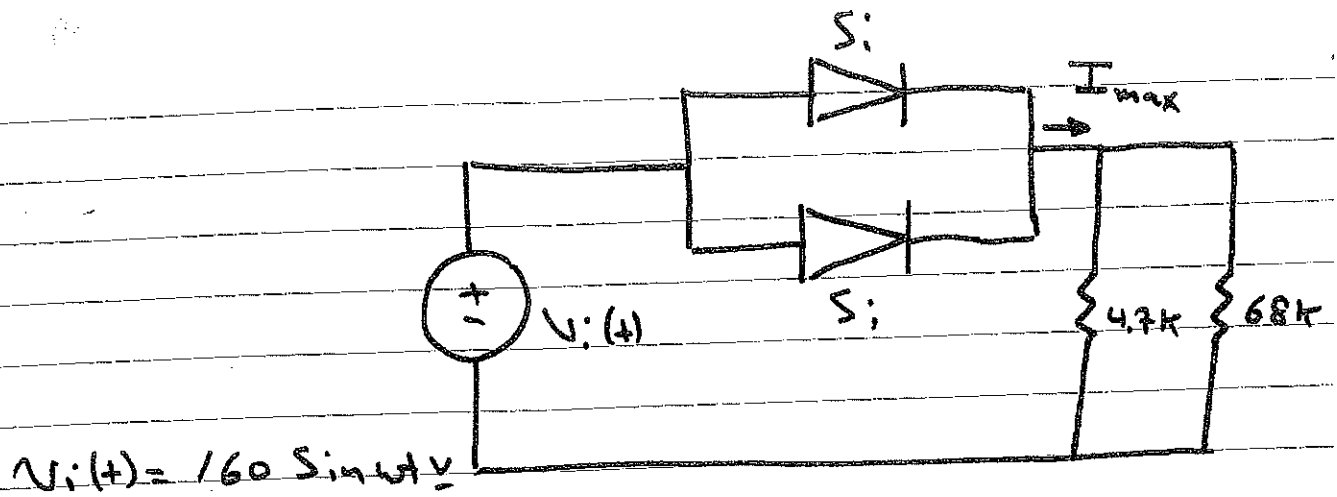


$$P_{max} = 0.7 I_{D,max} = 14 \text{ mW}$$

a) $\therefore I_{D,max} = 20 \text{ mA}$

b) $I_{max} = 2 I_{D,max} = 40 \text{ mA}$

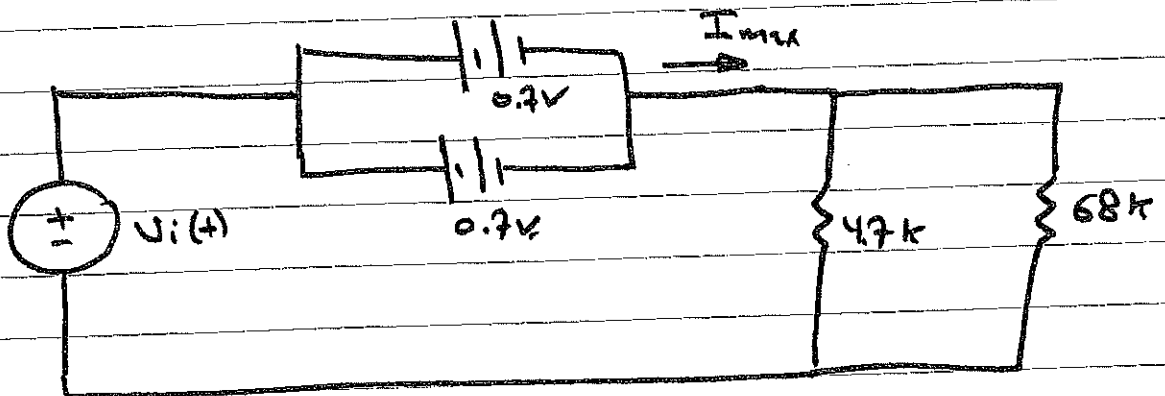c) When $V_i(t) = 160 \text{ V}$, both diodes are on




$$I_{max} = \frac{160 - 0.7}{4.7k \parallel 68k} = 36.2 \text{ mA}$$

$$I_D = \frac{I_{max}}{2} = 18.1 \text{ mA}$$

d) $I_D = 36.2 \text{ mA} > 20 \text{ mA}$


\therefore The diode will be damaged

31 :

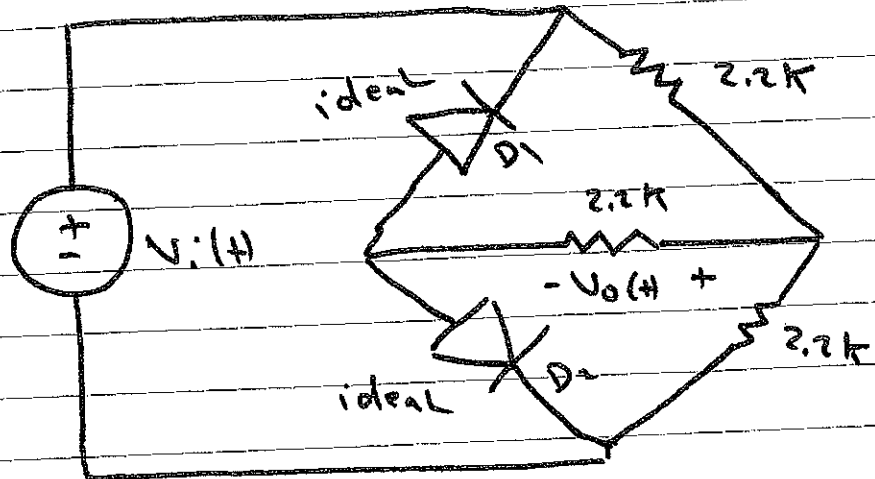

$$V_i(t) = 170 \sin \omega t \text{ V}$$

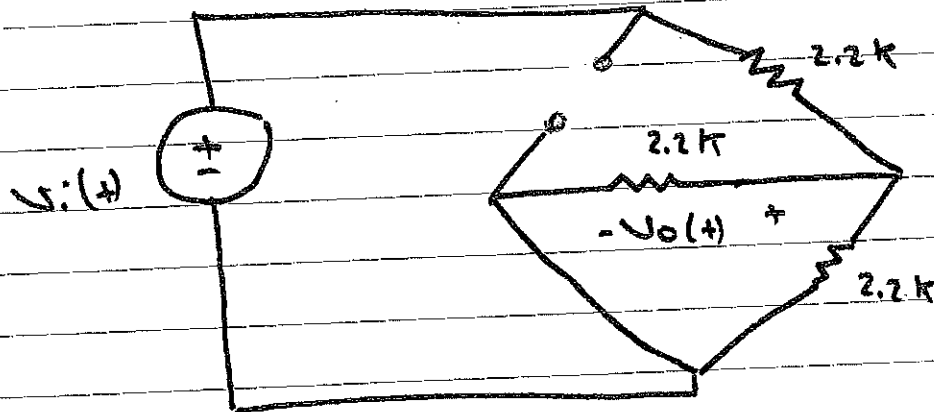
When $V_i(t) > 0$, D_1 is off and D_2 is on



$$V_o(t) = \frac{2.2\text{ k}\Omega \parallel 2.2\text{ k}\Omega}{2.2\text{ k}\Omega \parallel 2.2\text{ k}\Omega + 2.2\text{ k}\Omega} V_i(t)$$


$$V_o(t) = +0.333 V_i(t)$$

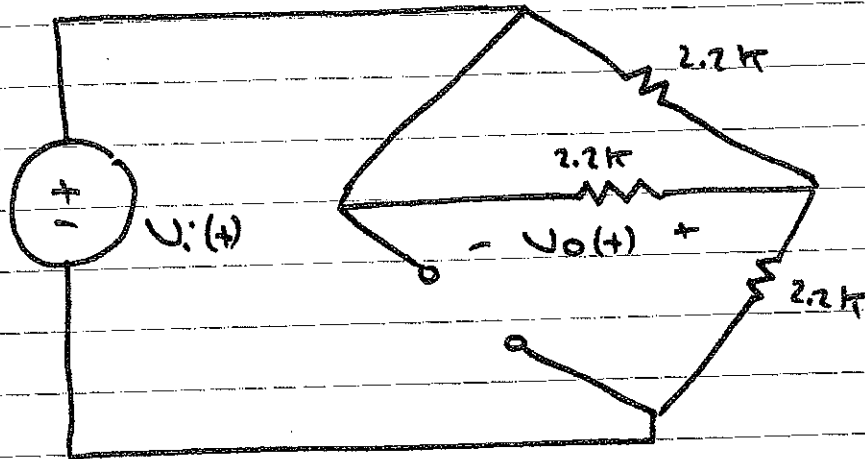When $V_i(t) < 0$, D_1 is on, and D_2 is off



$$V_o(t) = - \frac{2.2k \parallel 2.2k}{2.2k \parallel 2.2k + 2.2k} V_i(t)$$


$$V_o(t) = - 0.333 V_i(t)$$

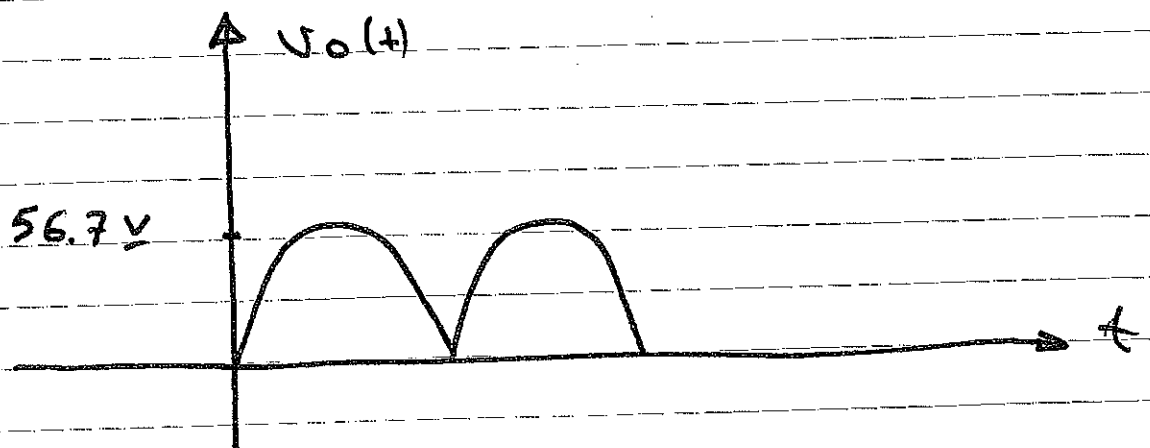

$$V_{o,dc} = \frac{2\sqrt{I_m}}{\pi} \approx 36 \text{ V}$$


35 :

a)

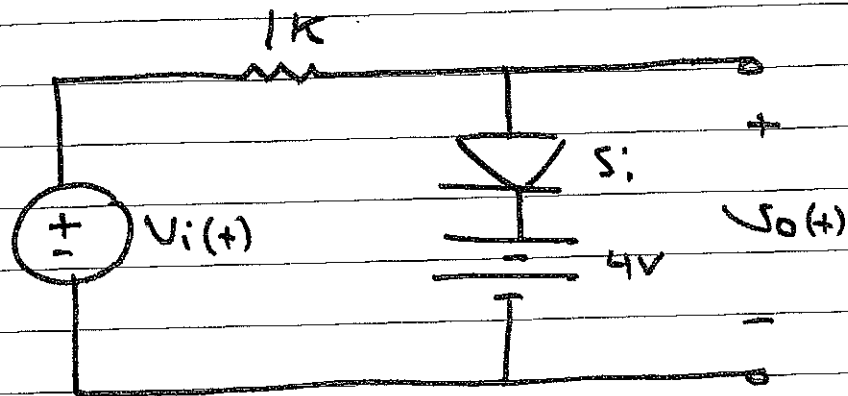

$$v_i(t) = 8 \sin \omega t \text{ V}$$

assume the diode is on

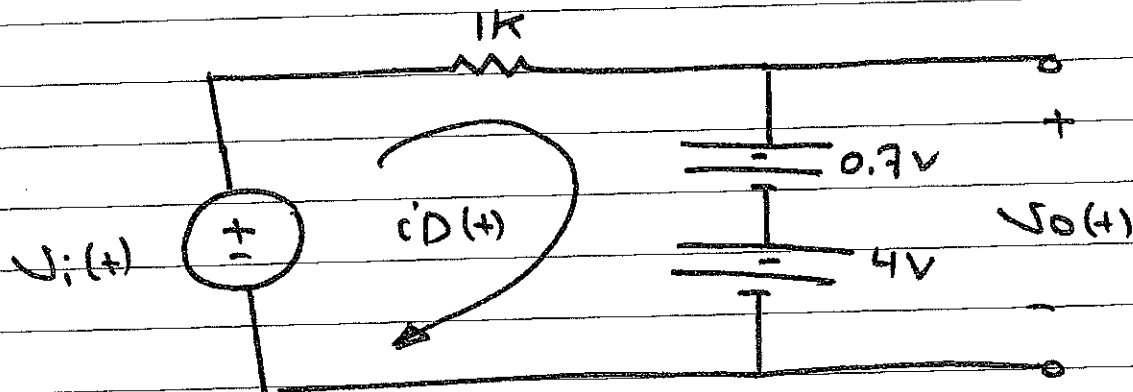

$$i_D(t) = \frac{v_i(t) - 4.7}{1k} > 0$$


$$\therefore v_i(t) > 4.7 \text{ V}$$

\therefore When $v_i(t) > 4.7 \text{ V}$, Diode is on


$$\text{and } v_o(t) = 4.7 \text{ V}$$

\therefore When $v_i(t) < 4.7 \text{ V}$, Diode is off


$$v_o(t) = v_i(t)$$

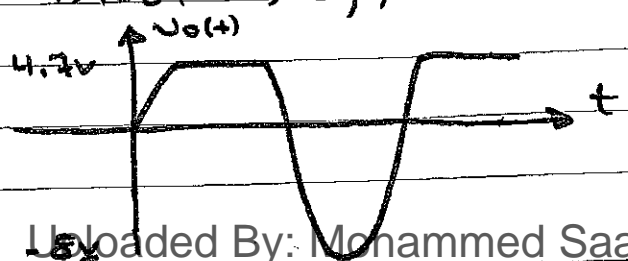

b)

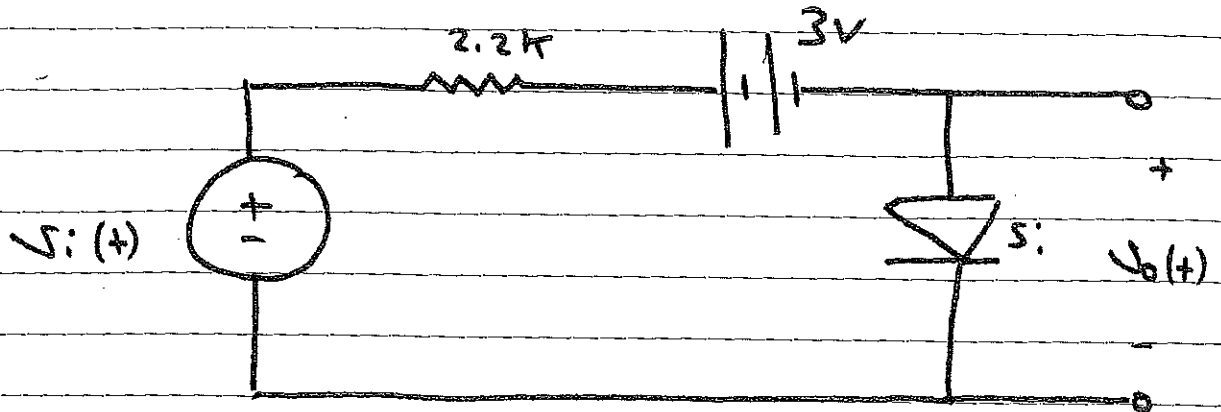

assume the diode is on

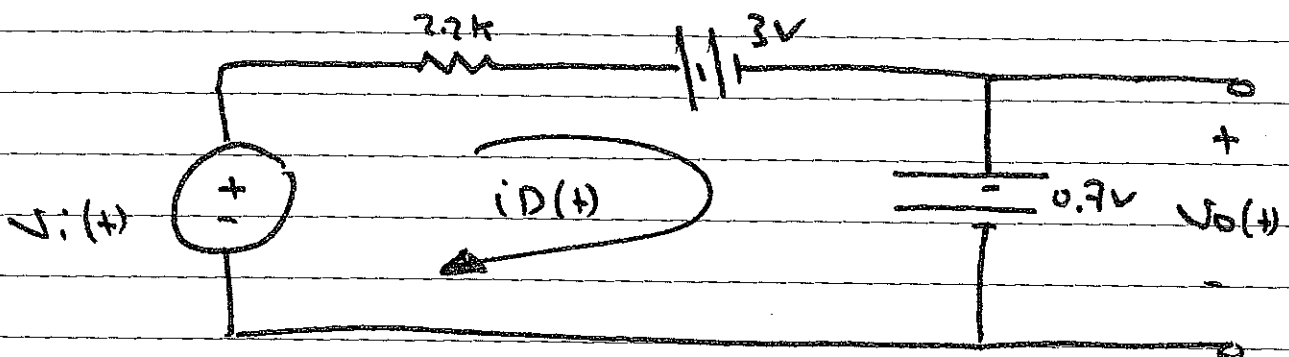

$$i_D(t) = \frac{v_i(t) - 3.7}{2.2k} > 0$$

$$\therefore v_i(t) > 3.7V$$

$$\therefore \text{When } v_i(t) > 3.7V, v_o(t) = 0.7V$$

$$\therefore \text{When } v_i(t) < 3.7V, v_o(t) = v_i(t) - 3$$

