



Instructor : Nasser Ismail


Biasing

Biasing: Applying DC voltages to a transistor in order to establish fixed level of voltage and current. For Amplifier (active/Linear) mode, the resulting dc voltage and current establish the operation point to turn it on so that it can amplify AC signals.

DC Biasing Circuits


1. Fixed-bias circuit
2. Emitter-stabilized bias circuit
3. DC bias with voltage feedback
4. Voltage divider bias circuit

1) Fixed Bias Configuration

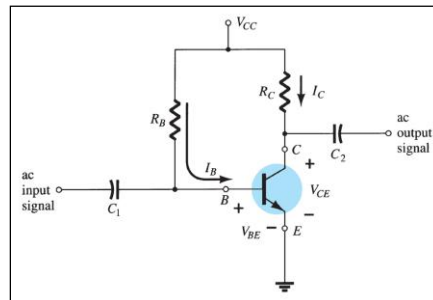

DC equivalent circuit $\Rightarrow$ means $f = 0$
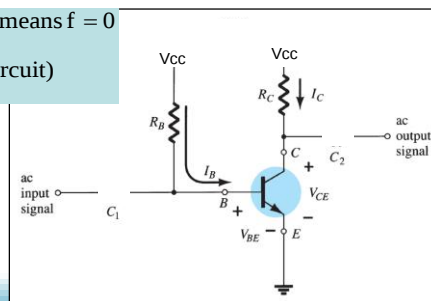
$$\Rightarrow X_C = \frac{1}{2\pi f C} \cong \infty \text{ (open circuit)}$$



The Base-Emitter Loop


From Kirchhoff's voltage law for Input:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

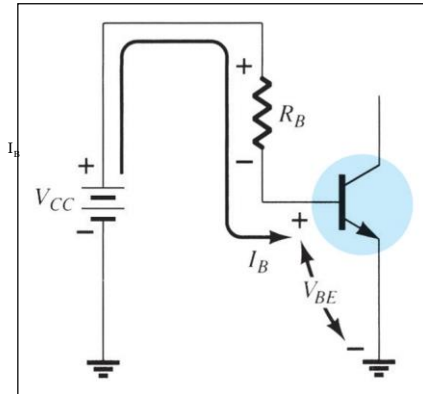Choosing R_B will establish the required level of I_B



Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$


$$\text{Since } V_E = 0 \Rightarrow \therefore V_{CE} = V_C$$

$$V_{CE} = V_{CC} - I_C R_C$$

Also

$$V_{BE} = V_B - V_E$$

$$\therefore V_{BE} = V_B$$

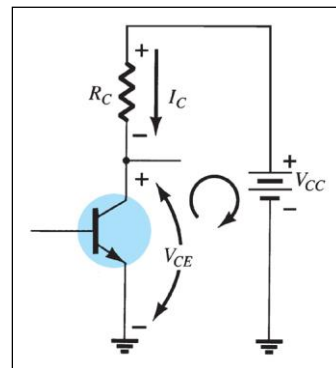

$$\begin{aligned} V_{BC} &= V_B - V_C \\ V_{BE} - V_{CE} - V_{BC} &= 0 \\ \therefore V_{BC} &= V_{BE} - V_{CE} \end{aligned}$$

Design of Fixed Bias Circuit

Assume $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$ (i.e find unknown component values R_B and R_C)

Solution

$$I_{BQ} = \frac{I_{CQ}}{\beta_{nominal}} = \frac{1mA}{100} = 10\mu A$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{10\mu A} = 930k\Omega$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 5 = 10 - I_C R_C$$
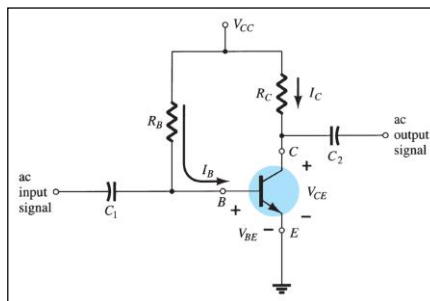
$$\therefore R_C = \frac{5}{1mA} = 5k\Omega$$



Fixed bias Stability

Assume $V_{CC} = 10V$, $\beta_{nominal} = 100$, $\beta_{min} = 50$, $\beta_{max} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution – continued

If $\beta = \beta_{min} = 50$

$$I_B = 10\mu A$$

$$I_C = \beta I_B = (50)(10\mu A) = 0.5mA$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 10 - (0.5mA)(5k\Omega) = 7.5V$$


If $\beta = \beta_{max} = 150$

$$I_B = 10\mu A$$

$$I_C = \beta I_B = (150)(10\mu A) = 1.5mA$$

$$V_{CE} = V_{CC} - I_C R_C$$
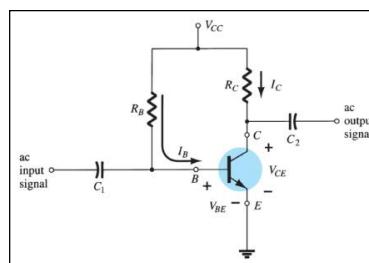
$$V_{CEQ} = 10 - (1.5mA)(5k\Omega) = 2.5V$$



for

$$50 \leq \beta \leq 150$$

$$I_B = 10\mu A \text{ fixed}$$


$$0.5mA \leq I_C \leq 1.5mA$$

$$7.5V \geq V_{CE} \geq 2.5V$$

$$\therefore \frac{I_{C(max)}}{I_{C(min)}} = \frac{1.5mA}{0.5mA} = 3 \quad \text{Not very stable}$$

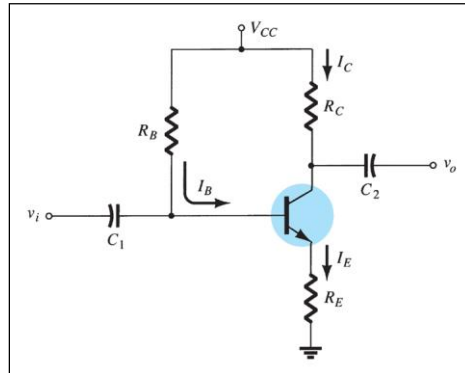2) Emitter-Stabilized Bias Circuit

Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.



Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$


Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for I_B :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

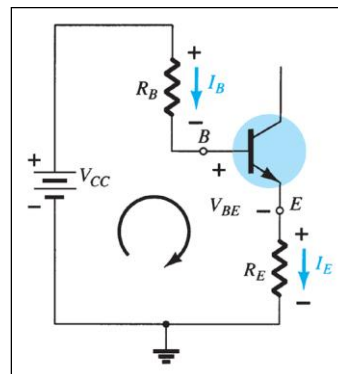$(\beta + 1)R_E$ ← is the emitter resistor as it appears in the base emitter loop



Base-Emitter Loop


Solving for I_E :

$$I_E = \frac{V_{CC} - V_{BE}}{\frac{R_B}{(\beta + 1)} + R_E}$$

In order to get I_E almost independent of β we choose:

$$R_E \gg \frac{R_B}{(\beta + 1)}$$
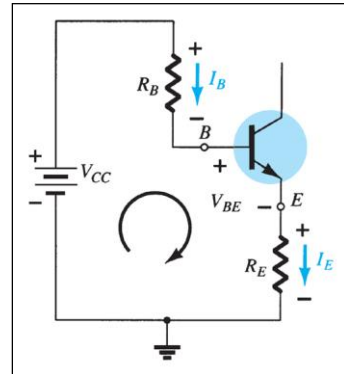
$$\Rightarrow I_E \cong \frac{V_{CC} - V_{BE}}{R_E}$$



Also, in order to guarantee operation in linear mode we choose $0.1V_{CC} \leq V_E < 0.2V_{CC}$

Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \cong I_C$:


$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
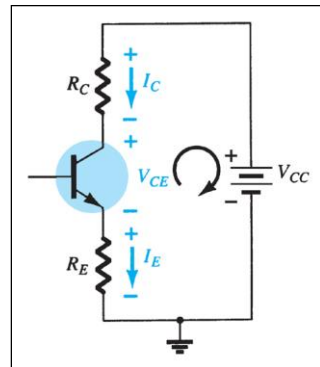
$$V_B = V_{CC} - I_B R_B = V_{BE} + V_E$$



Design: Emitter Stabilization bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q-point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution


– let $V_E = 0.1 V_{CC}$

$$V_E = 1V$$

$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01mA} \cong 1k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \Rightarrow$$
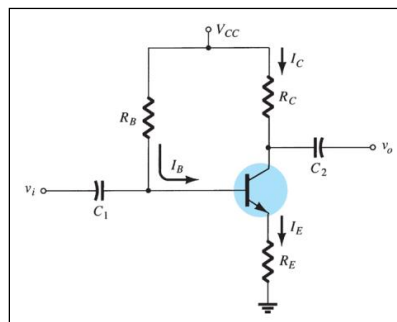
$$R_B I_B + I_B (\beta + 1) R_E = V_{CC} - V_{BE}$$



$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 5 = 10 - 1 - I_C R_C$$

$$\therefore R_C = \frac{4}{1mA} = 4k\Omega$$

Emitter bias Stability

If $\beta = \beta_{\text{min}} = 50$

$$I_B = \frac{9.3}{829k\Omega + 51k\Omega} = 10.56 \mu A$$

$$I_C = \beta I_B = (50)(10.56 \mu A) = 0.528 mA$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$V_{CEQ} = 10 - (0.528 mA)(4k\Omega) - 1 = 6.89 V$$


If $\beta = \beta_{\text{max}} = 150$

$$I_B = \frac{9.3}{829k\Omega + 151k\Omega} = 9.489 \mu A$$

$$I_C = \beta I_B = (150)(9.489 \mu A) = 1.423 mA$$

$$V_{CE} = V_{CC} - I_C R_C - V_E$$
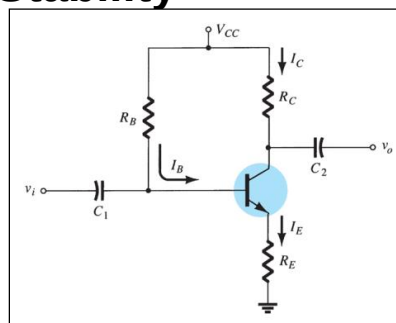
$$V_{CEQ} = 10 - (1.423 mA)(4k\Omega) - 1 = 3.31 V$$



for

$$50 \leq \beta \leq 150$$

$$10.56 \mu A \geq I_B \geq 9.489 \mu A$$


$$0.528 mA \leq I_C \leq 1.423 mA$$

$$6.89 V \geq V_{CE} \geq 3.31 V$$


$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.423 mA}{0.528 mA} \cong 2.7$$

Improved,
but not
very
stable

Fixed bias

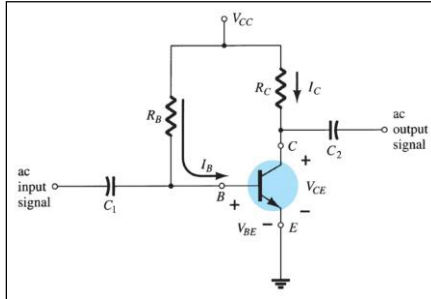


Emitter Stabilization bias

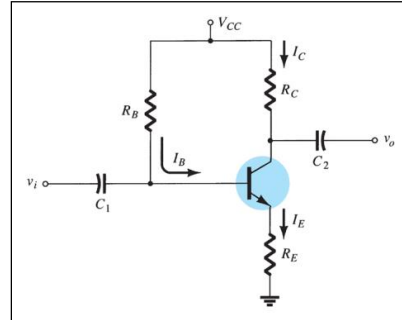

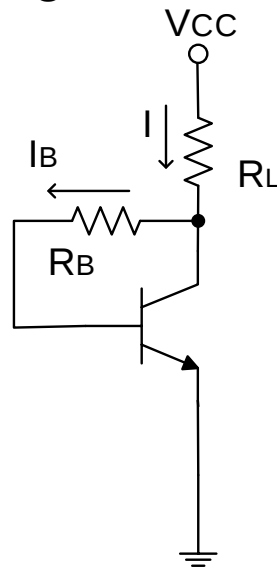3) DC Bias With Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .



Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I R_L - I_B R_B - V_{BE} = 0$$

$$I = I_C + I_B$$

$$I_C = \beta I_B$$

Solving for I_B :


$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$V_{CC} = I R_L + V_{CE}$$

$$I = I_C + I_B$$

$$V_{CE} = V_{CC} - (I_C + I_B) R_L$$

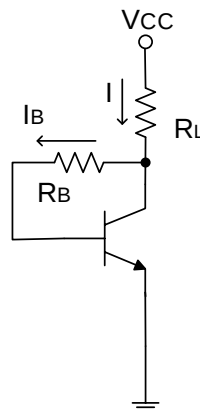suppose $\beta \uparrow, I_B \downarrow, I_C = \beta I_B \downarrow \cong \text{const}$
there is some kind of compensation effect



Design: Voltage feedback bias

Assume $V_{CC} = 10V, \beta_{\text{nominal}} = 100, \beta_{\text{min}} = 50, \beta_{\text{max}} = 150$

Design for Q-point: $V_{CEQ} = 5V, I_{CQ} = 1mA$

Solution

$$R_L = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{10 - 5}{1mA + \frac{1mA}{100}} = 4.95 \text{ k}\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_L(\beta + 1) + R_B}$$

$$\therefore R_B = 430 \text{ k}\Omega$$

$$\text{If } \beta = \beta_{\text{min}} = 50$$

$$I_B = 0.013627 \text{ mA}$$

$$I_C = 0.68 \text{ mA}$$

$$\text{If } \beta = \beta_{\text{max}} = 150$$

$$I_B = 0.00793 \text{ mA}$$

$$I_C = 1.19 \text{ mA}$$


for

$$50 \leq \beta \leq 150$$

$$0.68 \text{ mA} \leq I_C \leq 1.19 \text{ mA}$$

$$\therefore \frac{I_{C(\text{max})}}{I_{C(\text{min})}} = \frac{1.19 \text{ mA}}{0.68 \text{ mA}} \cong 1.75$$


Better
Q-point
stability

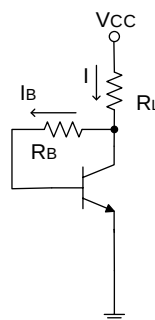

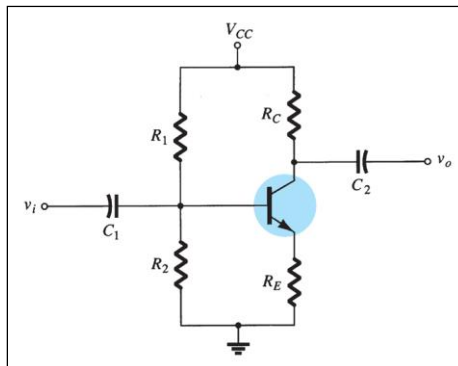4) Voltage Divider Bias

This is a very stable bias circuit.

The currents and voltages are nearly independent of any variations in β if the circuit is designed properly



Approximate Analysis

Where $I_B \ll I_1$ and $I_1 \cong I_2$:

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$I_{E(\text{approximate})} = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E}$$


From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

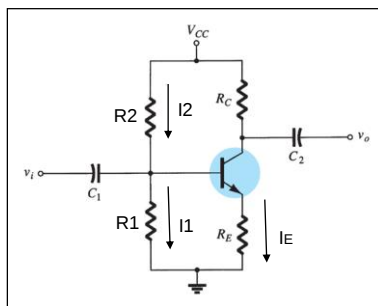Here we got I_C independent of β which provides good Q-point stability



Exact Analysis

We must try to make I_B as close as possible to zero

Thevenin Equivalent circuit for the circuit left of the base is done



$$V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\text{but } I_B = \frac{I_E}{\beta + 1}$$
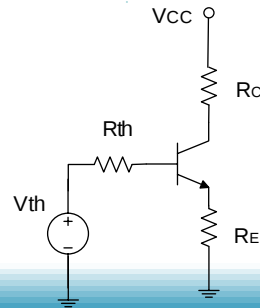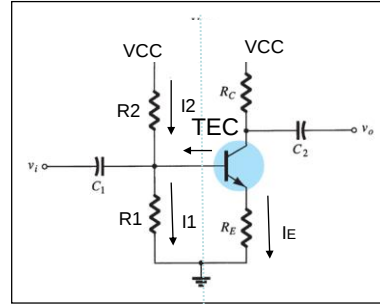
$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$



Exact Analysis

$$\therefore I_{E(\text{exact})} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$$

if we compare to approximate solution

$$I_{E(\text{approximate})} = \frac{V_B - V_{BE}}{R_E}$$

$\Rightarrow$ we must make the quantity $\frac{R_{th}}{\beta + 1} \ll R_E$



Here we got I_C independent of β

$$\therefore R_{th} \ll (\beta + 1) R_E$$

$$\text{as a rule let } R_{th} \ll \frac{(\beta + 1) R_E}{10}$$

or

$$R_{th} \ll \frac{\beta R_E}{10}$$

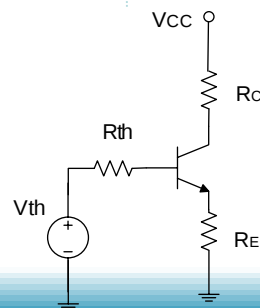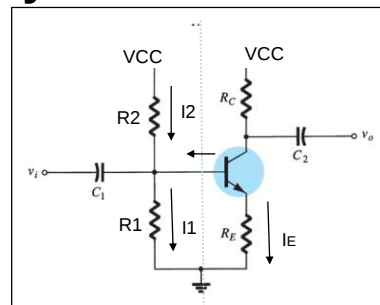

Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution

1) let $V_E = 0.1 V_{CC}$

$$V_E = 1V$$


$$I_E = \frac{V_E}{R_E} \Rightarrow R_E = \frac{1V}{1.01mA} \cong 1k\Omega$$

2) let $R_{th} = \frac{R_E \cdot \beta_{\text{nominal}}}{50} = \frac{1k\Omega \cdot 100}{50} = 2k\Omega$

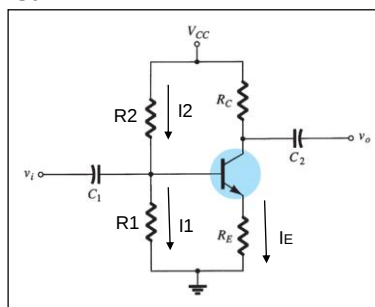3) $V_{CC} = R_C I_C + I_E R_E + V_{CE}$

$$V_{CEQ} = 5$$

$$\therefore R_C = \frac{V_{CC} - V_{CE} - V_E}{1mA} = \frac{10 - 5 - 1}{1mA} = 4k\Omega$$



Design: Voltage Divider bias

Assume $V_{CC} = 10V$, $\beta_{\text{nominal}} = 100$, $\beta_{\text{min}} = 50$, $\beta_{\text{max}} = 150$

Design for Q - point : $V_{CEQ} = 5V$, $I_{CQ} = 1mA$

Solution – continued

4) $I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E}$


$$\therefore V_{th} = \frac{R_1 V_{CC}}{R_1 + R_2} = I_E \left(\frac{R_{th}}{\beta + 1} + R_E \right) + V_{BE} = 1.72V \dots (1)$$

$$R_{th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = 2k\Omega \dots \dots \dots (2)$$

solving (1) & (2) yields:

$$R_1 = 2.42k\Omega$$

$$R_2 = 11.64k\Omega$$

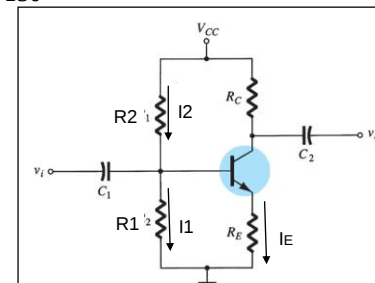

Voltage Divider bias Stability

If $\beta = \beta_{\min} = 50$

$I_C = 0.982 \text{ mA}$

If $\beta = \beta_{\max} = 150$

$I_C = 1.0069 \text{ mA}$

for

$50 \leq \beta \leq 150$

$0.982 \text{ mA} \leq I_C \leq 1.0067 \text{ mA}$

$$\therefore \frac{I_{C(\max)}}{I_{C(\min)}} = \frac{1.0067 \text{ mA}}{0.982 \text{ mA}} \cong 1.0254$$

Very good
Q-point
stability


PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *nnp* transistor circuits. The only difference is that the currents are flowing in the opposite direction.

Circuit using pnp transistor:

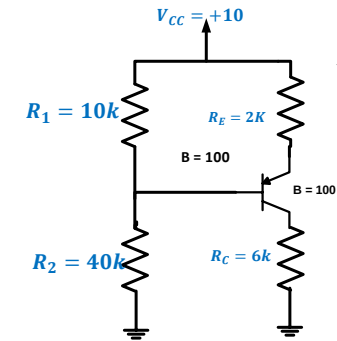Example:

Find I_E , V_{EC} , for the circuit below:



$V_{CE} = -5V$ Which is $< -0.2V$

Using thevenin's theorem:



$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 * 40}{10 + 40} k = 8k\Omega$$


$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{40}{10 + 40} * 10 = 8volt$$

KVL: $10 = 2kI_E + V_{EB} + R_{th}I_B + V_{th}$

$\Rightarrow I_E = 0.625mA$

KVL: $10 = 2kI_E + V_{EC} + 6kI_C$


$\Rightarrow V_{EC} = 5volt$

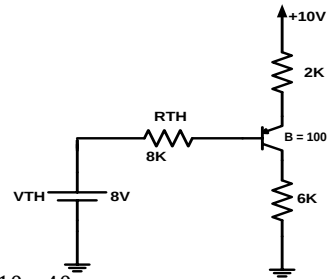

Example:

Find I_{E1} , I_{E2}

Solution

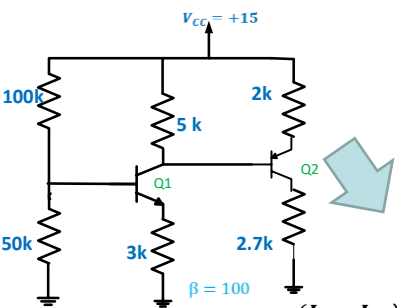

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{50 * 100}{50 + 100} k = 33.3k\Omega$$


$$V_{th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{50}{50 + 100} * 15 = 5 volt$$

KVL:

$$I_{E1} = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta + 1} + R_E} = \frac{5 - 0.7}{\left(\frac{33.3k}{101}\right) + 3k} = 1.28mA$$

KVL:
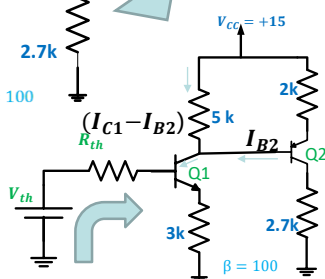
$$2kI_{E2} + V_{EB} - 5k(I_{C1} - I_{B2}) = 0$$
$$I_{E2} = 2.78mA$$






BJT Ac-Small signal analysis using Graphical method:

Graphical method:

KVL: $V_{CC} = R_C I_C + V_{CE}$
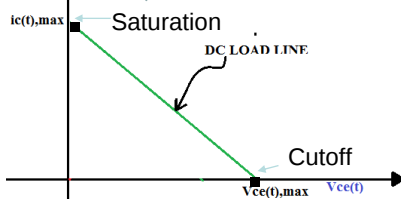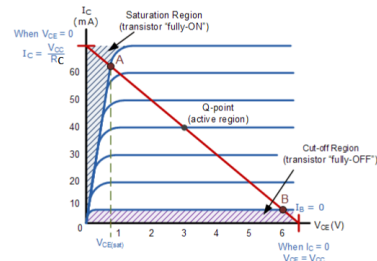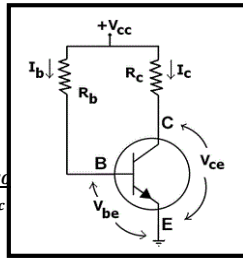
$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C}$$



$$i_{C(t),max} = \frac{V_{CC}}{R_C} \quad \text{Saturation}$$

$$V_{CE(t),max} = V_{CC} \quad \text{Cutoff}$$


BJT Amplifier

Using superposition

$$V_{BE}(t) = V_{BE} + v_{be}$$

$$i_C(t) = I_{CQ} + i_c$$

$$V_{CE}(t) = V_{CEQ} + v_{ce}$$

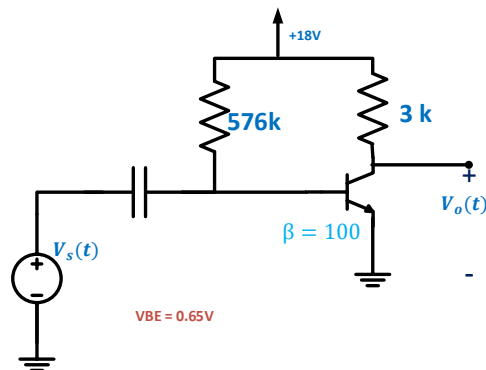

DC Load Lines

Assume $V_{CC} = 18V$, $\beta = 100$

$R_B = 576\text{ k}\Omega$; $R_C = 3\text{ k}\Omega$; $V_{BE} = 0.7\text{ V}$

FIRST: DC ANALYSIS

$$V_{CC} = V_{CE} + I_C R_C$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C} \Leftarrow I_C = f(V_{CE})$$


This is a straight line equation

$$Y = mX + b$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.7}{576\text{ k}\Omega} = 30\text{ }\mu\text{A}$$

$$I_C = \beta I_B = 3\text{ mA}$$
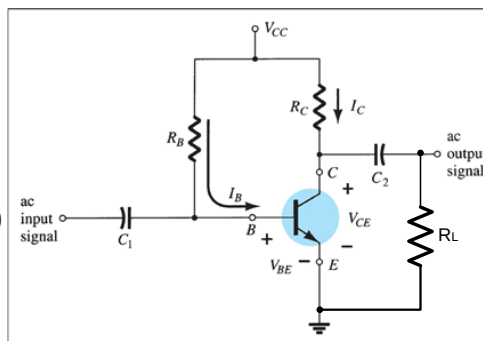
$$V_{CE} = V_{CC} - I_C R_C = 18 - (3\text{ mA})(3\text{ k}\Omega) = 9\text{ V}$$



DC Load Line

I_{Csat}


$$I_{Csat} = \frac{V_{CC}}{R_C}$$

$$V_{CE} = V_{CE(sat)} \cong 0\text{ V}$$

$V_{CEcutoff}$

$$V_{CE(cutoff)} = V_{CC}$$




$$I_C = 0\text{ mA}$$

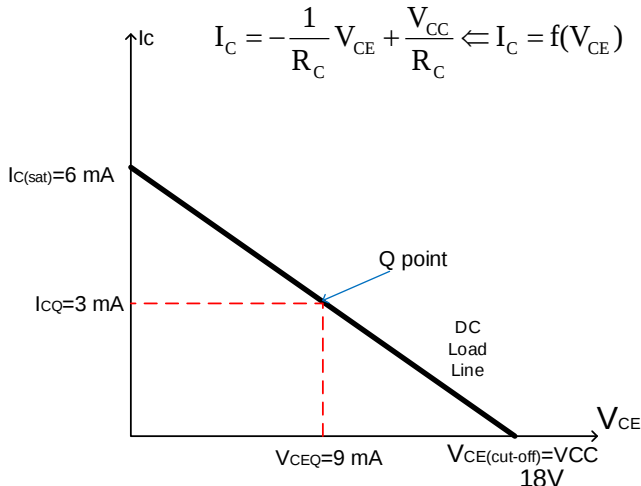

Basic BJT Amplifiers Circuits (for info only)

Graphical Analysis

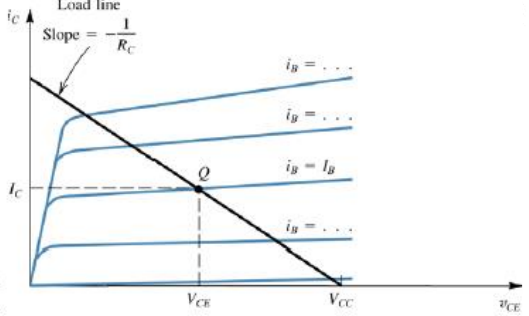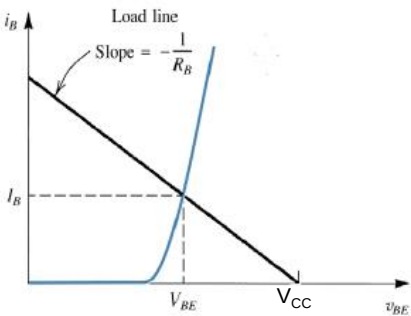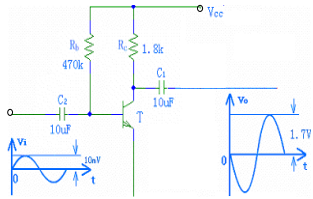- Can be useful to understand the operation of BJT circuits.
- First, establish DC conditions by finding I_B (or V_{BE})
- Second, figure out the DC operating point for I_C






Can get a feel for whether the BJT will stay in active region of operation
– What happens if R_C is larger or smaller?



Basic BJT Amplifiers Circuits

(for info only)

Graphical Analysis

Q-point is centered on the ac load line:

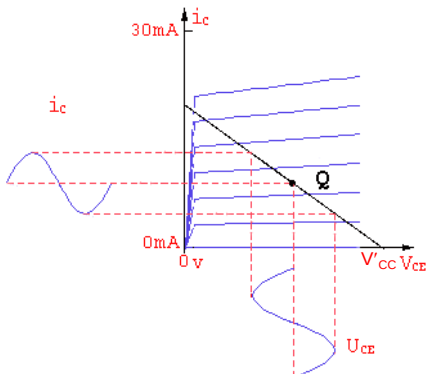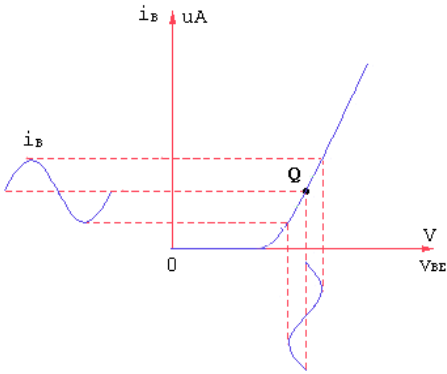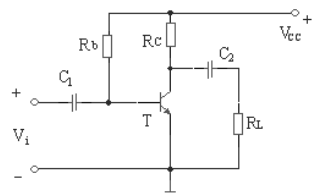

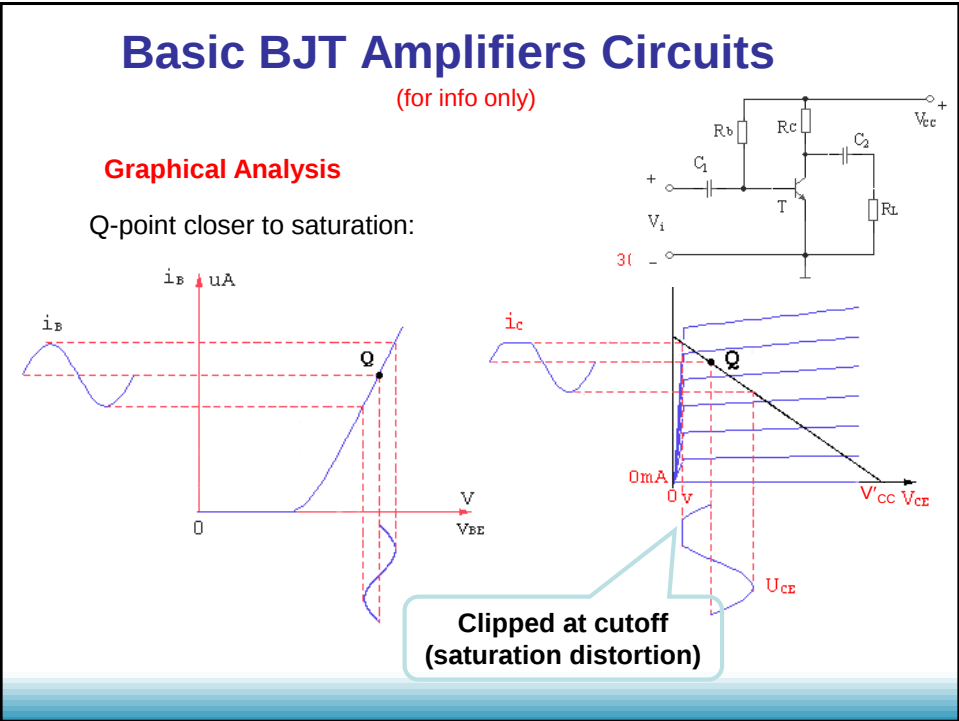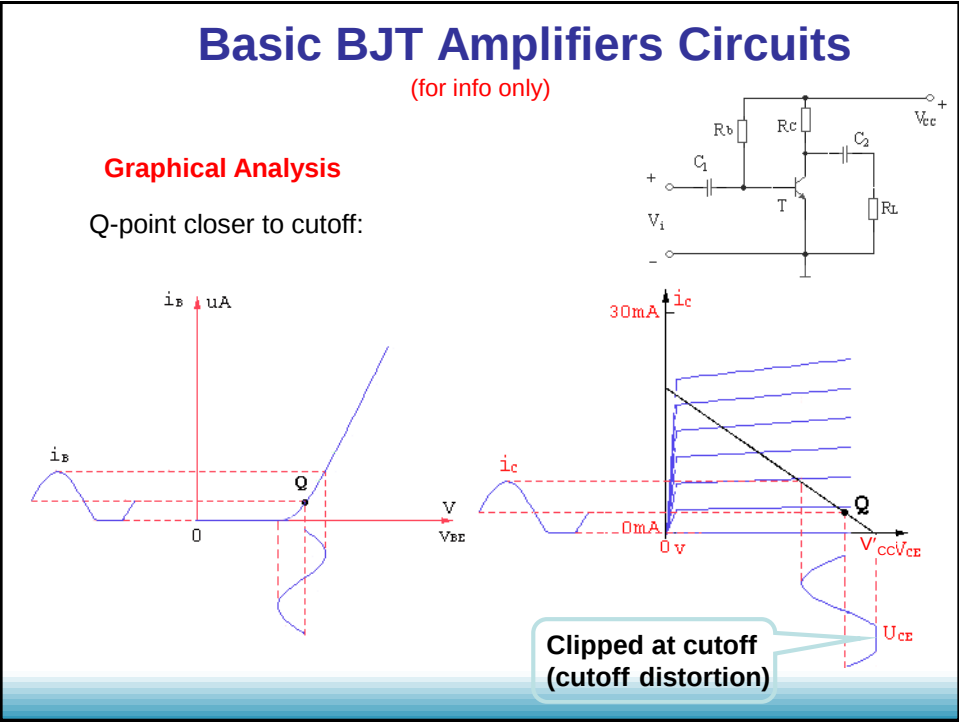

Basic BJT Amplifiers Circuits

(for info only)

Graphical Analysis

