



FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMPUTER
ENGINEERING

ENEE 2101

Circuits Laboratory

Experiment.9 Prelab

AC & DC Power Analysis and Design

Prepared by:

Malak Qasem 1210484

Supervised by:



Dr. Jaser Sa'ed

Teacher assistance:

Eng. Mohammed Deek

November 26, 2024

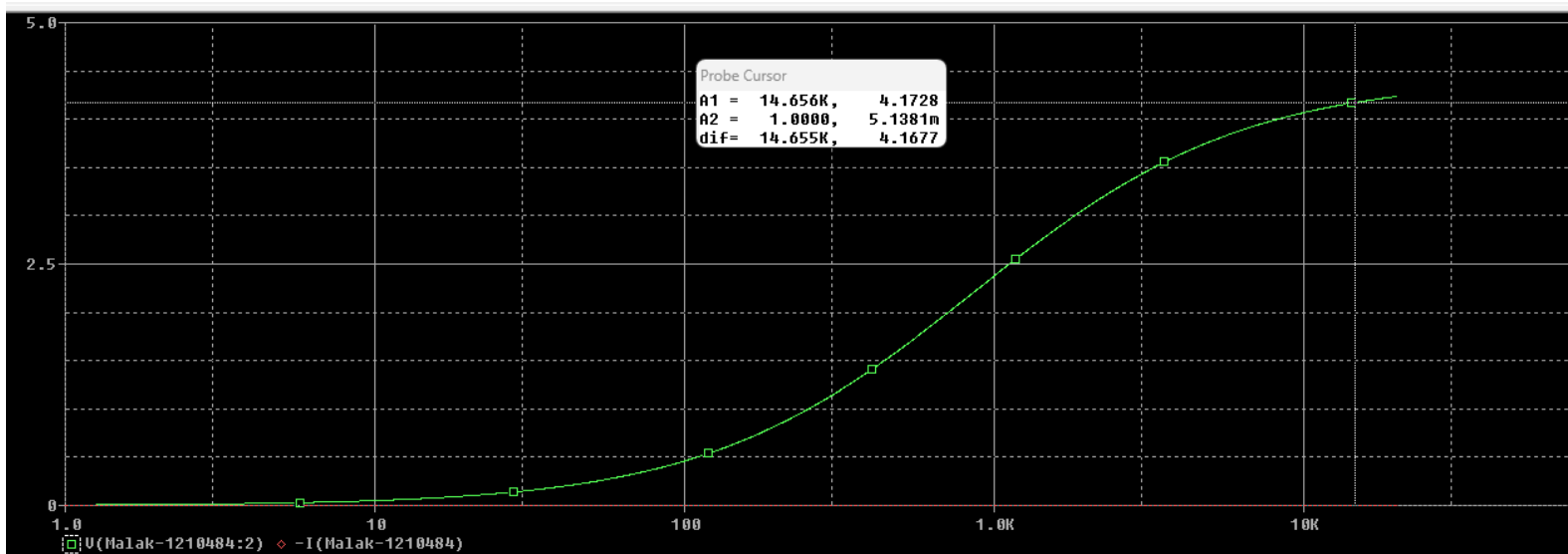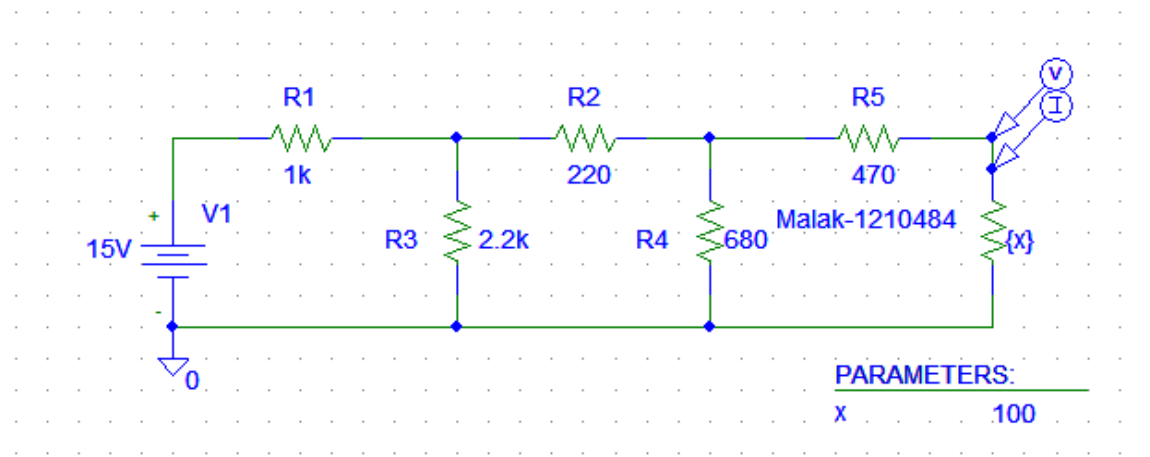1-Make a DC sweep for RL in the circuit of Figure 9.5 to produce a plot of (PLOAD vs. RL) for the range of values of RL shown in Table 9.2, use cursors to find the value of RL that results in maximum power transfer to RL.



2. For the circuit of Figure 9.6:

- Use phasor analysis to calculate VL and IL, assume the input voltage $V_{in} = 8 \angle 0^\circ$.
- Calculate the complex power of the load SL.
- Calculate the parallel capacitance needed to correct the load power factor to unity.

Malak Qasem
12/04/24

→ Exp. 9:

2) Find V_L and I_L when $V_{in} = 8V_{pp} \angle 0^\circ$

$$V_{rms} = \frac{V_{pp}}{2\sqrt{2}} = \frac{8}{2\sqrt{2}} \Rightarrow V_{rms} = 2.82 V$$

→ to calculate $I_L = \frac{V_{rms}}{Z}$; $V_{rms} = V_{in}$

$$\begin{aligned} \text{to find } Z &= R_1 + R_2 + j\omega L \\ &= 680 + 100 + j(2\pi(1000)(15 \times 10^{-3})) \end{aligned}$$

$$\omega Z = 780 + j942 = 1223 \angle 50.4^\circ$$

$$I_L = \frac{V_{in}}{Z} = \frac{2.82 \angle 0^\circ}{1223 \angle 50.4^\circ} \Rightarrow I_L = 2.306 \times 10^{-3} \angle -50.4^\circ \text{ mA}$$

→ to calculate $V_L = I_L Z_L$

$$V_L = I_L Z_L$$

$$= 2.306 \times 10^{-3} \angle -50.4^\circ \times 942 \angle 90^\circ$$

$$\Rightarrow V_L = 2.17 \angle 39.6^\circ$$

• Complex power of the load S_L

$$S_L = V_{in} I_L^* , I_L^* = I_L \angle -\theta_L = 2.306 \times 10^{-3} \angle 50.4^\circ$$

$$= 2.82 \angle 0^\circ \times 2.306 \times 10^{-3} \angle 50.4^\circ$$

$$= 6.5 \times 10^{-3} \angle 50.4^\circ = 0.00415 + j0.005$$

Q_C

• parallel capacitance C

$$Q_C = S_L \sin \theta_s$$

$$= 6.5 \times 10^{-3} (\sin(50.4^\circ)) \Rightarrow Q_L = 0.005$$

Same



$$\Rightarrow Q_C = \frac{V_{rms}^2}{\omega C} \Rightarrow X_C = \frac{V_{rms}^2}{Q} \Rightarrow X_C = \frac{(2.82)^2}{0.005}$$

$$\Rightarrow X_C = 1590.48 \mu F$$

$$X_C = \frac{1}{2(3.14)(1000)C}$$

$$\Rightarrow C = 1.0 \times 10^{-7}$$

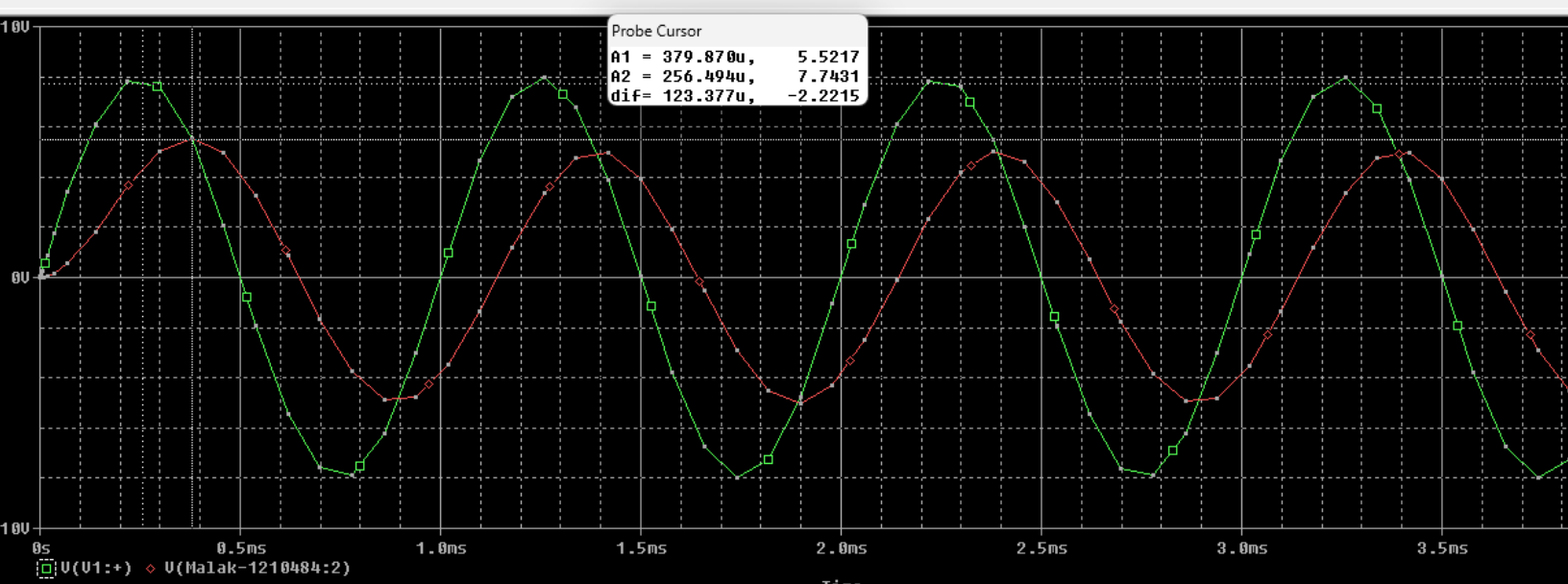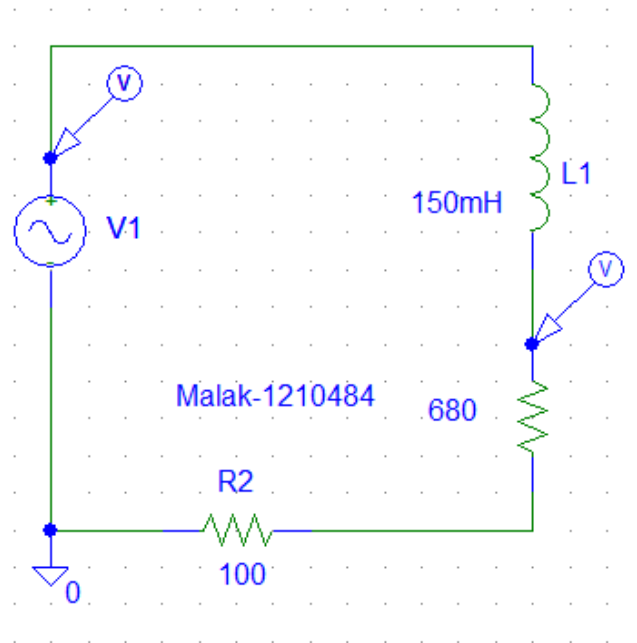- Use PSPICE to do transient analysis of the circuit in Figure 9.6, show $I_L(t)$ and $V_L(t)$ on one graph, you will need different Y-axis, and measure the power factor (from the time difference between the two waveforms).





$$\Delta t = (379.870 - 256.494) \mu s = 123.377 \mu s$$

$$\theta = 360 * f * \Delta t = 360 * 1000 * 123.377 * 10^{-6} = 44.41^\circ$$

$$P.F = \cos \theta = \cos 44.41^\circ = 0.71$$

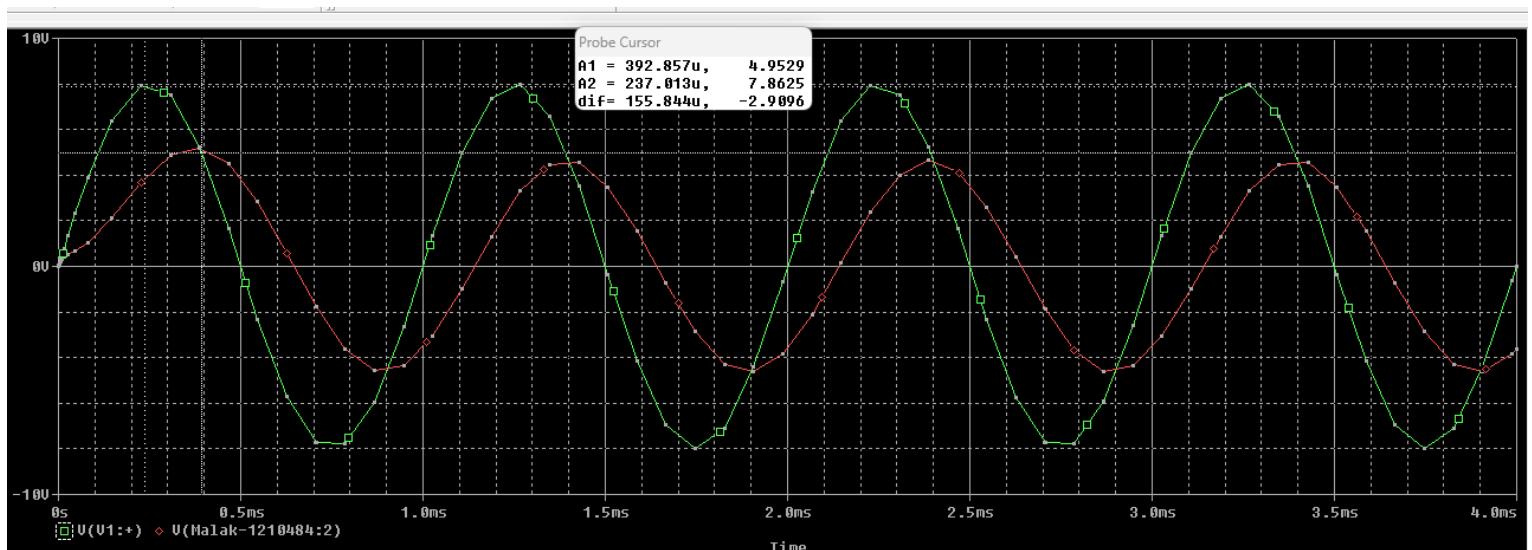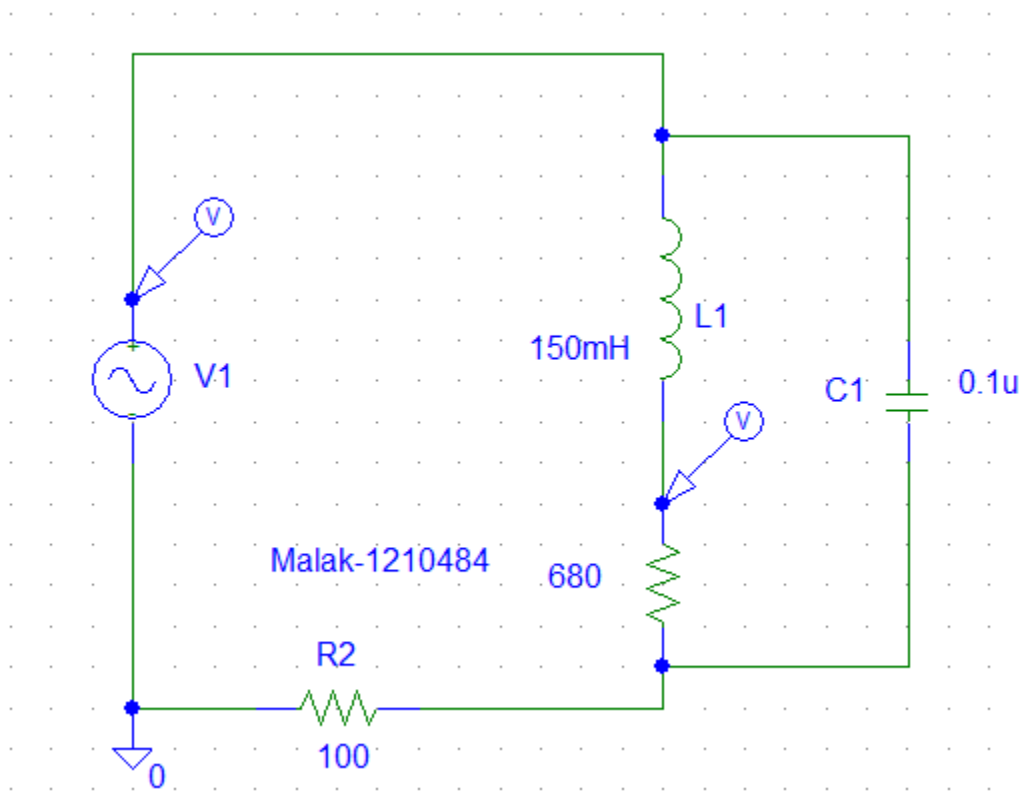- Repeat the previous step with the added capacitor to show power factor improvement.



$$\Delta t = (392.857 - 237.013) \mu s = 155.844 \mu s$$

$$\theta = 360 \times f \times \Delta t = 360 \times 1000 \times 155.844 \times 10^{-6} = 56.10^\circ$$

$$P.F = \cos \theta = \cos 56.10^\circ = 0.56$$

3. For the circuit of Figure 9.8, design a load that is when connected to the output terminals of the circuit will extract maximum average power, then calculate magnitude of P_{Max} .

Malak Qasem
1210484

→ Find the Value of L for the circuit:

$$Z_L = Z_{\text{total}} \Rightarrow Z_{\text{total}} = R - j(X_C) = Z_L$$

$$\sim Z_L = 40\angle 70^\circ + jX_L$$


$R_L = 40\angle 70^\circ$ & $X_L = X_C$

When $X_L = X_C$

$$2\pi f L = \frac{1}{2\pi f C} \Rightarrow L = \frac{1}{(2\pi f)^2 C}$$

$$= \frac{1}{2(3.14)(5 \times 10^3)(0.1 \times 10^{-6})}$$

→ $L = 10.14 \text{ mH}$

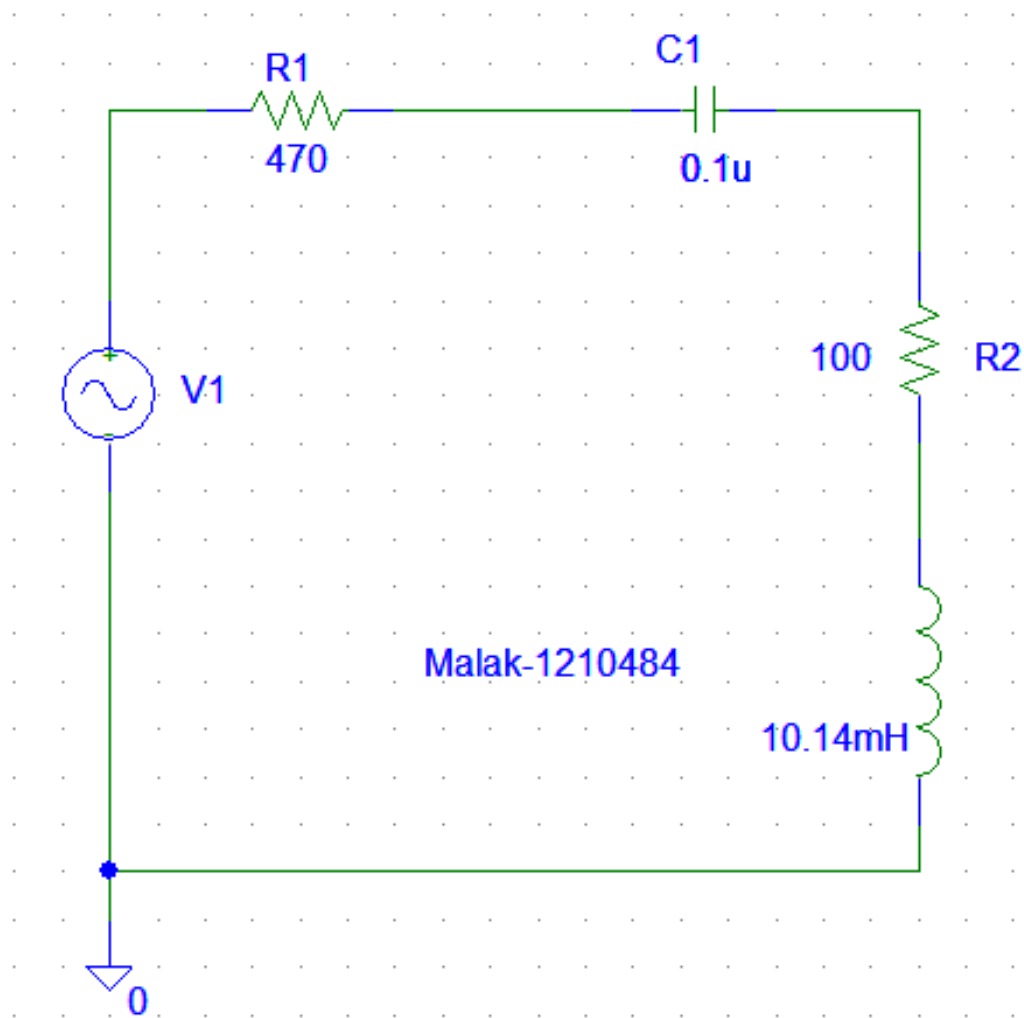

Malak Qasem
1210484

- Find the magnitude of p_{max} :

$$p_{max} = \frac{(V_{th})^2}{4R}$$

$$\rightarrow V_{th} = \frac{V_{PP}}{\sqrt{2}} = \frac{10}{\sqrt{2}} \Rightarrow V_{th} = 7.07 \text{ V}$$

$$\rightarrow R = 470 \Omega$$

$$\therefore p_{max} = \frac{(7.07)^2}{4(470)} \Rightarrow \boxed{p_{max} = 26.6 \text{ mW}}$$