

Chapter 3 :- Gate-Level Minimization

* The complexity of digital logic gates is directly proportional to the boolean expression from which the function is implemented.

$$F_1 = X + \bar{X}Y$$

$$= (X + \bar{X}) \cdot (X + Y)$$

$$= X + Y$$

$$X + \bar{X}Y \equiv X + Y$$

Less complex

we need to find the simplest boolean expression to describe the function

Minimize the function using algebra is a awkward approach

(Lacks of specific rules to predict the next step)

So we need another way for minimization which is

Map Method :- straight forward

- Truth table is unique (before and after minimization)

* Karnaugh map (K-map)

It is a diagram made of squares where each square represented one minterm.

2 variable map :-

2 variables $\rightarrow 2^2$ minterms = 4 minterms

X	Y	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

X \ Y	0	1
0	$\bar{x}\bar{y}$ m_0	$\bar{x}y$ m_1
1	$x\bar{y}$ m_2	xy m_3

Example:- Minimize the following function:-

$$F(x, y) = \bar{x}y + x\bar{y} + xy$$

$m_1 + m_2 + m_3$

using algebra

$$F = \bar{x}y + x(y + \bar{y})$$

$$= x + \bar{x}y$$

$$= (x + \bar{x}) \cdot (x + y)$$

$$= x + y$$


X \ Y	0	1
0	0	1
1	1	1

$x + y$

Example 0 - minimize the following expression

$$F = \bar{x}\bar{y} + \bar{x}y + x\bar{y}$$

$m_0 + m_1 + m_2$

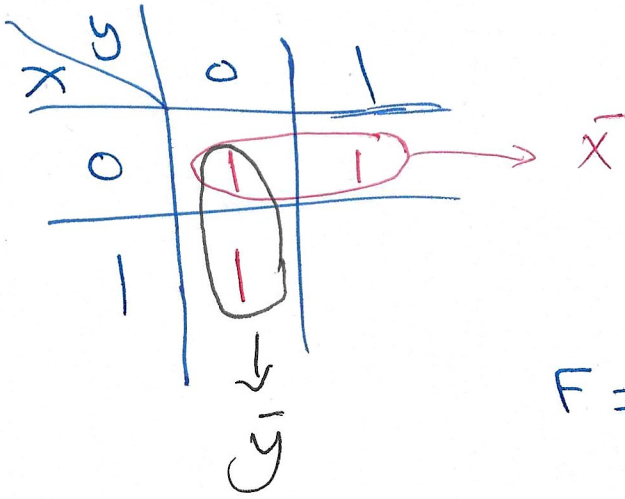


$$F = \bar{x} + \bar{y}$$

$$\begin{aligned} F &= \bar{x}(y + \bar{y}) + x\bar{y} \\ F &= \bar{x} + x\bar{y} \\ &= (\bar{x} + x)(\bar{x} + \bar{y}) \\ &= \bar{x} + \bar{y} \end{aligned}$$

Example 0 - minimize the following expression

$$F(x, y) = \bar{x}y + x\bar{y}$$

$m_1 + m_2$

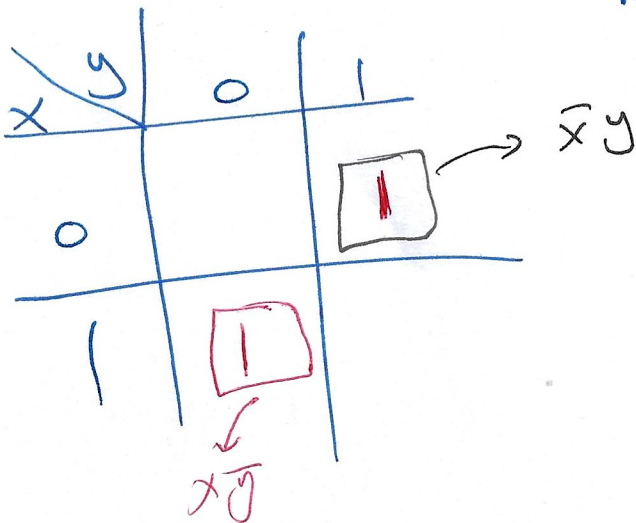

$$F = \bar{x}y + x\bar{y}$$

Example 8 minimize the following expression

$$F = \bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB$$

A \ B	0	1
0	1	1
1	1	1

→ 1

$$F = \bar{A}(B + \bar{B}) + A(\bar{B} + B)$$

$$= \bar{A} + A = 1$$

* Three Variables map

3 variables → $2^3 = 8$ minterms

$F(x, y, z)$


x \ yz	00	01	11	10
0	m ₀	m ₁	m ₃	m ₂
1	m ₄	m ₅	m ₇	m ₆

xy \ z	0	1
00	m ₀	m ₁
01	m ₂	m ₃
11	m ₆	m ₇
10	m ₄	m ₅

Example- Minimize the following function using K-map

$$F(x, y, z) = \sum(0, 1, 3, 7)$$

$$= m_0 + m_1 + m_3 + m_7$$

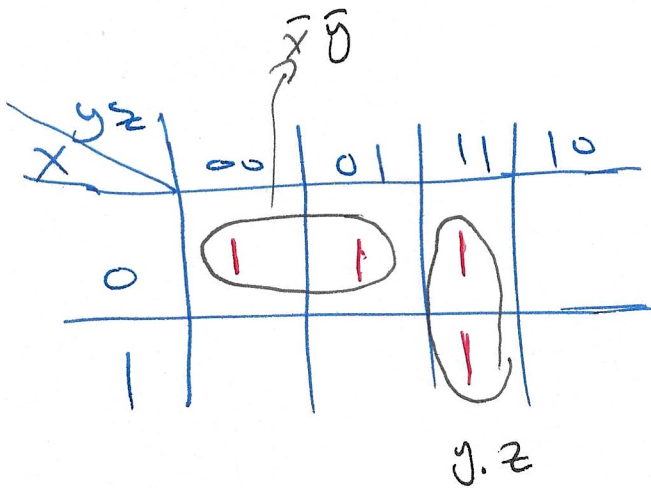


x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F = \bar{x}\bar{y} + yz$$

Example- Minimize the following expression


$$F(x, y, z) = \sum(0, 1, 2, 3)$$

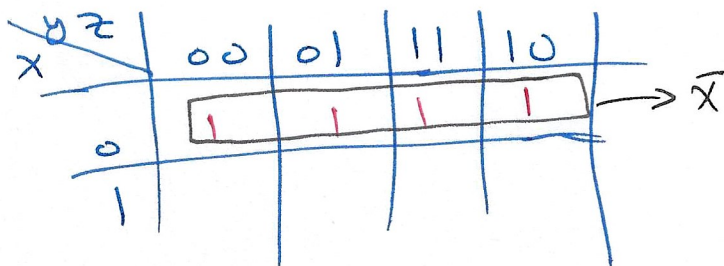

$$F = \bar{x}$$

Example:- Minimize the following function:-


$$F(A,B,C) = \sum(0,1,2,3,4,6)$$

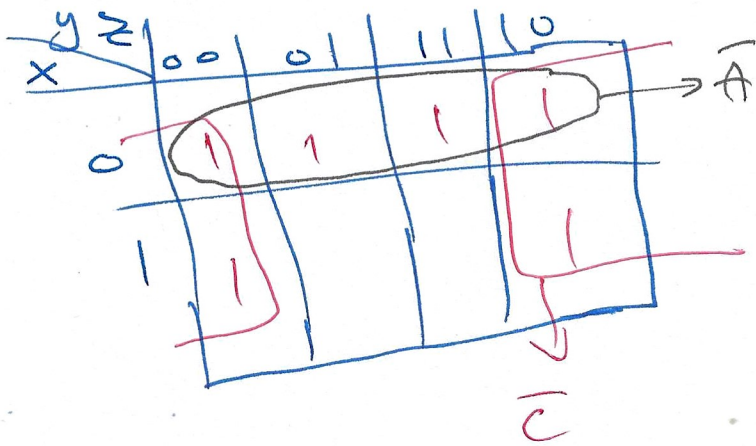

$$F = \bar{A} + \bar{C}$$

Example:- Minimize the following function

$$F(A,B,C) = m_3 + m_5 + m_6 + m_7$$

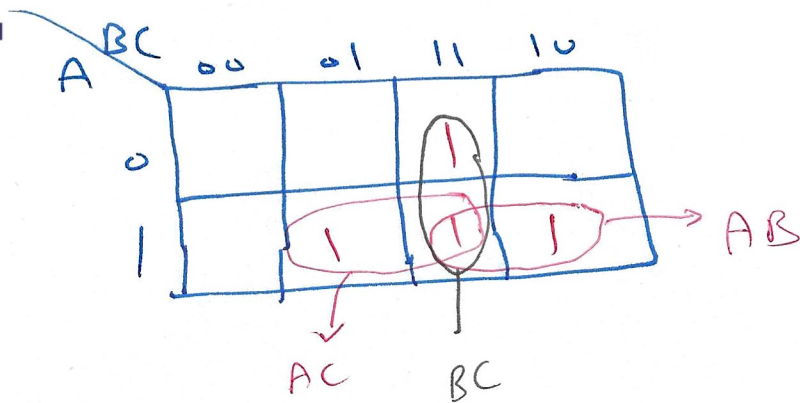

$$\therefore F = AB + AC + BC$$

* Four Variables Maps

$F(x, y, z, w) \Rightarrow 4 \text{ variables} \Rightarrow 2^4 = 16 \text{ minterms} = 16 \text{ squares}$

$x/y \backslash zw$	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

Example 8- $F(A, B, C, D) = \sum(0, 1, 4, 5, 7)$

$AB \backslash CD$	00	01	11	10
00	1	1		
01	1	1	1	1
11				
10				

Groupings: $\bar{A}\bar{C}$ (red box), $\bar{A}BD$ (blue oval)

$$F = \bar{A}\bar{C} + \bar{A}BD$$

Example 9- Minimize using K-map $F(A, B, C, D) = \sum(0, 2, 4, 6, 8, 10)$

$AB \backslash CD$	00	01	11	10
00	1			1
01	1			1
11				
10	1			1

Groupings: $\bar{A}\bar{D}$ (red box), $\bar{B}\bar{D}$ (blue box)

$$F = \bar{A}\bar{D} + \bar{B}\bar{D}$$

Example - $F(A, B, C, D) = \sum(0, 1, 2, 3, 5, 7, 13, 15, 9, 11)$

CD		00	01	11	10
AB	00	1	1	1	1
	01		1	1	
	11		1	1	
	10		1	1	

Diagram showing Karnaugh map for $F(A, B, C, D) = \sum(0, 1, 2, 3, 5, 7, 13, 15, 9, 11)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). A blue loop covers the top row (AB=00) and is labeled $\bar{A}\bar{B}$. A red loop covers the middle two rows (AB=01, 11) and the last two rows (AB=11, 10) for columns CD=01 and CD=11, and is labeled D .

$$F = \bar{A}\bar{B} + D$$

Example - $F(A, B, C, D) = \sum(0, 2, 4, 6, 8, 10, 12, 14)$

CD		00	01	11	10
AB	00	1			1
	01	1			
	11	1			
	10	1			1

Diagram showing Karnaugh map for $F(A, B, C, D) = \sum(0, 2, 4, 6, 8, 10, 12, 14)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). Two red loops are shown: one covering the first column (CD=00) and one covering the last column (CD=10). Both loops are labeled \bar{D} .

$$F = \bar{D}$$

Example - $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$


CD		00	01	11	10
AB	00	1			1
	01		1	1	
	11		1	1	
	10	1			1

Diagram showing Karnaugh map for $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). A red loop covers the middle two rows (AB=01, 11) for columns CD=01 and CD=11, labeled BD . Two blue loops cover the corners: (AB=00, CD=00) and (AB=10, CD=10) labeled $\bar{B}\bar{D}$, and (AB=00, CD=10) and (AB=10, CD=00) labeled $B\bar{D}$.

$$F = BD + \bar{B}\bar{D}$$


$$= \overline{(B \oplus D)} \quad \text{XNOR}$$

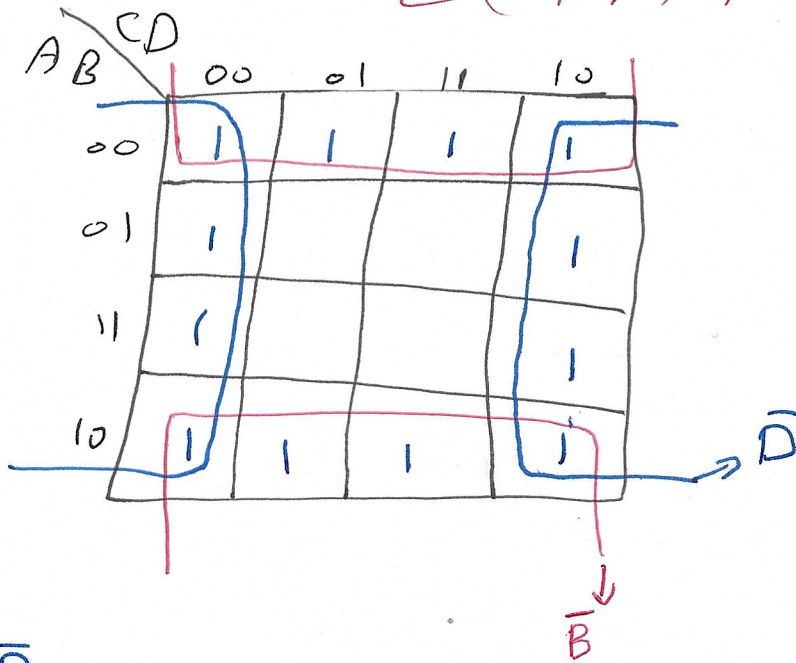Example 2- $F(A, B, C, D) = \sum (0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$



$$F = \bar{B} + \bar{D}$$

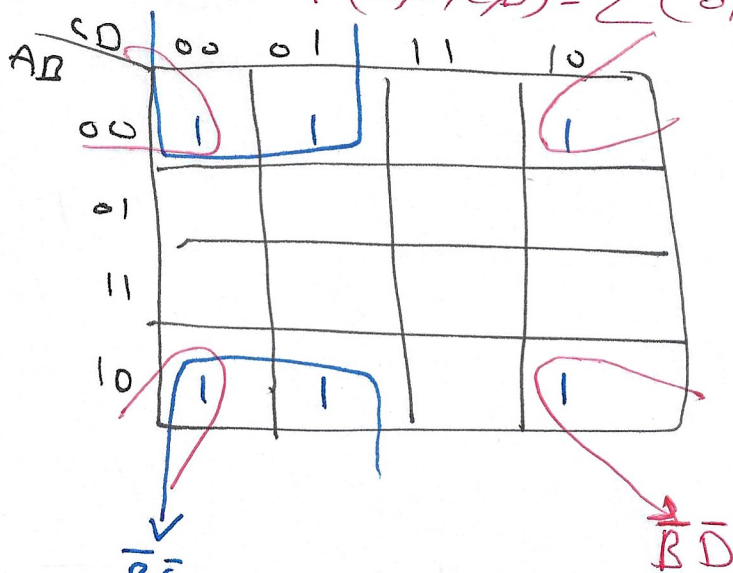Example 2- $F(A, B, C, D) = \sum (0, 1, 2, 8, 9, 10)$



$$F = \bar{B}\bar{C} + \bar{B}\bar{D}$$

* Five Variables Map

$F(A, B, C, D, E) \Rightarrow 5 \text{ Variable} \Rightarrow 2^5 = 32 \text{ minterms}$

$A = 0$

DE \ BC	00	01	11	10
00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

$A = 1$

DE \ BC	00	01	11	10
00	m ₁₆	m ₁₇	m ₁₉	m ₁₈
01	m ₂₀	m ₂₁	m ₂₃	m ₂₂
11	m ₂₈	m ₂₉	m ₃₁	m ₃₀
10	m ₂₄	m ₂₅	m ₂₇	m ₂₆


please note that m₀ is adjacent to m₁₆
 m₁ is adjacent to m₁₇
 and so on

A	B	C	D	E	F
0	0	0	0	0	m ₀
0	0	0	0	1	m ₁
0	0	0	1	0	m ₂
0	0	0	1	1	m ₃
0	0	1	0	0	m ₄
0	0	1	0	1	m ₅
0	0	1	1	0	m ₆
0	0	1	1	1	m ₇
0	1	0	0	0	m ₈
0	1	0	0	1	m ₉
0	1	0	1	0	m ₁₀
0	1	0	1	1	m ₁₁
0	1	1	0	0	m ₁₂
0	1	1	0	1	m ₁₃
0	1	1	1	0	m ₁₄
0	1	1	1	1	m ₁₅
1	0	0	0	0	m ₁₆
1	0	0	0	1	m ₁₇
1	0	0	1	0	m ₁₈
1	0	0	1	1	m ₁₉
1	0	1	0	0	m ₂₀
1	0	1	0	1	m ₂₁
1	0	1	1	0	m ₂₂
1	0	1	1	1	m ₂₃
1	1	0	0	0	m ₂₄
1	1	0	0	1	m ₂₅
1	1	0	1	0	m ₂₆
1	1	0	1	1	m ₂₇
1	1	1	0	0	m ₂₈
1	1	1	0	1	m ₂₉
1	1	1	1	0	m ₃₀
1	1	1	1	1	m ₃₁


$A = 1$

Example 8 - Minimize $F(A, B, C, D, E) = \sum(0, 4, 6, 9, 13, 21, 23, 25, 29, 31)$

$A = 0$

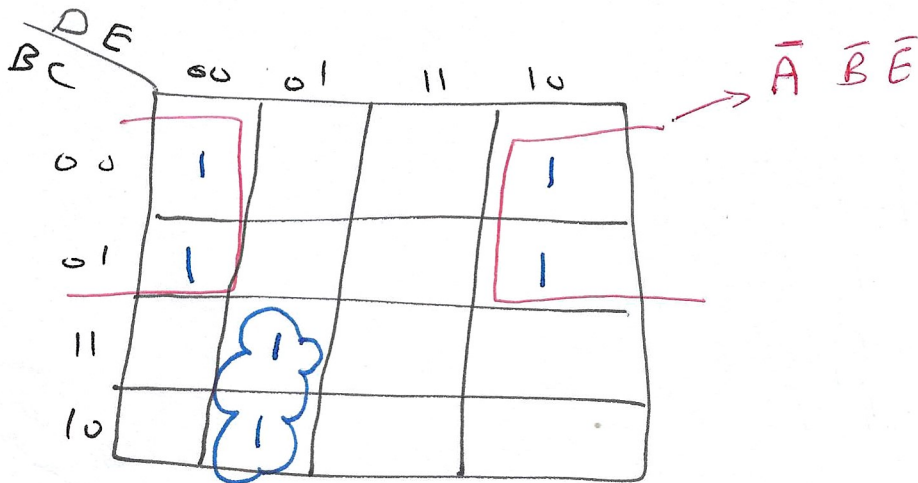

$A = 1$

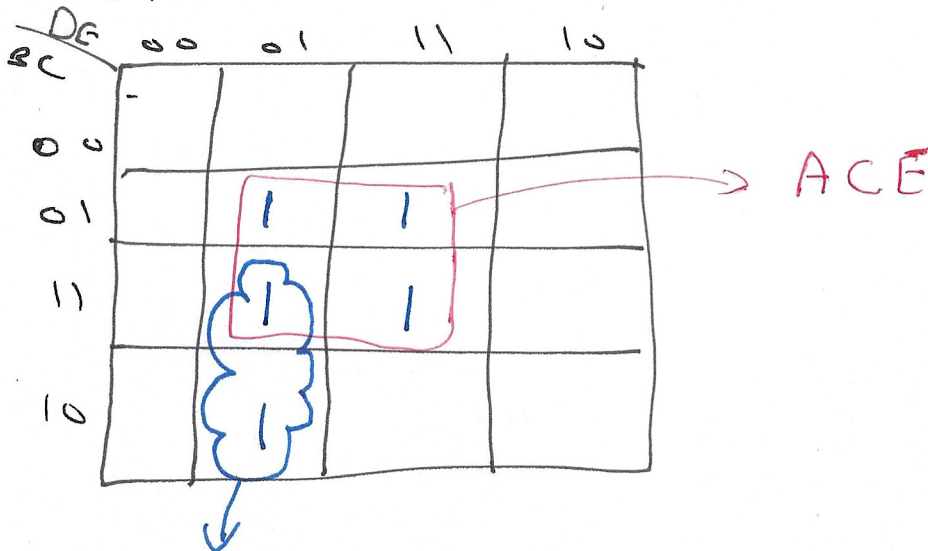

$$F = B \bar{D} E + \bar{A} \bar{B} \bar{E} + A C \bar{E}$$

Example - $F(A, B, C, D, E) = \sum(0, 1, 8, 9, 16, 17, 22, 23, 24, 25)$

$A = 0$

BC	DE 00	DE 01	DE 11	DE 10
00	1	1		
01				
11				
10	1	1		

$A = 1$


BC	DE 00	DE 01	DE 11	DE 10
00	1	1		
01			1	1
11				
10	1	1		

$\bar{C}\bar{D} +$

$$F = \bar{C}\bar{D} + A\bar{B}CD$$


* Product of Maxterms

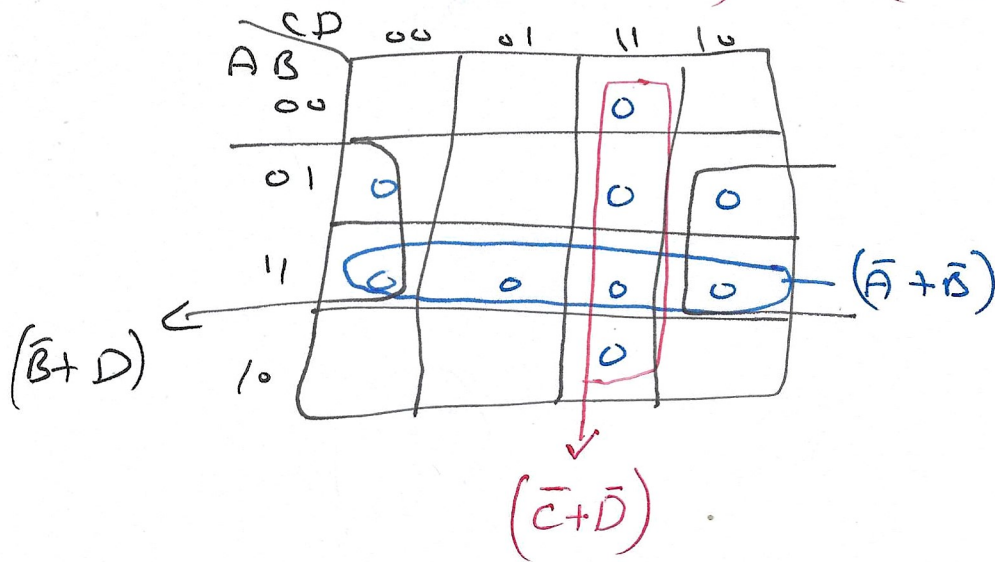Example:- Simplify $F(A, B, C, D) = \prod (3, 4, 6, 7, 11, 12, 13, 14, 15)$




$$F = (A + B) \cdot (B + D) \cdot (C + D)$$

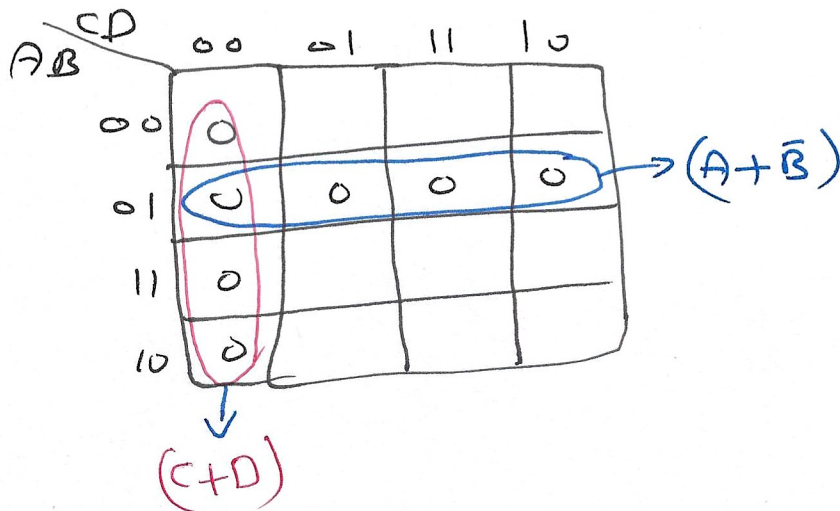Example:- $F(A, B, C, D) = \prod (0, 4, 5, 6, 7, 8, 12)$



$$F = (C + D) \cdot (A + B)$$

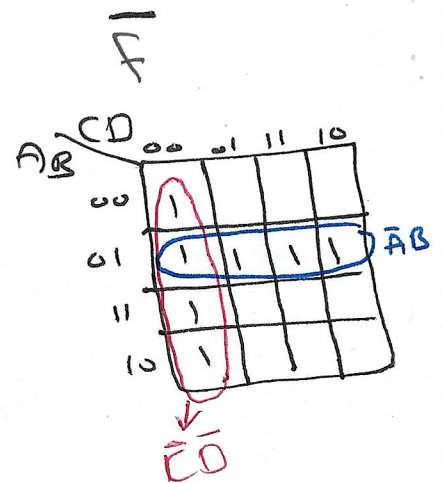

$$\bar{F} = \bar{C}\bar{D} + \bar{A}B$$

$$F = \overline{\bar{F}} = \overline{(\bar{C}\bar{D} + \bar{A}B)} \\ = (C + D) \cdot (A + B)$$

* Don't Care Conditions


A Function table may contain entries for which

- 1- The input values of the variables will never occur
- 2- The output value of the function is never used


Example 8 Consider a function (F) defined over BCD inputs where the function output is (0) if the BCD input is (0-4), and the function output is (1) if the BCD input is (5-9). The function output is (X) if the input is (10-15)

$$F = \sum_m(5, 6, 7, 8, 9) + \sum_d(10, 11, 12, 13, 14, 15)$$

min terms
don't care

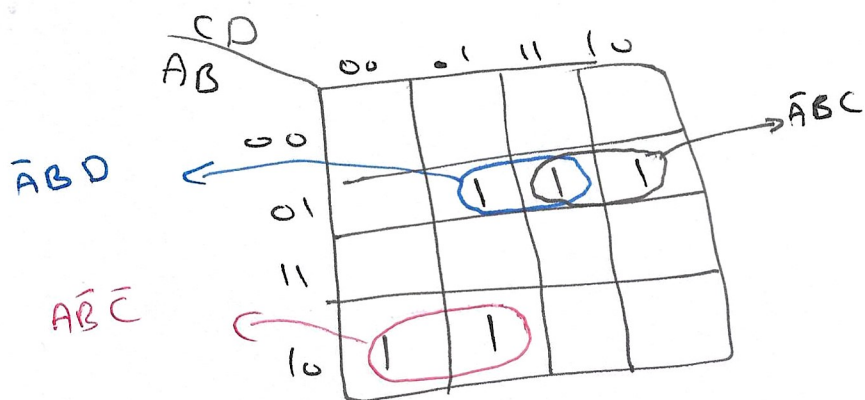


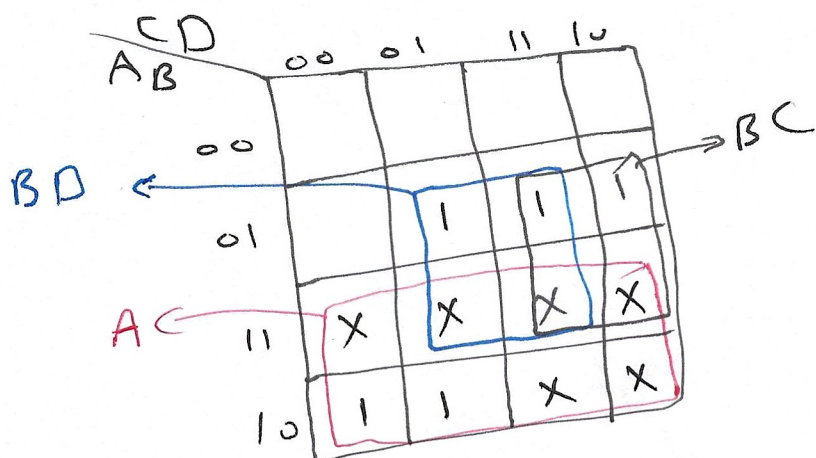
without using don't care $F = \bar{A}BD + A\bar{B}\bar{C} + \bar{A}BC$



with don't care $F = A + BD + BC$

A	B	C	D	
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

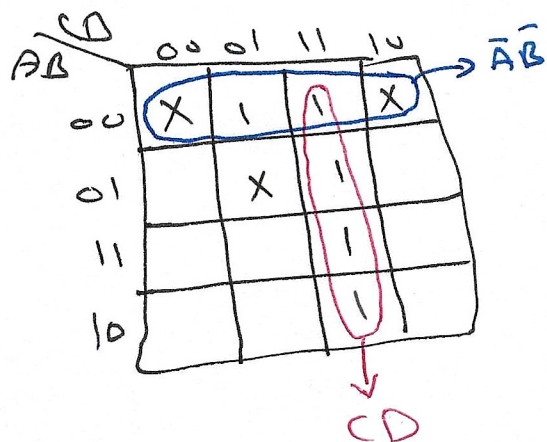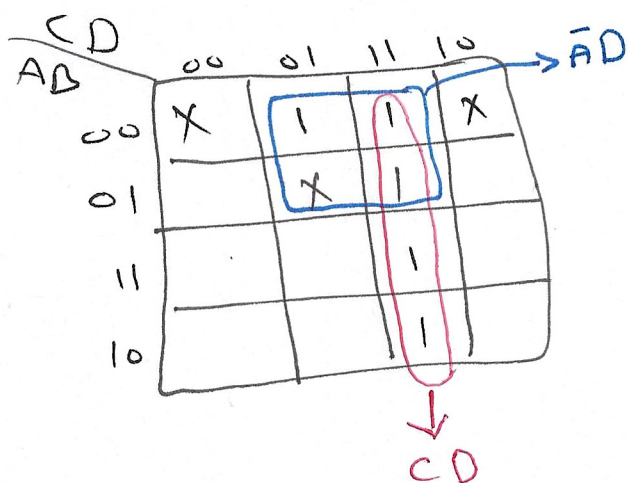Example:- Simplify $F = \sum_m(1,3,7,11,15) + \sum_d(0,2,5)$



$$F = \bar{A}D + CD$$

or

$$F = \bar{A}\bar{B} + CD$$


not all don't cares need to be covered

Example:- Simplify $F = \sum_m(1,3,7,11,15) + \sum_d(0,2,5)$

obtain a product of sums minimal expression

$$F(\text{pos}) = \bar{\bar{F}}(\text{SOM})$$
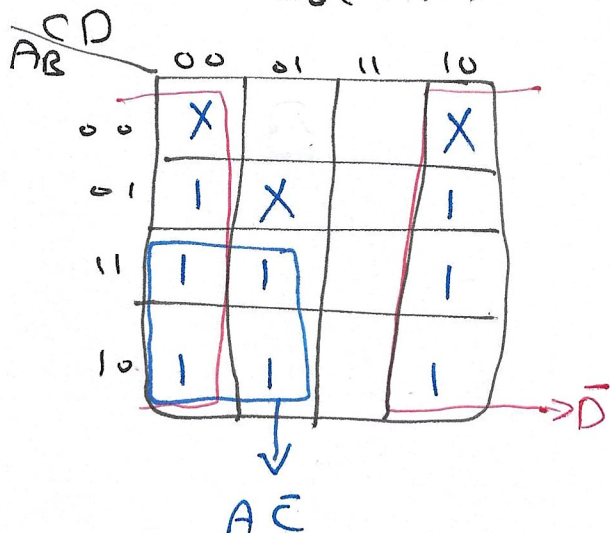
$$\bar{F}(\text{SOM}) = \sum_m(4,6,8,9,10,12,13,14) + \sum_d(0,2,5)$$




$$\bar{F} = A\bar{C} + \bar{D}$$

$$F = \bar{\bar{F}} = \overline{(A\bar{C} + \bar{D})}$$


STUDENTS HUB
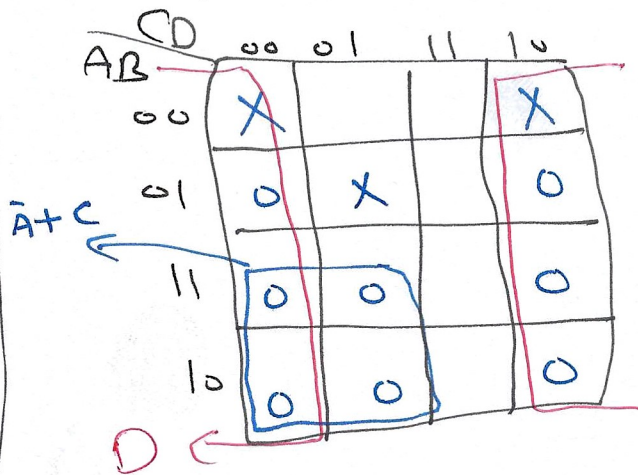
$$F = \prod(4,6,8,9,10,12,13,14) + \sum_d(0,2,5)$$



$$F = D \cdot (\bar{A} + C)$$

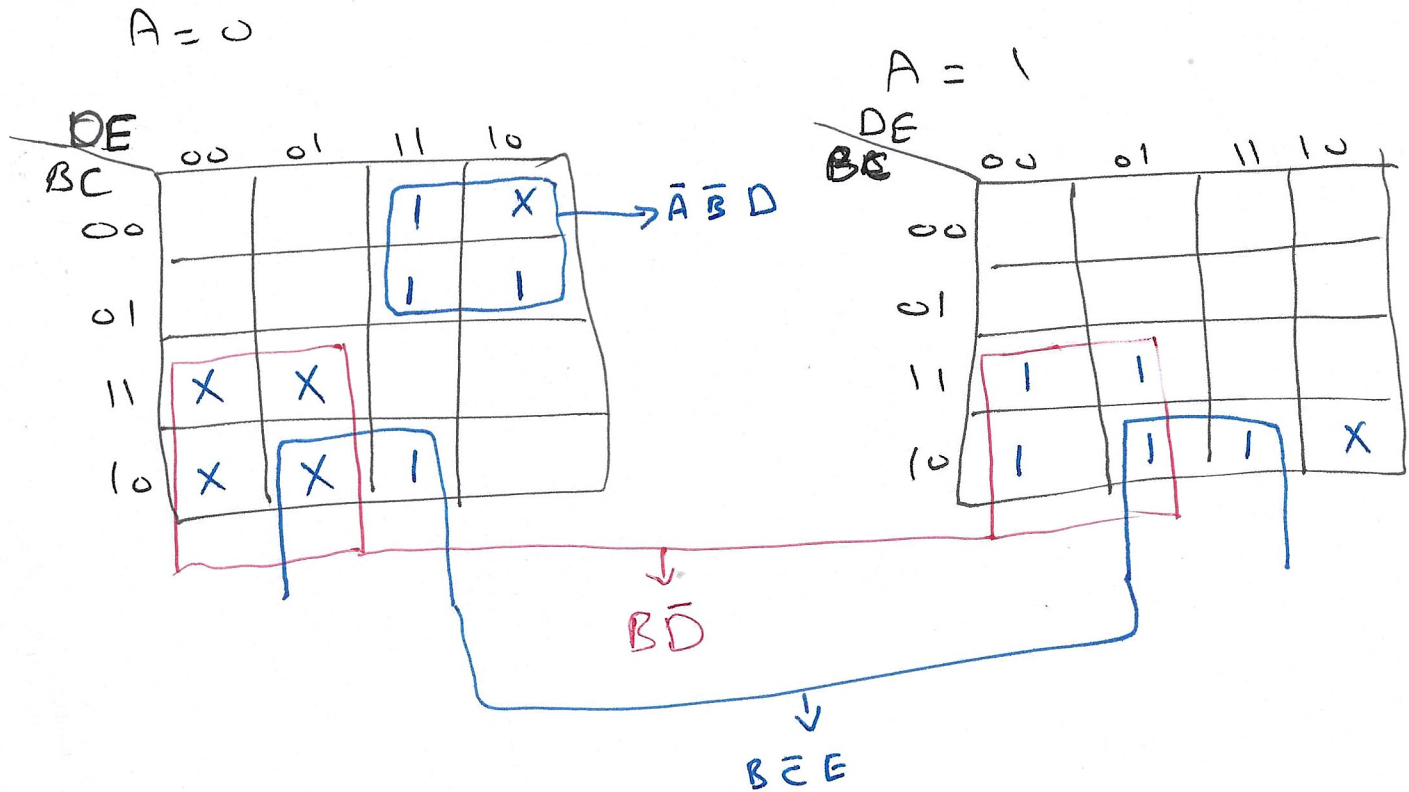Example:- $F(A, B, C, D, E) = \sum_m(3, 6, 7, 11, 24, 25, 27, 28, 29) + \sum_d(2, 8, 9, 12, 13, 26)$




$$F = \bar{A} \bar{B} D + B \bar{C} E + B \bar{D}$$

* Prime Implicant and Essential Prime Implicant

Prime Implicant:- a product term obtained by combining the maximum number of adjacent squares in the k-map (PI)


Essential prime Implicant:- is a prime implicant that covers at least one minterm not covered by the other prime implicants (EPI)

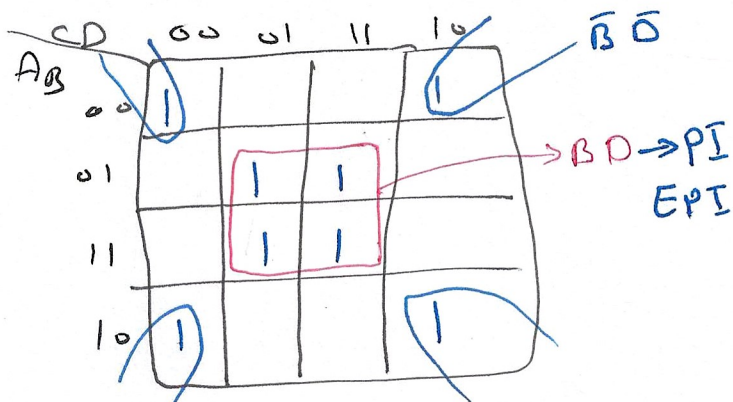Example:- $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$



In this example we have two prime implicants and they are both essential

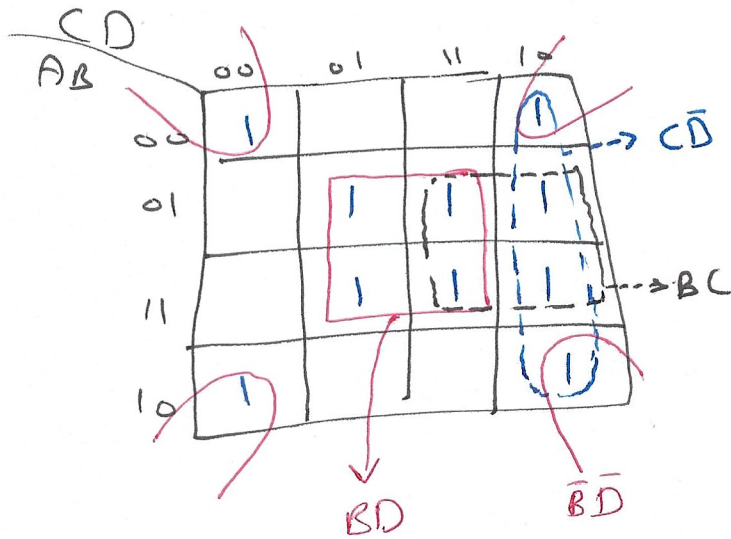Example:- $F(A,B,C,D) = \sum(0,2,5,6,7,8,10,13,14,15)$




$$F = BD + \bar{B}\bar{D} + C\bar{D} \leftarrow \text{PI}$$

$$F = BD + \bar{B}\bar{D} + BC$$

\uparrow \uparrow \uparrow
 EPI EPI PI

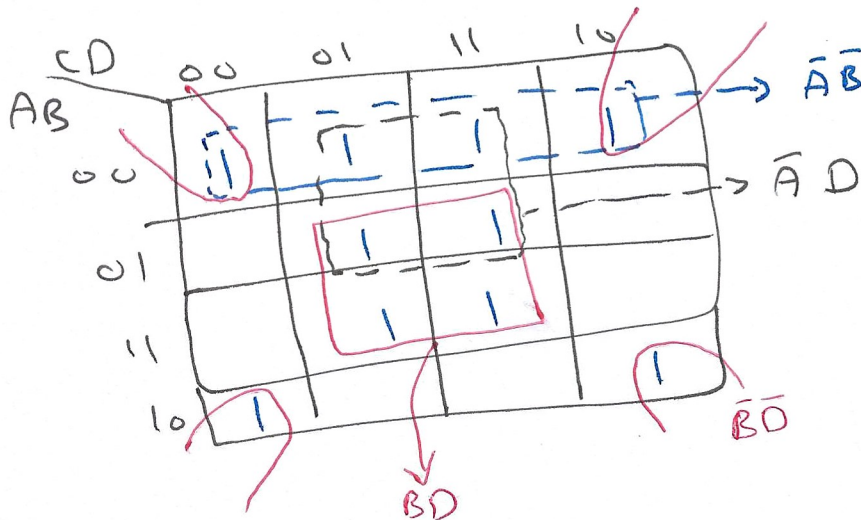Example:- $F(A,B,C,D) = \sum(0,1,2,3,5,7,8,10,13,15)$




$$F = BD + \bar{B}\bar{D} + \bar{A}\bar{B} \leftarrow \text{PI}$$

$$F = BD + \bar{B}\bar{D} + \bar{A}D \leftarrow \text{PI}$$

$\underbrace{\hspace{2cm}}$
 EPI

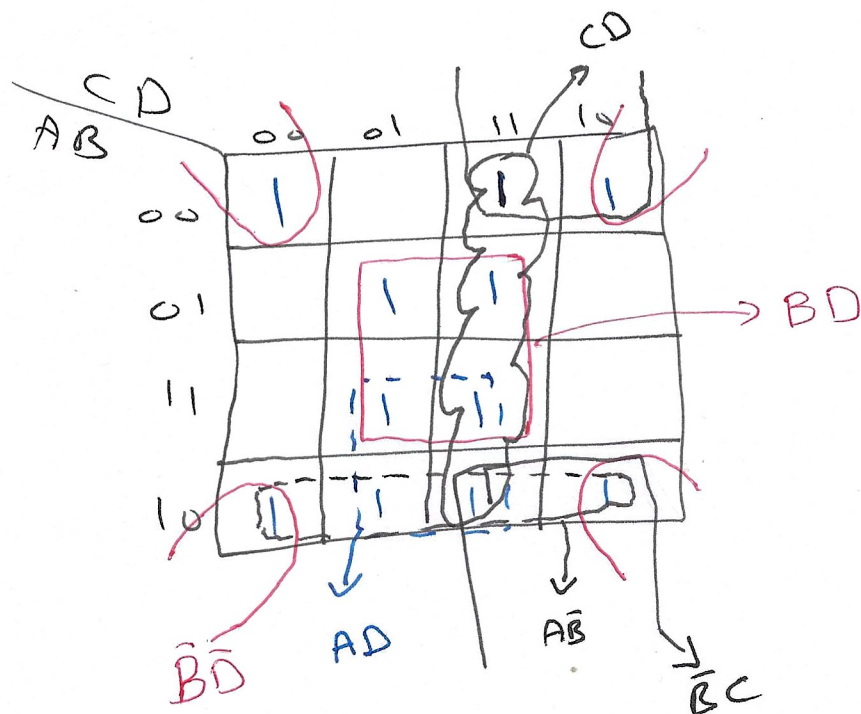Example 8: $F(A, B, C, D) = \Sigma(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$



So we have 6 prime Implicants

two are essential


$$F = BD + \bar{B}\bar{D} + A\bar{B} + CD$$

$$F = BD + \bar{B}\bar{D} + A\bar{B} + \bar{B}C$$


$$F = BD + \bar{B}\bar{D} + AD + \bar{B}C$$

$$F = BD + \bar{B}\bar{D} + AD + CD$$

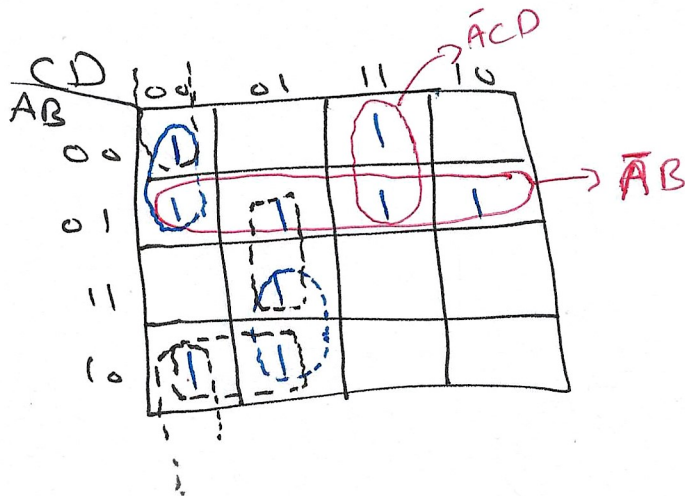Example 8 $F(A,B,C,D) = \Sigma(0,3,4,5,6,7,8,9,13)$



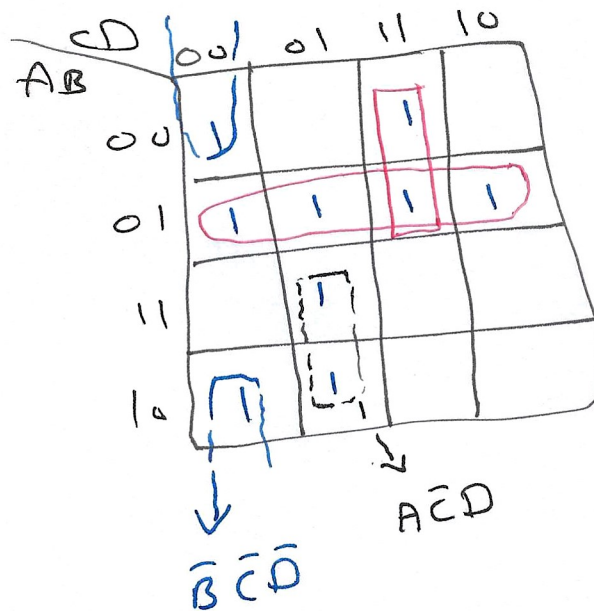So we have 7 prime implicants
two are Essential



$$F = \bar{A}B + \bar{A}CD + A\bar{C}D + \bar{B}\bar{C}\bar{D}$$

NAND / NOR Implementation

NAND and NOR gates are said to be universal gates because any logic circuit can be implemented with it.

Digital Circuits are frequently constructed with NAND or NOR gates rather than with AND and OR gates for the following reasons:-

① use fewer transistors

- ↳ Less cost
- ↳ Less delay
- ↳ Less space


② NAND and NOR are easier to fabricate.

* NAND gate


$$\begin{matrix} A \\ B \end{matrix} \Rightarrow \text{D} \text{ --- } F = (A \cdot B)' = \bar{A} + \bar{B} \quad \equiv \quad \begin{matrix} A \\ B \end{matrix} \Rightarrow \text{NAND} \text{ --- } F = \bar{A} + \bar{B}$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


① NAND gate as inverter

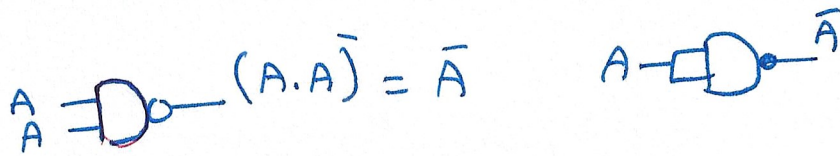


② NAND gate as AND

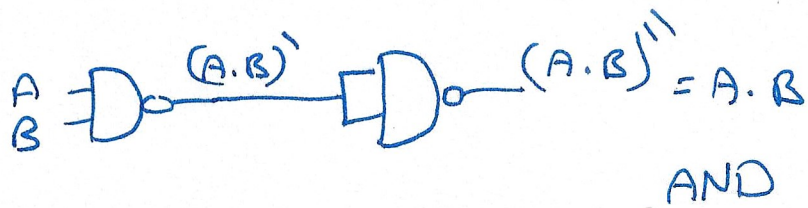

③ NAND gate as OR

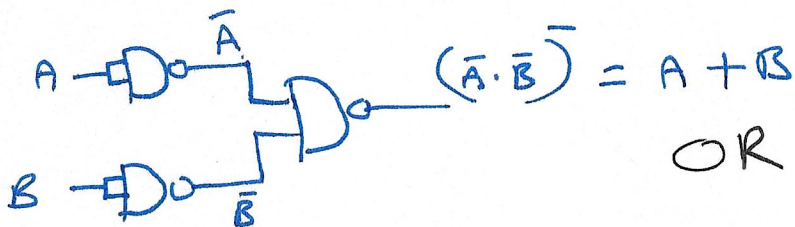


* NOR gate

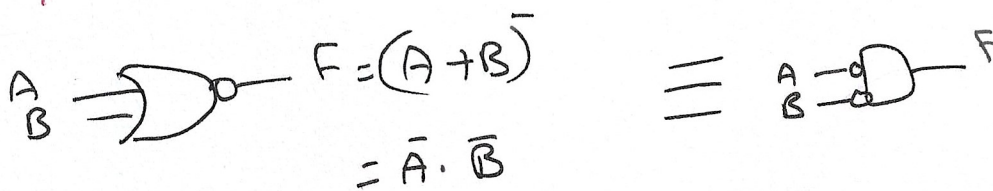


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


① NOR as inverter

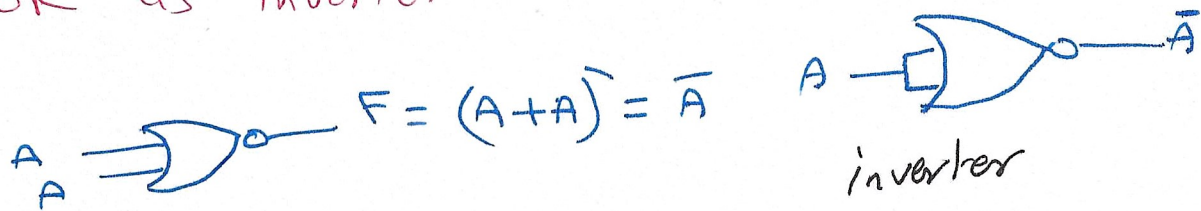

② NOR as OR

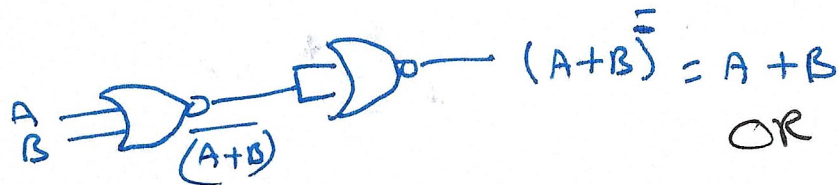



③ NOR as AND

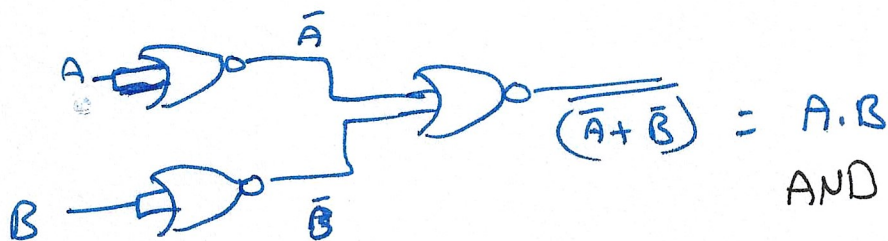

*AND-OR Implementation

$$F = A.B + B.C$$


(SOP)

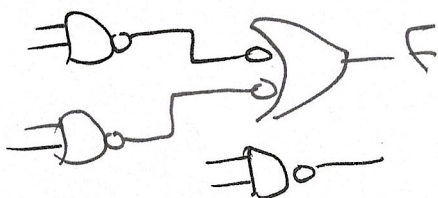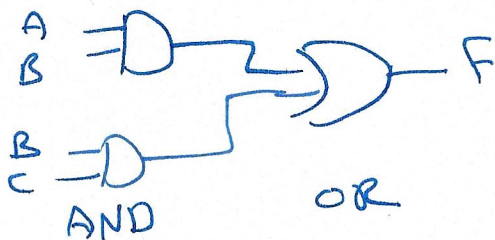



Example 8- Implement the following Function with NAND gates

$$F(A, B, C) = \sum (0, 1, 3, 7)$$




m₀ m₁ m₃ m₇

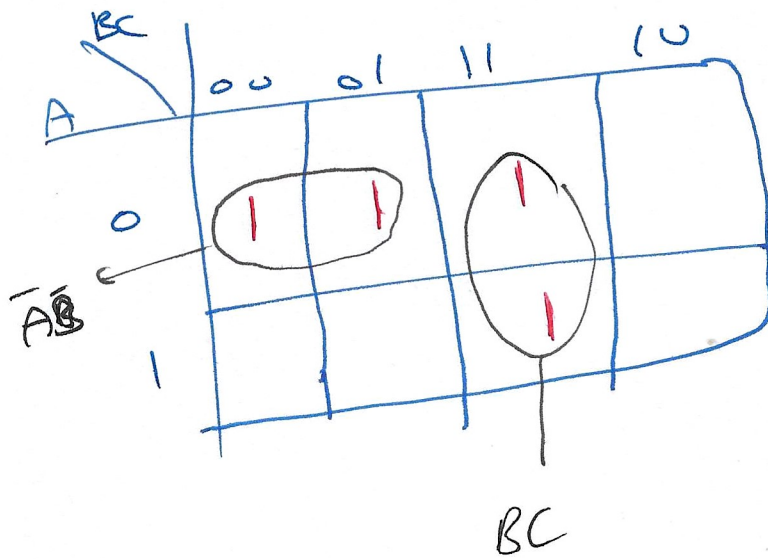

$$F = \bar{A}\bar{B} + BC$$

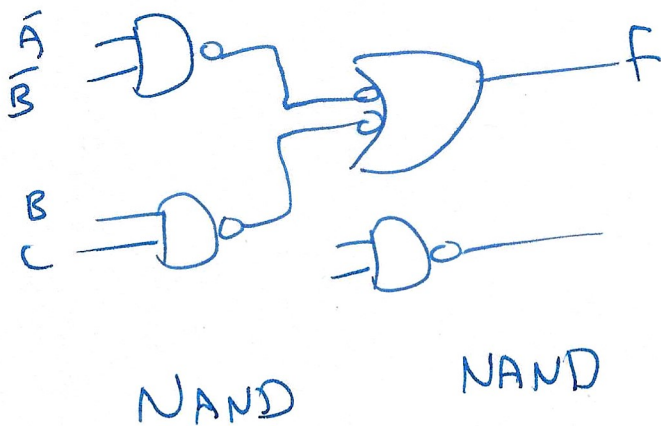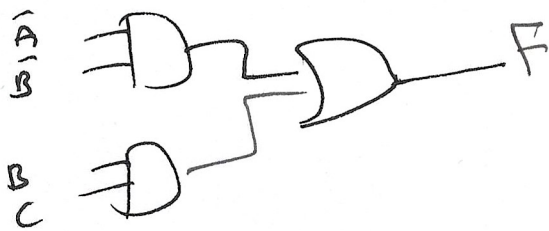

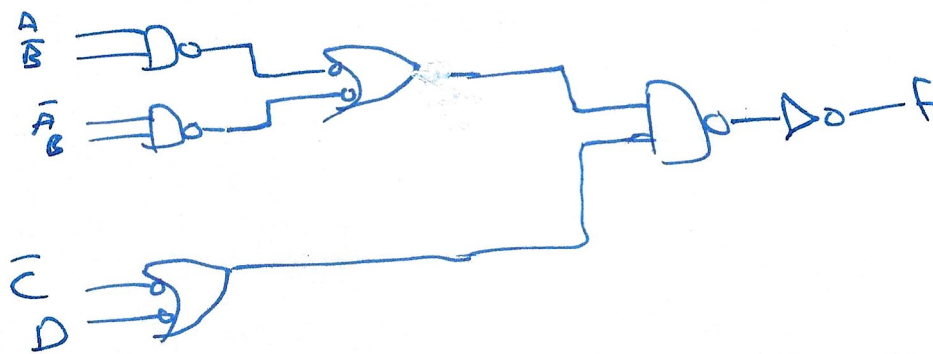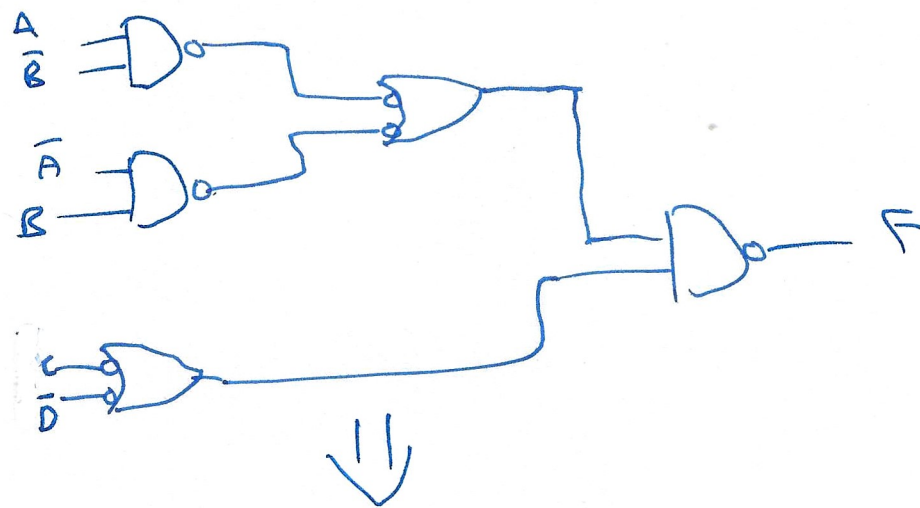
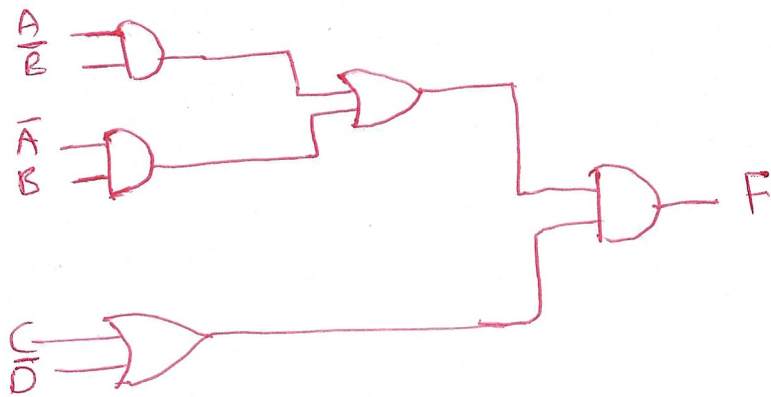
Example 2: $F = (A\bar{B} + \bar{A}B)(C + \bar{D})$



* OR-AND Implication


$$F = (A+B) \cdot (\bar{B}+C)$$

Product of Sum

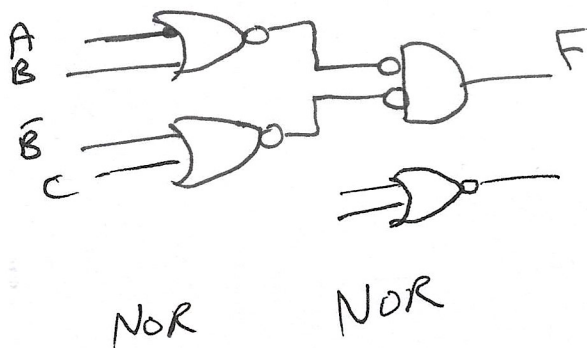
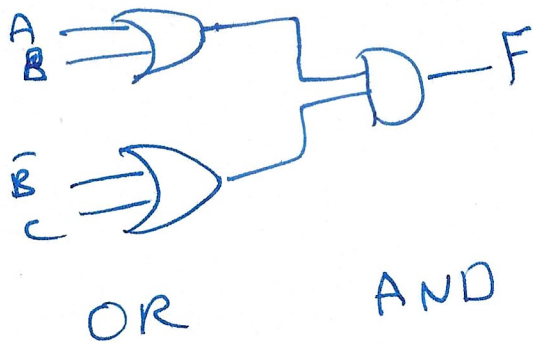


Example - Imply the following function using NOR-NOR gates

$$F(A, B, C) = \prod (0, 1, 3, 7)$$

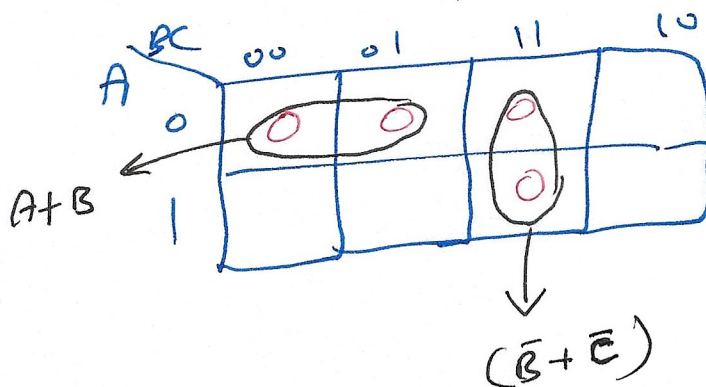

$$F = (A+B) \cdot (\bar{B}+C)$$

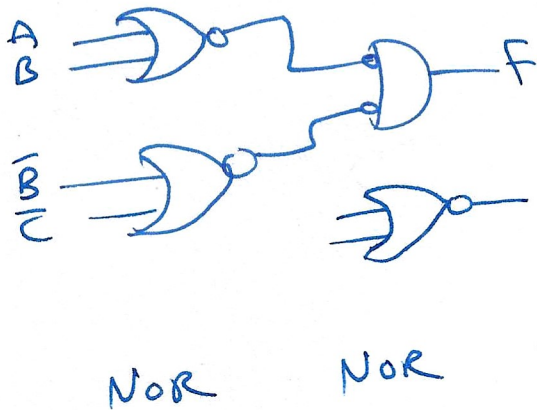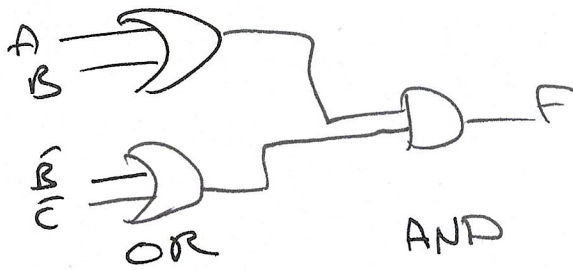

Example- $F(A, B, C, D) = \Sigma(2, 4, 6, 10, 12)$

$d(A, B, C, D) = \Sigma(0, 8, 9, 13)$



Implement the function using NOR gates

		CD			
		00	01	11	10
AB	00	X	0	0	1
	01	1	0	0	1
	11	1	X	0	0
	10	X	X	0	1

\bar{D}


$(\bar{A} + \bar{B} + \bar{C})$

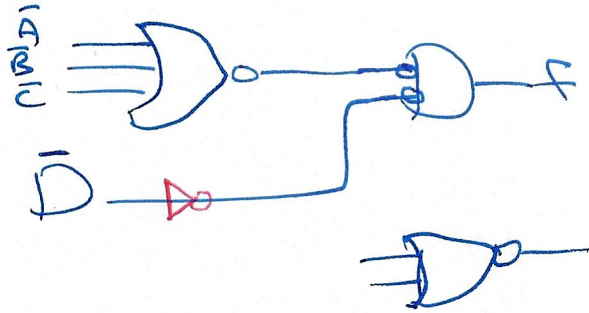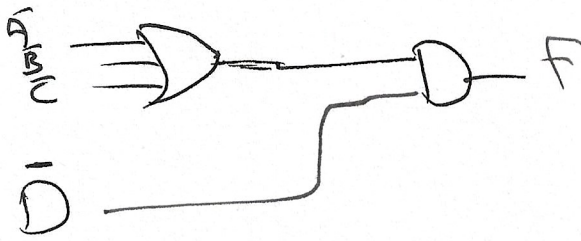$F = \bar{D} \cdot (\bar{A} + \bar{B} + \bar{C})$



* Parity Generator

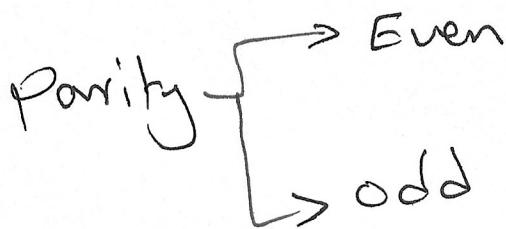Parity: Extra bit added to the message to check
If the received message is correct (single error)




Example: Design even parity generator and
Checker for 3-bit codes


Odd parity \rightarrow even Function

even parity \rightarrow odd Function

X	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

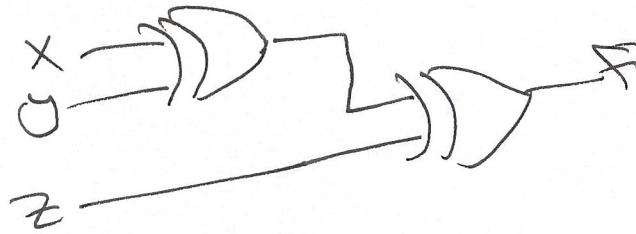

x	y	z	p	check
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0

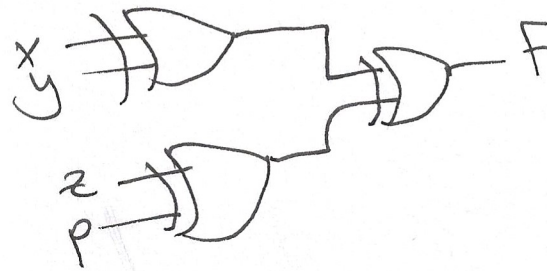

Example 2- $F = (A\bar{B} + \bar{A}B)E(C+\bar{D})$

