

# Synchronous Sequential Logic


# Combinational versus Sequential

## ❖ Two classes of digital circuits

- ✧ Combinational Circuits
- ✧ Sequential Circuits
 
## ❖ Combinational Circuit

- ✧  $\text{Outputs} = F(\text{Inputs})$
- ✧ Function of Inputs only
- ✧ NO internal memory



## ❖ Sequential Circuit

- ✧ Outputs is a function of Inputs and internal Memory
- ✧ There is an internal memory that stores the state of the circuit
- ✧ Time is very important: memory changes with time

# Introduction to Sequential Circuits

A Sequential circuit consists of:

## 1. Memory elements:

- ✧ **Latches or Flip-Flops**
- ✧ Store the **Present State**


## 2. Combinational Logic

- ✧ Computes the **Outputs** of the circuit

Outputs depend on Inputs and Current State

- ✧ Computes the **Next State** of the circuit

 Next State also depends on the Inputs and the Present State



# Two Types of Sequential Circuits


## 1. **Synchronous** Sequential Circuit

- ✧ Uses a clock signal as an additional input
- ✧ Changes in the memory elements are controlled by the clock
- ✧ Changes happen at discrete instances of time

## 2. **Asynchronous** Sequential Circuit


- ✧ No clock signal
  - ✧ Changes in the memory elements can happen at any instance of time
- ❖ Our focus will be on Synchronous Sequential Circuits
- ✧ Easier to design and analyze than asynchronous sequential circuits

# Synchronous Sequential Circuits

 


- ❖ Synchronous sequential circuits use a **clock signal**
- ❖ The clock signal is an input to the memory elements
- ❖ The clock determines **when** the memory should be updated
- ❖ The **present state** = output value of memory (stored)
- ❖ The **next state** = input value to memory (not stored yet)

# The Clock

 

- ❖ Clock is a periodic signal = Train of pulses (1's and 0's)
- ❖ The same clock cycle repeats indefinitely over time
- ❖ **Positive Pulse**: when the **level** of the clock is **1**
- ❖ **Negative Pulse**: when the **level** of the clock is **0**
- ❖ **Rising Edge**: when the clock goes **from 0 to 1**
- ❖ **Falling Edge**: when the clock goes **from 1 down to 0**

# Clock Cycle versus Clock Frequency

 

❖ Clock cycle (or period) is a time duration

✧ Measured in seconds, milli-, micro-, nano-, or pico-seconds

✧  $1 \text{ ms} = 10^{-3} \text{ sec}$ ,  $1 \mu\text{s} = 10^{-6} \text{ sec}$ ,  $1 \text{ ns} = 10^{-9} \text{ sec}$ ,  $1 \text{ ps} = 10^{-12} \text{ sec}$

❖ Clock frequency = number of cycles per second (Hertz)

✧  $1 \text{ Hz} = 1 \text{ cycle/sec}$ ,  $1 \text{ KHz} = 10^3 \text{ Hz}$ ,  $1 \text{ MHz} = 10^6 \text{ Hz}$ ,  $1 \text{ GHz} = 10^9 \text{ Hz}$

❖ Clock frequency =  $1 / \text{Clock Cycle}$

✧ Example: Given the clock cycle =  $0.5 \text{ ns} = 0.5 \times 10^{-9} \text{ sec}$



✧ Then, the clock frequency =  $1/(0.5 \times 10^{-9}) = 2 \times 10^9 \text{ Hz} = 2 \text{ GHz}$

# Memory Elements

- ❖ Memory can store and maintain binary state (0's or 1's)
  - ✧ Until directed by an input signal to change state
- ❖ Main difference between memory elements
  - ✧ Number of inputs they have
  - ✧ How the inputs affect the binary state
- ❖ Two main types:
  - ✧ Latches are level-sensitive (the level of the clock)
  - ✧ Flip-Flops are edge-sensitive (sensitive to the edge of the clock)
- ❖ Flip-Flops are used in synchronous sequential circuits
- ❖ Flip-Flops are built with latches




# Memory Elements - Latches

  

- ❖ A basic memory element, as shown in Figure (a), is the **latch**.
- ❖ A latch is a circuit capable of storing one bit of information.
- ❖ The latch circuit consists of two inverters; with the output of one connected to the input of the other.
- ❖ The latch circuit has two outputs, one for the stored value (**Q**) and one for its complement (**Q'**).
- ❖ Figure (b) shows the same latch circuit re-drawn to illustrate the two complementary outputs.
- ❖ The problem with the latch formed by **NOT gates** is that **we can't change the** stored value. For example, if the output of inverter B has logic 1, then it will be latched forever; and there is no way to change this value.
 
# SR Latch

- ❖ An **SR Latch** can be built using two NOR gates
- ❖ Two inputs:  $S$  (Set) and  $R$  (Reset)
- ❖ Two outputs:  $Q$  and  $\bar{Q}$



(a) Logic diagram


S	R	Q	$\bar{Q}$	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

# SR Latch Operation


- ❖ If  $S = 1$  and  $R = 0$  then **Set** ( $Q = 1, \bar{Q} = 0$ )
- ❖ If  $S = 0$  and  $R = 1$  then **Reset** ( $Q = 0, \bar{Q} = 1$ )
- ❖ When  $S = R = 0$ ,  $Q$  and  $\bar{Q}$  are unchanged
- ❖ The latch stores its outputs  $Q$  and  $\bar{Q}$  as long as  $S = R = 0$
- ❖ When  $S = R = 1$ ,  $Q$  and  $\bar{Q}$  are undefined (should never be used)

# SR Latch Timing Diagram

 


# Characteristic Equation of the SR Latch

$Q(t)$	$S$	$R$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Indeterminate

 

$$Q(t+1) = S + R'Q \quad SR = 0$$

 
# $\bar{S} \bar{R}$ Latch with NAND Gates



Known as  
the  $\bar{S} \bar{R}$  Latch

- ❖ If  $\bar{S} = 0$  and  $\bar{R} = 1$  then **Set** ( $Q = 1$ ,  $\bar{Q} = 0$ )
- ❖ If  $\bar{S} = 1$  and  $\bar{R} = 0$  then **Reset** ( $Q = 0$ ,  $\bar{Q} = 1$ )
- ❖ When  $\bar{S} = \bar{R} = 1$ ,  $Q$  and  $\bar{Q}$  are unchanged (remain the same)
- ❖ The latch stores its outputs  $Q$  and  $\bar{Q}$  as long as  $\bar{S} = \bar{R} = 1$
- ❖ When  $\bar{S} = \bar{R} = 0$ ,  $Q$  and  $\bar{Q}$  are undefined (should never be used)


# SR Latch with a Clock Input

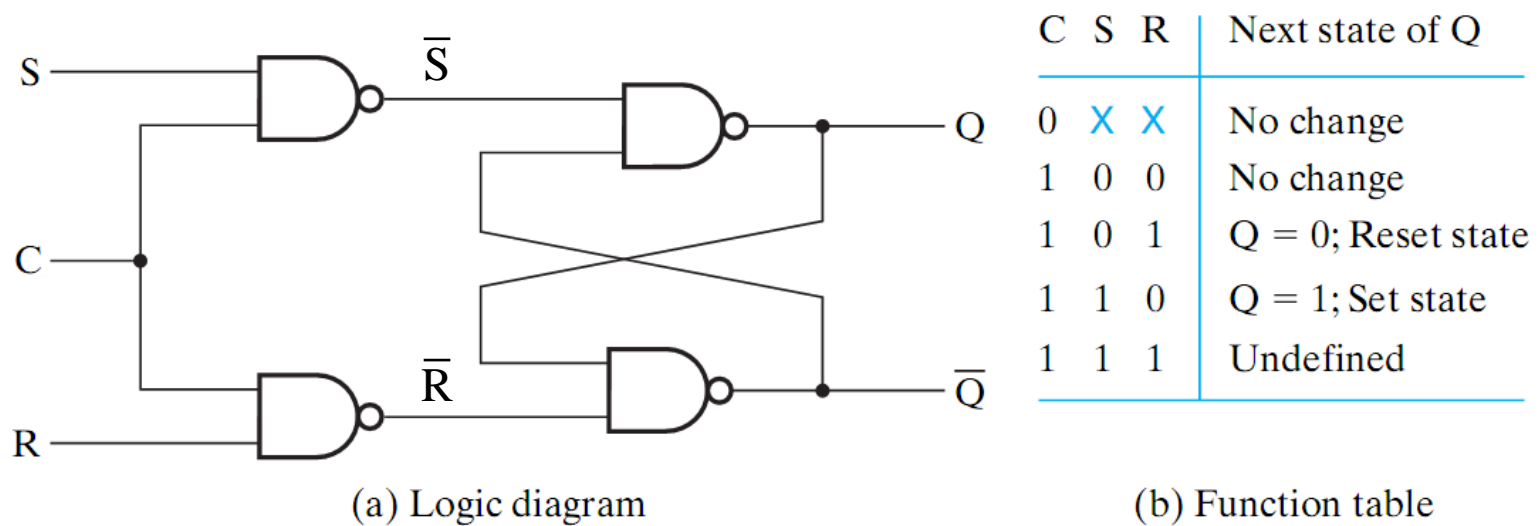

- ❖ An additional Clock input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch  
The latch will remain in the same state, regardless of S and R
- ❖ When **C=1**, then normal SR latch operation

# SR Latch with a Clock Input


Logic Diagram

 


Function Table

C	S	R	Next State
0	X	X	No Change
1	0	0	No Change
1	0	1	Q=0; Reset
1	1	0	Q=1; Set
1	1	1	Indeterminate


No Change

 


No Change

 

Set

 


Reset

 



 
# SR Latch with a Clock Input Timing Diagram



# D-Latch with a Clock Input

 

(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state


(b) Function table

## ❖ Elimination the undesirable condition of the indeterminate state in SR latch

- ❖ Only one data input  $D$
- ❖ An inverter is added:  $S = D$  and  $R = \bar{D}$
- ❖  $S$  and  $R$  can never be 11 simultaneously → No undefined state
- ❖ When  $C = 0$ ,  $Q$  remains the same (No change in state)
- ❖ When  $C = 1$ ,  $Q = D$  and  $\bar{Q} = \bar{D}$

# D-Latch with a Clock Input


Logic Diagram

 


Function Table

$C$	$D$	Next State
0	X	No Change
1	0	$Q=0$ ; Reset
1	1	$Q=1$ ; Set

No Change

 


Set

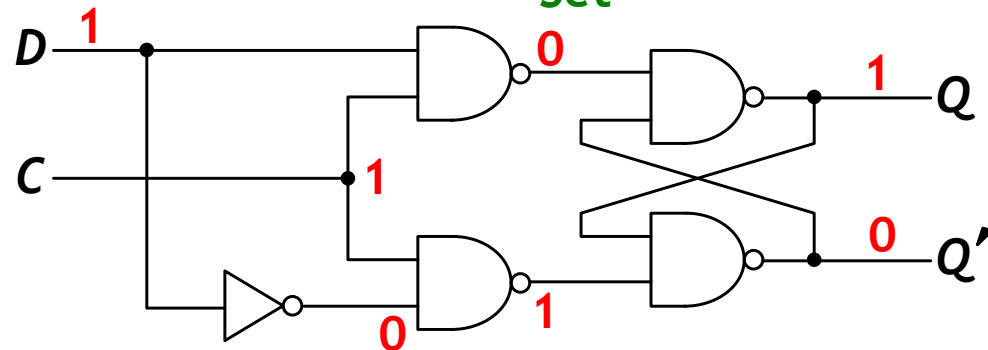

# D-Latch with a Clock Input Timing Diagram

## Regular D-latch response

 

*Outputs respond to input (D)  
during these time periods*


# Characteristic Equation of the D-Latch

$Q(t)$	$D$	$Q(t + 1)$
0	0	0
0	1	1
1	0	0
1	1	1

		$D$	
		0	1
$Q$	0		1
	1		1

$$Q(t+1) = D$$

# Graphic Symbols for Latches

 

❖ A bubble appears at the complemented output  $\bar{Q}$

Indicates that  $\bar{Q}$  is the complement of  $Q$


❖ A bubble also appears at the inputs of an  $\bar{S} \bar{R}$  latch

Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)
 
# Problem with Latches


- ❖ A latch is **level-sensitive** (sensitive to the level of the clock)
- ❖ As long as the clock signal is **high** ...
  - Any change in the value of input  $D$  appears in the output  $Q$
- ❖ Output  $Q$  keeps changing its value during a clock cycle
- ❖ Final value of output  $Q$  is uncertain

Due to this uncertainty, latches are NOT used as memory elements in synchronous circuits


 
# Flip-Flops

- ❖ A **Flip-Flop** is a better memory element for synchronous circuits
- ❖ Solves the problem of latches in synchronous sequential circuits
- ❖ A **latch** is sensitive to the **level** of the clock
- ❖ However, a **flip-flop** is sensitive to the **edge** of the clock
- ❖ A flip-flop is called an **edge-triggered** memory element
- ❖ It changes its output value at the **edge** of the clock






# Positive Edge-Triggered D Flip-Flop

- ❖ Built using two latches in a **master-slave** configuration
- ❖ A master latch (D-type) receives external inputs
- ❖ A slave latch (SR-type) receives inputs from the master latch
- ❖ Only one latch is enabled at any given time

When **C=0**, the master is enabled and the D input is latched (slave disabled)

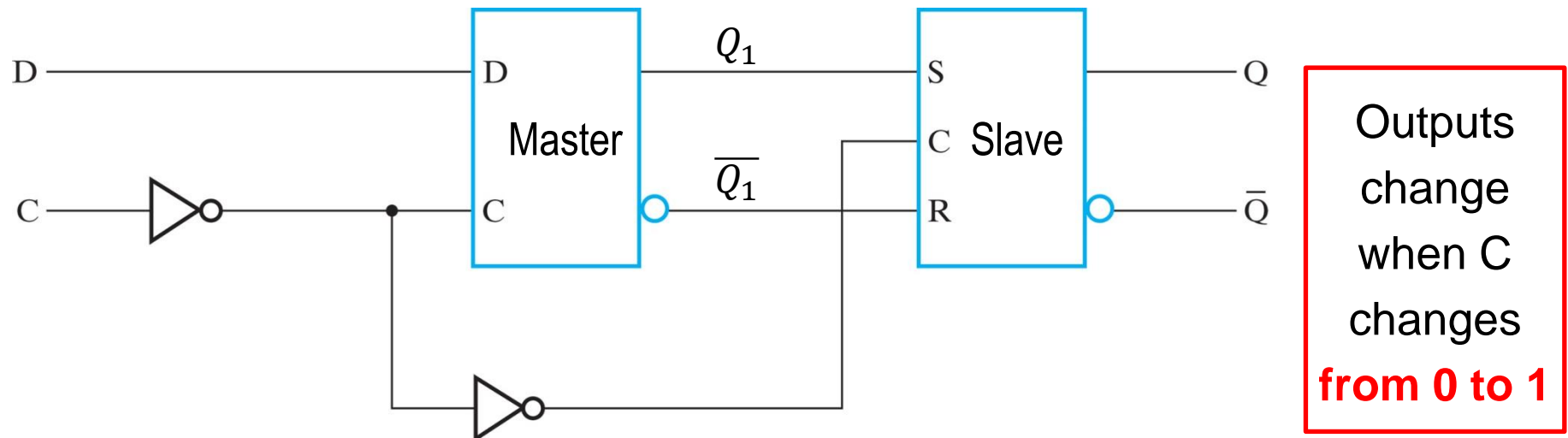When **C=1**, the slave is enabled to generate the outputs (master is disabled)




# Negative Edge-Triggered D Flip-Flop

- ❖ Similar to positive edge-triggered flip-flop
- ❖ The first inverter at the Master C input is removed
- ❖ Only one latch is enabled at any given time


When **C=1**, the master is enabled and the D input is latched (slave disabled)

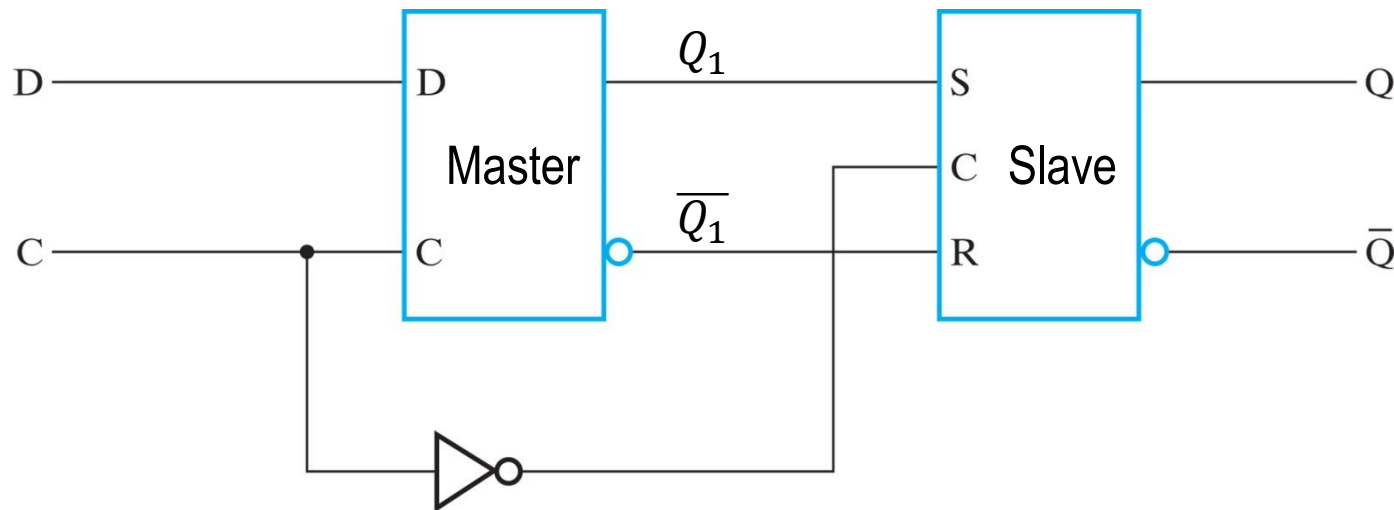When **C=0**, the slave is enabled to generate the outputs (master is disabled)




Outputs  
change  
when C  
changes  
**from 1 to 0**
 
# Negative-Edge D Flip-Flop Timing Diagram







(a) Circuit



 


(b) Timing diagram



# D-Latch vr. Edge-Triggered D Flip-Flop

 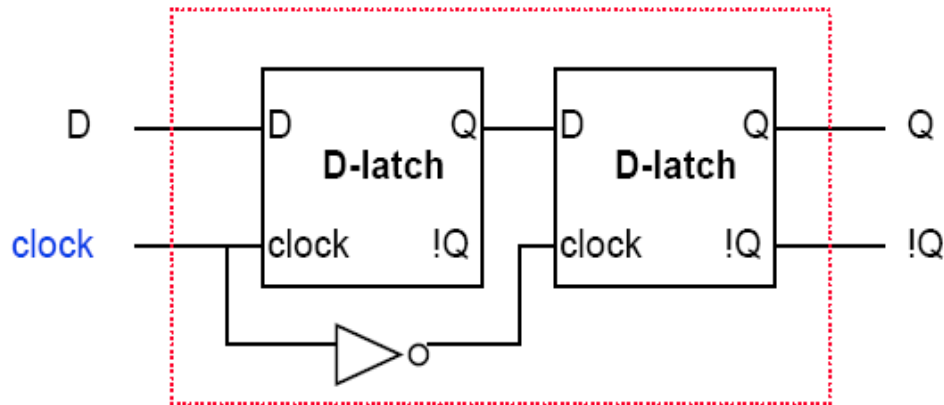  
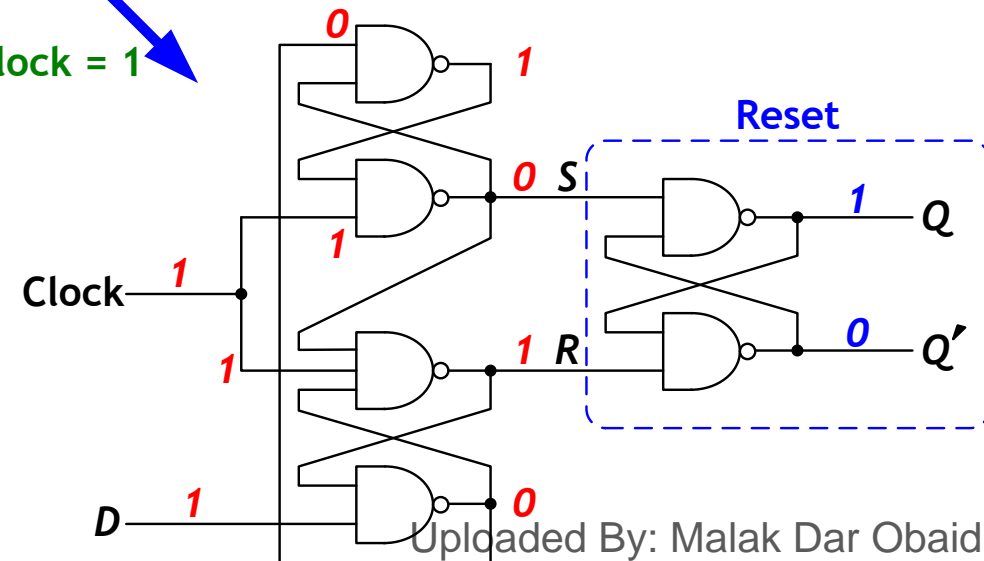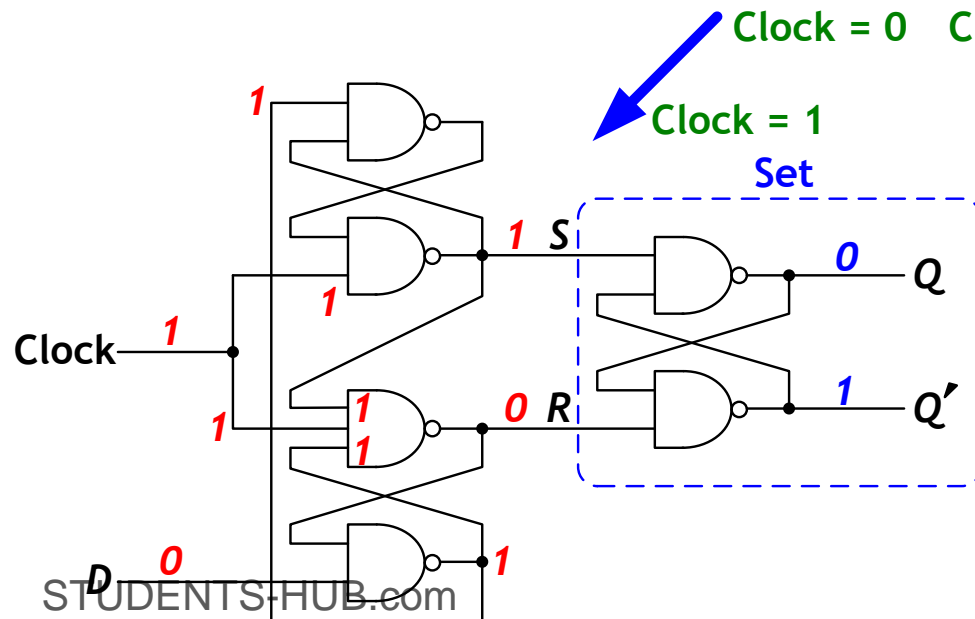 
# Positive Edge-Triggered D Flip-Flop Another Construction




# Graphic Symbols for Flip-Flops

  

- ❖ A Flip-Flop has a similar symbol to a Latch
- ❖ The difference is the arrowhead at the clock input  $C$
- ❖ The arrowhead indicates sensitivity to the edge of the clock
- ❖ A bubble at the  $C$  input indicates negative edge-triggered FF
 
# D Flip-Flop with Asynchronous Reset

- ❖ When Flip-Flops are powered, their initial state is unknown
- ❖ Some flip-flops have an **Asynchronous Reset** input  $R$
- ❖ Resets the state (to logic value **0**), independent of the clock
- ❖ This is required to initialize a circuit before operation
- ❖ If the  $R$  input is inverted (bubble) then  $R = 0$  resets the flip-flop





Inputs			Outputs	
$R$	$Data$	$Clk$	$Q$	$\bar{Q}$
0	X	X	0	1
1	0	$\uparrow$	0	1
1	1	$\uparrow$	1	0


Function Table

# D Flip-Flop with Asynchronous Reset

Circuit Diagram

  

Graphic Symbol

 


Function Table

$R$	$C$	$D$	$Q$	$Q'$
0	X	X	0	1
1	$\uparrow$	0	0	1
1	$\uparrow$	1	1	0




# D Flip-Flop with Asynchronous Reset

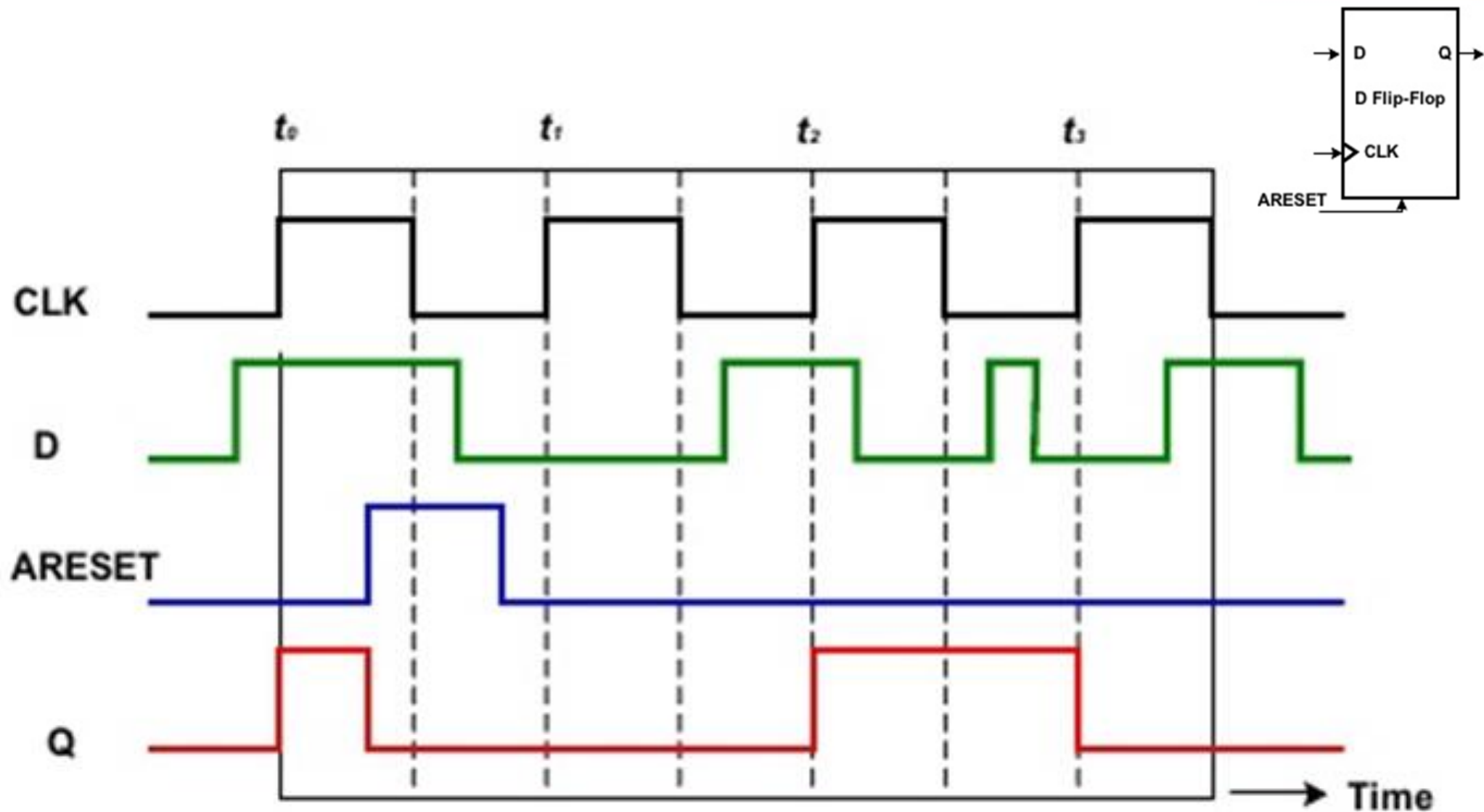


# JK Flip-Flop

- ❖ The D Flip-Flop is the most commonly used type
- ❖ The JK is another type of Flip-Flop with inputs: J, K, and Clk
- ❖ When  $JK = 10 \rightarrow$  Set, When  $JK = 01 \rightarrow$  Reset
- ❖ When  $JK = 00 \rightarrow$  No change, When  $JK = 11 \rightarrow$  Invert outputs
- ❖ JK can be implemented using D FF


J	K	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	1
1	1	$\bar{Q}_t$

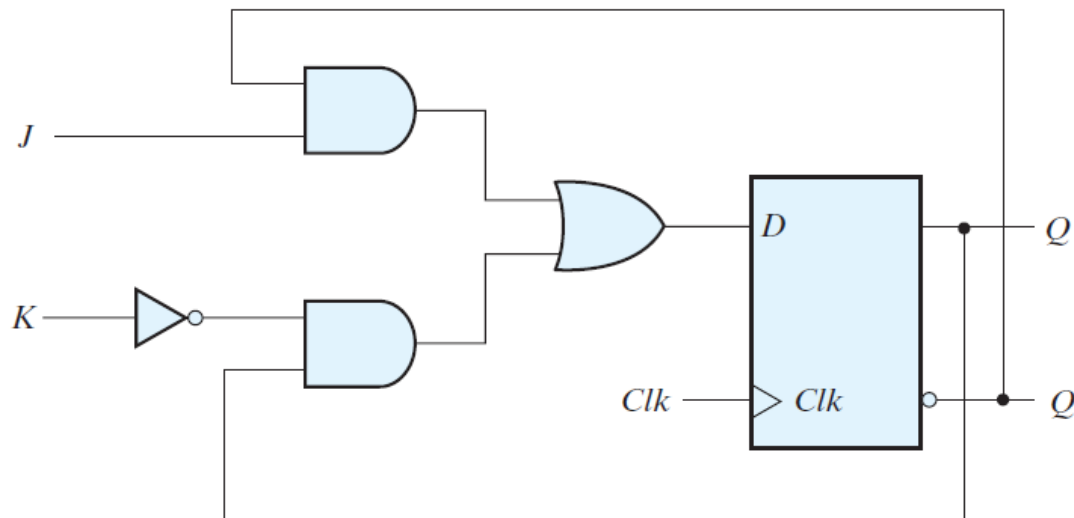

(a) Circuit diagram

 

# JK Flip-Flop Timing Diagram

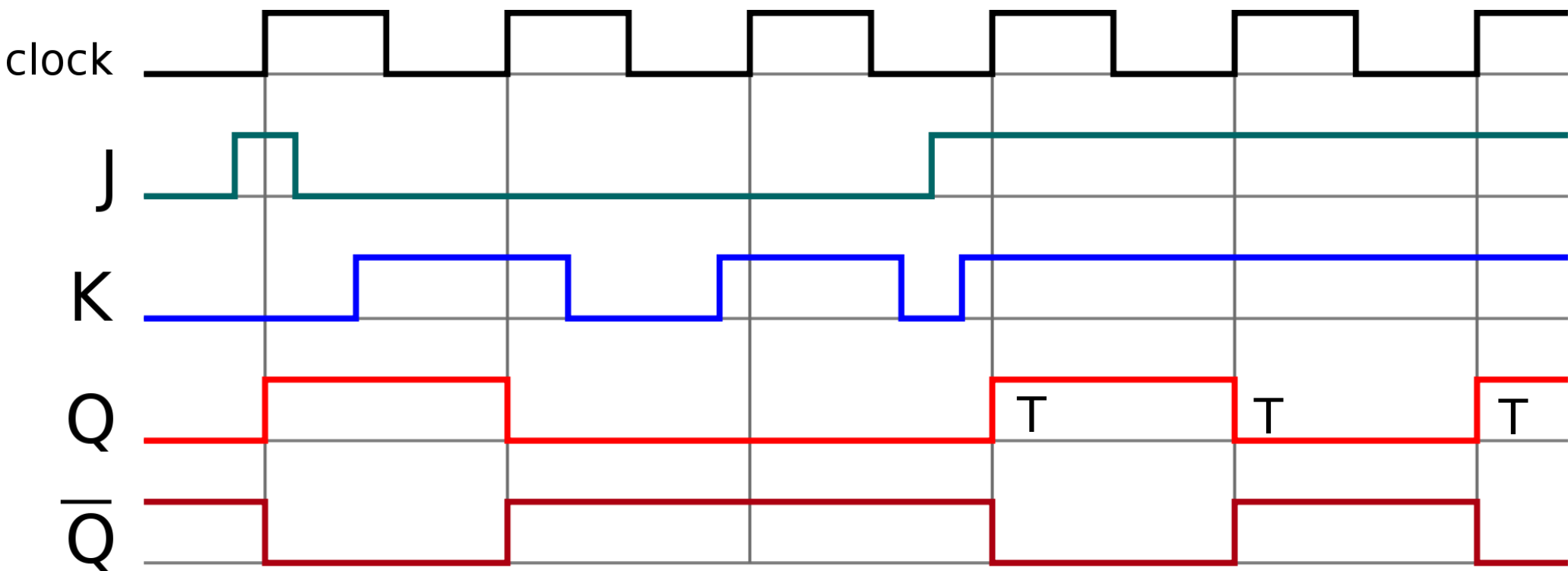

T = toggle

# Characteristic Equation of the JK Flip-Flop

$Q(t)$	$J$	$K$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


		$J$			
		00	01	11	10
$Q$	0			1	1
	1	1			1
		$K$			

$$Q(t+1) = JQ' + K'Q$$


# T Flip-Flop

- ❖ The T (Toggle) flip-flop has inputs: T and Clk
- ❖ When  $T = 0 \rightarrow$  No change, When  $T = 1 \rightarrow$  Invert outputs
- ❖ The T flip-flop can be implemented using a JK flip-flop
- ❖ It can also be implemented using a D flip-flop and a XOR gate


T	$Q_{t+1}$
0	$Q_t$
1	$\overline{Q}_t$

 

(a) From JK flip-flop

 


(b) From D flip-flop

 


(c) Graphic symbol

# T Flip-Flop Timing Diagram

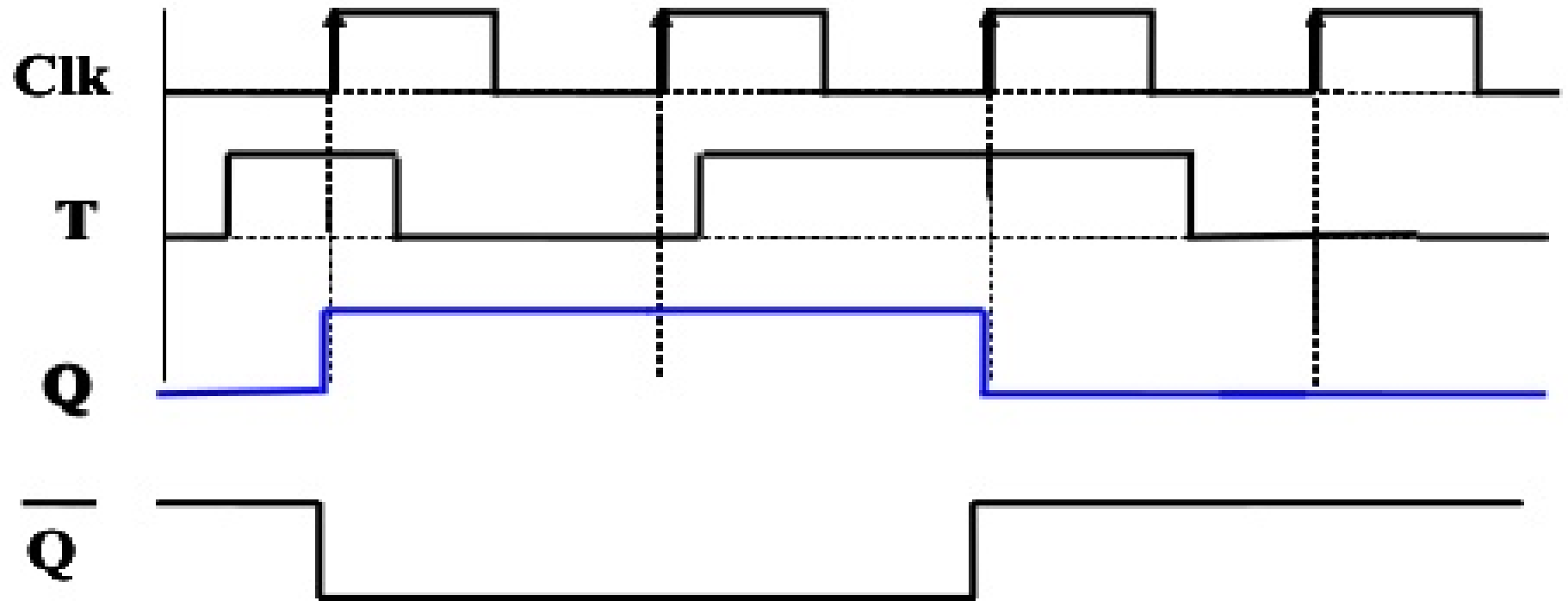

# Characteristic Equation of the T- Flip Flop

$Q(t)$	$T$	$Q(t + 1)$
0	0	0
0	1	1
1	0	1
1	1	0

 

$$Q(t+1) = TQ' + T'Q$$

# Flip-Flop Characteristic Table

- ❖ Defines the operation of a flip-flop in a tabular form
- ❖ Next state is defined in terms of the current state and the inputs

$Q(t)$  refers to current state **before** the clock edge arrives

$Q(t + 1)$  refers to next state **after** the clock edge arrives

D Flip-Flop		
$D$	$Q(t+1)$	
0	0	Reset
1	1	Set

JK Flip-Flop			
$J$	$K$	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip-Flop		
$T$	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement



# Flip-Flop Characteristic Equation

- ❖ The characteristic equation defines the operation of a flip-flop
- ❖ For D Flip-Flop:  $Q(t + 1) = D$
- ❖ For JK Flip-Flop:  $Q(t + 1) = J Q'(t) + K' Q(t)$
- ❖ For T Flip-Flop:  $Q(t + 1) = T \oplus Q(t)$
- ❖ Clearly, the D Flip-Flop is the simplest among the three


D Flip-Flop	
$D$	$Q(t+1)$
0	0 Reset
1	1 Set

JK Flip-Flop	
$J \ K$	$Q(t+1)$
0 0	$Q(t)$ No change
0 1	0 Reset
1 0	1 Set
1 1	$Q'(t)$ Complement

T Flip-Flop	
$T$	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement
 
# Timing Considerations for Flip-Flops

- ❖ **Setup Time ( $T_s$ ):** Time duration for which the data input must be valid and stable **before** the arrival of the clock edge.
- ❖ **Hold Time ( $T_h$ ):** Time duration for which the data input must not be changed **after** the clock transition occurs.
- ❖  $T_s$  and  $T_h$  must be ensured for the proper operation of flip-flops



# Analysis of Clocked Sequential Circuits

- ❖ Analysis is describing what a given circuit will do
- ❖ The output of a clocked sequential circuit is determined by
  1. Inputs
  2. State of the Flip-Flops

## ❖ **Analysis Procedure:**

1. Obtain the equations at the inputs of the Flip-Flops
2. Obtain the output equations
3. Fill the state table for all possible input and state values
4. Draw the state diagram

# Analysis Example

❖ Is this a clocked sequential circuit?

**YES!**

❖ What type of Memory?

**D Flip-Flops**

❖ How many state variables?


**Two state variables:  $A$  and  $B$**

❖ What are the Inputs?

**One Input:  $x$**

❖ What are the Outputs?

**One Output:  $y$**

 

# Flip-Flop Input Equations

❖ What are the equations on the  $D$  inputs of the flip-flops?

$$D_A = A x + B x$$

$$D_B = A' x$$


❖  $A$  and  $B$  are the **current state**

$$A(t) = A, \quad B(t) = B$$

❖  $D_A$  and  $D_B$  are the **next state**

$$A(t + 1) = D_A, \quad B(t + 1) = D_B$$

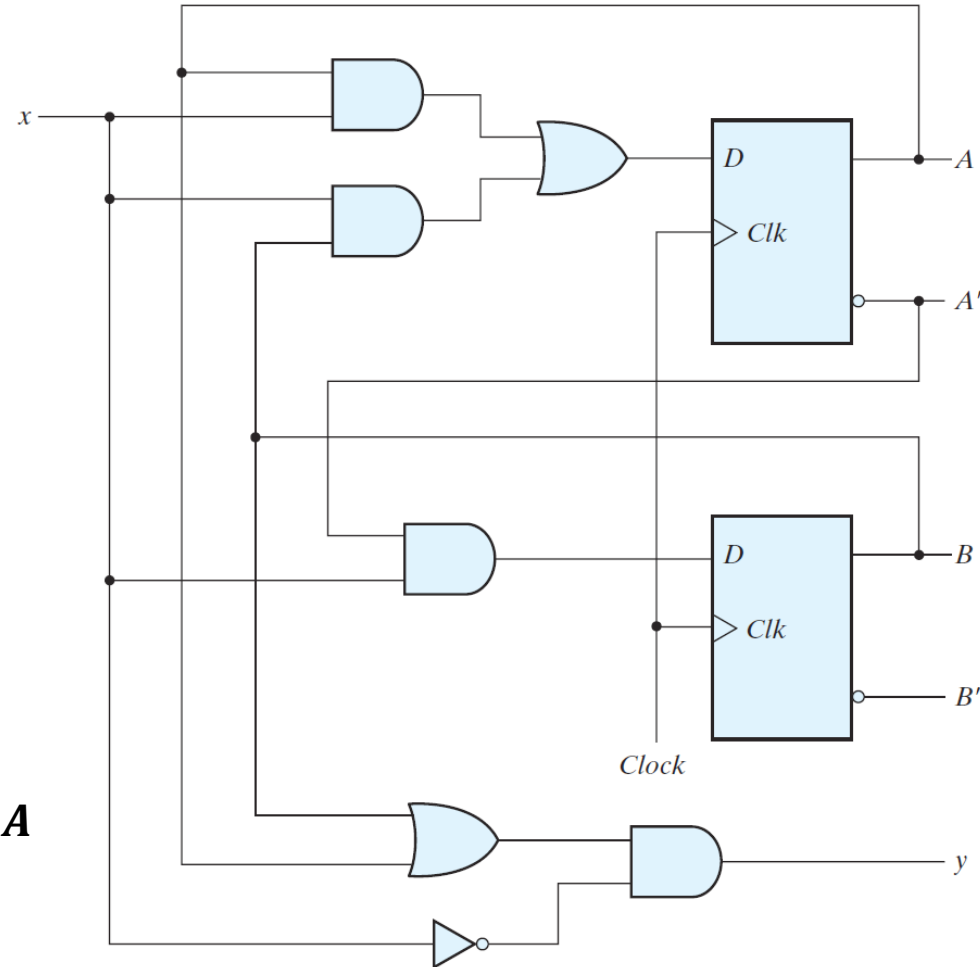❖ The values of  $A$  and  $B$  will be  $D_A$  and  $D_B$  at the next clock edge



# Next State and Output Equations

❖ The next state equations define the **next state**

At the **inputs** of the Flip-Flops

❖ Next state equations?


$$A(t + 1) = D_A = A x + B x$$

$$B(t + 1) = D_B = A' x$$

❖ There is only one output  $y$

❖ What is the output equation?

$$y = (A + B) x'$$

 

# State Table

- ❖ State table shows the Next State and Output in a tabular form
- ❖ Next State Equations:  $A(t + 1) = A x + B x$  and  $B(t + 1) = A' x$
- ❖ Output Equation:  $y = (A + B) x'$

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Another form of the state table


Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
		$A$	$B$	$A$	$B$	$y$	$y$
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

# State Diagram

- ❖ State diagram is a graphical representation of a state table
- ❖ The circles are the states
- ❖ Two state variable  $\rightarrow$  Four states (ALL values of  $A$  and  $B$ )
- ❖ Arcs are the state transitions

Labeled with: Input  $x$  / Output  $y$

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
$A$	$B$	$A$	$B$	$A$	$B$	$y$	$y$
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

 



# Combinational versus Sequential Analysis

## Analysis of Combinational Circuits

- ❖ Obtain the Boolean Equations
- ❖ Fill the Truth Table

Output is a function of input only

## Analysis of Sequential Circuits


- ❖ Obtain the Next State Equations
- ❖ Obtain the Output Equations
- ❖ Fill the State Table
- ❖ Draw the State Diagram

Next state is a function of input and current state


Output is a function of input and current state
 
# Example with Output = Current State

- ❖ Analyze the sequential circuit shown below
- ❖ Two inputs:  $x$  and  $y$
- ❖ One state variable  $A$
- ❖ No separate output  $\rightarrow$  Output = current state  $A$
- ❖ Obtain the next state equation, state table, and state diagram




# Example with Output = Current State

 

❖ Flip-Flop Input Equation:


$$D_A = A \oplus x \oplus y$$

 ❖ Next State Equation:  $A(t + 1) = A \oplus x \oplus y$



Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Sequential Circuit with T Flip-Flops

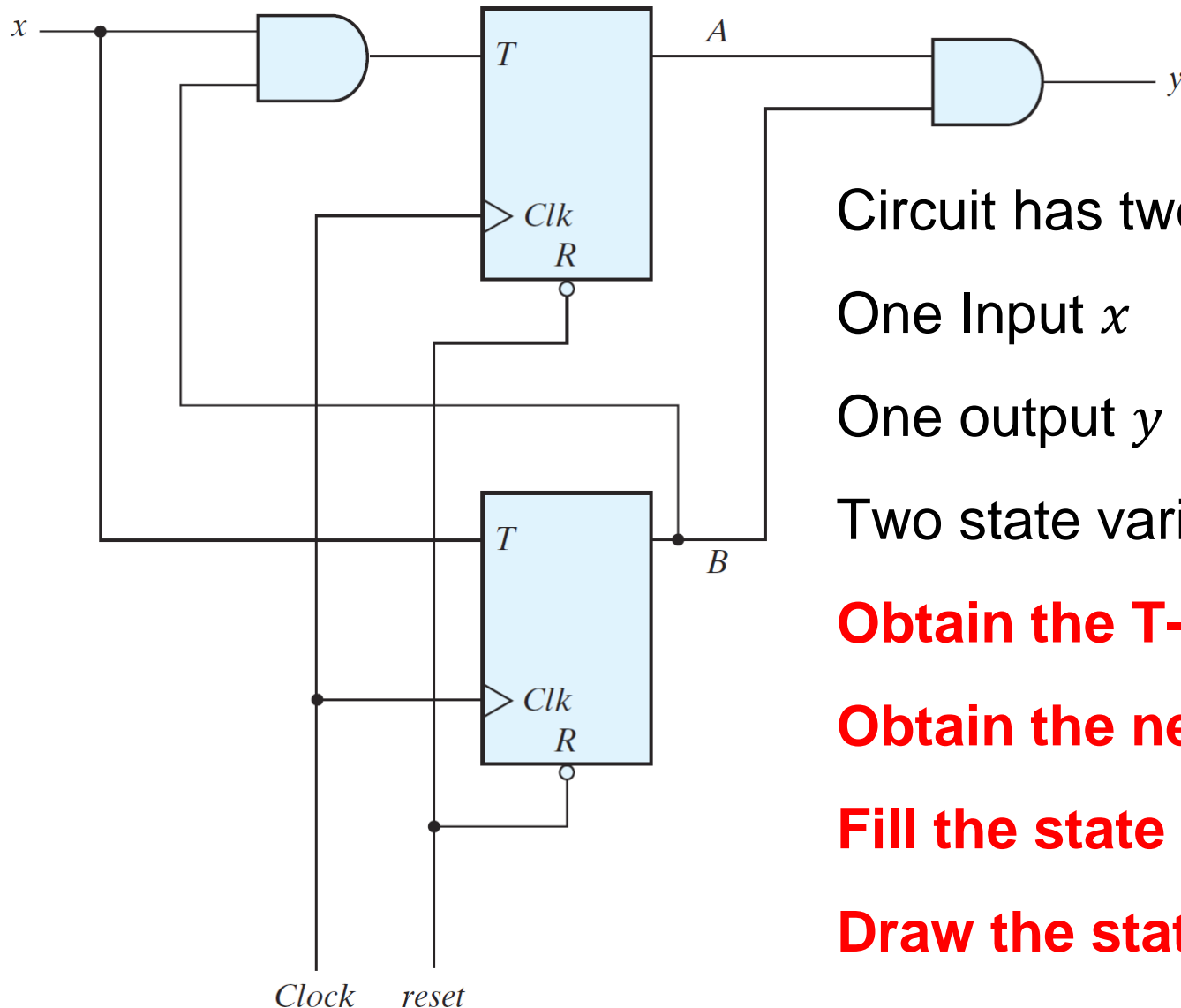

Circuit has two T Flip-Flops

One Input  $x$

One output  $y$

Two state variables:  $A$  and  $B$

**Obtain the T-FF input equations**

**Obtain the next state equations**

**Fill the state table**

**Draw the state diagram**

# Recall: Flip-Flop Characteristic Equation

❖ For D Flip-Flop:  $Q(t + 1) = D$

❖ For T Flip-Flop:  $Q(t + 1) = T \oplus Q(t)$

❖ For JK Flip-Flop:  $Q(t + 1) = J Q'(t) + K' Q(t)$


These equations  
define the Next State

D Flip-Flop		
$D$	$Q(t+1)$	
0	0	Reset
1	1	Set

T Flip-Flop		
$T$	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

JK Flip-Flop		
$J$	$K$	$Q(t+1)$
0	0	$Q(t)$ No change
0	1	0 Reset
1	0	1 Set
1	1	$Q'(t)$ Complement

# Sequential Circuit with T Flip-Flops

 

## T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

## Next State Equations:

$$A(t + 1) = T_A \oplus A = (B x) \oplus A$$

$$B(t + 1) = T_B \oplus B = x \oplus B$$

## Output Equation:

$$y = A B$$

# From Next State Equations to State Table

T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

Next State Equations:

$$A(t + 1) = (B x) \oplus A$$

$$B(t + 1) = x \oplus B$$

Output Equation:

$$y = A B$$


Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Notice that the output is a function of the present state only.

It does **NOT** depend on the input  $x$

# From State Table to State Diagram

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

- ❖ Four States:  $AB = 00, 01, 10, 11$  (drawn as circles)
- ❖ Output Equation:  $y = A B$  (does not depend on input  $x$ )
- ❖ Output  $y$  is shown inside the state circle ( $AB/y$ )



# Sequential Circuit with a JK Flip-Flops

One Input  $x$  and two state variables:  $A$  and  $B$  (outputs of Flip-Flops)


No separate output  $\rightarrow$  Output = Current state  $A B$

**Obtain the JK input equations**

**Obtain the next state equations**

**Fill the state table**

**Draw the state diagram**

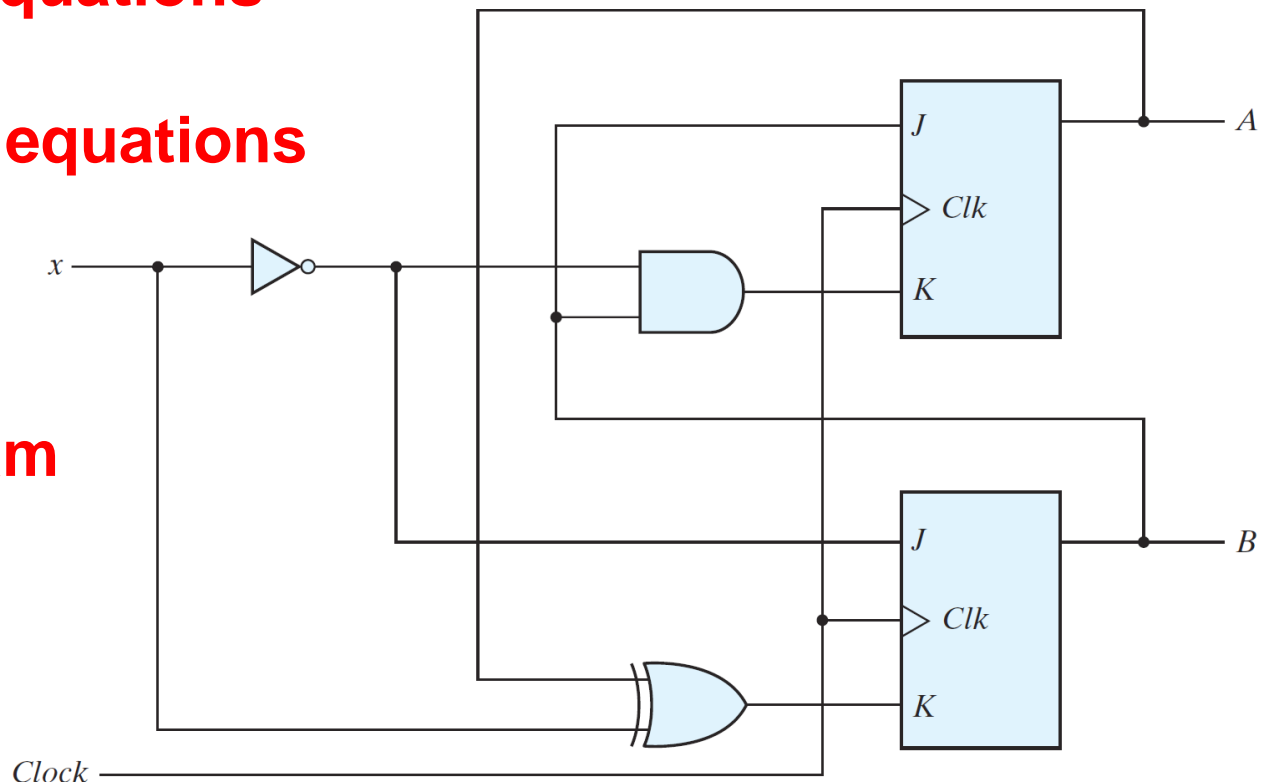

# JK Input and Next State Equations

## JK Flip-Flop Input Equations:

$$J_A = B \text{ and } K_A = B x'$$

$$J_B = x' \text{ and } K_B = A \oplus x$$

## Next State Equations:


$$A(t + 1) = J_A A' + K_A' A$$

$$B(t + 1) = J_B B' + K_B' B$$
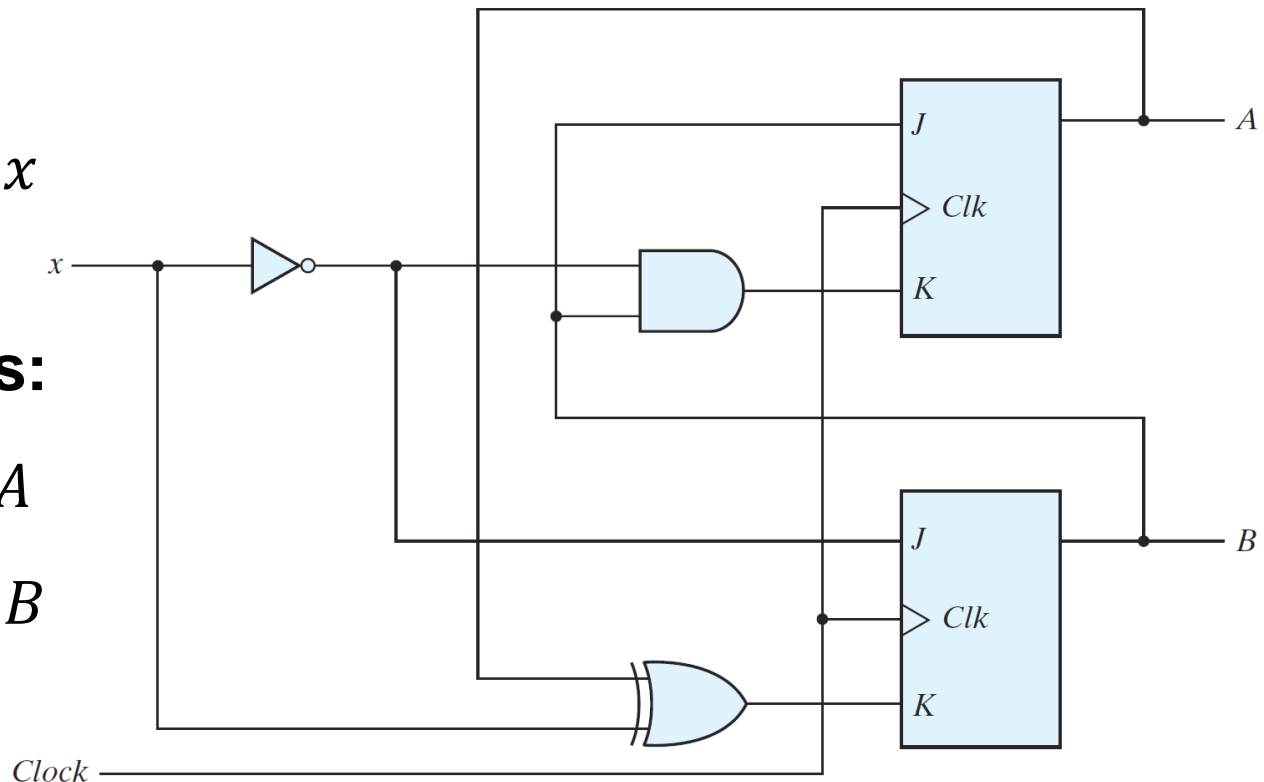
## Substituting:

$$A(t + 1) = B A' + (B x')' A = A' B + A B' + A x$$

$$B(t + 1) = x' B' + (A \oplus x)' B = B' x' + A B x + A' B x'$$



# From JK Input Equations to State Table

**JK Input Equations:**  $J_A = B$  ,  $K_A = B x'$  ,  $J_B = x'$  and  $K_B = A \oplus x$


Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

# From State Table to State Diagram

Four states:  $A B = 00, 01, 10, \text{ and } 11$  (drawn as circles)

Arcs show the input value  $x$  on the state transition



Present State		Input $x$	Next State	
$A$	$B$		$A$	$B$
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 

# Mealy versus Moore Sequential Circuits

There are two ways to design a clocked sequential circuit:

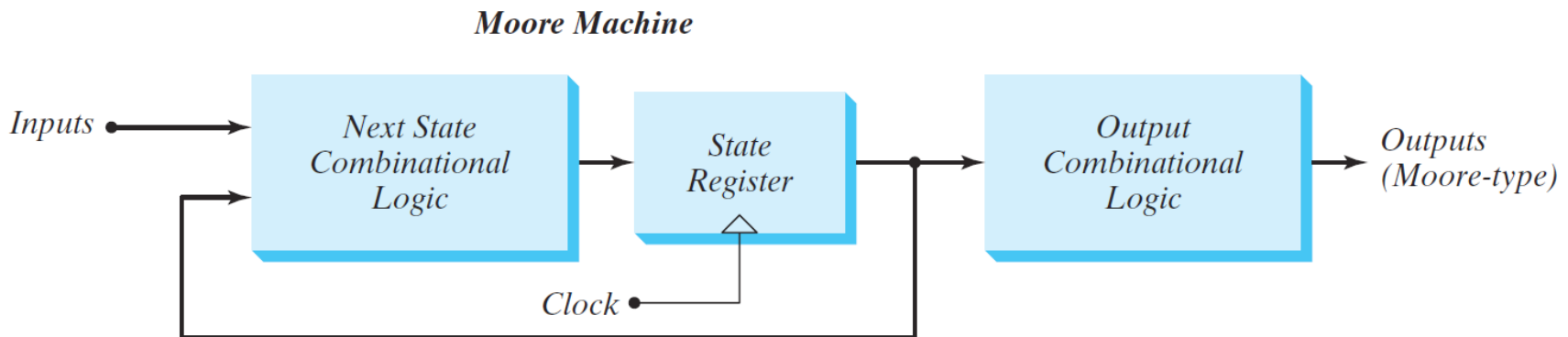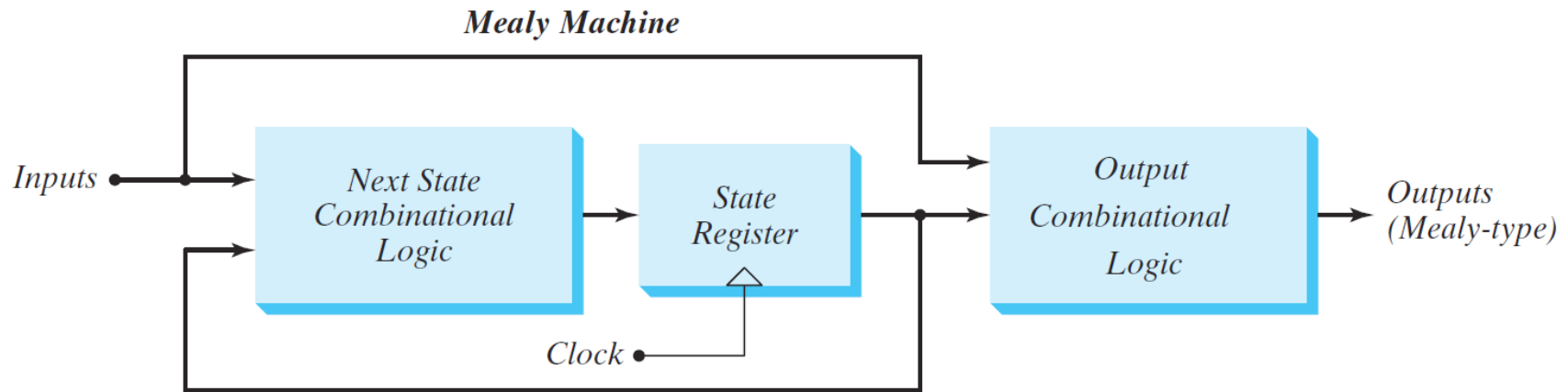
- 1. Mealy Machine:** Outputs depend on present state and inputs
- 2. Moore Machine:** Outputs depend on present state only



# Mealy Machine


- ❖ The outputs are a function of the present state and Inputs
- ❖ The outputs are **NOT** synchronized with the clock
- ❖ The outputs may change if inputs change during the clock cycle
- ❖ The outputs may have momentary false values (called glitches)
- ❖ The correct outputs are present just before the edge of the clock

*Mealy Machine*

 

 
# Mealy State Diagram

- ❖ An example of a Mealy state diagram is shown on the right
- ❖ Each arc is labeled with:  
**Input / Output**
- ❖ The output is shown on the arcs of the state diagram
- ❖ The output depends on the current state and input
- ❖ Notice that State 11 cannot be reached from the other states




# Example of Mealy Model

 



 
# Moore Machine

- ❖ The outputs are a function of the Flip-Flop outputs only
- ❖ The outputs depend on the current state only
- ❖ The outputs are synchronized with the clock
- ❖ Glitches cannot appear in the outputs (even if inputs change)
- ❖ A given design might mix between Mealy and Moore



 
# Moore State Diagram

- ❖ An example of a Moore state diagram is shown on the right
- ❖ Arcs are labeled with input only
- ❖ The output is shown inside the state: (State / Output)
- ❖ The output depends on the current state only




# Example of Moore Model

## Sequential Circuit with JK Flip-Flop

 
 
# State Reduction and Assignment


- ❖ Design starts with state table or diagram
- ❖ State reduction aims at exhibiting the same input-output behavior but with a **lower number** of internal states
- ❖ **State Reduction**
  - ✧ Reductions on the number of flip-flops and the number of gates.
  - ✧ A reduction in the number of states may result in a reduction in the **number of flip-flops**.
  - ✧ May lead to use more gates



# State Reduction

State:	a	a	b	c	d	e	f	f	g	f	g	a
Input:	0	1	0	1	0	1	1	0	1	0	0	
Output:	0	0	0	0	0	1	1	0	1	0	0	

 - ✧ Only the input-output sequences are important.
- ✧ Two circuits are **equivalent**
  - Have identical outputs for all input sequences;
  - The number of states is not important.



# Equivalent states

❖ Two states are said to be equivalent


❖ For each member of the set of inputs, they give exactly the same output and send the circuit to the same state or to an equivalent state.

❖ One of them can be removed.

**Table 5.6**  
*State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

**$e = g$**

 

**Equivalent states**

**Remove state**

# Reducing the state table

- ❖  $e = g$  (remove  $g$ );
- ❖  $d = f$  (remove  $f$ );

**Table 5.7**  
*Reducing the State Table*


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	0
$d$	$e$	$f$	0	1
$e$	$a$	$f$	0	1
$f$	$e$	$f$	0	1

# State Reduction

- ❖ The checking of each pair of states for possible equivalence can be done systematically
- ❖ The unused states are treated as **don't-care condition**  $\Rightarrow$  fewer combinational gates.

**Table 5.8**  
*Reduced State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	0
$d$	$e$	$d$	0	1
$e$	$a$	$d$	0	1

 



# State Assignment

- ❖ To minimize the cost of the combinational circuits.
- ❖ Three possible binary state assignments. ( $m$  states need  $n$ -bits, where  $2^n > m$ )

**Table 5.9**

*Three Possible Binary State Assignments*

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
$a$	000	000	00001
$b$	001	001	00010
$c$	010	011	00100
$d$	011	010	01000
$e$	100	110	10000

**What code assignment would you choose? Why?**

# State Assignment

- ❖ Any binary number assignment is satisfactory as long as each **state is assigned a unique number**.
- ❖ Use binary assignment 1.

**Table 5.10**

*Reduced State Table with Binary Assignment 1*

<b>Present State</b>	<b>Next State</b>		<b>Output</b>	
	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

# Implication Chart


- ❖ To check possible equivalent states in table with large number of states.
- ❖ Example

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0
 
# Implication Chart

❖ **Step1:** draw the implication chart and place (X) in any square of a pair of states whose outputs are not equivalent.

✧ Place (✓) for equivalent states (same outputs, same next state).



Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

# Implication Chart

❖ Step2: for remaining squares, enter the implied states

$a \equiv b \text{ iff } d \equiv e$

b	<del>a,b</del> d,e					
c	x	x				
d	x	x	x			
e	x	x	x	✓		
f	c,d <del>b,b</del>	c,e a,b	x	x	x	
g	x	x	x	d,e	d,e	x
	a	b	c	d	e	f

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

# Implication Chart

- ❖ **Step3:** Place ( $\checkmark$ ) for equivalent states and (X) for not equivalent states

b	<del>a,b</del> $\checkmark$ d,e					
c	X	x				
d	x	x	x			
e	x	x	x	$\checkmark$		
f	<del>c,d</del> $\times$ <del>b,b</del>	<del>c,e</del> $\times$ a,b	x	x	x	
g	x	x	x	<del>d,e</del> $\checkmark$	<del>d,e</del> $\checkmark$	x
	a	b	c	d	e	f

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0

# Implication Chart

- ❖ **Step4:** list equivalent states from squares with ( $\surd$ )

$(a, b), (d, e), (d, g), (e, g)$   
 $\underbrace{\hspace{1cm}} \quad \underbrace{\hspace{1cm}} \quad \underbrace{\hspace{1cm}}$   
 $d \quad \quad d \quad \quad d$

- ❖ **Step5:** combine pairs of states into large group

$(a, b), (d, e, g)$

b	<del>a,b</del> ✓d,e					
c	X	x				
d	x	x	x			
e	x	x	x	✓		
f	<del>c,d</del> ✗b,b	<del>c,e</del> ✗a,b	x	x	x	
g	x	x	x	✓d,e	✓d,e	x
	a	b	c	d	e	f

# Implication Chart

❖ **Step6:** the final states are the equivalent states and all remaining states in state table:

(a,b)  $\longrightarrow$  a

(c)

(d,e,g)  $\longrightarrow$  d

(f)



# Implication Chart

❖ The table can be reduced from seven states into four states:

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	b	0	0
<del>b</del>	<del>e</del>	<del>a</del>	<del>0</del>	<del>0</del>
c	g	f	0	1
d	a	d	1	0
<del>e</del>	<del>a</del>	<del>d</del>	<del>1</del>	<del>0</del>
f	c	b	0	0
<del>g</del>	<del>a</del>	<del>e</del>	<del>1</del>	<del>0</del>

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
a	d	a	0	0
c	d	f	0	1
d	a	d	1	0
f	c	a	0	0

# Design of Sequential Logic



## ❖ Design Procedure

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary
3. Assign binary values to the states
4. Obtain the binary-coded state table
5. Choose the type of flip-flops to be used
6. Derive the simplified flip-flop input equations and output equations
7. Draw the logic diagram

# Design of Clocked Sequential Circuits

## ❖ Example:

Detect 3 or more consecutive 1's

  


State	A	B
$S_0$	0	0
$S_1$	0	1
$S_2$	1	0
$S_3$	1	1


# Design of Clocked Sequential Circuits

## ❖ Example:

Detect 3 or more consecutive 1's

 


Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

 

# Design of Clocked Sequential Circuits

## ❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Synthesis using *D* Flip-Flops

$$A(t+1) = D_A(A, B, x) \\ = \sum (3, 5, 7)$$

$$B(t+1) = D_B(A, B, x) \\ = \sum (1, 5, 7)$$

$$y(A, B, x) = \sum (6, 7)$$

# Design of Clocked Sequential Circuits with D F.F.

## ❖ Example:





Detect 3 or more consecutive 1's

Synthesis using *D* Flip-Flops

$$D_A(A, B, x) = \sum (3, 5, 7) \\ = A x + B x$$

$$D_B(A, B, x) = \sum (1, 5, 7) \\ = A x + B' x$$


$$y(A, B, x) = \sum (6, 7) \\ = A B$$

    

# Design of Clocked Sequential Circuits with D F.F.

## ❖ Example:

Detect 3 or more consecutive 1's

 


Synthesis using *D* Flip-Flops

$$D_A = A x + B x$$

$$D_B = A x + B' x$$

$$y = A B$$

 

# Flip-Flop Excitation Tables

Present State	Next State	F.F. Input
$Q(t)$	$Q(t+1)$	$D$
0	0	0
0	1	1
1	0	0
1	1	1

Present State	Next State	F.F. Input	
$Q(t)$	$Q(t+1)$	$J$	$K$
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

0 0 (No change)

0 1 (Reset)

1 0 (Set)

1 1 (Toggle)

0 1 (Reset)

1 1 (Toggle)

0 0 (No change)

1 0 (Set)


$Q(t)$	$Q(t+1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0



# Design of Clocked Sequential Circuits with JK F.F.

## ❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	x	0	x
0	0	1	0	1	0	x	1	x
0	1	0	0	0	0	x	x	1
0	1	1	1	0	1	x	x	1
1	0	0	0	0	x	1	0	x
1	0	1	1	1	x	0	1	x
1	1	0	0	0	x	1	x	1
1	1	1	1	1	x	0	x	0

Synthesis using JK F.F.

$$J_A(A, B, x) = \sum (3)$$

$$d_{JA}(A, B, x) = \sum (4, 5, 6, 7)$$

$$K_A(A, B, x) = \sum (4, 6)$$

$$d_{KA}(A, B, x) = \sum (0, 1, 2, 3)$$

$$J_B(A, B, x) = \sum (1, 5)$$

$$d_{JB}(A, B, x) = \sum (2, 3, 6, 7)$$

$$K_B(A, B, x) = \sum (2, 3, 6)$$

$$d_{KB}(A, B, x) = \sum (0, 1, 4, 5)$$

# Design of Clocked Sequential Circuits with JK F.F.

## ❖ Example:

Detect 3 or more consecutive 1's



Synthesis using *JK* Flip-Flops

$$J_A = Bx$$

$$K_A = x'$$

$$J_B = x$$

$$K_B = A' + x'$$

  

	<i>B</i>			
	0	0	1	0
<i>A</i>	x	x	x	x
	<i>x</i>			

	<i>B</i>			
	x	x	x	x
<i>A</i>	1	0	0	1
	<i>x</i>			


	<i>B</i>			
	0	1	x	x
<i>A</i>	0	1	x	x
	<i>x</i>			

	<i>B</i>			
	x	x	1	1
<i>A</i>	x	x	0	1
	<i>x</i>			

# Design of Clocked Sequential Circuits with T F.F.

## ❖ Example:

Detect 3 or more consecutive 1's

 

Present State		Input	Next State		F.F. Input	
A	B	x	A	B	$T_A$	$T_B$
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	1
0	1	1	1	0	1	1
1	0	0	0	0	1	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	1	1	1	0	0

Synthesis using T Flip-Flops


$$T_A(A, B, x) = \sum (3, 4, 6)$$

$$T_B(A, B, x) = \sum (1, 2, 3, 5, 6)$$

# Design of Clocked Sequential Circuits with T F.F.

## ❖ Example:




Detect 3 or more consecutive 1's

 

Synthesis using *T* Flip-Flops

$$T_A = A x' + A' B x$$

$$T_B = A' B + B \oplus x$$

   

# Design of a Binary Counter

## Problem Specification:

- ❖ Design a circuit that counts up from 0 to 7 then back to 0


000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000

When reaching 7, the counter goes back to 0 then goes up again

- ❖ There is no input to the circuit
- ❖ The counter is incremented each cycle
- ❖ The output of the circuit is the present state (count value)
- ❖ The circuit should be designed using D-type Flip-Flops
 
# Designing the State Diagram

- ❖ Eight states are needed to store the count values 0 to 7
- ❖ No input, state transition happens at the edge of each cycle




Three Flip-Flops  
are required for  
the eight states

Each state is  
assigned a unique  
binary count value

# State Table

Only two columns: Present State and Next State

State changes each cycle

 

Present State $Q_2 Q_1 Q_0$	Next State $D_2 D_1 D_0$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

# Deriving the Next State Equations

Present State $Q_2 Q_1 Q_0$	Next State $D_2 D_1 D_0$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

		$Q_0$	
		0	1
$Q_2 Q_1$	00	0	0
	01	0	1
	11	1	0
	10	1	1

		$Q_0$	
		0	1
$Q_2 Q_1$	00	0	1
	01	1	0
	11	1	0
	10	0	1

		$Q_0$	
		0	1
$Q_2 Q_1$	00	1	0
	01	1	0
	11	1	0
	10	1	0

$$D_2 = Q_2 Q_1' + Q_2 Q_0' + Q_2' Q_1 Q_0$$

$$D_2 = Q_2 (Q_1' + Q_0') + Q_2' Q_1 Q_0$$

$$D_2 = Q_2 (Q_1 Q_0)' + Q_2' (Q_1 Q_0) = Q_2 \oplus (Q_1 Q_0)$$

$$D_1 = Q_1 Q_0' + Q_1' Q_0 = Q_1 \oplus Q_0$$

$$D_0 = Q_0'$$




# 3-Bit Counter Circuit Diagram

$$D_2 = Q_2 \oplus (Q_1 Q_0)$$

$$D_1 = Q_1 \oplus Q_0$$


$$D_0 = Q'_0$$

 

# Design Example: 3-bit Binary Counter Using T FFs.

## ❖ State Diagram and State Table of 3-bit Binary Counter

State Diagram

 

Excitation Table

$Q(t)$	$Q(t+1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

State Table

Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Refer to T-FF Excitation Table

# Design Example: 3-bit Binary Counter Using T FFs.

## ❖ K-Map Logic Simplification for 3-bit Binary Counter

$T_{A_2} = A_1 A_0$

$A_2 \backslash A_0 A_1$		$A_1$			
		00	01	11	10
0	0			1	
	1			1	

$A_2=1 \left\{ \begin{matrix} 1 \\ 1 \end{matrix} \right.$

$A_0$

$T_{A_1} = A_0$

$A_2 \backslash A_0 A_1$		$A_1$			
		00	01	11	10
0	0		1	1	
	1		1	1	

$A_2=1 \left\{ \begin{matrix} 1 \\ 1 \end{matrix} \right.$

$A_0$

$T_{A_0} = 1$


$A_2 \backslash A_0 A_1$		$A_1$			
		00	01	11	10
0	0	1	1	1	1
	1	1	1	1	1

$A_2=1 \left\{ \begin{matrix} 1 \\ 1 \end{matrix} \right.$

$A_0$
 
# Design Example: 3-bit Binary Counter Using T FFs.

❖ Draw the 3-bit Binary Counter Circuits with T FFs




# Up/Down Counter with Enable

- ❖ **Problem:** Design a synchronous up-down T flip-flop 2-bit binary counter with a select input line  $S$  and a count enable  $En$  input. When  $S = 0$ , the counter counts down; and when  $S = 1$ , the counter counts up. When  $En = 1$ , the counter is in normal up- or down- counting; and  $En = 0$  for disabling both counts.
- ❖ **Solution:** Required mode of operation:

Inputs		Operation
En	S	
0	x	Hold status
1	0	Count Down
1	1	Count Up
 
# State Diagram/Table for 2-bit Up-Down Binary Counter



Arc Label: EnS

T Flip-Flop

Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Present State			Inputs		Next State			T flip-flops	
No	Q1	Q0	En	S	No	Q1	Q0	T <sub>Q1</sub>	T <sub>Q0</sub>
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0
0	0	0	1	0	3	1	1	1	1
0	0	0	1	1	1	0	1	0	1
1	0	1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	1	0	0
1	0	1	1	0	0	0	0	0	1
1	0	1	1	1	2	1	0	1	1
2	1	0	0	0	2	1	0	0	0
2	1	0	0	1	2	1	0	0	0
2	1	0	1	0	1	0	1	1	1
2	1	0	1	1	3	1	1	0	1
3	1	1	0	0	3	1	1	0	0
3	1	1	0	1	3	1	1	0	0
3	1	1	1	0	2	1	0	0	1
3	1	1	1	1	0	0	0	1	1

# Input Equations for 2-bit Up-Down Binary Counter

- The carry out signals:

- $CO_{up}$  and  $CO_{down}$

$CO_{up} = Q_0 Q_1 EnS \rightarrow$  counter reached 11 and it is counting up

$CO_{down} = Q_0' Q_1' EnS' \rightarrow$  counter reached 00 and it is counting down


EnS Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	0	0	1	0
10	0	0	0	1

$$T_{Q_1} = Q_0 EnS + Q_0' EnS'$$

EnS Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$T_{Q_0} = En$$
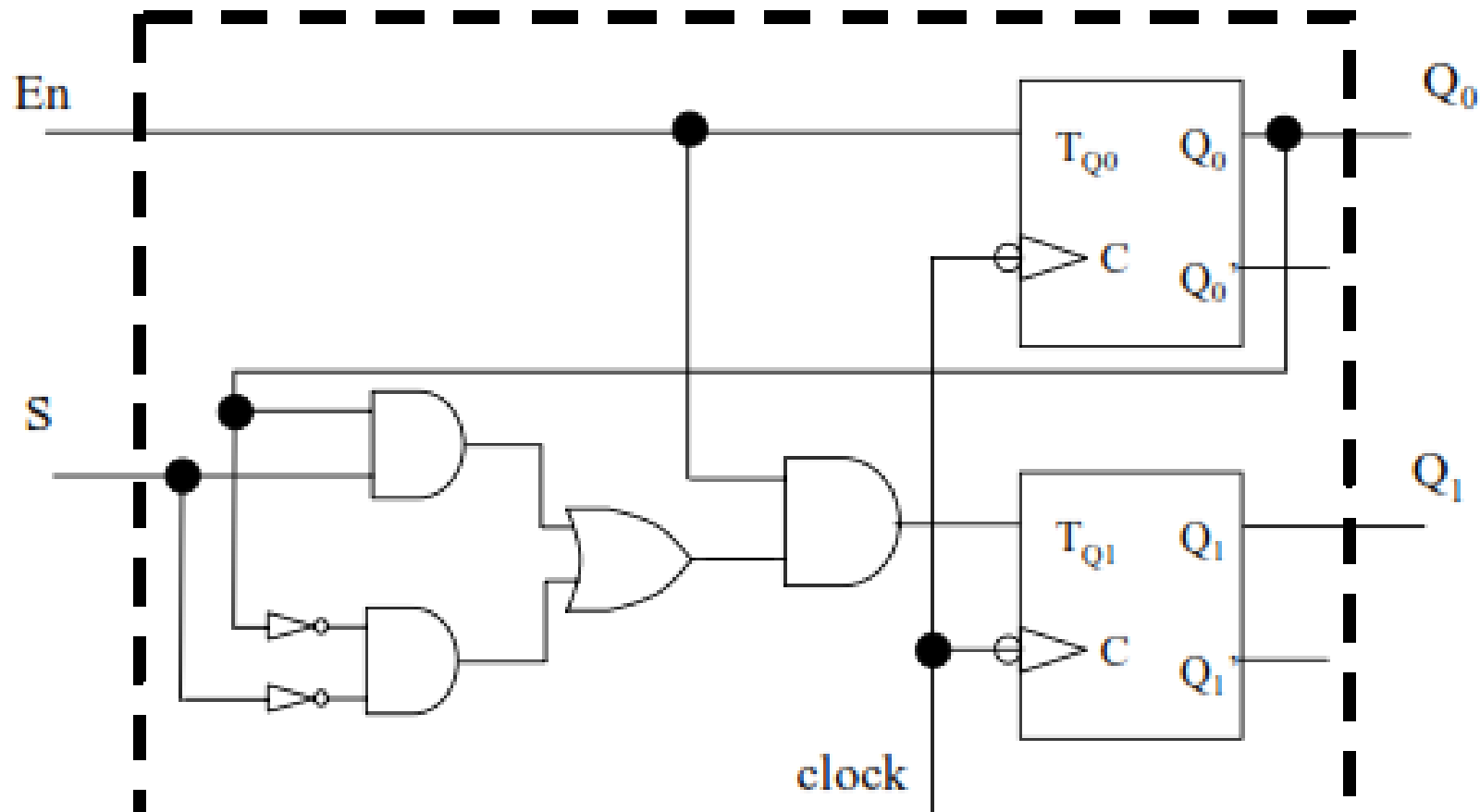
# Circuit for 2-bit Up-Down Binary Counter





# Dealing with Unused States

- ❖ An  $n$ -bit counter has  $2^n$  states, but there are occasions when we wish to use less than the total number of states available.
- ❖ The unused states may be treated as “don’t care” conditions (or assigned to specific next states).
- ❖ Because outside interference may land the counter in these states, we must ensure that the counter can find its way back to a valid state.

# Dealing with Unused States

## ❖ Self-correcting counter

- ✧ Ensure that when a counter enter one of its unused states, it eventually goes into one of the valid states after one or more clock pulses so it can resume normal operation.
- ✧ Analyze the counter to determine the next state from an unused state after it is designed
- ✧ If the unused states are assigned specific next states, this ensures that the circuit is self correcting by design
- ✧ An alternative design could use additional logic to direct every unused state to a specific next state.

## ❖ Design your counters to be self-starting

- ✧ Draw **all** states in the state diagram
- ✧ Fill in the **entire** state-transition table
- ✧ May limit your ability to exploit don't cares
  - Choose startup transitions that minimize the logic

# Counters with unused states

*State Table for Counter*

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

# K-Maps for JK Flip Flop Inputs

A \ BC	00	01	11	10
0		1	X	X
1		1	X	X

$J_B = C$

A \ BC	00	01	11	10
0	1	X	X	
1	1	X	X	

$J_C = B'$

A \ BC	00	01	11	10
0	X	X	X	1
1	X	X	X	1

$K_B = 1$

A \ BC	00	01	11	10
0	X	1	X	X
1	X	1	X	X

$K_C = 1$


A \ BC	00	01	11	10
0	1	X	X	
1	1	X	X	

$J_C = B'$

A \ BC	00	01	11	10
0	X	1	X	X
1	X	1	X	X

$K_C = 1$

# Counter with unused states

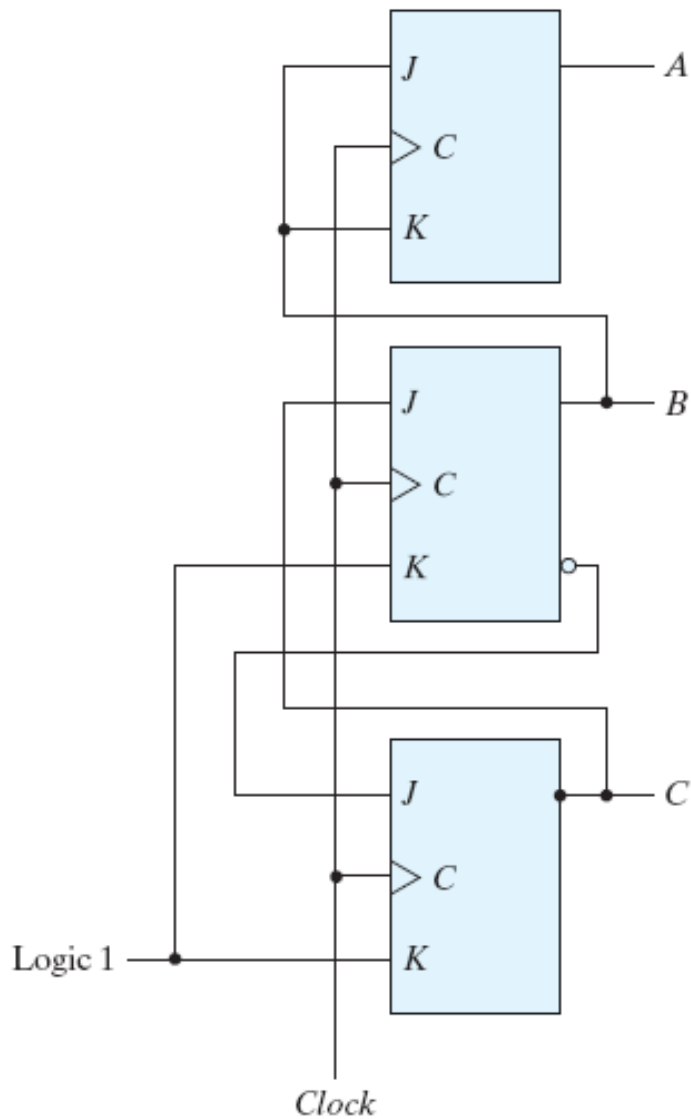

(a) Logic diagram


State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$

$$J_C = B' \quad K_C = 1$$

 


(b) State diagram

# Example: 5-state counter

❖ Counter repeats 5 states in sequence

✧ Sequence is 000, 010, 011, 101, 110, 000

## Step 1: State diagram

 

## Step 2: State transition table

Assume D flip-flops

Present State		Next State			
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	X	X	X
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	X	X	X

## Example: 5-state counter

### Step 3: Encode next state functions

[illegible]

$$C+ = A$$

B+

				C	
	1	1		0	X
A	X	0		X	1

B

$$B+ = B' + A'C'$$


A+

				C
	0	1		0
	X	1		X
A				
				B

$$A+ = BC'$$

# Example: 5-state counter

## Step 4: Implement the design

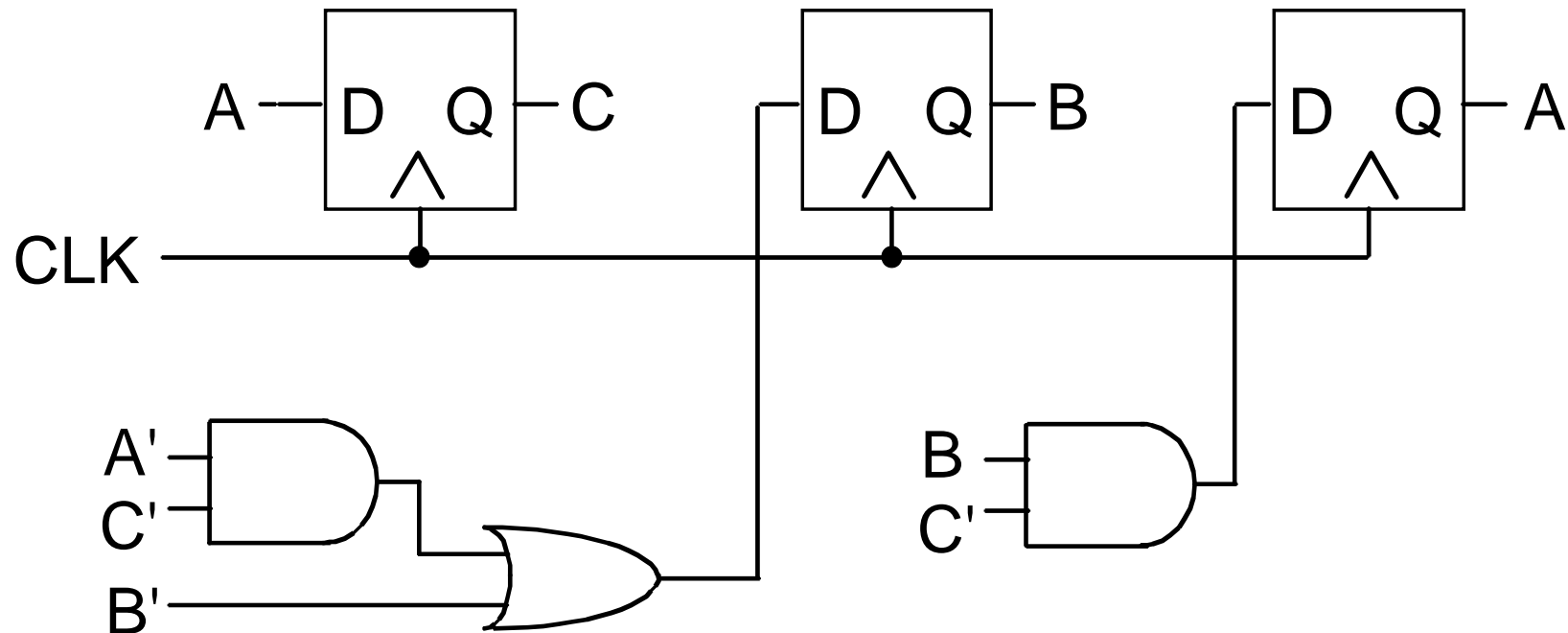


Recall that a D flip flop also produces  $Q'$  so  $A'$ ,  $B'$ , and  $C'$  would all be available without any extra inverters


 
# Is our design robust?

❖ What if the counter starts in a 111 state?



Does our counter get stuck in invalid states???

# 5-state counter

❖ Back-annotate our design to check it

Fill in state transition table


Present State		Next State			
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

$$A+ = BC'$$

$$B+ = B' + A'C'$$

$$C+ = A$$

Draw state diagram

 

The proper methodology is to **design** your counter to be self-starting