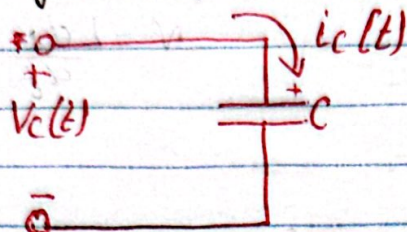


Chapter 7: First order RL, RC circuit

Some of the important characteristics of a capacitor



$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$\rightarrow V_c(t) = \underbrace{V_c(0^-)}_{\text{initial condition}} + \frac{1}{C} \int_0^t i_c(t) dt, \text{ for } t \geq 0.$$

at $t=0^+ \rightarrow V_c(0) = \underbrace{V_c(0^-)}_{\text{initial condition}} + \frac{1}{C} \int_0^0 i_c(t) dt$

$$\rightarrow \boxed{V_c(0) = V_c(0^-)}$$


1: the current through a capacitor is zero if the voltage across it is not changing with time $\rightarrow$ A capacitor is therefore an open circuit to dc.

2: A finite amount of energy can be stored in a capacitor even if the current through the capacitor is zero.


3: the capacitor never dissipate energy, but only store it.

4: It is impossible to change the voltage across a capacitor by a finite amount in zero time, for this requires an infinite current through the capacitor.


5: At $t=0^+$

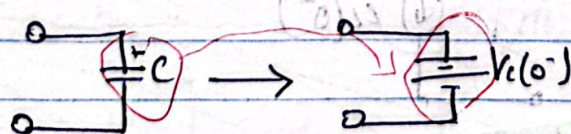

At $t=0^-$ and $t=\infty$

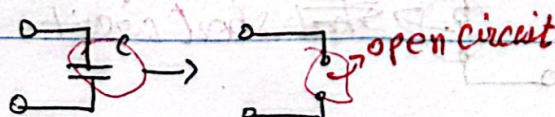

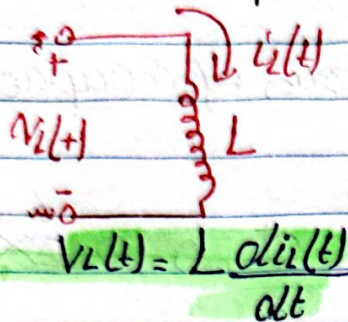Some of the important characteristics of an inductor



$$v = L \frac{di}{dt}$$

$$\rightarrow i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t v_L(t) dt, \text{ for } t \geq 0$$

$$\text{at } t = 0^+ \rightarrow i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_0^{t_0} v_L(t) dt$$

$$\rightarrow \boxed{i_L(0^-) = i_L(0^+)}$$


1: There is no voltage across an inductor if the current through it is not changing with time. An inductor is therefore a short circuit to dc.

2: A finite amount of energy can be stored in an inductor even if the voltage across the inductor is zero.


3: the inductor never dissipate energy, but only store it.

→ It is impossible to change the current through an inductor by a finite amount in zero time. For this requires an infinite voltage across the inductor.

At $t = 0^+$

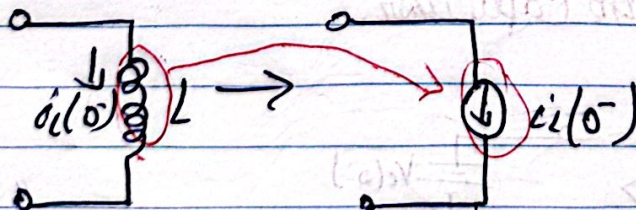

At $t = 0^-$ and $t = \infty$


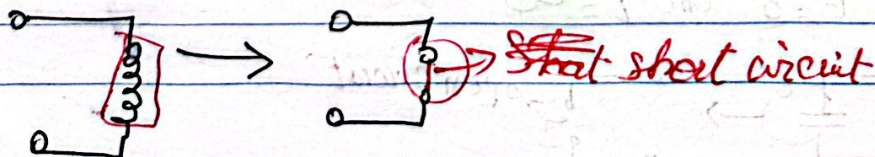


دایره ای که تکرار می شود

حالتی که در آن می توانیم حرکت سورها



دایره ای که تکرار می شود

Natural response
at 1st order circuit

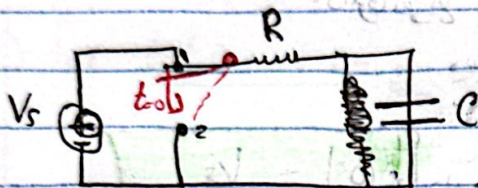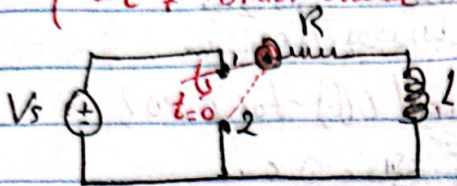

دایره ای که تکرار می شود


step response
of 1st order circuit

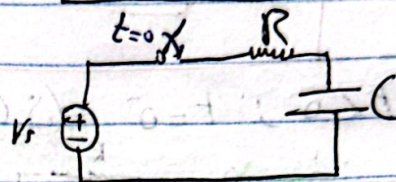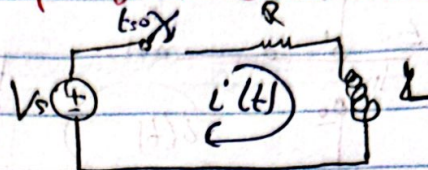

First order Circuit

- A first-order circuit can only contain one energy storage element (a capacitor or an inductor) or a combination of capacitors or inductors that can be reduced to one capacitor or inductor.
- The circuit will also contain one or more resistances.
- A first-order circuit is characterized by a first-order diff. eq.

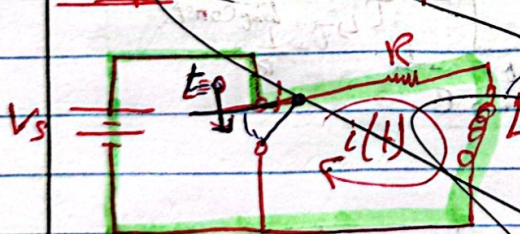
Exp: Natural Response of first-order circuit




Find $i(t)$ for $t > 0$?

① for $t < 0$; $t = 0^-$ S.C. $KVL \rightarrow V_R(t) + V_L(t) = 0 \rightarrow Ri(t) + L \frac{di(t)}{dt} = 0$


$\rightarrow i(t) = Ae^{st}$ for $t > 0$

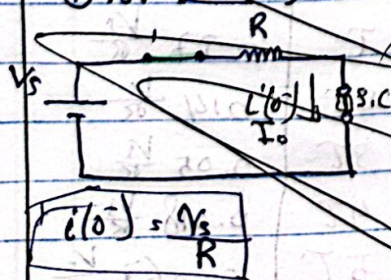


$i(0^-) = \frac{V_s}{R}$

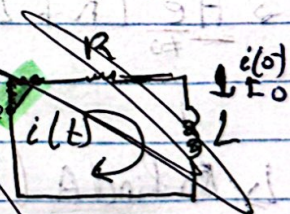

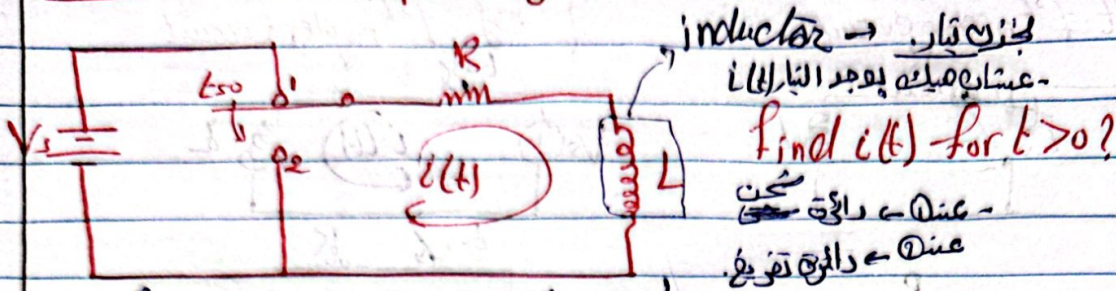Exp: Natural Response of first-order circuit




for $t < 0$; $t = 0^-$ (S.C.)

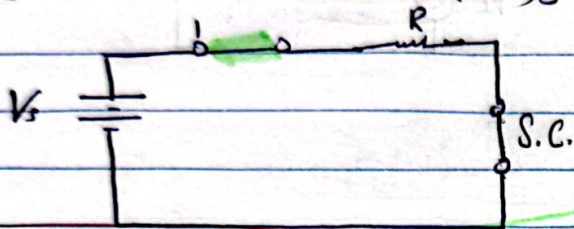

$$i(0^-) = \frac{V_s}{R}$$

for $t > 0$

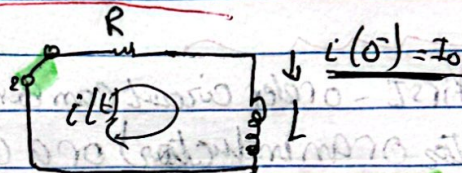

$$\text{KVL} \rightarrow V_R(t) + V_L(t) = 0 \rightarrow Ri(t) + L \frac{di(t)}{dt} = 0$$

$$\rightarrow i(t) = A e^{st} \text{ for } t > 0$$

$$\rightarrow R A e^{st} + L A s e^{st} = 0$$

$$\rightarrow A e^{st} (R + Ls) = 0 \Rightarrow s = -\frac{R}{L} \rightarrow \frac{1}{\tau} = \frac{1}{\text{time const.}} \rightarrow e^{-\frac{R}{L}t} \rightarrow e^{-\frac{t}{\tau}}$$

to find A (from initial conditions) $(0^+, 0^-)$

$$i(t) = A e^{st} \text{ for } t > 0$$

$$\rightarrow i(0^+) = i(0^-) = \frac{V_s}{R}$$


then,

$$i(0^+) = \frac{V_s}{R} = A \rightarrow A = \frac{V_s}{R}$$


$$\therefore i(t) = \frac{V_s}{R} e^{-\frac{R}{L}t} \text{ for } t > 0$$

$$\text{Let } \tau = \frac{L}{R}$$

Time const

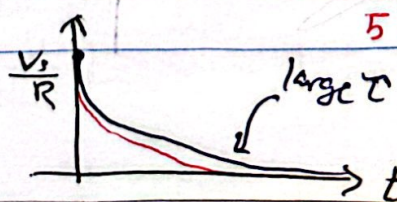


t	i(t)
0	$\frac{V_s}{R}$
τ	$0.37 \frac{V_s}{R}$
2τ	$0.14 \frac{V_s}{R}$
3τ	$0.05 \frac{V_s}{R}$
4τ	$0.018 \frac{V_s}{R}$
5τ	$0.0067 \frac{V_s}{R}$

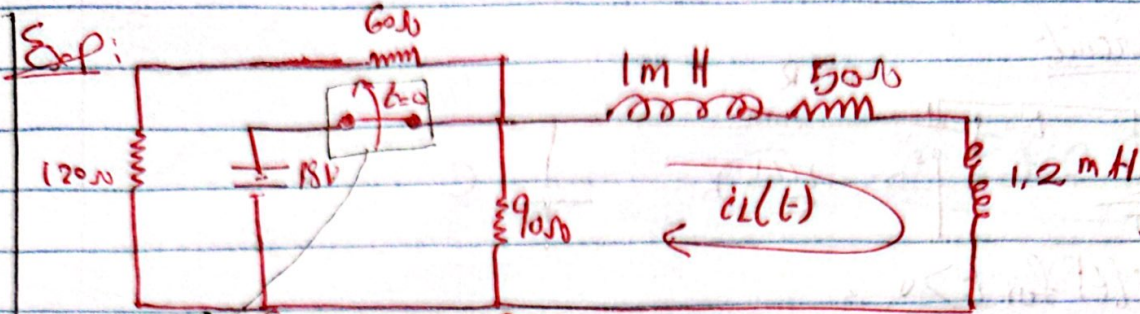

Find $i_L(t)$ for $t > 0$


① for $t < 0, t = 0$

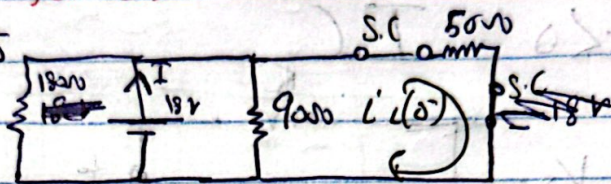

~~$(90/180)$~~
 ~~$(90/180) + 50$~~

$$i_L(0) = \frac{18}{50} = 0.36 \text{ A}$$

② for $t > 0$

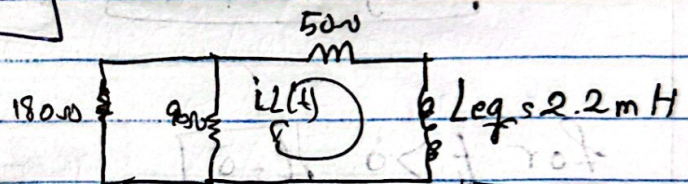


$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2}{10} = 0.22 \text{ s}$$

$$20 \text{ ms}$$


$$R_{eq} = (180/90) + 50 = 110 \Omega$$

$$i_L(t) = A e^{-\frac{t}{\tau}} \text{ for } t > 0$$
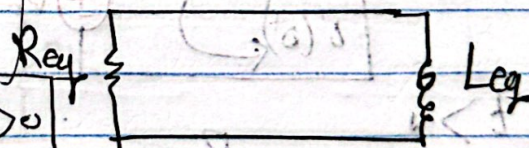
$$= 0.36 e^{-\frac{t}{0.22}} \text{ for } t > 0$$




RC circuit

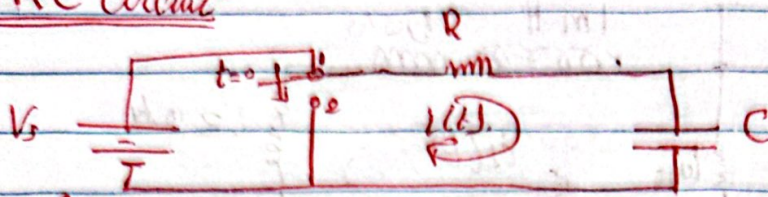

Find $i(t)$ for $t > 0$

For $t < 0$

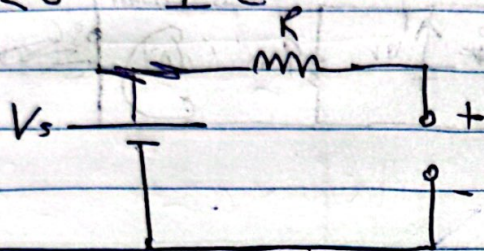


$$V_c(0^-) = V_o = V_s$$

$i(0^-)$ is zero.


for $t > 0$ $t = 0^+$

$$V_c(0^+) = V_c(0^-) = V_s$$

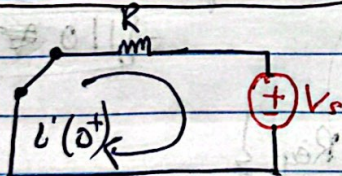

$$i(0^+) = -\frac{V_s}{R}$$

for $t > 0$

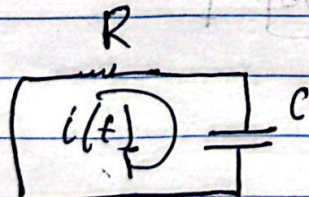

$$Ri(t) + V_c(t) = 0$$

$$Ri(t) + V_o + \frac{1}{C} \int i(t) dt = 0$$

$$R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0 \rightarrow i(t) = A e^{st}$$


→ to find S

$$R A S e^{st} + \frac{1}{C} A e^{st} = 0 \rightarrow \boxed{S = -\frac{1}{RC}} \quad \boxed{T = RC}$$


→ to find A

$$t = 0^+ \quad i(t) = A e^{st} = A e^{-\frac{t}{RC}}$$

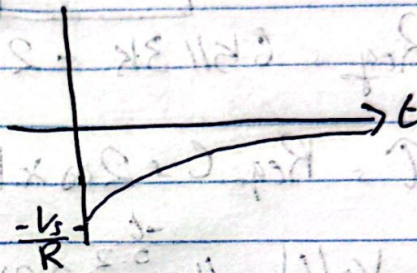
$$\boxed{i(0) = -\frac{V_s}{R} e^{-\frac{t}{RC}}}$$



Ex^o: find $i(t)$ for $t > 0$

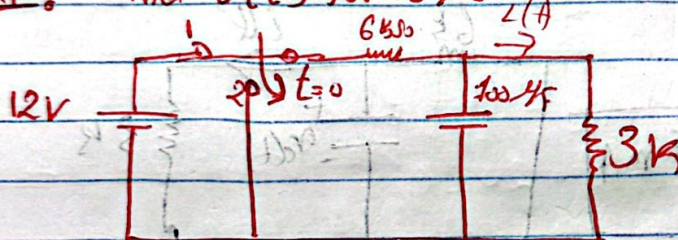

for $t < 0$ ($t \leq 0^-$)

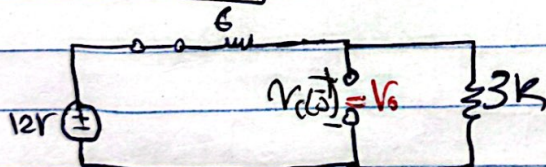

$$i(0) = \frac{12}{9} \text{ mA}$$



$$v_0 = v_c(0) = \frac{3}{3+6} \times 12 = \boxed{4 \text{ Volt}}$$

⊗ natural response $v_c(t) = A e^{st}$

to find $A \rightarrow t = 0^+$

at $t = 0^+ \rightarrow v_c(0), i(0^+) = 4 \text{ V}, i(0^+) = \frac{4}{3} \text{ mA}$


$$\boxed{A = v_c(0^+) = 4 \text{ V}}$$

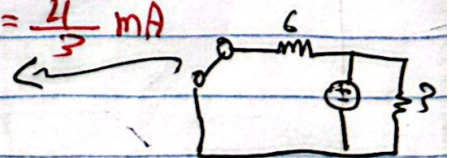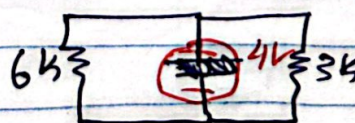

to find S

$$S = \frac{1}{RC} \quad s = -\frac{1}{R_{eq}C}$$

$$\rightarrow t = R_{eq}C$$

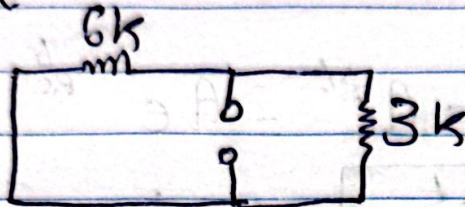

$$R_{eq} = 6k \parallel 3k = 2k$$


$$\tau = R_{eq}C = 2000 \times 100 \times 10^{-6} = 0.2$$

$$\therefore v_c(t) = 4e^{-\frac{t}{0.2}} \text{ V at } t \geq 0$$

$$i(t) = \frac{v_c(t)}{3k}$$

$$= \frac{4}{3} e^{-\frac{t}{0.2}} \text{ mA}$$

$$t > 0$$

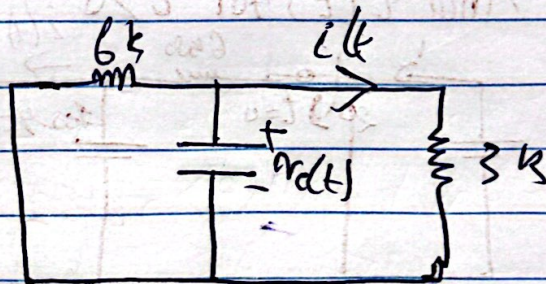

step response RL/RC

forced

$$x(t) = \underbrace{x_n(t)}_{\text{natural}} + \underbrace{x_f(t)}_{\text{forced}}$$

$$Ae^{s_n t} \quad \text{Const}$$

general Solution

$$x(t) = x(\infty) + [x(0^+) - x(\infty)] e^{-t/\tau}$$


Current Voltage = $x_f + [x_0 - x_f] e^{-t/\tau}$

$\tau = \text{Time constant}$

$\tau = R_{eq} C$

$\tau = \frac{L}{R_{eq}}$

Exp:

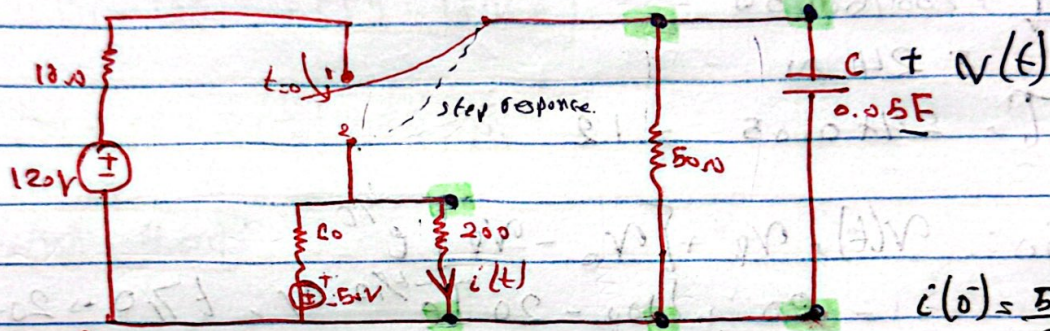

$$i(0) = \frac{50}{260}$$

Find $i(t)$ for $t > 0$

$$v(t) = v_f + [v_0 - v_f] e^{-t/\tau}$$

$$\therefore i(t) = \frac{v(t)}{R} = \frac{v(t)}{200} \quad (\text{Parallel}) \quad v(t) \parallel i(t)$$



at $t < 0$ $[t \rightarrow 0^-]$

$$v(0^-) = \frac{50}{50+10} \times 120 = 100V$$


$$v(0^-) = v(0^+) = 100V$$

@ $t = 0^+$

$$i(0^+) = \frac{100}{200}$$

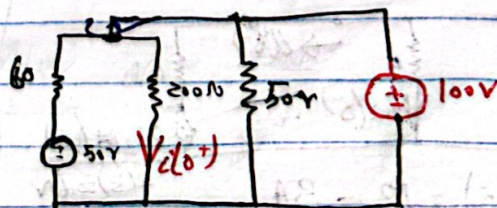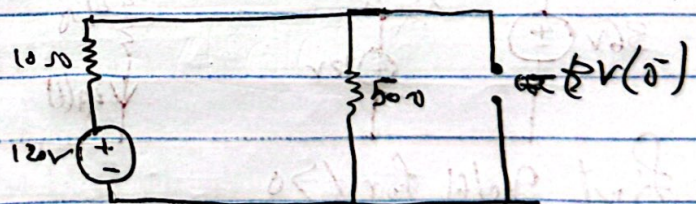


$t > 0 \quad t \rightarrow \infty$

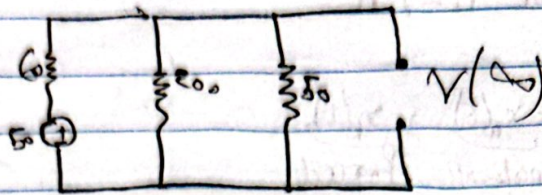

$$V(\infty) = \frac{40}{\frac{200 \parallel 50}{\frac{20 \parallel 60}{100}} + 50} = 20V$$

To find τ :
 $\tau = R_{eq} C$

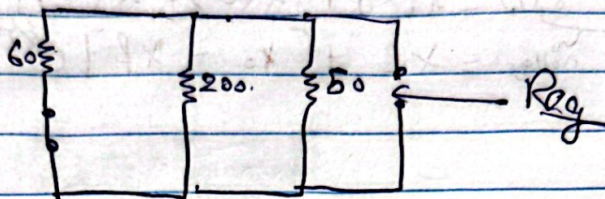

$$R_{eq} = 200 \parallel 50 + 60 = 24 \Omega$$


$$\tau = 24 \times 0.05 = 1.2$$

$$So: V(t) = V_f + [V_o - V_f] e^{-t/\tau}$$

$$= 20 + [100 - 20] e^{-t/1.2} V, t > 0 \Rightarrow 20 + 80e^{-t/1.2}$$


$$\therefore i(t) = \frac{V(t)}{200} = \frac{20}{200} + \frac{80e^{-t/1.2}}{200} A, t > 0$$

Ex:-

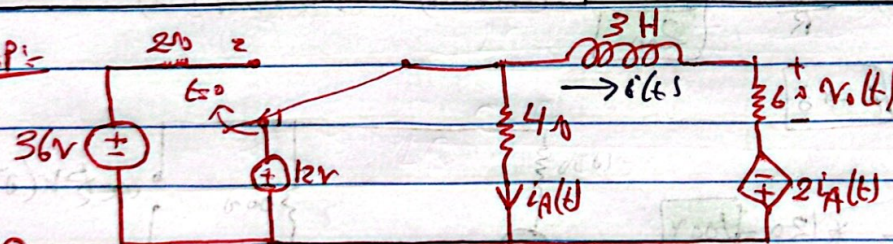

Find $v(t)$ for $t > 0$

For $t < 0, [t \rightarrow 0^-]$

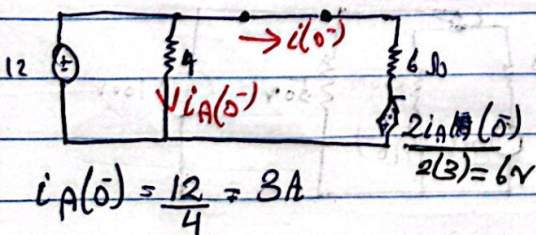


$$i(0^-) \rightarrow -12 + 6i(0^-) = 6 = 0$$

$$6i(0^-) = 18 \Rightarrow i(0^-) = 3A$$

$$OR \rightarrow i(0^-) = \frac{18}{6} = 3A$$

$$i(0^-) = i(0^+) = 3A$$

$t \rightarrow \infty$

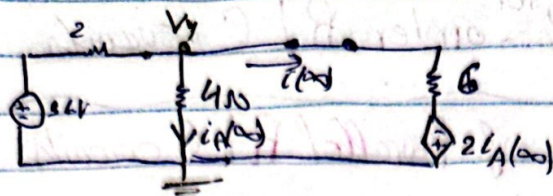

$$\frac{V_y - 36}{2} + \frac{V_y}{4} + \frac{V_y + 2i_A(\infty)}{6} = 0, \quad i_A(\infty) = \frac{V_y}{4}$$

$$6 \times \left(\frac{V_y - 36}{2} + \frac{V_y}{4} + \frac{V_y + 2 \cdot \frac{V_y}{4}}{6} \right) = 0$$

$$3V_y - 108 + \frac{3}{2}V_y + V_y + \frac{1}{2}V_y = 0$$


$$6V_y = 108 \rightarrow \boxed{V_y = 18 \text{ Volts}}$$

$$i(\infty) = \frac{18 + 2(\frac{18}{4})}{6} = \boxed{4.5 \text{ A}}$$

$$\boxed{i(\infty) = 4.5 \text{ A}}$$

$$T = \frac{L}{R_{eq}}, \quad t > 0$$
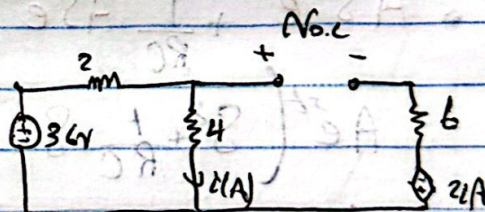
$$R_{eq} = \frac{V_{o.c}}{I_{s.c}} = \frac{V_{o.c}}{4.5}$$



$$V_{o.c} = V_{4\Omega} + 2 \cdot i(A)$$

$$= \left(\frac{4}{4+2} \right) 36 + 2 \left(\frac{36}{6} \right)$$

$$= 24 + 12 = \boxed{36 \text{ V}}$$

$$\rightarrow R_{eq} = \frac{36}{4.5} = \boxed{8 \Omega}$$

$$\boxed{T = \frac{3}{8}}$$

$$\therefore i(t) = I_h + \{i(0) + i_h\} e^{-t/\tau}$$

$$i(t) = 4.5 + \{3 - 4.5\} e^{-\frac{8}{3}t} \text{ A}, \quad t \geq 0$$

$$\therefore v(t) = 8 R_i(t)$$

$$= \boxed{6 i(t)}$$