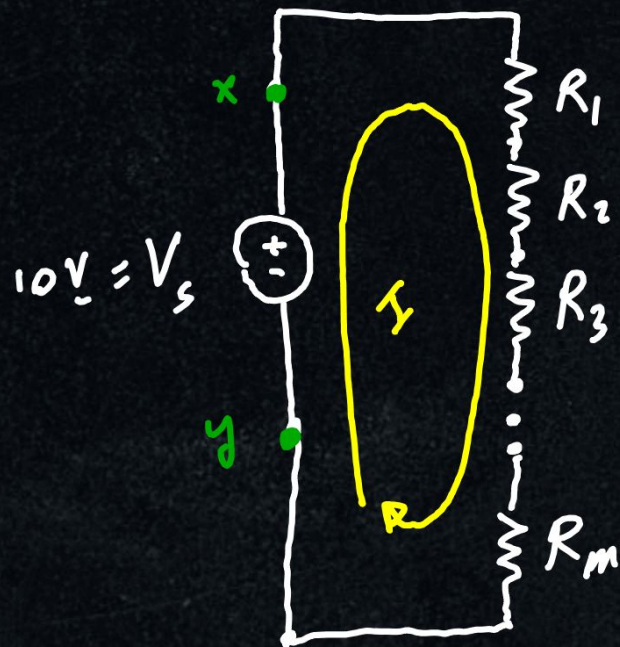


CH3: Simple Resistive Circuits

Resistors in series



series connected resistors carry the same current

using KVL:



$$-V_s + R_1 I + R_2 I + R_3 I + \dots + R_m I = 0$$

$$V_s = (R_1 + R_2 + \dots + R_m) I$$

$$V_s = R_{eq} I$$

$$R_{eq} = \sum_{i=1}^m R_i$$

Resistors in parallel

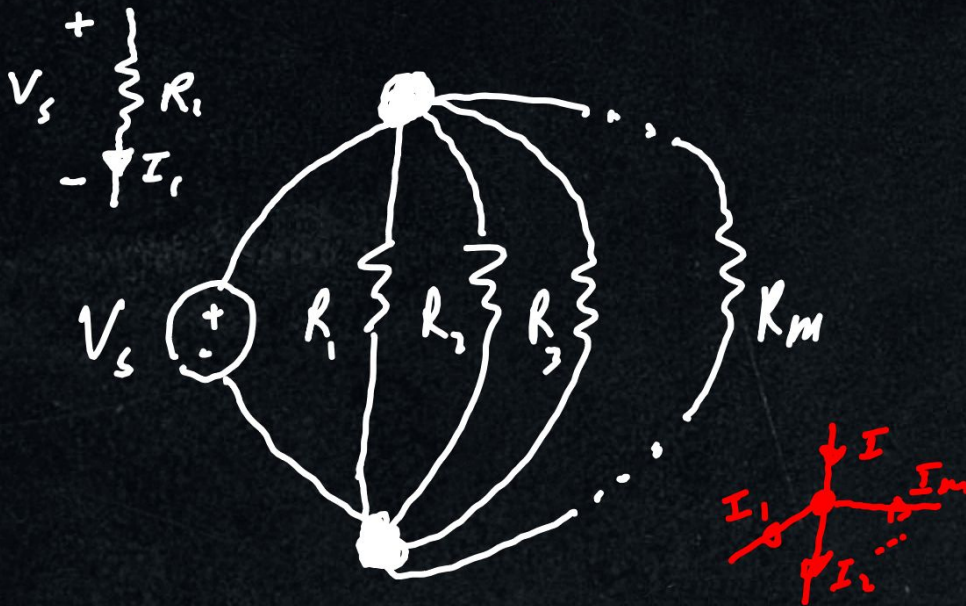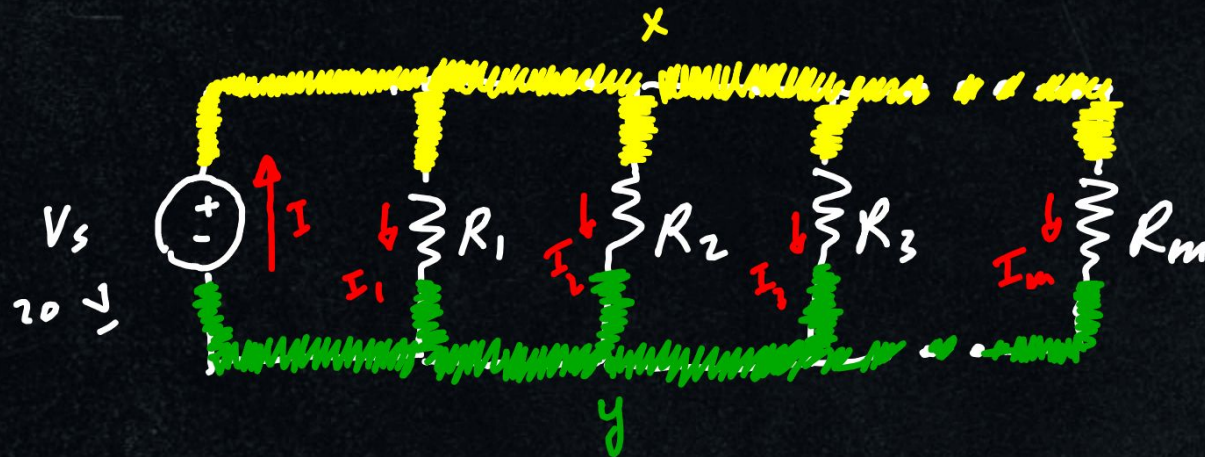

parallel connected resistors have the same voltage across their terminal,


Number of nodes = 2

Based on using KCL:

$$\sum I \Big|_{\text{Node x}} = 0$$

$$I_1 + I_2 + I_3 + \dots + I_m - I = 0$$

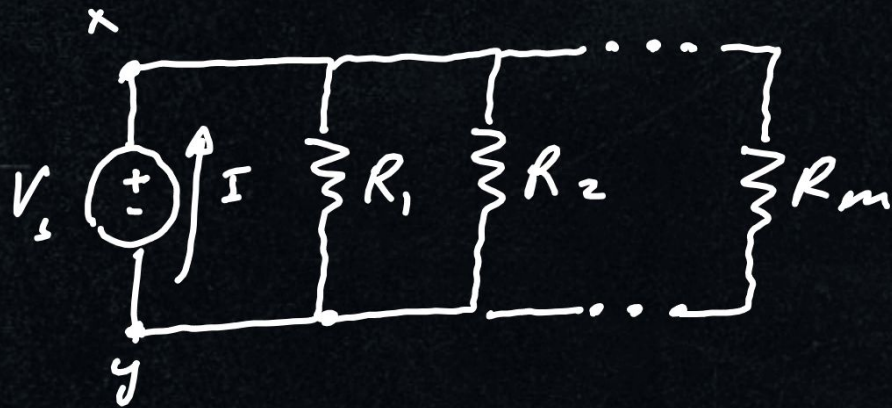
$$\frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3} + \dots + \frac{V_s}{R_m} = I$$



$$\frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3} + \dots + \frac{V_s}{R_m} = I$$

$$V_s \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m} \right] = I$$

$$V_s = R_{eq} I$$

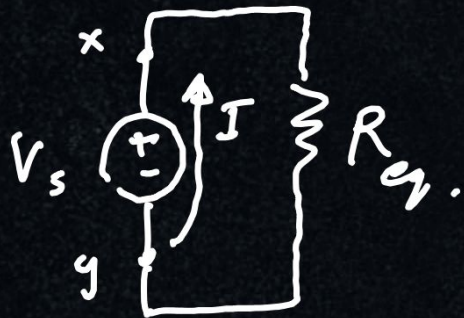

$$I = \frac{V_s}{R_{eq}}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m}}$$

or


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m}$$

1) If $m=2$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \boxed{R_{eq} = \frac{R_1 R_2}{R_1 + R_2}}$$

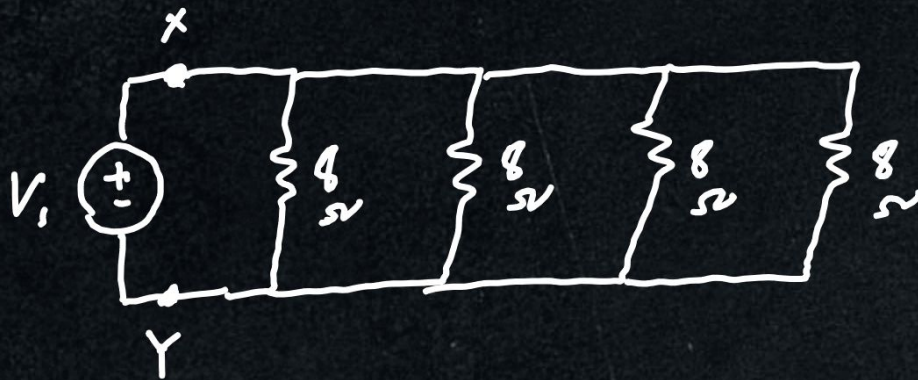
2) If $R_1 = R_2 = R_3 = \dots = R_m = R$

$$\frac{1}{R_{eq}} = \underbrace{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}}_{m \text{ terms}} = \frac{m}{R} \Rightarrow R_{eq} = \frac{R}{m}$$




$$R_{xy} = \frac{8}{4} = 2\ \Omega$$

Ex :-


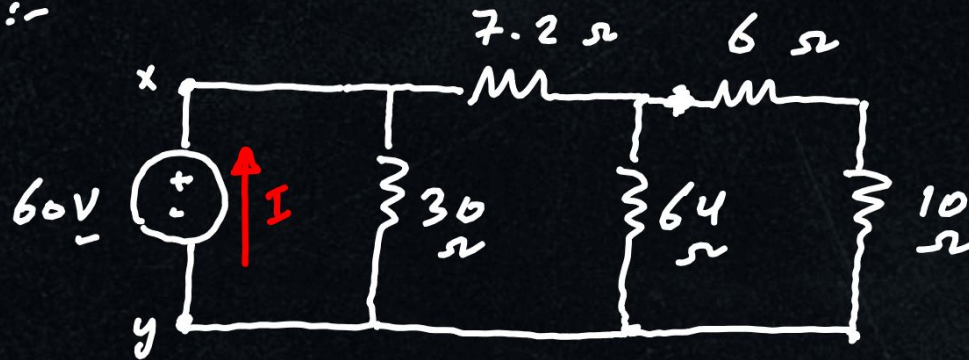


① Calculate R_{xy}
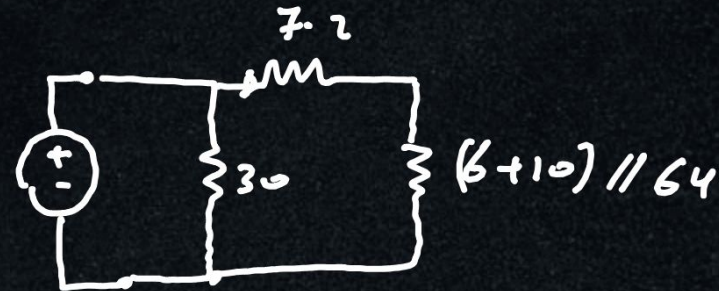
$$R_{xy} = \left[\underbrace{\left((6+10) \parallel 64 \right) + 7.2}_{12.8} \parallel 30 \right]$$




$$R_{xy} = 12 \Omega$$

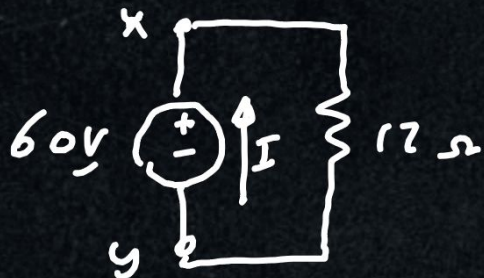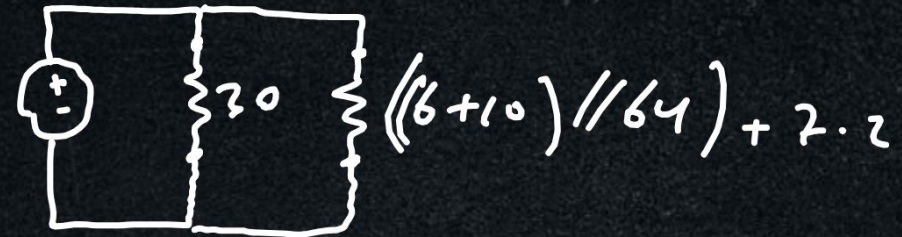

② Calculate I

$$I = \frac{60}{12} = 5 A$$

Voltage Divider

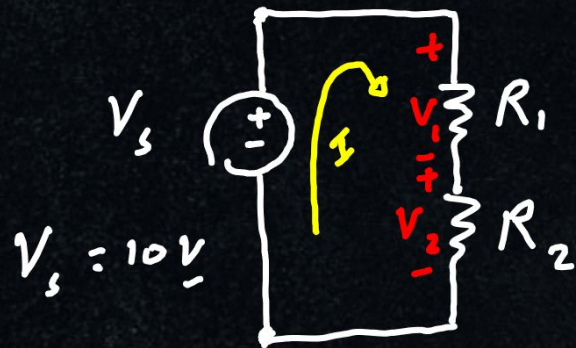



$$-V_s + R_1 I + R_2 I = 0$$

solve for I

$$I = \frac{V_s}{R_1 + R_2}$$

$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V_s$$

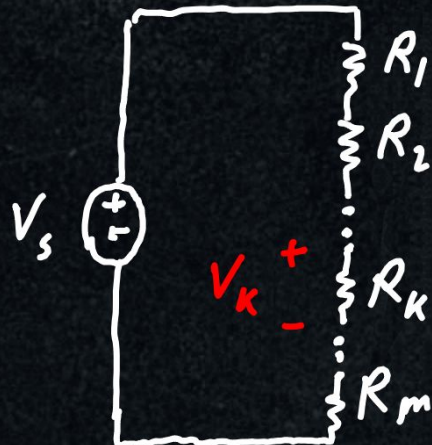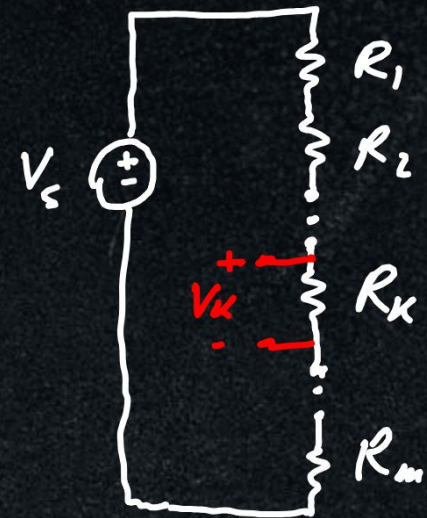
$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V_s$$



$k = 3, 4, \dots, m-1$

$$V_k = \frac{R_k}{R_1 + R_2 + \dots + R_m} \cdot V_s$$

Current Divider

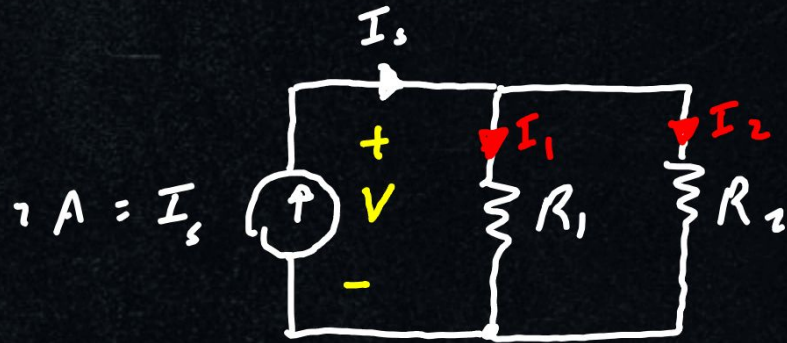

$$V = R_1 I_1 = R_2 I_2 = \overbrace{(R_1 \parallel R_2)}^{R_{eq}} I_s$$

$$I_1 = \frac{R_{eq}}{R_1} \cdot I_s$$


$$I_2 = \frac{R_{eq}}{R_2} \cdot I_s$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I_s$$


$$k = 3, 4, \dots, m-1$$

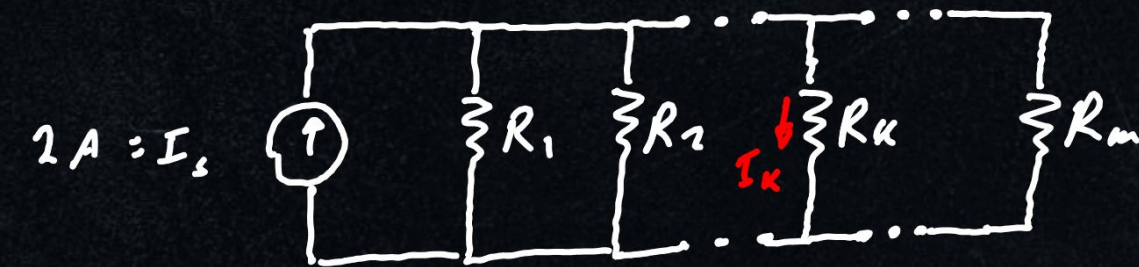

$$I_k = \frac{R_{eq}}{R_k} \cdot I_s, \quad R_{eq} = R_1 \parallel R_2 \parallel \dots \parallel R_m$$

$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m}}$$

EX:

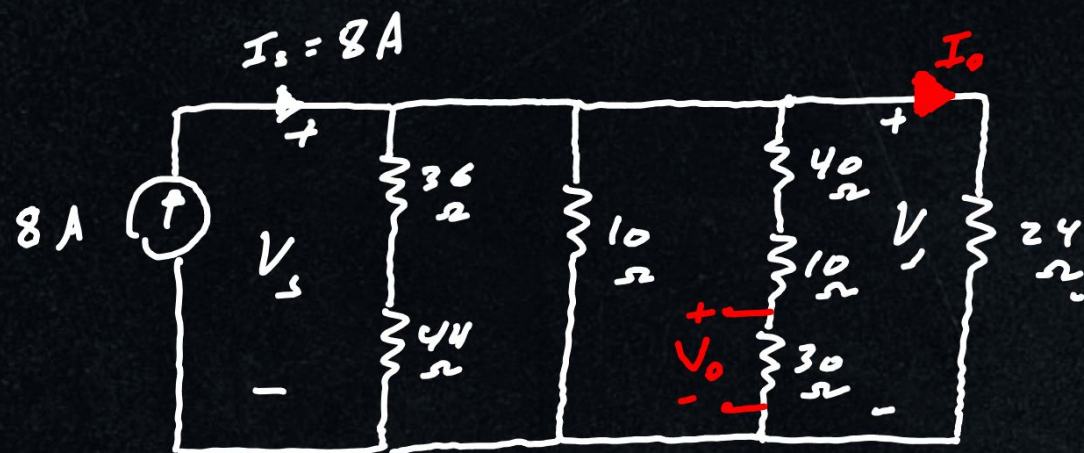

Find $I_o + V_o$??
using voltage +
current divider.

$$I_o = \frac{R_{eq}}{24} \cdot I_s ; R_{eq} = (36+44) // 10 // (40+10+30) // 24$$

$$R_{eq} : 80 // 10 // 80 // 24 = \frac{1}{\frac{1}{80} + \frac{1}{10} + \frac{1}{80} + \frac{1}{24}} = 6\Omega$$


$$I_o = \frac{6}{24} (8) = \boxed{2A}$$

$$V_o = \frac{30}{30+10+40} \cdot V_s ; V_s = 8 R_{eq} = 2(24) = 48V$$


$$\Rightarrow V_o = \frac{30}{80} \cdot 48 = \boxed{18V}$$

Delta - Wye Equivalent Circuits

Y-connection

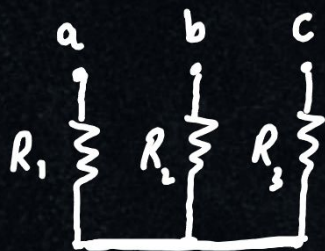


$\Leftrightarrow$

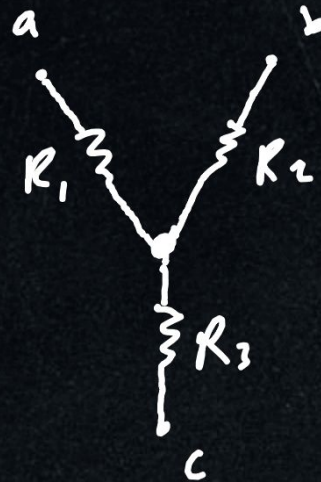


Y or star connection




Δ-connection

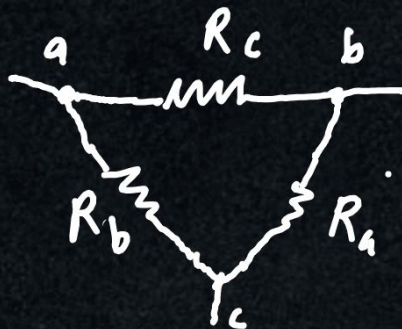


$\Leftrightarrow$

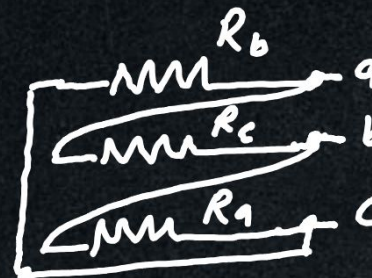

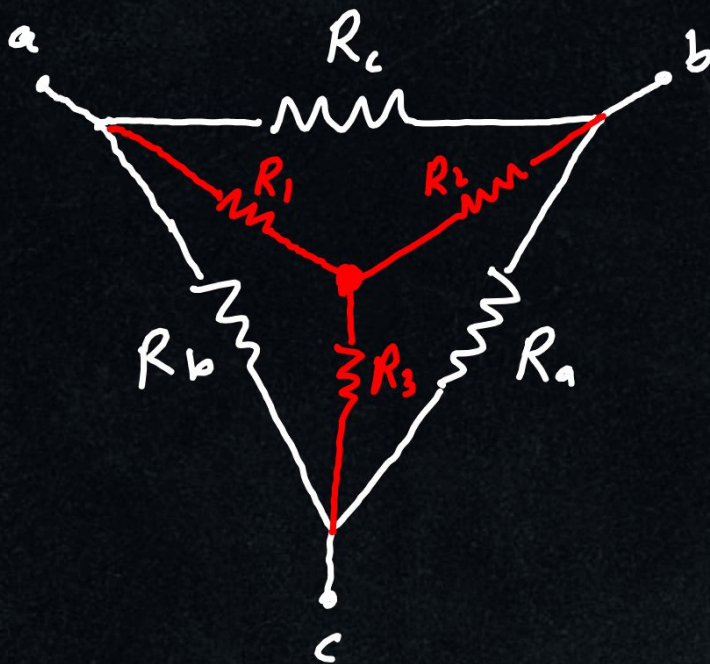

γ - Δ Transformation

Δ - γ Transformation

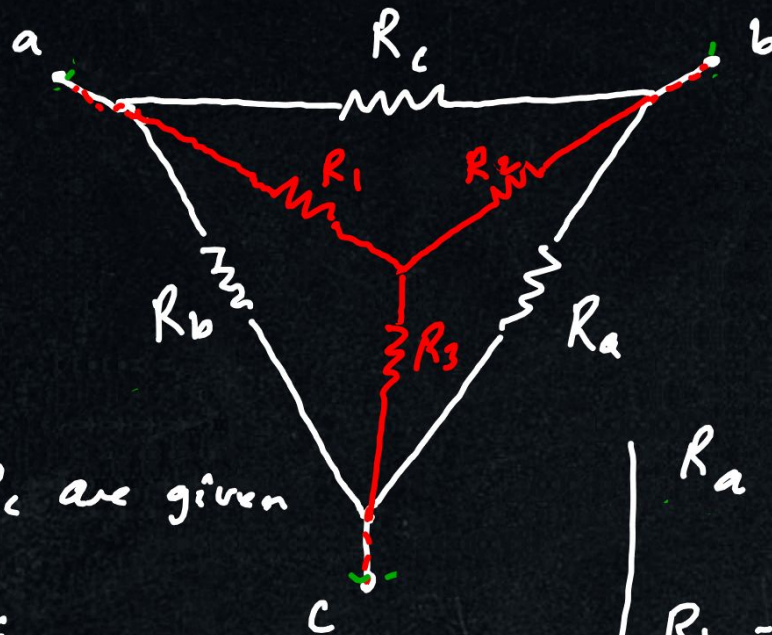

$\Delta \rightarrow \gamma$

$R_a, R_b \text{ \& } R_c$ are given

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} \quad , \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_{ab} = R_1 + R_2 = (R_a + R_b) \parallel R_c$$

$$R_{bc} = R_2 + R_3 = (R_b + R_c) \parallel R_a$$

$$R_{ca} = R_1 + R_3 = (R_a + R_c) \parallel R_b$$


$\gamma \rightarrow \Delta$ $R_1, R_2 \text{ \& } R_3$ are given

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

EX :- Calculate I

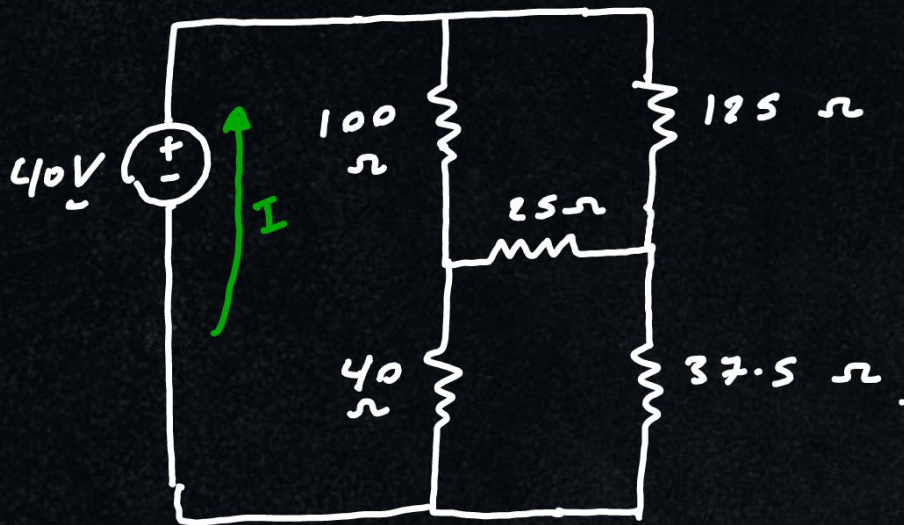

EX

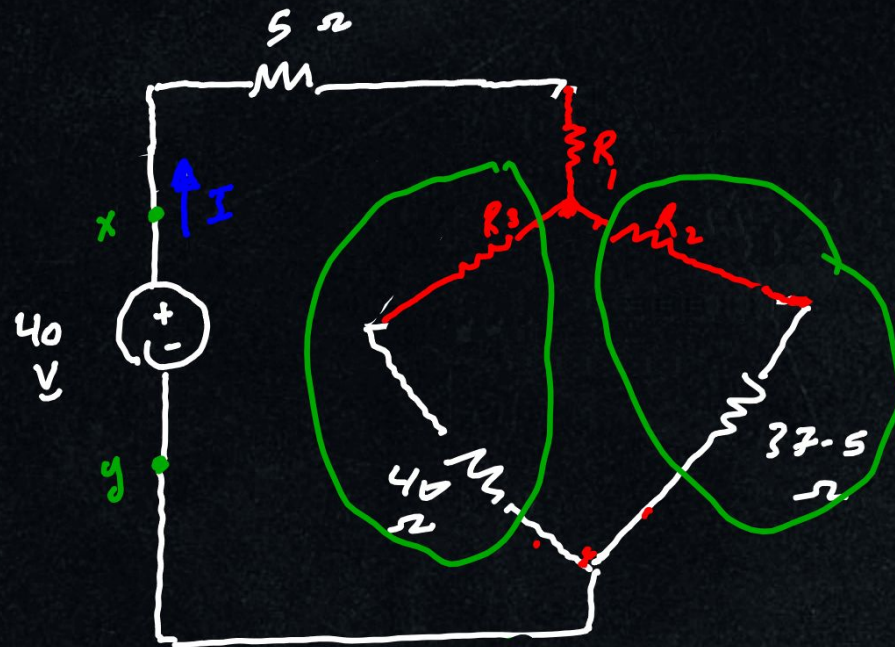


calculate I ?

$$R_1 = \frac{100(125)}{250} = 50 \Omega$$

$$R_2 = \frac{125(25)}{250} = 12.5 \Omega$$
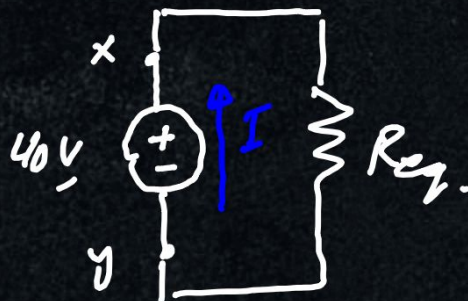
$$R_3 = \frac{100(25)}{250} = 10 \Omega$$



$$I = \frac{40}{R_{eq}}$$

$$R_{eq} = [(12.5 + 37.5) \parallel (10 + 40)] + 50 + 5$$

$$R_{eq} = 80 \Omega$$

$$I = \frac{40}{80} = 0.5 A$$