

Question 2: The phase shift between the current and the input voltage is shown in the below figure for a series RLC circuit driven by a sinusoidal wave. If the inductance $L = 3 \text{ mH}$ and the resistance $R = 2 \text{ k}\Omega$ then the capacitance is

