

# Oscillators

# Oscillators

## Role of oscillators:

\*oscillators are used to generate signal

\*it converts power from the dc power supply into an ac power

**Harmonic oscillators → sinusoidal wave form**

**Relaxation oscillators → produce non sinusoidal**

## They are used in :

**1. Electronic Communication Devices .**

**2. Lab.**

# Oscillators


**For the circuit to operate as an oscillator it must satisfy the Barkhausen criterial for sustained oscillation.**

**#1-The feedback must be positive ,this means that the feedback signal must be phased so that it adds to the amplifiers input signal .**

**#2-The loop gain (AB) must be greater than unity to allow oscillation to build up and equal to unity to sustain the oscillation .**

# Audio frequency Oscillators


## 1) Phase-shift Oscillator

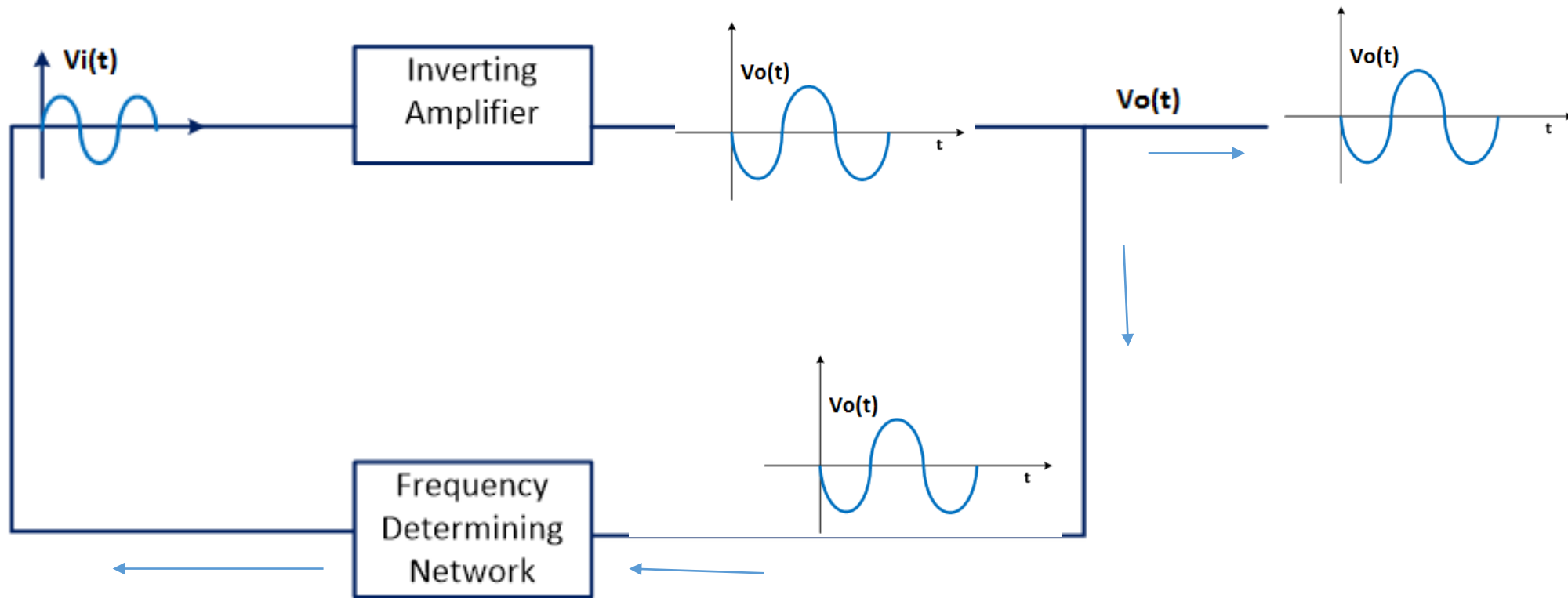

**180 phase shift at  $\omega_0$**

# Audio frequency Oscillators

## 1) Phase-shift Oscillator

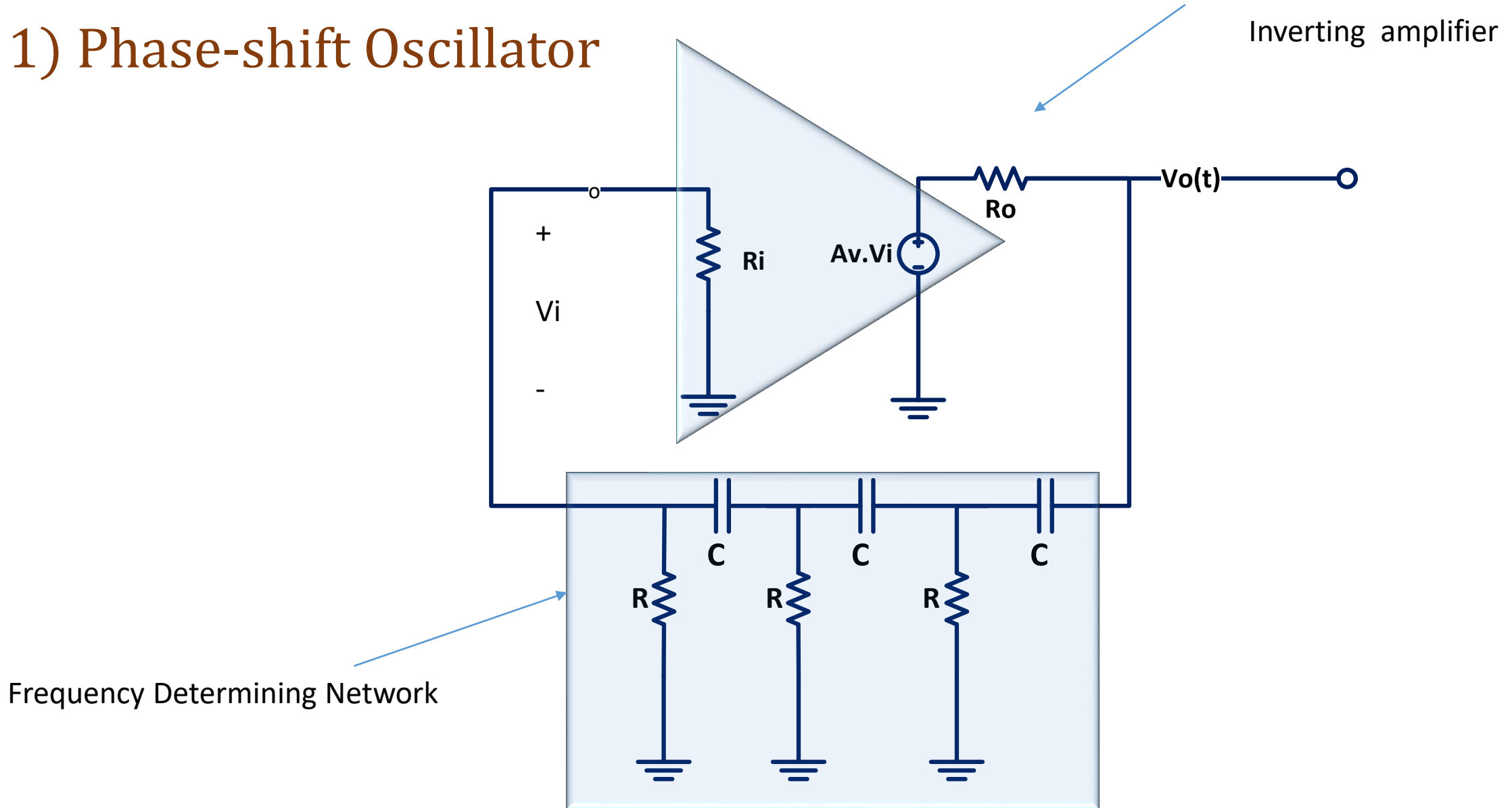

# Oscillators

## 1) Phase-shift Oscillator


To find  $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$(R - j\frac{1}{\omega C}) I_1 - RI_2 = V_i$$


$$-RI_1 + (2R - j\frac{1}{\omega C}) I_2 - RI_3 = 0$$

$$-RI_3 + (2R - j\frac{1}{\omega C}) I_3 = 0$$
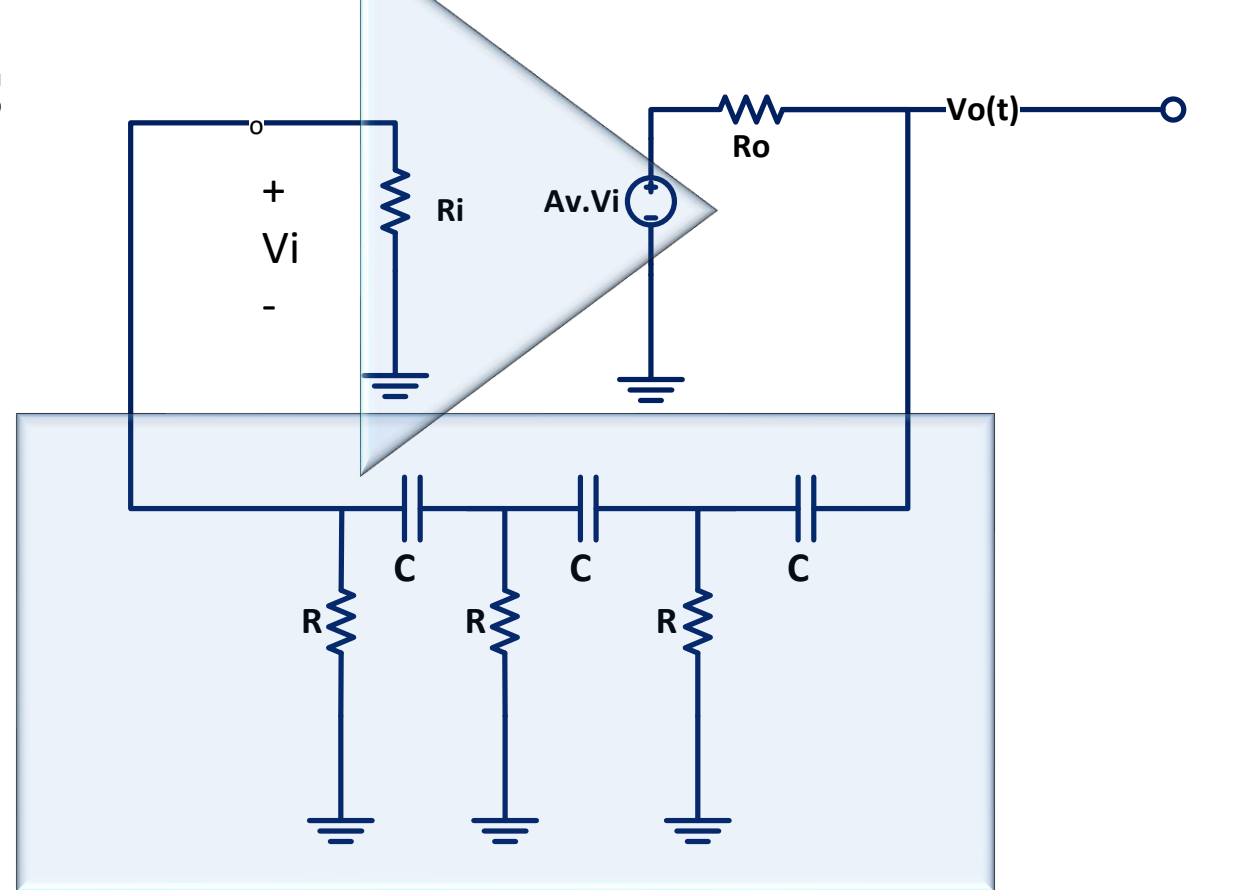
$$I_3 = \frac{R^2 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C})}$$



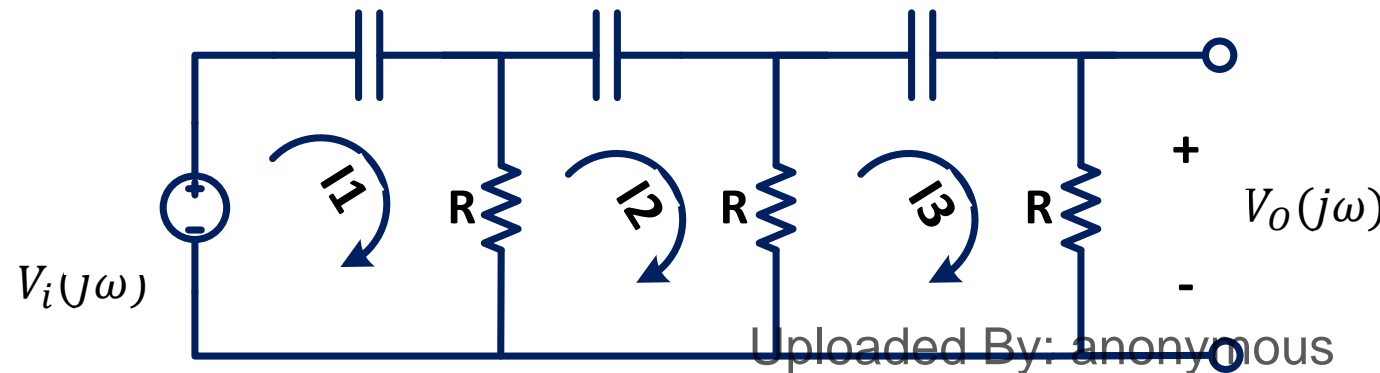$1/j\omega C$     $1/j\omega C$     $1/j\omega C$     $R_i \gg R$




# Oscillators

## 1) Phase-shift Oscillator


To find  $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$I_3 = \frac{R^2 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j\left(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C}\right)}$$
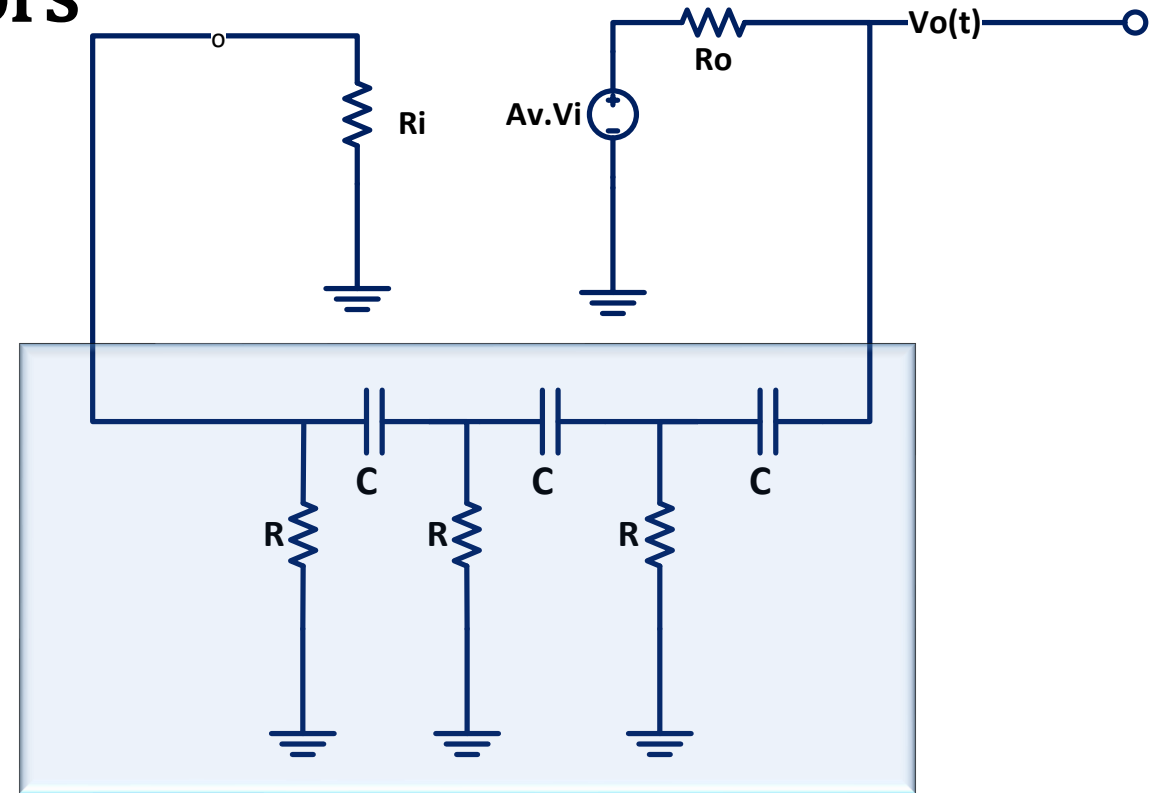
$$V_o = \frac{R^3 V_i}{R^3 - \frac{5R}{\omega^2 C^2} + j\left(\frac{1}{\omega^3 C^3} - \frac{6R^2}{\omega C}\right)}$$



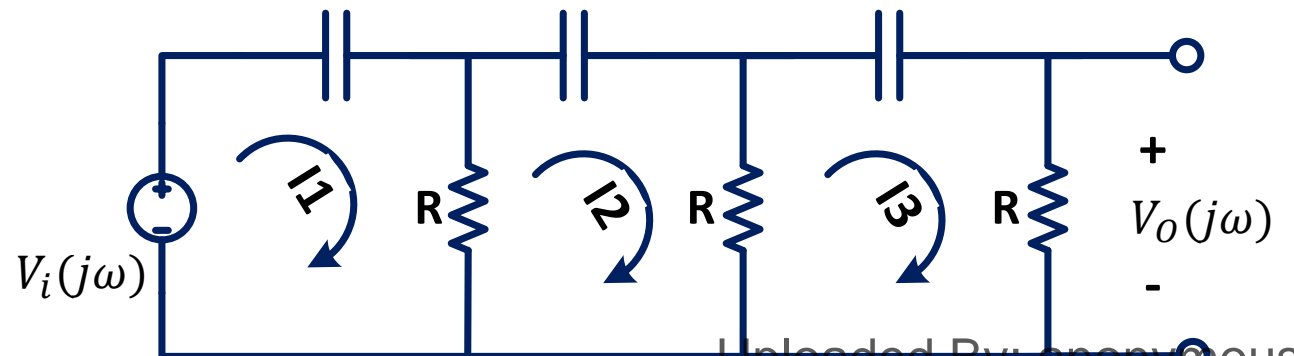$1/j\omega C$      $1/j\omega C$      $1/j\omega C$




# Audio frequency Oscillators

## 1) Phase-shift Oscillator

To find  $\beta(j\omega) = \frac{V_O(j\omega)}{V_i(j\omega)}$

$$\beta = \frac{V_O(j\omega)}{V_i(j\omega)}$$
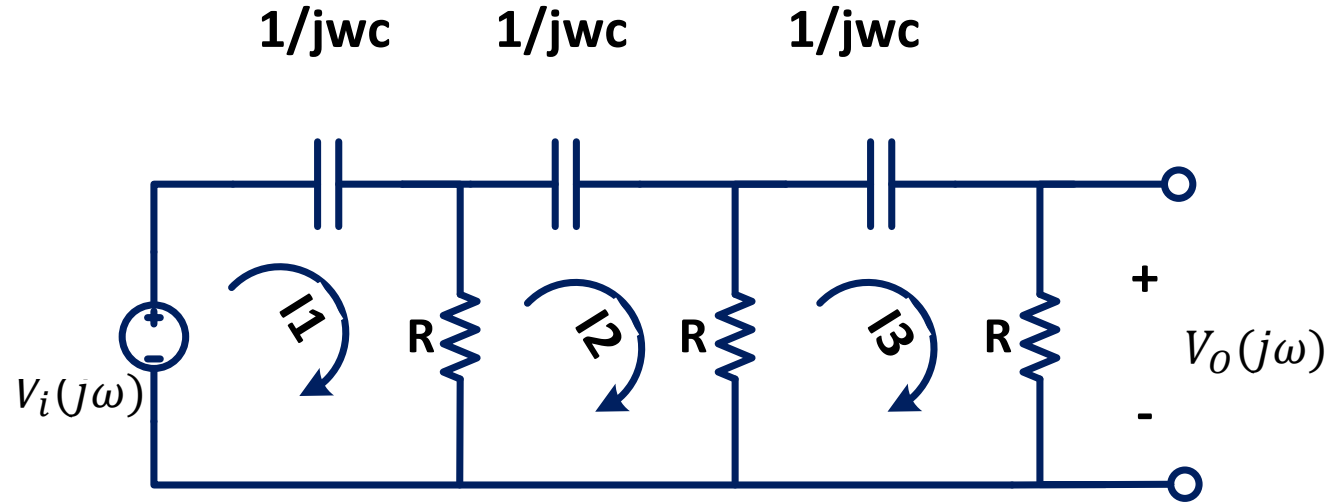
$$\beta(j\omega) = \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2}\right) + j\left(\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR}\right)}$$



At  $\omega_o$  ;  $\beta(j\omega)$  must be real and negative

$$\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR} = 0$$


$$\therefore \omega_o = \frac{1}{\sqrt{6} RC}$$



# Audio frequency Oscillators
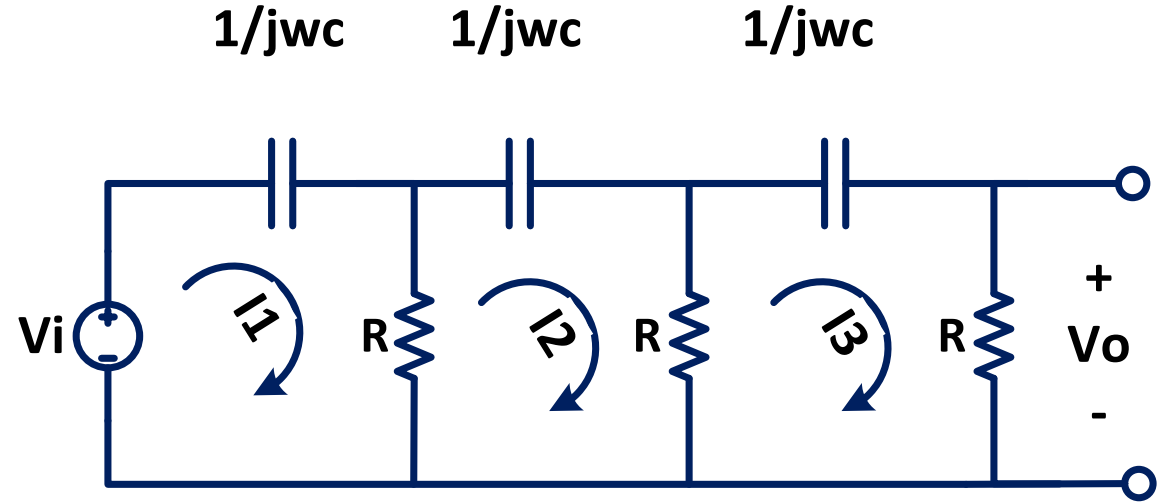
## 1) Phase-shift Oscillator

To find  $\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$



$$\beta(j\omega) = \frac{1}{\left(1 - \frac{5}{\omega^2 C^2 R^2}\right) + j\left(\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR}\right)}$$

At  $\omega_0$   $\beta(j\omega) = -\frac{1}{29} = \frac{1}{29} \angle 180$

$\therefore A_V \geq 29 \angle 180$

$A_V \beta \geq 1 \angle 0$


# Audio frequency Oscillators

## 1) Phase-shift Oscillator

$$f_o = \frac{1}{2\pi\sqrt{6}RC} = 197\text{Hz}$$


$$A_V = - \left( \frac{R_2 + R_3}{R_1} \right) = \begin{cases} -33.9 \\ -27.6 \end{cases}$$

$$A_V \leq -29$$

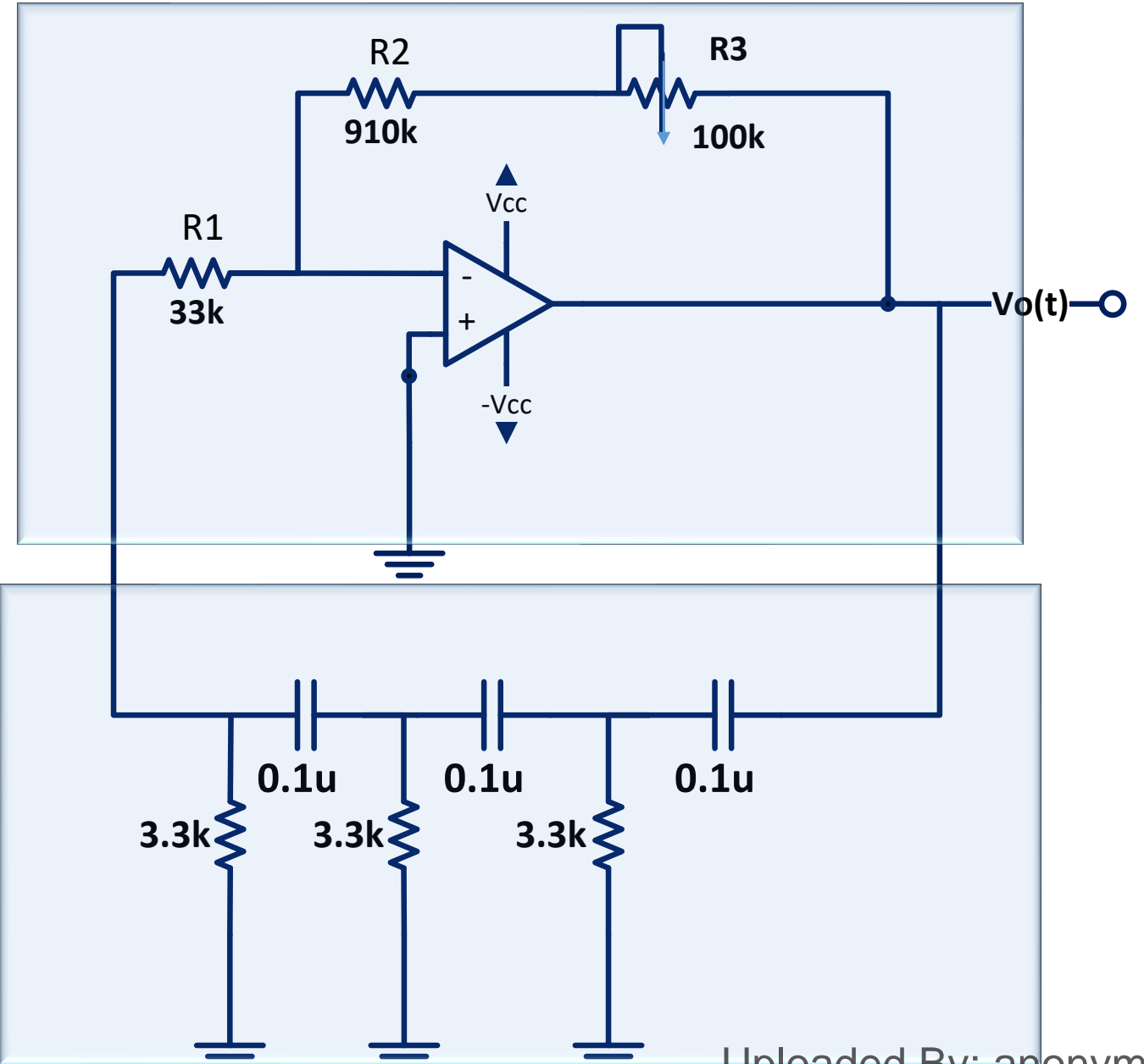

# Audio frequency Oscillators



## 2- Wien Bridge Oscillator

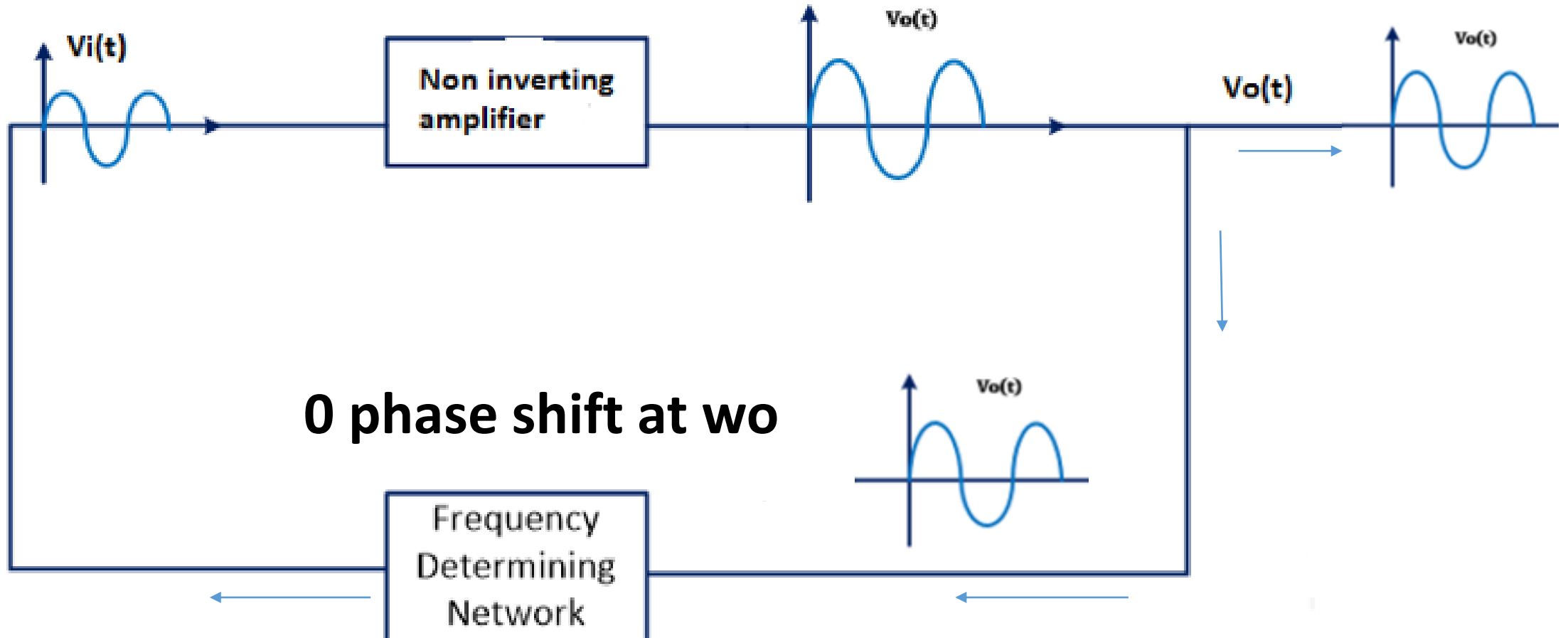

# Audio frequency Oscillators
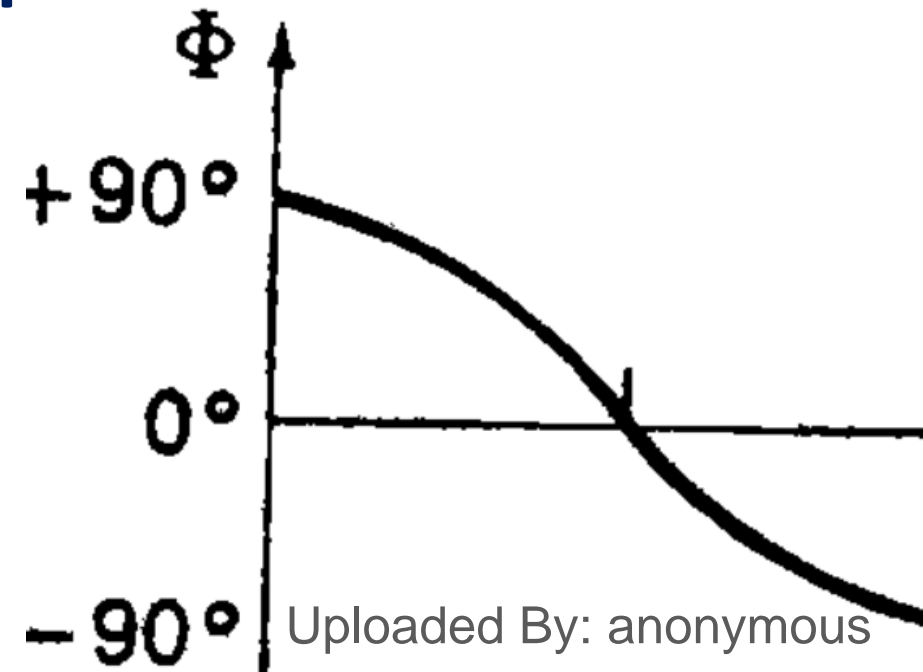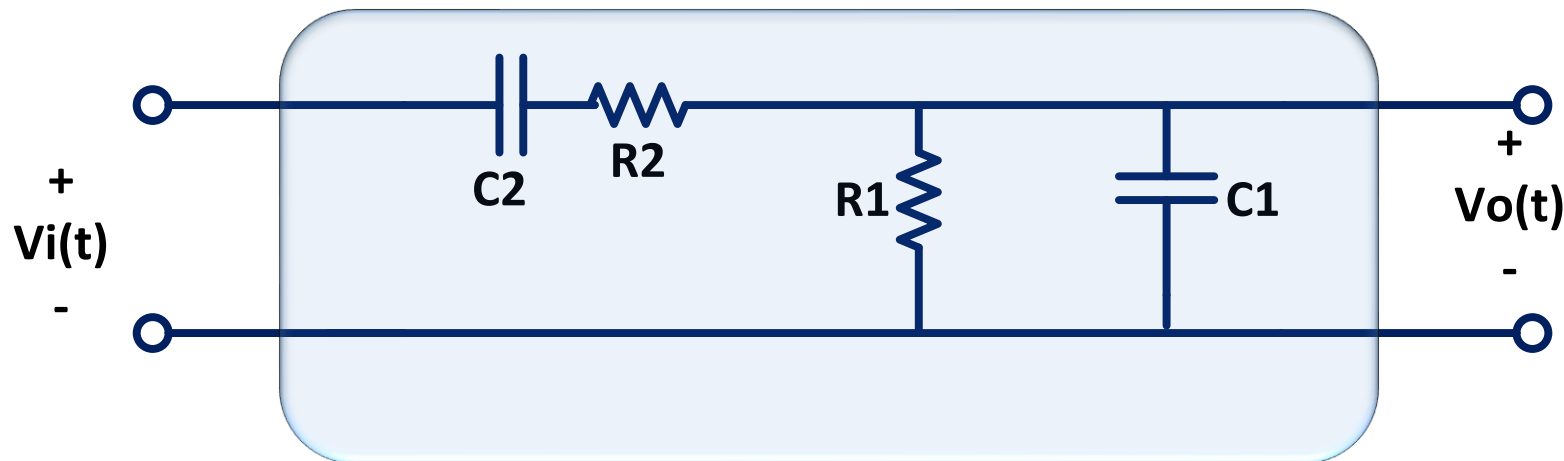
## 2- Wien Bridge Oscillator

- The Wien bridge oscillator employs a lead-lag network.
- At one particular frequency, the phase shift across the network is 0, therefore the feedback network is connected to the Op.Amp's noninverting input terminal.



# Audio frequency Oscillators

## 2- Wien Bridge Oscillator

$$Z_1 = R_1 \parallel \frac{1}{j\omega C_1} = \frac{R_1}{1+jR_1\omega C_1}$$


$$Z_2 = R_2 + \frac{1}{j\omega C_2}$$

$$\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_1}{Z_1+Z_2}$$

$$\beta(j\omega) = \frac{\omega R_1 C_2}{\omega(R_1 C_1 + R_2 C_2 + R_1 C_2) + j(\omega^2 R_1 R_2 C_1 C_2 - 1)}$$

At  $\omega_o$  ;  $\beta(j\omega)$  must be real and positive


$$\omega^2 R_1 R_2 C_1 C_2 - 1 = 0$$

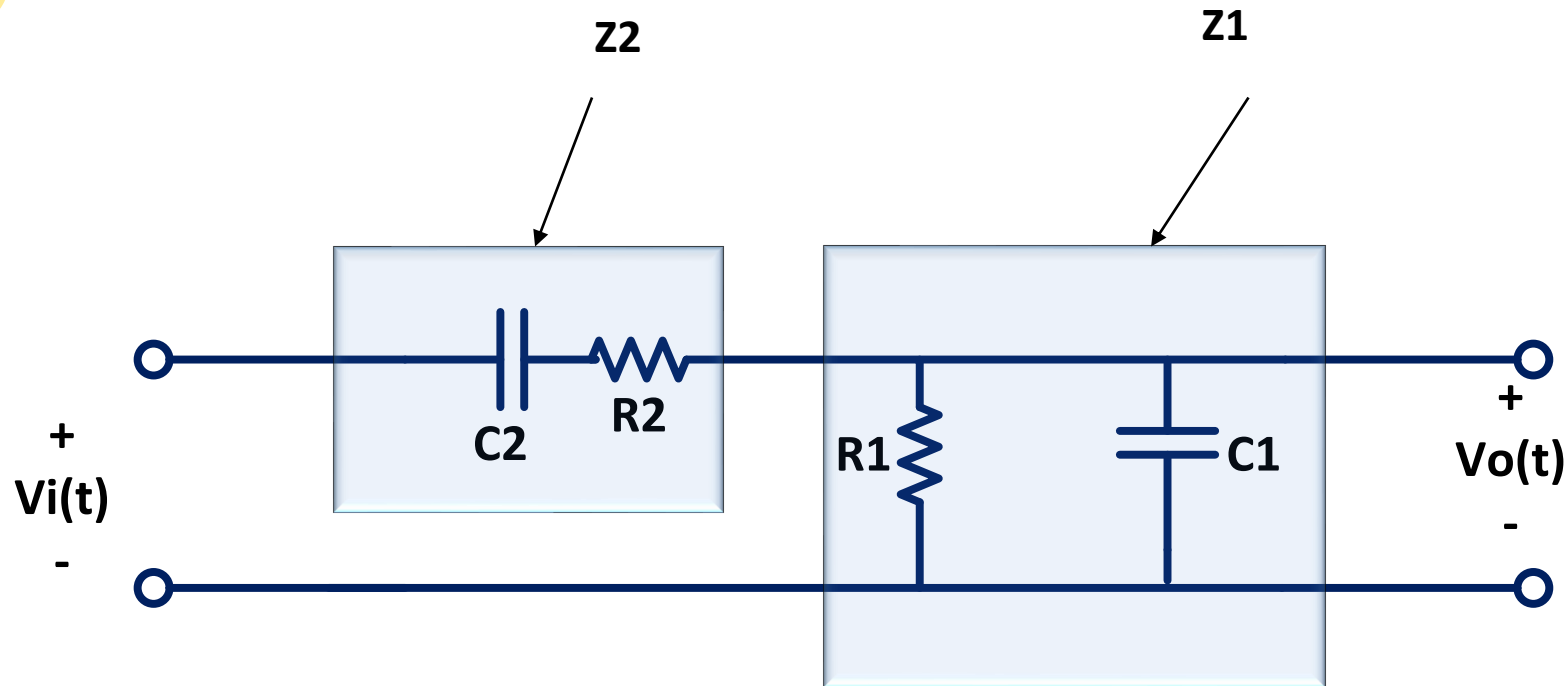

# Audio frequency Oscillators
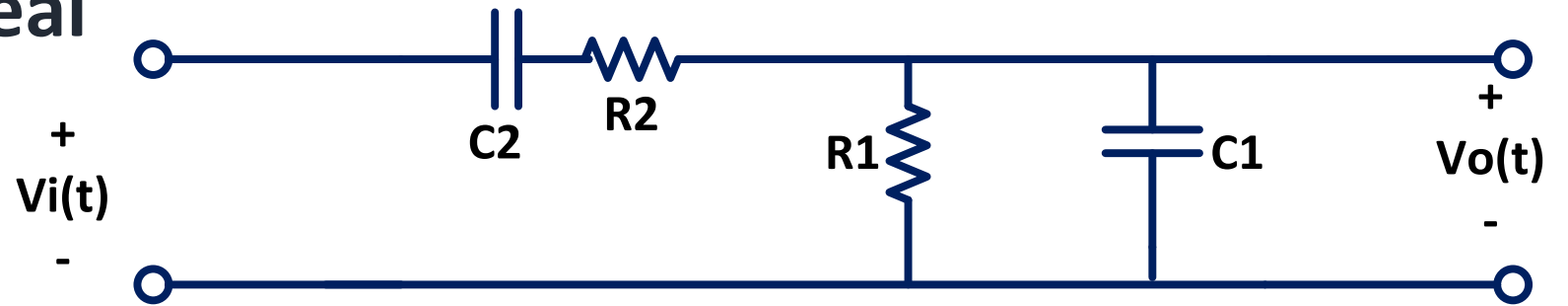
## 2- Wien Bridge Oscillator

At  $\omega_o$  ;  $\beta(j\omega)$  must be real and positive



$$\therefore \omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\text{At } \omega_o ; \beta(j\omega) = \frac{1}{1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}}$$

- If  $R_1 = R_2 = R$ ; and  $C_1 = C_2 = C$

$$\omega_o = \frac{1}{RC}$$

$$\beta = \frac{1}{3} = \frac{1}{3} \angle 0$$

$$\therefore A_v \geq 3 \angle 0$$

$$A_v \beta \geq 1 \angle 0$$

# Audio frequency Oscillators

## 2- Wien Bridge Oscillator

Frequency Determining Network


Since  $C1 = C2$  and  $R1 = R2$

$$- f_o = \frac{1}{2\pi RC} = 1.06\text{KHz}$$

$$\beta = \frac{1}{3}$$

$$\therefore A_v \geq 3$$
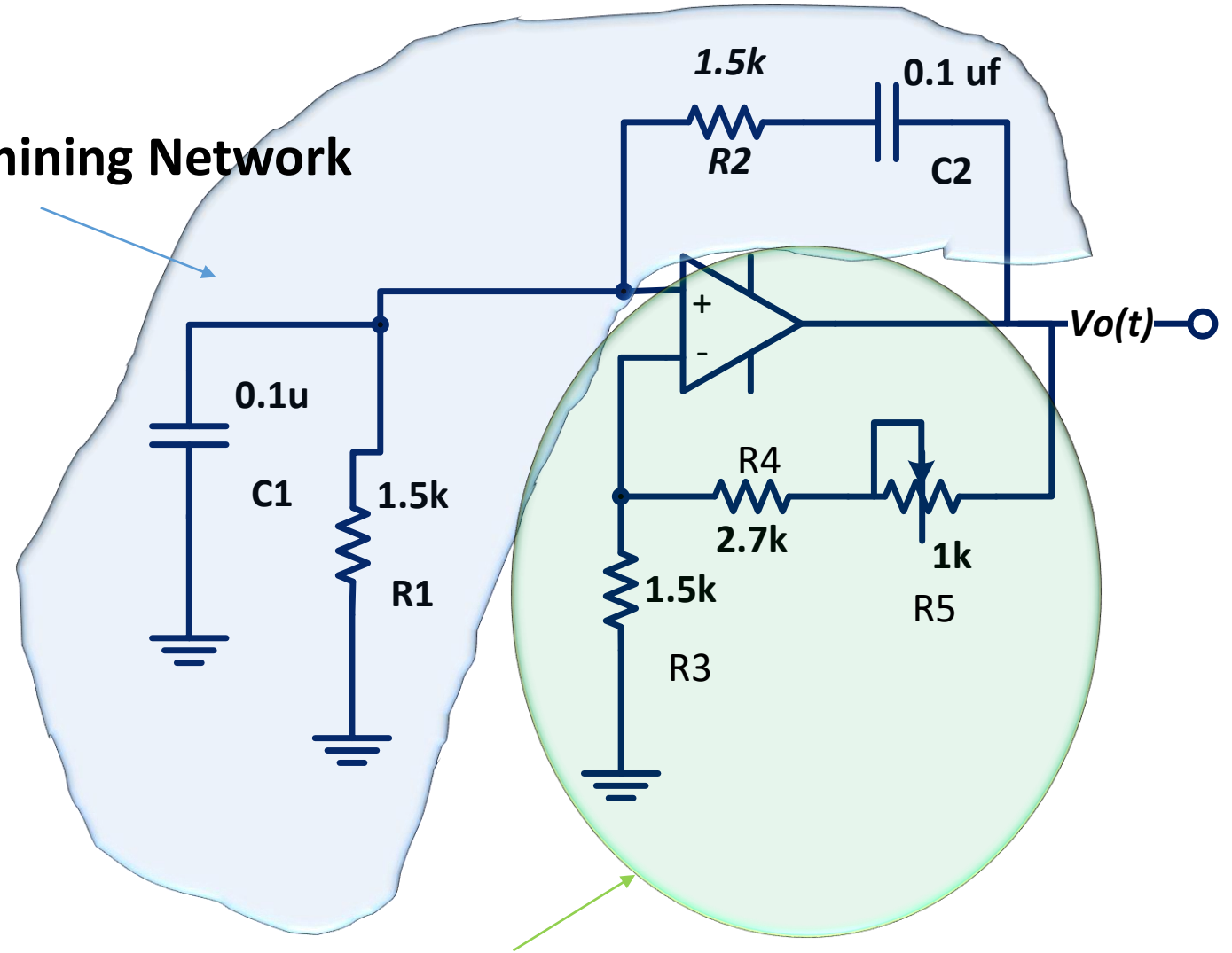
$$A_v = 1 + \frac{R_4 + R_5}{R_3} = \begin{cases} 2.8 \\ 3.47 \end{cases}$$



Non Inverting Amplifier

# Audio frequency Oscillators

## Adaptive Negative Feedback

At the beginning


D1,D2 are off to build up the oscillation

$$A_v = 1 + \frac{R_4}{R_3} = 3.2 > 3$$

Later on D1,D2 are on

$$A_v = 1 + \frac{R_4 // R_5}{R_3} = 3$$


$$\beta = \frac{1}{3}$$

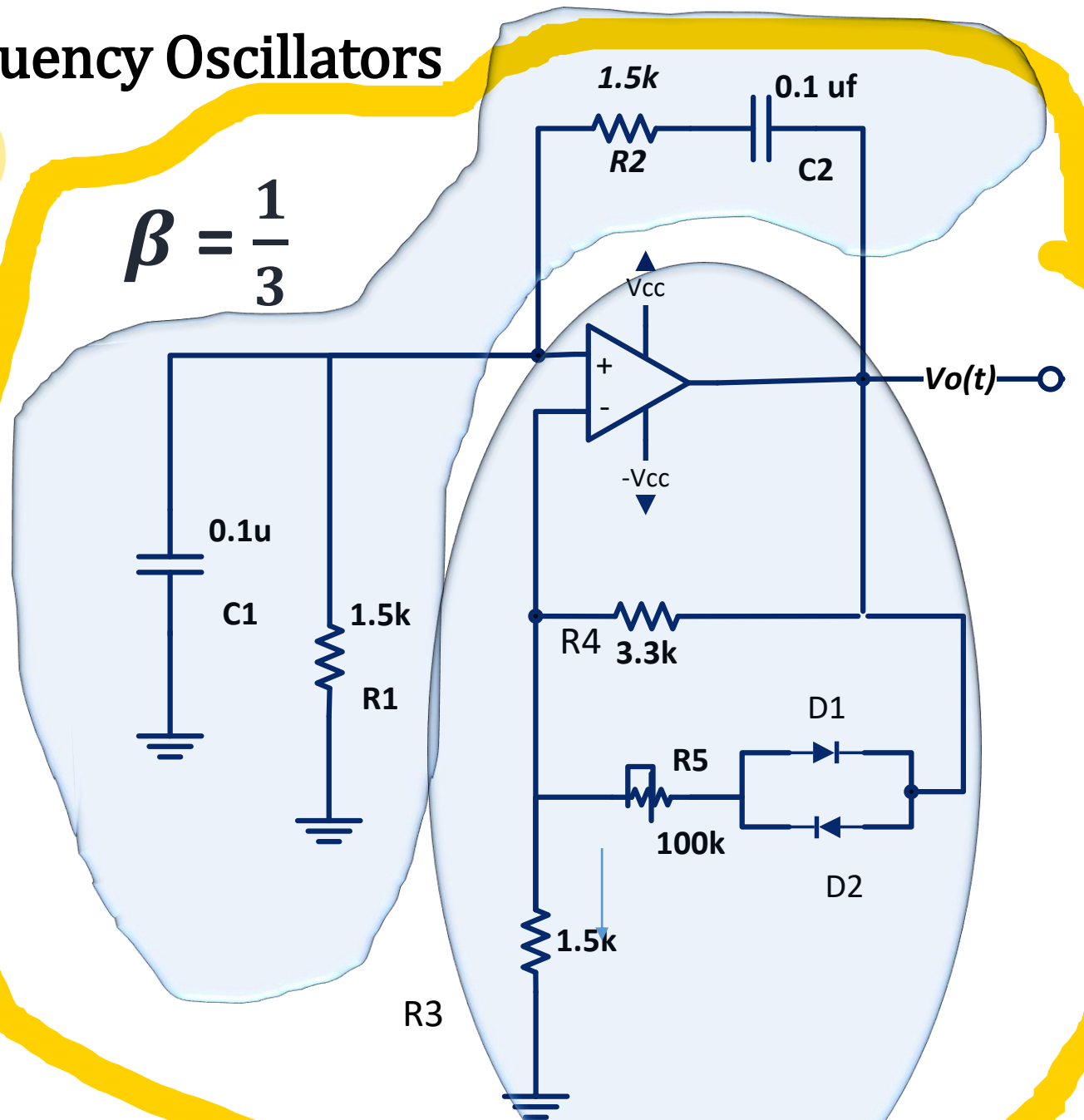




# High Frequency Harmonic Oscillators

## General LC Oscillator

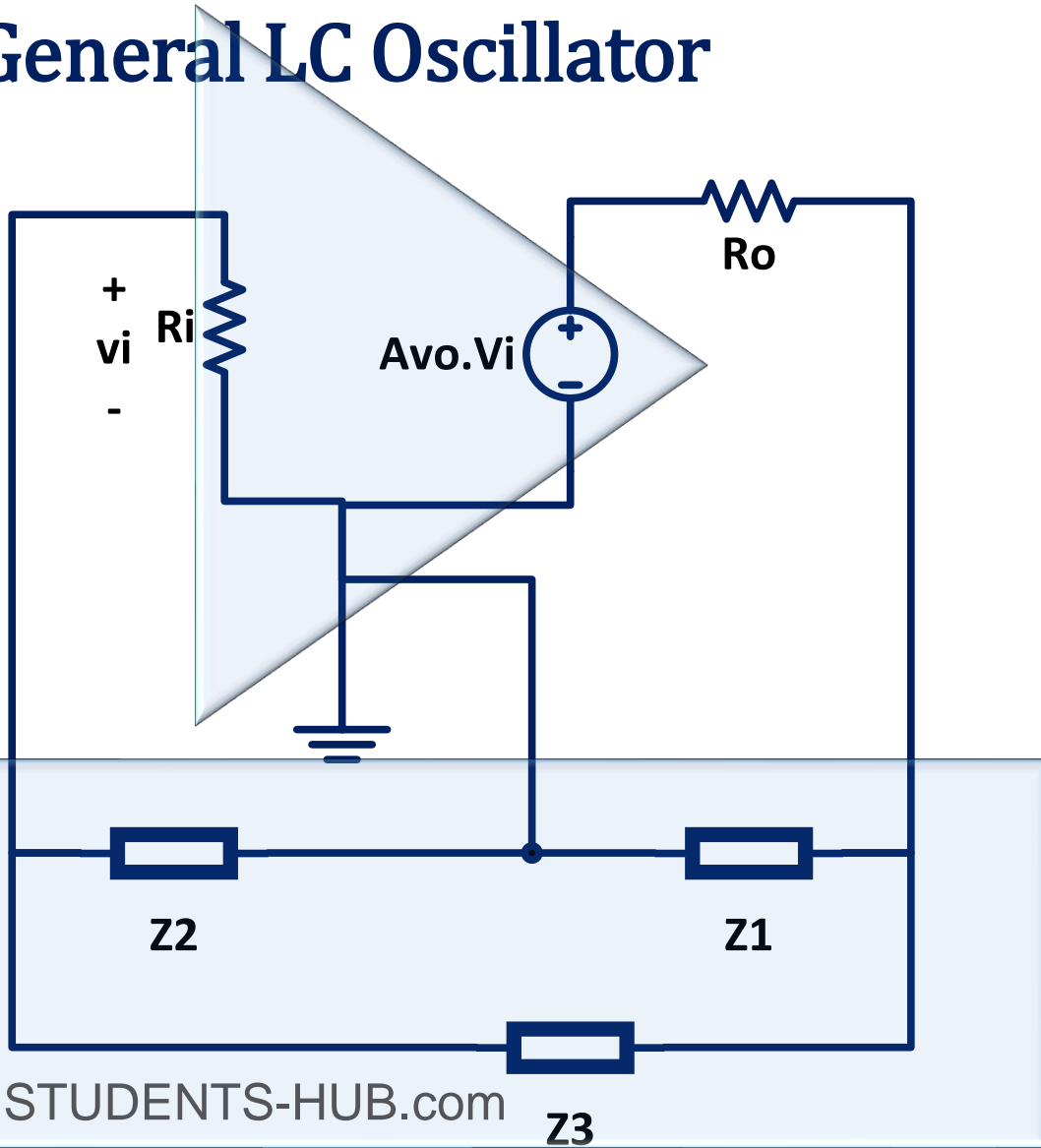

## The feedback network

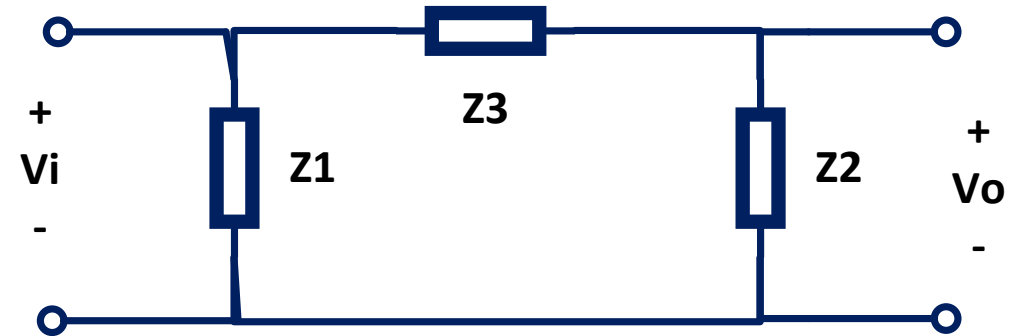

$$R_i \gg Z_2$$

$$\beta(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_2}{Z_2 + Z_3}$$


**$Z_1$  ,  $Z_2$  , and  $Z_3$  are pure reactive impedances**

# High Frequency Harmonic Oscillators

ZL

## General LC Oscillator

To determine  $A_v$

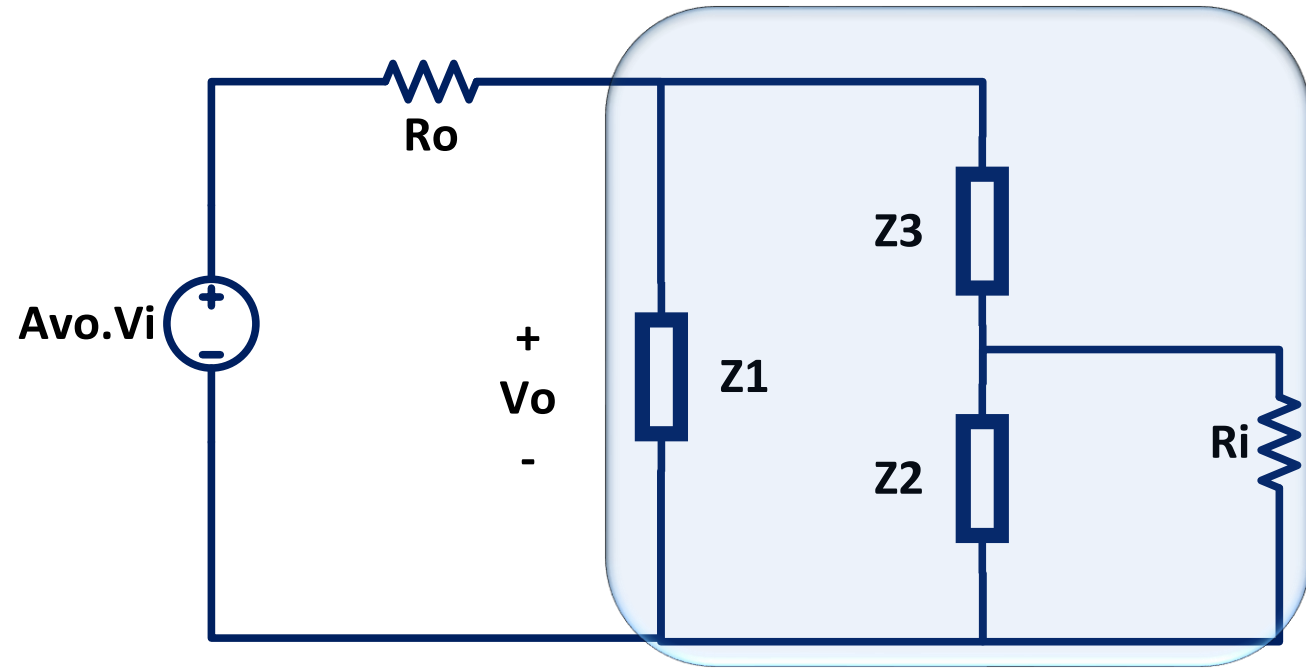

$$A_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_l}{Z_l + R_o} A_{vo} V_i$$

$$Z_l = Z_1 \parallel (Z_2 + Z_3)$$

$$\therefore A_v(j\omega) = \frac{Z_1 (Z_2 + Z_3) A_{vo}}{Z_1 (Z_2 + Z_3) + R_o (Z_1 + Z_2 + Z_3)}$$

$$A_v \beta = \frac{Z_1 Z_2 A_{vo}}{Z_1 (Z_2 + Z_3) + R_o (Z_1 + Z_2 + Z_3)}$$

$R_i \gg Z_2$

$\therefore$  At  $\omega_o$

$$1. Z_1 + Z_2 + Z_3 = 0$$

$$2. A_v \beta = -\frac{Z_2}{Z_1} A_{vo}$$

$$A_v \beta \geq 1 \angle 0$$

$$\therefore A_{vo} \leq -\frac{Z_1}{Z_2}$$

$Z_1, Z_2$  and  $Z_3$  pure reactive impedances

# High Frequency Harmonic Oscillators

## Example of LC Oscillators

Oscillator type	Z1	Z2	Z3	Amplifier
Hartley	L	L	C	Inverting
	L	C	L	Follower
Colpitts	C	C	L	Inverting
	L	C	C	Non-Inverting
Clapp	C	C	LC	Inverting
Pierce crystal	C	C	XTAL	Inverting

# High Frequency Harmonic Oscillators

## Colpitts Oscillator

At  $\omega_o$ :

$$Z_1 + Z_2 + Z_3 = 0$$

$$-j \frac{1}{\omega_o C_1} - j \frac{1}{\omega_o C_2} + j\omega_o L = 0$$

$$\therefore \omega_o = \frac{1}{\sqrt{LC_T}}, \quad C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$f_o = \frac{\omega_o}{2\pi} = 1.02\text{MHz}$$


$$A_{vo} \leq -\frac{Z_1}{Z_2} = -\frac{C_2}{C_1}$$

$$A_{vo} \leq -2.06$$

$$C_1 = 330\text{pF}$$

$$C_2 = 680\text{pF}$$



$$L = 110\mu\text{H}$$

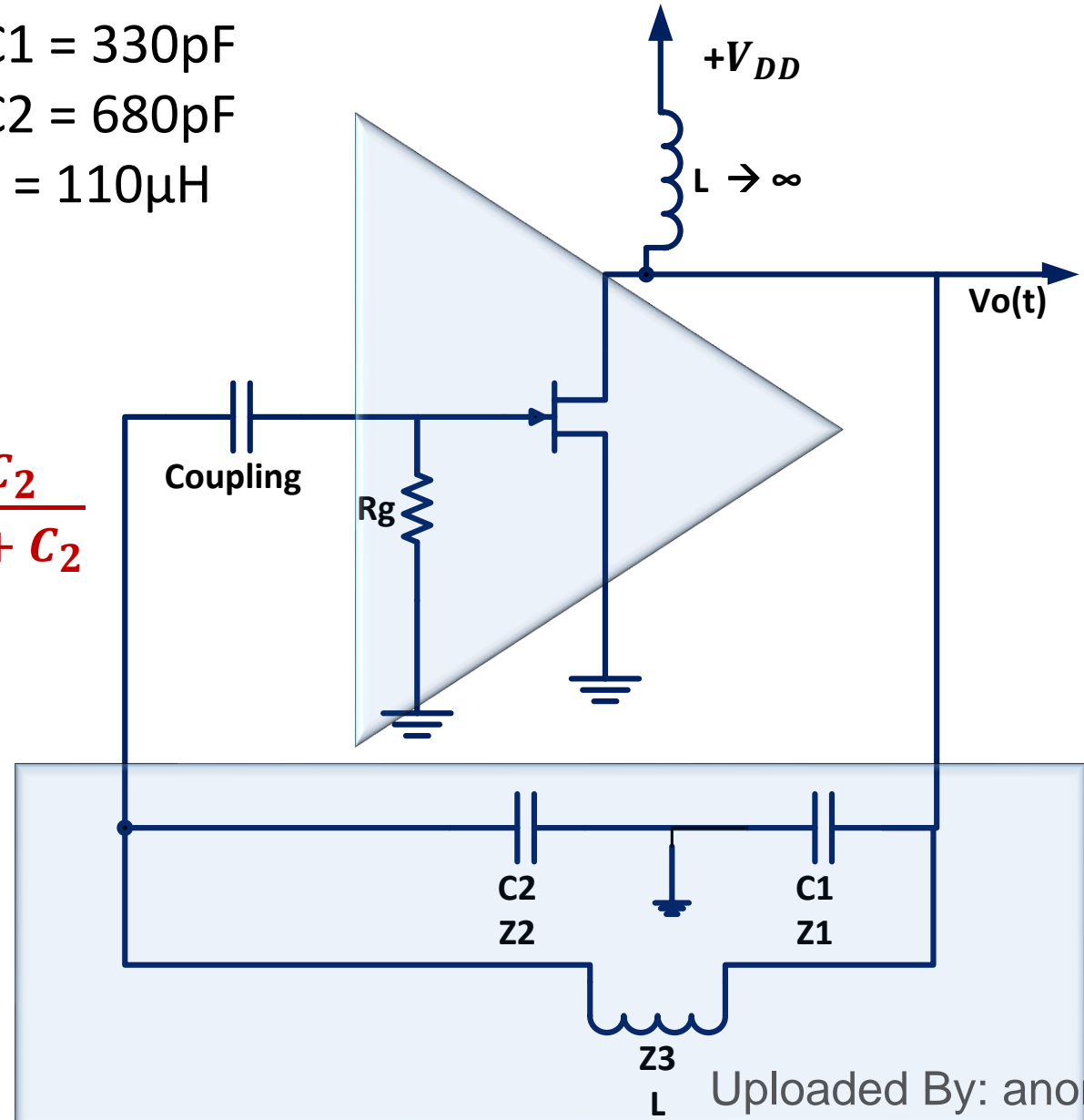

At high frequency

$$C1' = C1 + C_{om}$$

$$C2' = C2 + C_{gs} + C_{im}$$

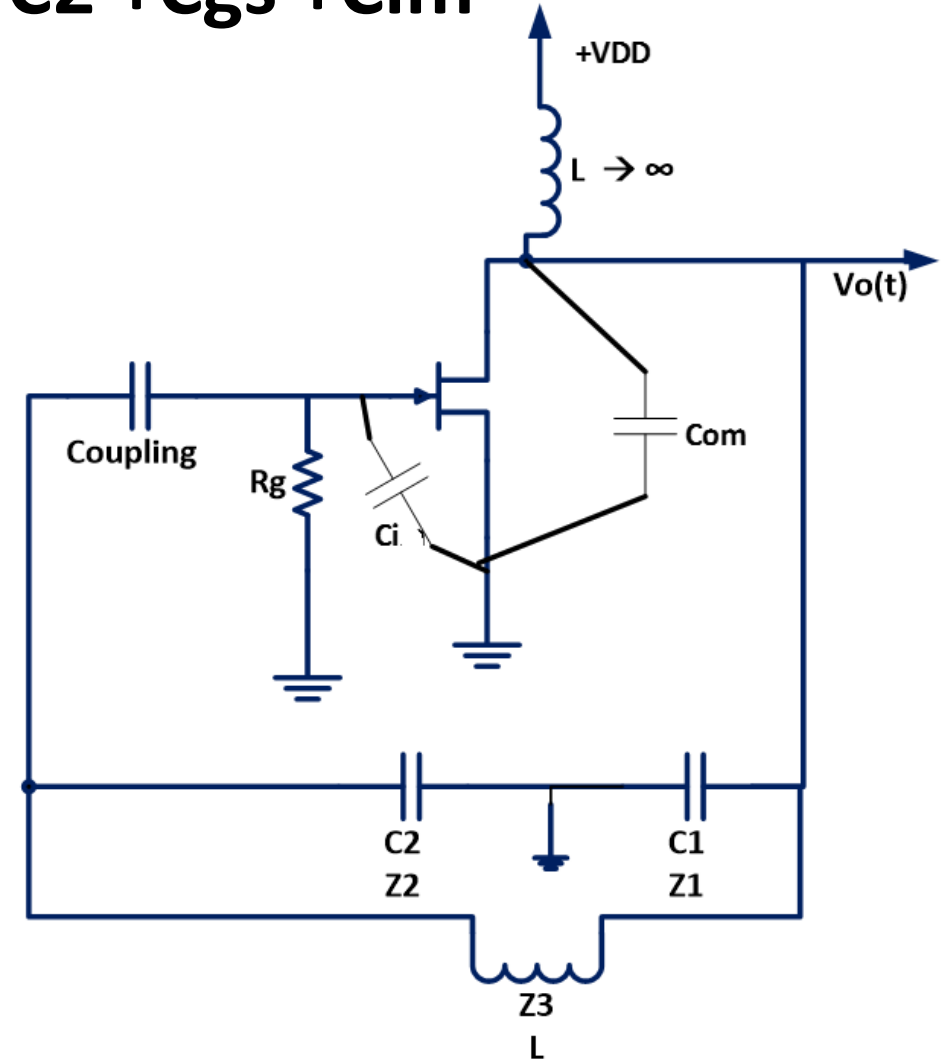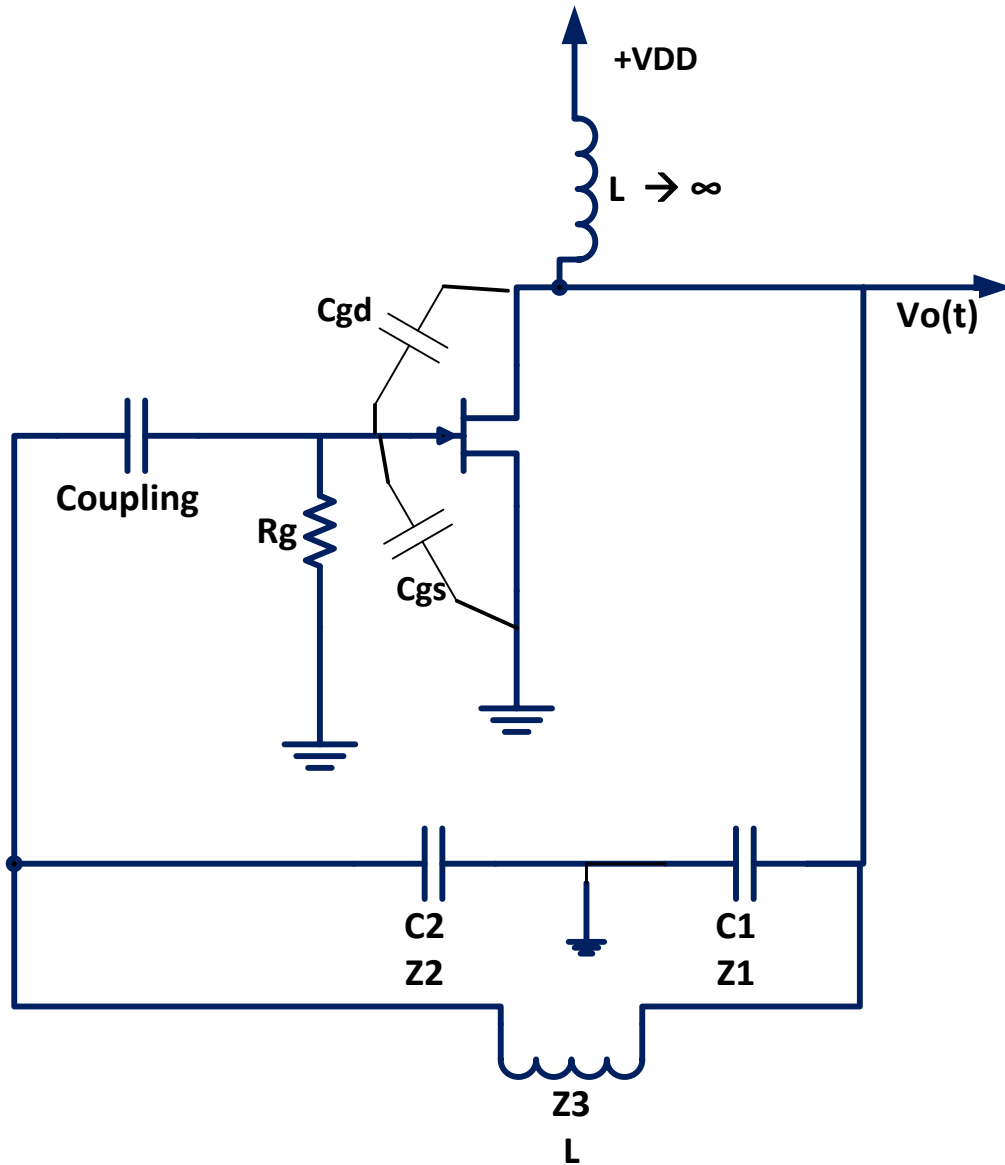

# High Frequency Harmonic Oscillators

## Clapp Oscillator

At  $\omega_0$

$$Z_1 + Z_2 + Z_3 = 0$$

$$-j \frac{1}{\omega_0 C_1} - j \frac{1}{\omega_0 C_2} - j \frac{1}{\omega_0 C_3} + j\omega_0 L = 0$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC_T}}$$


$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_T = 212.7 \text{PF}$$

$$f_o = \frac{\omega_0}{2\pi} = 1.04 \text{MHz}$$




$$A_{vo} \leq -\frac{Z_1}{Z_2} = -\frac{C_2}{C_1}$$

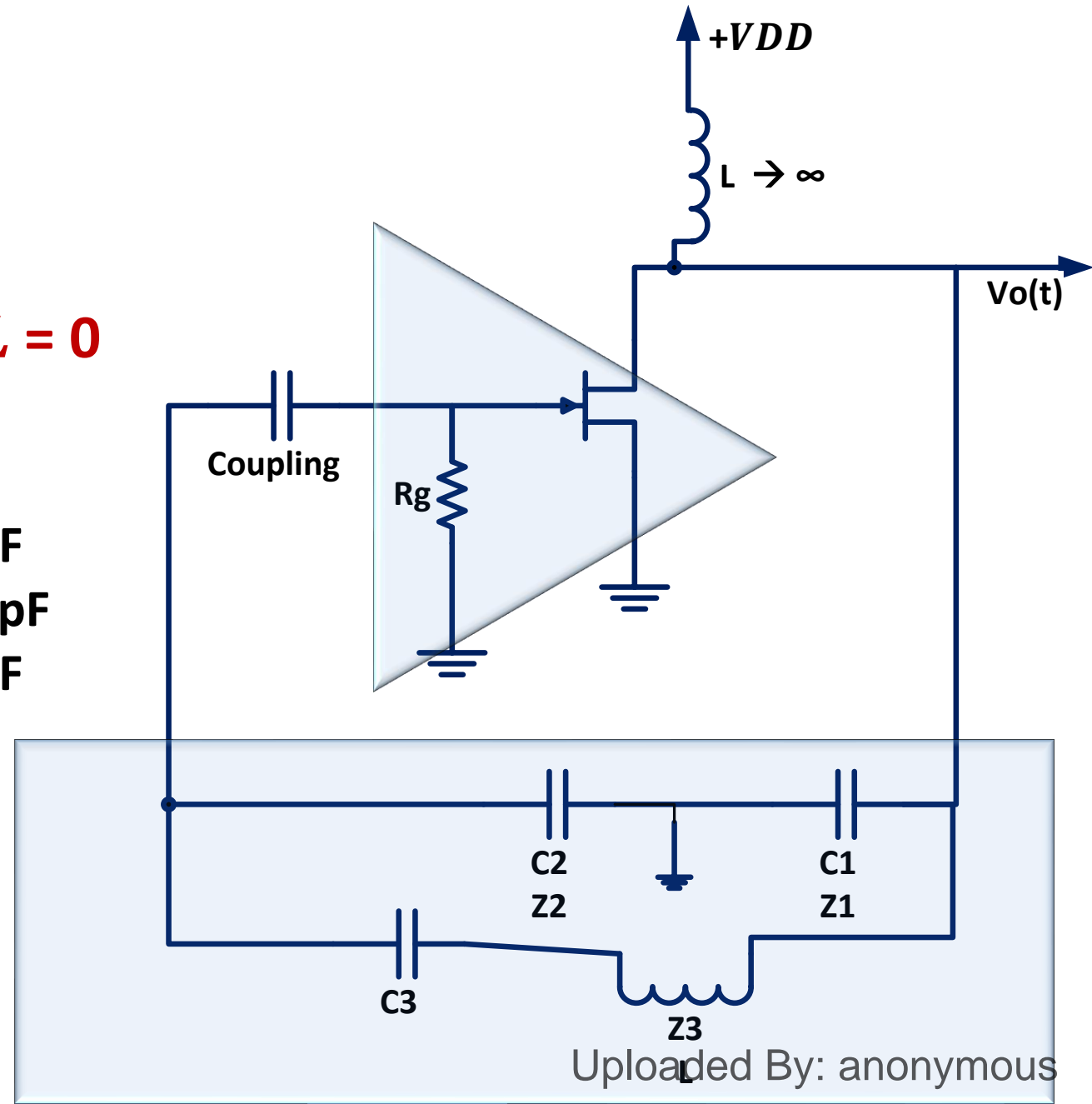$C_1 = 680 \text{pF}$   
 $C_2 = 1500 \text{pF}$   
 $C_3 = 390 \text{pF}$   
 $L = 110 \mu\text{H}$



# High Frequency Harmonic Oscillators

## The Crystal

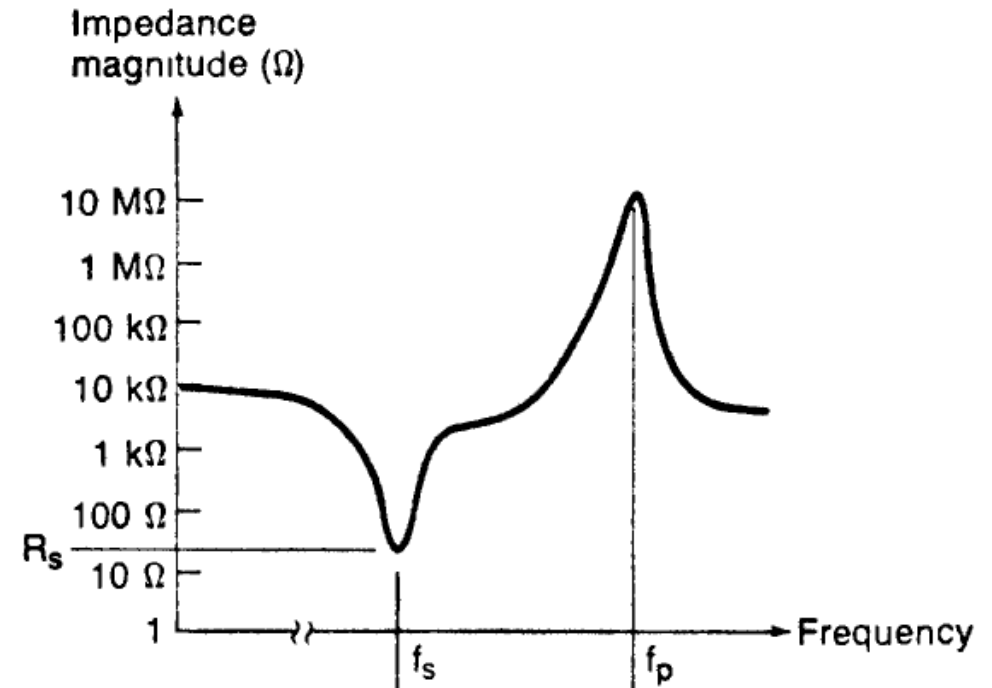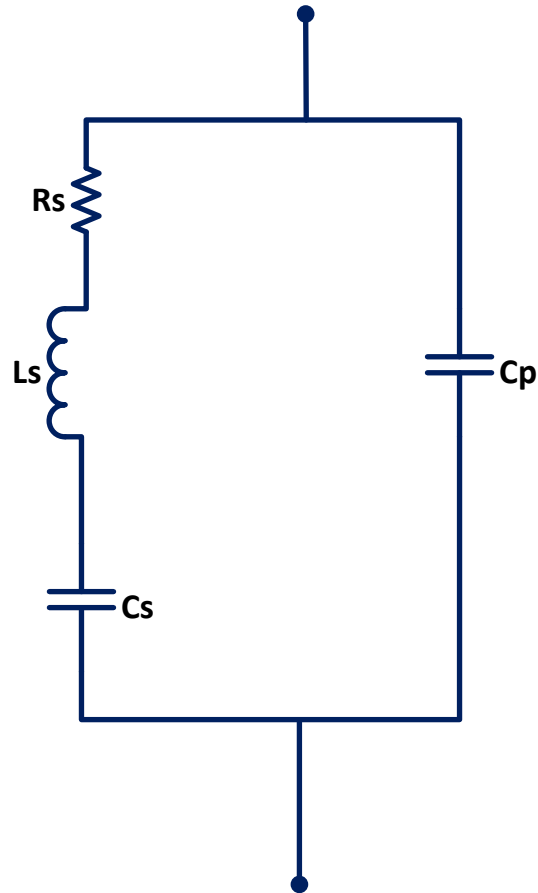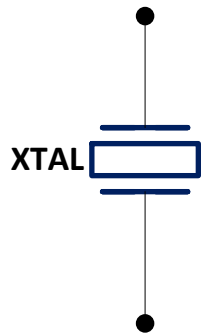

# Oscillators

## High Frequency Harmonic Oscillators

### The Crystal

$R_s$  is very small

$$Z(j\omega) = \frac{(j\omega L_s + \frac{1}{j\omega C_3}) \frac{1}{j\omega C_p}}{j\omega L_s + \frac{1}{j\omega C_3} + \frac{1}{j\omega C_p}}$$

$$Z(j\omega) = \frac{-j}{\omega C_p} \frac{\omega^2 - \frac{1}{L_s C_s}}{\omega^2 - \frac{C_s + C_p}{L_s C_s C_p}}$$


$$\omega^2 - \frac{1}{L_s C_s} = 0$$

$$\therefore \omega_s = \frac{1}{\sqrt{L_s C_s}}$$

Series resonance  
STUDENTS-HUB.com

$$\omega^2 - \frac{C_s + C_p}{L_s C_s C_p} = 0$$
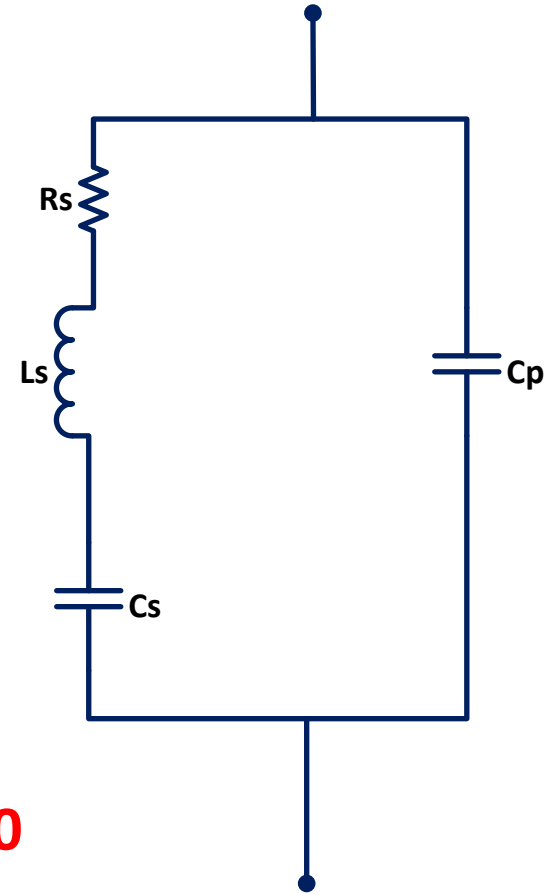
$$\therefore \omega_p = \frac{1}{\sqrt{L_s \left( \frac{C_s C_p}{C_s + C_p} \right)}}$$



Parallel resonance  
Uploaded By: anonymous



# Oscillators

## High Frequency Harmonic Oscillators


### The Crystal

$$C_s = 0.0060\text{PF}$$

$$L_s = 0.165609\text{H}$$

$$R_s = 10\Omega$$

$$C_p = 13.0\text{PF}$$

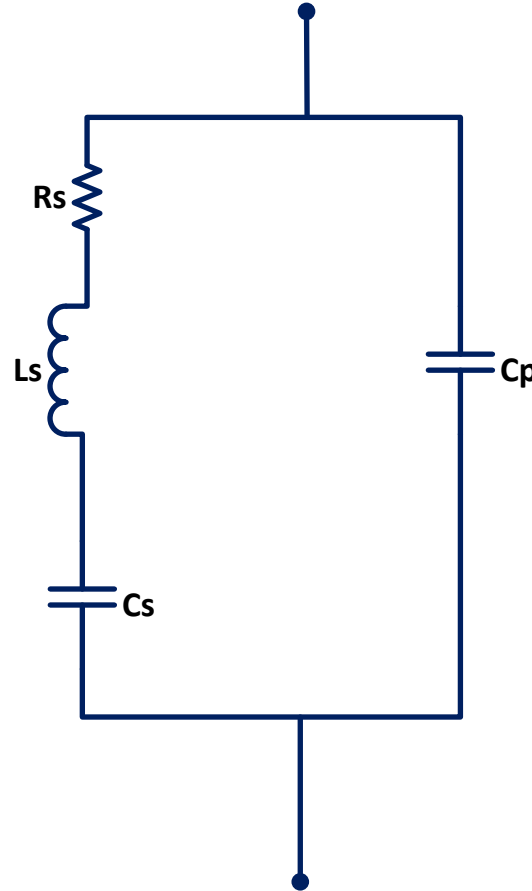

$$f_p - f_s = 1.179\text{KHz}$$

$$f_s = \frac{1}{2\pi \sqrt{L_s C_s}}$$

$$f_s = 5.048967\text{MHz}$$

$$\omega_p = \frac{1}{\sqrt{L_s \left( \frac{C_s C_p}{C_s + C_p} \right)}}$$


$$f_p = 5.050145\text{MHz}$$

# Oscillators


## High Frequency Harmonic Oscillators

### Pierce crystal oscillator.

$$\omega_p > \omega_o > \omega_s$$

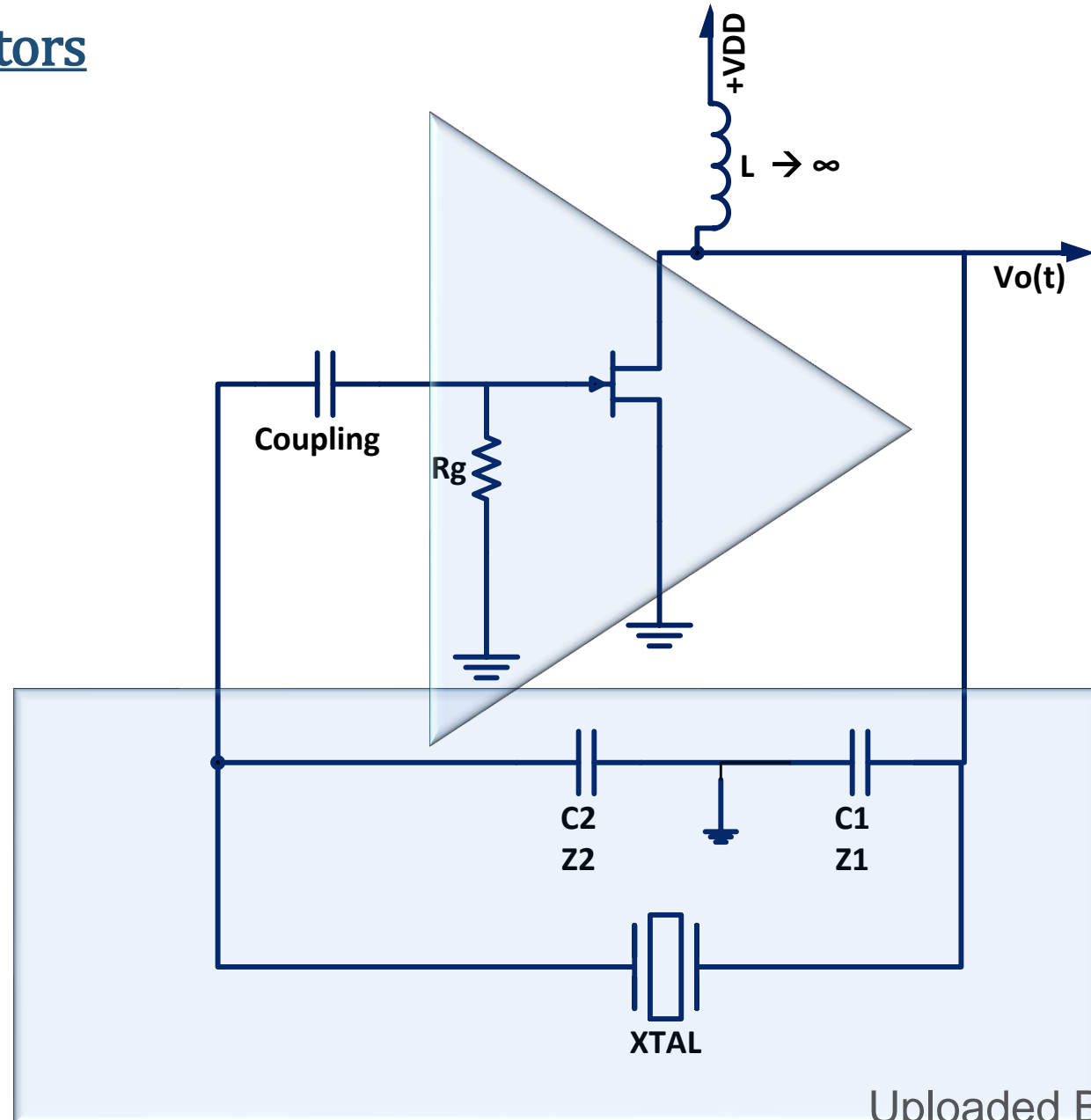

# Oscillators

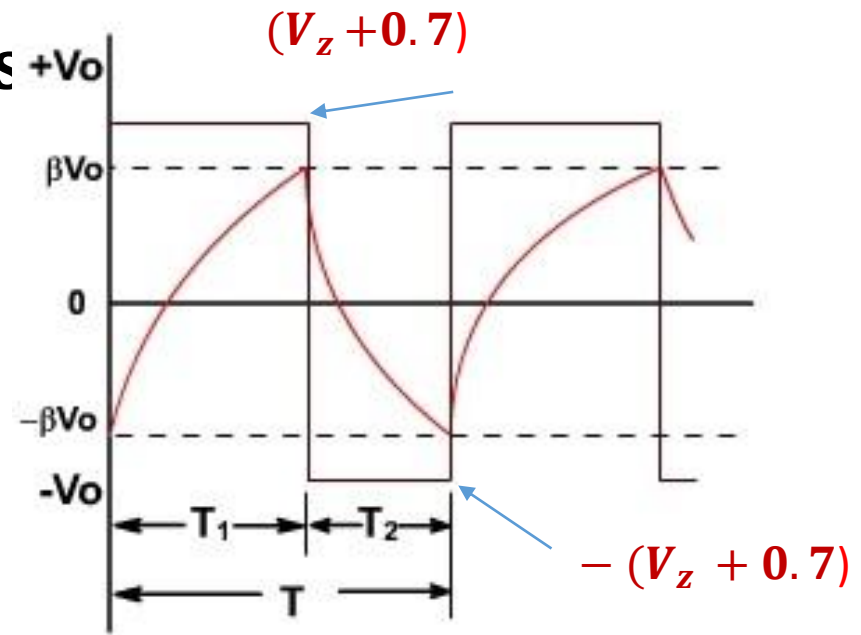


-The Op. Amp relaxation oscillator shown is a square \_wave generator .

-The circuit's frequency of oscillation is dependent on the charge and discharge of a capacitor  $C_1$  through a resistor  $R_1$ .

- The "heart" of the oscillator is an inverting Op. Amp comparator . the comparator uses positive feedback .

## An OP Relaxation Oscillator

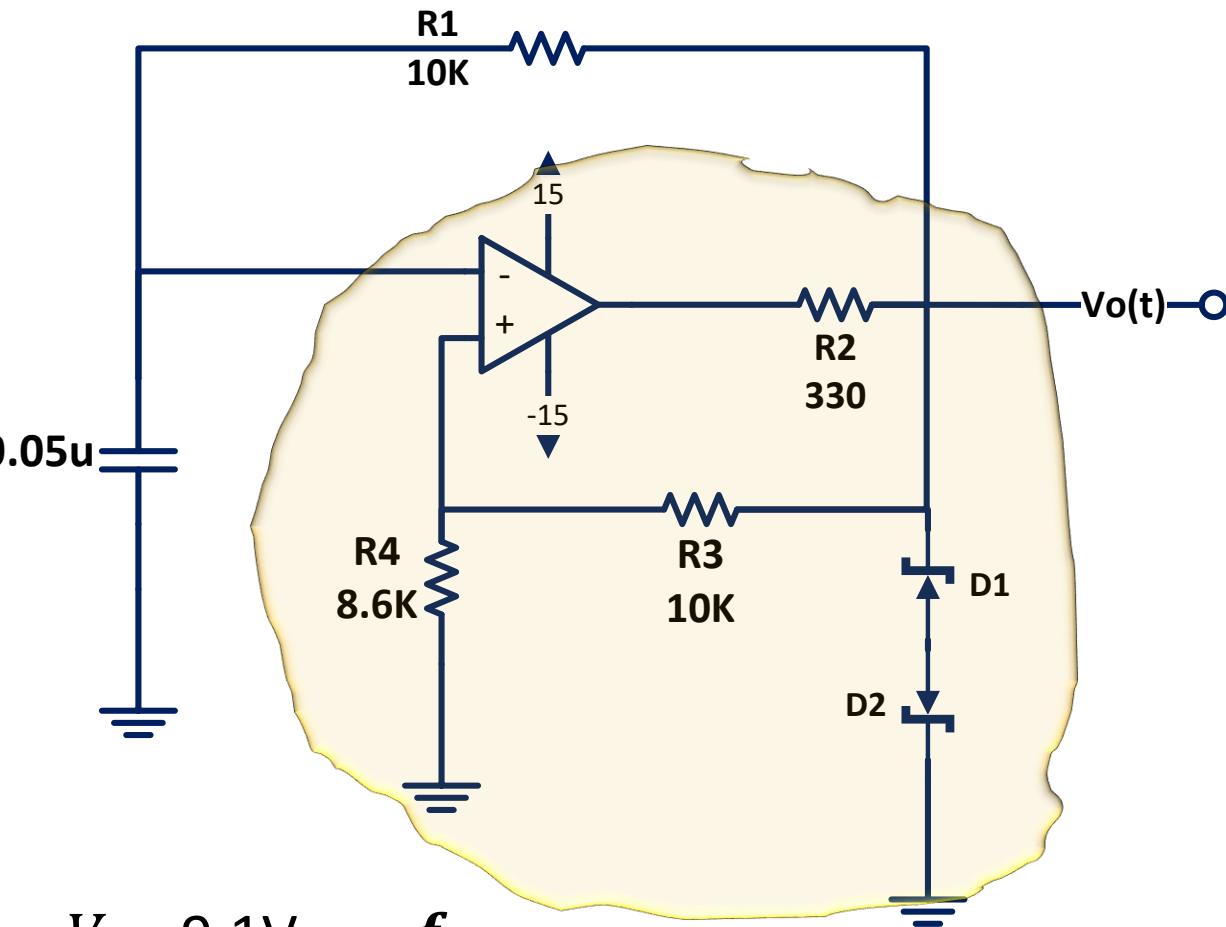



$V_z = 9.1V$        $f_o = 1KHz$

# An OP Relaxation Oscillator

# Oscillators

- The “heart” of the oscillator is an inverting Op. Amp comparator . the comparator uses positive feedback .



Inverting Schmitt trigger

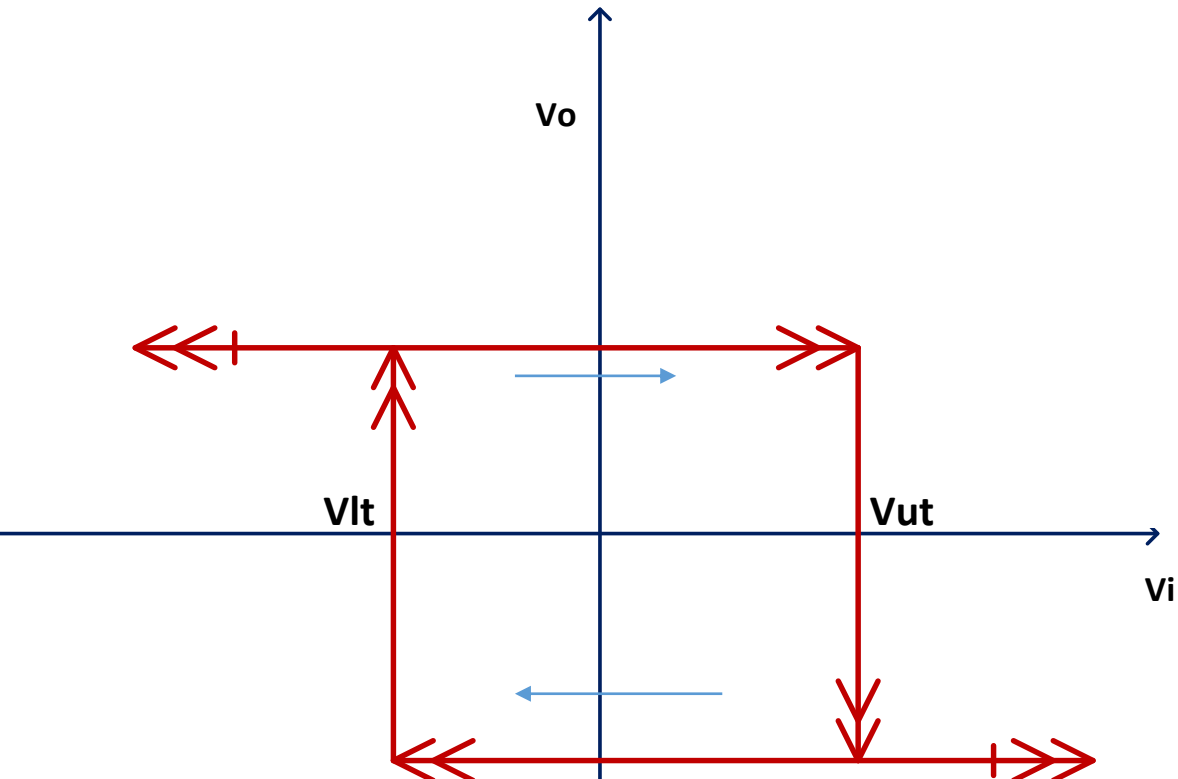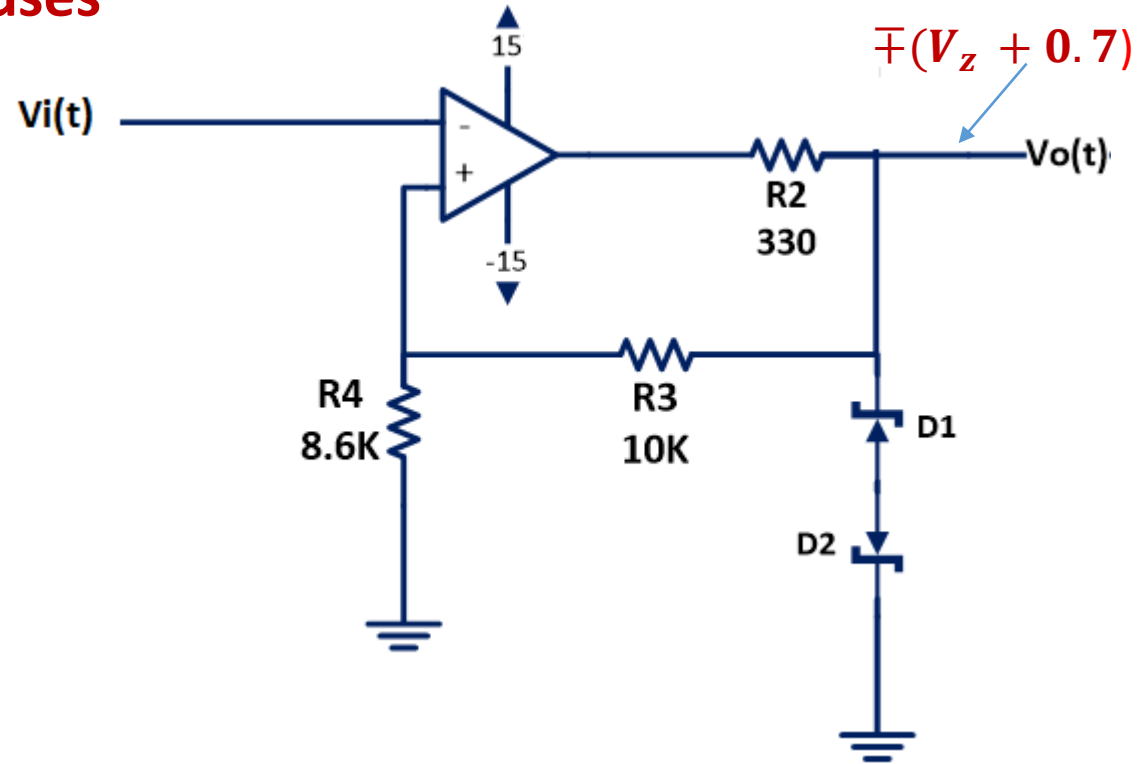

- $V_{UT} = \frac{R_4}{R_4 + R_3} (V_z + 0.7) = \beta (V_z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4 + R_3} (V_z + 0.7) = -\beta (V_z + 0.7)$

# Oscillators

## An OP Relaxation Oscillator


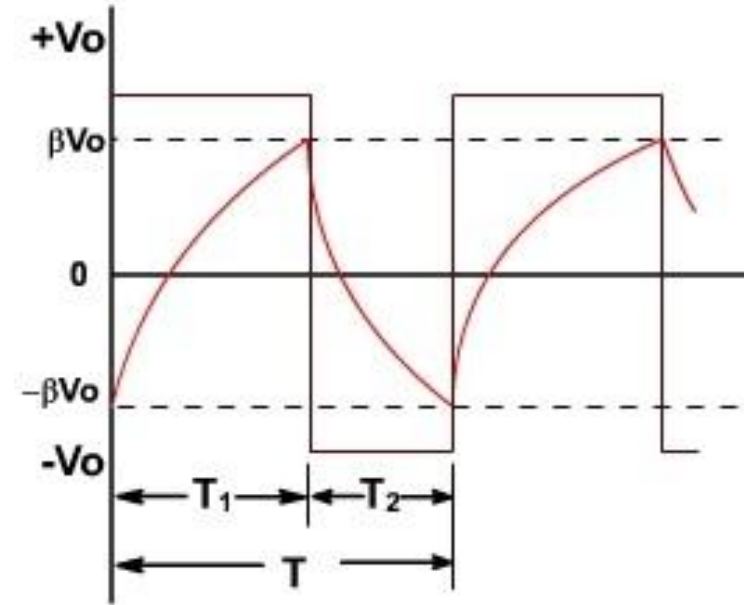
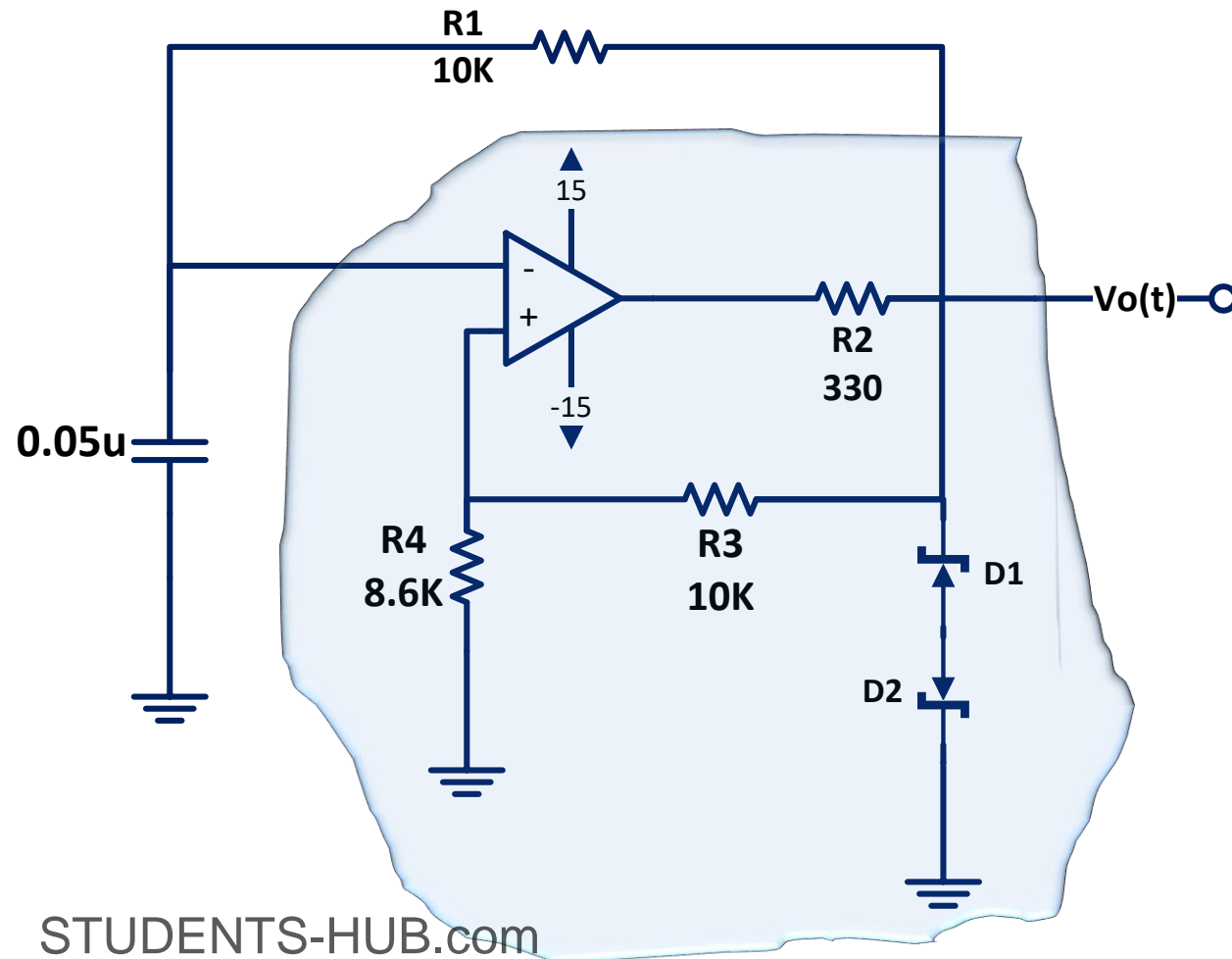


- $V_{out} = \pm(V_z + 0.7)$
- $V_{UT} = \frac{R_4}{R_4 + R_3} (V_z + 0.7) = \beta(V_z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4 + R_3} (V_z + 0.7) = -\beta(V_z + 0.7)$



# Oscillators
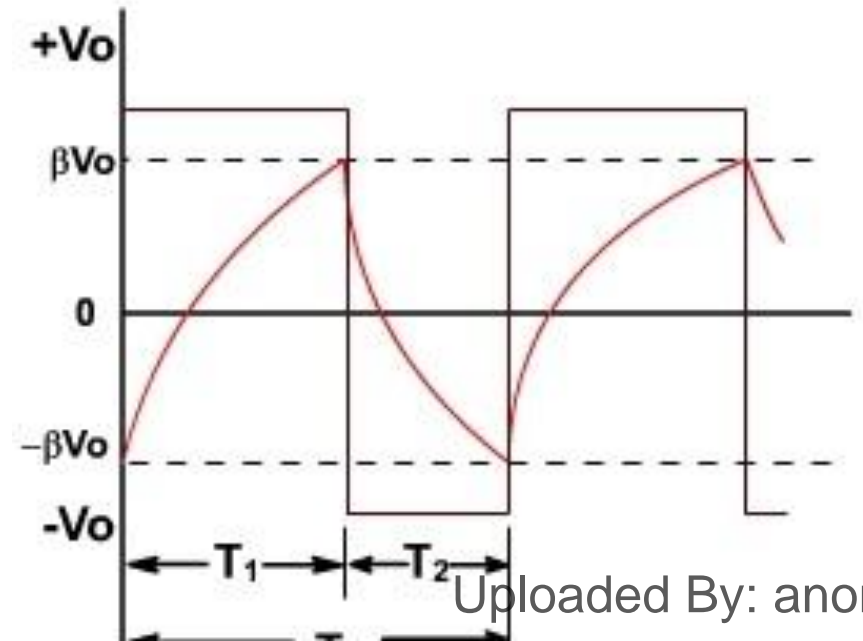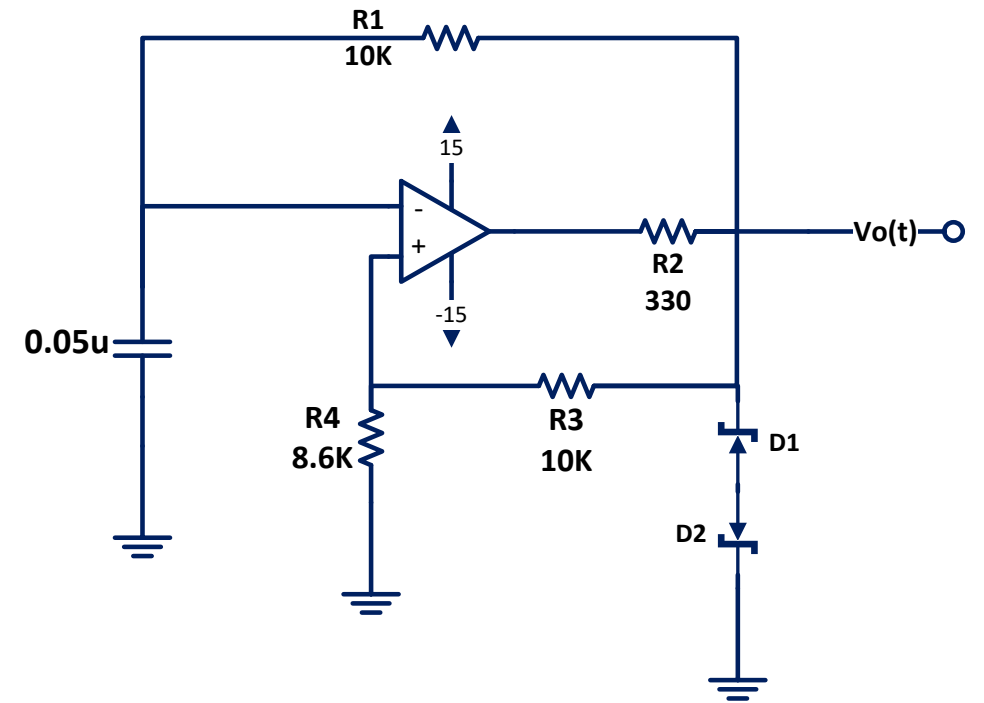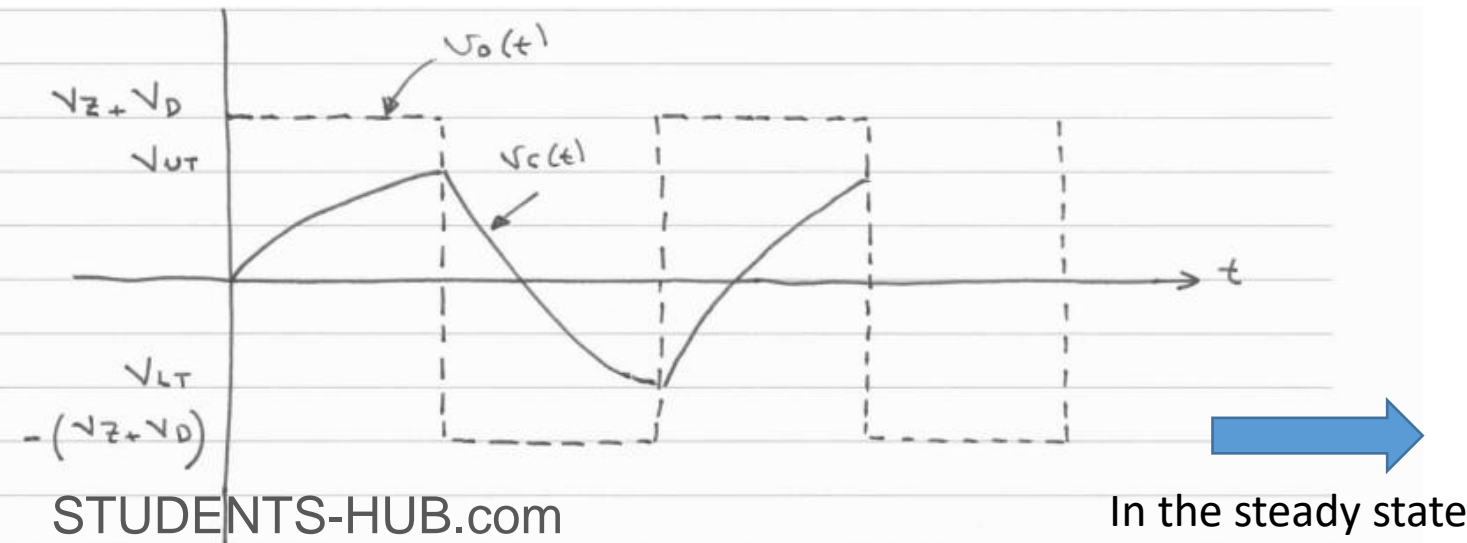
## An OP Relaxation Oscillator




- $V_{out} = \pm(V_Z + 0.7)$
- $V_{UT} = \frac{R_4}{R_4+R_3} (V_Z + 0.7) = \beta (V_Z + 0.7)$
- $V_{LT} = -\frac{R_4}{R_4+R_3} (V_Z + 0.7) = -\beta (V_Z + 0.7)$



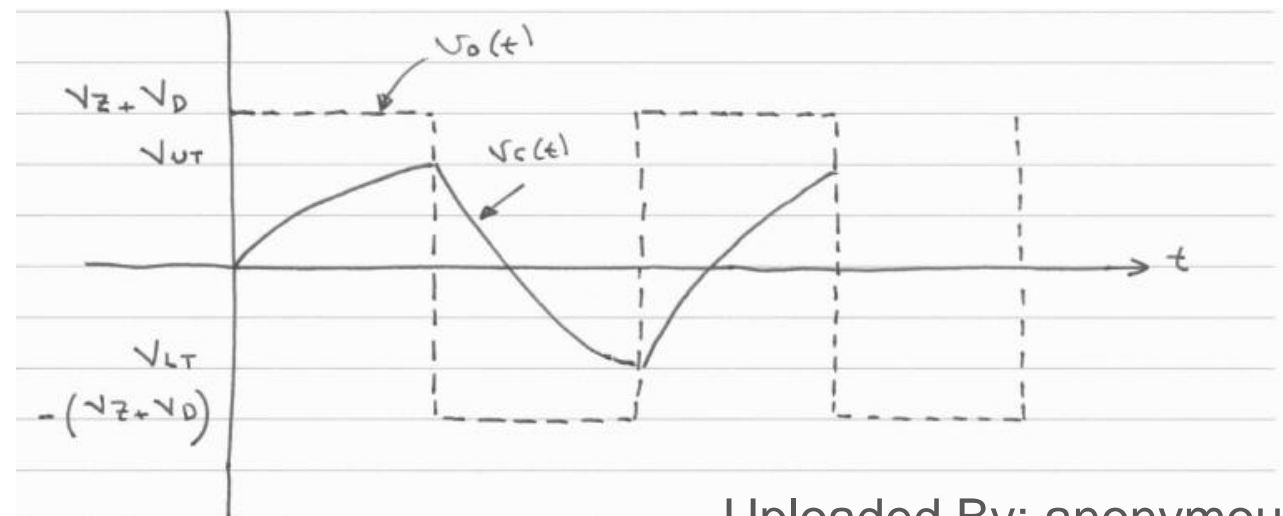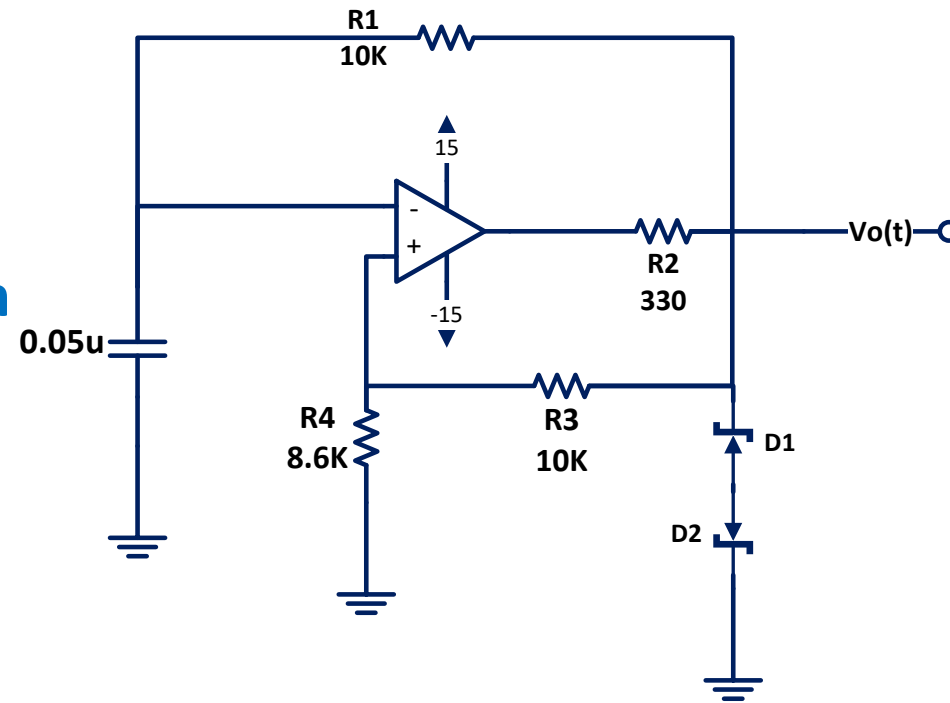- When the output of the comparator is positive, capacitor  $C_1$  will charge through resistor  $R_1$ .
- The capacitor will attempt to charge to  $V_{out} = V_z + 0.7$ .
- When the voltage across the capacitor reaches the upper threshold voltage  $V_{UT}$ , the comparators output will immediately switch to  $V_{out} = -(V_z + 0.7)$ .



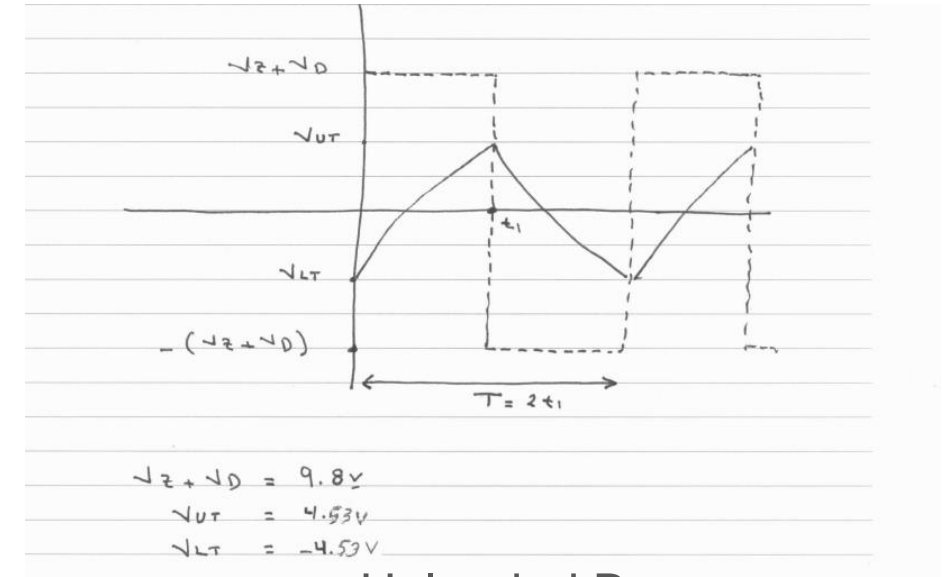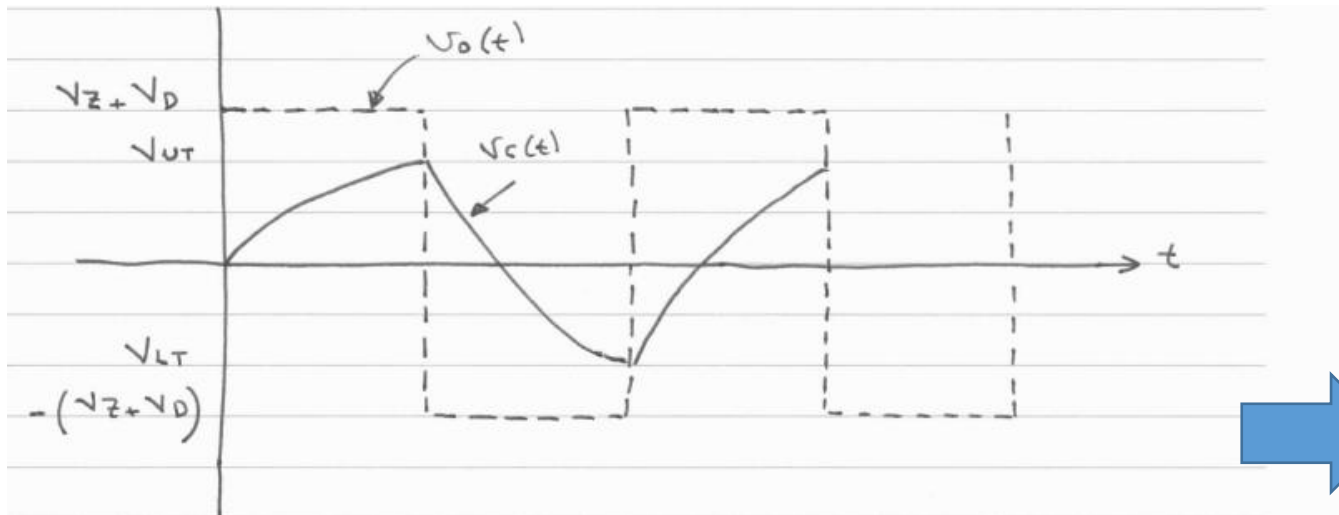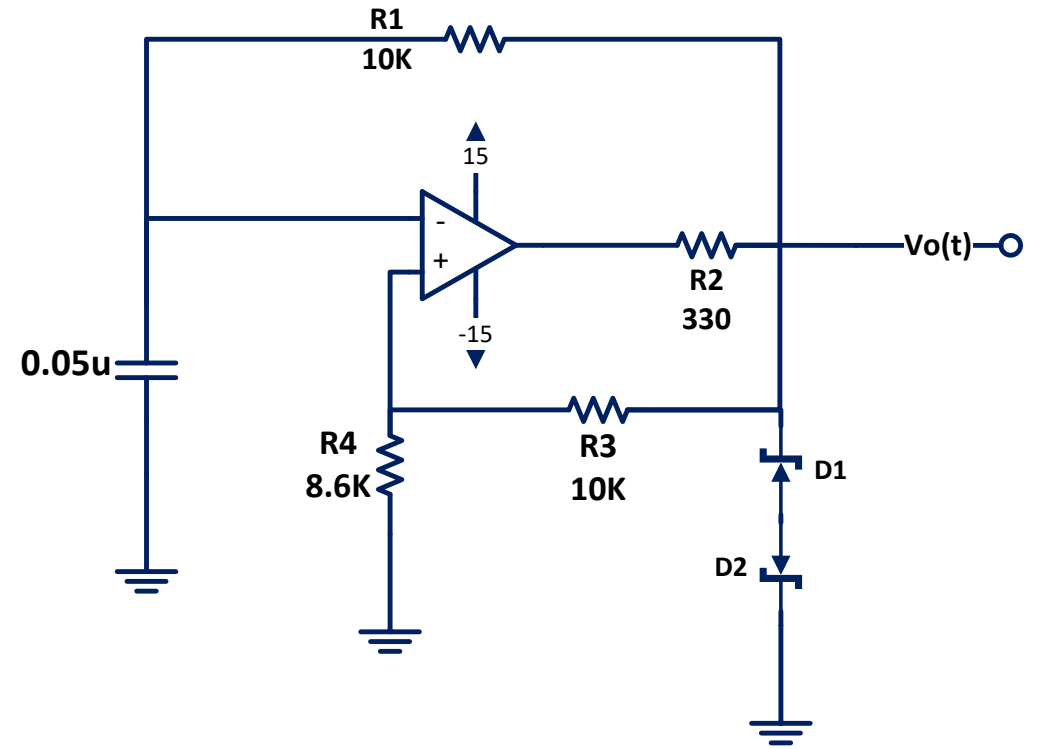- The capacitor will then start to discharge from the positive upper threshold voltage toward the negative output voltage .
- When the voltage across the capacitor reaches the lower threshold voltage  $V_{LT}$  , the comparators output will immediately switch to  $V_{out} = + (V_Z + 0.7)$ .





# Oscillators

To determine the frequency of oscillation

- $V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$

- At  $t_1$  :  $V_c(t_1) = \beta V_{out}$

$$\frac{R_4}{R_4 + R_3} = \beta$$

$$V_{out} = V_z + V_D$$



- $\beta V_{out} = -\beta V_{out} + (V_{out} - (-\beta V_{out})) (1 - e^{-\frac{t_1}{\tau}})$

- dividing both side by  $V_{out}$

- $\beta = -\beta + (1 + \beta) (1 - e^{-\frac{t_1}{\tau}})$

- $2\beta = (1 + \beta) (1 - e^{-\frac{t_1}{\tau}})$

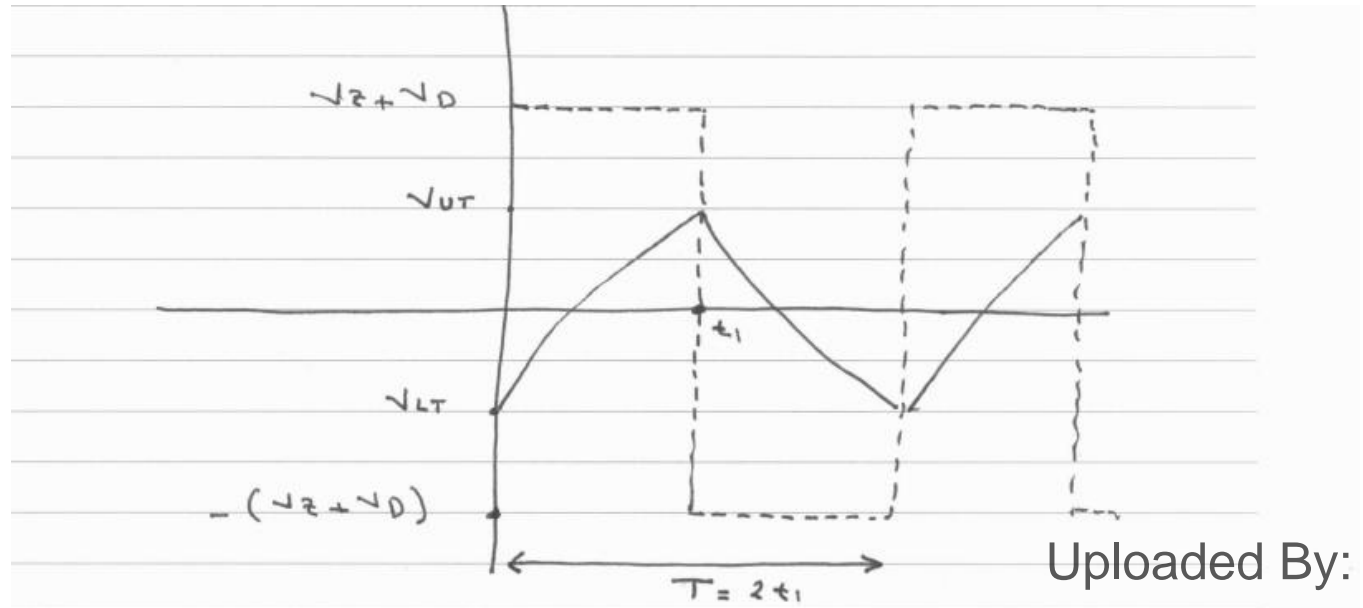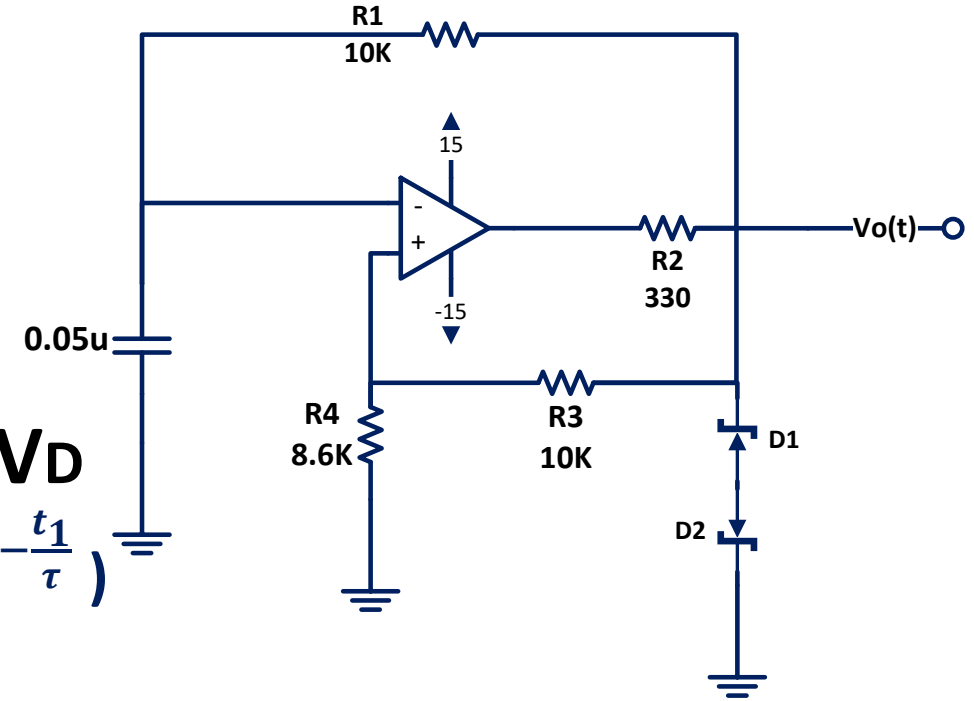- $\frac{2\beta}{(1 + \beta)} = (1 - e^{-\frac{t_1}{\tau}})$



- $e^{-\frac{t_1}{\tau}} = \frac{1-\beta}{1+\beta}$

- $-\frac{t_1}{\tau} = \ln \frac{1-\beta}{1+\beta}$

- $t_1 = \tau \ln \frac{1+\beta}{1-\beta} = R_1 C_1 \ln \frac{1+\beta}{1-\beta}$


- $T = 2t_1 = 2R_1 C_1 \ln \left( \frac{1+\beta}{1-\beta} \right)$

$$f_o = \frac{1}{T}$$

- $\therefore f_o = \frac{1}{T} = \frac{1}{2R_1 C_1 \ln \left( \frac{1+\beta}{1-\beta} \right)}$

- If  $R_4 = 0.859R_3 \rightarrow \beta = 0.462$



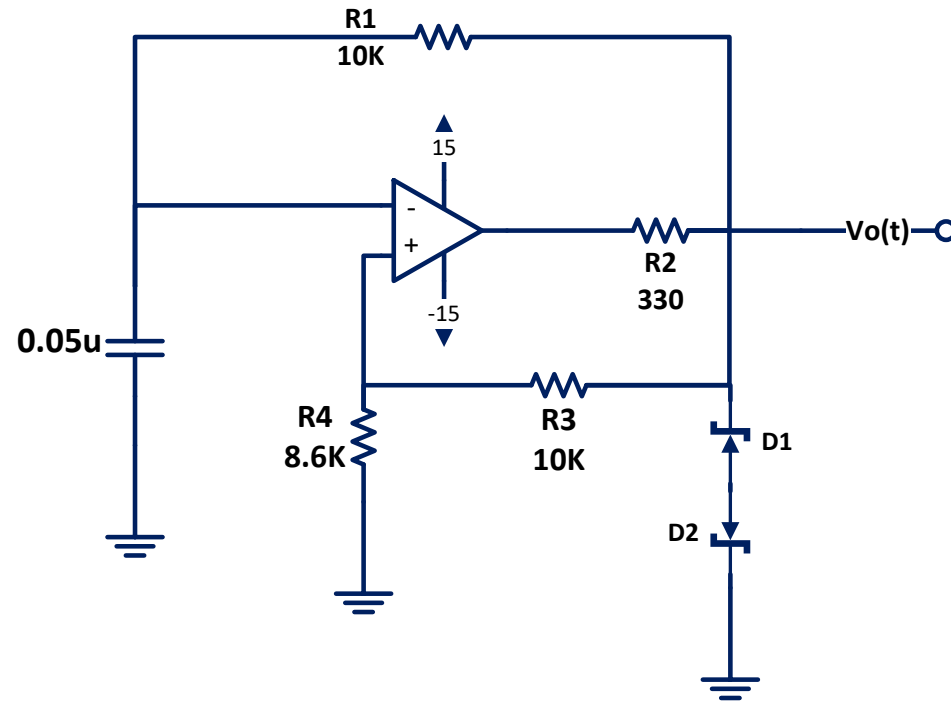
- $\ln \left( \frac{1+\beta}{1-\beta} \right) = 1$



$$\therefore f_o = \frac{1}{2R_1 C_1}$$

# Oscillators

## An Op-Amp Triangle Generator

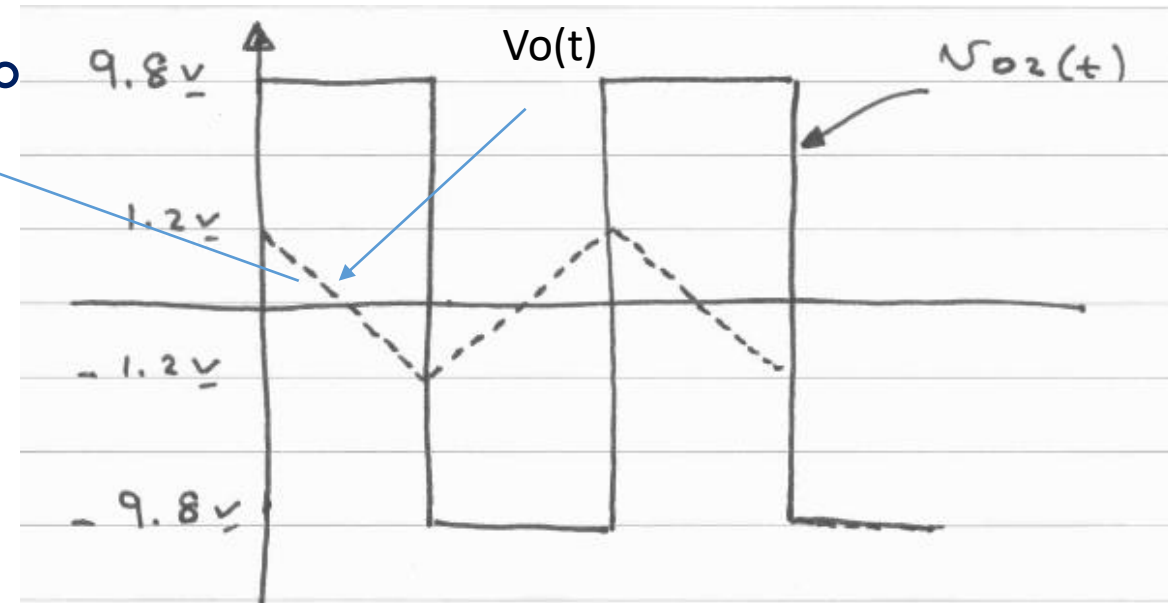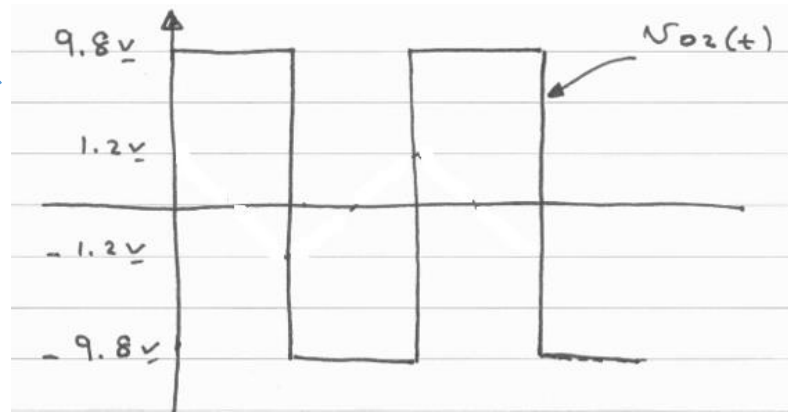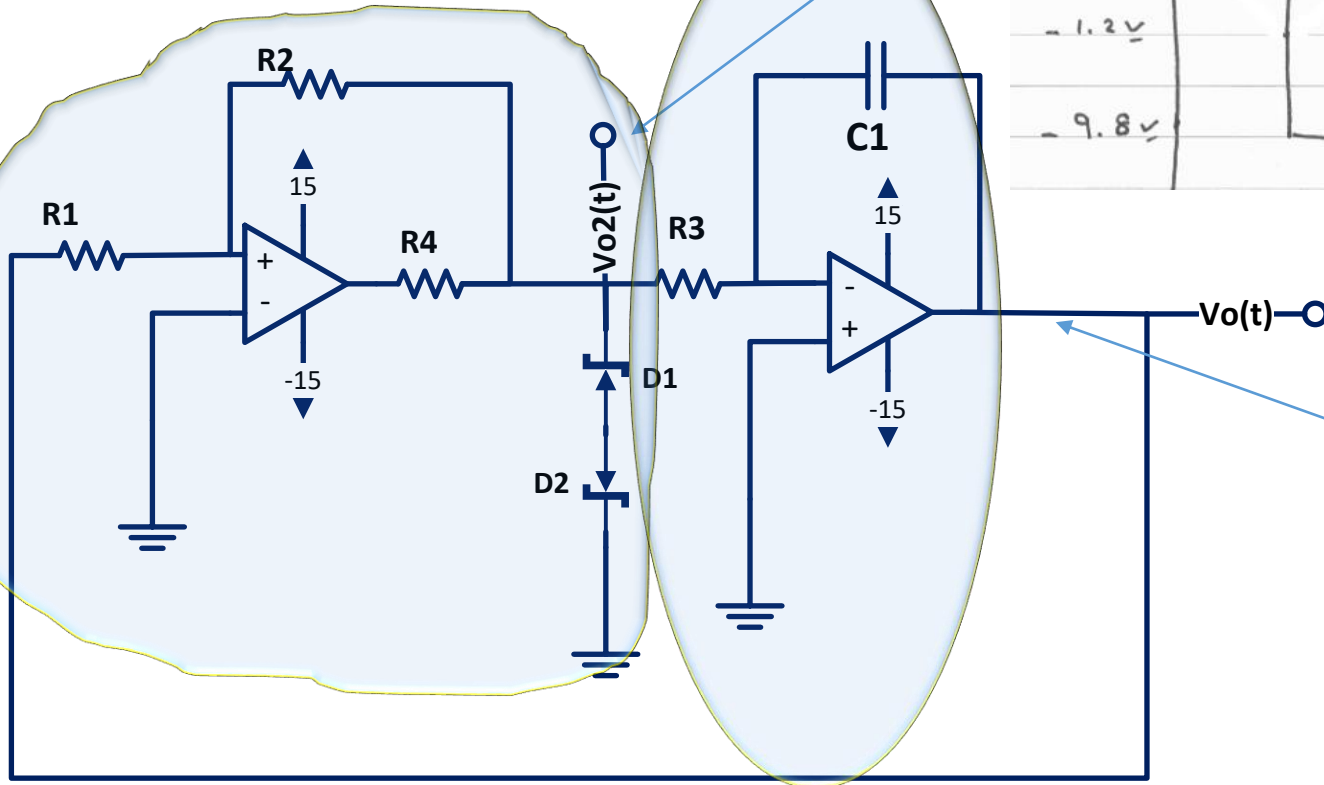

$$V_Z = 9.1\text{v}$$

$$R_1 = 100\text{K}\Omega$$

$$R_2 = 820\text{K}\Omega$$

$$V_Z + V_D = 9.8\text{v}$$

$$\frac{R_1}{R_2} (V_Z + V_D) = 1.2\text{v}$$

# Oscillators

## An Op-Amp Triangle Generator

It consists of two stages




- a) Non inverting Schmitt trigger comparator
- b) Inverting integrator

It provide two different output waveforms

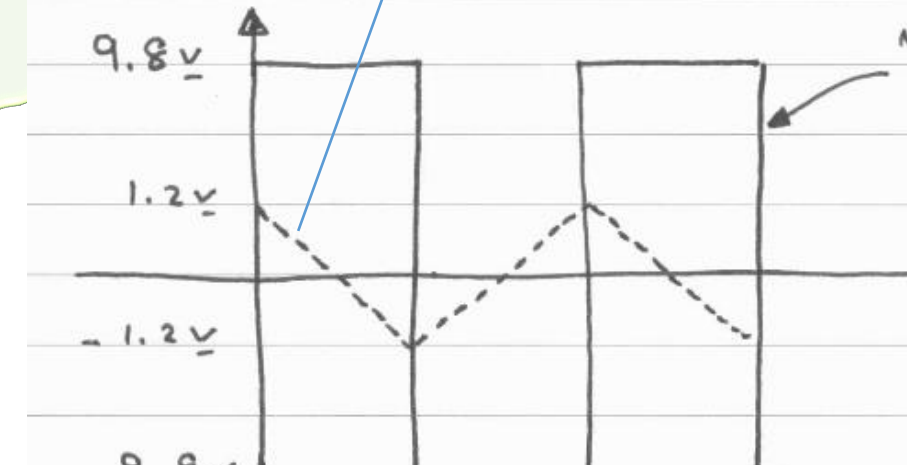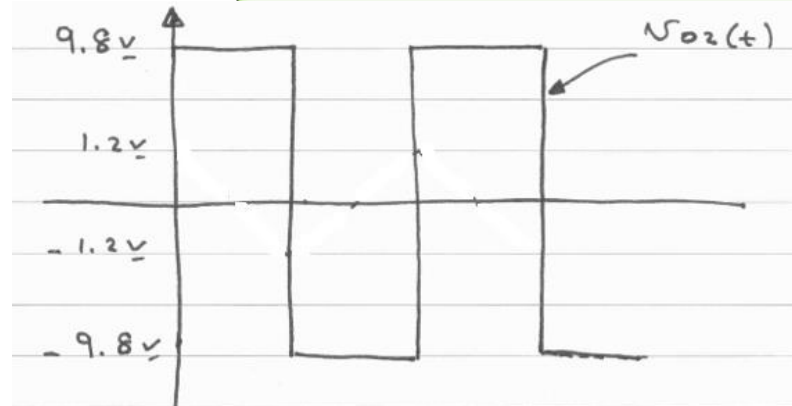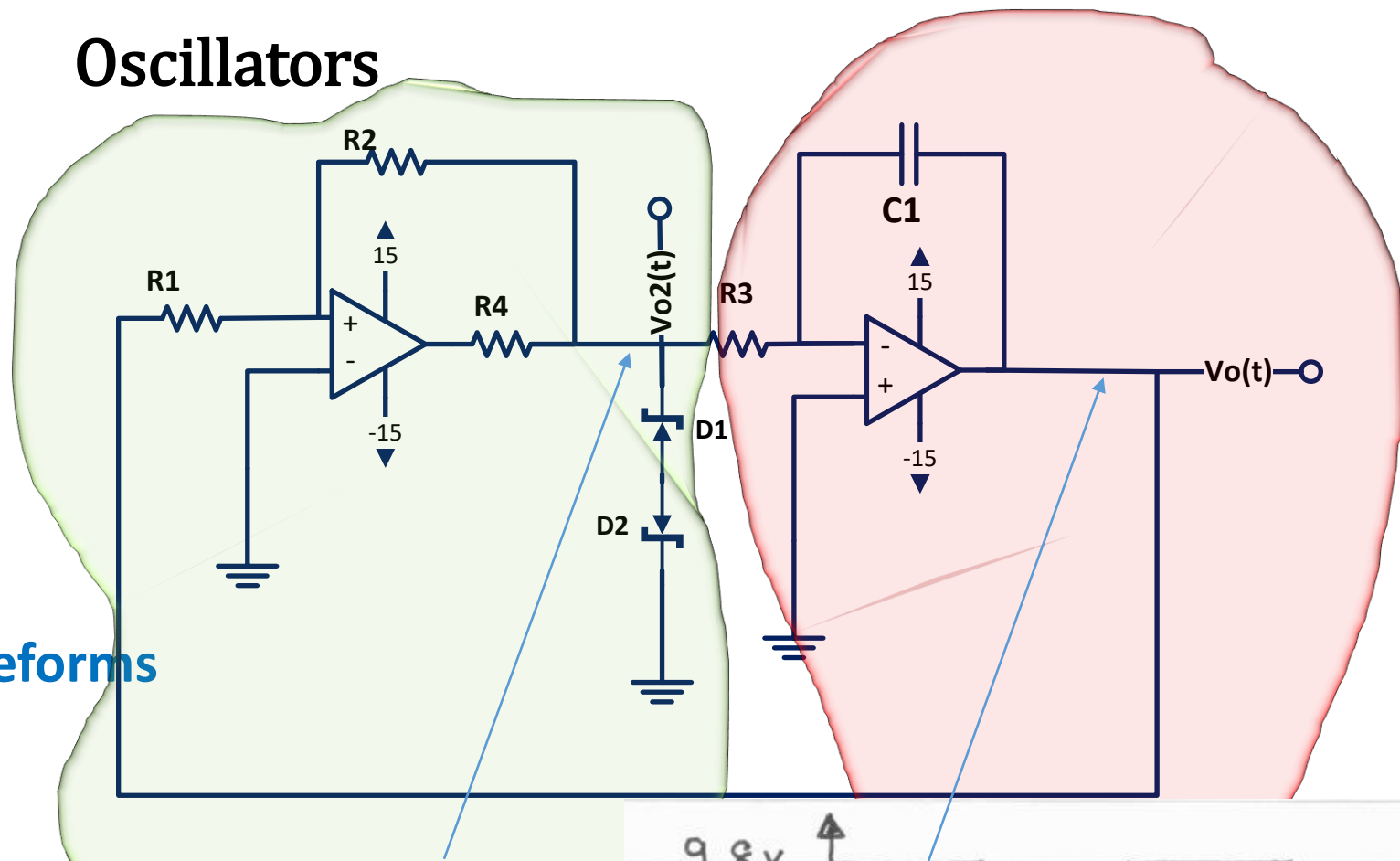- a) Square wave
- b) Triangle wave

$$V_{UT} = \frac{R_1}{R_2} (V_Z + V_D) = 1.2v$$

$$V_{LT} = -\frac{R_1}{R_2} (V_Z + V_D) = -1.2v$$



# Inverting Integrator

Assuming that  $V_c(0^-) = 0$

$$V_{out} = -V_c(t)$$


$$V_c(t) = \frac{1}{C_1} \int_0^t i_{in}(t) dt$$

$$i_{in}(t) = \frac{V_{in}(t)}{R_3}$$

$$V_{out} = -\frac{1}{R_3 C_1} \int_0^t V_{in}(t) dt$$

$$V_{in}(t) = V_{in}, \text{ DC}$$
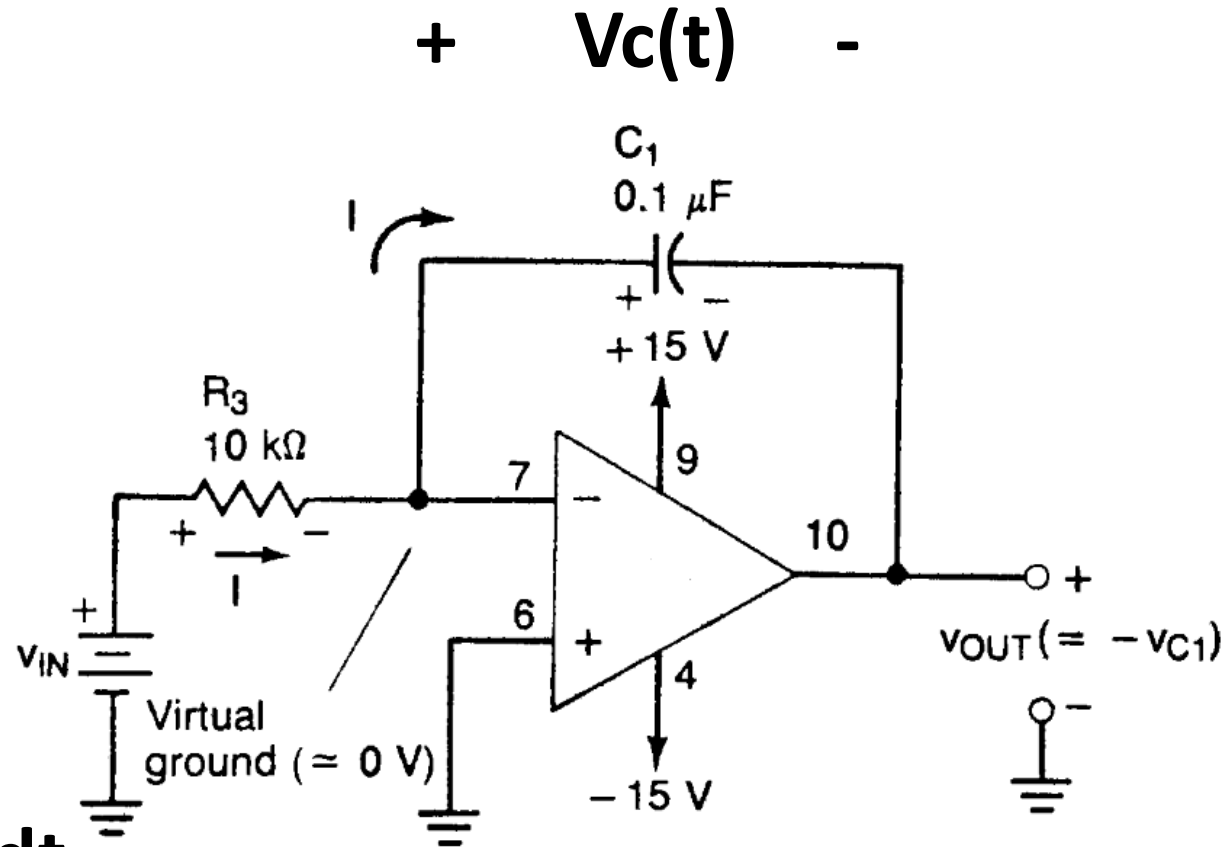
$$\therefore V_{out} = -\frac{V_{in}}{R_3 C_1} t$$



# Inverting Integrator

Assuming that  $V_i = -10\text{mV}$ ,

find  $V_o(t)$  at 0.1s and 0.2s


$$V_{out} = -\frac{V_{in}}{R_3 C_1} t = -\frac{V_{in}}{(10\text{k}\Omega)(0.1\mu\text{F})} t = -1000V_{in} t$$

If  $v_{in}$  is  $-10\text{mV}$  and  $t$  is 0.1s

$$V_{out} = -1000V_{in} t = -(1000)(-10\text{mV})(0.1\text{s}) = 1\text{V}$$

And in 0.2s
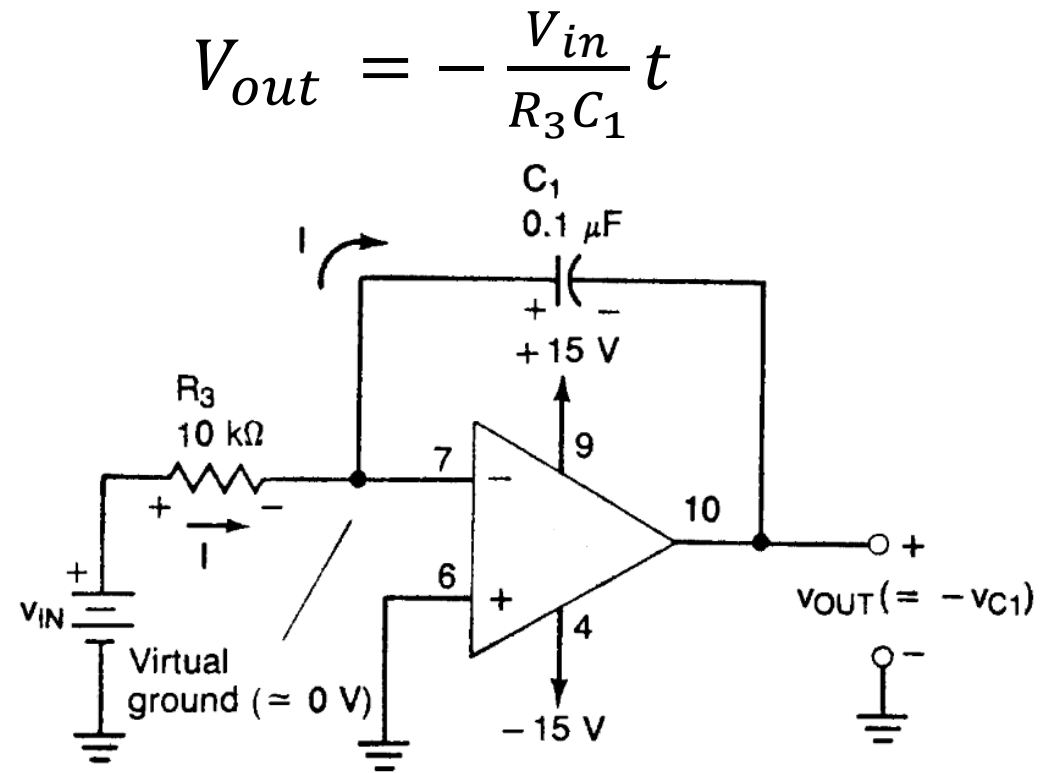
$$V_{out} = -1000V_{in} t = -(1000)(-10\text{mV})(0.2\text{s}) = 2\text{V}$$



Assuming that  $+V_{sat}$  is 13 v we may solve the time to reach saturation


$$V_{out} = -\frac{V_{in}}{R_3 C_1} t = +V_{sat}$$

$$t = \frac{+V_{sat}}{-v_{in}} R_3 C_1 = \frac{13\text{V}}{-(-10\text{mV})} (10\text{k}\Omega)(0.1\mu\text{F})$$

$$= (1300)(1\text{ms}) = 1.3\text{s}$$

# Oscillators


## Inverting Integrator

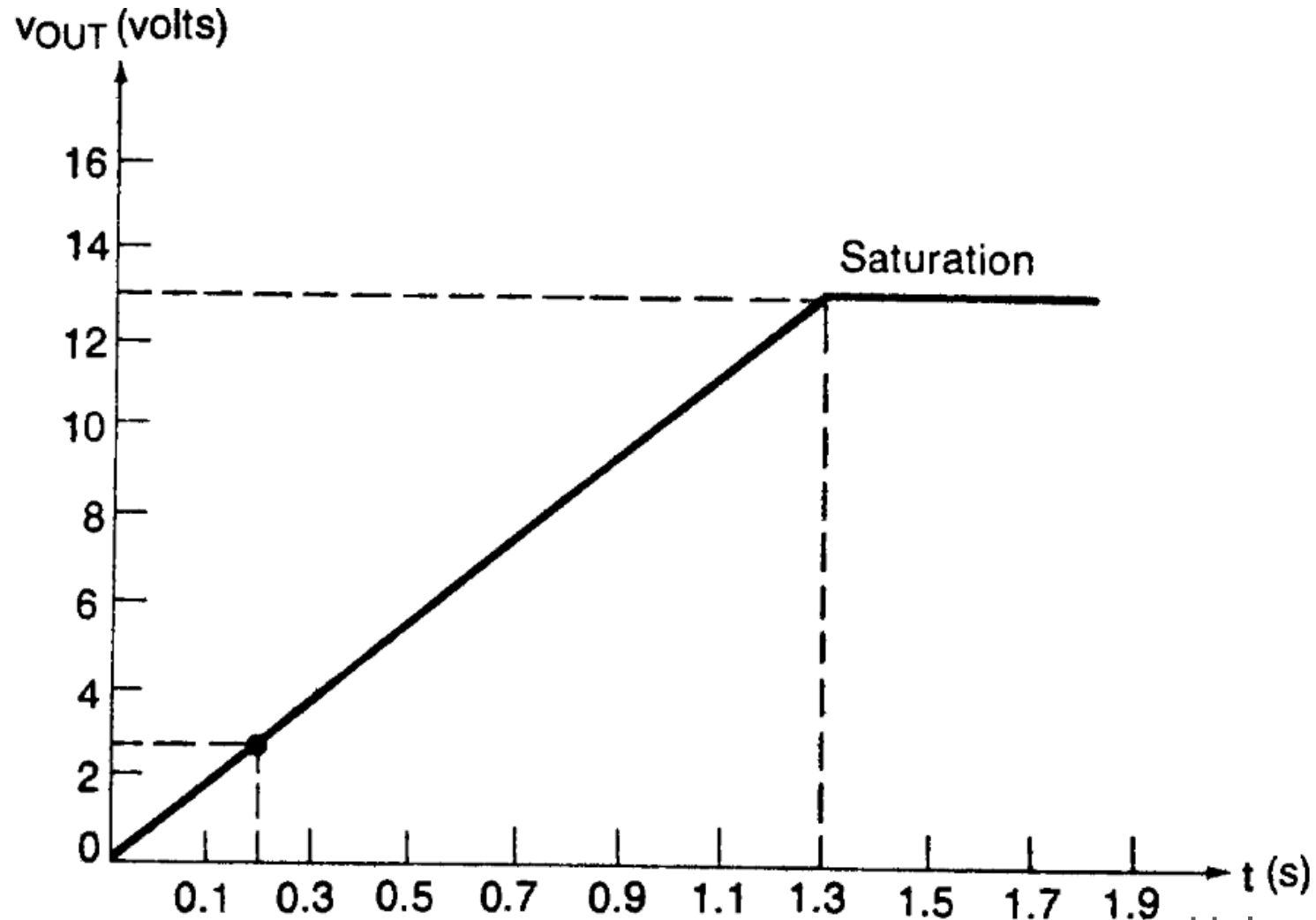

# Oscillators

## Inverting Integrator

To determine  $f_o$

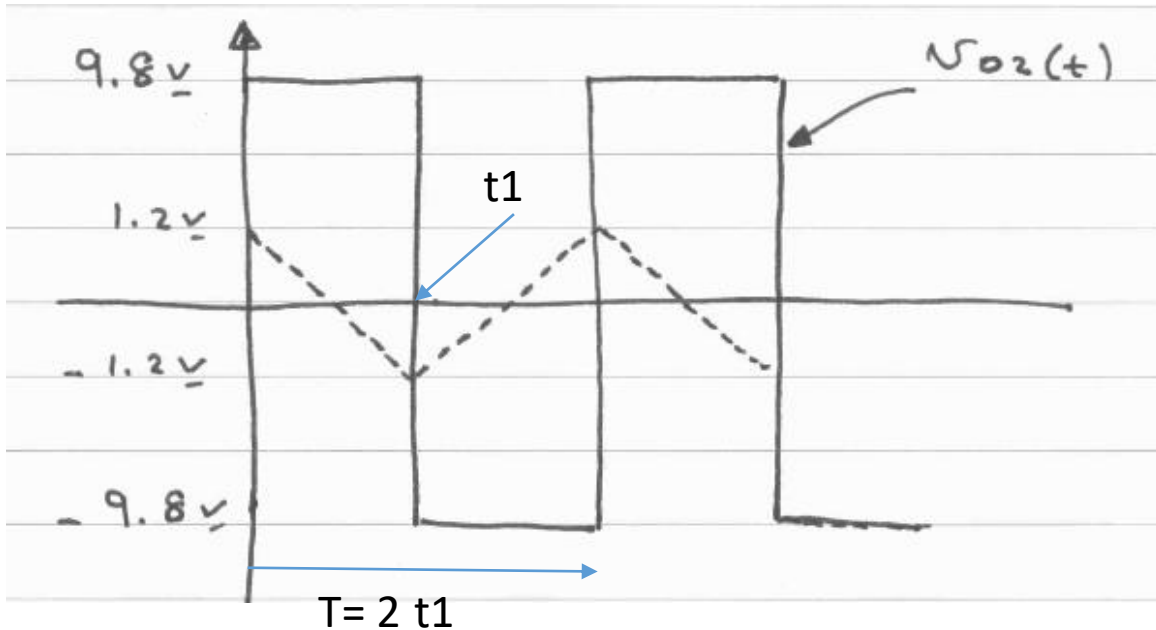

For  $t_1 \geq t \geq 0$

$$V_o(t) = V_{UT} - \frac{V_{in}}{R_3 C_1} t$$

$$V_{UT} = \frac{R_1}{R_2} (V_Z + V_D)$$

$$V_{in} = V_Z + V_D$$

$$V_o(t) = \frac{R_1}{R_2} (V_Z + V_D) - \frac{V_Z + V_D}{R_3 C_1} t$$

$$\text{At } t = t_1 ; V_o(t_1) = - \frac{R_1}{R_2} (V_Z + V_D) = V_{LT}$$


$$\therefore t_1 = \frac{2R_1 R_3 C_1}{R_2}$$

$$f_o = \frac{1}{T} = \frac{1}{2t_1} = \frac{R_2}{4R_1 R_3 C_1}$$




# Oscillators

## The 555 Timer As an Oscillator.

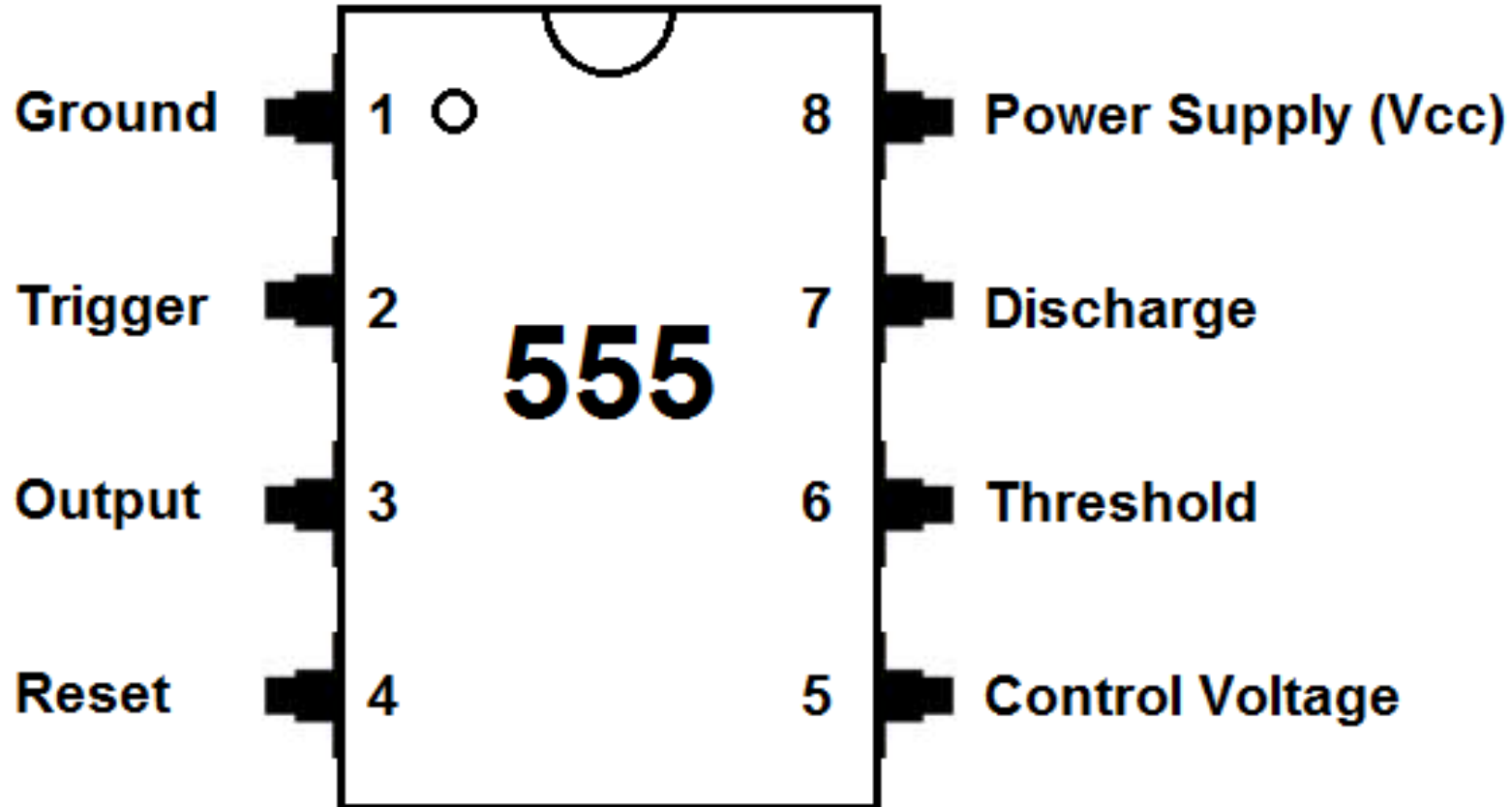

# Oscillators


## The 555 Timer As an Oscillator.

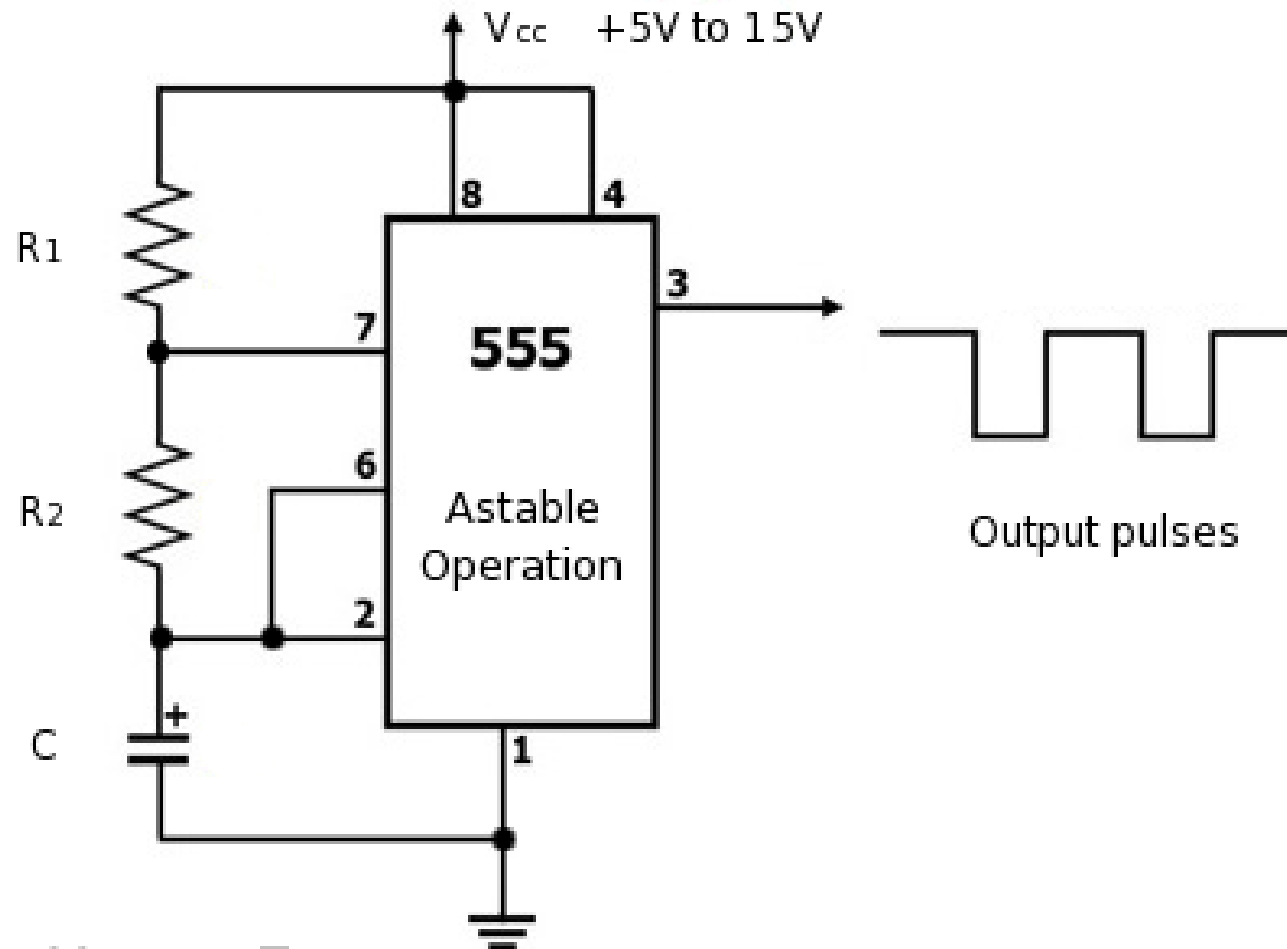

# Oscillators
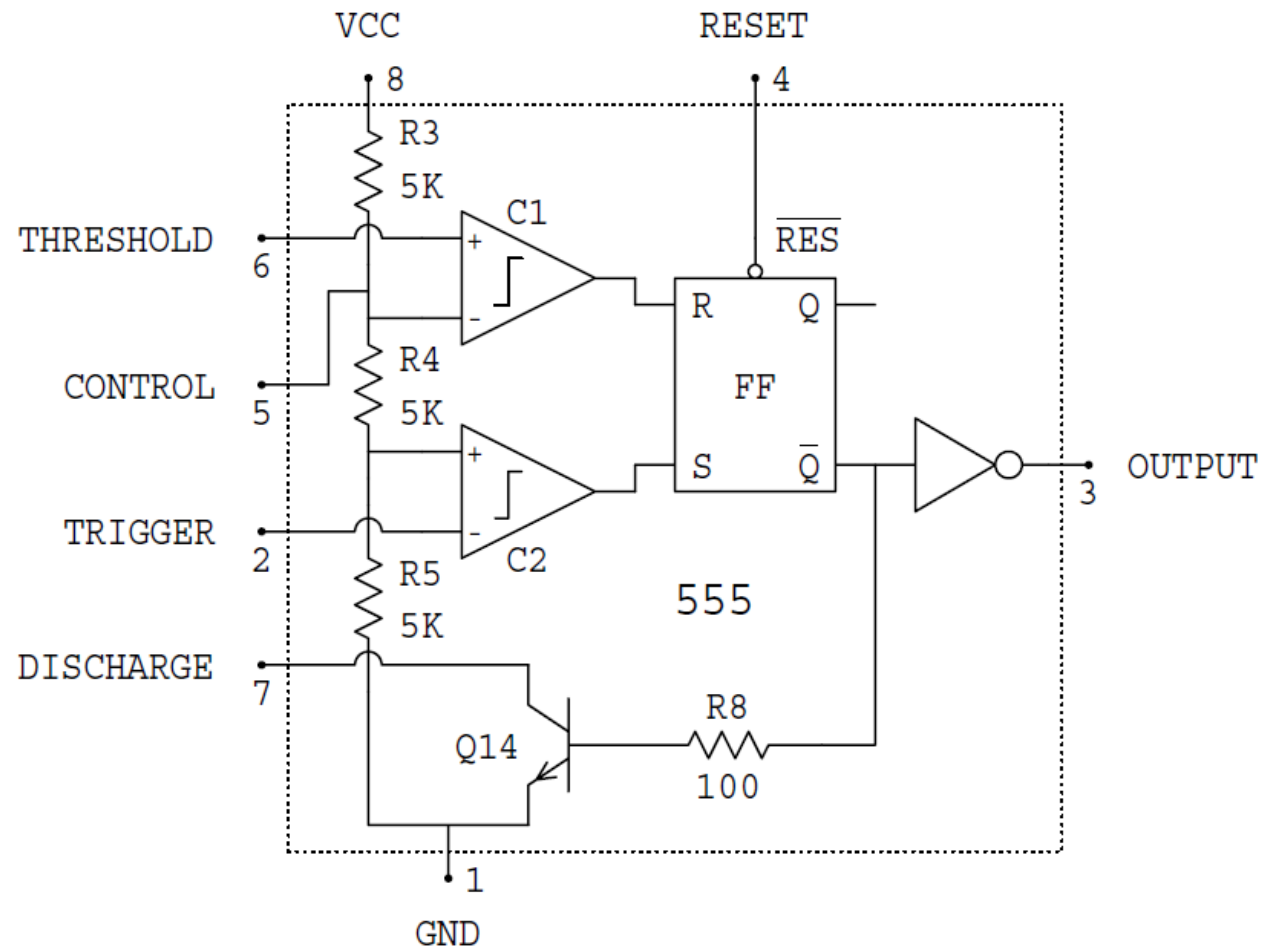
## The 555 Timer As an Oscillator.

Functional block diagram of the 555 integrated circuit timer




# Oscillators

## The 555 Timer As an Oscillator.

### Internal Component of 555

- Two comparators
- Three R (5K) that set the trigger Levels
- Transistor that act as a switch
- S R Latch


•	<b>S</b>	<b>R</b>	$Q_n$
	<b>0</b>	<b>0</b>	$Q_n$ no change
	<b>1</b>	<b>0</b>	<b>1</b>
	<b>0</b>	<b>1</b>	<b>0</b>
	<b>1</b>	<b>1</b>	<b>Forbidden</b>

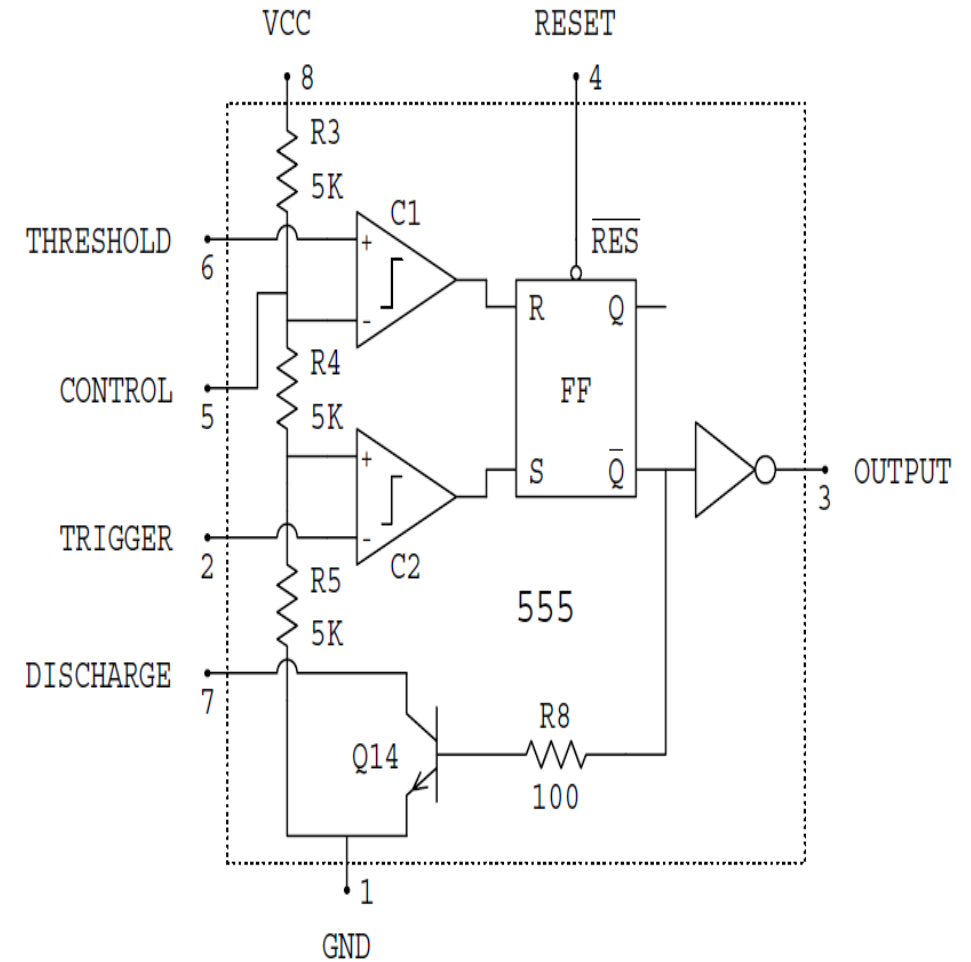

# Oscillators

## The 555 Timer As an Oscillator.

### 555 timer as an a stable circuit

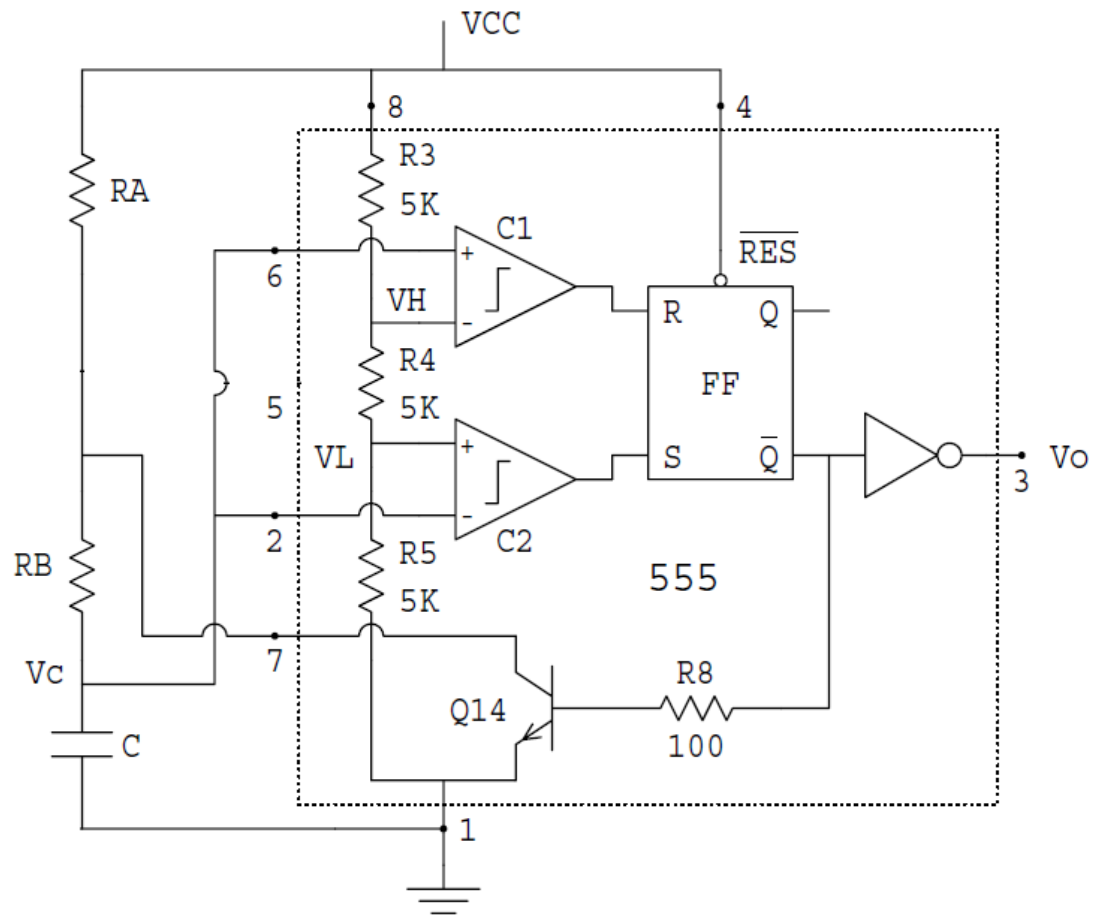

# The 555 Timer As an Oscillator.

## Operation of the 555 timer oscillator.

At the beginning

$$V_C(0^+) = V_C(0^-) = 0$$



$$\therefore R = 0, S = 1$$

$$\therefore Q = 1, \bar{Q} = 0$$

∴ Transistor is off

∴ The capacitor starts charging

$$\tau_C = (R_A + R_B)C$$

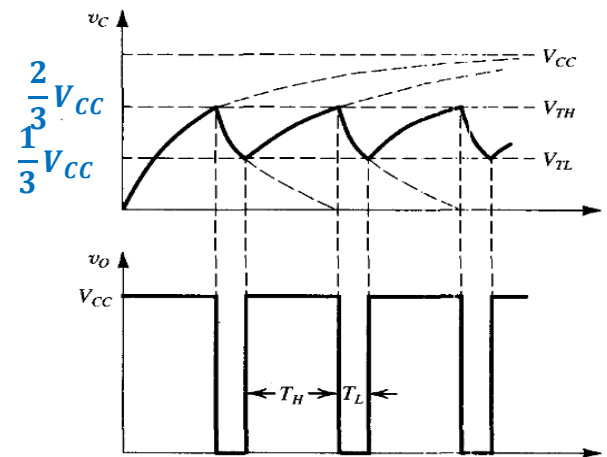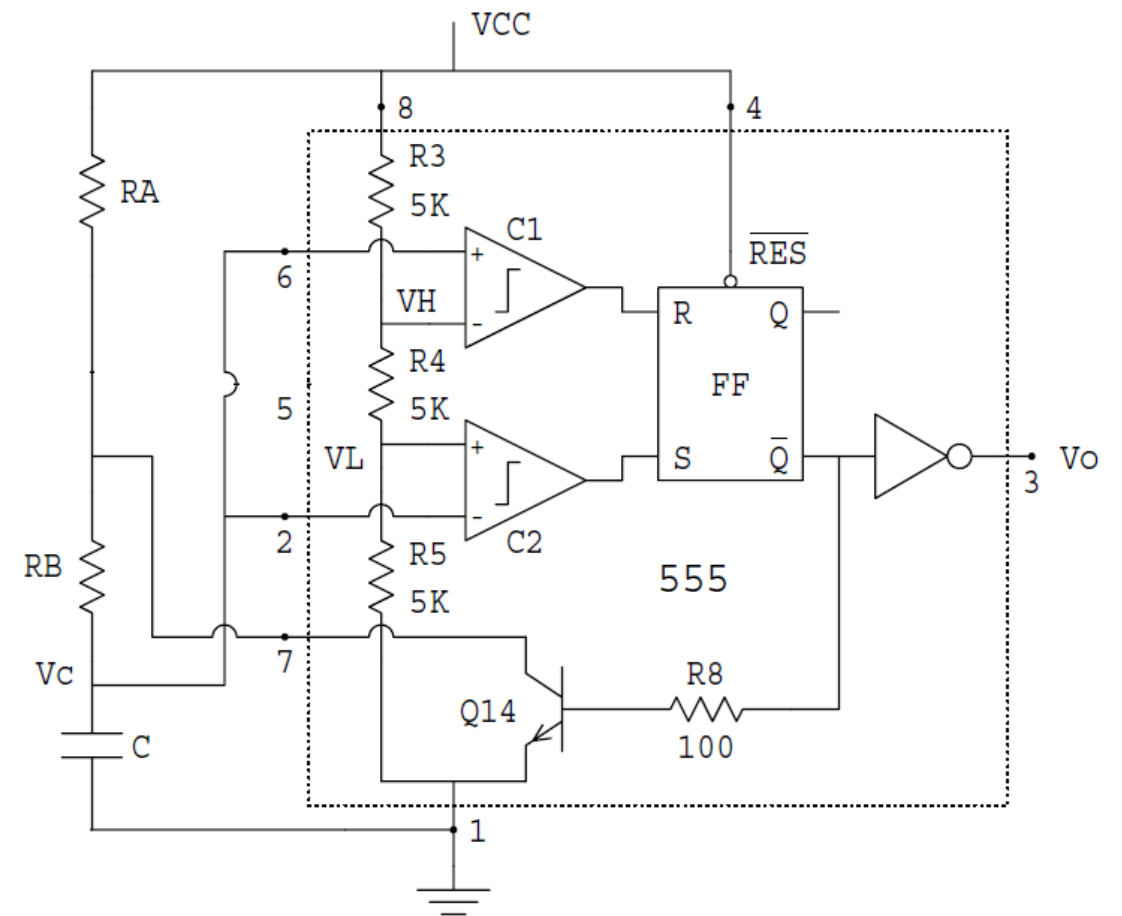

• When  $V_C(t) > \frac{1}{3}V_{CC}$

∴  $R = 0$  , and  $S = 0$



No change

∴  $Q = 1$  , and  $\bar{Q} = 0$

∴ The transistor is still off

∴ The capacitor is still charging

$$\tau_c = (R_A + R_B)C$$

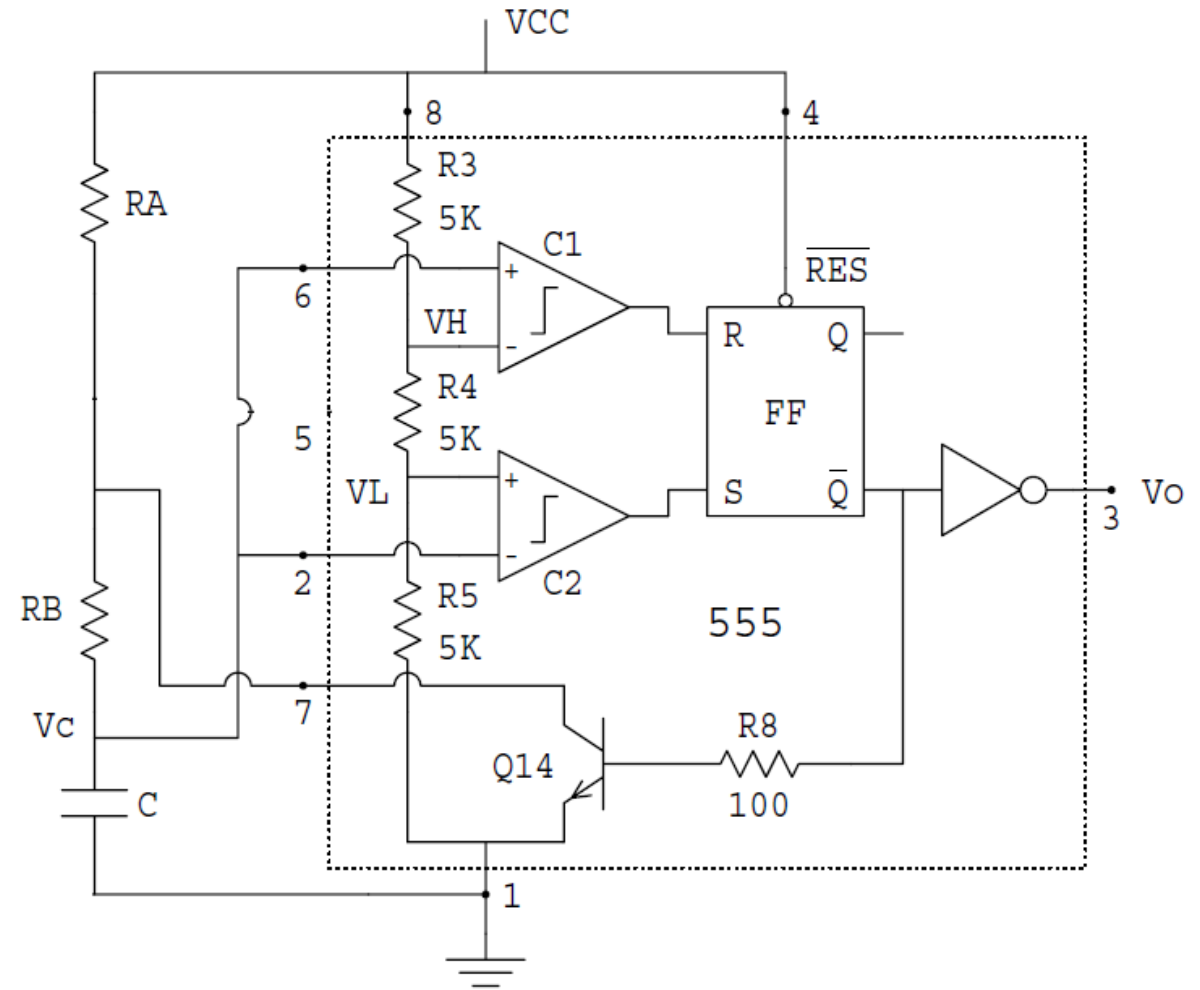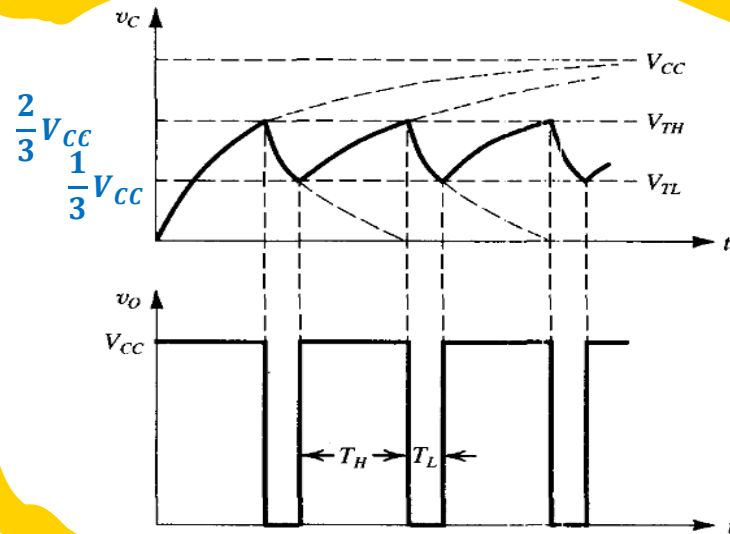

- When  $V_C(t) > \frac{2}{3}V_{CC}$



∴  $R = 1$  , and  $S = 0$

∴  $Q = 0$  , and  $\bar{Q} = 1$

∴ The transistor turns on

∴ The capacitor starts discharging

$$\tau_d = R_B C$$

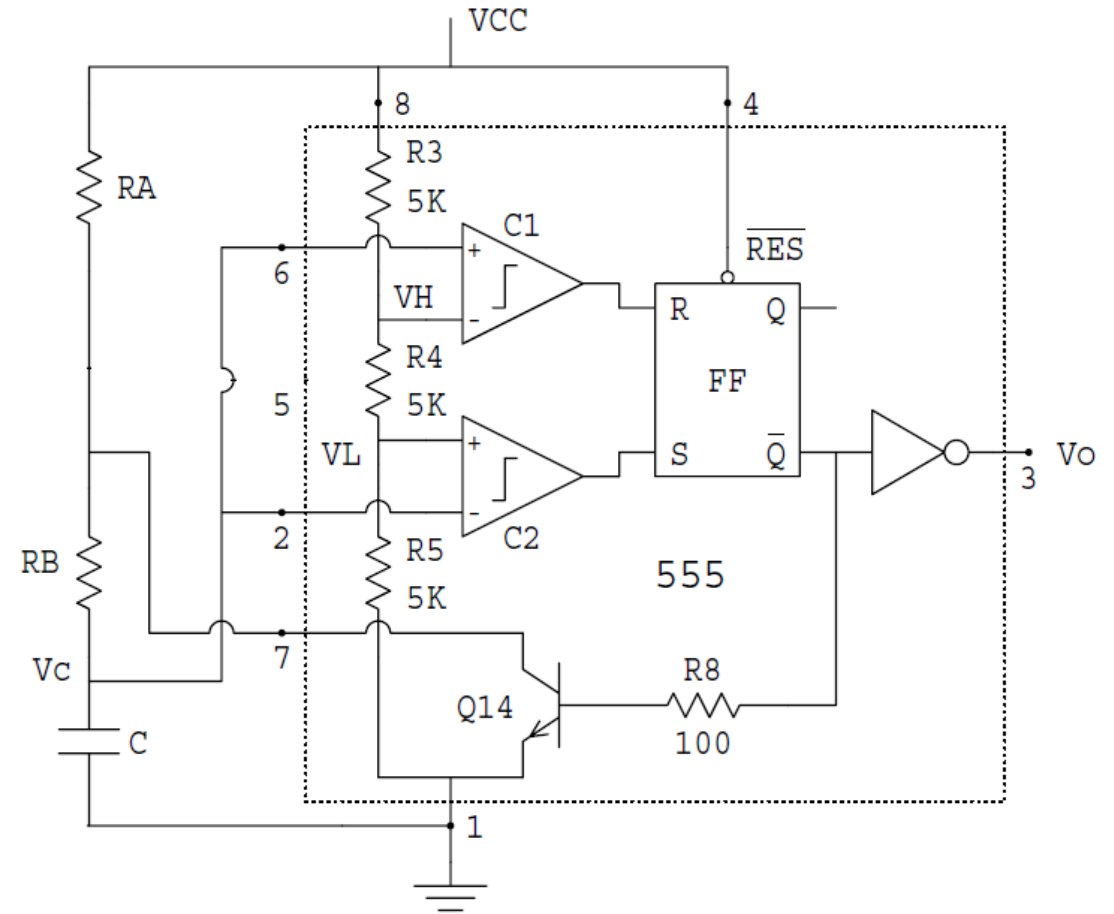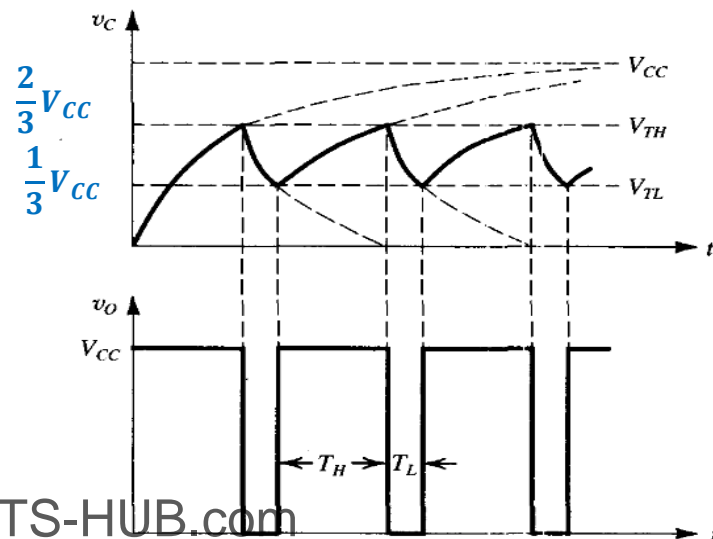





When  $V_C(t) < \frac{1}{3} V_{CC}$

$\therefore S = 1$ , and  $R = 0$

$\therefore Q = 1$ , and  $\bar{Q} = 0$

$\therefore$  The transistor turn Off

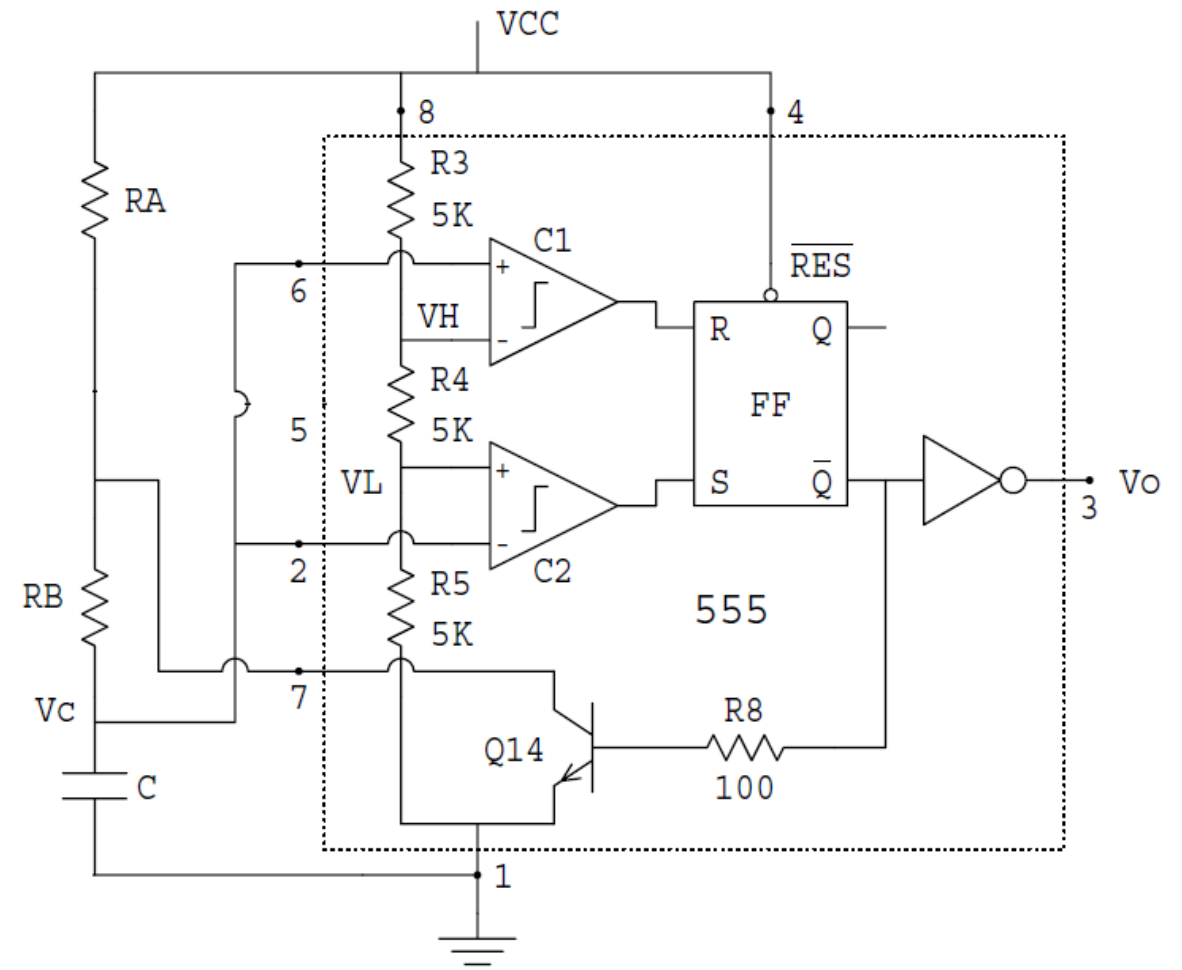
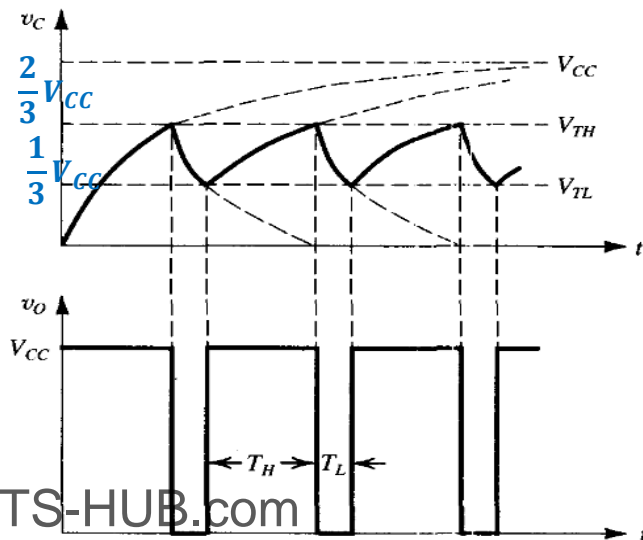
$\therefore$  The capacitor starts charging



# Oscillators

## The 555 Timer As an Oscillator.
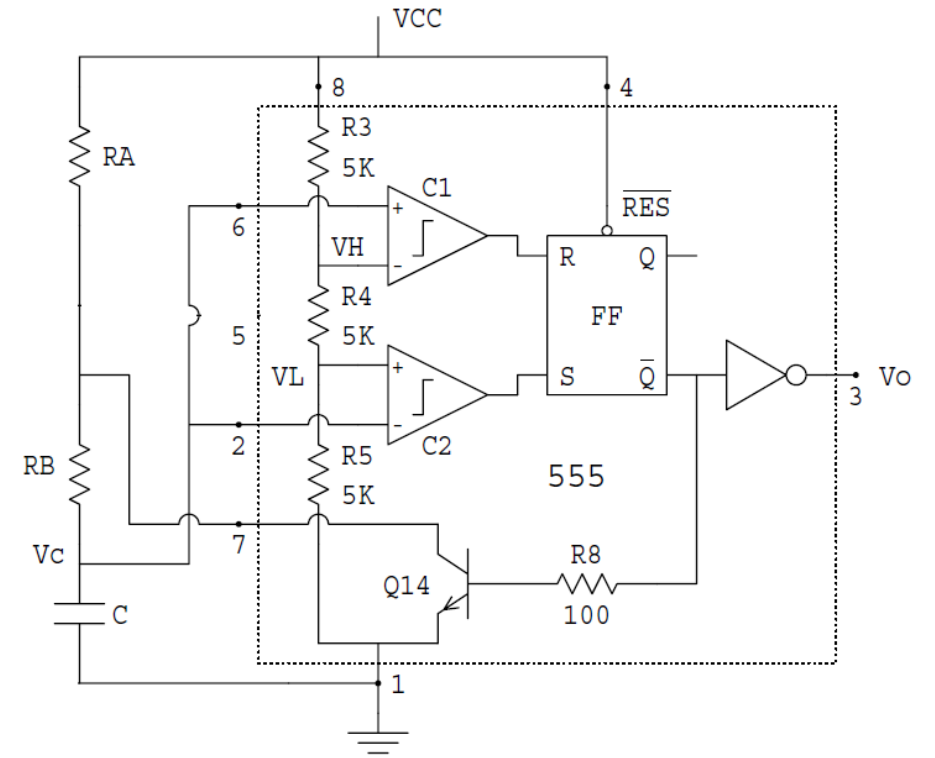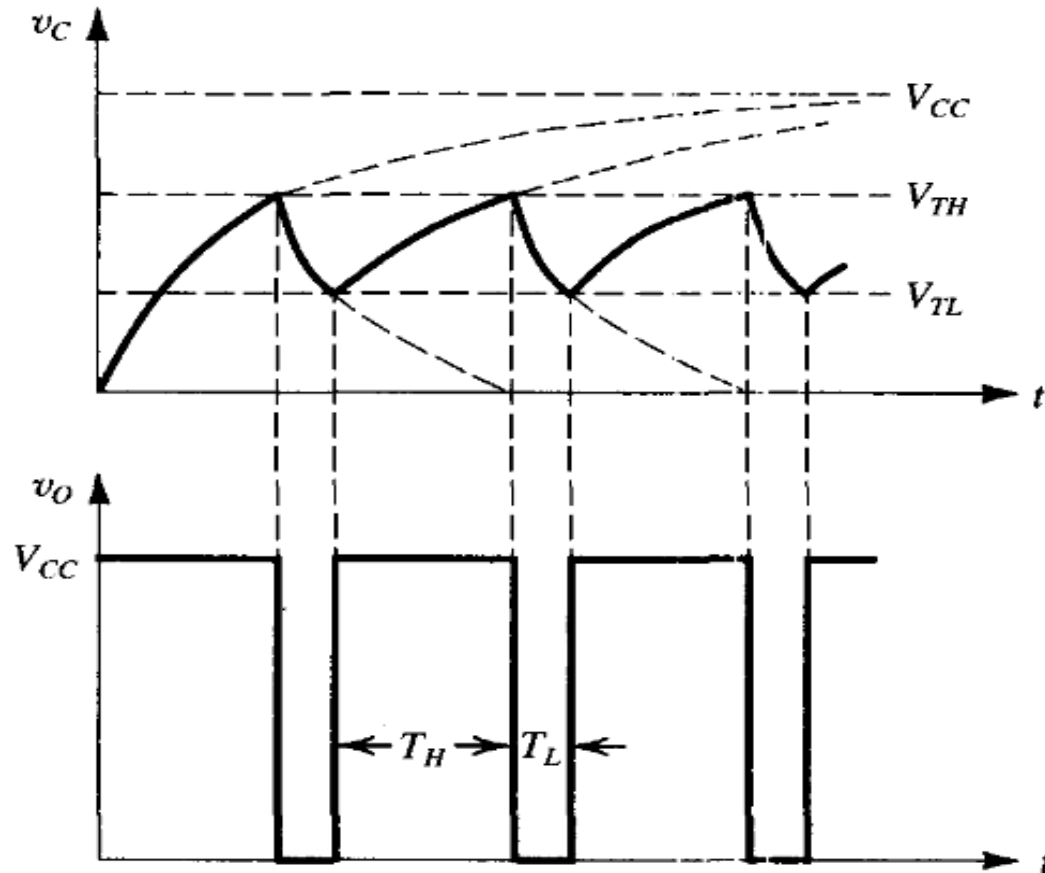
### Operation of the 555 timer oscillator.



# Oscillators

## The 555 Timer As an Oscillator.

### Operation of the 555 timer oscillator.

#### 1. To find $T_C$


$$V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$$

$$V_c(T_C) = \frac{2}{3}V_{CC} ; \quad V_I = \frac{1}{3}V_{CC} ; \quad V_f = V_{CC}$$

$$\tau_c = (R_A + R_B)C$$

$$V_c(T_C) = \frac{2}{3}V_{CC} = \frac{1}{3}V_{CC} + (V_{CC} - \frac{1}{3}V_{CC})(1 - e^{-\frac{t}{\tau}})$$
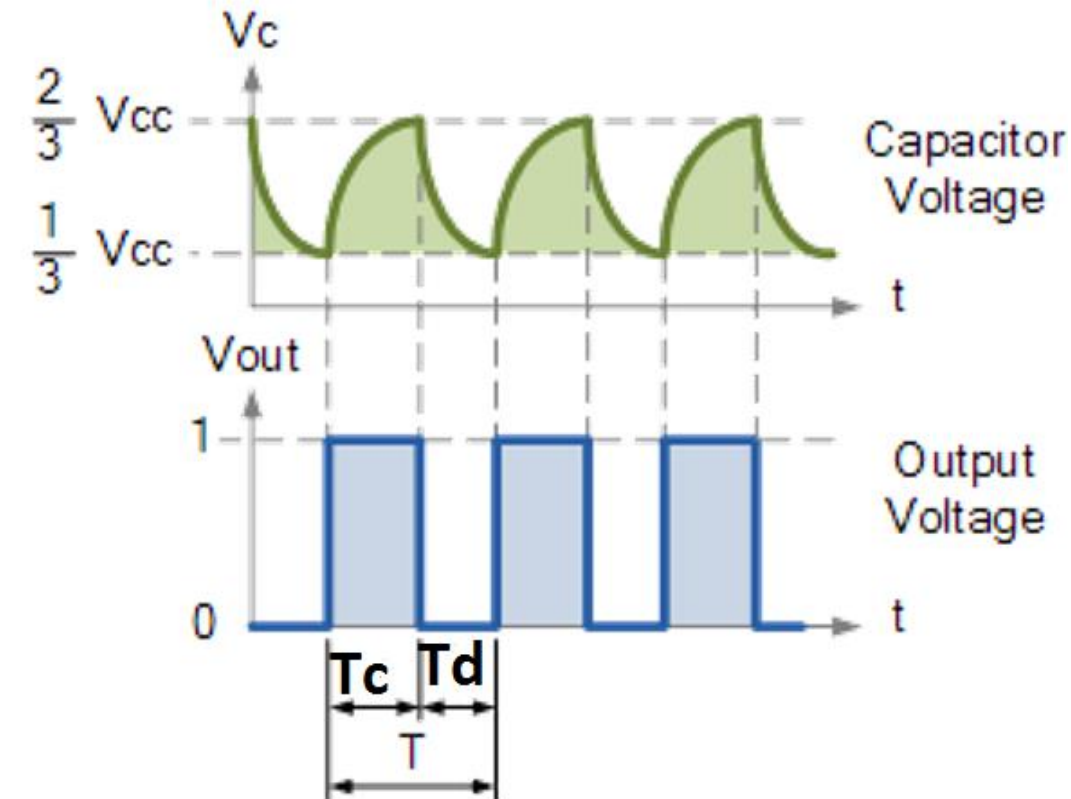
$$T_C = \tau_c \ln 2 = (R_A + R_B)C \ln 2$$



# Oscillators

## The 555 Timer As an Oscillator.

### Operation of the 555 timer oscillator.

#### 2-To find $T_d$


$$V_c(t) = V_I + (V_f - V_I)(1 - e^{-\frac{t}{\tau}})$$

$$V_c(T_d) = \frac{1}{3}V_{CC} ; \quad V_I = \frac{2}{3}V_{CC} ; \quad V_f = 0$$

$$\tau_d = R_B C$$

$$V_c(T_d) = \frac{1}{3}V_{CC} = \frac{2}{3}V_{CC} (0 - \frac{2}{3}V_{CC}) (1 - e^{-\frac{t}{\tau}})$$
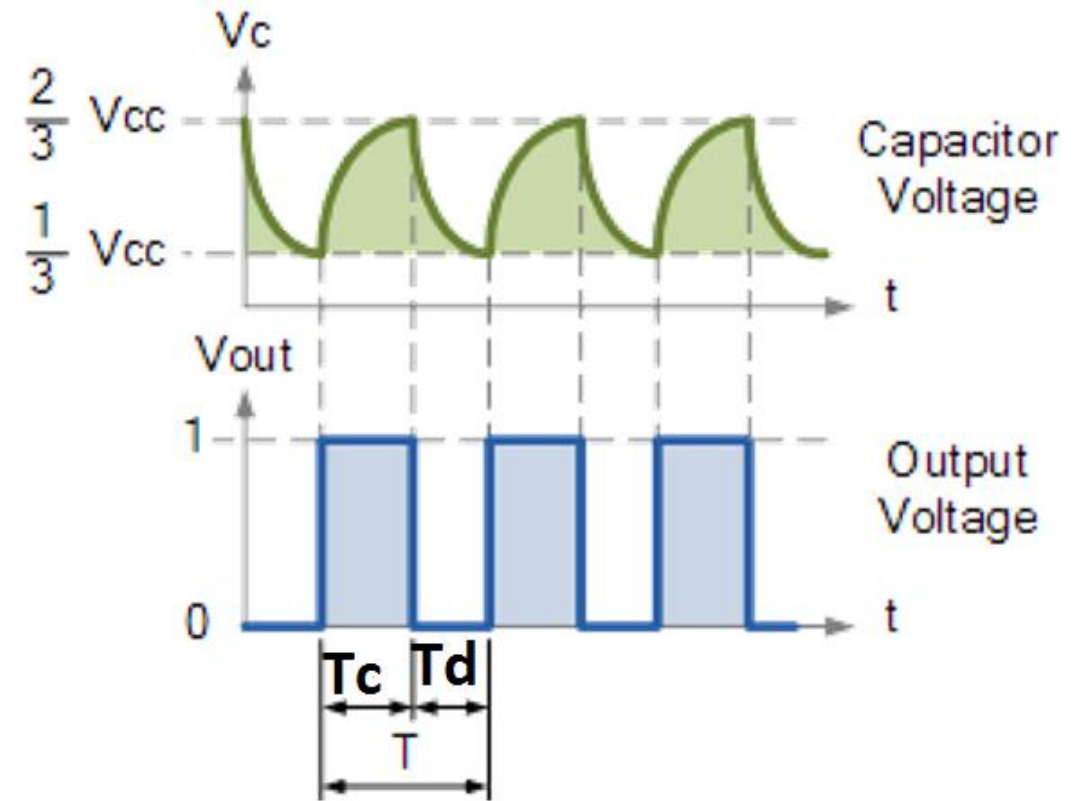
$$\therefore T_d = \tau_d \ln 2 = R_B C \ln 2$$



# Oscillators

## The 555 Timer As an Oscillator.

### Operation of the 555 timer oscillator.

#### 3- To find T

$$T = T_C + T_d = (R_A + 2R_B)C \ln 2$$

$$T = 0.693 (R_A + 2R_B)C$$


#### 4- To find F

$$F = \frac{1}{T} = \frac{1}{0.693 (R_A + 2R_B)C}$$

#### 5- To find Duty cycle

$$\text{Duty cycle} = D = \frac{T_C}{T} = \frac{R_A + R_B}{R_A + 2R_B}$$

# Function Generator

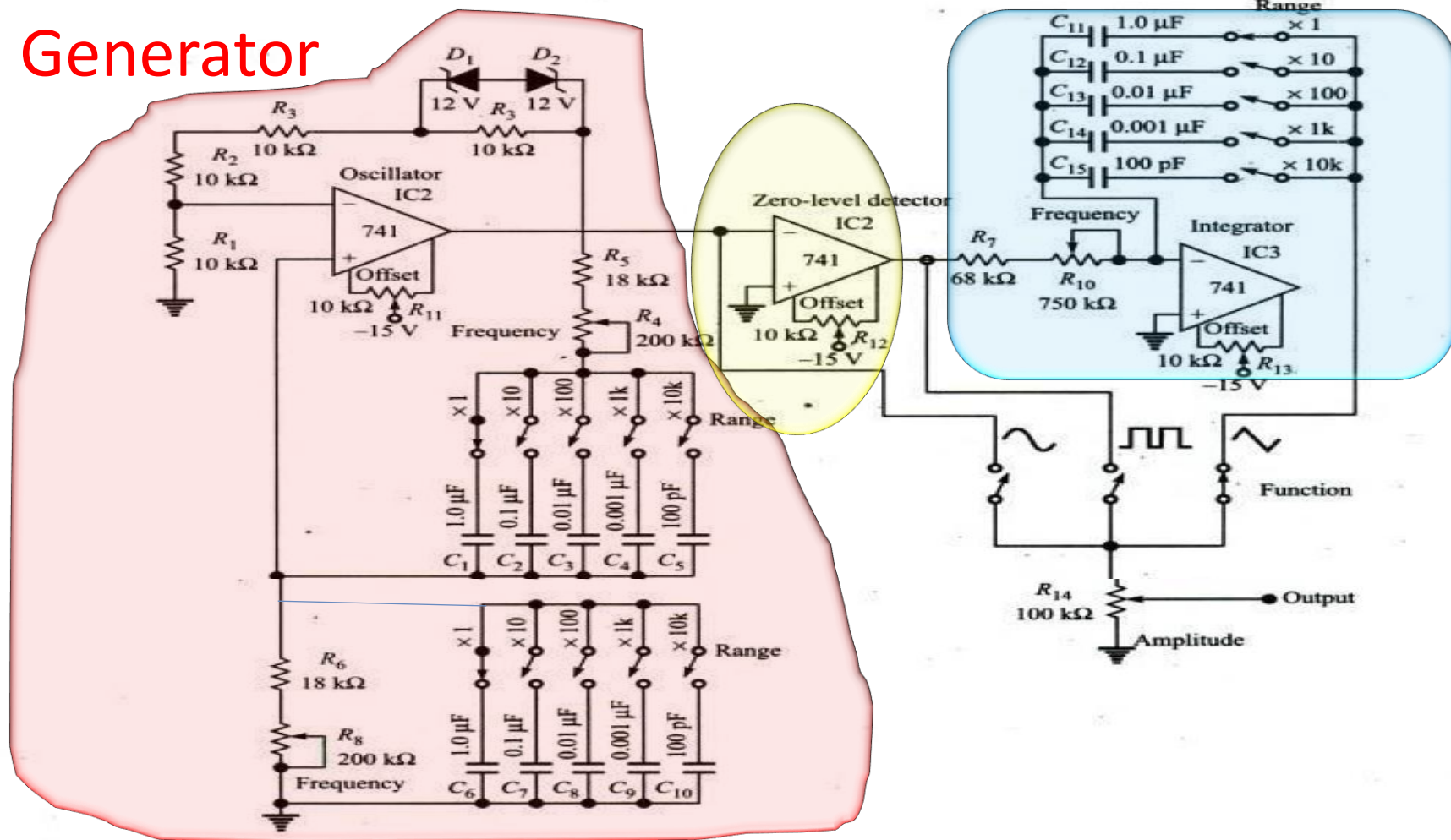

**Fig. 16.3** Schematic of the function generator

