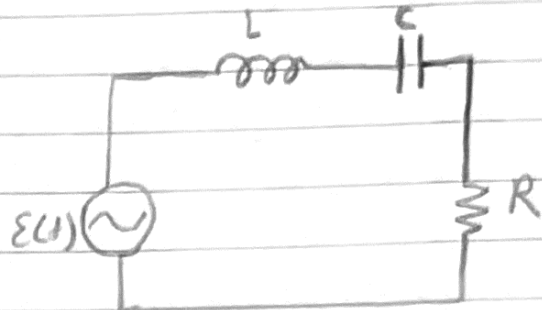


عنوان

## Experiment 9

①

### Resonance



$$* I(t) = \frac{E(t)}{Z_{eq}}$$

Amplitude

$$I_0 \cos(\omega t + \phi) = \frac{E_0 \cos(\omega t + \phi)}{Z_{eq}}$$

$$I_0 = \frac{E_0}{Z_{eq}} = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$I_0$ : the amplitude of the current passing through the circuit.

\*  $I_0$  has a maximum value when  $\omega L - \frac{1}{\omega C} = 0$

$$\Rightarrow \omega L = \frac{1}{\omega C} \quad \Rightarrow \omega^2 = \frac{1}{LC} \quad \Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$\omega_0$ : the natural angular frequency of the circuit

(2)

\* The current in the circuit assumes its maximum value when the driving voltage frequency equals the natural frequency of the RLC circuit. This phenomenon is called resonance.

⇒ At resonance  $\omega L - \frac{1}{\omega C} = 0$


⇒  $I_0 = \frac{E_0}{R}$

In other word Resonance is a phenomenon that occurs when the reactance of the capacitor and inductor is the same.

$\omega_0 = \frac{1}{\sqrt{LC}}$  (Resonance frequency)

↳ driving voltage

↳ natural freq from RLC circuit

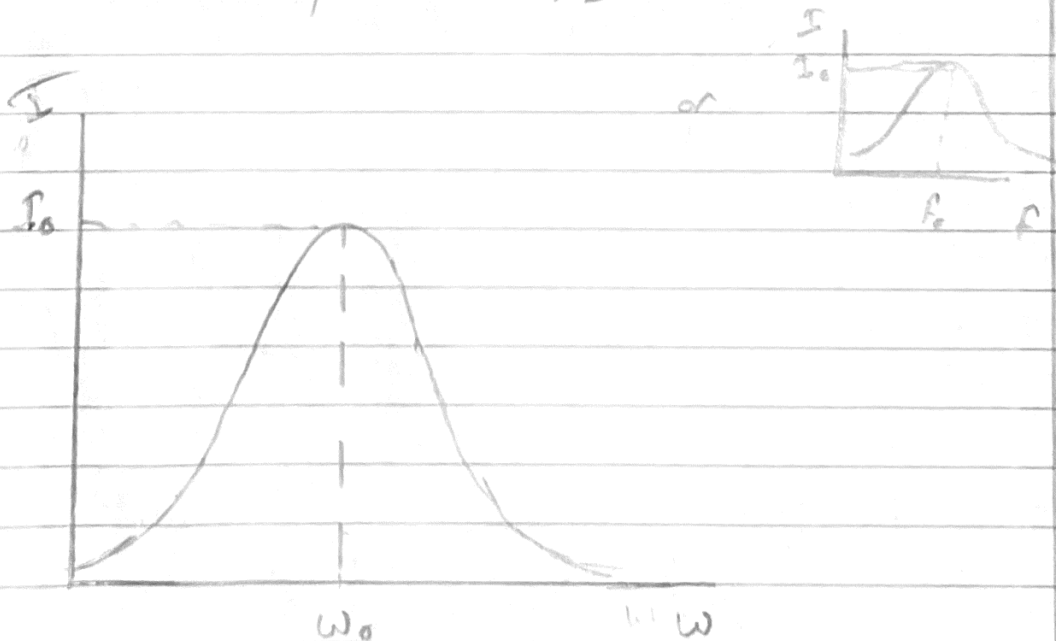

المعيار

« The quality Factor (Q) : A measure of the Sharpness of the resonance curve

كلما زاد Q كلما زاد الحدة Sharpness

$$Q = \frac{\omega L}{R} \quad \text{but } \omega = \frac{1}{\sqrt{LC}} \text{ at resonance}$$

$$Q = \frac{1}{R} \frac{L}{\sqrt{LC}}$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$


(Theo)  
القيمة النظرية

\* Experimentally

$$I_0 = \frac{E}{R}$$


$$I_{rms} = \frac{I_0}{\sqrt{2}} = 0.7 I_0$$

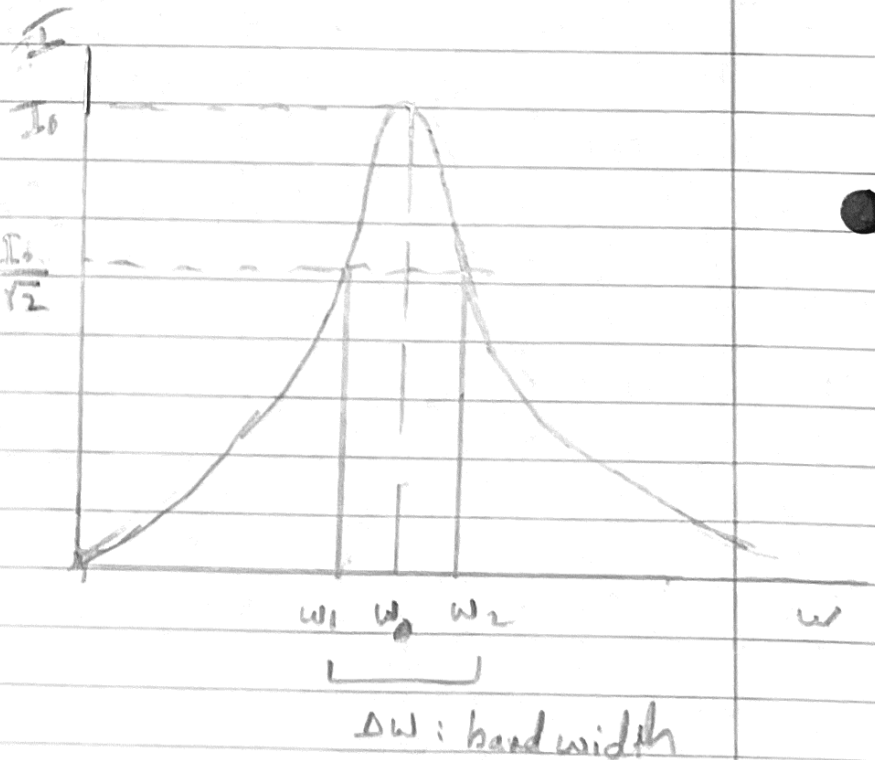هو التيار الذي يتدفق في  
الطاقة المترددة AC  
الطاقة المترددة AC



$$Q = \frac{\omega_0}{|\Delta\omega|}$$

or

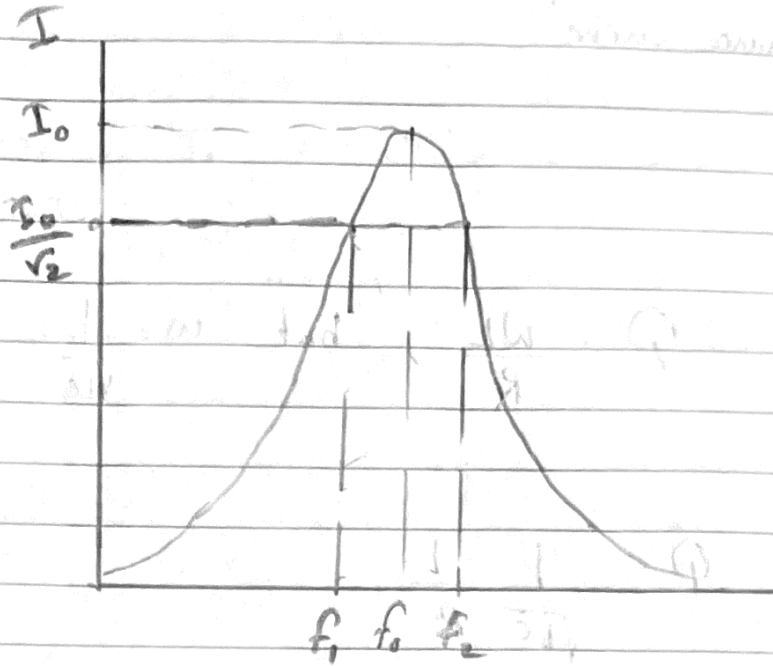

f  
Log scale

$$p = \frac{f_2 - f_1}{\Delta f}$$


(4)

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Just at resonance  $\left( \begin{array}{l} \text{سارو بيا} \\ \varphi = \frac{\omega L}{R}, \omega = \omega_0 = \frac{1}{\sqrt{LC}} \\ \varphi = \frac{1}{R} \sqrt{\frac{L}{C}} \end{array} \right)$

$Q \propto \sqrt{\frac{L}{C}} \Rightarrow Q$  is directly proportional to  $\sqrt{\frac{L}{C}}$

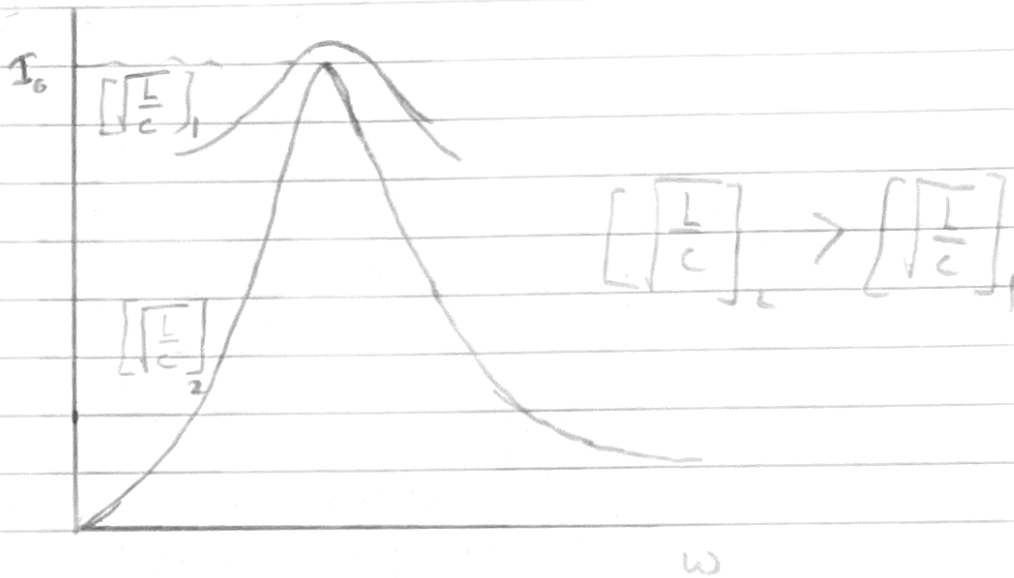Sharpness لاس زيادون  $Q$  لاس زيادون  $\sqrt{\frac{L}{C}}$



$$\left[ \sqrt{\frac{L}{C}} \right]_2 > \left[ \sqrt{\frac{L}{C}} \right]_1 \rightarrow Q_2 > Q_1$$

In fact from the sharpness we know that

$$Q_2 > Q_1 \text{ so that } \left[ \sqrt{\frac{L}{C}} \right]_2 > \left[ \sqrt{\frac{L}{C}} \right]_1$$


(5)

سوال کا جواب

$\phi \propto \frac{1}{R} \Rightarrow \phi$  is inversely proportional to  $R$

or  $\phi \propto \frac{1}{R}$

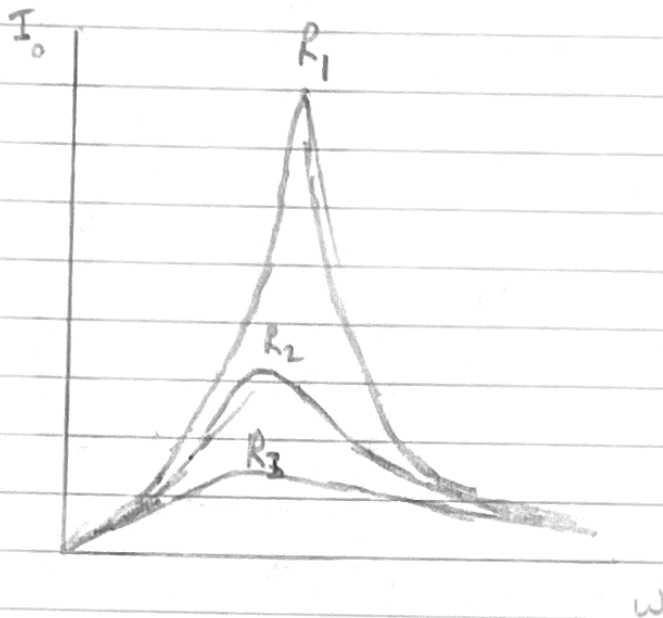sharpness of the  $\phi$  is inversely proportional to  $R$  i.e.,



$$\phi_1 > \phi_2 > \phi_3$$

$$\Rightarrow R_3 > R_2 > R_1$$

