

## Nodal and Mesh Analysis

- As Circuits get more Complicated, we need an organized method of applying KVL, KCL, and Ohm's
- Nodal analysis assigns voltages to each node then we apply KCL
- Mesh analysis assigns currents to each mesh, and then we apply KVL


# Nodal Analysis

## Steps to Determine Node Voltages:

1. Select a node as the **reference node**. Assign voltage  $V_1, V_2, \dots, V_{n-1}$  to the remaining  $n-1$  nodes. The voltages are referenced with respect to the reference node.
2. Apply **KCL** to each of the  $n-1$  **nonreference nodes**. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.
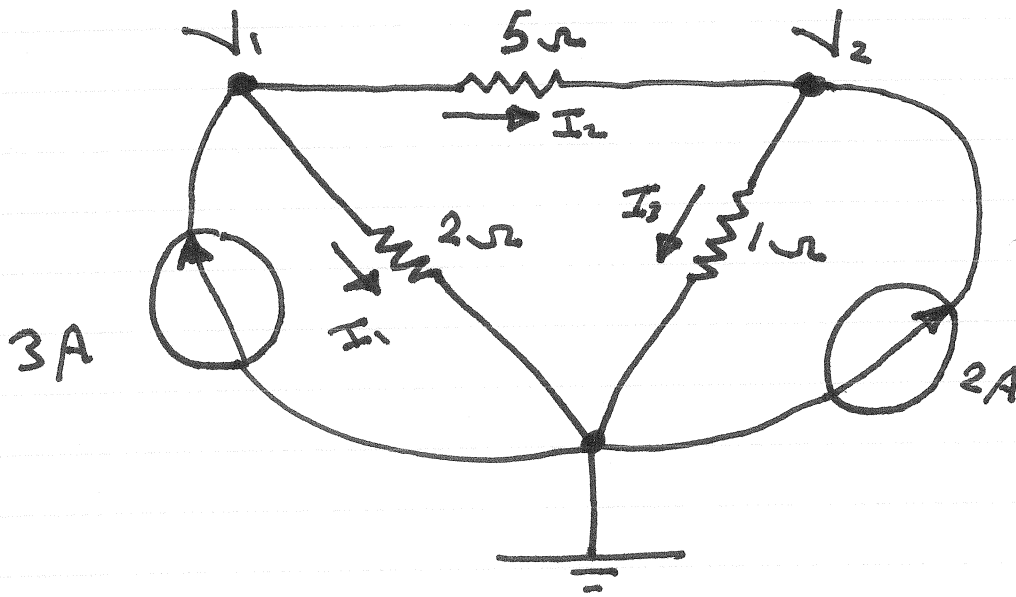
# The Nodal Analysis Method

assign voltages to every node relative to a reference node.



Apply KCL to node ①

$$3 = I_1 + I_2$$

$$3 = \frac{V_1}{2} + \frac{V_1 - V_2}{5}$$

$$3 = 0.7V_1 - 0.2V_2 \quad \text{--- ①}$$

Apply KCL to node ②

$$2 + I_2 = I_3$$

$$2 = I_3 - I_2$$


$$2 = \frac{V_2}{1} - \frac{V_1 - V_2}{5}$$

$$2 = -0.2V_1 + 1.2V_2 \quad \text{—————} \quad \textcircled{2}$$

Solving equations ① and ②, we get

$$V_1 = 5V$$

$$V_2 = 2.5V$$

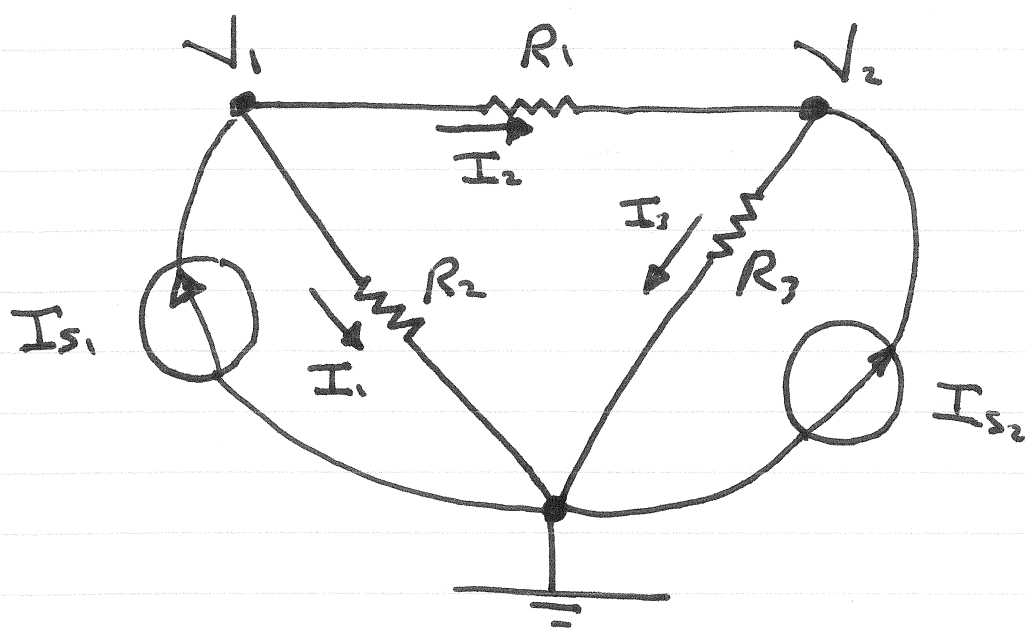

Applying KCL to node ①

$$I_{s1} = I_1 + I_2$$

$$I_{s1} = \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_1}$$

$$I_{s1} = \left( \frac{1}{R_2} + \frac{1}{R_1} \right) V_1 - \frac{1}{R_1} V_2$$

$$I_{s1} = (G_2 + G_1) V_1 - G_1 V_2$$

Self Conductance =  $G_2 + G_1$

mutual Conductance =  $-G_1$

Applying KCL to node ②

$$I_{s2} + I_2 = I_3$$

$$I_{s2} = I_3 - I_2$$

$$I_{s2} = \frac{V_2}{R_3} - \frac{V_1 - V_2}{R_1}$$

$$I_{s2} = -\frac{1}{R_1} V_1 + \left( \frac{1}{R_3} + \frac{1}{R_1} \right) V_2$$


$$I_{s2} = -G_1 V_1 + (G_3 + G_1) V_2$$

Self Conductance of node ② =  $(G_3 + G_1)$

mutual Conductance between nodes ① and ②

$$= -G_1$$

# Writing Nodal equations by inspection

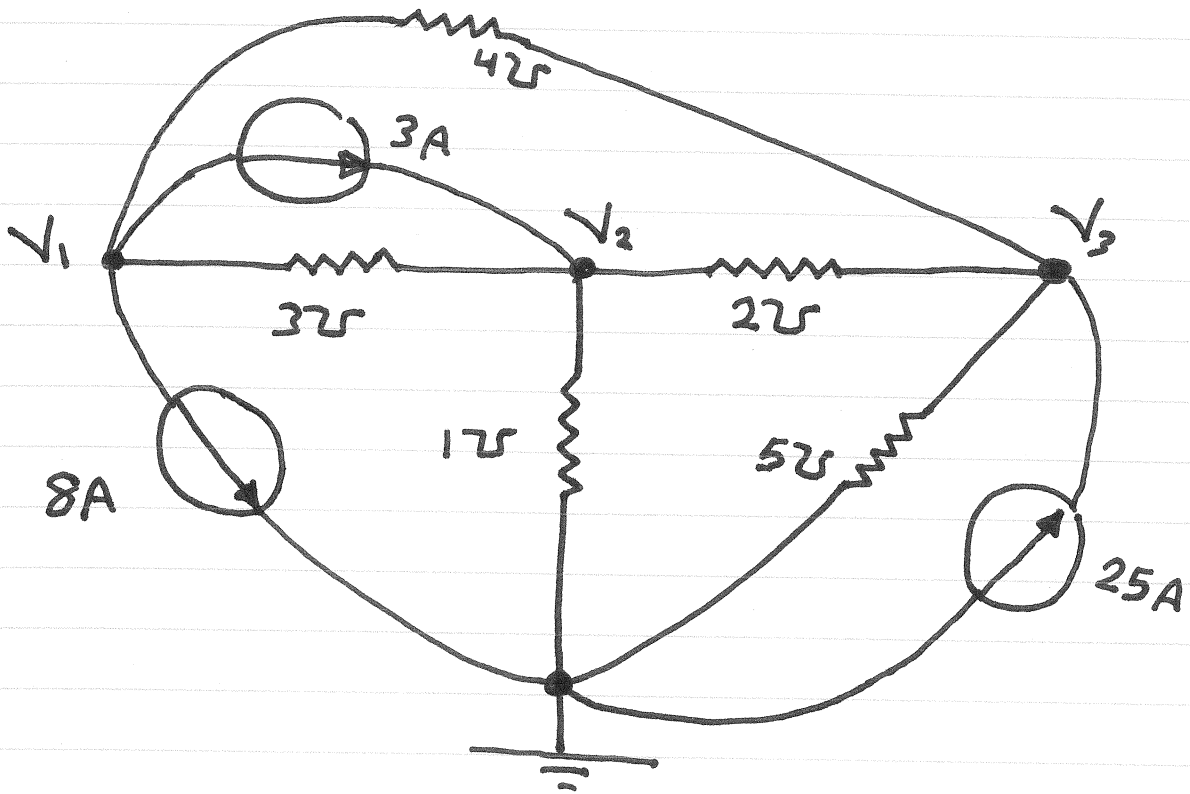

KCL at node ① :

$$7V_1 - 3V_2 - 4V_3 = -11$$

KCL at node ② :

$$-3V_1 + 6V_2 - 2V_3 = 3$$

KCL at node ③ :

$$-4V_1 - 2V_2 + 11V_3 = 25$$

Solving :

$$V_1 = 1\text{V} \quad ; \quad V_2 = 2\text{V} \quad ; \quad V_3 = 3\text{V}$$

# Nodal Analysis with Voltage Sources


**Case 1:** The voltage source is connected between a non reference node and the reference node: The non reference node voltage is equal to the magnitude of voltage source and the number of unknown non reference nodes is reduced by one.

**Case 2:** The voltage source is connected between two non referenced nodes: a generalized node (**supernode**) is formed.




# Nodal Analysis with Voltage Sources

A circuit with a **supernode**.

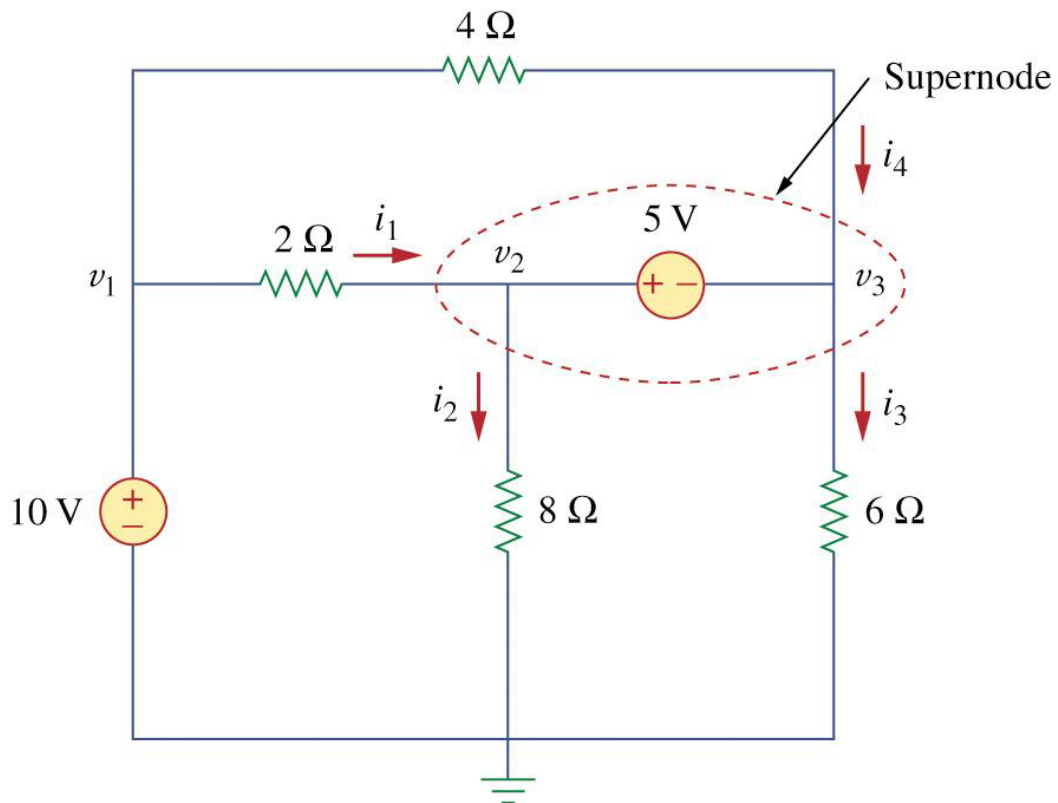

## Voltage Sources and the supernode

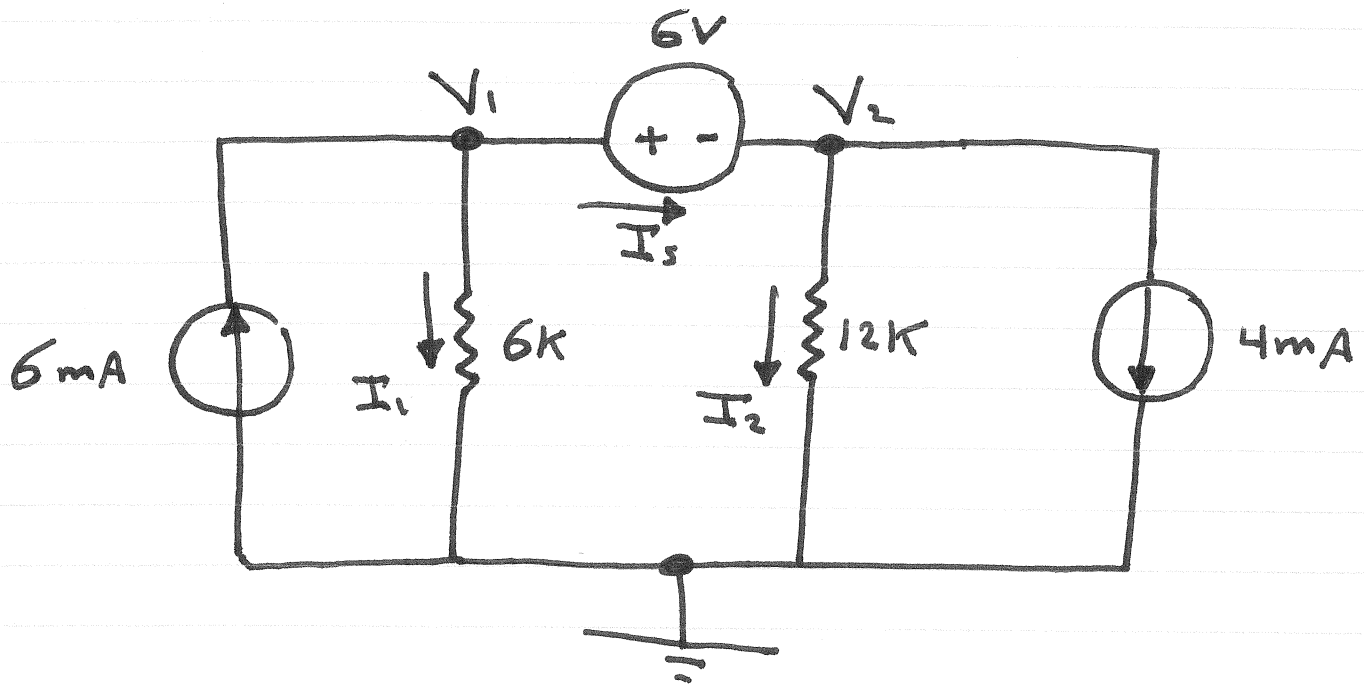

Constraint equation :

$$V_1 - V_2 = 6 \quad \text{--- (1)}$$

KCL at node (1) :

$$6mA = I_1 + I_s$$

$$6mA = \frac{V_1}{6K} + I_s \quad \text{--- (2)}$$

KCL at node (2) :

$$I_s = I_2 + 4mA$$

$$4mA = I_s - I_2$$

$$4 \text{ mA} = I_s - \frac{V_2}{12\text{K}} \quad \text{--- (3)}$$

Subtracting (3) from (2)

$$2 \text{ mA} = \frac{V_1}{6\text{K}} + \frac{V_2}{12\text{K}} \quad \text{--- (4)}$$

This is the supernode equation


Solving (1) and (4)

we get

$$V_1 = 10 \text{ V}$$

$$V_2 = 4 \text{ V}$$

# Supernode equation by inspection

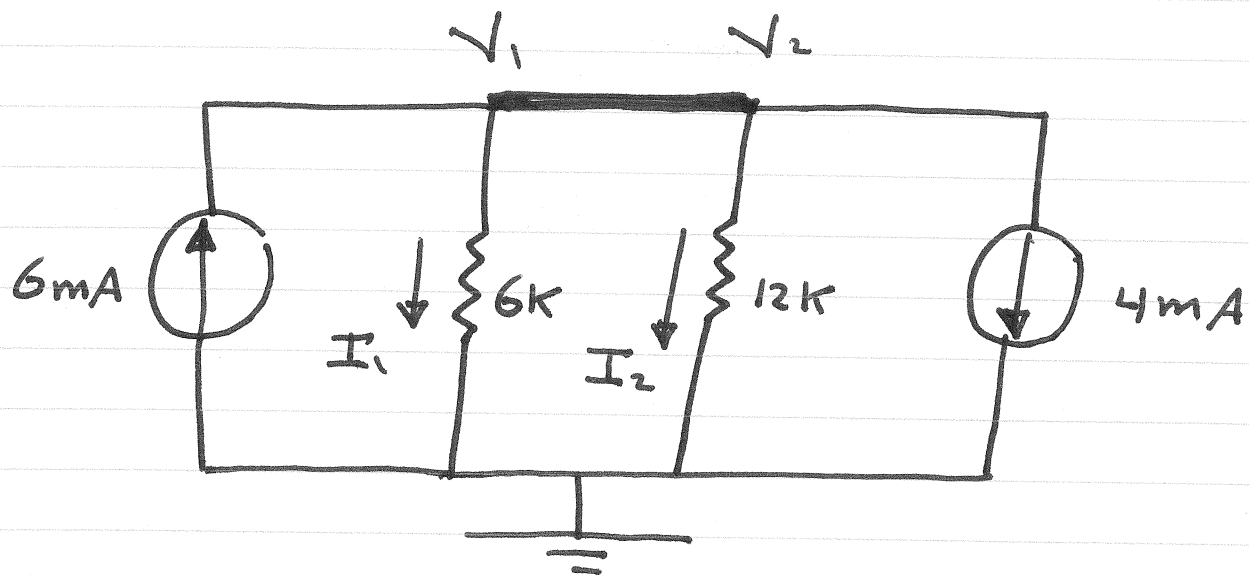


$$6\text{mA} = I_1 + I_2 + 4\text{mA}$$

$$2\text{mA} = I_1 + I_2$$

$$2\text{mA} = \frac{v_1}{6\text{k}} + \frac{v_2}{12\text{k}}$$

-72-

## Voltage Sources and the Supernode

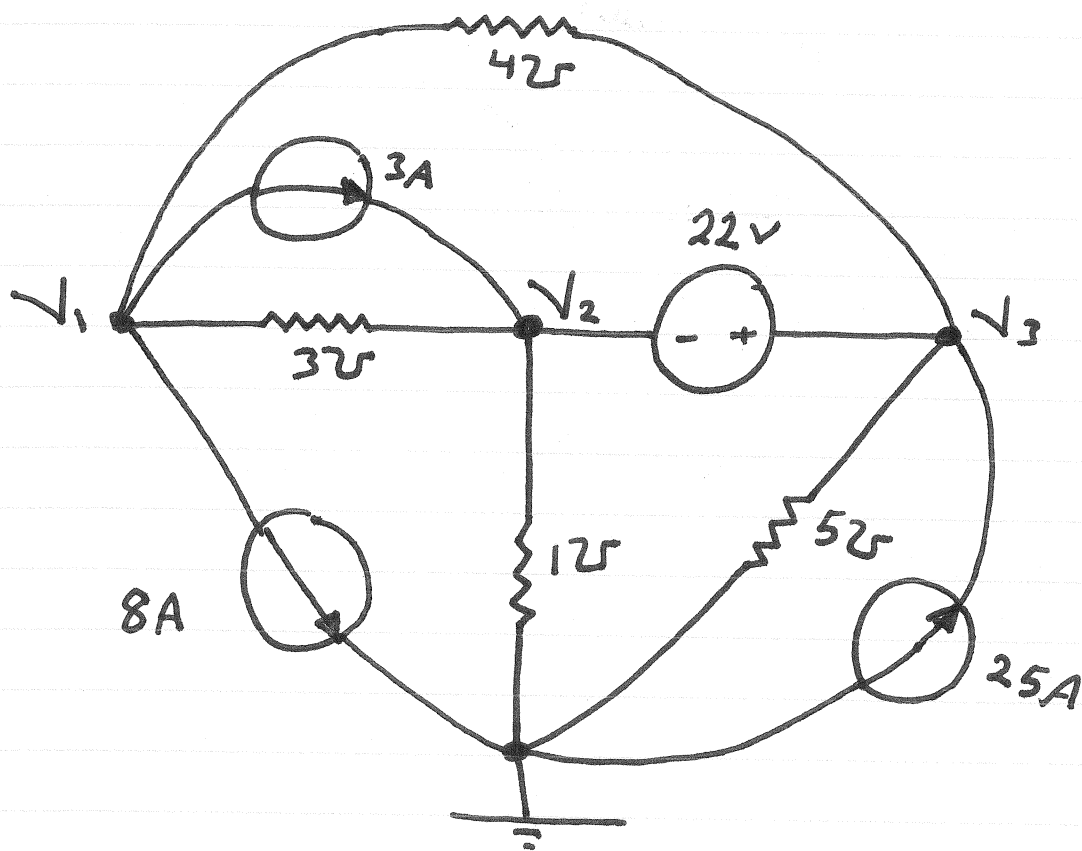

Constraint equation :

$$V_3 - V_2 = 22$$

KCL at node ① :


$$7V_1 - 3V_2 - 4V_3 = -11$$

Supernode equation :

$$-7V_1 + 4V_2 + 9V_3 = 28$$

Solving for  $V_1 \Rightarrow V_1 = -4.5\text{V}$


## Supernode equation by inspection

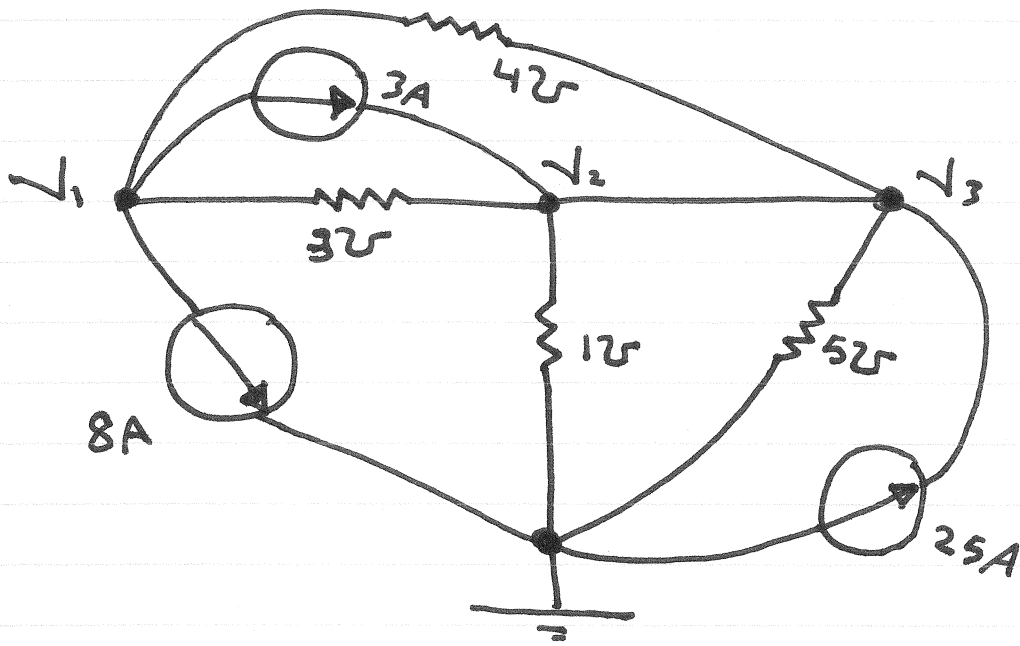

$$25 + 3 = (1 + 3)V_2 + (5 + 4)V_3 - (3 + 4)V_1$$

$$28 = 4V_2 + 9V_3 - 7V_1$$

## Circuits with dependent sources

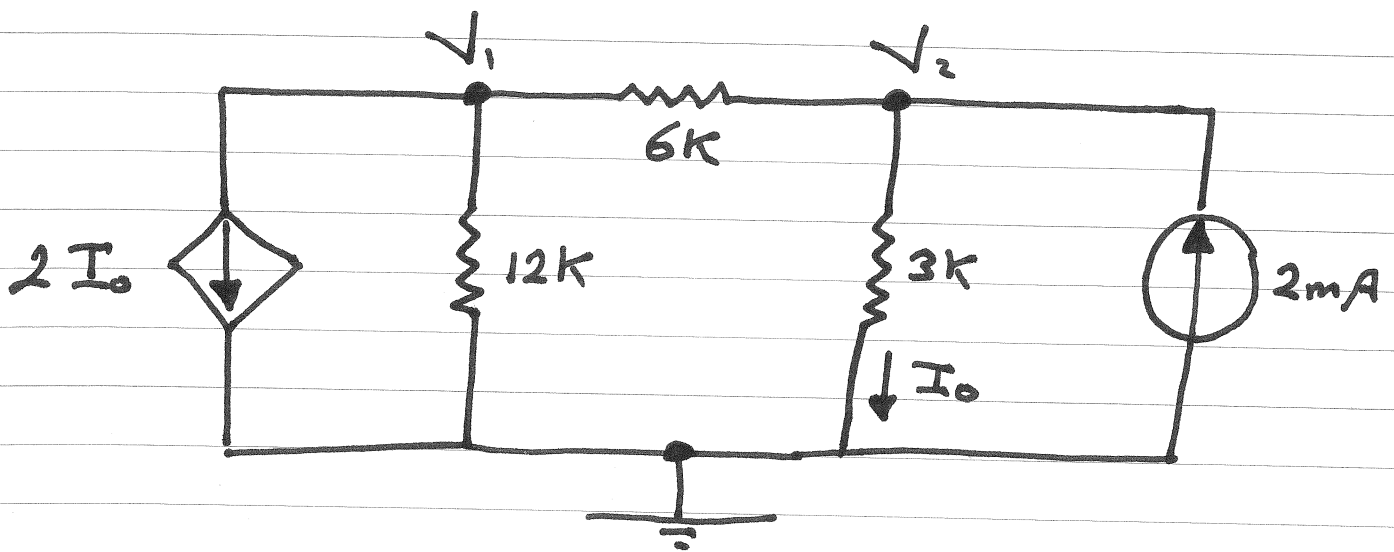

KCL at node 1 :

$$-2I_0 = \left( \frac{1}{12k} + \frac{1}{6k} \right) V_1 - \frac{1}{6k} V_2$$

$$I_0 = \frac{V_2}{3k}$$

$$0 = \left( \frac{1}{12k} + \frac{1}{6k} \right) V_1 + \left( \frac{2}{3k} - \frac{1}{6k} \right) V_2$$


KCL at node 2 :

$$2mA = -\frac{1}{6k} V_1 + \left( \frac{1}{3k} + \frac{1}{6k} \right) V_2$$

Solving for  $V_1$  and  $V_2$ , we get

$$V_1 = -\frac{24}{5} V ; \quad V_2 = \frac{12}{5} V$$

# Nodal Analysis : Supernode

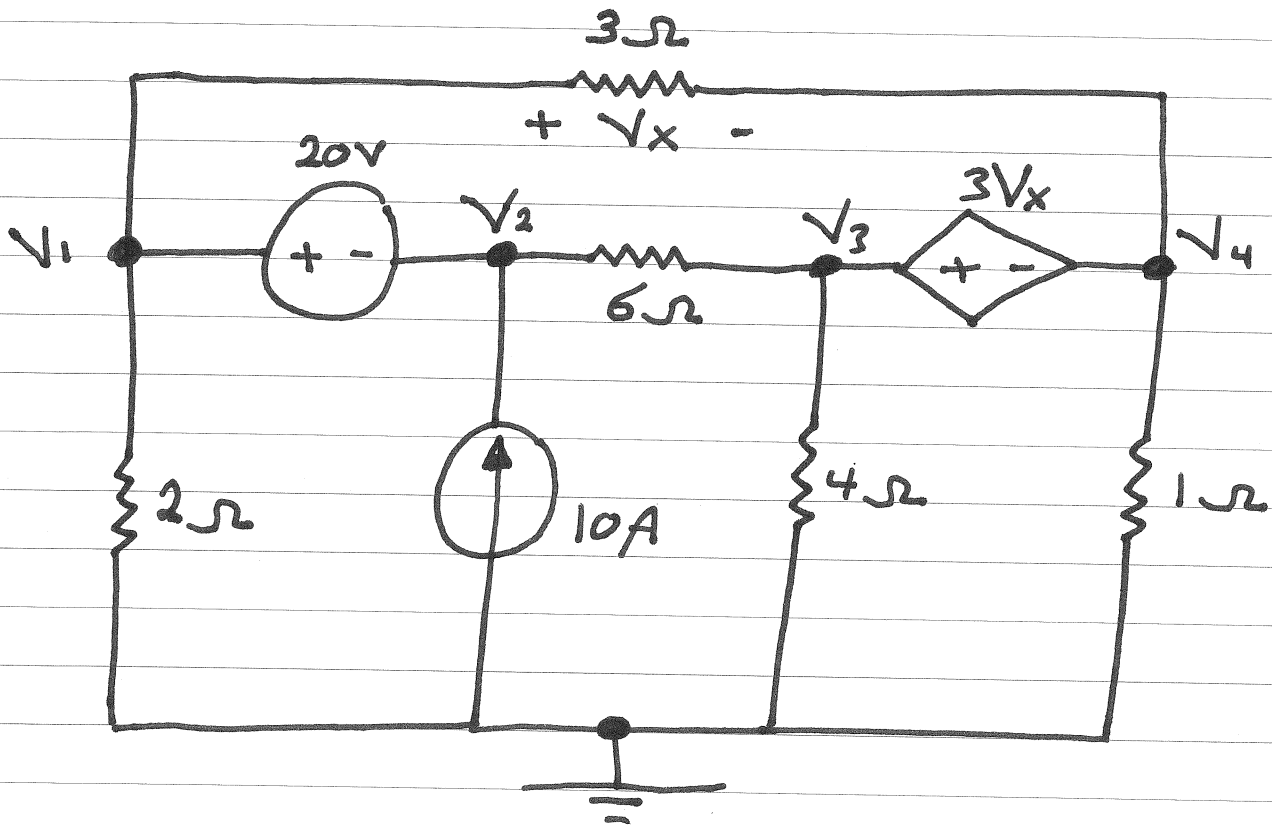

KCL at Supernode 1,2 :

$$10 = \left(\frac{1}{2} + \frac{1}{3}\right)V_1 + \frac{1}{6}V_2 - \frac{1}{6}V_3 - \frac{1}{3}V_4$$

KCL at Supernode 3,4 :

$$0 = \left(\frac{1}{4} + \frac{1}{6}\right)V_3 + \left(\frac{1}{1} + \frac{1}{3}\right)V_4 - \frac{1}{6}V_2 - \frac{1}{3}V_1$$

Constraint equation :

$$V_1 - V_2 = 20$$



Constrain equation :

$$-V_3 - V_4 = 3V_x$$

$$V_x = V_1 - V_4$$

$$0 = 3V_1 - V_3 - 2V_4$$

What is the current through the independent voltage source ?