



BIRZEIT UNIVERSITY

Electrical and Computer Engineering Department  
Circuits Analysis ENEE 2304

Short Exam # 1 (10 minutes)

Student Name:

ID:


8<sup>th</sup> Oct, 2024

**Problem 1:** For the circuit shown is a FET common-source amplifier or BJT common-emitter amplifier.

If  $R_1 = 100 \Omega$ ,  $R_2 = 1k\Omega$ ,  $g_m = 0.04S$ ,  $R_3 = 50k\Omega$ , and  $R_4 = R_5 = 10 k\Omega$ , and  $V_s = 12V$ , then use Kirchhoff's laws and Ohm's law and series/parallel reduction to:

A) Find  $V_o$ , and  $I_x$

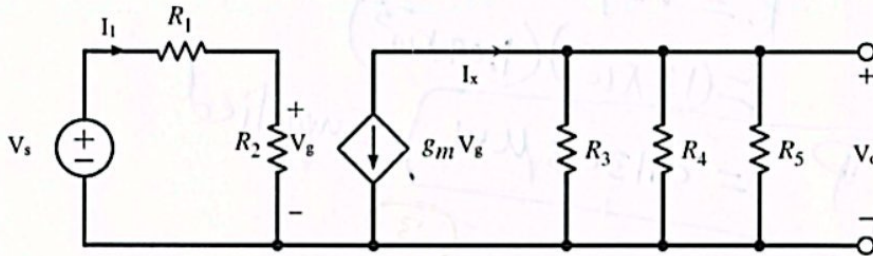B) Calculate the power of the  $V_s$  source, state whether it is supplied or absorbed!



To find  $I_1$

$$-V_s + R_1 I_1 + R_2 I_1 = 0$$


$$-12 \times 10^3 + 100 I_1 + 1000 I_1 = 0$$

$$I_1 = \frac{12 \times 10^3}{1.1k} = 1.09 \times 10^{-5} A \quad (3)$$

$$V_g = I_1 R_2 = 1.09 \times 10^{-5} (1k) = 0.0109V$$

$$I_x = -g_m V_g$$
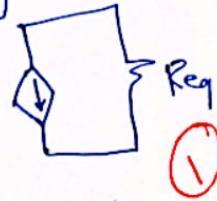
$$I_x = -0.04 (0.0109) = -4.36 \times 10^{-4} A$$




$$\frac{1}{R_{eq}} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \Rightarrow R_{eq} = 4.545k$$

$$V_o = (-g_m V_g) R_{eq}$$

$$= (-4.36 \times 10^{-4}) 4545k$$

$$V_o = (-g_m V_g) R_{eq}$$

$$= (-4.36 \times 10^{-4}) 4545k$$

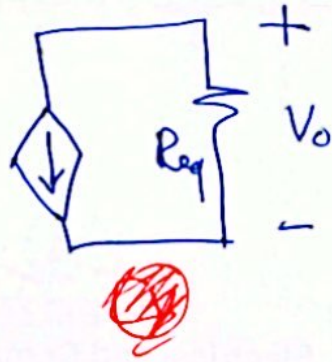

$$V_o = -1.98V$$

B) Power supplied by  $V_s$

$$P = VI$$

$$= (12 \times 10^{-3})(1.09 \times 10^{-5})$$

$$P = 0.1308 \mu W$$

Supplied