



Birzeit University
Faculty of Engineering and Technology
Department of Electrical and Computer Engineering
Circuit Analysis – ENEE 2304
Quiz #4

1 February 2023


Dr. Jaser Sa'ed

Time: 10 min

Student Name:

ID Number:

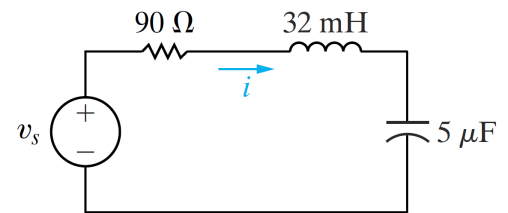A 90Ω resistor, a 32 mH inductor, and a $5 \mu\text{F}$ capacitor are connected in series across the terminals of a sinusoidal voltage source, as shown in the Fig. . The steady-state expression for the source voltage v_s is $750 \cos(5000t + 30^\circ) \text{ V}$.



- Construct the frequency-domain equivalent circuit.
- Calculate the steady-state current i by the phasor method.

Solution

- From the expression for v_s , we have $\omega = 5000 \text{ rad/s}$. Therefore the impedance of the 32 mH inductor is

$$Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \Omega,$$


and the impedance of the capacitor is

$$Z_C = j \frac{-1}{\omega C} = -j \frac{10^6}{(5000)(5)} = -j40 \Omega.$$

The phasor transform of v_s is

$$\mathbf{V}_s = 750 \angle 30^\circ \text{ V}.$$

Figure 9.16 illustrates the frequency-domain equivalent circuit of the circuit shown in Fig. 9.15.

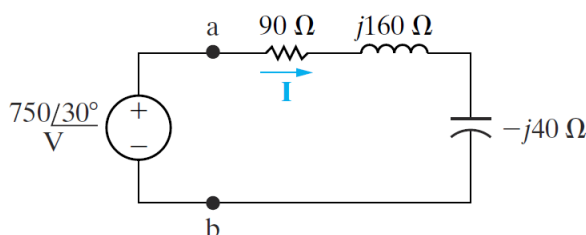

- We compute the phasor current simply by dividing the voltage of the voltage source by the equivalent impedance between the terminals a,b. From Eq. 9.45,

$$\begin{aligned} Z_{ab} &= 90 + j160 - j40 \\ &= 90 + j120 = 150 \angle 53.13^\circ \Omega. \end{aligned}$$

Thus

$$\mathbf{I} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A}.$$

We may now write the steady-state expression for i directly:

$$i = 5 \cos(5000t - 23.13^\circ) \text{ A}.$$