


Isp, Lu

Experiment 6

Capacitors and Inductors

Ⓐ RC circuits : A circuit that contains a resistor and capacitor connected in series and powered by power supply but in our experiment by signal generator

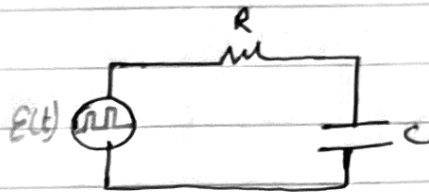Ⓜ Charging capacitor
During the positive half period of the square wave




The voltage across the capacitor

$$V_c = \frac{Q}{C}$$

$$Q = \epsilon C (1 - e^{-t/RC})$$
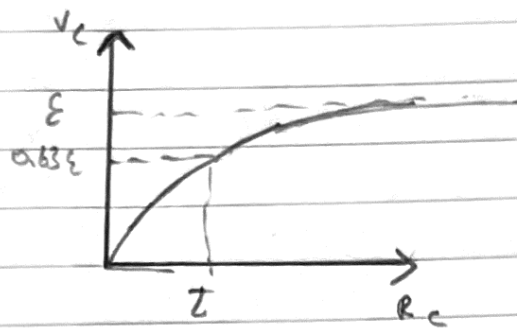
$$\Rightarrow V_c = \epsilon (1 - e^{-t/RC})$$



- at $t=0 \rightarrow V_c = \epsilon(1 - e^0) = 0$
- at $t = \infty \rightarrow V_c = \epsilon(1 - e^{-\infty}) = \epsilon$
- at $t = T = RC \rightarrow V_c = \epsilon(1 - e^{-\frac{RC}{RC}}) = 0.63 \epsilon$

T : time constant is a measure of how fast the voltage across the capacitor rises or how fast the charging is
 \times time constant : the time needed for the potential difference on capacitors to reach 0.63 of the max voltage ϵ


سوال 2

The voltage across the resistor

V_R = IR, I = dQ/dt, Q = Cε(1 - e^{-t/RC})

V_R = dQ/dt * R = εε/R * e^{-t/RC} * R

V_R = ε e^{-t/RC}

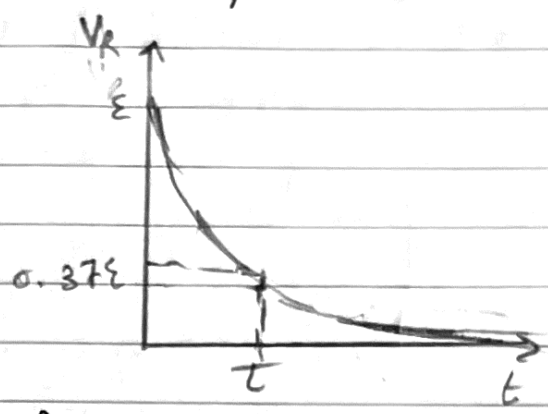

- at t=0 -> V_R = ε e^0 = ε
• at t=∞ -> V_R = ε e^{-∞} = 0
• at t=RC -> V_R = ε e^{-1} = 0.37ε

Discharging a capacitor


(During the negative half period of the square wave)

Q(t) = Cε e^{-t/RC}


The voltage across the capacitor

V_C = Q/C = ε e^{-t/RC}

V_C = ε e^{-t/RC}

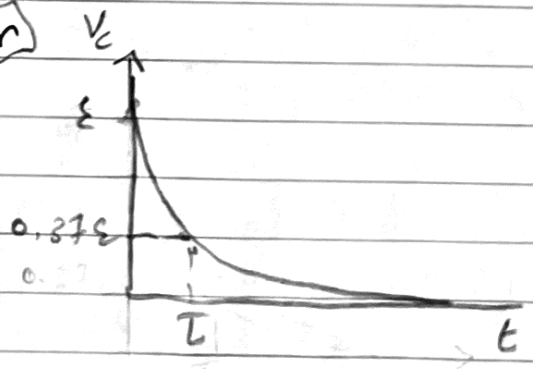


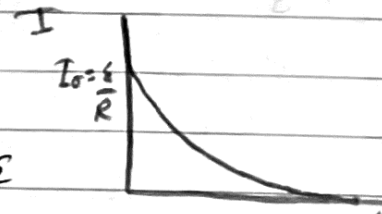- at t=0 -> V_C = ε e^0 = ε
• at t=∞ -> V_C = ε e^{-∞} = 0
• at t=RC (=τ) -> V_C = ε e^{-1} = 0.37ε



τ: a measure of how fast the voltage across capacitor decreases

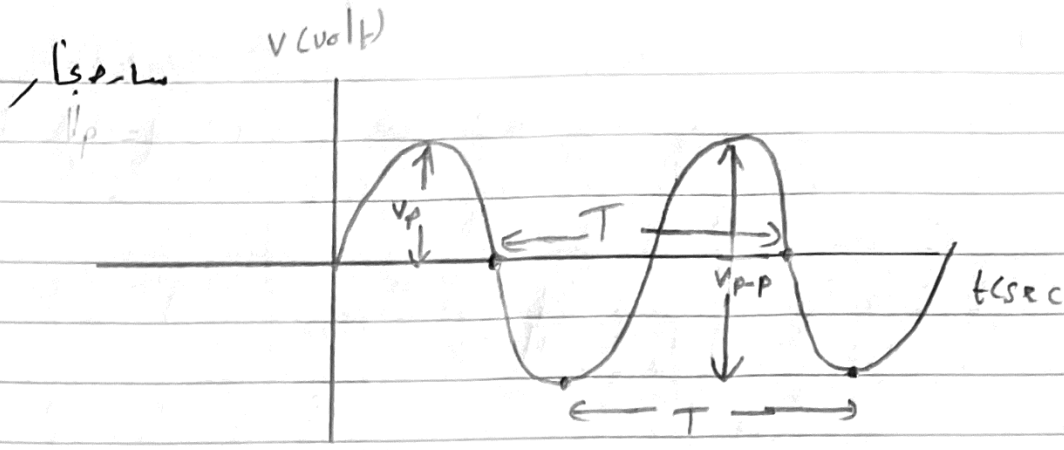τ: the time needed for potential difference on capacitor to reach 0.37 of the max voltage




$$f = \frac{1}{T} \quad (\text{unit: Hz})$$


$$V_{p-p} = 2\sqrt{2} V_{rms}$$

$$V_{rms} = \frac{1}{2\sqrt{2}} V_{p-p}$$

$$V_{rms} = \frac{1}{\sqrt{2}} V_p$$

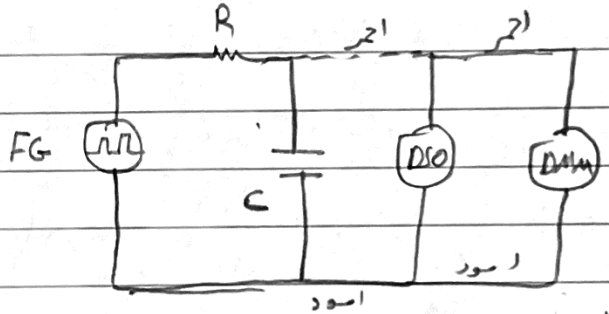

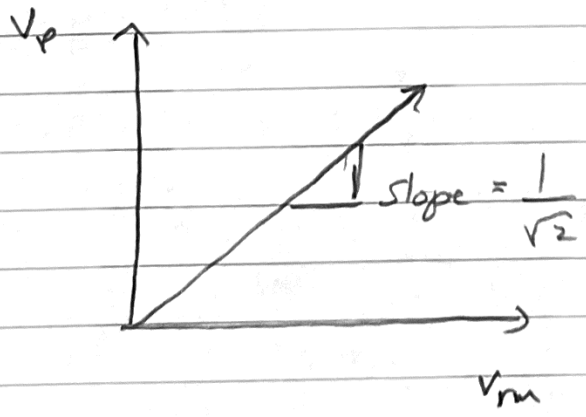قراءة DMM
 هي V_{rms}
 قراءة DSO
 هي V_p
 او V_{p-p}



هي قيمه الجهد التي تكون عندها V_{rms}
 هي الطاقة الكهربائية عندها يمر به DC voltage
 هي نفس قيمه الطاقة الكهربائية عندها يمر
 AC voltage

(4)

بنا و لسا

The voltage across the Resistor



V_R = IR , I = dQ/dt , Q = Cε e^{-t/RC} dis

V_R = dQ/dt R


V_R = -1/RC Cε e^{-t/RC} R , I = dQ/dt = -ε/R e^{-t/RC}

V_R = -ε e^{-t/RC}

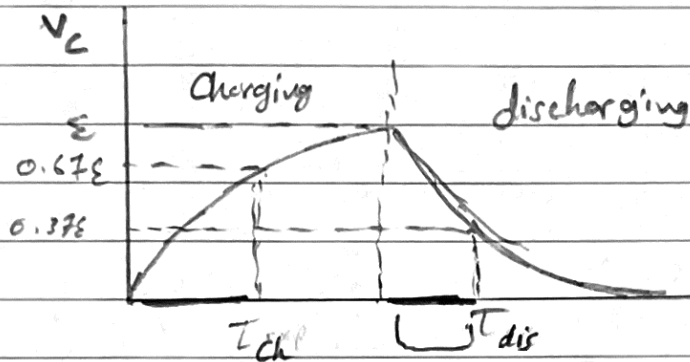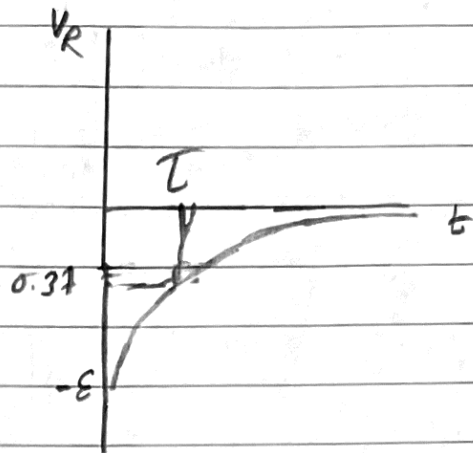- at t=0 = -ε e^0 = -ε
• at t=∞ = -ε e^{-∞} = 0
• at t=RC = -ε e^{-1} = 0.37ε




T_exp = (T_ch + T_dis) / 2 , T_theo = RC

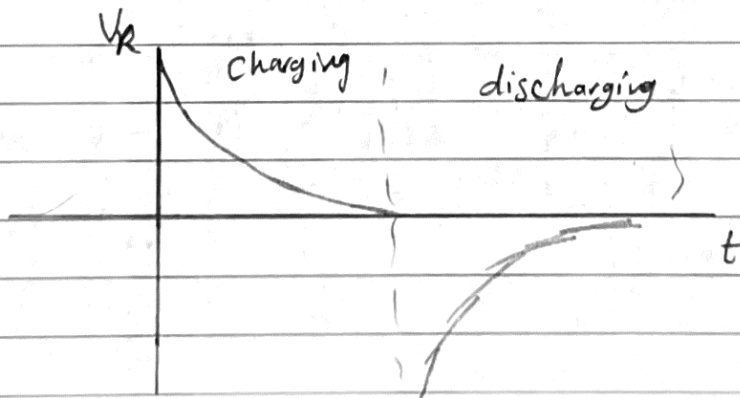

ⓑ RL Circuit: A circuit that contains an inductor connected in series with a resistance and powered by a power supply but in our experiment by a signal generator
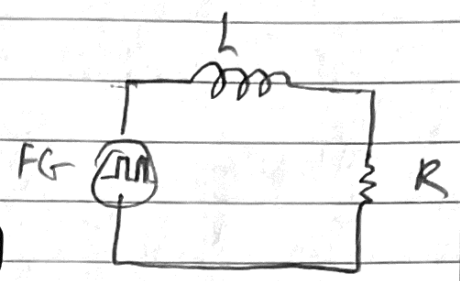
$$I(t) = \frac{\epsilon}{R} (1 - e^{-Rt/L})$$



The voltage across the inductor L


$$V_L = L \frac{dI}{dt} = L \frac{\epsilon}{R} \frac{R}{L} e^{-Rt/L}$$

$$\Rightarrow V_L = \epsilon e^{-Rt/L}$$

• at $t=0 \rightarrow V_L = \epsilon e^0 = \epsilon$

• at $t=\infty \rightarrow V_L = \epsilon e^{-\infty} = 0$

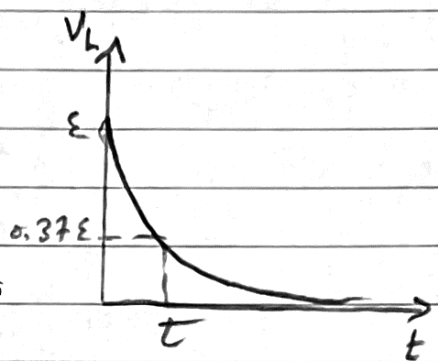• at $t=\tau = \frac{L}{R} \rightarrow V_L = \epsilon e^{-1} = 0.37 \epsilon$



τ : a measure of how fast the current rises in the circuit

The voltage across the resistor R

$$V_R = IR = \frac{\epsilon}{R} (1 - e^{-Rt/L}) R$$

$$V_R = \epsilon (1 - e^{-Rt/L})$$




• at $t=0 \rightarrow V_R = \epsilon (1 - e^0) = 0$

(B)

3, 4, 5

- at $t = \infty \rightarrow V_R = \epsilon (1 - e^{-\infty}) = \epsilon$

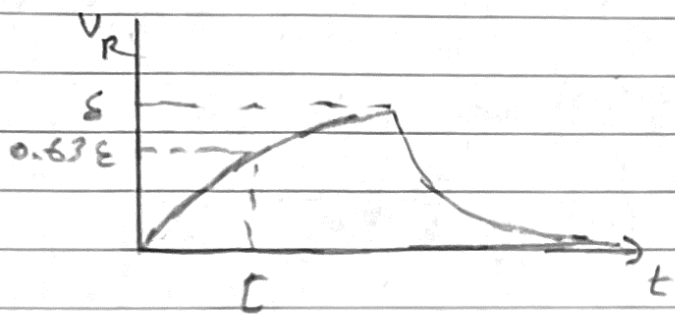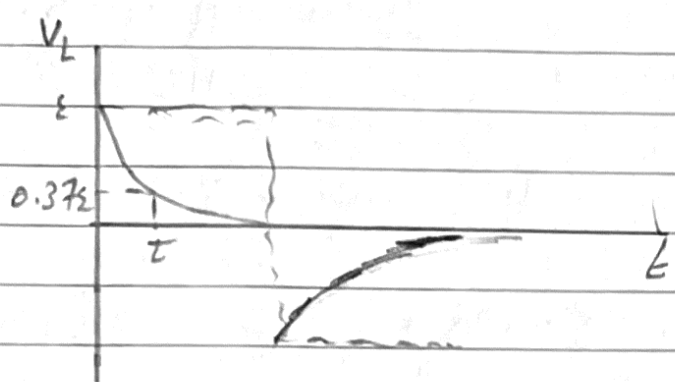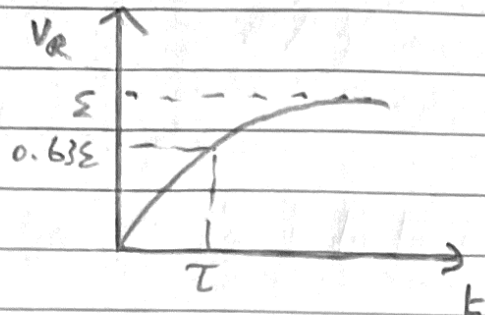- at $t = \frac{L}{R} \rightarrow V_R = \epsilon (1 - e^{-1}) = 0.63 \epsilon$



$$\tau_{\text{exp}} = \tau_{\text{th } R} + \tau_{\text{dis } R/L}$$

$$\tau_{\text{th } R} = \frac{L}{R}$$


$$\tau_{\text{th } R} = L/R$$

7

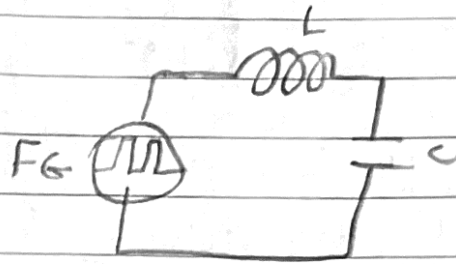(c) LC circuit (LC tank or LC-oscillator)

سلسلہ

$$\varepsilon = L \frac{d^2 Q}{dt^2} + \frac{Q}{C}$$



$$\Rightarrow Q(t) = Q_0 \cos(\omega t + \phi)$$

$$V_c = \frac{Q}{C} = \frac{Q_0}{C} \cos(\omega t + \phi)$$

$$\Rightarrow V_c = V_0 \cos(\omega t + \phi) \quad \text{simple harmonic oscillator}$$

$$\omega = \frac{1}{\sqrt{LC}} \quad \text{natural angular frequency}$$

$$X_L = \omega L = 2\pi f L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

→ at resonance

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$\Rightarrow f = \frac{1}{2\pi \sqrt{LC}}$$