


السؤال

Experiment 4 Network Analysis II

The Thevenin and Norton Techniques

- * kirchoff's laws and SPP are useful techniques for analyzing networks that contain a few circuit element
- * complicated networks requires methods such as the equivalent circuit techniques of Thevenin and Norton
- * Thevenin's theorem states that : any network of resistors and supplies having two out put terminals can be replaced by a series combination of a voltage source (ϵ_{eq}) and a resistor (R_{eq})

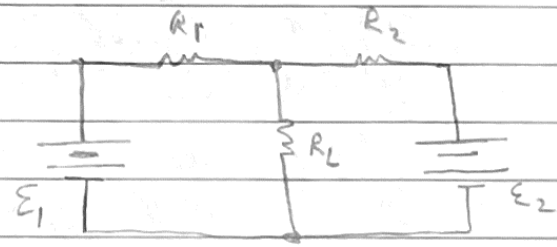- $R_1 = 1k\Omega$
- $R_2 = 3.3k\Omega$
- $R_3 = 6.2k\Omega$
- $\epsilon_1 = 12 \text{ volt}$
- $\epsilon_2 = 6 \text{ volt}$




* Thevenin :

(A) Finding $I_B \Rightarrow$ (So let $R_L = R_B$)

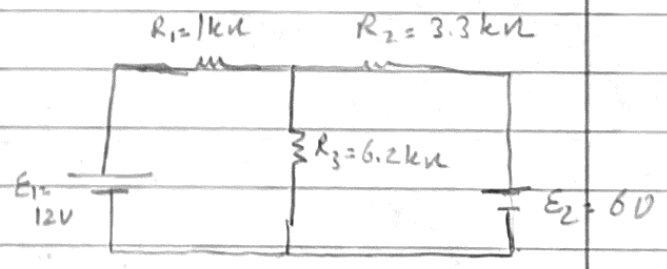(1) Remove R_L (Which is R_B in our case A), kill both sources

and Find R_{eq} (by connecting ohmmeter or multimeter on ohm's mode)




calculation

$$R_{eq} = R_1 \parallel R_2$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{1 \times 3.3}{1 + 3.3}$$

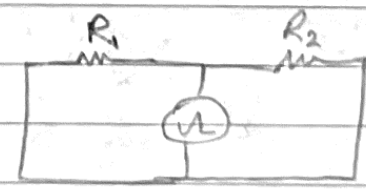كل المقاومات في
k\Omega \rightarrow 9681\Omega




②

$R_{eq} = 0.767 \text{ k}\Omega$

- ② Return both sources (ϵ_1, ϵ_2) and find ϵ_{eq}, I_{eq}
 - by connecting voltmeter or multimeter for ϵ_{eq}
 - by connecting Ammeter or multimeter for I_{eq}

From the large loop

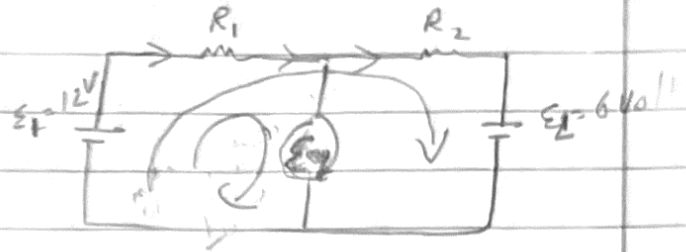

$$\epsilon_1 - IR_1 - IR_2 - \epsilon_2 = 0$$

$$\epsilon_1 - \epsilon_2 - I(R_1 + R_2) = 0$$

$$I = \frac{\epsilon_1 - \epsilon_2}{R_1 + R_2} = \frac{12 - 6}{(1 + 3.3) \text{ k}\Omega} = 1.395 \text{ mA}$$

From the small loop


$$\epsilon_1 - IR_1 - \epsilon_{eq} = 0 \Rightarrow \epsilon_{eq} = \epsilon_1 - IR_1 = 12 - 1.395 \text{ mA} \times 1 \text{ k}\Omega = 10.605 \text{ Volt}$$

لقد وجدنا $I_{eq} = \frac{\epsilon_{eq}}{R_{eq}} = \frac{10.605}{0.767 \times 10^3} = 13.83 \text{ mA}$

- ③ construct Thevenin's circuit

$$I_{L3} = \frac{\epsilon_{eq}}{R_{eq} + R_3}$$
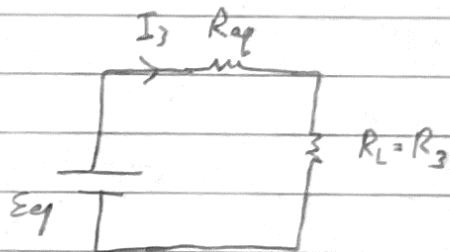
$$= \frac{10.605}{(0.767 + 6.2) \text{ k}\Omega}$$




$I_3 = 1.522 \text{ mA} \Rightarrow I_{L3} = 1.522 \text{ mA}$

(3)

(B) Finding $I_1 \Rightarrow$ (so let $R_L = R_1$)

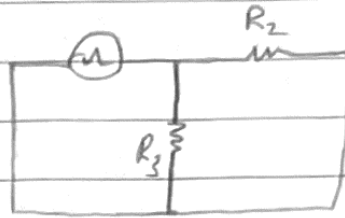(1) Remove R_L , kill both sources and find R_{eq}



$$R_{eq} = R_2 \parallel R_3$$

$$= \frac{R_2 R_3}{R_2 + R_3}$$

$$= \frac{3.3 \times 6.2}{3.3 + 6.2}$$


كلتا المقاومتين كلتا المقاومتين

$$R_{eq} = 2.15 \text{ k}\Omega$$

(2) Return both sources and find E_{eq}

(D)

$$I R_3 + I R_2 - E_2 = 0$$

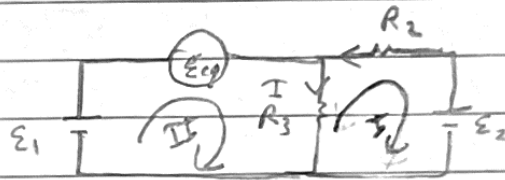

$$I(R_3 + R_2) - E_2 = 0$$

$$I_2 = \frac{E_2}{R_3 + R_2} = \frac{6}{(6.2 + 3.3) \text{ k}\Omega} = 0.63 \text{ mA}$$

$$E_1 - E_{eq} - I R_3 = 0$$

$$E_{eq} = E_1 - I R_3$$

$$= 12 - 0.63 \times 6.2$$


كلتا المقاومتين

$$E_{eq} = 8.094 \text{ Volt}$$

$$I_{eq} = \frac{E_{eq}}{R_{eq}} = 3.76 \text{ mA}$$

مثال
 (3) construct Thevenin's circuit, وجد المتاحه R_L و R_{eq} من التوال ϵ_{eq} الكبر ϵ_{eq}
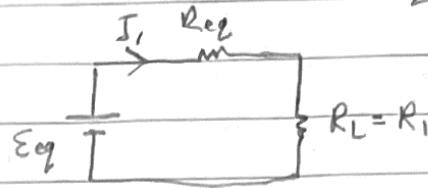
$$I_1 = \frac{\epsilon_{eq}}{R_{eq} + R_L}$$



$$I_1 = \frac{8.094}{(2.15 + 1) \text{ k}\Omega}$$

$$\boxed{I_1 = 2.569 \text{ mA}} \Rightarrow I_{L_1} = 2.569 \text{ mA}$$

5

$I_{s, p, L}$


Norton's

Finding I_{L3} let $R_L = R_3$

① Remove $R_L \rightarrow (R_3)$, killing sources and find R_{eq} by connecting to ohmmeter

$$R_{eq} = R_1 \parallel R_3$$

$$R_{eq} = \frac{R_1 R_3}{R_1 + R_3}$$

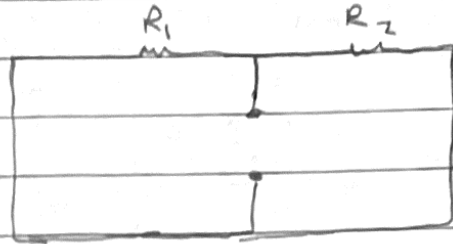

$$\Rightarrow R_{eq} = 0.767 \text{ k}\Omega$$

② Return both sources and calculate


I_{eq} (by connecting Ammeter or multimeter)

then find I_{eq} (I_{Norton})

$$I_{eq} + I_2 = I_1$$

$$I_{eq} = I_1 - I_2$$

small 100 pA

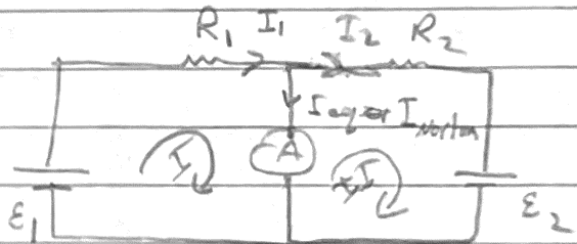

$$E_1 - I_1 R_1 = 0$$

$$I_1 = \frac{E_1}{R_1} = \frac{12}{1 \text{ k}\Omega} = 12 \text{ mA}$$

$$-I_2 R_2 - E_2 = 0$$

$$I_2 = \frac{-E_2}{R_2} = \frac{-6}{3.3 \text{ k}\Omega} = -1.82 \text{ mA}$$

$$I_{eq} = I_1 - I_2 = 12 \text{ mA} - (-1.82 \text{ mA}) = 13.82 \text{ mA}$$

6

3) construct Norton circuit

لحساب I_{eq} و R_{eq} و $R_L = R_3$

$$I_3 R_3 = I_{eq} (R_3 \parallel R_{eq})$$


$$I_3 R_3 = I_{eq} \frac{R_3 R_{eq}}{R_3 + R_{eq}}$$

$$I_3 = \frac{I_{eq}}{R_3} \frac{R_3 R_{eq}}{R_3 + R_{eq}}$$

$$I_3 = \frac{I_{eq} R_{eq}}{R_3 + R_{eq}}$$

$$= \frac{13.82 \times 0.767}{6.2 + 0.767}$$
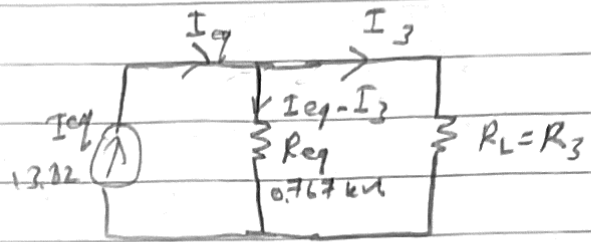
$$I_3 = 1.52 \text{ mA} \Rightarrow I_{L_3} = 1.52 \text{ mA}$$




(7)

Norton

For $R_1 = R_1$, Finding I_{N1}

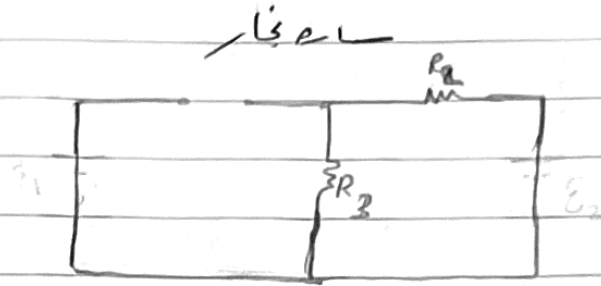
- ① Remove R_1 ($\times R_1$), killing sources and find R_{eq}



$$R_{eq} = R_2 \parallel R_3$$

$$= \frac{R_2 R_3}{R_2 + R_3} \Rightarrow R_{eq} = 2.15 \text{ k}\Omega$$

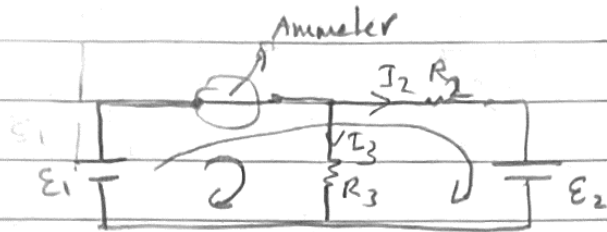- ② Return both sources and calculate I_{eq} (by connecting Ammeter or multimeter) then find I_{eq} (I_{Norton})



$$I_{eq} = I_2 + I_3$$

From small loop:

$$E_1 - I_3 R_3 = 0$$

$$I_3 = \frac{E_1}{R_3} = \frac{12}{6.2 \text{ k}\Omega} = 1.935 \text{ mA}$$

From the large loop:

$$E_1 - I_2 R_2 - E_2 = 0$$

$$I_2 R_2 = E_1 - E_2$$

$$I_2 = \frac{E_1 - E_2}{R_2} = \frac{12 - 6}{3.3 \text{ k}\Omega} = 1.82 \text{ mA}$$

$$\Rightarrow I_{eq} = I_3 + I_2 = 1.935 + 1.82 = 3.755 \text{ mA}$$

(8)


8

③ construct Norton circuit I_{eq} & R_{eq} & R_L does

$$V_{th\text{ across } R_1} = V_{th\text{ across } (R_1 \parallel R_{eq})}$$

$$I_1 R_1 = I_{eq} (R_1 \parallel R_{eq})$$
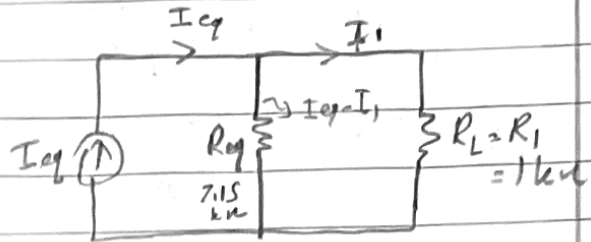
$$I_1 R_1 = I_{eq} \frac{R_1 R_{eq}}{R_1 + R_{eq}}$$



$$I_1 = I_{eq} \frac{R_1 R_{eq}}{R_1 + R_{eq}}$$

$$I_1 = \frac{I_{eq} R_{eq}}{R_1 + R_{eq}}$$

$$= \frac{3.753 \times 2.15}{(1 + 2.15) \text{ k}\Omega}$$

$\times 10^{-3} \times 10^{-3}$

$$I_1 = 2.56 \text{ mA}$$


or $I_L = 2.56 \text{ mA}$

①

Thevenin


Step ①

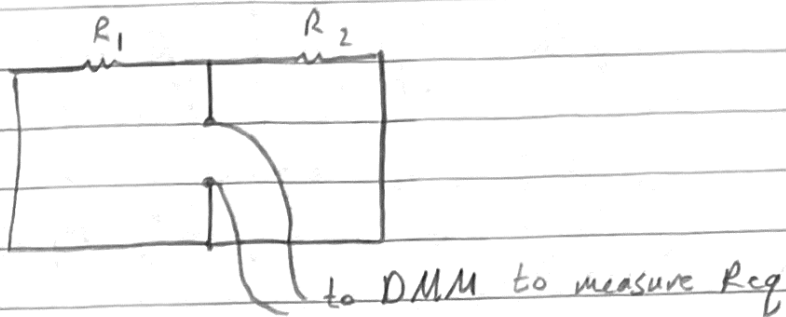قوس بازياب ϵ_1, ϵ_2
و R_3 و R_1, R_2 و DMM
و R_{eq} ليد




Step ②

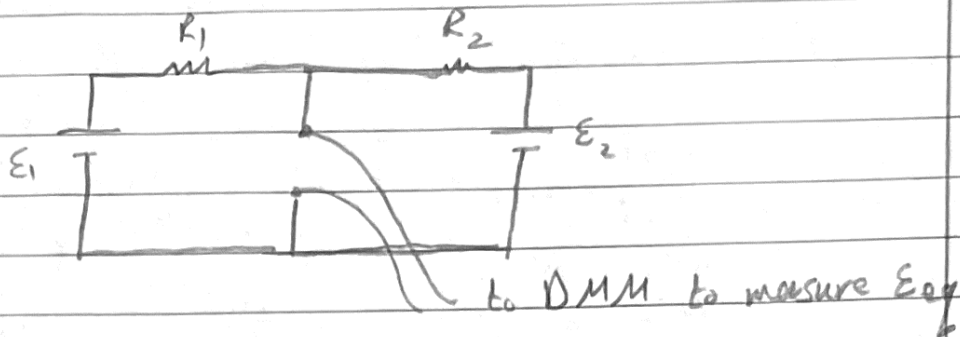قوس بازياب ϵ_1, ϵ_2
و R_3 و R_1, R_2 و DMM
و R_{eq} ليد



Step ③

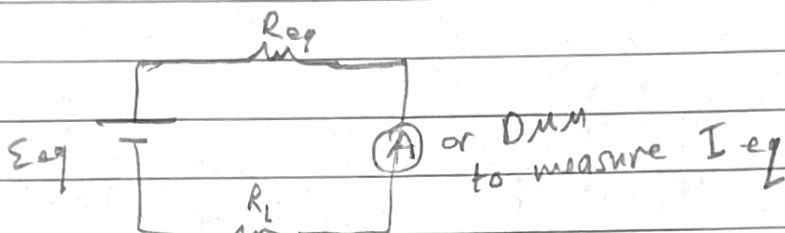


قياس I_{eq} و R_{eq} و E_{eq} و R_L و R_{eq} و R_3 و R_1, R_2 و ϵ_1, ϵ_2

①

Norton


Step ①

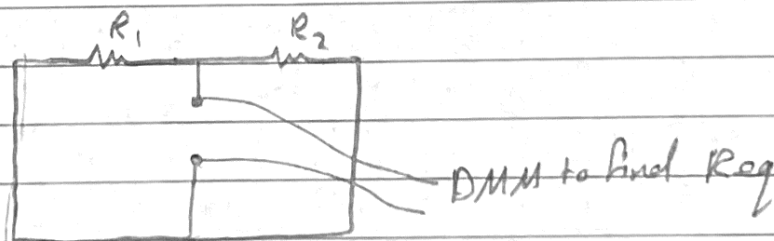قوس بازياب ϵ_1, ϵ_2
و R_3 و R_1, R_2 و DMM




Step ②

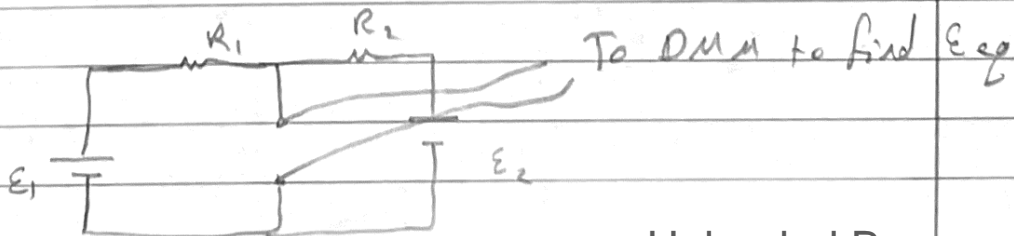قياس E_{eq} و R_{eq} و R_L و R_{eq} و R_3 و R_1, R_2 و ϵ_1, ϵ_2



step 3

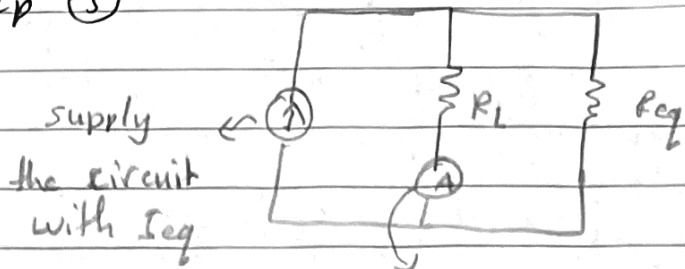

measure I_3 or I_L using DMM or A