
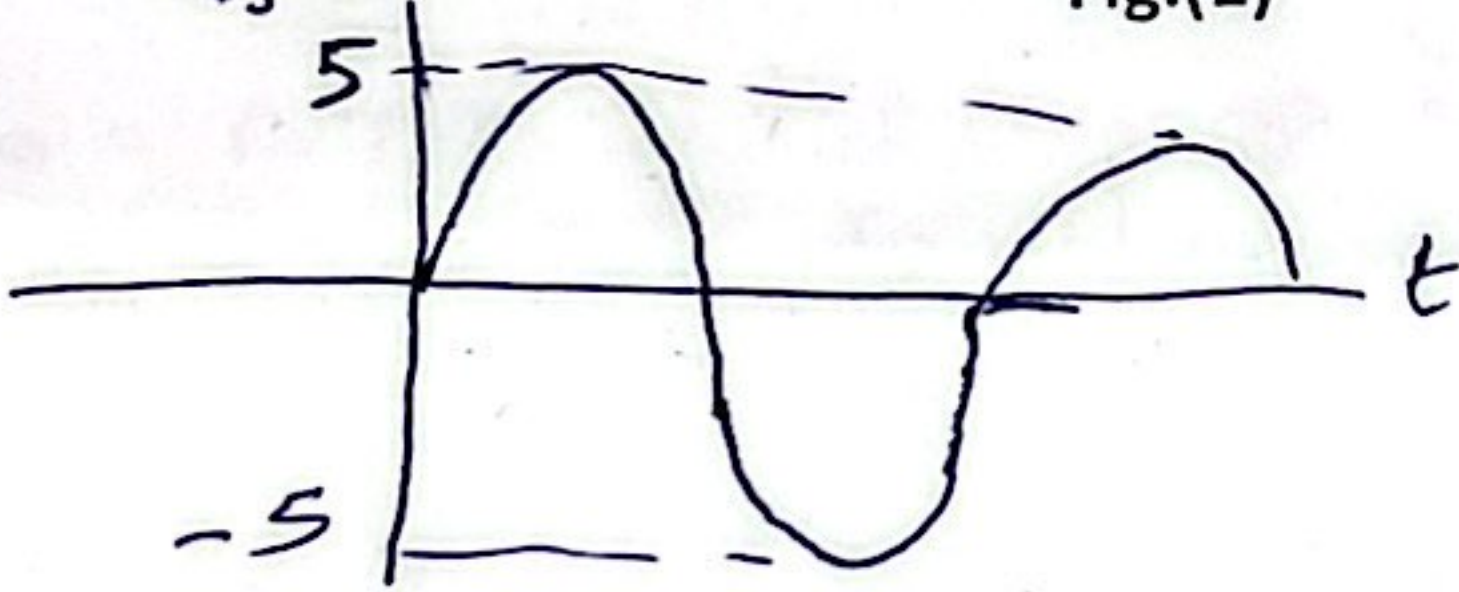


Instructor: Mr. Mohammad Al-Jubeh  
Student Name: Mahammed Jami Saada  
Student ID: 1221972


10/10

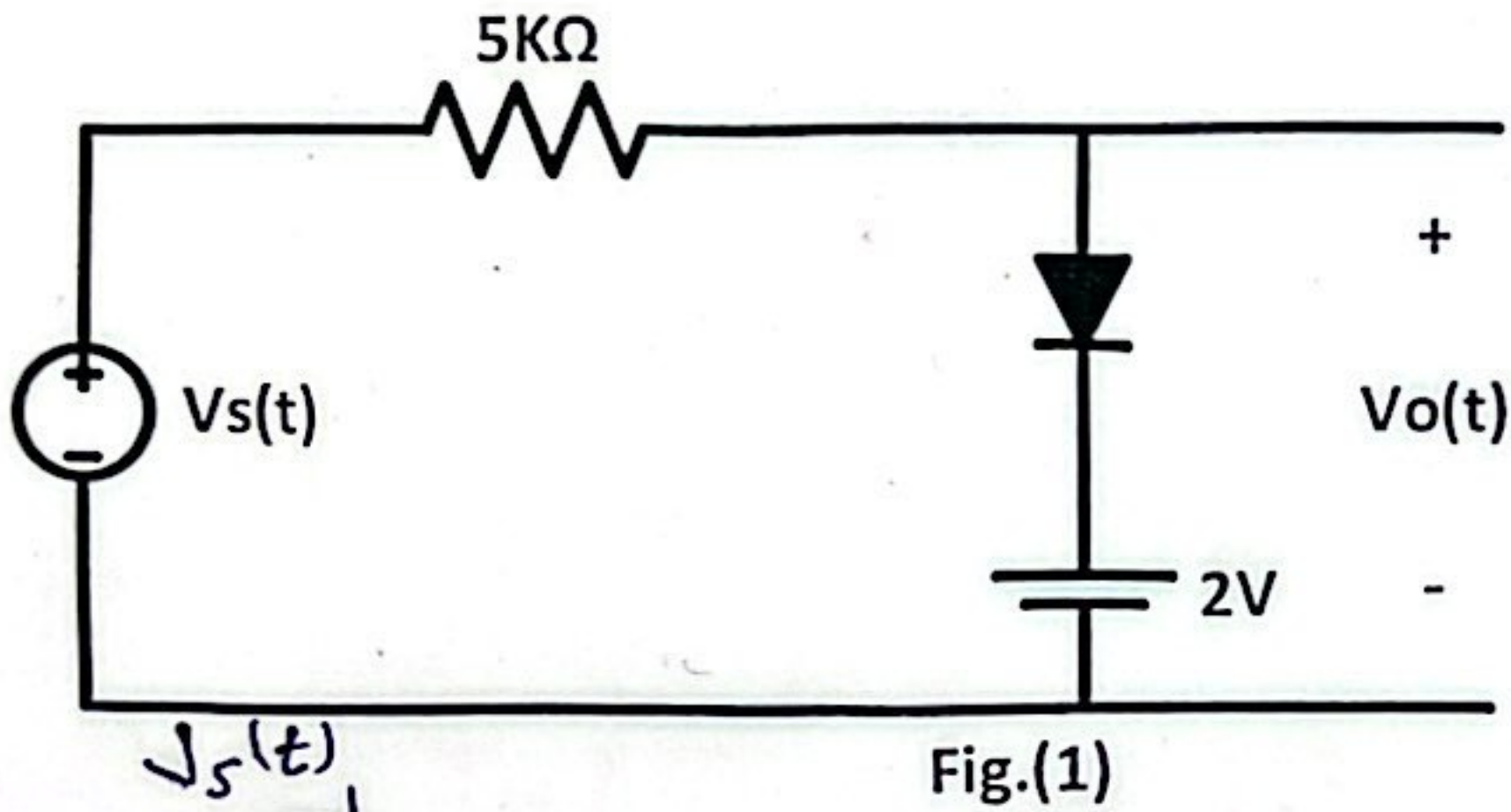The diode in the circuit shown in Fig.(1) has  $V_K = 0.7V$ .  
Calculate and Plot  $V_o(t)$  for  $V_s(t) = 5 \sin \omega t$  V.



~~Assume the diode is on~~

① Assume the Diode is on ( $V_K$ )

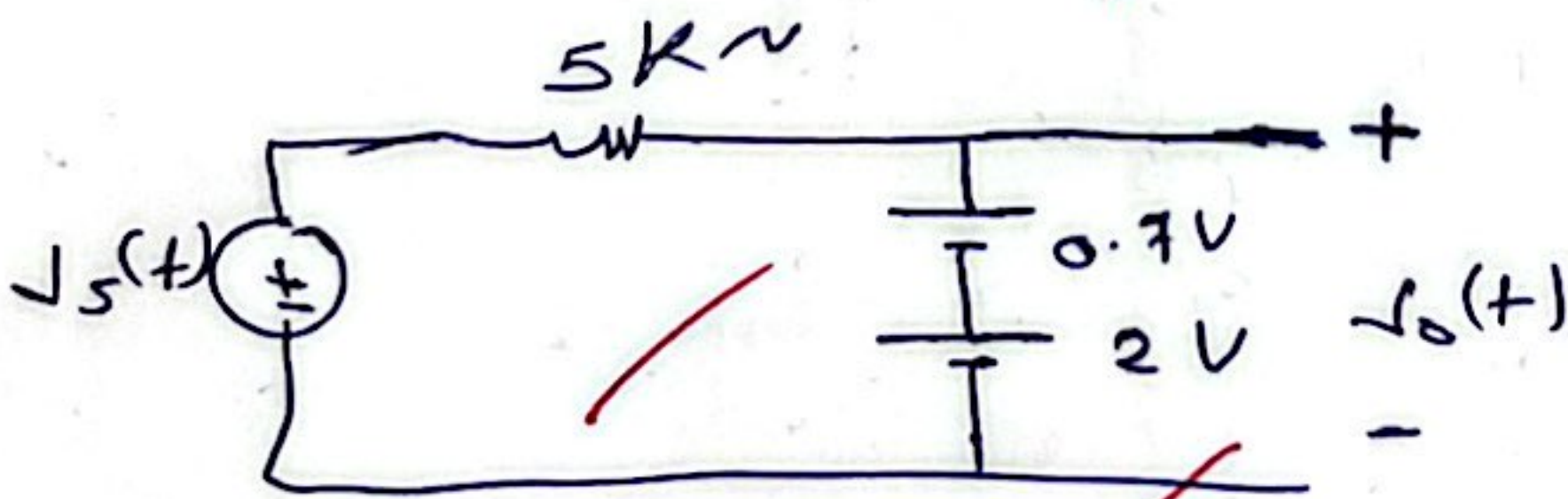

$V_D = 0.7$  Volt


$i_D = \frac{V_s(t) - 0.7 - 2}{5K} > 0$

$= \frac{V_s(t) - 2.7}{5K} > 0$

$V_s(t) > 2.7$  Volt


∴ When  $V_s(t) > 2.7$  Volt  
the Diode is on  
 $V_D = 0.7$  Volt  
 $V_o(t) = 0.7 + 2$   
 $= 2.7$  Volt

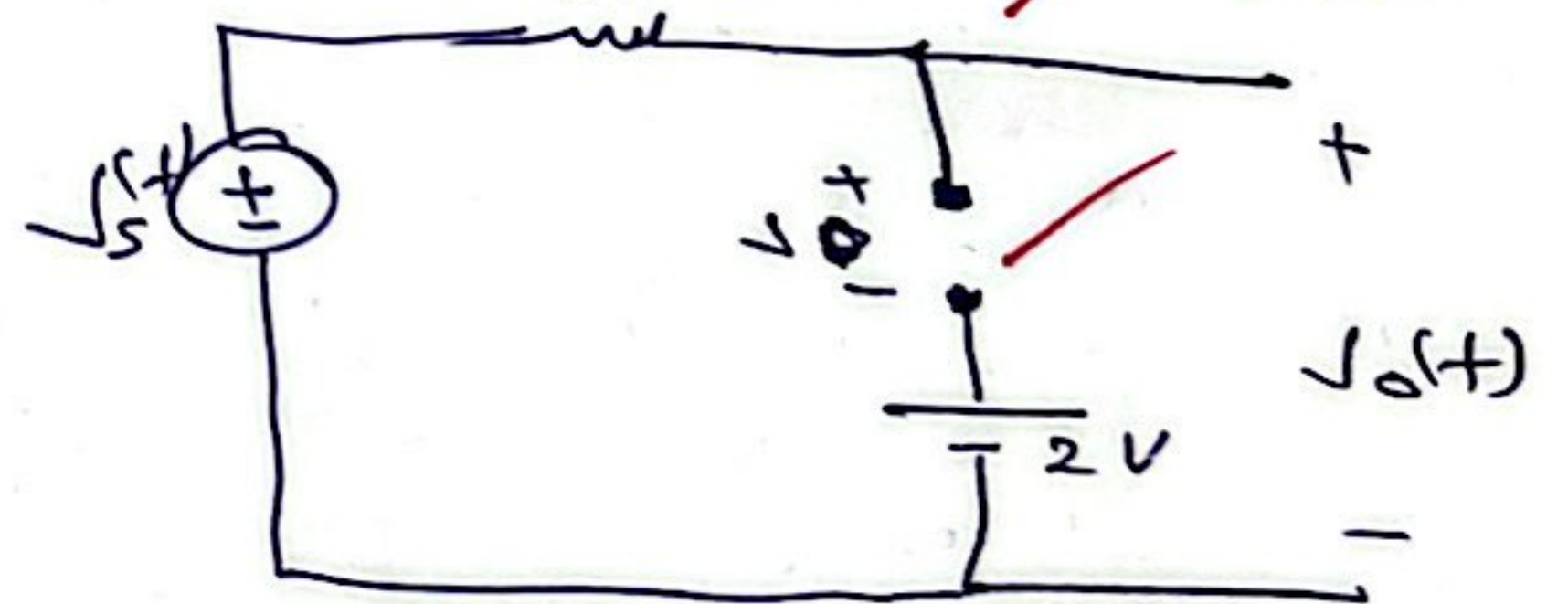② When  $V_s(t) < 2.7$  Volt  
the Diode is off (open circuit)



$-V_s(t) + V_D + 2 = 0$   
 $V_D = V_s(t) - 2$  Volt

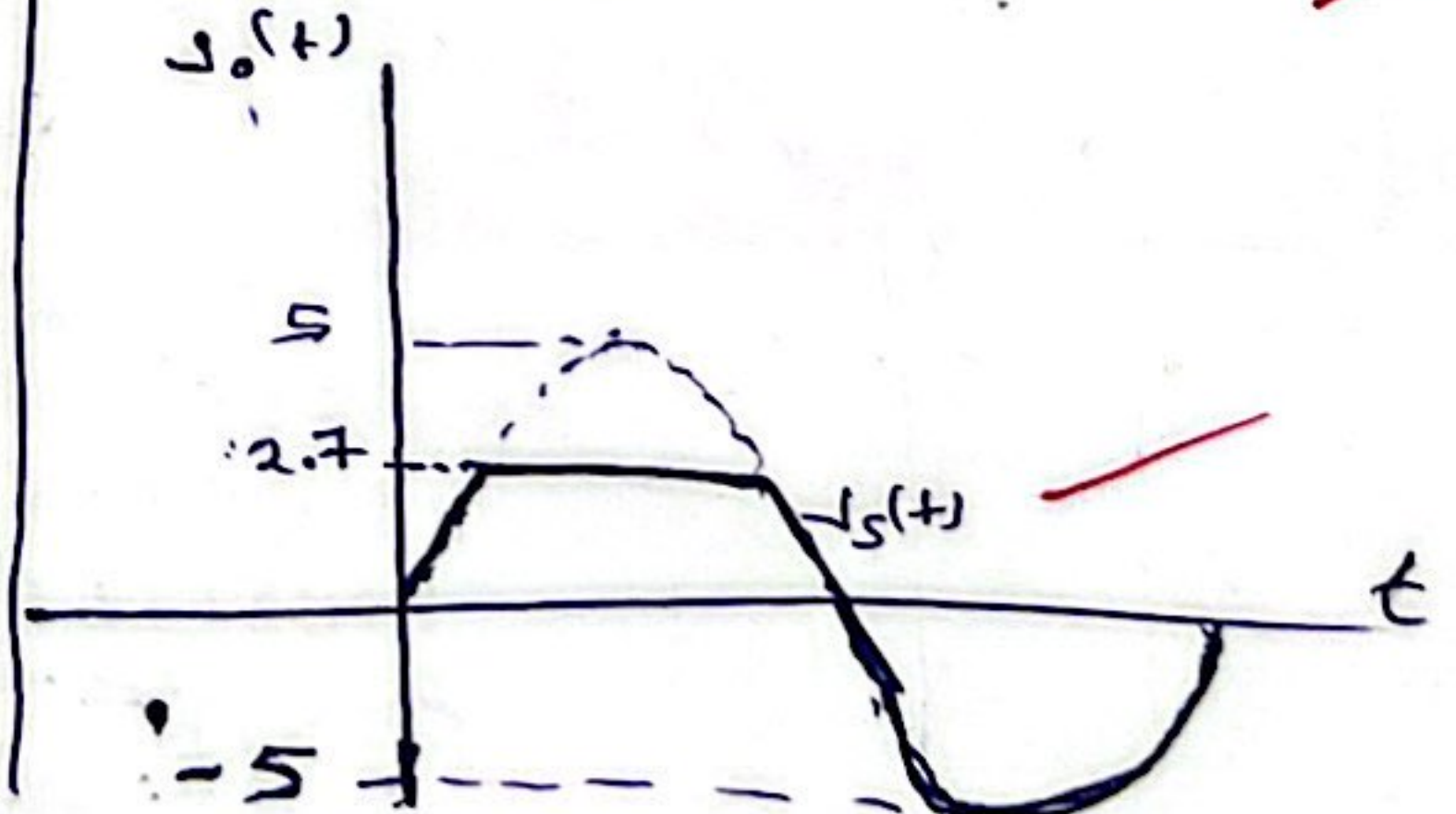$V_o(t) = V_D + 2$   
 $= V_s(t) - 2 + 2$   
 $= V_s(t)$  Volt







Instructor: Mr. Mohammad Al - Jubeh

Student Name: Mohammed Jamil Saada

Student ID: 1221972

10/10

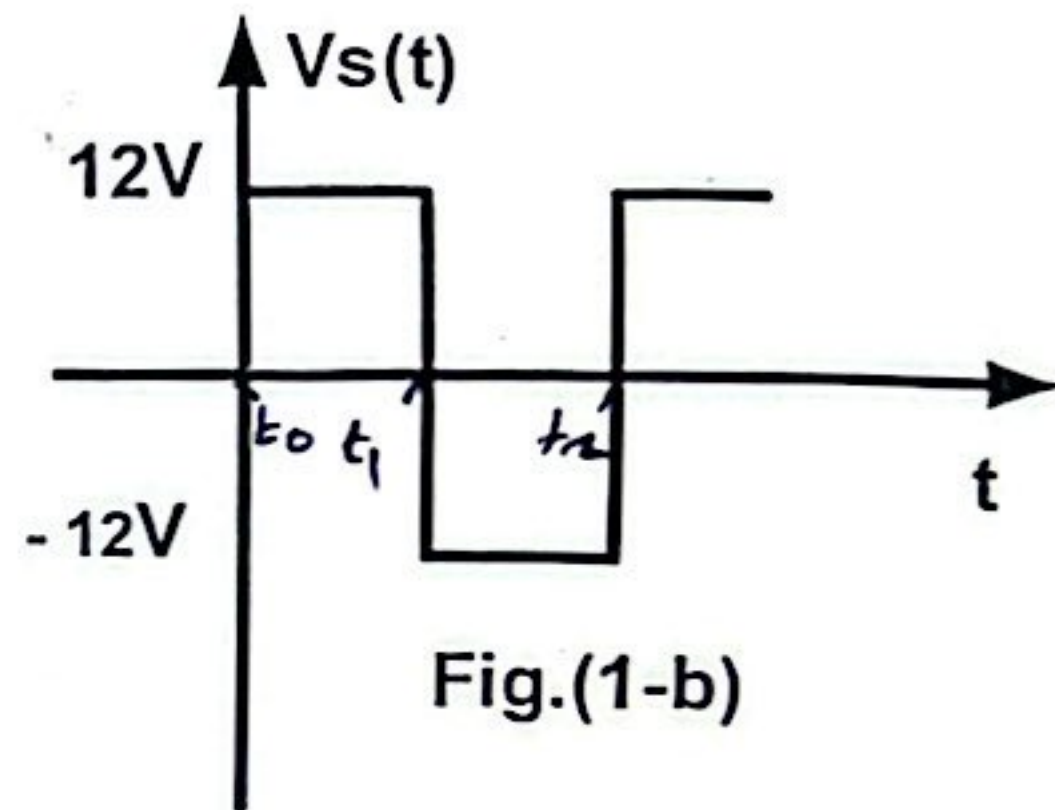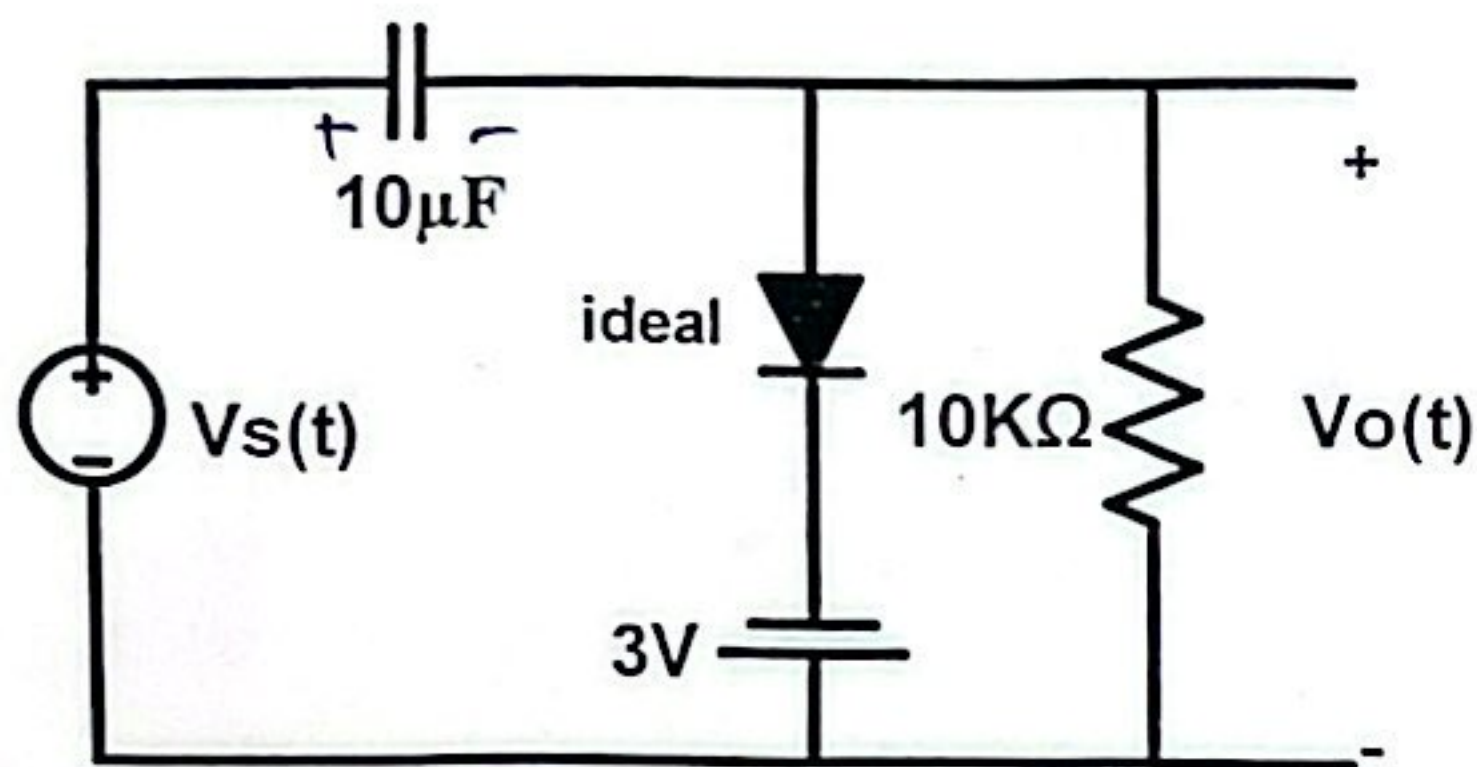Calculate and plot  $V_o(t)$  for the circuit shown in Fig.(1-a) for the input voltage shown in Fig. (1-b). Assume the diode is ideal.




clamping circuit

$V_c(0^-) = V_c(0^+) = 0$  volt.

$V_s(0^+) = 12$  Volt.

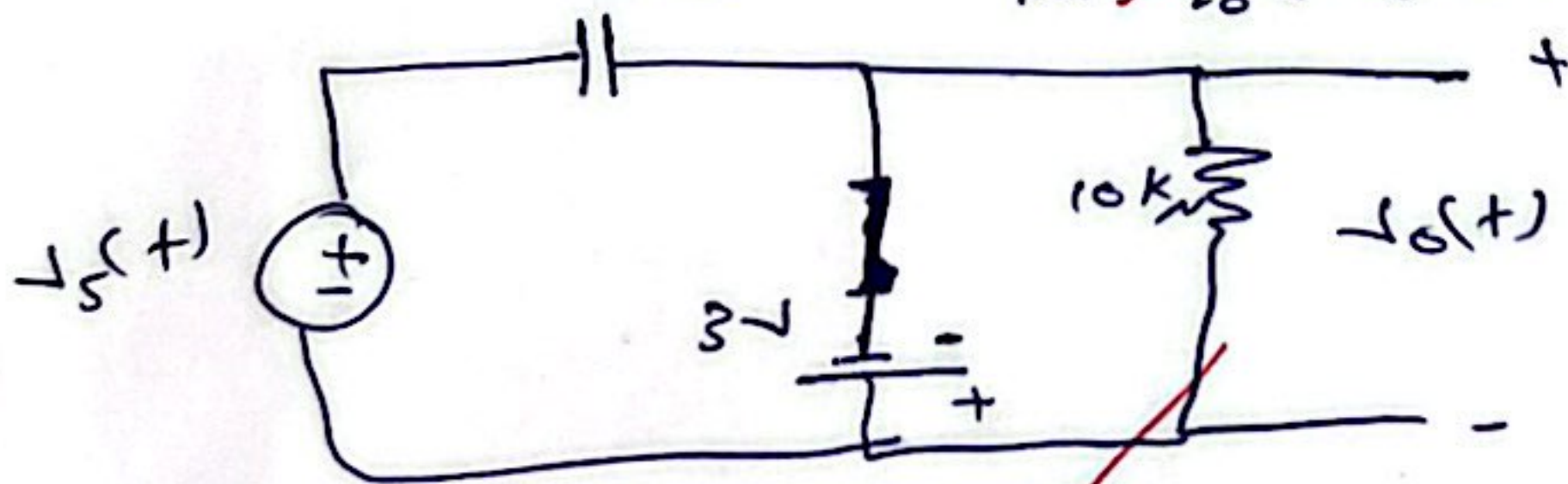When  $V_s(0^+) > 0$  the Diode is ON  
 For  $t_0 < t < t_1$  (short circuit)




$V_o(t) = -3$  Volt.

$-V_s(t) + V_c - 3 = 0$

$V_c = 15$  Volt.

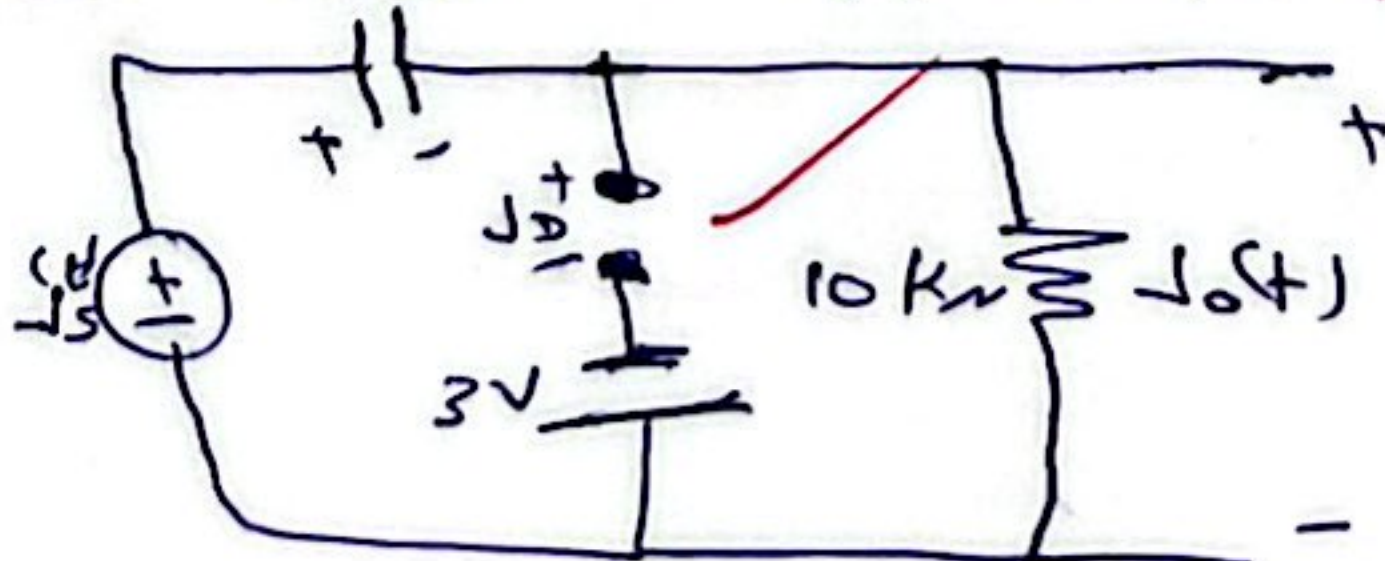When  $t_1 < t < t_2$  the  $V_s(t) < 0 = -12$  volt  
 the Diode is OFF  $\rightarrow$  open circuit




~~$-V_s(t) + V_c + V_o(t) = 0$~~   
 ~~$12 + 15 + V_o(t) = 0$~~

$-V_s(t) + V_c + V_o(t) = 0$

$12 + 15 + V_o(t) = 0$

$V_o(t) = -27$  Volt.

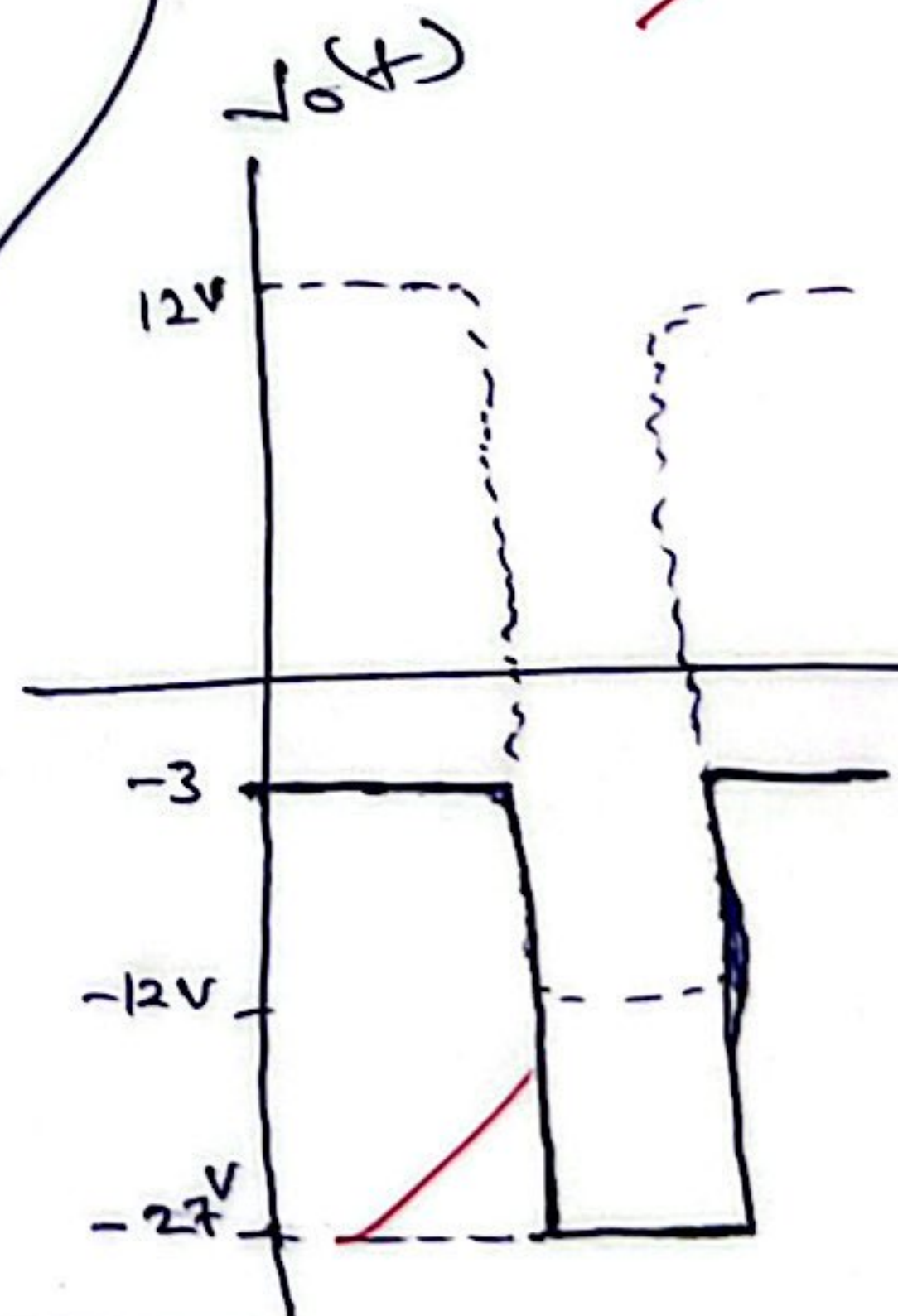

Name:

ID:



Instructor: Mr. Mohammad Al-Jubeh

Student Name: Mohammed Jamil Saada


Student ID: 1221972

محمد جميل سعد

10/10

The BJT in the circuit shown has  $\beta = 120$

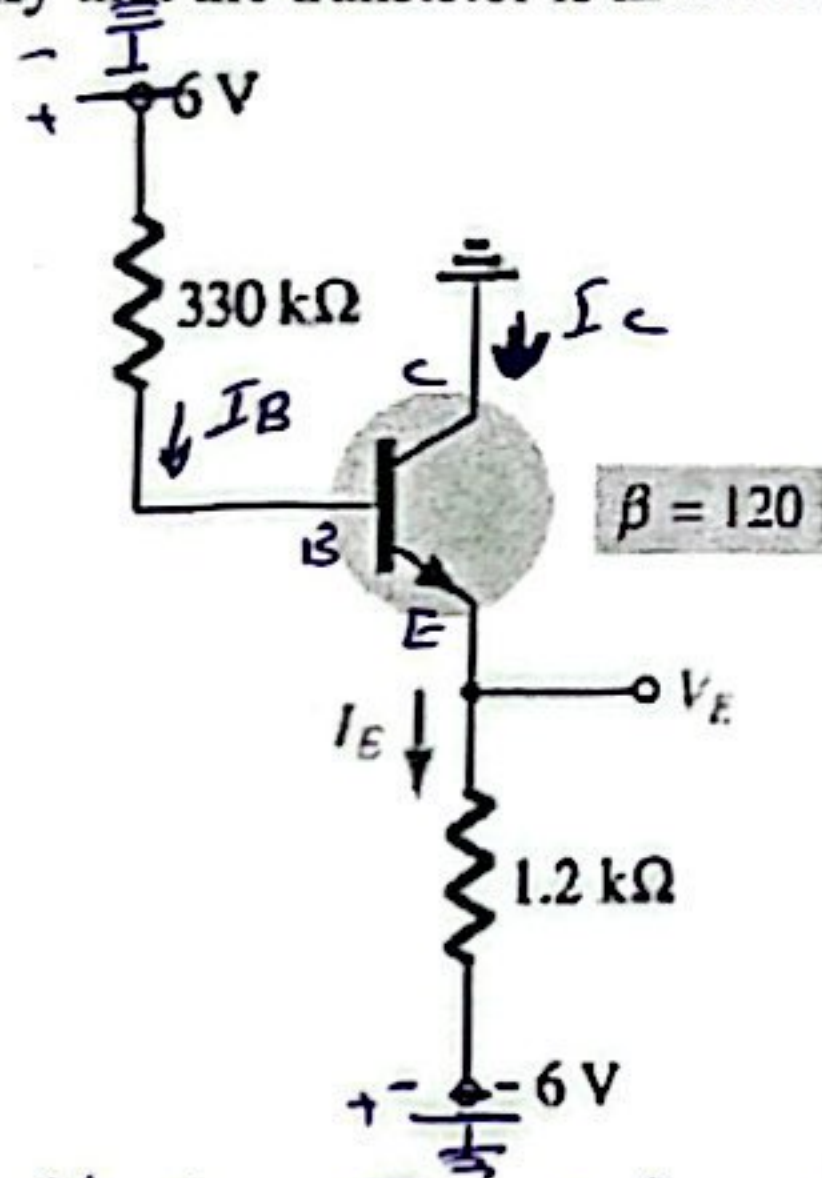- Calculate  $I_{CQ}$
- Calculate  $V_E$
- Calculate  $V_B$
- Verify that the transistor is in the active region



assume that Transistor is in active region.

④ Verify that Transistor is in active region.

KVL:

$$V_{CE} + (1.2k)\bar{I}_E - 6 = 0$$

$$V_{CE} = 6 - (1.2k)\bar{I}_E$$

$$V_{CE} = 6 - (1.2)(2.877)$$

$$= 6 - 3.4524$$

$$= 2.5476 \text{ Volt}$$

Since  $V_{CE} = 2.54 > V_{CE,sat} = 0.2$

then, the assumption is correct and the transistor is in active region

$$6 = I_B(330k) + V_{BE} + I_E(1.2k) - 6$$

$$12 = (330k)I_B + 0.7 + (1.2k)(121I_B)$$

$$11.3 = (330k)I_B + (145.2k)I_B$$

$$11.3 = 475.2k I_B \rightarrow I_B = 0.0238 \text{ mA}$$

$$\textcircled{a} I_{CQ} = \beta I_B = (120)(0.0238) \Rightarrow I_{CQ} = 2.85 \text{ mA}$$

$$\textcircled{b} I_E = (\beta + 1) I_B = 121 I_B = 2.877 \text{ mA}$$

$$V_E = I_E(1.2k) - 6 = (2.877)(1.2) - 6 = -2.547 \text{ Volt}$$

$$\textcircled{c} V_{BE} = 0.7 = V_B - V_E \Rightarrow V_B = 0.7 + V_E$$

$$V_B = -1.847 \text{ Volt}$$

Name:

ID:




Instructor: Mr. Mohammad Al - Jubeh

Student Name: .....

Student ID: .....

For the circuit shown

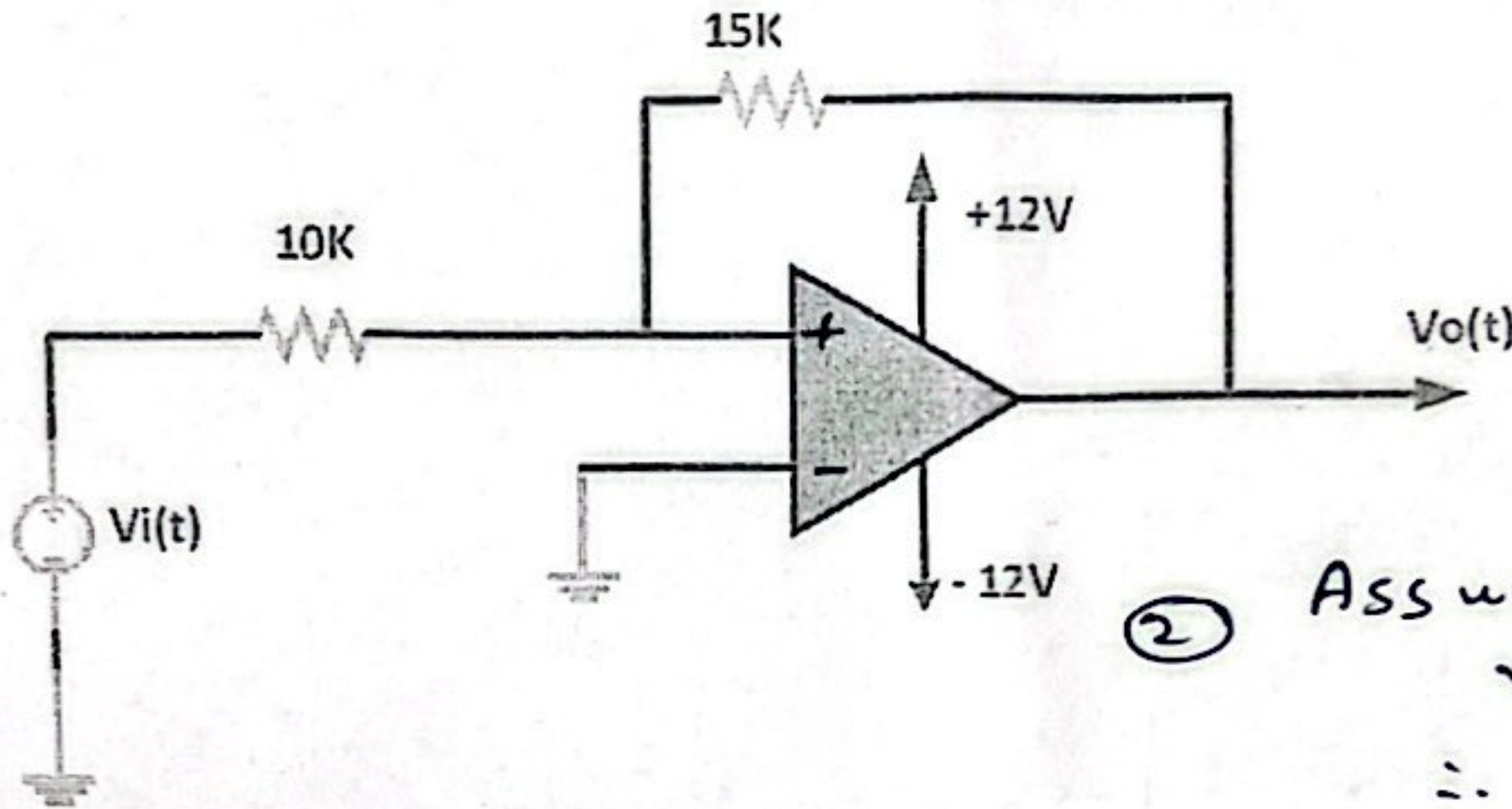- a) Calculate the lower and upper threshold voltages
- b) Based on results in (a) sketch  $V_o(t)$  as a function of  $V_s(t)$  (Hysteresis)



① Assume  $V_o = +V_{sat}$

$$V_d > 0$$

$$V(+)-V(-) > 0$$

$$V(+)>V(-)$$

$$V(-) = 0$$

$$\therefore V(+)>0$$

By superposition.

$$V(+)=\frac{10K}{10K+15K}(+V_{sat})+\frac{15K}{10K+15K}V_i$$

$$V(+)=4+0.6V_i > 0$$

$$0.6V_i > -4$$


$$V_i > -6.67$$

when  $V_i > -6.67$  Volt

$$V_o = +V_{sat}$$

when  $V_i < -6.67$  Volt.

$V_o$  switch to  $-V_{sat}$

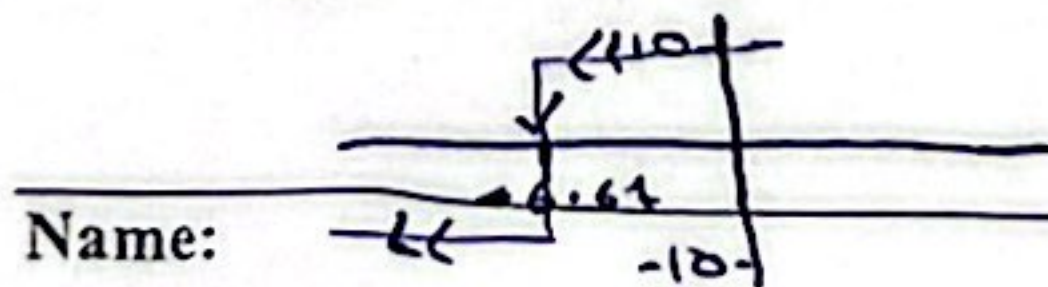

Name: \_\_\_\_\_

ID: \_\_\_\_\_

② Assume  $V_o = -V_{sat}$   
 $V_d < 0$   
 $\therefore V(+)<0$

$$V(+)=\frac{10K}{10K+15K}(-V_{sat})+\frac{15K}{10K+15K}V_i$$


$$V(+)= -4+0.6V_i < 0$$

$$0.6V_i < 4$$

$$V_i < 6.67 \text{ Volt.}$$


when  $V_i < 6.67$  Volt  $\rightarrow V_o = -V_{sat}$

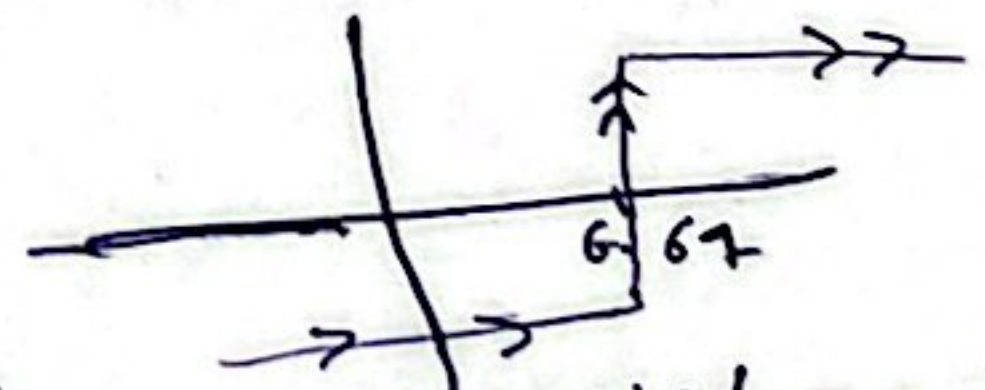when  $V_i > 6.67 \rightarrow V_o$  switch to  $+V_{sat}$



$$V_{LT} = -6.67V, V_{UT} = 6.67V$$

③

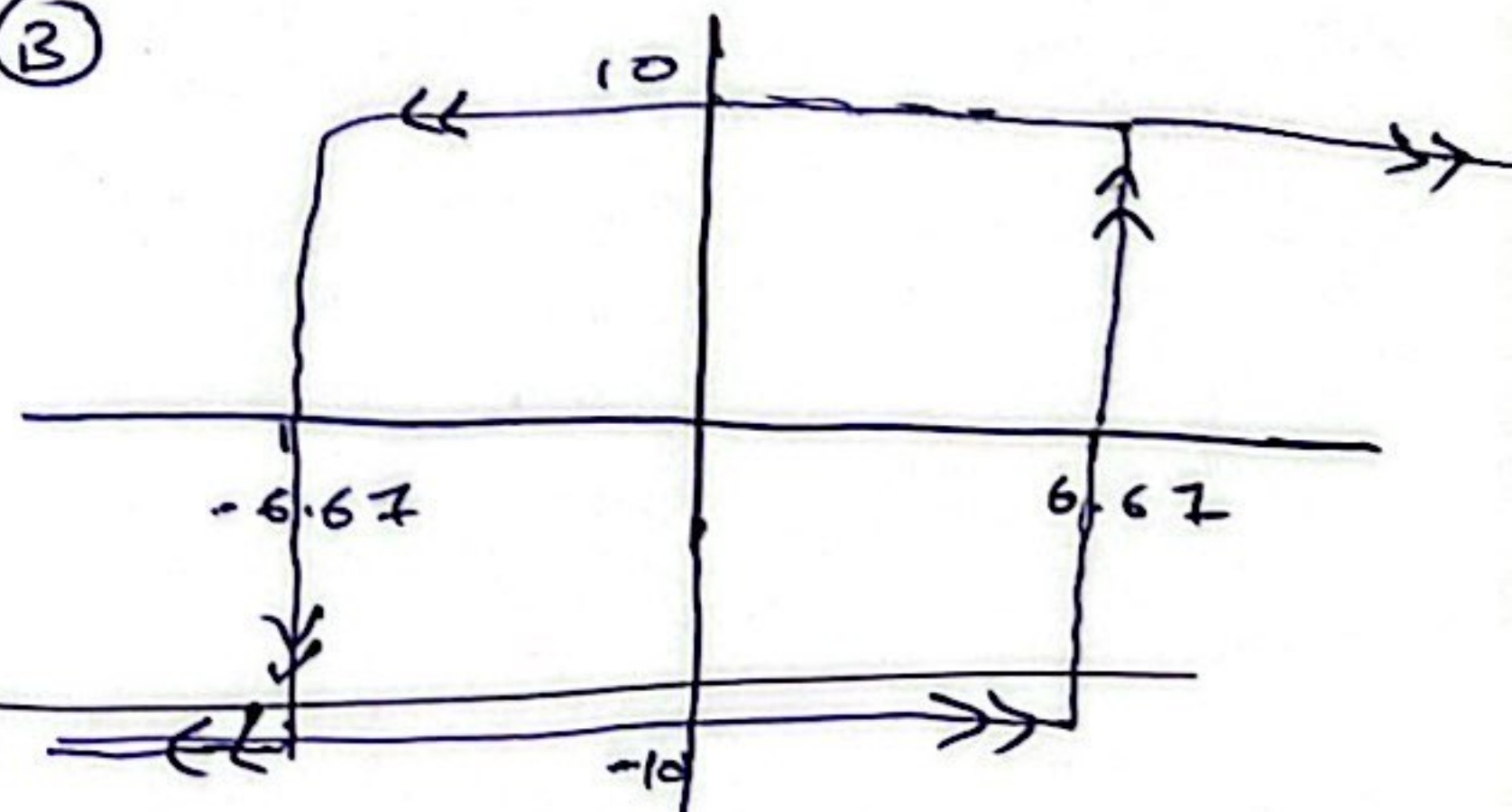




Instructor: Mr.Mohammad Al - Jubeh

Student Name: .....

Student ID: .....

The op.amps in the circuit shown are ideal

- a) Calculate Vo1
- b) Calculate Vo2

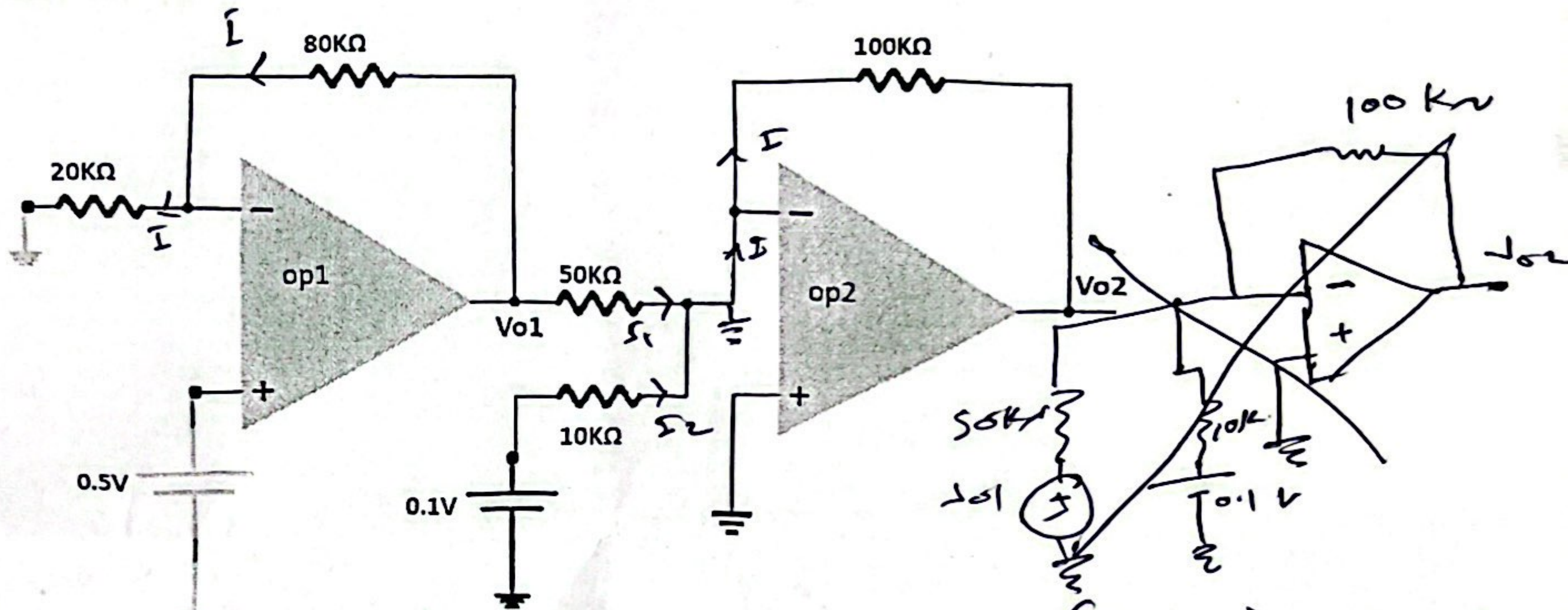

op1 and op2 in the linear region (there is negative feedback)

For op1

$$V_d = 0 \text{ (Linear region)}$$

$$V(+) = V(-)$$

$$V(+) = 0.5 \text{ Volt.}$$

$$\therefore V(-) = 0.5 \text{ Volt.}$$

$$I = \frac{0.5}{20k} = 0.025 \text{ mA}$$

$$V_{o1} = I(80k + 20k)$$

$$= (0.025 \text{ m})(100k)$$

$$= 2.5 \text{ Volt}$$

For op2

$$V_d = 0 \text{ (Linear region)}$$

$$V(+) = V(-)$$

$$V(+) = 0$$

$$\therefore V(-) = 0$$

$$I_1 = \frac{V_{o1}}{50k} = \frac{2.5}{50k} = 0.05 \text{ mA}$$

$$I_2 = \frac{0.1}{10k} = 0.01 \text{ mA}$$

$$I = I_1 + I_2 = 0.06 \text{ mA}$$

$$V_{o2} = (-I)(100k)$$

$$= (-0.06)(100)$$

$$= -6 \text{ Volt.}$$

Name:

ID: