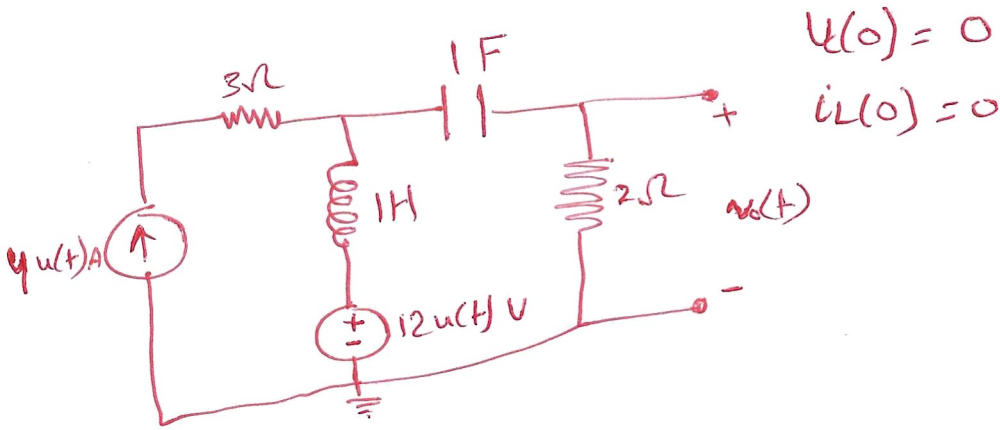


Analysis techniques

All the analysis techniques are applicable in the s-domain

For the circuit shown, find $V_o(t)$ using node analysis, mesh analysis, superposition, source transformation, Thevenin's theorem and Norton theorem



1) Node analysis :-

1 node :-

at node ①

$$-\frac{4}{s} + \frac{V_1 - \frac{12}{s}}{s} + \frac{V_1 - 0}{2 + \frac{1}{s}} = 0$$


$$-\frac{4}{s} + \frac{V_1}{s} - \frac{12}{s^2} + \frac{V_1}{\frac{2s+1}{s}} = 0$$

$$V_1 \left(\frac{1}{s} + \frac{s}{2s+1} \right) = \frac{12+4s}{s^2}$$

$$V_1 \left(\frac{s^2 + 2s + 1}{2s^2 + s} \right) = \frac{12+4s}{s^2}$$

$$V_1 = \frac{\frac{12+4s}{s^2}}{\frac{s^2 + 2s + 1}{2s^2 + s}} = \frac{12+4s}{s^2} \cdot \frac{2s^2 + s}{s^2 + 2s + 1} = \frac{(12+4s)(2s+1)}{s(s^2 + 2s + 1)}$$

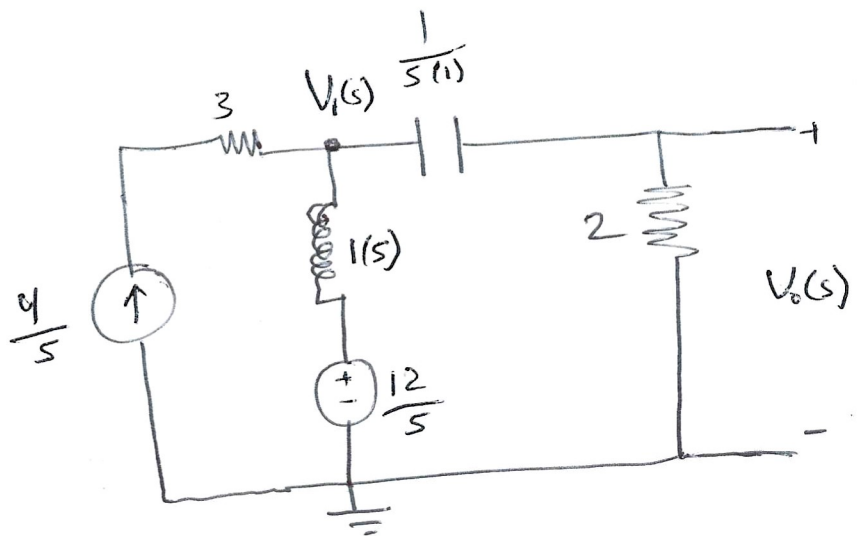but $V_o = \frac{V_1 (2)}{2 + \frac{1}{s}} = \frac{2 V_1}{\frac{2s+1}{s}} = \frac{2s V_1}{2s+1}$



$$\therefore V_o = \frac{2s}{2s+1} \cdot \frac{(12+4s)(2s+1)}{s(s^2+2s+1)}$$

$$= \frac{2(12+4s)}{s^2+2s+1} = \frac{8(s+3)}{(s+1)^2}$$

2) Mesh Analysis of

Mesh (1)

$$I_1 = \frac{4}{s}$$

Mesh (2)

$$-\frac{12}{s} + I_2(s + \frac{1}{s} + 2) - I_1(s) = 0$$


$$I_2 \left(\frac{s^2+2s+1}{s} \right) = \frac{12}{s} + 4$$

$$I_2 \left(\frac{s^2+2s+1}{s} \right) = \frac{12+4s}{s}$$

$$I_2 = \frac{12+4s}{s^2+2s+1}$$

but $V_o = I_2(2)$
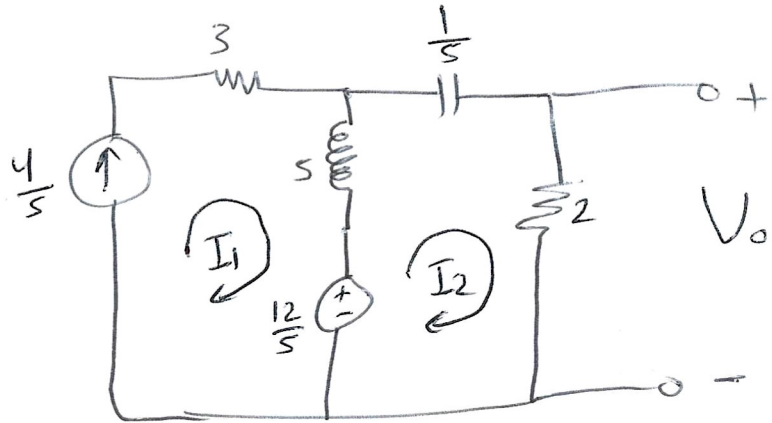
$$V_o = \frac{2(12+4s)}{s^2+2s+1} = \frac{8(s+3)}{(s+1)^2}$$



3) Superposition

applying Current source

$$V_{o1} = I_2(2) = \frac{I(s)}{s + \frac{1}{s} + 2} \quad \text{current divider}$$



$$= \frac{4}{s} \times 2 \times \frac{s}{s + \frac{1}{s} + 2}$$

$$= \frac{8s}{s^2+2s+1}$$

applying voltage source

$$V_{o2} = \frac{\frac{12}{s} \times 2}{s + \frac{1}{s} + 2} = \frac{24}{s^2+2s+1}$$

STUDENTS-HUB.com

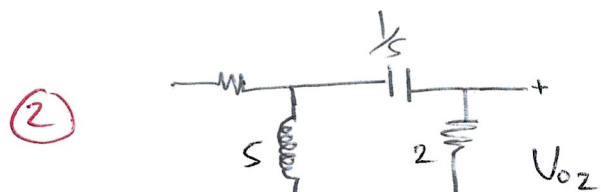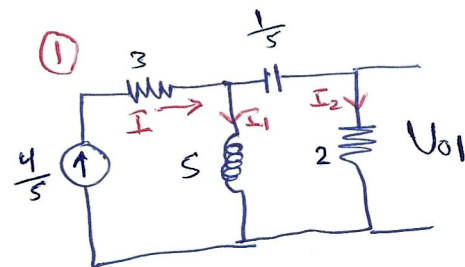


$$\therefore V_0 = V_{01} + V_{02}$$

$$= \frac{8s}{s^2 + 2s + 1} + \frac{24}{s^2 + 2s + 1}$$

$$= \frac{8(s+3)}{(s+1)^2}$$

Source transformation

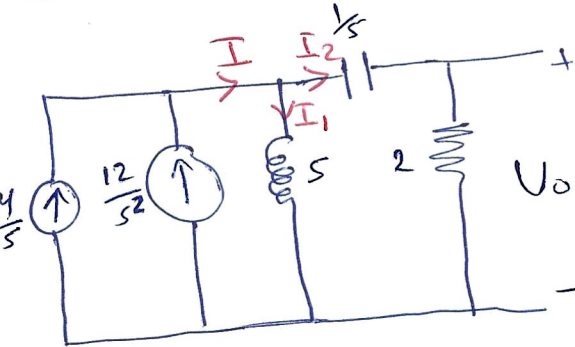

$$V_0 = I_2(2)$$

$$I_2 = \frac{I(s)}{s + \frac{1}{s} + 2}$$


$$I = \frac{4}{s} + \frac{12}{s^2} = \frac{4s^2 + 12s}{s^3}$$

$$V_0 = \frac{4s^2 + 12s}{s^3} \left(\frac{s}{s + \frac{1}{s} + 2} \right) (2)$$

$$= \frac{4s^2 + 12s}{s^2} \cdot \frac{s^2}{s^2 + 2s + 1} (2)$$



$$= \frac{8(s+3)}{(s+1)^2}$$

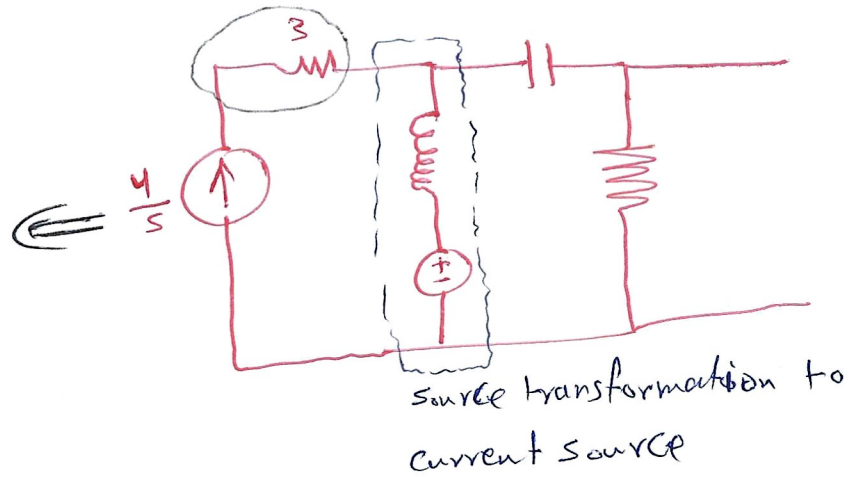resistor in series with current source so the resistance is redundant




source transformation to current source

5) Thevenin's theorem

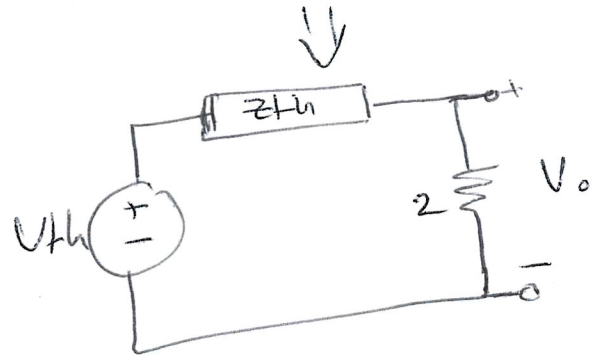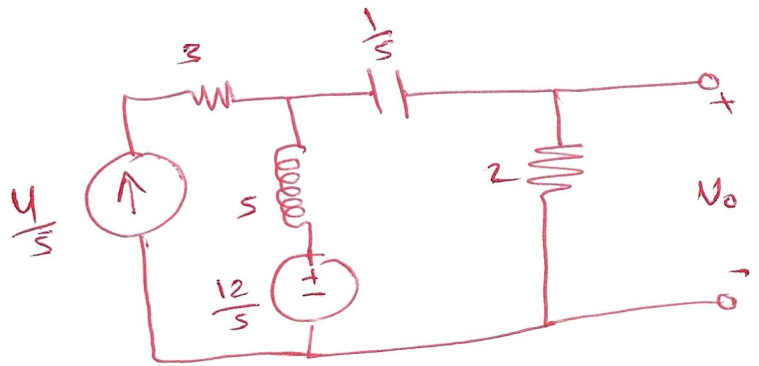

$$I = \frac{4}{s}$$
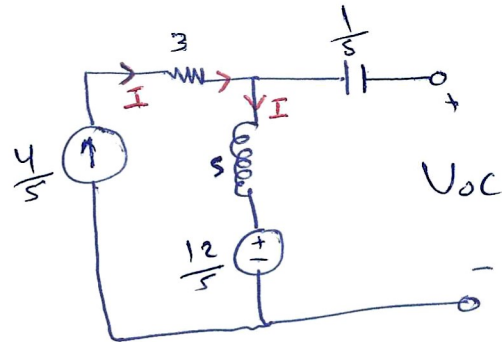
$$\therefore V_{oc} = \frac{12}{s} + \frac{4}{s}(s) = \frac{12 + 4s}{s}$$




$$Z_{th} = \frac{1}{s} + s = \frac{s^2 + 1}{s}$$


$$\therefore V_o = \frac{V_{th} (2)}{Z_{th} + 2}$$

$$= \frac{\frac{12 + 4s}{s} (2)}{\frac{s^2 + 1}{s} + 2}$$

$$= \frac{8(s + 3)}{(s + 1)^2}$$

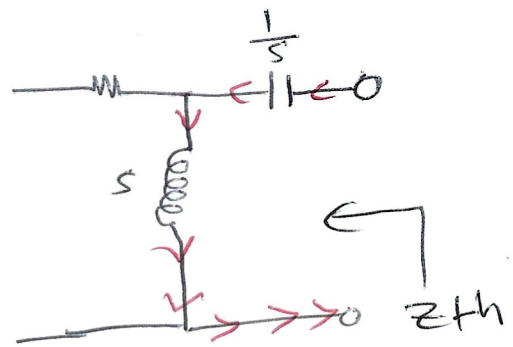

Example 8- Find $i_1(t)$ and $i_2(t)$

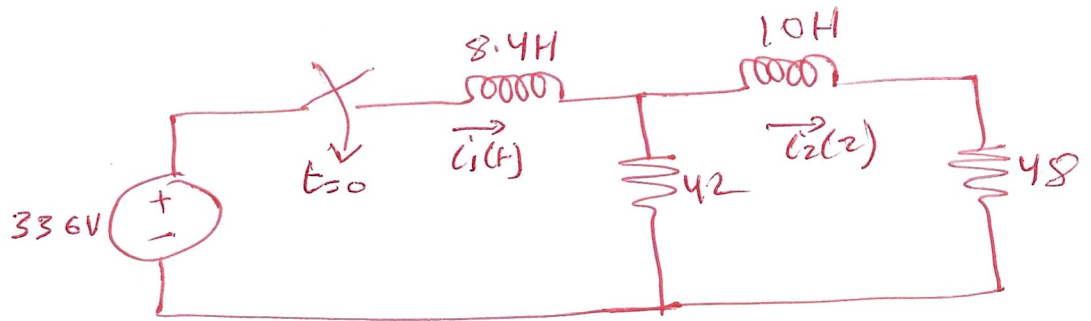


Mesh (1)

$$-\frac{336}{s} + \bar{I}_1(8.4s + 42) - \bar{I}_2(42) = 0$$

Mesh (2)
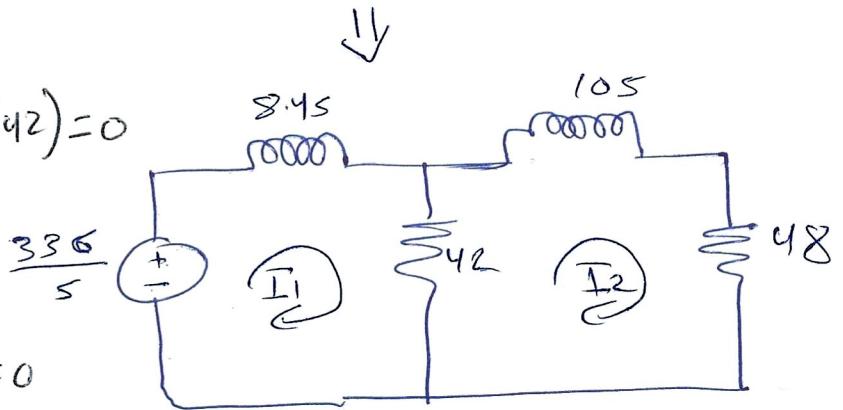
$$\bar{I}_2(42 + 48 + 10s) - \bar{I}_1(42) = 0$$



$$\begin{bmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} \frac{336}{s} \\ 0 \end{bmatrix}$$

$$D = (42 + 8.4s)(90 + 10s) - (42)(42)$$

$$= 3780 + 756s + 420s + 84s^2 - 1764$$

$$= 84s^2 + 1176s + 2016$$

$$\bar{I}_1 = \begin{bmatrix} \frac{336}{s} & -42 \\ 0 & 90 + 10s \end{bmatrix}$$

$$D_{I_1} = \frac{30240 + 3360s}{s}$$

$$D_{I_2} = \begin{bmatrix} 42 + 8.4s & \frac{336}{s} \\ -42 & 0 \end{bmatrix}$$

$$D_{I_2} = \frac{14112}{s}$$

$$I_1 = \frac{3360s + 30240}{s(84s^2 + 1176s + 2016)}$$

$$I_1 = \frac{40s + 360}{s(s^2 + 14s + 24)} = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+12}$$

$$I_1 = \frac{15}{s} - \frac{14}{s+2} - \frac{1}{s+12}$$

$$i_1(t) = (15 - 14e^{-2t} - e^{-12t})u(t)$$


$$I_2 = \frac{14112}{s(84s^2 + 1176s + 2016)}$$

$$I_2 = \frac{168}{s(s^2 + 14s + 24)} = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+12}$$

$$I_2 = \frac{7}{s} - \frac{8.4}{s+2} + \frac{1.4}{s+12}$$

$$i_2(t) = (7 - 8.4e^{-2t} + 1.4e^{-12t})u(t)$$

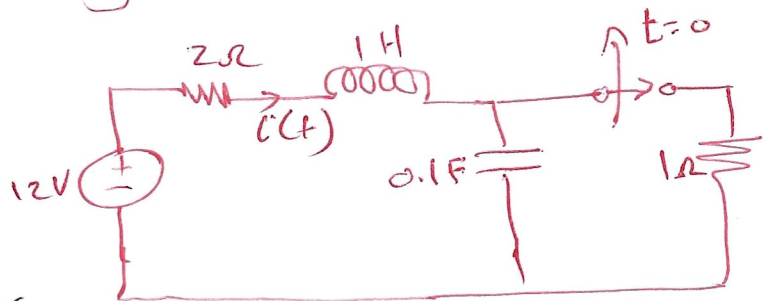Example - Given the following circuit, find $i(t)$ for $t > 0$




to calculate the initial conditions for the capacitor and the inductor for $t = 0^-$

for $t < 0$,

$$V_C(0) = \frac{1}{1+2} (12) = 4V$$

$$i_L(0) = \frac{12}{1+2} = 4A$$

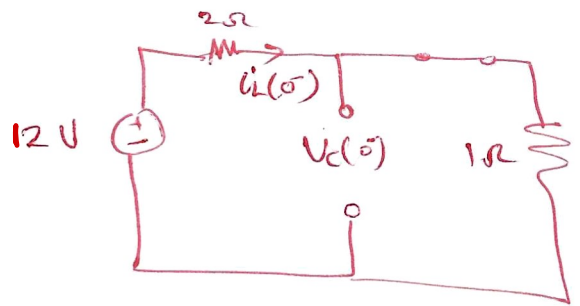


for $t > 0$

$$-\frac{12}{s} - 4 + \frac{4}{s} + I(2 + s + \frac{10}{s}) = 0$$

$$I\left(\frac{s^2 + 2s + 10}{s}\right) = \frac{12}{s} + 4 - \frac{4}{s}$$

$$= \frac{4s + 8}{s}$$

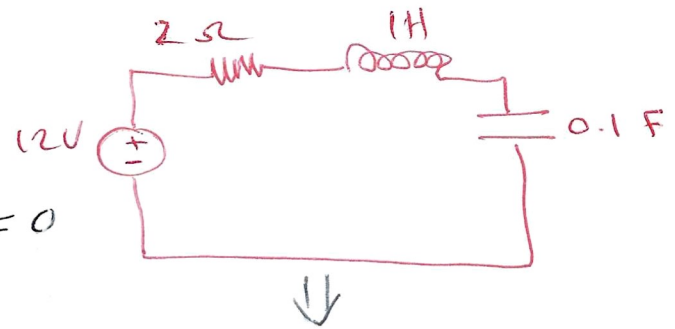


$$I = \frac{4(s+2)}{s^2 + 2s + 10} = \frac{4(s+2)}{(s+1-j3)(s+1+j3)} \cdot \frac{12}{s}$$

$$= \frac{K_1}{s+1-j3} + \frac{K_1^*}{s+1+j3}$$

$$= \frac{2.11 \angle -18.4}{s+1-j3} + \frac{2.11 \angle 18.4}{s+1+j3}$$



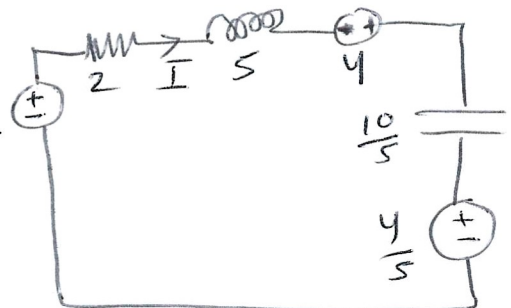
$$i(t) = 2(2.11) e^{-t} \cos(3t - 18.4)$$



Find $i_L(t)$ for $t > 0$ using Thevenin


$V_C(0) = 0$

$i_L(0) = 0$

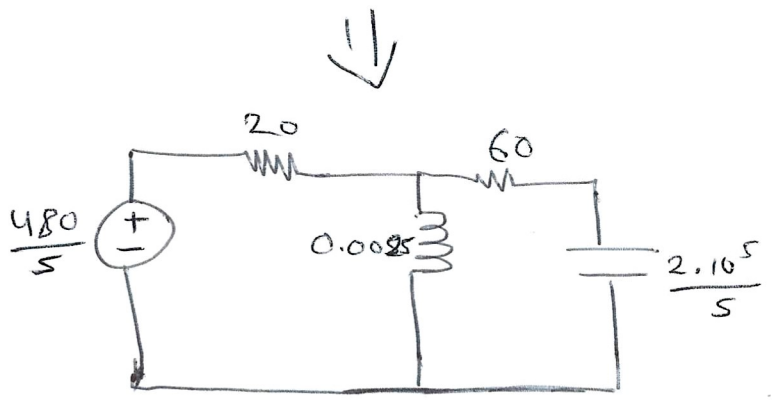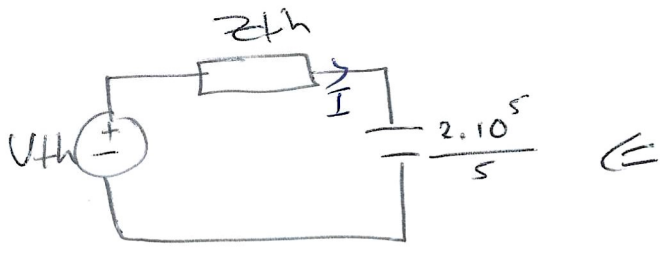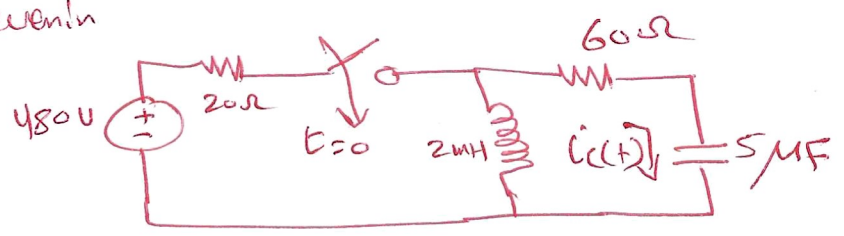


$I = \frac{V_{th}}{Z_{th} + \frac{2.10^5}{s}}$

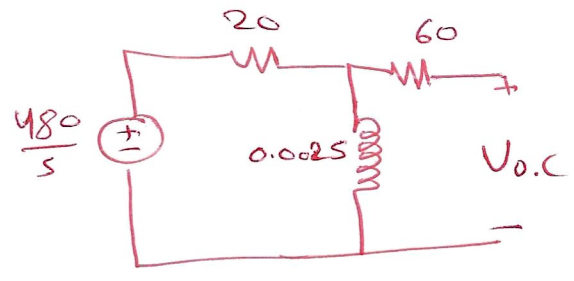$V_{th} = V_{o.c} = \frac{480}{s} * \frac{0.0025}{0.0025 + 20}$
 $= \frac{480}{s + 10^4}$



$Z_{th} = 60 + (20 || 0.0025)$
 $= 60 + \frac{20 * 0.0025}{20 + 0.0025}$
 $= \frac{1200 + 0.165}{20 + 0.0025}$

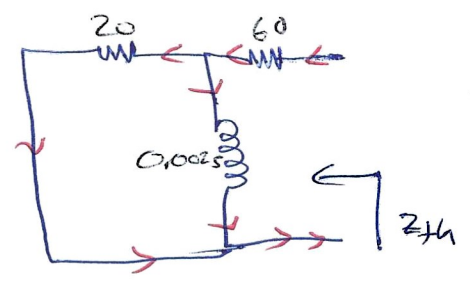


$I_s = \frac{\frac{480}{s + 10^4}}{\frac{1200 + 0.165}{20 + 0.0025}} = \frac{480}{s + 10^4} * \frac{20 + 0.0025}{1200 + 0.165}$

$= \frac{6s}{(s + 5000)^2} = \frac{k_1}{(s + 5000)^2} + \frac{k_2}{(s + 5000)}$
 $= \frac{-30/000}{(s + 5000)^2} + \frac{6}{(s + 5000)} \Rightarrow i(t) = (-30,000e^{-5000t} + 6e^{-5000t})u(t)$


Quiz # 5

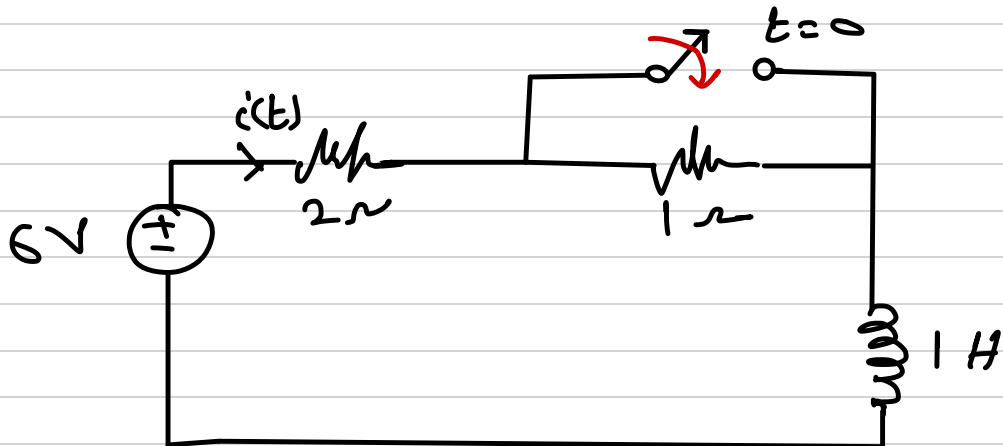① For the circuit shown, obtain $i(t)$ for $t > 0$



Solution: $i(t) = (3 - e^{-2t}) u(t)$

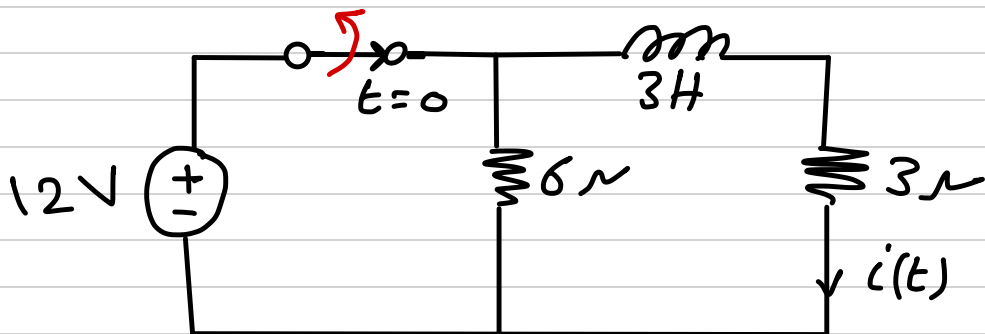② For the circuit shown, obtain $i(t)$ for $t > 0$



Solution: $i(t) = 4 e^{-3t}$