



BIRZEIT UNIVERSITY

كلية العلوم Faculty of Science

دائرة الفيزياء Department of Physics

Phys111 Report

Experiment #4: DC Circuit

Name:	Bayan Saleem Alkamel	ID #:	1231030
Partner:		ID #:	
Section:	12		
Date:			

(1) Abstract:

- Aim of the experiment:

To test the material and find out if it is ohmic or non-ohmic, and to find the value of R_s , R_p practically.

- The main results are:

$$R = 100 \pm 11\Omega$$

$$R_s = 310 \pm 50\Omega$$

$$R_p = 62 \pm 14\Omega$$

(2) Data:

Part A: One resistor circuit

	1.	2.	3.	4.	5.	6.
I (mA)	5	10	15	20	25	30
V (volts)	0.5	1.0	1.5	2.0	2.5	3.0

$\Delta I = 1 \text{ mA}$	$\Delta V = 0.1 \text{ V}$
---------------------------	----------------------------

Part B: Two resistors in series

$I_s = 16 \text{ mA}$	$V_s = 5 \text{ V}$
$\Delta I_s = 1 \text{ mA}$	$\Delta V_s = 0.5 \text{ V}$

Part C: Two resistors in parallel

$I_p = 80 \text{ mA}$	$V_p = 5 \text{ V}$
$\Delta I_p = 10 \text{ mA}$	$\Delta V_p = 0.5 \text{ V}$

(3) Calculations:

Part A: One resistor circuit

From Graph $R = \text{Slope}$ $\Delta R \rightarrow \frac{\Delta R}{R} = \frac{\Delta V}{V} + \frac{\Delta I}{I}$	$R = 100\Omega$	From Color code $R1 = 100\Omega$ $\Delta R1 = 5\Omega$
	$\Delta R = \left(\frac{0.1}{1.75} + \frac{1}{17.5}\right) \times 100$ $\Delta R = 11.42857143\Omega \approx 11$	

Resistance form color code:

Brown	Black	Brown	Gold
$R_1 = 100 \pm 5 \Omega$			

Red	Black	Brown	Gold
$R_2 = 200 \pm 10 \Omega$			

Part B: Two resistors in series

From Experiment $\frac{\Delta R_s}{R_s} = \frac{\Delta V_s}{V_s} + \frac{\Delta I_s}{I_s}$	$R_s = \frac{V_s}{I_s} = \frac{5}{16 \times 10^{-3}} = 312.5\Omega$	From Color code $R_s = R_1 + R_2$ $\Delta R = \Delta R_1 + \Delta R_2$	$R_s = 100 + 200 = 300\Omega$
	$\Delta R_s = \left(\frac{0.5}{5} + \frac{1}{16}\right) \times 312.5$ $\Delta R_s = 50.78125\Omega \approx 50$		$\Delta R_s = 5 + 10 = 15\Omega$

Part C: Two resistors in series

From Experiment $\frac{\Delta R_p}{R_p} = \frac{\Delta V_p}{V_p} + \frac{\Delta I_p}{I_p}$	$R_p = \frac{V_p}{I_p} = \frac{5}{80 \times 10^{-3}} = 62.5\Omega$	From Color code $R_p = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{A}{B}$ $\Delta R_p = \frac{\Delta R_p}{R_p} = \frac{\Delta A}{A} + \frac{\Delta B}{B}$	$R_p = \frac{100 \times 200}{100 + 200} = 66.666\Omega \approx 70$
	$\Delta R_p = \left(\frac{0.5}{5} + \frac{10}{80}\right) \times 62.5$ $\Delta R_p = 14.0625\Omega \approx 14$		$\Delta R_p = 9.9999\Omega \approx 10$

(4) Results:

$R = 100 \pm 11 \Omega$
$R_s = 310 \pm 50 \Omega$
$R_p = 62 \pm 14 \Omega$

(5)Conclusions:

∴The result for part (A) →


$$R_{Th} = 100 \pm 5 \Omega$$

$$R_{exp} = 100 \pm 11 \Omega$$

☼ RANGE TEST:

$$R_{exp} = [100-11, 100+10] = [89,111] \rightarrow 89 \leftarrow \quad \rightarrow 111$$
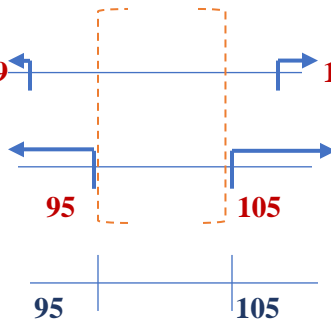
$$R_{Th} = [100-5, 100+5] = [95,105] \rightarrow$$



so, the result is accepted.

∴The result for part (B) →


$$R_{Th} = 300 \pm 15 \Omega$$

$$R_{exp} = 310 \pm 50 \Omega$$

☼ RANGE TEST:

$$R_{exp} = [310-50, 310+50] = [260,360] \rightarrow 260 \leftarrow \quad \rightarrow 360$$
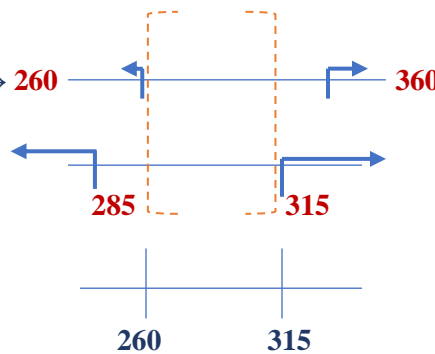
$$R_{Th} = [300-15, 300+15] = [285,315] \rightarrow$$



so, the result is accepted.

∴The result for part (C) →


$$R_{Th} = 70 \pm 10 \Omega$$

$$R_{exp} = 62 \pm 14 \Omega$$

☼ RANGE TEST:

$$R_{exp} = [62-14, 62+14] = [48,76] \rightarrow 48 \leftarrow \quad \rightarrow 76$$
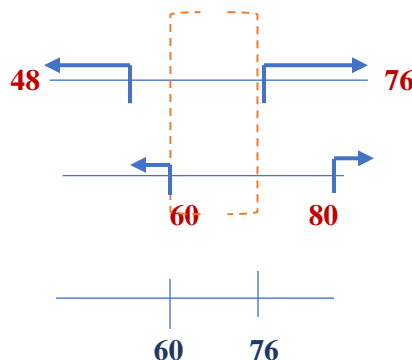
$$R_{Th} = [70-10, 70+10] = [60,80] \rightarrow$$



so, the result is accepted.

☞ The result is accepted in all parts, the value I measured is very close to the true value.

Its due to many possible reasons:

- The way that the measurements was took is accurate (note that the measurements has taken from the photos).
- I focused on taking measurements perfectly.

☞ There are many mistakes that I could have made if I had not measured properly.

(Expected errors) :

The actual current through the resistor is less than the measured current. This is because the ammeter has a finite resistance, and therefore draws a small amount of current itself. Also, the temperature of the room: If the ambient temperature deviates significantly from room temperature, the resistance may change significantly. This is because the resistance of most materials is temperature dependent. It is also possible that the wire may be connected in the wrong places, or the reading may be taken in the wrong place or in a wrong way, so the readings are not completely accurate.

☞ To reduce the errors, the following steps can be taken: Use an ammeter with a low resistance. Take the reading as quickly as possible to minimize the loading effect. Keeping the ambient temperature constant. Checking the connections and make sure that the reading is taken in the correct place and in the correct way.

V vs I

Two points:

A1(3,3.3)

B1(33,3.3)

Slope(R)= $\Delta V/\Delta I$

= $(3.3-0.3)$

$\frac{\quad}{(33-3)\times 10^{-3}}$

R=100 Ω

