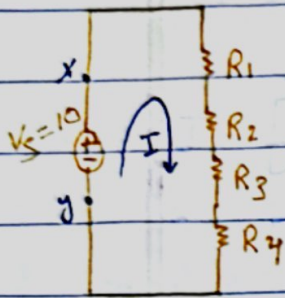


chapter 3:

Simple Resistive circuits


Resistors in series



Series connected resistors carry the same current.

using KVL
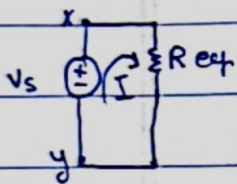
$$-V_s + R_1 I + R_2 I + R_3 I + \dots + R_m I = 0$$




$$I = \frac{V_s}{R_{eq}}$$

$$V_s = (R_1 + R_2 + \dots + R_m) I$$


$$V_s = R_{eq} I$$

$$R_{eq} = \sum_{i=1}^m R_i$$

Resistors in parallel

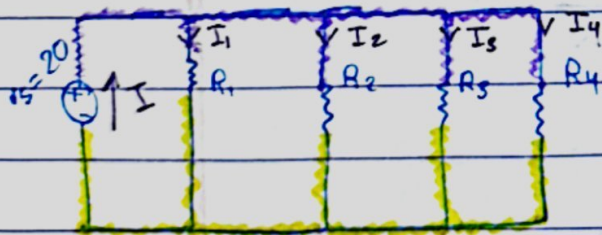

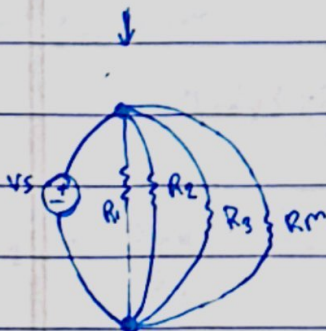parallel connected resistors have the same voltage across their terminal.



Number of nodes = 2


Based on KCL

$$\sum I = 0$$

التيارات الداخلة إلى العقدة الموجبة ← node


$$I = I_1 + I_2 + I_3 + I_4$$

$$I_1 + I_2 + I_3 + I_4 - I = 0$$

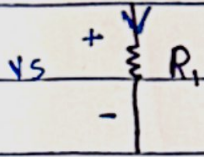

$$I_1 + I_2 + I_3 + I_4 - I = 0$$
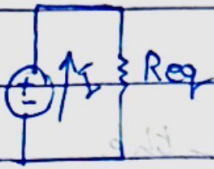
$$\frac{V_s}{R_1} + \frac{V_s}{R_2} + \dots + \frac{V_s}{R_m} = I$$



$$I = \frac{V_s}{R_{eq}}$$

$$\frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3} + \dots = I$$

$$V_s \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \right] = I$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_m}}$$

Cases:

1. IP $m=2$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

2. IP $R_1 = R_2 = R_3 = \dots = R_m$


$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} = \frac{m}{R}$$

$$R_{eq} = \frac{R}{m}$$

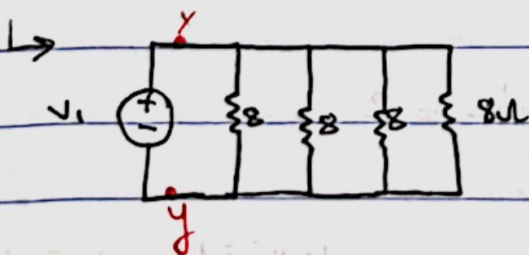Divide the sum of resistances by the number of resistors



$$R_{xy} = \frac{8}{4} = 2\Omega$$

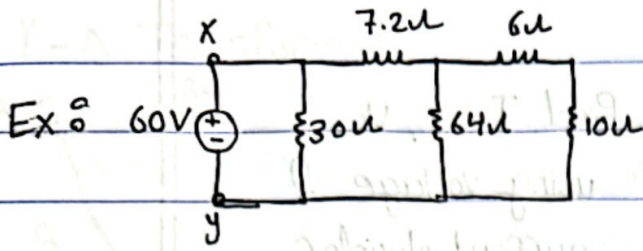


1. calculate R_{xy}

$$((6+10) // 64) = 12.8$$

$$(20 // 30) = 12$$

$$R_{xy} = 12$$

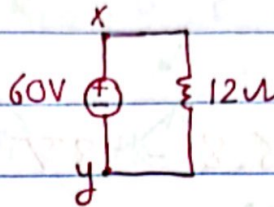


2. calculate I

$$V = RI$$

$$60 = 12 I$$

$$I = 5A$$

Voltage Divider

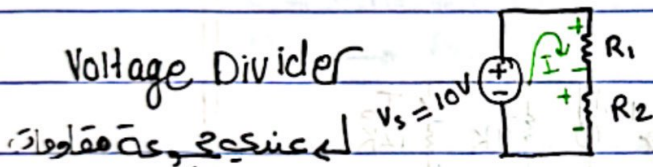

$$-V_s + R_1 I + R_2 I = 0$$

$$I (R_1 + R_2) = V_s$$

$$I = \frac{V_s}{R_1 + R_2}$$

$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V_s$$

$$1. R_{eq} = R_1 + R_2$$


$$2. I_s = \frac{V_s}{R_{eq}}$$

$$3. V_1 = R_1 I_s = \frac{R_1}{R_1 + R_2} V_s$$

$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V_s$$

$$V_2 = R_2 I_s$$

Current Divider

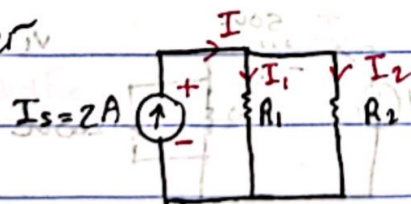

$$V = R_1 I_1 = R_2 I_2 = (R_1 // R_2) I_s$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$


النسبة العكسية

$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

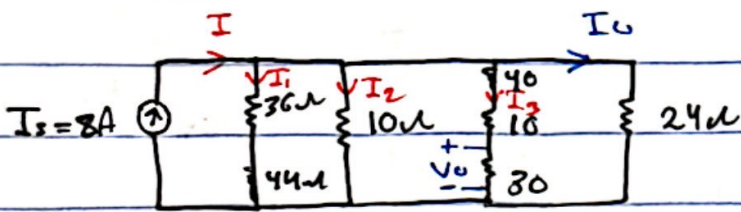

Find I_0 , V_0
using voltage & current divider.

$$R_{eq} = 6\Omega$$

$$V = RI \rightarrow V = 6 \cdot 8 = 48V$$

$$48 = I_1 \cdot 80 \rightarrow I_1 = 0.6A$$

$$48 = 24 I_0 \rightarrow I_0 = 2A$$

$$48 = I_3 \cdot 80 \rightarrow I_3 = 0.6A$$

$$V_0 = I_3 \cdot 30 \rightarrow V_0 = 18V$$



current $4 - 1 - 2 = 1mA \downarrow$

ds Req
للقدوات
12K و 4K


Find I_0 ?

$$V = I_0 R$$

$$-V = 2T \quad I_1 = -I_0$$

$$V = \dots \quad V_1 - V_2 = 0$$

$$12K I_1 - 4K I_2 = 0$$

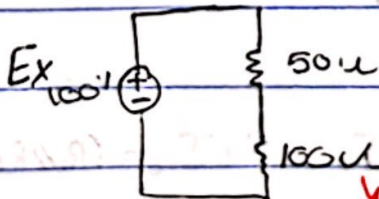

للقاومة الأكبر يتوقف التيار الأكبر



$V_1 = ??$


$$R_{eq} = 150$$

$$V_1 = \left(- \right) \frac{50}{100+50} \times 100$$

$$I_s = \frac{V_s}{R_{eq}} = \frac{100}{150}$$

$$V_1 = \frac{50}{150} \cdot 100 = 33.33$$

Y-Δ Transformation

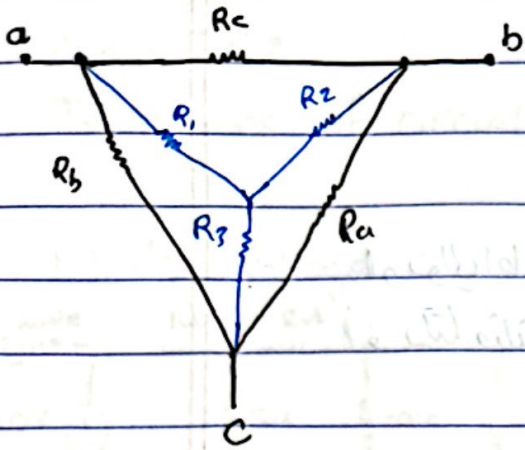


$$R_{ab} = R_1 + R_2 = (R_a + R_b) // R_c$$

$$R_{bc} = R_2 + R_3 = (R_c + R_b) // R_a$$

$$R_{ca} = R_1 + R_3 = (R_c + R_a) // R_b$$

لو بنوف بـ الأزرق ←

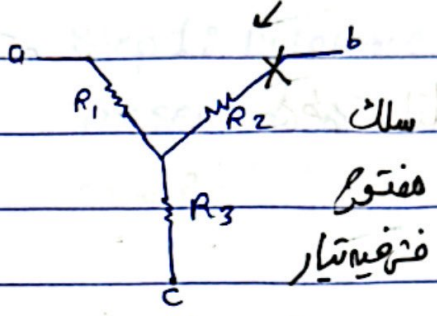

سلك
فتحة
فترقبتار

Y → Δ R_1, R_2, R_3 are given

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$R_1 \rightarrow R_{a \text{ بـ الأزرق}}$

R_3

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

R_2


Δ → Y R_a, R_b, R_c are given

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Ex

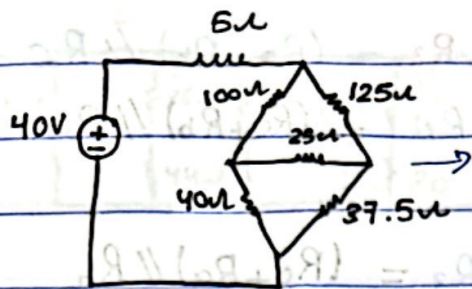


calculate I ?

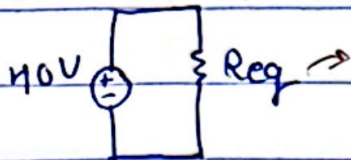بقدرتنا على التوازي
أو التوالي إذا فعلنا
دلتنا صلتنا فوقه



عن طريق دلتنا

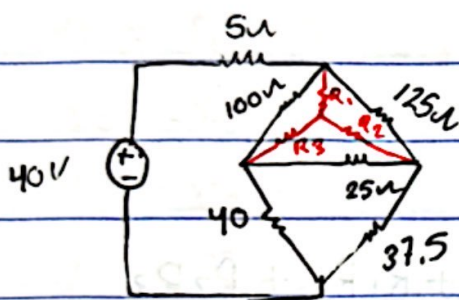

$$R_1 = \frac{100 \times 125}{125 + 125} = 50 \mu$$


العبارتين

المجموع

بتحول نسألها

$$R_2 = \frac{125 \times 25}{250} = 12.5 \mu$$
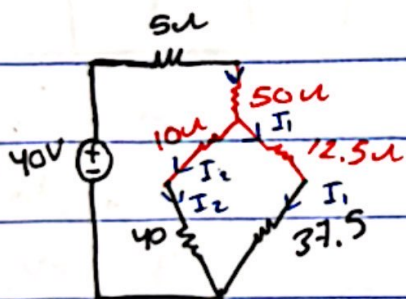
$$R_3 = \frac{100 \times 25}{250} = 10 \mu$$




صرت بقدرنا عليها
تواليا وتوازي

$$R_{eq} = [(12.5 + 37.5) \parallel (10 + 40)] + 50 + 5$$

$$= 25 + 55 = 80$$


$$I = \frac{V}{R} = \frac{40}{80} = 0.5 A$$

Extra on voltage & current divider

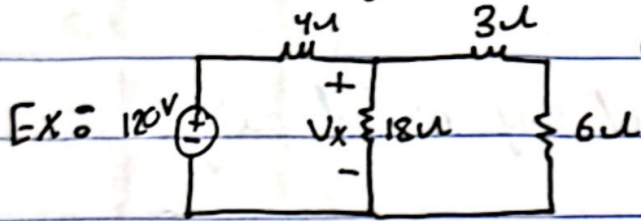

نقطة = ينقسم القوية
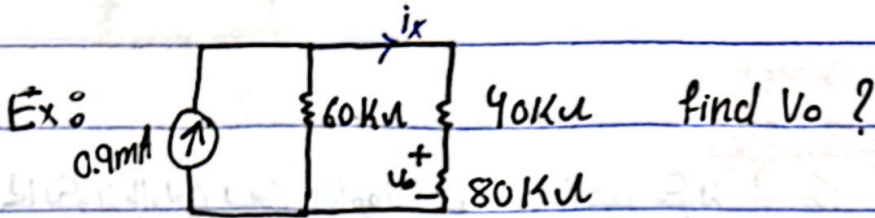
$$V_x = \frac{(18/9)}{(18/9)+4} \times 120 = \frac{6}{10} \times 120 = 72$$



$$V_0 = (80K) (i_x) \quad \text{current}$$

$$= (80K) \left(\frac{60K}{60K + 140 + 80K} \right) \cdot 0.9 \text{ mA}$$

$$= 24 \text{ V}$$

