

# Chapter 9 - Sinusoidal steady-state Analysis

## 9.1 - the sinusoidal source



$$v_s(t) = V_m \sin(\omega t)$$

$T$  - period in seconds

$$f = \frac{1}{T} \text{ frequency in Hz}$$

$$\omega = 2\pi f \text{ angular frequency in radian/sec.}$$

$$v_s(t) = V_m \cos(\omega t + \phi)$$

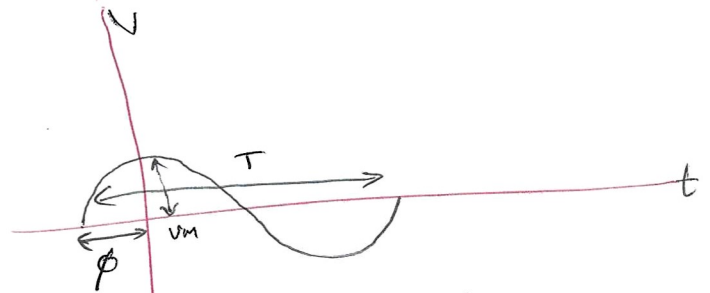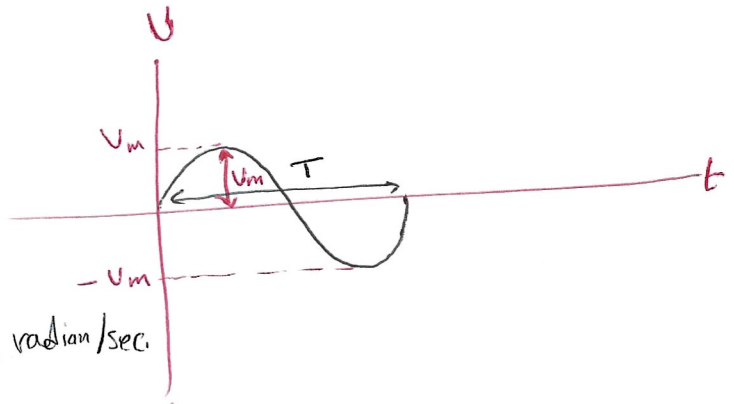

A sinusoidal voltage/current source (independent or dependent) produce a voltage/current that varies sinusoidally with time.


$V_{rms}$  Root Mean square value

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt} = \frac{V_m}{\sqrt{2}}$$

$v_2$  Leads  $v_1$  by phase  $\phi$

$v_1$  lags  $v_2$  by phase  $\phi$

$v_1$  and  $v_2$  are out of phase

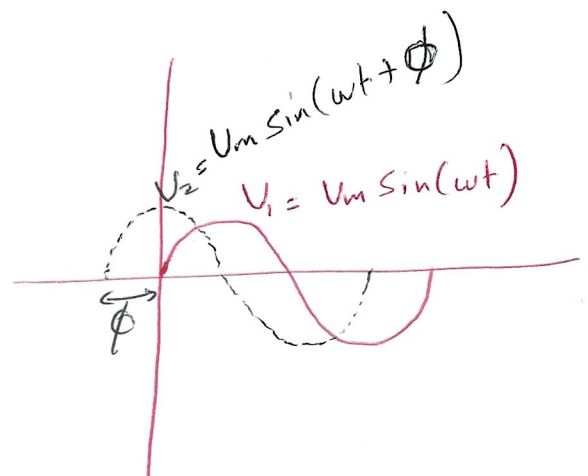

Example - let  $V_1(t) = 10 \sin(\omega t - 30^\circ)$

$$V_2(t) = 15 \sin(\omega t + 10^\circ)$$

$\therefore V_2$  leads  $V_1$  by  $40^\circ$

$V_1$  lags  $V_2$  by  $40^\circ$

Example - let  $i_1(t) = 2 \sin(377t + 45^\circ)$


$$i_2(t) = 0.5 \cos(377t + 10^\circ)$$

$$-\sin \alpha = \cos(\alpha + 90^\circ)$$

$$\cos \alpha = \sin(\alpha + 90^\circ)$$

$$0.5 \cos(377t + 10^\circ) = 0.5 \sin(377t + 100^\circ)$$

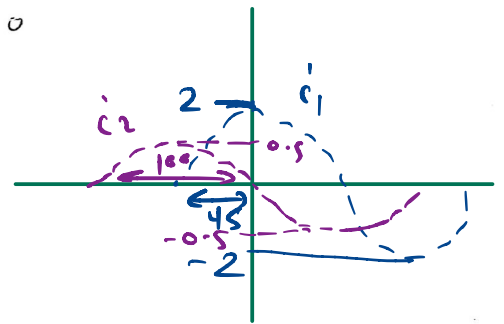$\therefore i_2$  leads  $i_1(t)$  by  $55^\circ$



### Trigonometric Identities

$$\sin(A \pm B) = \sin(A) \cos(B) \pm \cos(A) \sin(B)$$

$$\cos(A \pm B) = \cos(A) \cos(B) \mp \sin(A) \sin(B)$$

$$\sin(\omega t \pm 180^\circ) = -\sin(\omega t)$$

$$\cos(\omega t \pm 180^\circ) = -\cos(\omega t)$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos(\omega t)$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin(\omega t)$$


$$A \cos(\omega t) + B \sin(\omega t) = C \cos(\omega t - \theta)$$

$$C = \sqrt{A^2 + B^2}$$

$$\theta = \tan^{-1}\left(\frac{B}{A}\right)$$

\* Complex numbers :

→ Rectangular / cartesian  $z = a + jb$   
→ exponential  $|z| e^{j\theta}$   
→ phasor / polar  $|z| \angle \theta$

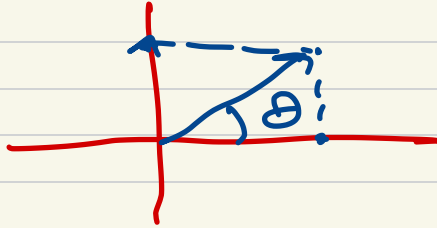

$$a = |z| \cos \theta$$

$$b = |z| \sin \theta$$

$$z = a + jb \Rightarrow |z| = \sqrt{a^2 + b^2}$$

$$\angle \theta = \tan^{-1} \frac{b}{a}$$

\* Euler

$$A e^{j\theta} = A (\cos \theta + j \sin \theta)$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

Example: A sinusoidal current has a maximum amplitude of 20A.

The current passes through one complete cycle in 1ms.

The magnitude of the current at zero time is 10A.

$$I_m = 20A$$

$$T = 1ms$$

$$I(0) = 10A$$

a) what is the frequency of the current in hertz?

$$T = 1ms \Rightarrow f = \frac{1}{T} = 1000 \text{ Hz}$$

b) what is the frequency in radians per second?

$$\omega = 2\pi f = 2\pi(1000) = 2000\pi \text{ rad/s}$$

c) write the expression for  $i(t)$  using the cosine function. Express  $\phi$  in degree.

$$i(t) = I_m \cos(\omega t + \phi)$$

$$= 20 \cos(2000\pi t + \phi)$$

$$\text{but at } t=0 \quad i(0) = 10A$$

$$i(0) = 10A = 20 \cos(\phi)$$

$$\Rightarrow \phi = 60^\circ$$

$$\therefore i(t) = 20 \cos(2000\pi t + 60^\circ) \text{ A}$$

d) what is the rms value of the current?

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.14 \text{ A}$$

## 9.2 The Sinusoidal Response

Find  $i(t)$  for  $t > 0$

Given  $V_s(t) = V_m \cos(\omega t)$  V

KVL

$$V_s(t) = Ri(t) + L \frac{di(t)}{dt}$$

$$V_m \cos(\omega t) = Ri(t) + L \frac{di(t)}{dt} \quad (\text{first order nonhomogeneous differential equation})$$

$$\therefore i(t) = i_n(t) + i_p(t)$$

in: initial  
A: final

$$= Ae^{-t/\tau} + i_p(t)$$

$$i_p(t) = I_1 \cos(\omega t) + I_2 \sin(\omega t)$$

to find  $I_1$  and  $I_2$

$$V_m \cos(\omega t) = Ri(t) + L \frac{di}{dt}$$

$$V_m \cos(\omega t) = R [I_1 \cos(\omega t) + I_2 \sin(\omega t)] + L\omega [-I_1 \sin(\omega t) + I_2 \cos(\omega t)]$$

$$= (-LI_1\omega + RI_2) \sin(\omega t) + (LI_2\omega + RI_1) \cos(\omega t)$$

$$\therefore -\omega L I_1 + R I_2 = 0 \quad \dots (1)$$

$$\omega L I_2 + R I_1 = V_m \quad \dots (2)$$

$$I_1 = \frac{R V_m}{R^2 + \omega^2 L^2}$$


$$I_2 = \frac{\omega L V_m}{R^2 + \omega^2 L^2}$$

$$\therefore i_p(t) = \frac{R V_m}{R^2 + \omega^2 L^2} \cos(\omega t) + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin(\omega t)$$

From the identity  $A \cos(\omega t) + B \sin(\omega t)$

$$i_p(t) = C \cos(\omega t - \phi)$$
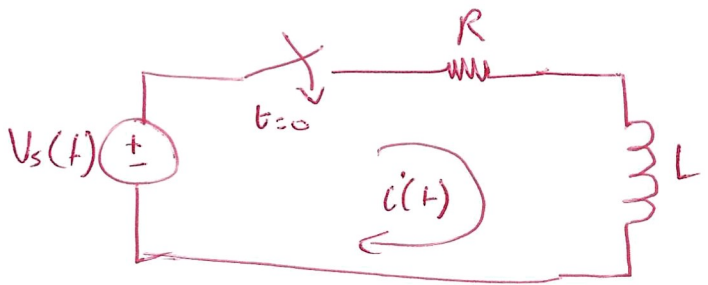
$$C \cos(\omega t - \phi) = C \cos(\omega t) \cos(\phi) + C \sin(\omega t) \sin(\phi)$$



given that  $i_L(0^-) = 0$

$$I_1 = C \cos(\phi)$$

$$I_2 = C \sin(\phi)$$

$$\frac{I_2}{I_1} = \frac{C \sin(\phi)}{C \cos(\phi)} = \tan \phi$$

$$\phi = \tan^{-1}\left(\frac{I_2}{I_1}\right) = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\begin{aligned} I_1^2 + I_2^2 &= C^2 \cos^2 \phi + C^2 \sin^2 \phi \\ &= C^2 (1) \\ &= C^2 \end{aligned}$$

$$\therefore C = \sqrt{I_1^2 + I_2^2}$$

$$C = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\therefore i_p(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$

$$\begin{aligned} \therefore i(t) &= i_n(t) + i_p(t) \\ &= A e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right) \end{aligned}$$

$$i(0) = 0$$

$$\therefore 0 = A + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(-\tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$

$$\therefore A = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(-\tan^{-1}\left(\frac{\omega L}{R}\right)\right)$$

$i(t)$  = transient component + steady state component

the steady state solution

$$i(t) = \frac{U_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \tan^{-1}(\frac{\omega L}{R}))$$

- \* the steady state solution is sinusoidal function
- \* the frequency of the solution is the same as the frequency of the source
- \* the maximum amplitude of the solution differs from the maximum amplitude of the source  $U_m$  for the source and  $\frac{U_m}{\sqrt{R^2 + \omega^2 L^2}}$  for the solution
- \* the phase angle of the solution differs from the phase angle of the source.

## 9.3 The phasor

The phasor is a complex number carries the amplitude and phase angle information of a sinusoidal function.

$$e^{\pm j\theta} = \cos(\theta) \pm j \sin(\theta)$$

$$\cos(\theta) = \operatorname{Re}\{e^{j\theta}\} \quad \sin(\theta) = \operatorname{Im}\{e^{j\theta}\}$$

$$\cos(\omega t + \theta) = \operatorname{Re}\{e^{j(\omega t + \theta)}\}$$

$$U_m \cos(\omega t + \theta) = U_m \operatorname{Re}\{e^{j(\omega t + \theta)}\} = \operatorname{Re}\{U_m e^{j\omega t} e^{j\theta}\}$$

So phasor transform of  $p(V_m \cos(\omega t + \theta)) = V_m e^{j\theta} = \vec{V}$

$$\vec{V} = V_m e^{j\theta} = V_m \angle \theta$$

Example:-  $i(t) = 6 \cos(50t - 40^\circ) \text{ A}$

$$\vec{I} = 6 \angle -40^\circ \text{ A}$$

Example:-  $v(t) = -4 \sin(30t + 50^\circ) \text{ V}$

$$= 4 \cos(30t + 140^\circ) \text{ V}$$

$$\vec{V} = 4 \angle 140^\circ \text{ V}$$

$$\begin{aligned} \cos \theta &= \sin(\theta + 90^\circ) \\ \sin \theta &= -\cos(\theta + 90^\circ) \\ \sin \theta &= \cos(\theta - 90^\circ) \\ \cos \theta &= -\sin(\theta - 90^\circ) \end{aligned}$$

Example:- If  $y_1 = 20 \cos(\omega t - 30^\circ)$  and  $y_2 = 40 \cos(\omega t + 60^\circ)$ , express

$y = y_1 + y_2$  as a single sinusoidal function.

$$\vec{Y}_1 = 20 \angle -30^\circ$$

$$\vec{Y}_2 = 40 \angle 60^\circ$$

$$\vec{Y} = \vec{Y}_1 + \vec{Y}_2 = 20 \angle -30^\circ + 40 \angle 60^\circ$$

$$= (17.32 - j10) + (20 + j34.64)$$


$$= 37.32 + j24.64 = 44.72 \angle 33.43^\circ$$

$$\therefore y = 44.72 \cos(\omega t + 33.43^\circ)$$



# 9.4 The passive Circuit Elements in the Frequency Domain

## \* Resistor

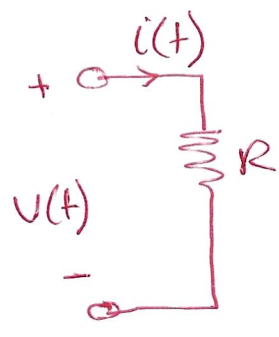

$$V(t) = R i(t)$$

$$U_m e^{j(\omega t + \theta_v)} = R I_m e^{j(\omega t + \theta_i)}$$


$$U_m e^{j\theta_v} = R I_m e^{j\theta_i}$$

$$U_m \angle \theta_v = R I_m \angle \theta_i$$


$$U_m = R I_m$$

$$\angle \theta_v = \angle \theta_i$$

$$\vec{U} = R \vec{I}$$

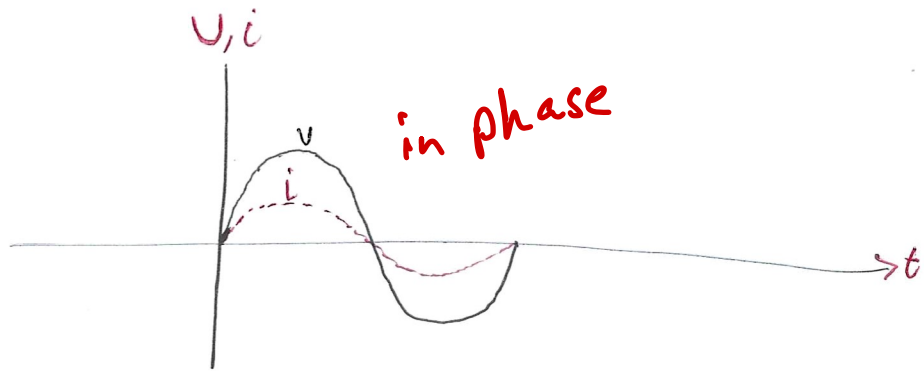


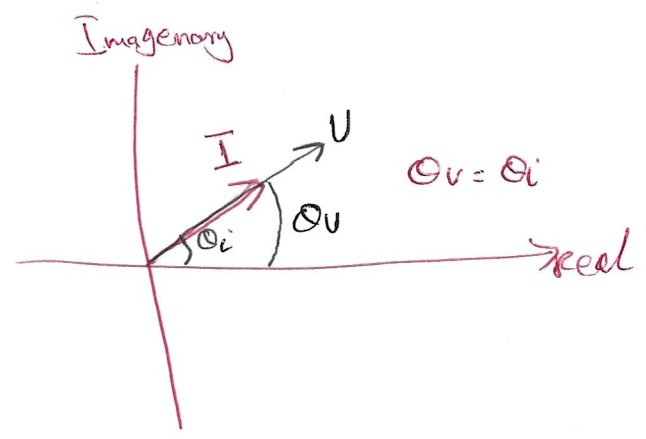\* Voltage and current of a resistor are in phase



# \* Inductor

$$v(t) = L \frac{di(t)}{dt}$$

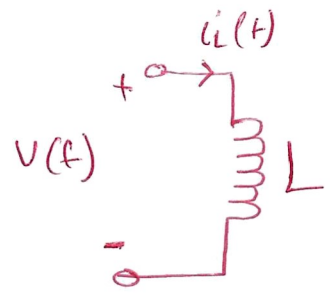

$$V_m e^{j(\omega t + \phi_v)} = L \frac{d}{dt} (I_m e^{j(\omega t + \phi_i)})$$

$$V_m e^{j(\omega t + \phi_v)} = j\omega L I_m e^{j(\omega t + \phi_i)}$$


$$V_m e^{j\phi_v} = j\omega L I_m e^{j\phi_i}$$

$$V_m \angle \phi_v = j\omega L I_m \angle \phi_i = \omega L I_m \angle \phi_i + 90^\circ$$

$$\vec{V} = j\omega L \vec{I}$$


$$V_m = \omega L I_m$$

$$\phi_v = \phi_i + 90^\circ$$

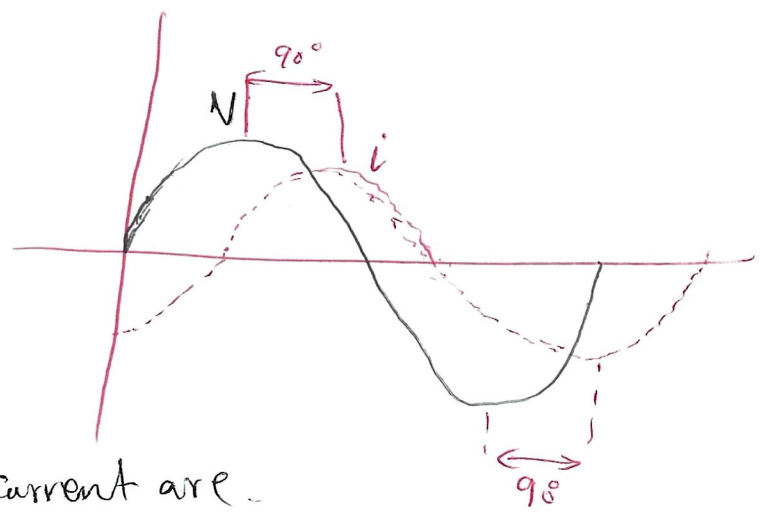

The sinusoidal voltage and current are out of phase of \$90^\circ\$

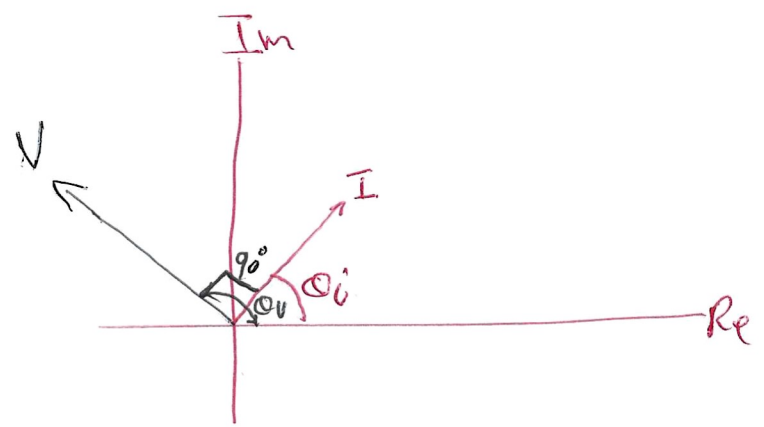The voltage leads the current by \$90^\circ\$ and the current lags the voltage by \$90^\circ\$



# \* Capacitor $C$

$$i(t) = C \frac{dV(t)}{dt}$$

$$I_m e^{j(\omega t + \theta_i)} = C \frac{d}{dt} (V_m e^{j(\omega t + \theta_v)})$$

$$I_m e^{j(\omega t + \theta_i)} = j\omega C V_m e^{j(\omega t + \theta_v)}$$

$$I_m e^{j\theta_i} = j\omega C V_m e^{j\theta_v}$$

$$I_m \angle \theta_i = j\omega C V_m \angle \theta_v$$

$$= \omega C V_m \angle \theta_v + 90^\circ$$




$$\vec{I} = j\omega C \vec{V}$$

$$I_m = \omega C V_m$$




$$\Rightarrow V_m = I_m \left( \frac{1}{\omega C} \right)$$

$$\theta_i = \theta_v + 90^\circ$$


$$\theta_v = \theta_i - 90^\circ$$

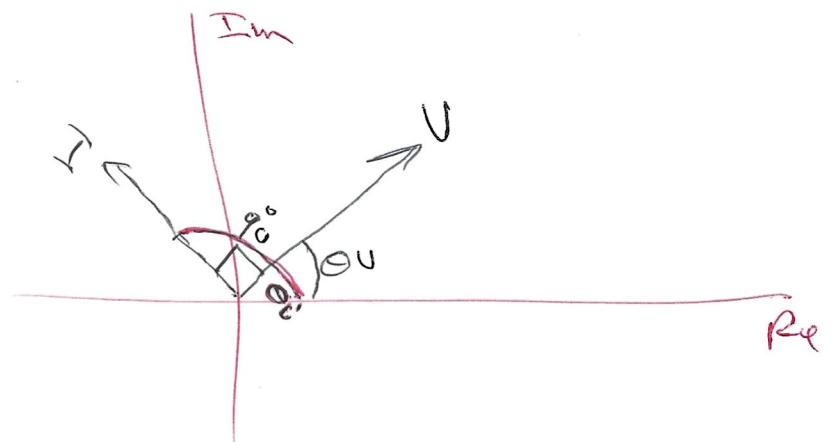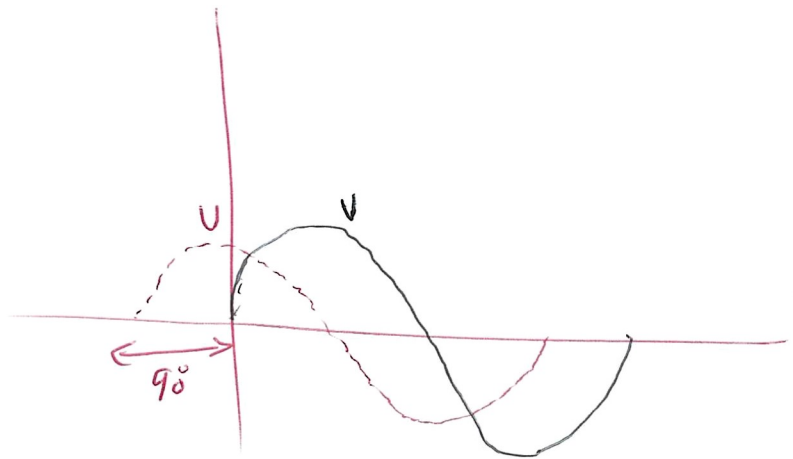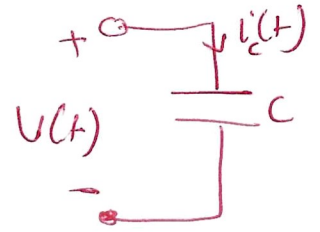

# Passive Elements in Phasor-domain :

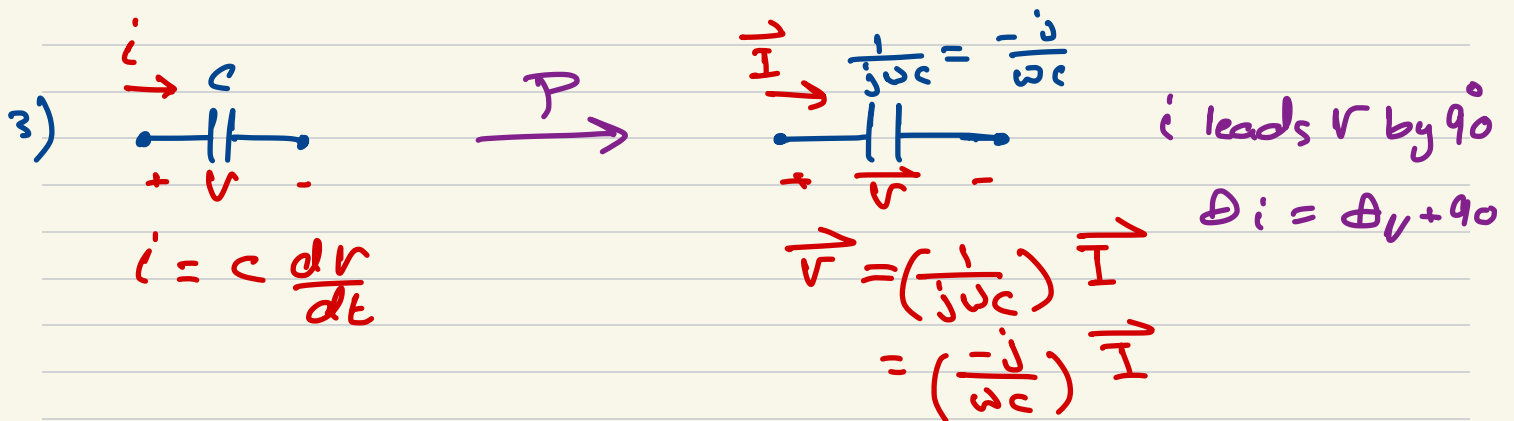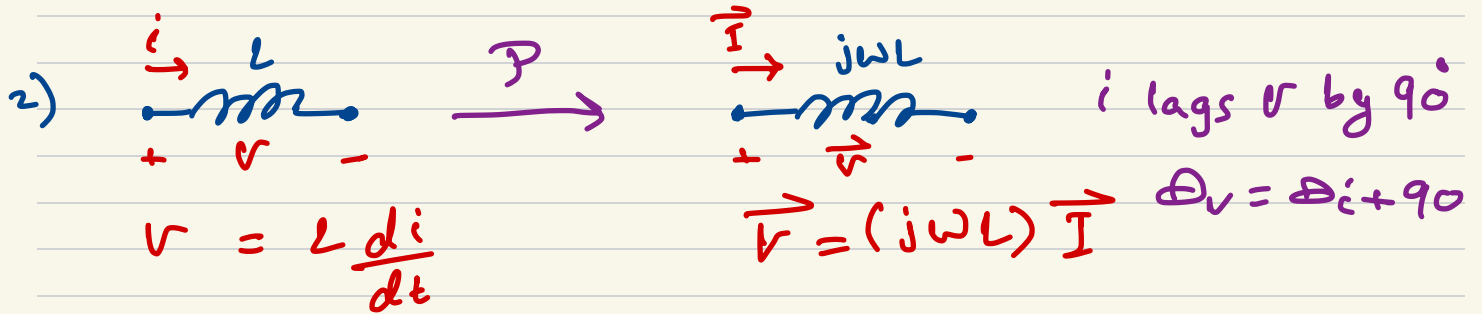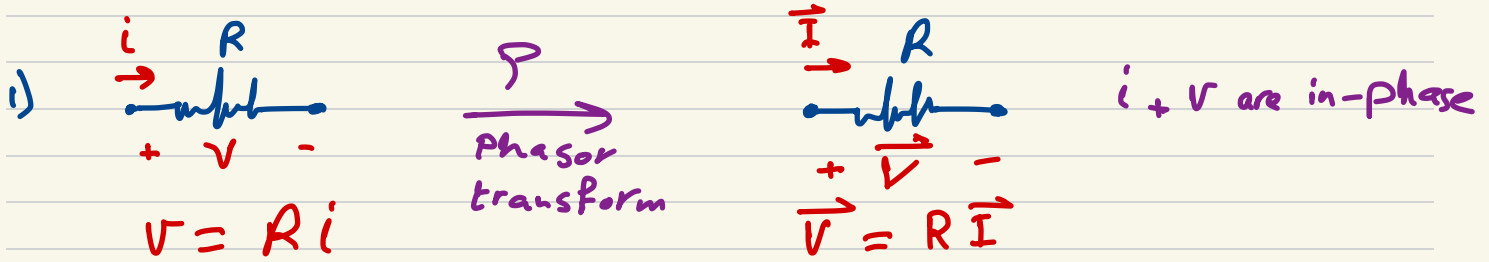

Impedance

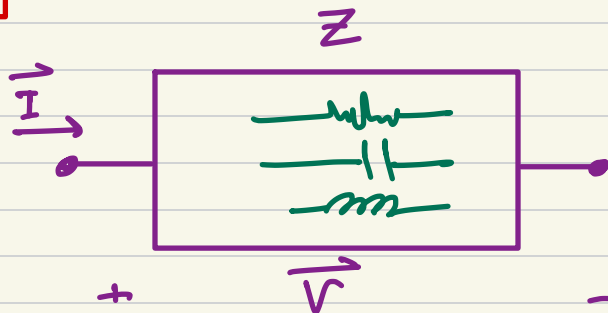

$$\vec{V} = Z \vec{I}$$

impedance

# Impedance, Reactance and Admittance

The relation between the voltage and current on the phasor domain (Complex or frequency) for the three elements

$$\vec{V}_R = R \vec{I}$$

$$\vec{V}_L = j\omega L \vec{I}$$

$$\vec{V}_C = \frac{1}{j\omega C} \vec{I}$$

$$V = Z I$$

$$Z_R = R$$

Impedance of a resistor

$$a = R, \quad b = 0, \quad Z = a + jb$$

$$Z_L = j\omega L$$

impedance of an inductor

$$a = 0, \quad b = \omega L$$

$$Z_C = \frac{1}{j\omega C}$$

Impedance of a capacitor

$$a = 0, \quad b = \frac{-1}{\omega C} = \frac{-j}{\omega C}$$

The imaginary part of the impedance is called Reactance

$$Z = a + jb$$

a : Resistive  
b : Reactance

Reactance of a resistor

$$X_R = 0$$

Reactance of an inductor

$$X_L = \omega L$$

Reactance of a capacitor

$$X_C = \frac{-1}{\omega C}$$

The Admittance is the reciprocal of the impedance

$$Y = \frac{1}{Z}$$

$$Y_R = \frac{1}{Z_R} = \frac{1}{R}$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{j\omega L} = -\frac{j}{\omega L}$$

$$Z(j\omega) = \frac{\vec{V}}{\vec{I}} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i}$$

$$= \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$= |Z| \angle \theta_z$$

$$= R + jX$$

$R \equiv$  Resistive part

$X \equiv$  Reactive part


$$|Z| = \sqrt{R^2 + X^2}$$

$$R = |Z| \cos(\theta_z)$$


$$X = |Z| \sin(\theta_z)$$

$$\theta_z = \tan^{-1}\left(\frac{X}{R}\right)$$


Time domain

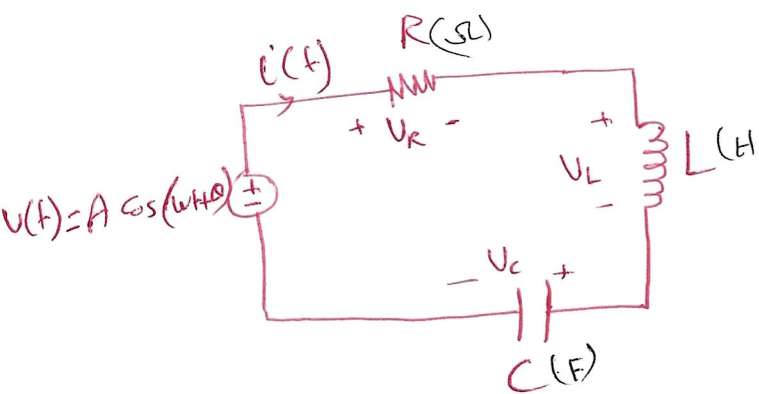

Phasor (Complex, frequency) domain

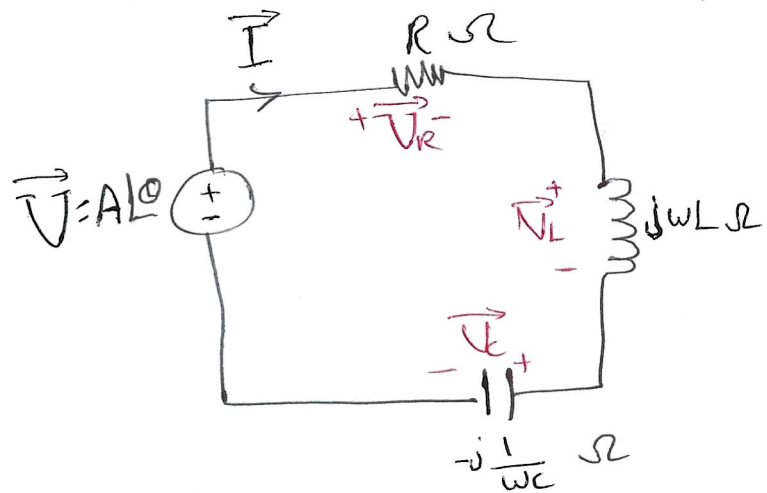

Example

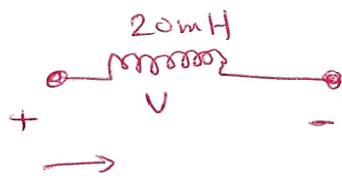

$$i(t) = 10 \cos(10000t + 30^\circ) \text{ mA}$$

Calculate:-

a) The inductive Reactance:-

$$\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$$

b) The impedance of the inductor:-

$$Z_L = j\omega L = j200 \Omega$$

$$\begin{aligned} Z_1 * Z_2 &= (|Z_1| \angle \theta_1) (|Z_2| \angle \theta_2) \\ &= |Z_1| |Z_2| \angle \theta_1 + \theta_2 \\ \frac{Z_1}{Z_2} &= \frac{|Z_1| \angle \theta_1}{|Z_2| \angle \theta_2} = \frac{|Z_1|}{|Z_2|} \angle \theta_1 - \theta_2 \end{aligned}$$


c) The phasor Voltage  $\vec{V}$

$$\vec{V}_L = \vec{I} Z_L = (10 \angle 30^\circ) (200 \angle 90^\circ) \times 10^{-3} = 2 \angle 120^\circ \text{ V}$$

d) the steady state expression for  $u(t)$

$$u_L(t) = 2 \cos(10,000t + 120^\circ) \text{ V}$$

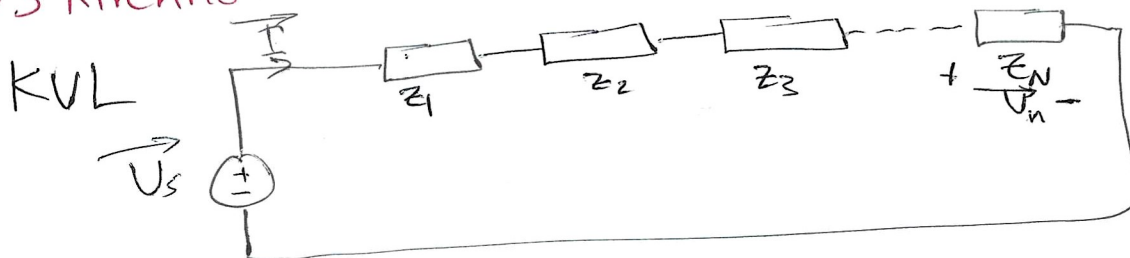9.5 Kirchhoff's Laws in the Frequency Domain:-




$$\vec{U}_s = \vec{U}_1 + \vec{U}_2 + \vec{U}_3 + \dots + \vec{U}_n$$

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots + Z_N$$


$$\vec{U}_n = \frac{Z_n}{Z_1 + Z_2 + \dots + Z_N} \vec{U}_s$$
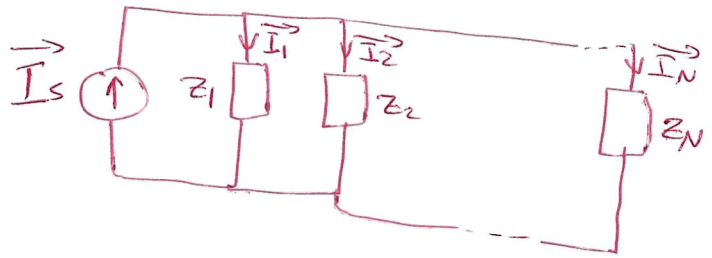
# KCL


$$\vec{I}_S = \vec{I}_1 + \vec{I}_2 + \dots + \vec{I}_N$$


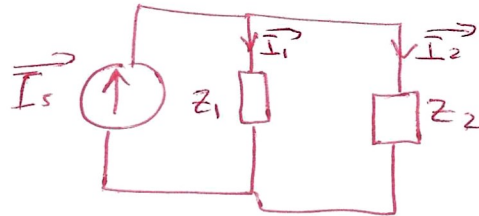
$$\vec{I}_1 = \frac{Z_2}{Z_1 + Z_2} \vec{I}_S$$



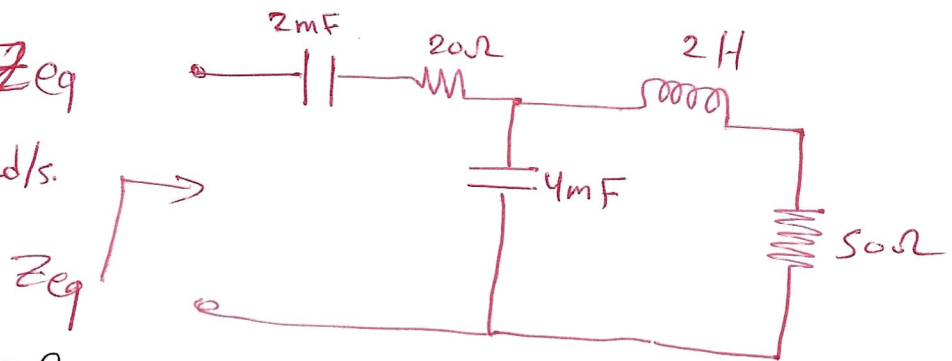
Example: find  $Z_{eq}$   
given that  $\omega = 10 \text{ rad/s}$ .



$$Z_{2mF} = -j \left( \frac{1}{10 \times 2 \times 10^{-3}} \right) = -j50 \Omega$$

$$Z_{2H} = j(10)(2) = j20 \Omega$$
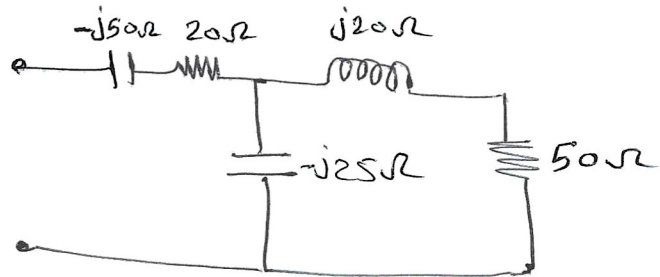
$$Z_{4mF} = -j \left( \frac{1}{10 \times 4 \times 10^{-3}} \right) = -j25 \Omega$$





$$Z_1 = 50 + j20$$

$$Z_2 = (-j25 \parallel Z_1)$$

$$= \frac{-j25(50 + j20)}{50 + j20 - j25}$$
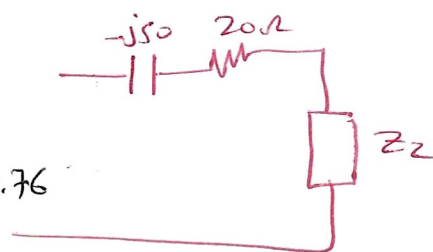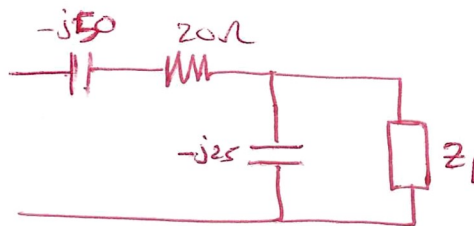
$$= \frac{-j1250 + 500}{50 - j5} = 12.38 - j23.76$$



$$Z_{eq} = -j50 + 20 + Z_2$$


$$= 32.38 - j73.76 \Omega$$



Example 8 - For the circuit shown below, the source voltage is

sinusoidal

$$V_s(t) = 750 \cos(5000t + 30^\circ)$$

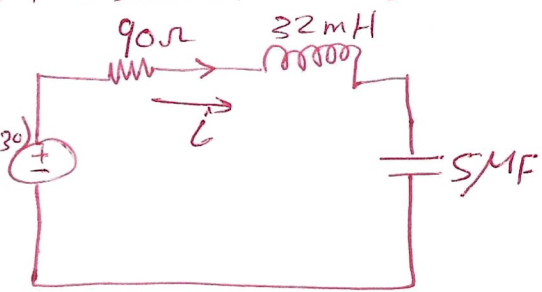


a) construct the frequency-domain equivalent circuit?

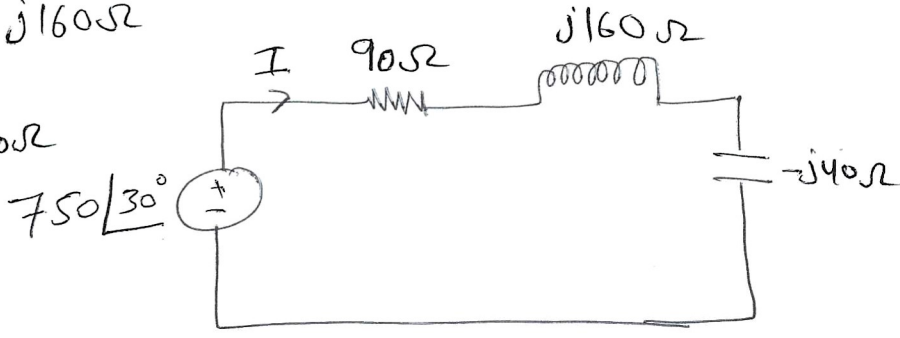b) calculate the steady state current  $i(t)$

$$Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \Omega$$

$$Z_C = -j\left(\frac{1}{\omega C}\right) = -j\left(\frac{1}{(5000)(5 \times 10^{-6})}\right) = -j40 \Omega$$




$$\vec{I} = \frac{\vec{V}}{Z} = \frac{750 \angle 30^\circ}{90 + j160 - j40} = \frac{750 \angle 30^\circ}{90 + j120}$$

$$= \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A}$$

$$\therefore i(t) = 5 \cos(5000t - 23.13^\circ) \text{ A}$$

Example 9 - Calculate  $V_o(t)$


$$V_s(t) = 10 \cos(10t + 75^\circ)$$

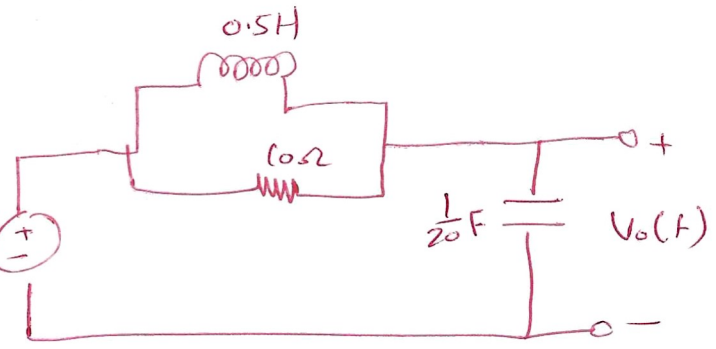

$$\vec{V}_o = \frac{-j2}{-j2 + (10 || j5)} \cdot 10 \angle 75^\circ$$

$$\vec{V}_o = 7.071 \angle -60^\circ \text{ V } \angle 75^\circ$$

$$V_o(t) = 7.07 \cos(10t - 60^\circ) \text{ V}$$

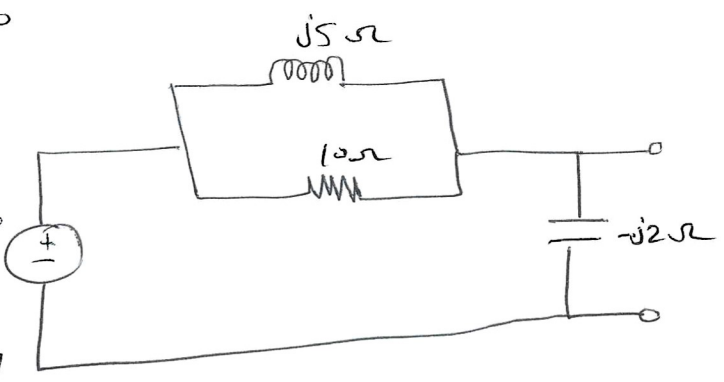



Example 8 - Calculate  $i_o(t)$

$$i_s(t) = 0.05 \cos(2000t) \text{ A}$$


$$I_o = \frac{-j500}{-j500 + j1000 + 500} (0.05 \angle 0^\circ)$$

$$= 0.03535 \angle -45^\circ - 135^\circ$$
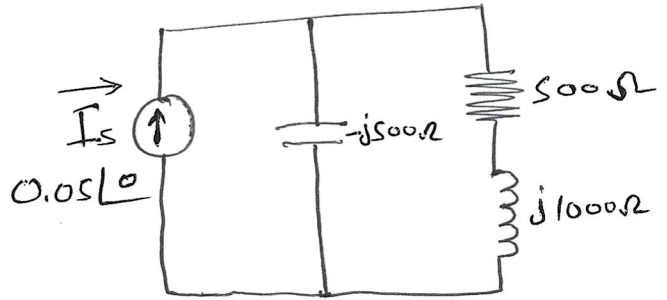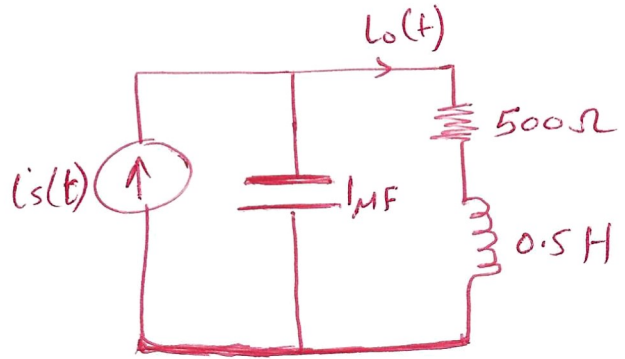
$$\therefore i_o(t) = 0.03535 \cos(2000t - 45^\circ) \text{ A}$$



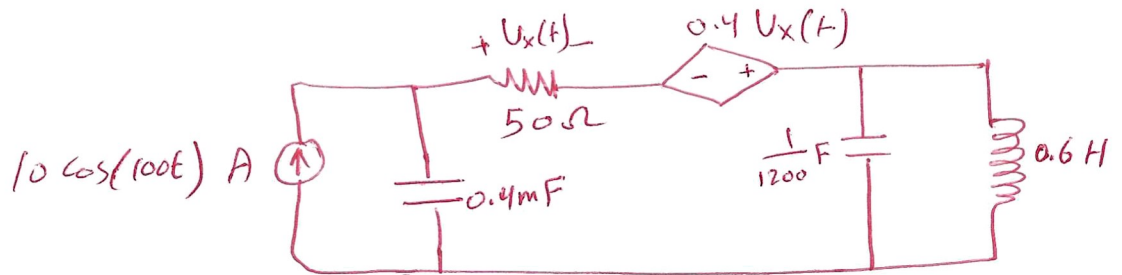Example 9 For the circuit shown, find  $U_x(t)$ ?




$$Z_1 = -j12 \parallel j60$$

$$= \frac{(-j12)(+j60)}{j60 - j12}$$

$$= \frac{720}{j48} = \frac{720 \angle 0^\circ}{48 \angle 90^\circ}$$

$$= -j15 \Omega$$

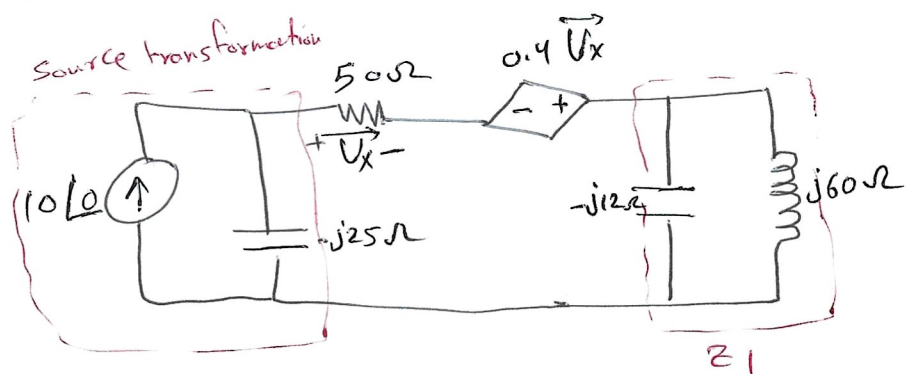


KVL

$$-250 \angle 90^\circ + I(-j15 - j25 + 50) - 0.4 U_x = 0$$

$$250 \angle 90^\circ$$

$$U_x = 50I$$
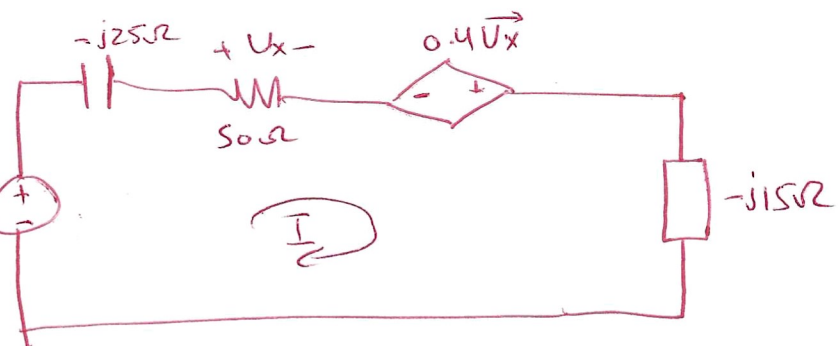
$$-250 \angle 90^\circ + 50I - 20I - j40I = 0$$




$$I = \frac{250 \angle 90^\circ}{36.87} \text{ A}$$

$$\vec{V}_x = 50 \vec{I}$$

$$= (50 \angle 0^\circ) (5 \angle -36.87^\circ) = 250 \angle -36.87^\circ \text{ V}$$

$$V_x(t) = 250 \cos(\omega t - 36.87^\circ) \text{ V}$$

Delta to Wye Transformation

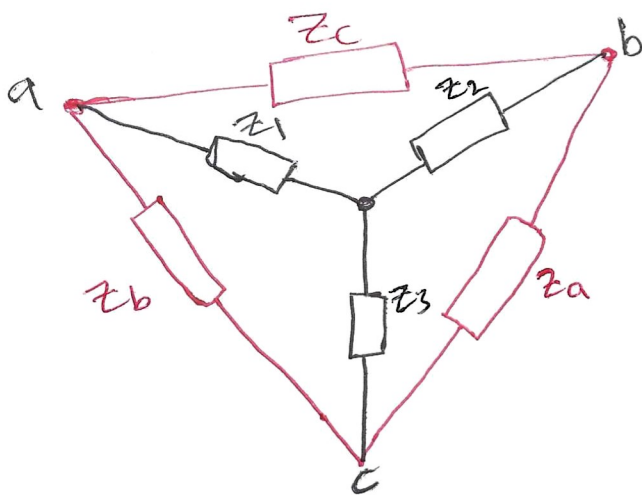

$\Delta$  to  $Y$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$Y$  to  $\Delta$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

## Nodal Analysis

Example 8- Use the node Voltage method to find the branch currents

$I_a$ ,  $I_b$  and  $I_c$  in the circuit shown

at node (1)

$$-10.6 + \frac{V_1}{10} + \frac{V_1 - V_2}{1 + j2} = 0$$

$$V_1(1.1 + j0.2) - V_2 = 10.6 + j21.2$$

at node (2)

$$\frac{V_2 - V_1}{1 + j2} + \frac{V_2}{-j5} + \frac{V_2 - 20I_x}{5} = 0 \quad \text{since} \quad I_x = \frac{V_1 - V_2}{1 + j2}$$

$$-5V_1 + (4.8 + j0.6)V_2 = 0$$

$$\Rightarrow V_1 = 68.4 - j16.8 \text{ V}$$


$$V_2 = 68 - j26 \text{ V}$$

$$I_a = \frac{V_1}{10} = 6.84 - j1.68 \text{ A}$$

$$I_b = \frac{V_2 - 20I_x}{5} = -1.44 - j11.92 \text{ A}$$


$$I_c = \frac{V_2}{-j5} = 5.2 + j13.6 \text{ A}$$
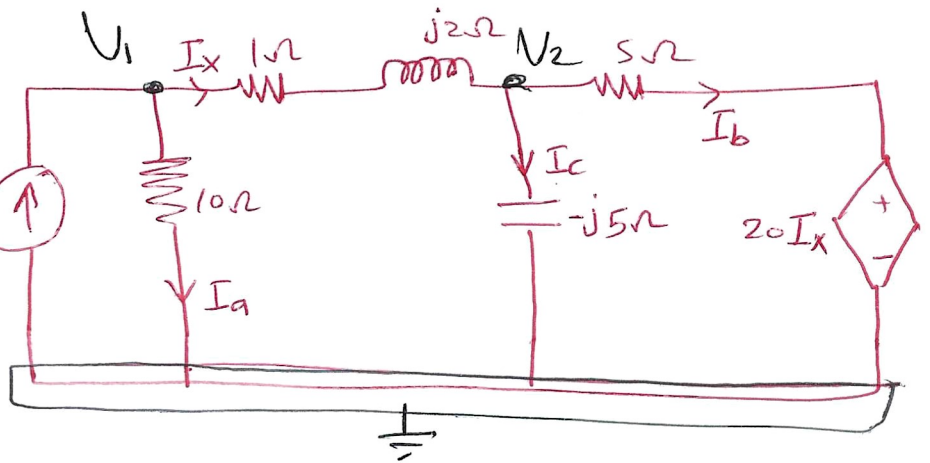
$$I_x = \frac{V_1 - V_2}{1 + j2} = 3.76 + j1.68 \text{ A}$$



Mesh Analysis 5

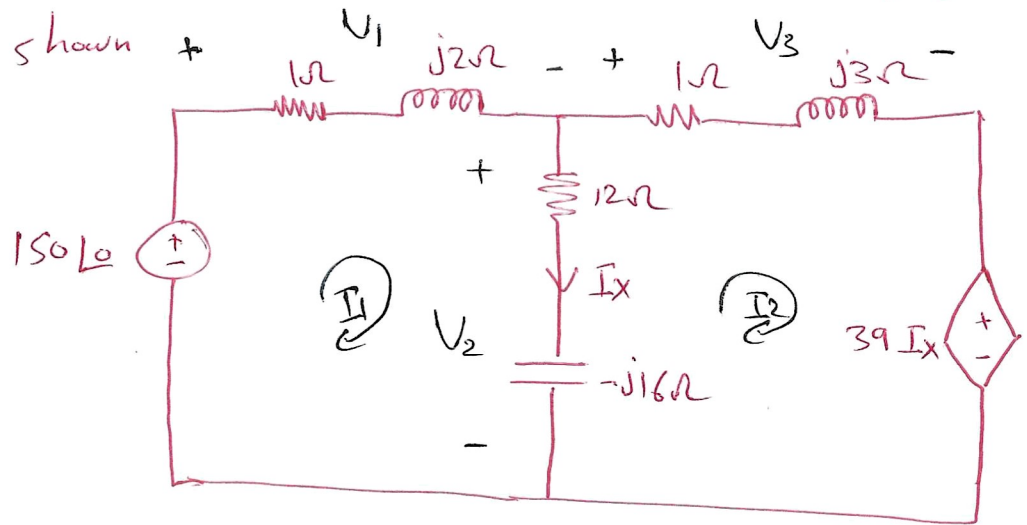Example 3 - use the mesh current method to find the voltages  $V_1$ ,  $V_2$  and  $V_3$  in the circuit shown



for mesh ①

$$-150\angle 0 + I_2(1+12+j2+j16) - I_2(12-j16) = 0$$

for mesh ②

$$I_2(1+12+j3-j16) - I_1(12-j16) + 39I_x = 0$$

$$I_x = I_1 - I_2$$

solving for  $I_1$  and  $I_2$

$$I_1 = -26 - j52 \text{ A}$$

$$I_2 = -24 - j58 \text{ A}$$

$$I_x = I_1 - I_2 = -2 + j6 \text{ A}$$


$$V_1 = (1+j2)I_1 = 78 - j104 \text{ V}$$

$$V_2 = (12-j16)I_x = 72 + j104 \text{ V}$$


$$V_3 = (1+j3)I_2 = 150 - j130 \text{ V}$$

# \* Source Transformation

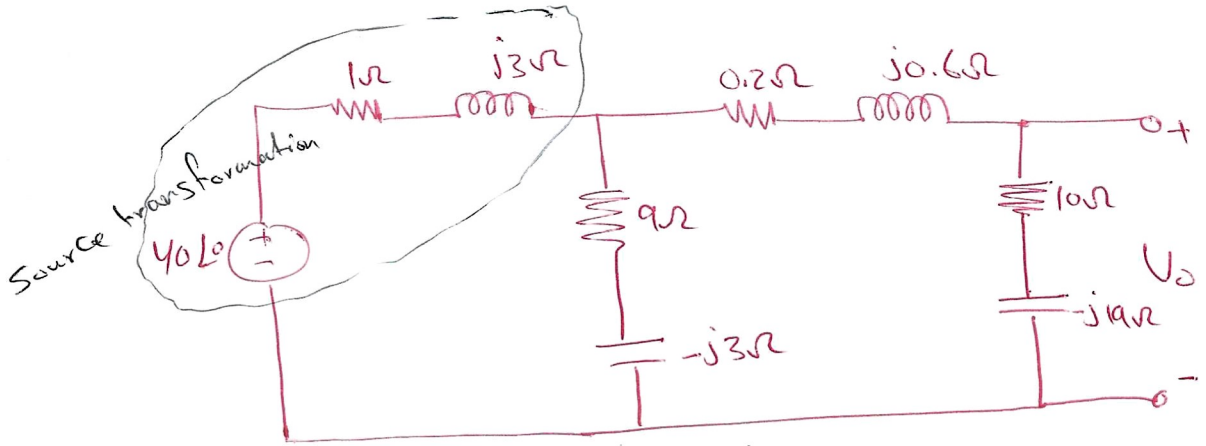
Example- use the concept of source transformation to find the phasor voltage  $V_o$  in the circuit shown



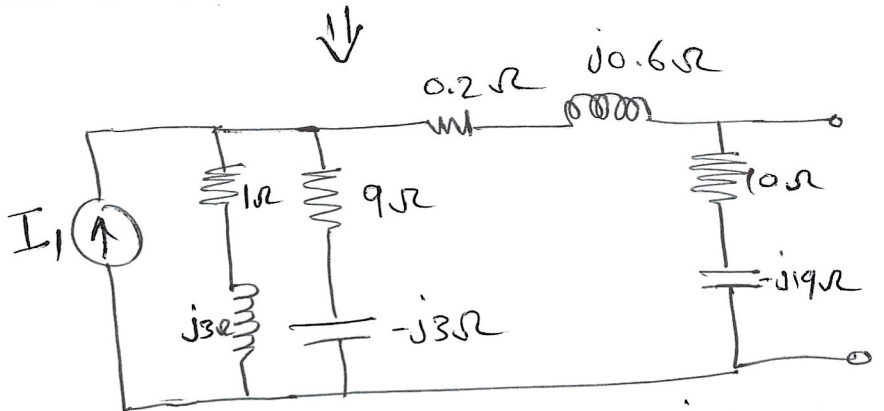
$$I_1 = \frac{40\angle 0}{1 + j3} = \frac{40\angle 0}{3.16 \angle 71.565} = 12.658 \angle -71.565 = 4 - j12$$



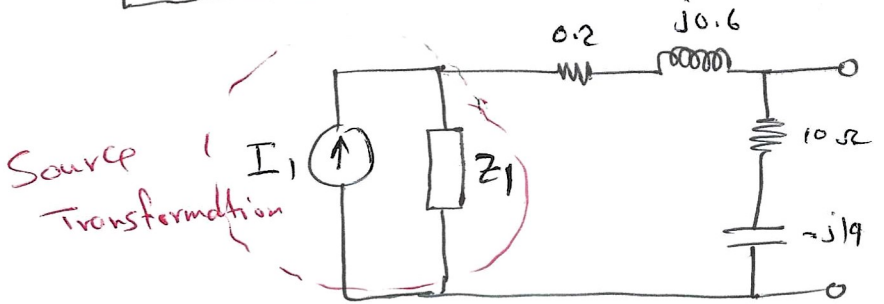
$$Z_1 = \frac{(1 + j3)(9 - j3)}{1 + 9 + j3 - j3} = \frac{9 - j3 + j27 + 9}{10} = \frac{18 + j24}{10} = 1.8 + j2.4$$


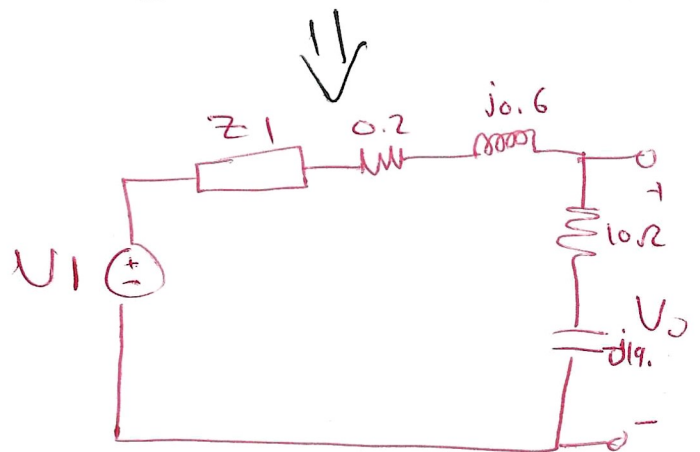
$$V_1 = I_1 Z_1 = (4 - j12)(1.8 + j2.4) = 36 - j12 \text{ V}$$


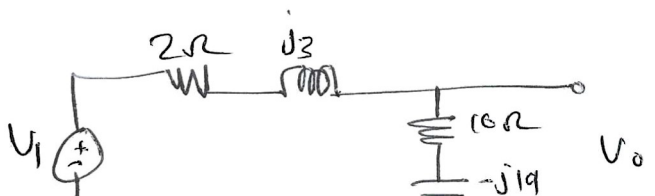
$$V_o = \frac{(10 - j19) V_1}{2 + j3 + 10 - j19}$$



STUDENTS14UB.com 8.84 V

Uploaded By: Mohammed Saada

# The power of superposition


Superposition is the only method to analyse a circuit of two sources with 2 different frequencies

For the circuit shown, find

$i(t)$

$$V_{s1}(t) = 100 \cos(10t)$$

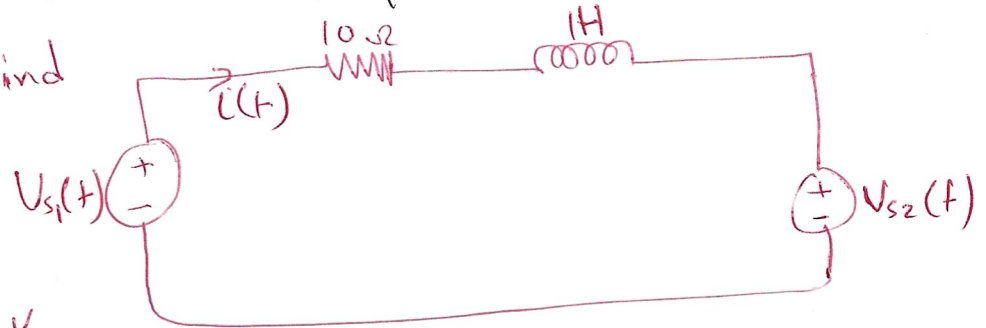
$$V_{s2}(t) = 50 \cos(20t - 10^\circ) \text{ V}$$




$$i(t) = i_1(t) + i_2(t)$$

① Let  $V_{s2}(t)$  off, and  $V_{s1}(t)$  on
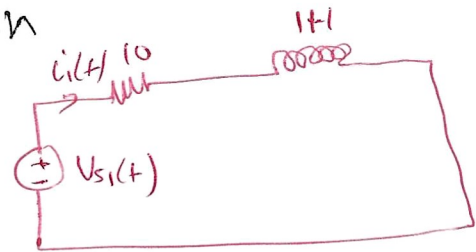
$$I_1 = \frac{100 \angle 0^\circ}{10 + j10} = 7.07 \angle -45^\circ \text{ A}$$


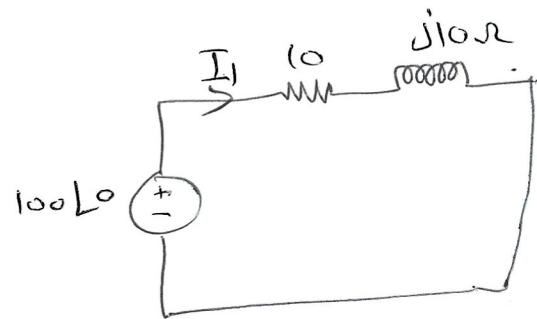
$$i_1(t) = 7.07 \cos(10t - 45^\circ) \text{ A}$$





② Let  $V_{s1}(t)$  off and  $V_{s2}(t)$  on

$$I_2 = \frac{-50 \angle -10^\circ}{10 + j20} = \frac{50 \angle 170^\circ}{22.36 \angle 63.43^\circ}$$

$$= 2.24 \angle 106.57^\circ \text{ A}$$
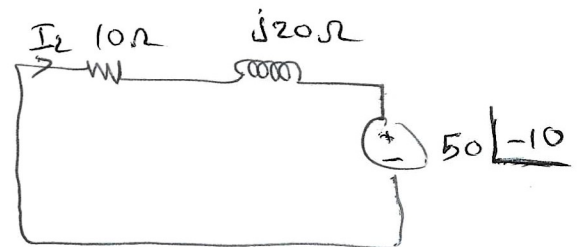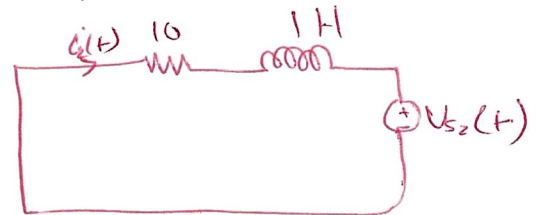
$$i_2(t) = 2.24 \cos(20t + 106.57^\circ)$$




$$\therefore i(t) = 7.07 \cos(10t - 45^\circ) + 2.24 \cos(20t + 106.57^\circ) \text{ A}$$

# Thevenin's and Norton's theorems

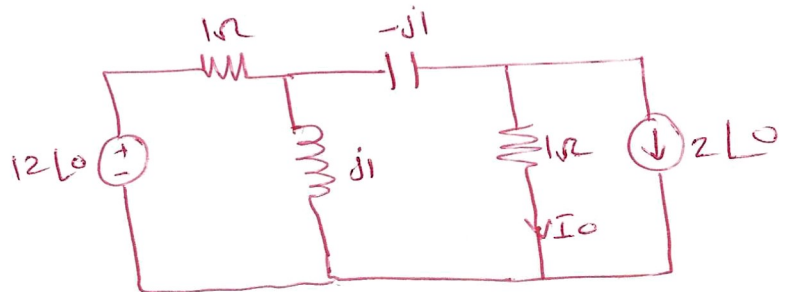Example 8- Find  $I_o$  using thevenin's theorem

$$I_o = \frac{V_{th}}{Z_{th} + 1\Omega}$$



1) To find  $V_{th}$

$$V_{th} + I_2(j1 - j1) - I_1(j1) = 0$$

$$\Rightarrow V_{th} = jI_1$$

$$I_2 = 2\angle 0 \text{ A}$$




For mesh ①

$$-12\angle 0 + \bar{I}_1(1+j) - \bar{I}_2(j) = 0$$

$$-12\angle 0 + \bar{I}_1(1+j) - 2\angle 0(j) = 0$$
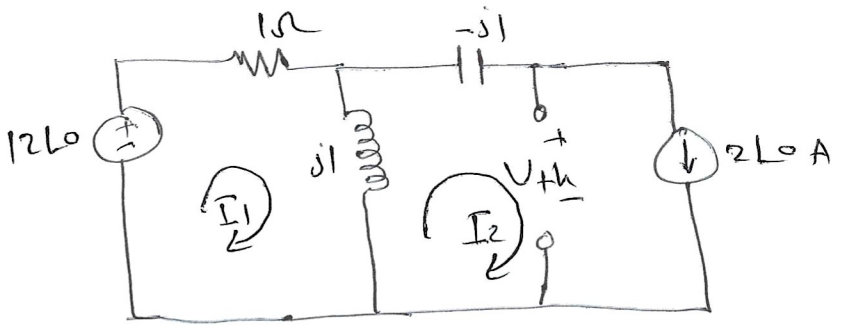
$$\therefore I_1 = \frac{12 + j2}{1+j} \text{ A}$$




$$\Rightarrow V_{th} = \left( \frac{-2 + j12}{1+j} \right) \text{ V} = 5 + j7$$

2) to find  $Z_{th}$ , set all the independent sources to zero

$$Z_{th} = -j1 + (1 \parallel j1)$$

$$= -j1 + \frac{1}{\frac{1}{1} + \frac{1}{j1}}$$

$$= \frac{1}{2} - j\frac{1}{2}$$

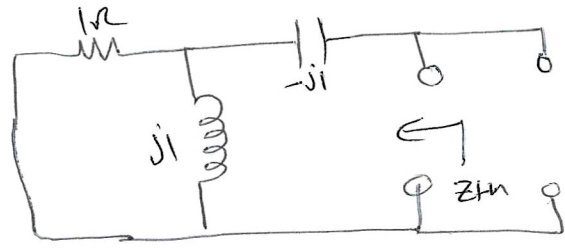


$$\therefore I_o = \frac{V_{th}}{Z_{th} + 1\Omega} = \frac{5 + j7}{1.5 - j\frac{1}{2}} = \left( \frac{8}{5} + j \frac{26}{5} \right) \text{ A}$$


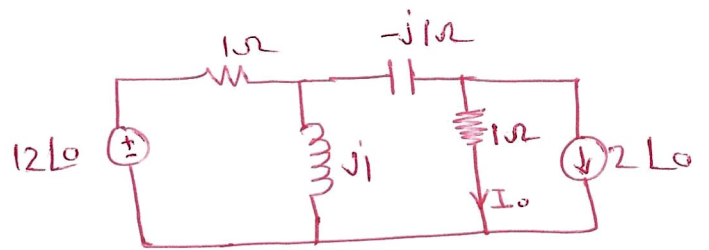
# Norton's theorem


Find  $\vec{I}_0$  using Norton's theorem



$$I_0 = I_N \frac{Z_N}{Z_N + 1\Omega}$$

$$I_N = I_2 - I_3$$

$$I_3 = 2 \angle 0 \text{ A}$$

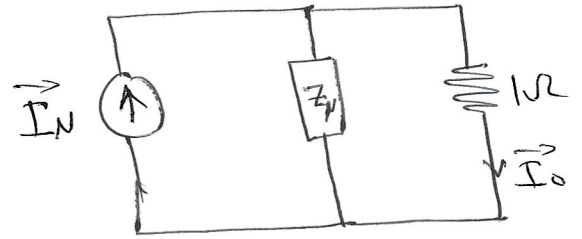

for mesh ①

$$-12 + I_1(1+j) - I_2(j) = 0$$

for mesh ②

$$I_2(j-j) - I_1(j) = 0$$

$$-jI_1 = 0$$

$$\therefore I_1 = 0$$


$$\Rightarrow I_2 = 12 \angle 90^\circ \text{ A}$$

$$\therefore I_N = I_2 - I_3 = -2 + j12$$

$$Z_N = Z_{th} = \frac{1}{2} - j\frac{1}{2}$$

$$I_0 = \frac{I_N Z_N}{Z_N + 1}$$


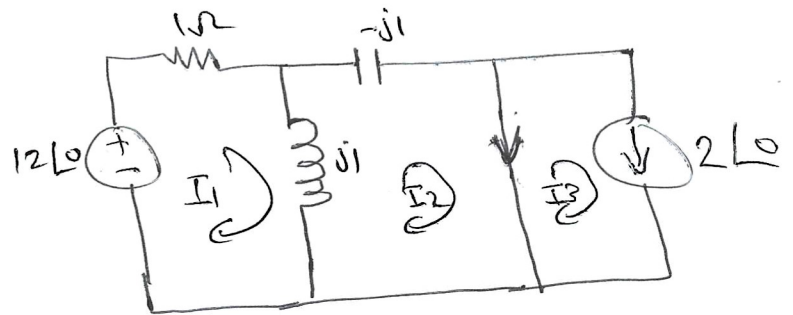
$$= \frac{8}{5} + j\frac{26}{5} \text{ A}$$



Example:- for the circuit shown, find  $V_o$  using Thevenin's theorem

$$V_o = \frac{1}{1 + Z_{th}} V_{th}$$

① To find  $V_{th}$

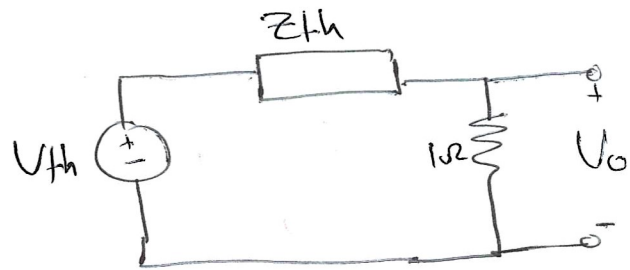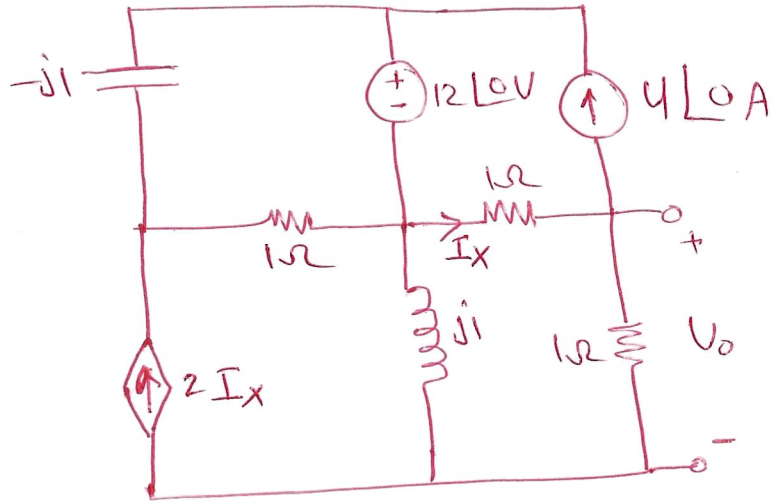

$$V_{th} = (-1\Omega)(I_x) + j1\Omega(2I_x)$$

$$I_x = 4L_0 \text{ A}$$

$$\therefore V_{th} = -4 + j8 \text{ A}$$

② to find  $Z_{th}$

$$Z_{th} = \frac{V_{th}}{I_{sc}}$$



$$I_{sc} = I_x - 4L_0$$

$$\vec{I}_x = \frac{\vec{V}_3}{1\Omega} = \vec{V}_3$$

node 1 and node 3 are supernodes

$$V_1 - V_3 = 12L_0$$
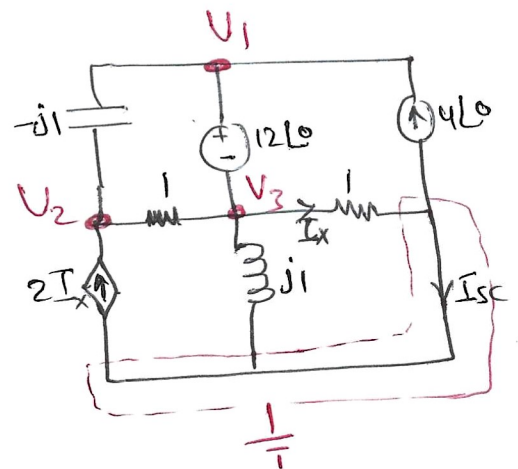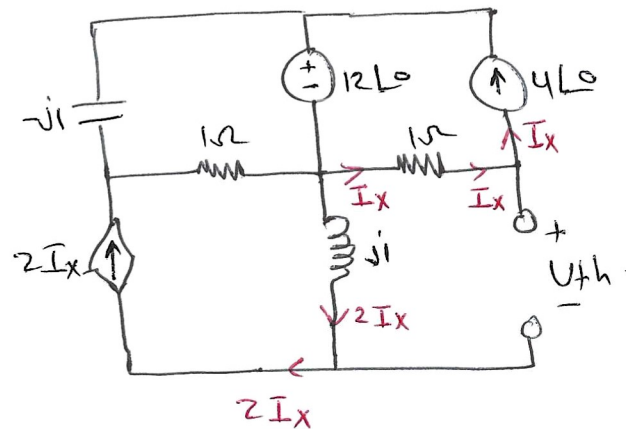
$$-4L_0 + \frac{V_1 - V_2}{1} + \frac{V_3 - V_2}{1} + \frac{V_3}{j} + \frac{V_3}{1} = 0$$



at node (2)

$$-2I_x + \frac{V_2 - V_1}{-j} + \frac{V_2 - V_3}{1} = 0$$

Solving for  $V_1$ ,  $V_2$  and  $V_3$

$$V_3 = \frac{4j}{1-j}$$

$$\therefore I_{sc} = - \left( \frac{8 + j4}{1 + j1} \right)$$

$$\therefore Z_{th} = \frac{V_{th}}{I_{sc}} = \underline{1-j} \quad \text{Capacitive}$$

$$\Rightarrow V_o = \frac{-4 + j8}{1 + 1 - j} = 4 \angle 143.13^\circ \text{ V}$$