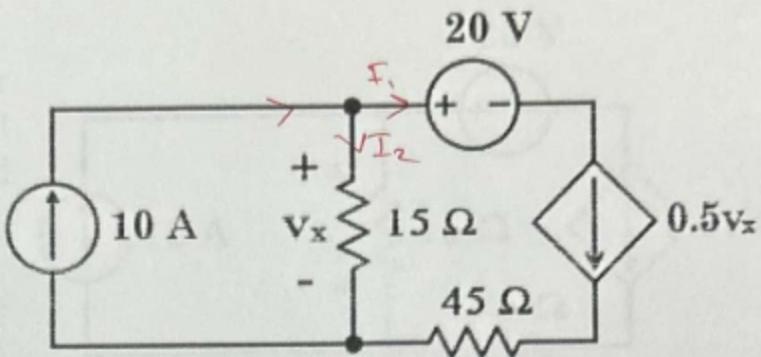


For the following circuit, calculate the power supplied or absorbed by the 10A current source, 20V voltage source and the 15ohm resistor.



Key Solution 8

KCL :

$$10 \text{ A} = I_1 + I_2$$

$$10 \text{ A} = \frac{v_x}{2} + \frac{v_x}{15}$$

$$10 = \frac{17}{30} v_x$$

$$v_x = \frac{300}{17} = 17.647 \text{ Volt}$$

$$\textcircled{1} \quad P_{10 \text{ A}} = -v_x I = -17.647 * 10 = -176.47 \text{ Watt supplied}$$

$$\textcircled{2} \quad P_{20 \text{ V}} = I_1 V = (0.5v_x)V = 0.5 * 17.647 * 20 \\ = 176.47 \text{ Watt Abs.}$$

$$\textcircled{3} \quad P_{15 \Omega} = \frac{v_x^2}{15} = \frac{(17.647)^2}{15} = 20.76 \text{ Watt Abs.}$$