

Q2: : For the LC circuit shown , if $L = 6 \text{ mH}$ and $C = 0.6 \mu\text{F}$. Then

- a) Find the drive frequency at which the maximum V_C will occur .
- b) What is the other name for this circuit ?

