


$v_s(t) = V_m \sin(\omega t)$

$\omega \rightarrow$ angular freq. (rad/sec)

$\omega = 2\pi f$

$f = \frac{\omega}{2\pi} \text{ (Hz)} = \frac{1}{T}$


$T =$ period in seconds

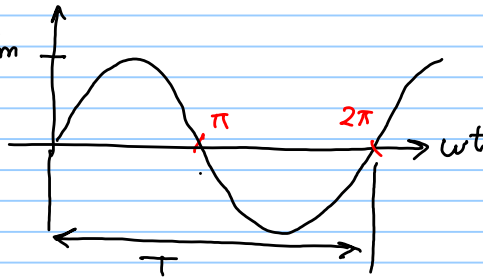

phase of sinusoids

lead lag

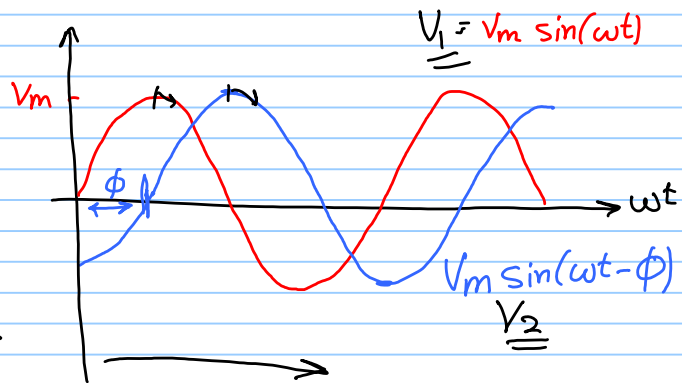$\rightarrow V_1$ leads V_2 by phase ϕ
 V_2 lags V_1 " " "
 V_1 & V_2 are out of phase



$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$
 where $C = \sqrt{A^2 + B^2}$ and $\theta = \tan^{-1} \frac{B}{A}$ * phasors

EX] $v_1(t) = 10 \sin(\omega t - 30^\circ)$, $v_2(t) = 15 \sin(\omega t + 10^\circ)$


v_2 leads v_1 by 40°

EX] $i_1(t) = 2 \sin(377t + 45^\circ)$, $i_2(t) = 0.5 \cos(377t + 10^\circ)$


$i_1(t) = 2 \cos(377t + 45^\circ - 90^\circ)$

$= 2 \cos(377t - 45^\circ)$

$i_2(t)$ leads $i_1(t)$ by 55°

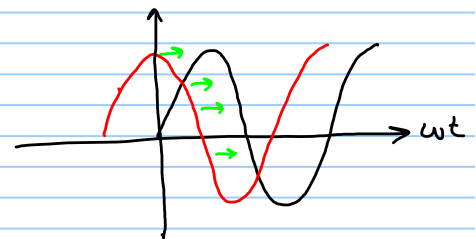

The sinusoidal response

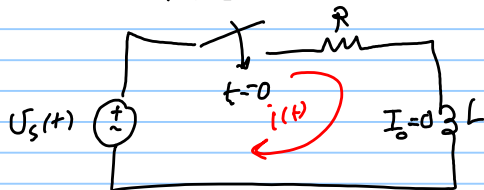

find $i(t)$ for $t > 0$

where $v_s(t) = V_m \cos(\omega t)$ V

KVL $-v_s(t) + R i(t) + L \frac{d}{dt} i(t) = 0$

$R i(t) + L \frac{d}{dt} i(t) = V_m \cos(\omega t)$

$$i(t) = A e^{-t/\tau} + i_p(t)$$

$$\rightarrow i_p(t) = \underline{I_1} \cos \omega t + \underline{I_2} \sin \omega t \quad (\text{see the notes})$$

$$= \frac{R V_m}{R^2 + (\omega L)^2} \cos \omega t + \frac{\omega L V_m}{R^2 + (\omega L)^2} \sin \omega t$$

$$= C \cos(\omega t - \Theta)$$

$$i_p(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

$$\rightarrow i(t) = A e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

transient part

steady state component



The steady state sol. is a sinusoidal function with the same freq. as the source signal

Find $i(t)$ for $t > 0$

$$\text{where } v_s(t) = V_m \cos(\omega t) \text{ V}$$

Complex Numbers (page 10-15) review

Rectangular form

$$Z = x + jy$$

Polar form

$$Z = |Z| \angle \Theta$$

Exponential form

$$Z = |Z| e^{j\Theta}$$

$$= |Z| (\cos \Theta + j \sin \Theta)$$

$$= |Z| \cos \Theta + j |Z| \sin \Theta$$

$$= x + jy$$

$$\rightarrow Z = 10 \angle 35^\circ \text{ (Polar)}$$


$$= 10 \cos 35^\circ + j 10 \sin 35^\circ$$

$$= x + jy$$

$$\rightarrow Z = 5 + j10 \text{ (Rectangular)}$$

$$= \sqrt{5^2 + 10^2} \angle \tan^{-1} \frac{10}{5}$$

Imag. axis

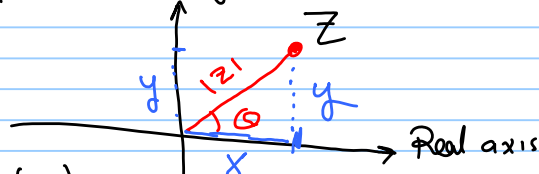

$$= \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x}$$

$$= |Z| \angle \Theta$$

Pol | rec |

$$\text{Pol } (5 + j10) = 11.1803 \angle 63.43^\circ \checkmark$$

Rec | Pol

Ex) $Z_1 = 4 + j3 = 5 \angle 36.9^\circ$

$Z_2 = 3 + j4 = 5 \angle 53.1^\circ$

$Z_1 + Z_2 = (4 + j3) + (3 + j4)$
 $= 7 + j7$

$Z_1 - Z_2 = (4 + j3) - (3 + j4)$
 $= 1 - j1$




$Z_1 \times Z_2 = (4 + j3)(3 + j4) = (5 \angle 36.9^\circ)(5 \angle 53.1^\circ)$
 $= 12 + j16 + j9 - 12 = j25 = 25 \angle 90^\circ$
 $= 25 \angle 36.9^\circ + 53.1^\circ = 25 \angle 90^\circ$

$\frac{Z_1}{Z_2} = \frac{5 \angle 36.9^\circ}{5 \angle 53.1^\circ} = 1 \angle 36.9^\circ - 53.1^\circ = 1 \angle -16.2^\circ$


$= \frac{4 + j3}{3 + j4} \cdot \frac{3 - j4}{3 - j4}$ } try it

page 15

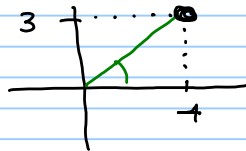$Z_1 = 4 + j3$
 $= \sqrt{4^2 + 3^2} \angle \tan^{-1} \frac{3}{4}$
 $= 5 \angle 36.9^\circ$



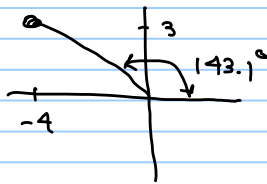
$Z_2 = -4 + j3$
 $= 5 \angle 143.1^\circ$



$Z_4 = 4 - j3$
 $= 5 \angle -36.9^\circ$



phasors

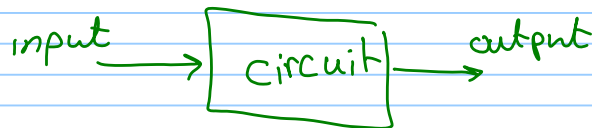

$V_m \cos(\omega t + \theta)$


$V_m \sin(\omega t + \theta)$

$j V_m \sin(\omega t + \theta)$

$I_m \cos(\omega t + \phi)$

$I_m \sin(\omega t + \phi)$

$j I_m \sin(\omega t + \phi)$

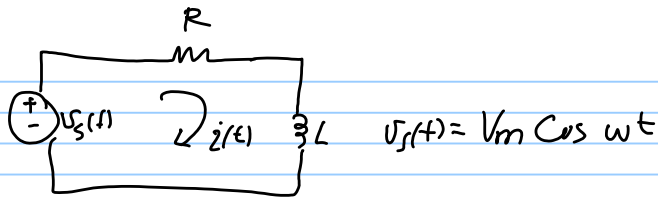

$$i(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

Phasor $v(t) = V_m \cos(\omega t + \theta_v)$



phasor Form $\vec{V} = V_m \angle \theta_v$

$i(t) = 6 \cos(50t - 40^\circ) \text{ A}$
phasor Form $\vec{I} = 6 \angle -40^\circ \text{ A}$

our reference is **cosine**

* any source, must be written in cos, if it was written in sin then \rightarrow Convert to cos

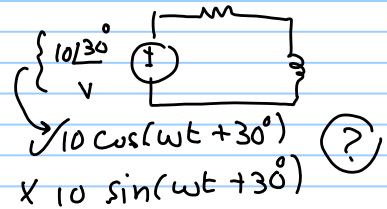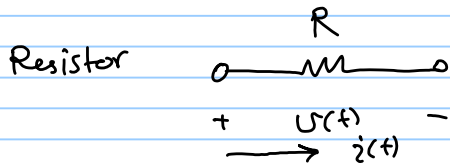* Phasor relationships for circuit elements




if $i(t) = I_m \cos(\omega t + \theta_i)$

then, $v(t) = R i(t)$

$$= R I_m \cos(\omega t + \theta_i)$$



$$\vec{V} = R I_m \angle \theta_i \iff \vec{I} = I_m \angle \theta_i$$

$$\vec{V} = R \vec{I}$$

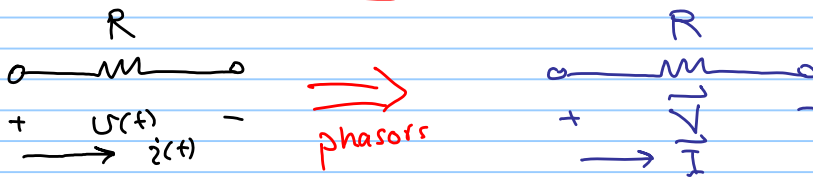


Note There is no phase shift between the current & voltage across R!

$v(t)$ & $i(t)$ are in phase

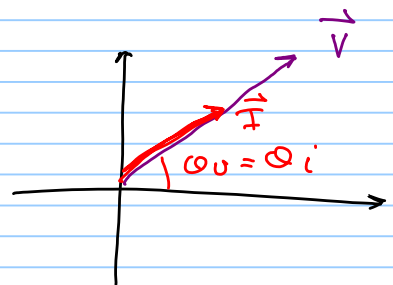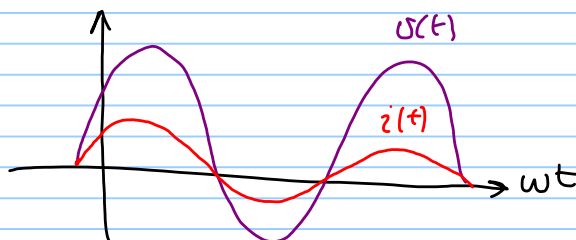

V-I relationship for inductors

$$i(t) = I_m \cos(\omega t + \theta_i)$$

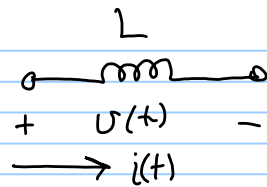

$$\begin{aligned} \text{then } V(t) &= L \frac{d}{dt} i(t) \\ &= L I_m \frac{d}{dt} [\cos(\omega t + \theta_i)] \\ &= -\omega L I_m \sin(\omega t + \theta_i) \end{aligned}$$

But \rightarrow our ref. is cosine


$$\therefore V(t) = -\omega L I_m \cos(\omega t + \theta_i - 90^\circ)$$

The phasor representation of the voltage is

$$\begin{aligned} \vec{V} &= -\omega L I_m e^{j(\theta_i - 90^\circ)} \\ &= -\omega L I_m e^{j\theta_i} e^{-j90^\circ} \\ &= j\omega L I_m e^{j\theta_i} \end{aligned}$$



$$\begin{aligned} e^{-j90^\circ} &= \cos(-90^\circ) + j\sin(-90^\circ) \\ &= 0 - j \\ &= -j \end{aligned}$$

$$\boxed{\vec{V} = j\omega L \vec{I}}$$

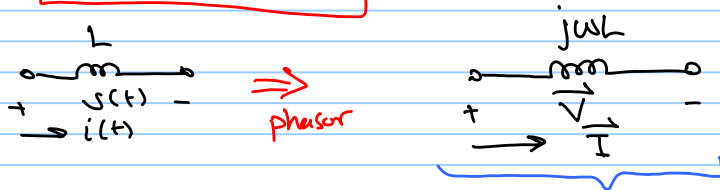


$$\begin{aligned} \vec{V} &= j\omega L \vec{I} \\ &= (\omega L \angle 90^\circ) (I_m \angle \theta_i) \\ &= \omega L I_m \angle \theta_i + 90^\circ \end{aligned}$$
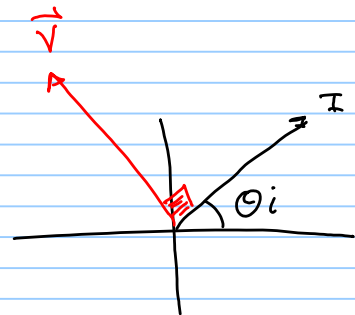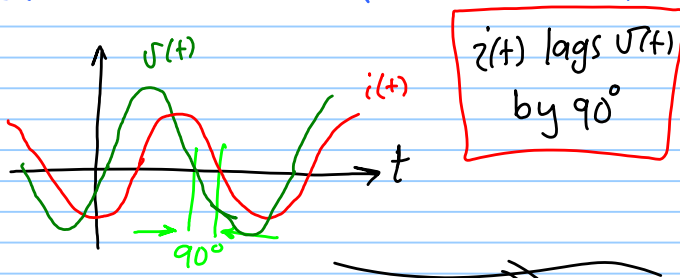
$$v(t) = \omega L I_m \cos(\omega t + \theta_i + 90^\circ)$$



V-I relationships for a capacitor

$$i(t) = C \frac{d}{dt} v(t)$$

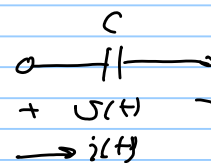


$$\begin{aligned} \text{assume } v(t) &= V_m \cos(\omega t + \theta_v) \\ i(t) &= C V_m [-\omega \sin(\omega t + \theta_v)] \\ &= -\omega C V_m \cos(\omega t + \theta_v - 90^\circ) \\ \vec{I} &= -\omega C V_m e^{j(\theta_v - 90^\circ)} \end{aligned}$$

$$\vec{I} = -\omega c V_m e^{j\omega t} e^{-j90^\circ}$$

$$= j\omega c V_m e^{j\omega t}$$

$$\vec{I} = j\omega c \vec{V}$$

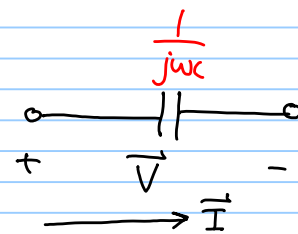

$$j\omega c = \frac{\vec{I}}{\vec{V}} \quad !!$$








$$\Rightarrow \frac{\vec{V}}{\vec{I}} = \frac{1}{j\omega c} = -j \frac{1}{\omega c}$$

$$\vec{V} = \frac{1}{j\omega c} \vec{I} = (-j \frac{1}{\omega c}) (\text{Im} \angle \Theta_i)$$

$$= (\frac{1}{\omega c} \angle -90^\circ) (\text{Im} \angle \Theta_i)$$

$$\vec{V} = \frac{\text{Im}}{\omega c} \angle \Theta_i - 90^\circ$$

i leads v by 90°
 v lags i by 90°

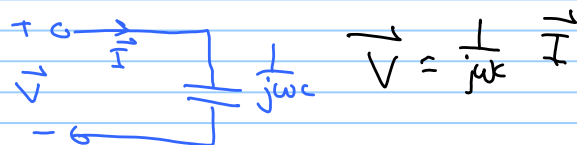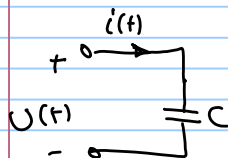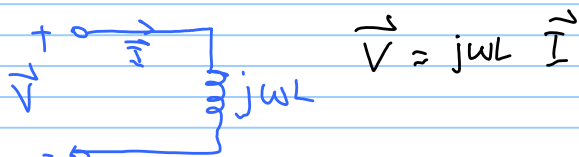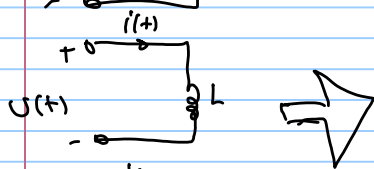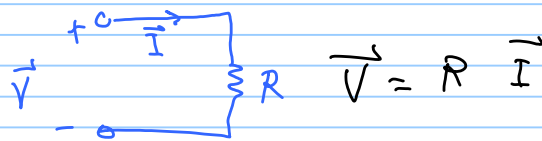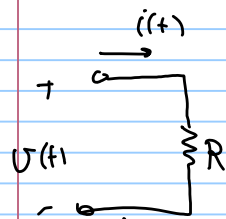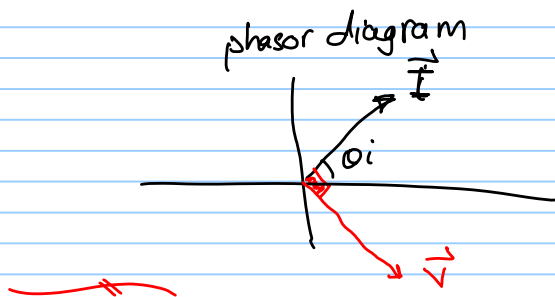

$$\vec{V} = Z(j\omega) \vec{I}$$

Impedance & admittance

$$Z(j\omega) = \frac{\vec{V}}{\vec{I}} \quad \text{Impedance } (\Omega)$$

$$\vec{V} = Z \vec{I}$$

$$Y(j\omega) = \frac{\vec{I}}{\vec{V}} \quad \text{Admittance } (\mathcal{S})$$