

# Digital Systems

## Section 2

### Verilog (Combinational)



☯ In the world of programming, tasks can be executed in two ways:

- 🔹 **Serial Programming:** Operations are executed one after another, step-by-step, in a sequential order. This is common in **software programming**, where the focus is on algorithms and data manipulation (e.g., Python, C++).
- 🔹 **Parallel Programming:** Multiple operations happen simultaneously. This is essential in **hardware programming**, where circuits can handle multiple tasks at the same time (e.g., multiple logic gates working concurrently).

★ **Hardware programming** languages like **Verilog** and **VHDL** help describe how digital circuits perform these parallel operations efficiently. This shift from sequential software logic to parallel hardware logic is key to understanding HDLs.



## 🌀 What is Hardware Programming?

- 📌 Describes the behavior and structure of digital circuits.

## 🌀 Key Languages:

- 📌 VHDL: Strongly typed, verbose, suited for large, complex systems.
- 📌 **Verilog**: Compact syntax, simpler, often used in commercial applications.

## 🌀 Difference from Software Programming:

- 📌 HDLs describe hardware **behavior**, not algorithms.
- 📌 Parallel operations are at the core, unlike the sequential nature of traditional software.



## 🌀 What is Verilog?

- 📌 A hardware description language used to **model** digital circuits.
- 📌 Popular in both academia and industry for **designing** FPGAs and ASICs.

## 🌀 Why Use Verilog?

- 📌 **Compact** and easy to learn.
- 📌 Allows testing and simulating circuit designs before physical implementation.

## 🌀 Key Concepts Covered:

- 📌 Modules, gates, and behavioral/structural modeling.

**Verilog** ≡ **Verifying Logic**

🌀 A technique used to **verify** the **behavior** and **functionality** of digital circuits before physical implementation.

🌀 **Purpose:**

- 🕒 Identifies **errors early** in the design process.
- 🕒 Ensures the circuit works **as expected** under different input conditions.

🌀 **Applications in Hardware Design:**

- 🕒 Used extensively with Verilog and VHDL models.
- 🕒 **Simulates** gate-level designs, timing constraints, and functional behavior.
- 🕒 **Timing Diagrams:** Visual representation of the state of a digital signal over time, illustrating how signals interact within the circuit.
- 🕒 **Test Bench:** A simulation environment where input signals are applied to the design under test (DUT) to verify its operation.

🌀 **Tools:**

- 🕒 ModelSim, Cadence, **Quartus II**

🌀 **Key Benefit:**

- 🕒 Saves time and cost by avoiding rework during fabrication



## 🌀 Overview:

- 🕒 Logic synthesis is similar to **translating** a program.
- 🕒 The output of logic synthesis is a **digital circuit**.

## 🌀 Key Concepts:

- 🕒 A digital circuit modeled in Verilog can be translated into a list of components and their interconnections, known as a **netlist**.
- 🕒 Synthesis can be used to **fabricate** an integrated circuit.
- 🕒 Synthesis can also target a Field Programmable Gate Array (**FPGA**).

## 🌀 FPGA Configuration:

- 🕒 An FPGA chip can be **configured** to **implement** a digital circuit.
- 🕒 The digital circuit can be **modified** by **reconfiguring** the FPGA.

## 🌀 Automation in Design:

- 🕒 Logic simulation and synthesis are **automated** processes.
- 🕒 This is accomplished using special software known as Electronic Design Automation (**EDA**) tools.




- ⌘ A **digital circuit** is described in Verilog as a **set of modules**
- ⌘ A **module** is the **design entity** in Verilog
- ⌘ A module is declared using the **module** keyword
- ⌘ A module is terminated using the **endmodule** keyword
- ⌘ Each module has a **name** and a list of **input** and **output ports**
- ⌘ The module is described by a **group** of **statements**
- ⌘ Statements can describe the module's **structure** or **behavior**

**Example:**

```
module simple_circuit(input A, B, C, output x, y);  
  wire w; Optional  
  and g1(w, A, B);  
  not g2(y, C);  
  or g3(x, w, y);  
endmodule
```

Order is NOT important

 

- ☪ The **input** keyword **defines** the input **ports**: A, B, C
- ☪ The **output** keyword **defines** the output **ports**: x, y
- ☪ The **wire** keyword **defines** an **internal connection**: w
- ☪ The **structure** of simple\_circuit is defined by three gates: and, not, or
- ☪ Each gate has an **optional name**, followed by the gate **output** then **inputs**



- 🌀 **Keywords:** have special meaning in Verilog
  - ★ Many keywords: **module, input, output, wire, and, or**, etc.
  - ★ Keywords **can NOT** be used as **identifiers**
- 🌀 **Identifiers:** are user-defined names for modules, ports, etc.
  - ★ Verilog is **case-sensitive: A** and **a** are **different** names
- 🌀 **Comments:** can be specified in two ways (similar to C)
  - ★ **Single-line** comments begin with **//** and terminate at end of line
  - ★ **Multi-line** comments are enclosed between **/\* and \*/**
- 🌀 **White space:** space, tab, newline can be used **freely** in Verilog
- 🌀 **Operators:** operate on variables (similar to C: **~ & | ^ + -** etc.)

- ⌘ Basic gates: **and, nand, or, nor, xor, xnor, not, buf**
- ⌘ Verilog define these gates as **keywords**
- ⌘ Each gate has an **optional** name
- ⌘ Each gate has an **output (listed first)** and one or more **inputs**
- ⌘ The **not** and **buf** gates can have **only one** input (**Unary**)

### Examples:

```
and g1(x,a,b);           // 2-input and gate named g1
or  g2(y,a,b,c);        // 3-input or gate named g2
nor g3(z,a,b,c,d);      // 4-input nor gate named g3
```

```
module Half_Adder(x, y, C, S);
```

```
input x, y;
```

```
output S, C;
```


```
and (C, x, y);
```

```
xor (S, x, y);
```


```
endmodule
```

**Alternative** way to  
define **Input/Output**

<b>x</b>	<b>y</b>	<b>C</b>	<b>S</b>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 
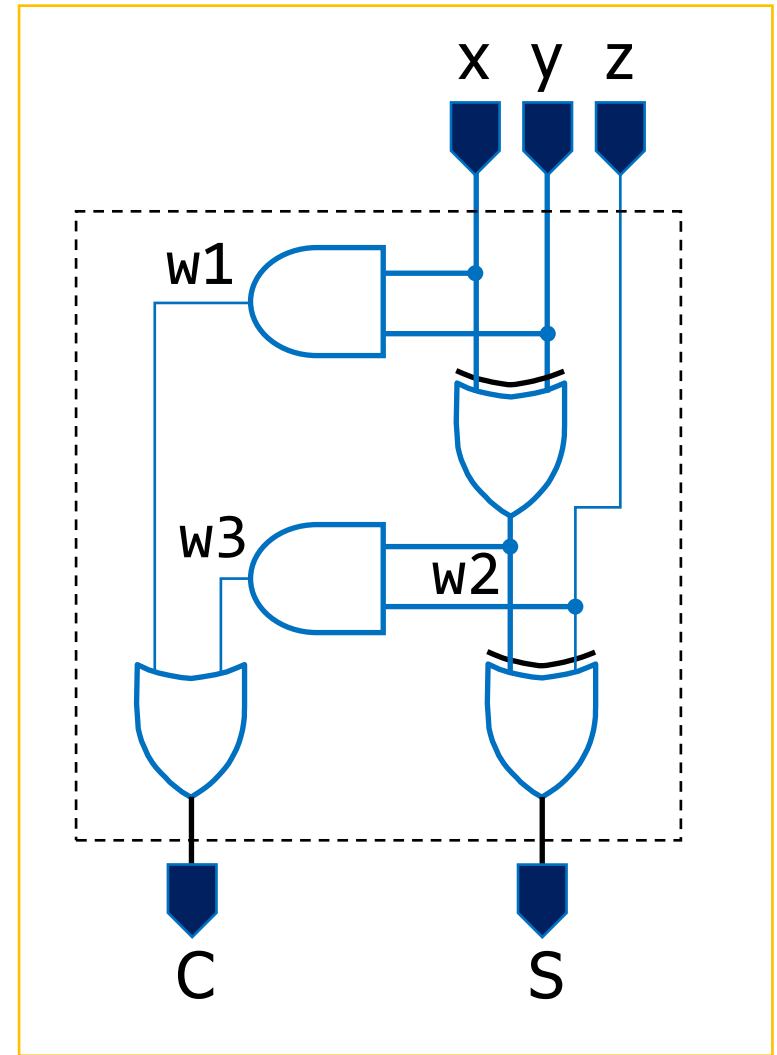
```
module Full_Adder(input x, y, z, output C, S);  
  wire w1, w2, w3;  
  and (w1, x, y);  
  xor (w2, x, y);  
  and (w3, w2, z);  
  xor (S, w2, z);  
  or (C, w1, w3);  
endmodule
```



- When simulating Verilog modules, it is sometime necessary to specify the **delay** of gates using the **#** symbol
- The **timescale** directive specifies the time **unit** and **precision**
- timescale** is also used as a simulator option

**timescale** 1ns/100ps

Time unit = 1ns =  $10^{-9}$  sec

Precision = 100ps = 0.1ns

```
module Half_Adder(input a, b, output cout, sum);  
  and #2 (cout, a, b);           // gate delay = 2ns  
  xor #3 (sum, a, b);          // gate delay = 3ns  
endmodule
```



```
module Full_Adder(input x, y, z, output C, S);  
    wire w1, w2, w3;  
    and #2 (w1, x, y);  
    xor #3 (w2, x, y);  
    and #2 (w3, w2, z);  
    xor #3 (S, w2, z);  
    or #2 (C, w1, w3);  
endmodule
```

- 🌀 The **assign** statement defines **continuous** assignment
- 🌀 Syntax: ***assign name = expression;***
- 🌀 Assigns expression value to name (output port or wire)

### Examples:

```
assign x = a&b | c&~d;           // x = ab + cd'  
assign y = (a | b) & ~c;        // y = (a+b)c'  
assign z = ~(a | b | c);        // z = (a+b+c)'  
assign sum = (a^b) ^ c;         // sum = (a ⊕ b) ⊕ c
```

- ★ Verilog uses the **bit** operators:  $\sim$  (not),  $\&$  (and),  $|$  (or),  $\wedge$  (xor)
- ★ Operator **precedence**: (parentheses),  $\sim$ ,  $\&$ ,  $|$ ,  $\wedge$

🌀 Syntax: **assign #delay name = expression;**

### Example:

```
module Full_Adder (input x, y, z, output C, S);  
  assign #6 S = (x^y)^z;           // delay = 6  
  assign #7 C = x&y | (x^y)&z;     // delay = 7  
endmodule
```

- ★ The **order** of the assign statements does **NOT matter**
- ★ They are **sensitive** to **inputs** (x, y, z) that appear in the expressions
- ★ Any **change** in value of the input ports (x, y, z) will **re-evaluate** the outputs S and C of the assign statements



☯ Verilog has **two** major data types

- 1) **Net** data types: are **connections** between parts of a design
- 2) **Variable** data types: can **store** data values

☯ The **wire** is a **net** data type

- ☰ A wire **cannot store** a value
- ☰ Its value is determined by its driver, such as a gate, a module output, or continuous assignment

☯ The **reg** is a **variable** data type

- ☰ **Can store** a value from one assignment to the next
- ☰ Used only in procedural blocks, such as the **initial block**



- ⌘ The **initial** statement is a **procedural block** of **statements**
- ⌘ The **body** of the initial statement surrounded by **begin-end** is **sequential**
- ⌘ **Procedural** assignments are used **inside** the **initial** block
- ⌘ Procedural assignment statements are **executed in sequence**
- ⌘ Syntax: **#delay variable = expression;**
- ⌘ Procedural assignment statements **can be delayed**
- ⌘ The optional **#delay** indicates that the variable (of reg type) should be **updated after the time delay**



- ⌚ In order to **simulate** a circuit, it is necessary to **apply inputs** to the circuit for the simulator to **generate** an **output response**
- ⌚ A **test bench** is written to **verify** the **correctness** of a design
- ⌚ A **test bench** is written as a Verilog **module with no ports**
- ⌚ It **instantiates** the module that should be tested
- ⌚ It **provides inputs** to the module that should be tested
- ⌚ **Test benches** can be **complex and lengthy**, depending on the complexity of the design

**Example:**

```
module Test_Full_Adder;                                // No need for Ports
  reg x, y, z;                                         // reg (variable) inputs
  wire S, C;                                           // wire (net) outputs


// Instantiate the module to be tested
Full_Adder FA (x, y, z, C, S);

initial begin                                         // initial block
  x=0; y=0; z=0;                                       // at t=0 time units
  #20 x=1; y=1;                                       // at t=20 time units
  #20 x=0; y=0; z=1;                                   // at t=40 time units
  #20 x=1; z=0;                                       // at t=60 time units
  #20 $finish;                                        // at t=80 finish simulation
end                                                    // end of initial block

endmodule
```


**Change the Inputs  
&  
Monitor the Effect on Outputs**

## Simulator Run:

 

- ✦ Examine the **waveforms** to verify the correctness of your design
- ✦ At  $t = 0$  ns, the values of **cout** and **sum** are **unknown** (shown in red)
- ✦ The **cout** and **sum** signals are **delayed** by **7ns** and **6ns**, respectively

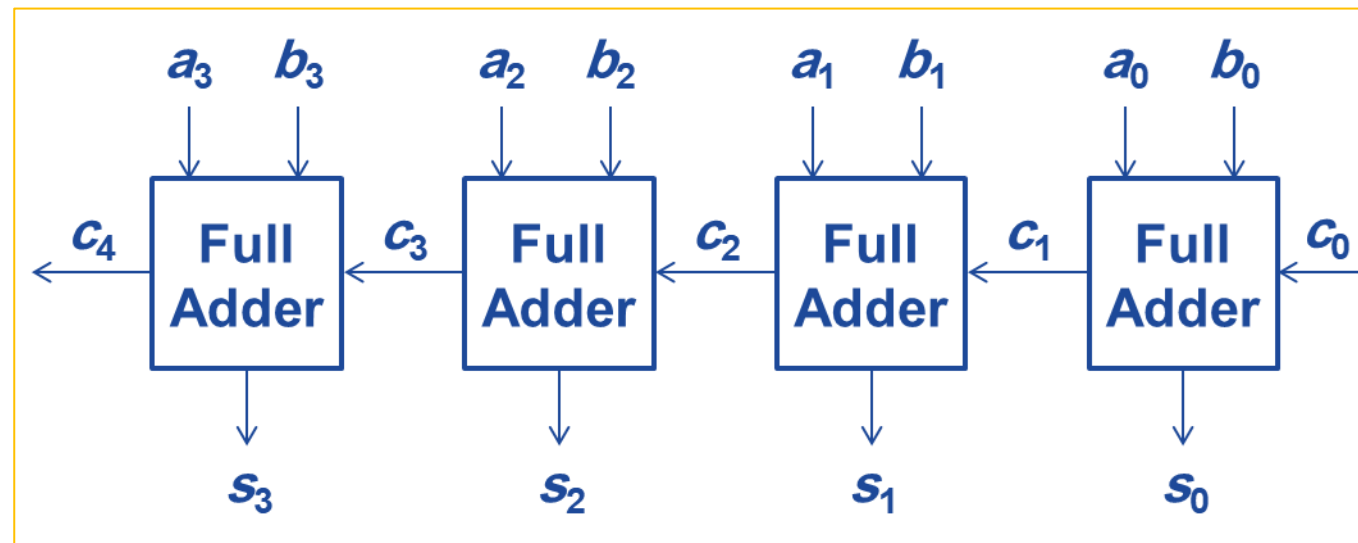- Uses **identical copies** of a full adder to **build** a **large adder**
- Simple to implement: the cell (**iterative block**) is a full adder
- Carry-out** of cell  **$i$**  becomes **carry-in** to cell ( **$i + 1$** )
- Can be **extended** to add **any number of bits**





- ⌘ Module **declarations** are like **templates**
- ⌘ Module **instantiation** is like **creating an object**
- ⌘ Modules are **instantiated inside** other modules at different levels
- ⌘ The **top-level** module does **NOT** require **instantiation**
- ⌘ Module instantiation **defines** the **structure** of a digital design
- ⌘ It **produces** module **instances** at different levels
- ⌘ The **ports** of a module **instance** must **match** those **declared**
- ⌘ The **matching** of the **ports** can be done by **name** or by **position**



```
module Adder4 (input a0, a1, a2, a3, b0, b1, b2, b3, c0, output s0, s1, s2, s3, c4);  
    wire c1, c2, c3;      // Internal wires for the carries  
    // Instantiate Four Full Adders: FA0, FA1, FA2, FA3  
    // The ports are matched by position  
    Full_Adder FA0 (a0, b0, c0, c1, s0);  
    Full_Adder FA1 (a1, b1, c1, c2, s1);  
    Full_Adder FA2 (a2, b2, c2, c3, s2);  
    Full_Adder FA3 (a3, b3, c3, c4, s3);  
    // Can also match the ports by name  
    // Full Adder FA0 (.a(a0), .b(b0), .c(c0), .cout(c1), .sum(s0));  
endmodule
```



```
module Adder4_TestBench;                                // No Ports
  reg a0, a1, a2, a3;                                   // variable inputs
  reg b0, b1, b2, b3, cin;                             // variable inputs
  wire s0, s1, s2, s3, cout;                          // net outputs
  // Instantiate the module to be tested
  Adder4 Add4 (a0,a1,a2,a3, b0,b1,b2,b3, cin, s0,s1,s2,s3, cout);
  initial begin                                       // initial block
    a0=0;a1=0;a2=0;a3=0;                               // at t=0
    b0=0;b1=0;b2=0;b3=0;cin=0;                       // at t=0
    #100 a1=1;a3=1;b2=1;b3=1;                         // at t=100
    #100 a0=1;a1=0;b1=1;b2=0;                        // at t=200
    #100 a2=1;a3=0;cin=1;                            // at t=300
    #100 $finish;                                    // at t=400 finish simulation
  end                                                // end of initial block
endmodule
```



- ☉ Verilog **Value Set** consists of **four** basic values:
  - a) 0 – represents a logic **zero**, or **false** condition
  - b) 1 – represents a logic **one**, or **true** condition
  - c) X – represents an **unknown** logic value
  - d) Z – represents a **high-impedance** value
  
- ☉ x or X represents an unknown or **uninitialized** value
  
- ☉ z or Z represents the output of a **disabled** tri-state buffer



- ☯ **Recall:** Verilog has **two** major **data types**:
  - ☉ **Net** data types: are **connections** between parts of a design
  - ☉ **Variable** data types: can **store** data values
- ☯ The **wire** is a **net** data type (**physical** connection)
  - ☉ A wire can **NOT** store the value of a procedural assignment
  - ☉ However, a wire can be **driven by continuous assignment**
- ☯ The **reg** is a **variable** data type
  - ☉ Can **store** the value of a procedural assignment
  - ☉ However, can **NOT** be driven by continuous assignment
- ☯ Other **variable** types: **integer, time, real, and realtime**

## 🌀 Four levels of modeling circuits in Verilog

### 1) Gate-Level Modeling

- 🕒 Lowest-level modeling using Verilog **primitive gates**

### 2) Structural Modeling using module **instantiation**

- 🕒 Describes the structure of a circuit with modules at different levels

### 3) Dataflow Modeling using **concurrent assign** statements

- 🕒 Describes the **flow** of data between **input and output**

### 4) Behavioral Modeling using **procedural** blocks and statements

- 🕒 Describes what the **circuit does** at a higher level of **abstraction**

🌀 Can also **mix** different models in the same design

### 🌀 Dataflow Modeling using **Continuous Assignment**

- ⦿ Used mostly for **describing** Boolean equations and combinational logic
- ⦿ Verilog provides a **rich set of operators**
- ⦿ Can describe: **adders, comparators, multiplexers**, etc.
- ⦿ Synthesis tool can **map a dataflow** model into a **target** technology

### 🌀 Behavioral Modeling using **Procedural Blocks and Statements**

- ⦿ Describes what the circuit does at a **functional and algorithmic** level
- ⦿ Encourages designers to **rapidly** create a **prototype**
- ⦿ Can be **verified easily** with a simulator
- ⦿ **Some** procedural statements are **synthesizable** (Others are NOT)



- ⌘ The **assign** statement defines **continuous** assignment
  - ⦿ Syntax: **assign** [#delay] **net\_name** = **expression**;
  - ⦿ Assigns expression value to **net\_name** (**wire or output port**)
  - ⦿ The **optional** #delay specifies the delay of the assignment
  
- ⌘ **Continuous** assignment statements are **concurrent**
- ⌘ Can **appear in any order** inside a module
- ⌘ Continuous assignment can **model combinational** circuits
- ⌘ Describes the flow of data between input and output

### Bitwise Operators

$\sim a$  Bitwise NOT

$a \& b$  Bitwise AND

$a | b$  Bitwise OR

$a \wedge b$  Bitwise XOR

$a \sim \wedge b$  Bitwise XNOR

$a \wedge \sim b$  Same as  $\sim \wedge$

### Arithmetic Operators

$a + b$  ADD

$a - b$  Subtract

$-a$  Negate

$a * b$  Multiply

$a / b$  Divide

$a \% b$  Remainder

### Relational Operators

$a == b$  Equality

$a != b$  Inequality

$a < b$  Less than

$a > b$  Greater than

$a <= b$  Less or equal

$a >= b$  Greater or equal

### Reduction Operators

$\&a$  AND all bits

$|a$  OR all bits

$\wedge a$  XOR all bits

$\sim \&a$  NAND all bits

$\sim |a$  NOR all bits

$\sim \wedge a$  XNOR all bits

### Shift Operators

$a \ll n$  Shift Left

$a \gg n$  Shift Right

### Miscellaneous Operators

$sel?a:b$  Conditional

$\{a, b\}$  Concatenate

Reduction operators produce a 1-bit result

Relational operators produce a 1-bit result

$\{a, b\}$  concatenates the bits of **a** and **b**

- ☉ A **Bit Vector** is **multi-bit** declaration that uses a single name
- ☉ A Bit Vector is specified as a **Range** [**msb:lsb**]
  - ☉ **msb** → *most-significant bit* , **lsb** → *least-significant bit*
- ☉ **Bit select**: **W[1]** is bit **1** of **W**
- ☉ **Part select**: **A[11:8]** is a **4-bit** select of **A** with range [**11:8**]
- ☉ The **part select range** must be **consistent** with vector declaration

### Example:

```
input  [15:0] A;           // A is a 16-bit input vector
output [0:15] B;          // Bit 0 is most-significant bit
wire   [3:0] W;           // Bit 3 is most-significant bit
```



**module** Reduce

```
( input [3:0] A, B, output X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are 1-bit outputs
```

```
// X = A[3] | A[2] | A[1] | A[0];
```

```
assign X = |A;
```

```
// Y = B[3] & B[2] & B[1] & B[0];
```

```
assign Y = &B;
```

```
// Z = X & (B[3] ^ B[2] ^ B[1] ^ B[0]);
```

```
assign Z = X & (^B);
```

```
endmodule
```

**module Concatenate**

```
( input [7:0] A, B, output [7:0] X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are output vectors
```

```
// X = A is right-shifted 3 bits using { } operator
```

```
assign X = {3'b000, A[7:3]};
```

```
// Y = A is right-rotated 3 bits using { } operator
```

```
assign Y = {A[2:0], A[7:3]};
```

```
// Z = selecting and concatenating bits of A and B
```

```
assign Z = {A[5:4], B[6:3], A[1:0]};
```

```
endmodule
```

☪ Syntax: [ size ][ 'base ] value

- ☉ **size** (**optional**) is the **number** of bits in the value
- ☉ **'base** can be: 'b(binary), 'o(octal), 'd(decimal), or 'h(hex)
- ☉ **value** can be in binary, octal, decimal, or hexadecimal
- ☉ If the **'base** is **NOT** specified then the **default** is **decimal** value

☪ **Examples:**

- ☞ 8'b1011\_1101 (8-bit **binary**),      'hA3F0 (16-bit hexadecimal)
- ☞ 16'o56377 (16-bit **octal**),      32'd999 (32-bit decimal)

☪ The underscore \_ can be used to enhance **readability** of value

☪ When **size** is **fewer** bits than **value**, **upper** bits are **truncated**

```
// Input ports: 16-bit a and b, 1-bit cin (carry input)
// Output ports: 16-bit sum, 1-bit cout (carry output)
```

```
module Adder_16 (input [15:0] a, b, input cin, output [15:0] sum, output cout);
```


```
    wire [16:0] c;           // carry bits
    assign c[0] = cin;      // carry input
    assign cout = c[16];    // carry output
```

```
// Instantiate an array of 16 Full Adders
// Each instance [i] is connected to bit select [i]
```

```
    Full_Adder FA [15:0] (a[15:0], b[15:0], c[15:0], c[16:1], sum[15:0]);
```

```
endmodule
```

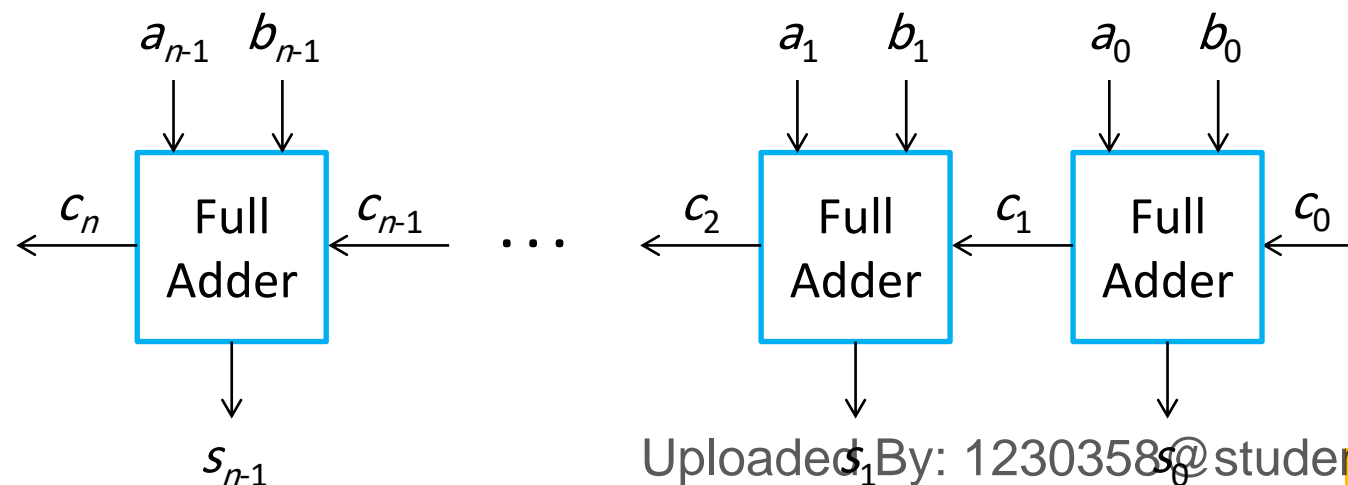**Array Instantiation** of identical modules by a **single** statement



```
// Input ports: 16-bit a and b, 1-bit cin (carry input)
// Output ports: 16-bit sum, 1-bit cout (carry output)

module Adder_16 (input [15:0] a, b, input cin, output [15:0] sum, output cout);

    wire [16:0] c;           // carry bits
    assign c[0] = cin;      // carry input
    assign cout = c[16];    // carry output

    // assignment of 16-bit vectors
    assign sum[15:0] = (a[15:0] ^ b[15:0]) ^ c[15:0];
    assign c[16:1] = (a[15:0] & b[15:0]) | (a[15:0] ^ b[15:0]) & c[15:0];

endmodule
```



```
module Adder16 ( input [15:0] A, B, input cin, output [15:0] Sum, output cout );  
  
    // A and B are 16-bit input vectors  
    // Sum is a 16-bit output vector  
  
    // {cout, Sum} is a concatenated 17-bit vector  
    // A + B + cin is 16-bit addition + input carry  
    // The + operator is translated into an adder  
  
    assign {cout, Sum} = A + B + cin;  
  
endmodule
```



```
// Parametric n-bit adder, default value for n = 16
```

```
module Adder #(parameter n = 16)
```

```
( input [n-1:0] A, B, input cin, output [n-1:0] Sum, output cout );
```

```
// A and B are n-bit input vectors
```

```
// Sum is an n-bit output vector
```

```
// The + operator is translated into an n-bit adder
```

```
// Only one assign statement is used
```

```
assign {cout, Sum} = A + B + cin;
```

```
endmodule
```



```
// Instantiate a 16-bit adder (parameter n = 16)
// A1, B1, and Sum1 must be 16-bit vectors
Adder #(16) adder16 (A1, B1, Cin1, Sum1, Cout1);

// Instantiate a 32-bit adder (parameter n = 32)
// A2, B2, and Sum2 must be 32-bit vectors
Adder #(32) adder32 (A2, B2, Cin2, Sum2, Cout2);

// If parameter is not specified, it defaults to 16
Adder adder16 (A1, B1, Cin1, Sum1, Cout1);
```




```
// n-bit magnitude comparator, No default value for n
module Comparator #(parameter n)
  (input [n-1:0] A, B, output GT, EQ, LT);

  // A and B are n-bit input vectors (unsigned)
  // GT, EQ, and LT are 1-bit outputs

  assign GT = (A > B);
  assign EQ = (A == B);
  assign LT = (A < B);

endmodule
```

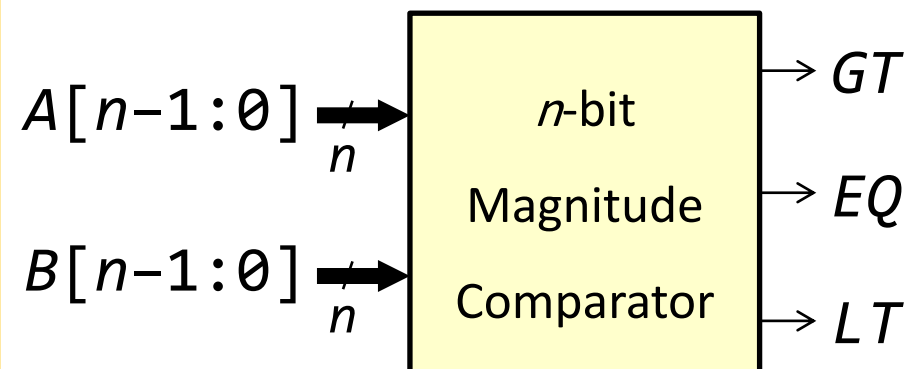



```
// Instantiate a 16-bit comparator (n = 16)
```

```
// A1 and B1 must be declared as 16-bit vectors
```

```
Comparator #(16) comp16 (A1, B1, GT1, EQ1, LT1);
```

```
// Instantiate a 32-bit comparator (n = 32)
```

```
// A2 and B2 must be declared as 32-bit vectors
```

```
Comparator #(32) comp32 (A2, B2, GT2, EQ2, LT2);
```

```
// WRONG Instantiation: Must specify parameter n
```

```
Comparator comp32 (A2, B2, GT2, EQ2, LT2);
```

### 🌀 Syntax:

- 🌀 Boolean\_expr ? True\_expression : False\_expression
- 🌀 **If** Boolean\_expr is true then select True\_expression
- 🌀 **Else** select False\_Expression
- 🌀 Conditional operators can be **nested**

### Example:

```
assign max = (a>b)? a : b;           // maximum of a and b
assign min = (a>b)? b : a;           // minimum of a and b
```

```
// Parametric 2x1 Mux, default value for n = 1
```

```
module Mux2 #(parameter n = 1)
```

```
( input [n-1:0] A, B, input sel, output [n-1:0] Z);
```

```
// A and B are n-bit input vectors
```


```
// Z is the n-bit output vector
```

```
// if (sel==0) Z = A; else Z = B;
```

```
// Conditional operator used for selection
```

```
assign Z = (sel == 0)? A : B;
```

```
endmodule
```

 

```
// Parametric 2x1 Mux, default value for n = 1
```

```
module Mux4 #(parameter n = 1)
```

```
( input [n-1:0] A,B,C, D, input [1:0] sel, output [n-1:0] Z);
```

```
// sel is a 2-bit vector
```


```
// Nested conditional operators
```

```
assign Z = (sel[1] == 0) ?
```

```
    ((sel[0] == 0) ? A : B) :
```

```
    ((sel[0] == 1) ? C : D);
```

```
endmodule
```

 

- ☉ Uses **procedural blocks** and procedural **statements**
- ☉ There are **two types** of procedural blocks in Verilog
  - ☉ The **initial** block
    - ★ Executes the enclosed statement(s) **one time only**
  - ☉ The **always** block
    - ★ Executes the enclosed statement(s) **repeatedly** until simulation **terminates**
- ☉ The **body** of the initial and always blocks is **procedural**
- ☉ Can enclose **one or more** procedural statements
- ☉ Procedural statements are **surrounded** by **begin ... end**
- ☉ Multiple procedural blocks can appear in **any order** inside a module and **run in parallel** inside the simulator

```
module behave;
reg clk;           // 1-bit variable
reg [15:0] A;      // 16-bit variable

initial begin     // executed once
    clk = 0;      // initialize clk
    A = 16'h1234; // initialize A
    #200 $finish
end

always begin      // executed always
    #10 clk = ~clk; // invert clk every 10 ns
end

always begin      // executed always
    #20 A = A + 1; // increment A every 20 ns
end

endmodule
```



☯ Syntax:

```
always @(sensitivity list) begin
```

```
    procedural statements
```

```
end
```

- ☯ An **always** block can have a **sensitivity list**
- ☯ Sensitivity list is a list of **signals**: @(signal1, signal2, ...)
- ☯ The sensitivity list **triggers** the execution of the always block, when there is a **change of value in any listed signal**. Otherwise, the always block **does nothing** until another change occurs on a signal in the sensitivity list





🌀 For combinational logic, the sensitivity list **must include**:

🕒 **ALL** the signals that are read inside the always block

🌀 Combinational logic can also use: **@(\*)** or **@\***

**@(\*)** is **automatically** sensitive to all the signals that are read inside the **always** block

**Example:** **A**, **B**, and **sel** must be in the sensitivity list below:

```
always @(A, B, sel) begin
    if (sel == 0) Z = A;
    else Z = B;
end
```

**A**, **B**, and **sel** are read  
inside the **always** block

☼ The **if** statement is **procedural**

- ☉ Can only be used inside a procedural block

☼ **Syntax:**

**if** (*expression*) *statement*

[**else** *statement*]

☼ The **else** part is **optional**

☼ A statement can be **simple or compound**

☼ A **compound** statement is surrounded by **begin ... end**

☼ **if** statements can be **nested**

- ☉ Can be nested under if or under else part

```
// Behavioral Modeling of a Parametric 2x1 Mux
```

```
module Mux2 #(parameter n = 1)
```

```
( input [n-1:0] A, B, input sel, output reg [n-1:0] Z);
```

```
// Output Z must be of type reg
```

```
// Sensitivity list = @(A, B, sel)
```


```
always @(A, B, sel) begin
```

```
    if (sel == 0) Z = A;
```

```
    else Z = B;
```

```
end
```

```
endmodule
```

 



```
module Decoder3x8 (input [2:0] A, output reg [7:0] D);  
    // Sensitivity list = @(A)  
  
    always @(A) begin  
        if (A == 0) D = 8'b00000001;  
        else if (A == 1) D = 8'b00000010;  
        else if (A == 2) D = 8'b00000100;  
        else if (A == 3) D = 8'b00001000;  
        else if (A == 4) D = 8'b00010000;  
        else if (A == 5) D = 8'b00100000;  
        else if (A == 6) D = 8'b01000000;  
        else  
            D = 8'b10000000;  
    end  
  
endmodule
```



```
module Priority_Encoder4x2 (input [3:0] D, output reg V, output reg [1:0] A);  
  
    // sensitivity list = @(D)  
    always @(D) begin  
        if      (D[3]) {V, A} = 3'b111;  
        else if (D[2]) {V, A} = 3'b110;  
        else if (D[1]) {V, A} = 3'b101;  
        else if (D[0]) {V, A} = 3'b100;  
        else      {V, A} = 3'b000;  
    end  
  
endmodule
```



☯ The **case** statement is procedural (used inside always block)

☯ **Syntax:**

**case** (expression)

case\_item1:statement

case\_item2:statement

...

**default:** statement


**endcase**

☯ The **default** case is optional

☯ A statement can be **simple or compound**

☯ A **compound** statement is surrounded by **begin ... end**
 
```
module Mux4 #(parameter n = 1)
  ( input [n-1:0] A, B, C, D, input [1:0] sel, output reg [n-1:0] Z );
  // @(*) is @(A, B, C, D, sel)
  always @(*) begin
    case (sel)
      2'b00: Z = A;
      2'b01: Z = B;
      2'b10: Z = C;
      default: Z = D;
    endcase
  end
endmodule
```




```
// Behavioral Modeling of an ALU
module ALU #(parameter n = 16)
  ( input [n-1:0] A, B, input [1:0] F,
    output reg [n-1:0] Z, output reg Cout );

// @(*) is @(A, B, F)
always @(*) begin
  case (F)
    2'b00: {Cout,Z} = A+B;
    2'b01: {Cout,Z} = A-B;
    2'b10: {Cout,Z} = A&B;
    default: {Cout,Z} = A | B;
  endcase
end


endmodule
```

## ALU Symbol

 



```
module BCD_to_7Seg_Decoder ( input [3:0] BCD, output reg [6:0] Seg )  
  
always @(BCD) begin  
    case (BCD)  
        0: Seg = 7'b1111110;  1: Seg = 7'b0110000;  
        2: Seg = 7'b1101101;  3: Seg = 7'b1111001;  
        4: Seg = 7'b0110011;  5: Seg = 7'b1011011;  
        6: Seg = 7'b1011111;  7: Seg = 7'b1110000;  
        8: Seg = 7'b1111111;  9: Seg = 7'b1111011;  
        default: Seg = 7'b0000000;  
    endcase  
end  
  
endmodule
```

 

A row of ten 7-segment displays showing the digits 0 through 9. The digit '1' is shown with a dashed outline to indicate its segments.