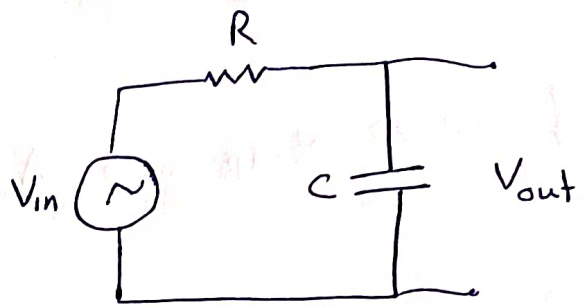


# Exp 10: RC Filters

→ low-pass filter:



$$I(t) = \frac{V_{in}(t)}{Z_{eq}} = \frac{V_{in}(t)}{R - \frac{j}{\omega C}}$$

$$V_{in}(t) = V_{in0} \cos \omega t \Rightarrow I(t) = \frac{V_{in0} \cos \omega t}{R - j/\omega C}$$

$$V_{out} = V_c(t) = I(t) Z_c = \frac{V_{in0} \cos \omega t}{R - j/\omega C} \left( \frac{-j}{\omega C} \right)$$

$$V_c(t) = \frac{V_{in0} \cos \omega t}{1 + j\omega RC}$$

$$V_{co} = \frac{V_{in0}}{\sqrt{1 + \omega^2 C^2 R^2}}$$


$V_{co}$ : Amp. of  $V_c(t)$  [output]

$V_{in0}$ : Amp. of  $V_{in}(t)$  [input]

\* The Attenuation factor (A) =  $\frac{V_{co}}{V_{in0}} = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$

$$\omega_{-3dB} = \frac{1}{RC}$$
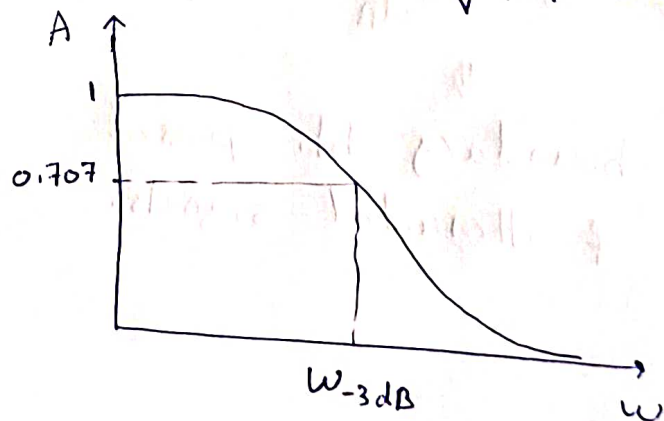
$$\Rightarrow A = \frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_{-3dB}} \right)^2}}$$



1- if  $\omega \ll \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{1+0}} = 1 \Rightarrow \text{Pass}$


2- if  $\omega \gg \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{1+\infty}} \Rightarrow 0 \Rightarrow \text{Attenuated}$

3- if  $\omega = \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$

↓  
practical boundary between passed signals & highly attenuated ones.

⇒ low pass filter (small  $\omega$ )

\* High pass RC filter:

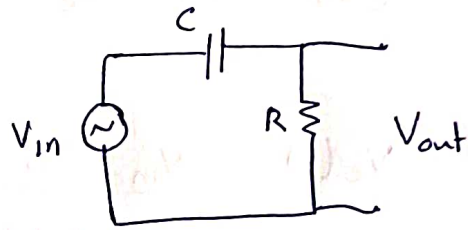


$$A = \frac{1}{\sqrt{1 + \left(\frac{\omega_{-3dB}}{\omega}\right)^2}}$$

① if  $\omega \ll \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{1+\infty}} \Rightarrow 0 \text{ (Attenuated)}$

② if  $\omega \gg \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{1+0}} = 1 \text{ (Pass)}$

③ if  $\omega = \omega_{-3dB} \Rightarrow A = \frac{1}{\sqrt{2}} = 0.707$

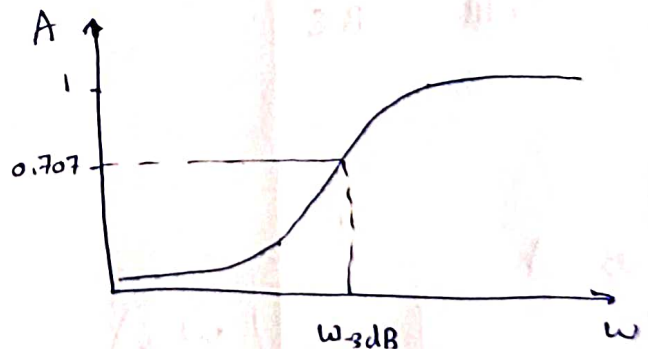
↓  
boundary bt. passed & attenuated signals.




\* Differentiators & Integrators.

→ Low pass filter:

when  $\omega \gg \omega_{-3dB}$

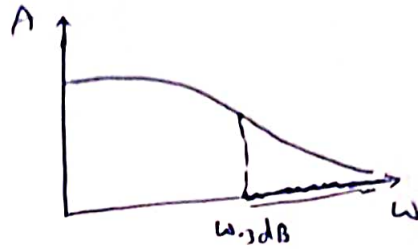


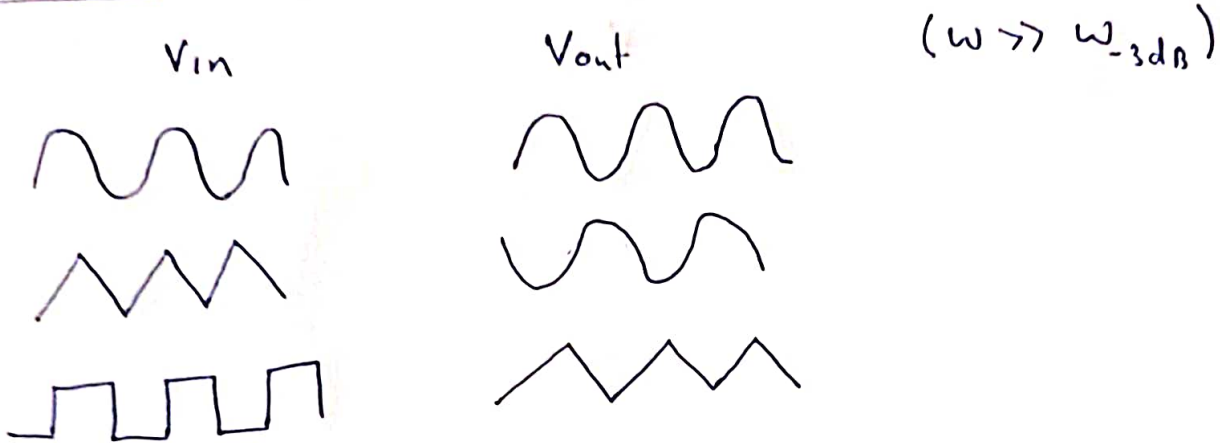The output voltage is just the integral of the input voltage. ⇒ (Integrator)



→ High pass filter:

when  $\omega \ll \omega_{-3dB}$

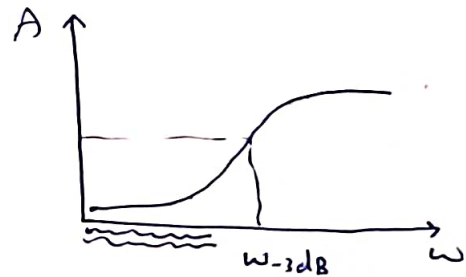

The output voltage is just the derivative of the input voltage ⇒ (differentiator)

