

# Digital Systems

## Section 2

### Chapter (3)



- ⊖ A Boolean **Function** is **uniquely** represented by a **truth table**
- ⊖ Boolean **Function** can be implemented (**NOT Uniquely**) by a Boolean **Equation** and the corresponding **logic diagram**
- ⊖ Simplest Functions use the **smallest** number of the **smallest** gates and therefore give the *most economical* and *efficient* circuit implementations
- ⊖ Boolean **Function** can be **simplified** by **algebraic methods** learned earlier
  - ★ This process is **not** always **straight-forward** and may **not** result in the **simplest** form of an expression
- ⊖ A **formal** approach for simplification is needed (**systematic** procedure)

Requires: Minimization

**The Map Method**

⊖ A **Straight-forward/Simpler** method to achieve minimization **systemically** **K-Map**

✧ **Graphical** representation of a Truth Table

⊖ A K-map is a **diagram** made up of **squares** representing **minterms**

✧ K-map for **n** variables is a collection of  **$2^n$**  squares/cells [**n variables** →  **$2^n$  minterms**]


✧ Each **Square/Cell** → **Minterm**

✧ **Squares** arranged such that physically **adjacent cells** differ in the value of **only one literal**

⊖ Different **patterns** in this diagram can be **detected** to simplify expressions

⊖ **Adjacent** minterms can be **combined** to form simpler terms

 
⊖ The **simplified** expression will always be in sum-of-products or product-of-sums form




⊖ K-Map produces a circuit diagram with **minimum** number of **gates**

⊖ K-Map produces circuits with gates having **minimum** number of **inputs**

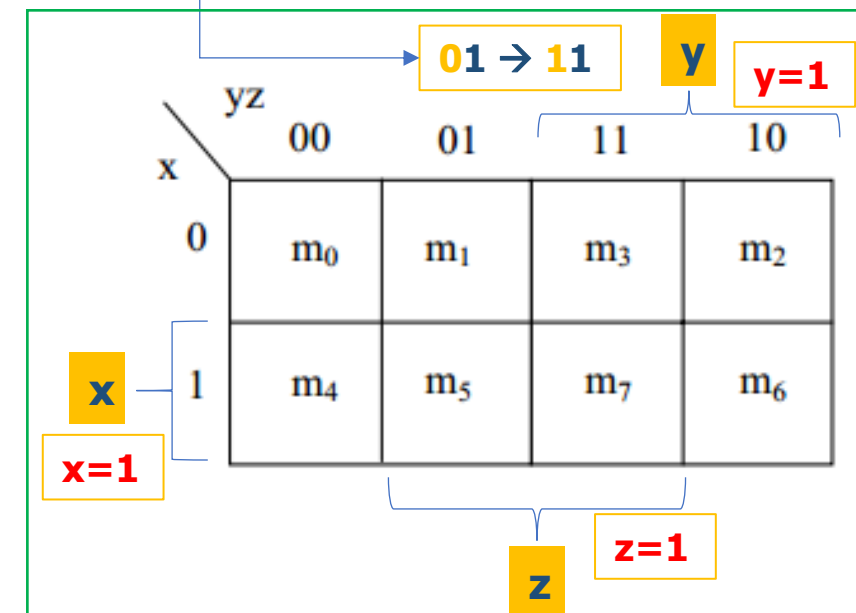
⊖ The simplest expression is **not unique** – two or more **optimal** expressions may exist



 - ⊖ Boolean functions having **two** variables  $x$  and  $y$
- ⊖ There are  $2^2 = 4$  minterms for **two** variables  $xy, x'y, xy', x'y'$
- ⊖ A K-map for **two** variables will have **four squares** → Each cell will represent a **minterm**



Each **cell** represents the **minterm** of the corresponding **row** in the truth table

 **Example:**

$$F = x \cdot y$$

$$F = x + y$$

⊖ Boolean functions having **three** variables  $x, y$  and  $z$

⊖ There are  $2^3 = 8$  minterms for **three** variables

$$x'y'z', x'y'z, x'yz, x'yz', xy'z', xy'z, xyz, xyz'$$

⊖ A K-map for **three** variables will have **eight squares** → Each cell will represent a **minterm**

		$y$			
		00	01	11	10
$x$	$yz$	00	01	11	10
	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$
1	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$
		$z$			

### Be Careful:

The order is **not** sequential  
 $m_3$  before  $m_2$   
 $m_7$  before  $m_6$

Each **cell** represents the **minterm**  
of the corresponding **row** in the truth table

- ⊖ Boolean functions having **Four** variables  $w, x, y$  and  $z$
- ⊖ There are  $2^4 = 16$  minterms for **Four** variables
- ⊖ A K-map for **Four** variables will have **sixteen squares** → Each cell will represent a **minterm**

**Be Careful:**

The order is **not** sequential  
 $m_3$  before  $m_2$   
 $m_7$  before  $m_6$   
 $m_{12} - m_{15}$  before  $m_8 - m_{11}$

Each **cell** represents the **minterm**  
of the corresponding **row** in the truth table

		$y$				
		00	01	11	10	
$w$	$wx$	$yz$				
	00	$m_0$ $w'x'y'z'$	$m_1$ $w'x'y'z$	$m_3$ $w'x'yz$	$m_2$ $w'x'yz'$	} $x$
	01	$m_4$ $w'xy'z'$	$m_5$ $w'xy'z$	$m_7$ $w'xyz$	$m_6$ $w'xyz'$	
	11	$m_{12}$ $wxy'z'$	$m_{13}$ $wxy'z$	$m_{15}$ $wxyz$	$m_{14}$ $wxyz'$	
10	$m_8$ $wx'y'z'$	$m_9$ $wx'y'z$	$m_{11}$ $wx'yz$	$m_{10}$ $wx'yz'$		
		$z$				

- ⊖ **Construct** the corresponding map (based on number of variables)
- ⊖ **Enter** function **output (1's)** values on the map (from Truth Table or Canonical Form) to the corresponding cell/square

**Map** the following Function on a K-map

$$F_1(A, B, C) = A'B'C + A'BC' + ABC' + ABC$$

Canonical Form

- 1) Three variables  $\rightarrow 2^3 = \mathbf{8}$ -cell K-map
- 2) Place a **1** on the K-map in the cell having the **same** minterm index/value

$$A'B'C = 001, A'BC' = 010, ABC' = 110, ABC = 111$$

Primed  $\rightarrow 0$   
Unprimed  $\rightarrow 1$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0		1		1
	1			1	1

**Be Careful:**

The order is **not** sequential  
 $m_3$  before  $m_2$   
 $m_7$  before  $m_6$



**Example:**

$$F = \sum (0, 1, 6, 7)$$

		yz			
		00	01	11	10
x	0	1 m <sub>0</sub>	1 m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
	1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub> 1	m <sub>6</sub> 1



		yz			
		00	01	11	10
x	0	1	1		
	1			1	1

**Map** the following Function on a K-map

$$F_3(A, B, C) = A'C + A'BC' + ABC' + A$$

**Convert** to Canonical Form



**Expand** each term to represent  $F_3$  as a sum-of-minterms (SOM) form

$A'C$  will expand to  $A'BC + A'B'C$

$A$  will expand to  $ABC + ABC' + AB'C + AB'C'$

Therefore,  $F_3(A, B, C) =$

$$A'BC + A'B'C + A'BC' + ABC' + ABC + \cancel{ABC'} + AB'C + AB'C'$$

$$F_3(A, B, C) = A'BC + A'B'C + A'BC' + ABC' + ABC + AB'C + AB'C'$$

011

001

010

110

111

101

100

Canonical Form

Primed  $\rightarrow$  0

Unprimed  $\rightarrow$  1

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

**Be Careful:**

The order is **not** sequential  
11 before 10

**Map** the following Function on a K-map

$$F_2(A, B, C, D) = A'BCD' + ABCD' + ABC'D' + ABCD$$

Canonical Form

- 1) Four variables  $\rightarrow 2^4 = \mathbf{16}$ -cell K-map
- 2) Place a **1** on the K-map in the cell having the **same** minterm index/value

$$F_2(A, B, C, D) = A'BCD' + ABCD' + ABC'D' + ABCD$$

0110

1110

1100

1111

Primed  $\rightarrow 0$

Unprimed  $\rightarrow 1$

		$CD$			
		00	01	11	10
$AB$	00				
	01				1
	11	1		1	1
	10				

**Be Careful:**

The order is **not** sequential  
11 before 10 (in Rows & Columns)

- ⊖ **Single** variable **changes** in **adjacent** cells
- ⊖ Cells that **differ** by only **one** variable are called **adjacent** cells
- ⊖ Example:
  - ★ 011 is adjacent to 010
  - ★ 011 is **not** adjacent to 101
- ⊖ **Wrap-around** adjacency:
  - ★ Cells in the **left-most** column are **adjacent** to the cells in the **right-most** column (100 & 110)

What is the **sum** of minterms in two adjacent squares?

$$\begin{aligned}
 m_0 + m_4 &= x'y'z' + xy'z' \\
 &= (x' + x)y'z' = y'z' \\
 m_7 + m_6 &= xyz + xyz' \\
 &= xy(z + z') = xy \\
 m_0 + m_2 &= x'y'z' + x'yz' \\
 &= x'z'(y' + y) = x'z'
 \end{aligned}$$

		y			
		00	01	11	10
x	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$
	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$

z

**Sum** of two minterms in **adjacent** squares can be simplified to a **single product** term consisting of only **two literals**. The **dissimilar** variable will go away.

⊖ Once a SOM expression has been **mapped** on the K-map, there are three steps in obtaining a simplified form

- 1) **Group** 1's
- 2) **Determine** the **product** term for each group
- 3) **Sum** the resulting **terms**

⊖ Group 1's with the following goal in mind: **Maximize** the **size** of the groups and **minimize** the **number** of groups

⊖ Group 1's according to the following rules:

- ✓ Group **size** must be **powers** of **2** (1, 2, 4, 8, or 16,.. Cells)
- ✓ Each **cell** in a group must be **adjacent** to one or more cells in that **same** group.  
(**Not** all cells in a group have to be adjacent to each other)
- ✓ Always include the **largest** possible number of **1's** in a group
- ✓ Each **1** on the map must be included in at **least one** group
- ✓ The **1's** already in a group can be included in another group as long as the **overlapping** groups include **non-common 1's**

**Example:**

3-Variables

$$F = A'B'C + A'BC' + ABC + ABC'$$

Map

		BC			
		00	01	11	10
A	0		1		1
	1			1	1

Group

		BC			
		00	01	11	10
A	0		1		1
	1			1	1

**Example:**

$$F(A, B, C) = \Sigma(1, 2, 3, 4, 5, 6, 7)$$

Map

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

Group

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

Grouping: A 2x2 square of 1s in the rightmost columns (BC=11 and 10) is highlighted in red.

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

Grouping: A 2x2 square of 1s in the middle columns (BC=01 and 11) is highlighted in blue, a 2x2 square of 1s in the rightmost columns (BC=11 and 10) is highlighted in red, and a 2x2 square of 1s in the bottom row (A=1) is highlighted in green.

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

Grouping: A 2x2 square of 1s in the middle columns (BC=01 and 11) is highlighted in blue, a 2x2 square of 1s in the rightmost columns (BC=11 and 10) is highlighted in red, and a 2x4 horizontal row of 1s (A=1) is highlighted in green.

✓ Maximize Group Size

2 - Choices

		BC			
		00	01	11	10
A	0		1	1	1
	1	1	1	1	1

Grouping: A 2x2 square of 1s in the middle columns (BC=01 and 11) is highlighted in blue, a 2x2 square of 1s in the rightmost columns (BC=11 and 10) is highlighted in red, and a single 1 in the bottom-left cell (A=1, BC=00) is highlighted in green.

**Example:**

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00				
	01				1
	11	1		1	1
	10				

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00				
	01				1
	11	1		1	1
	10				

**NOT**  
Optimal

2 - Choices

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00				
	01				1
	11	1		1	1
	10				

**Maximize**  
Group Size



**Example:**

✘ **NOT**  
Optimal

AB \ CD	CD			
	00	01	11	10
00			1	1
01				1
11				1
10			1	1

AB \ CD	CD			
	00	01	11	10
00			1	1
01				1
11				1
10			1	1

✓ **Maximize**  
Group Size

AB \ CD	CD			
	00	01	11	10
00			1	1
01				1
11				1
10			1	1

**Example:****☒ Unnecessary/Duplications**

AB \ CD	00	01	11	10
00			1	1
01	1			1
11	1			1
10			1	1

K-map showing groupings for the function  $f(A,B,C,D) = \sum m(3,4,5,6,7,11,12,13,14)$ . The map is annotated with several overlapping groups: a green group covering cells (00,11), (00,10), (10,11), and (10,10); a purple group covering cells (01,00), (01,01), (11,00), and (11,01); a red group covering cells (00,10), (01,10), (11,10), and (10,10); and a blue group covering cells (01,00), (01,01), (11,00), and (11,01). These overlapping groups represent unnecessary or duplicated prime implicants.

**✓ Optimal/No Duplication**

AB \ CD	00	01	11	10
00			1	1
01	1			1
11	1			1
10			1	1

K-map showing groupings for the function  $f(A,B,C,D) = \sum m(3,4,5,6,7,11,12,13,14)$ . The map is annotated with four non-overlapping prime implicants: a green group covering cells (00,11), (00,10), (10,11), and (10,10); a purple group covering cells (01,00), (01,01), (11,00), and (11,01); a red group covering cells (00,10), (01,10), (11,10), and (10,10); and a blue group covering cells (01,00), (01,01), (11,00), and (11,01). These groups represent an optimal solution with no duplications.

**Example:**


✗ Groups of (2 Minterms) → Not **Maximized Size**

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	1		1	1
	01				1
	11				1
	10	1		1	1


		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	1		1	1
	01				1
	11				1
	10	1		1	1

✓ **Maximize** Group Size

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	1		1	1
	01				1
	11				1
	10	1		1	1

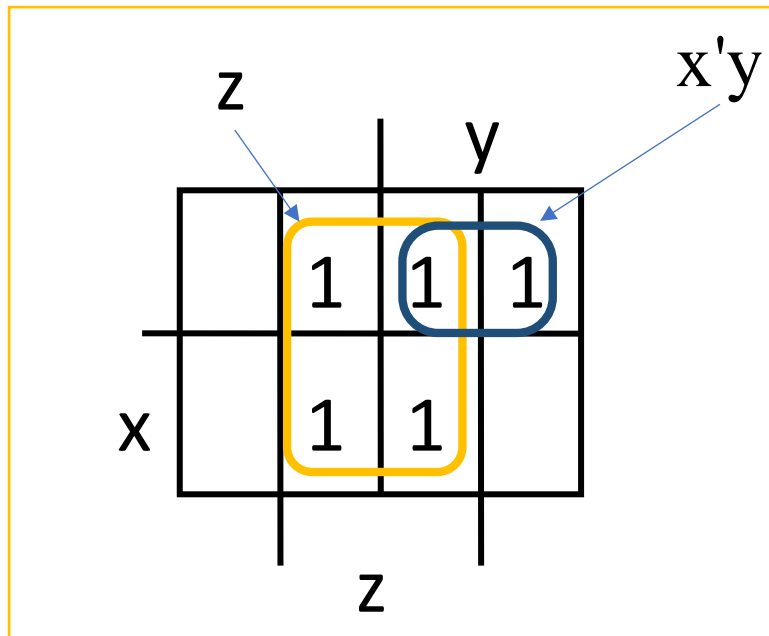**Examples:**


$$F(x, y, z) = z + x'y$$

 

$$F = z' + xy'$$

 **Examples:**

$$F(W, X, Y, Z) = \Sigma_m(0, 2, 3, 4, 5, 6, 7, 8, 10, 13, 15)$$



$$F(W, X, Y, Z) = ZX + \bar{W}Y + \bar{X}\bar{Z} + \bar{W}X$$


No. of **literals** in an expression = Total No. of variables -  $\log_2$  (No. of cells in group)

3-Variables		
No. Cells	Literals	e.g.
1	3	xyz
2	2	xy
4	1	x
8	Zero	F=1


4-Variables		
No. Cells	Literals	e.g.
1	4	wxyz
2	3	xyz
4	2	xy
8	1	x
16	Zero	F=1

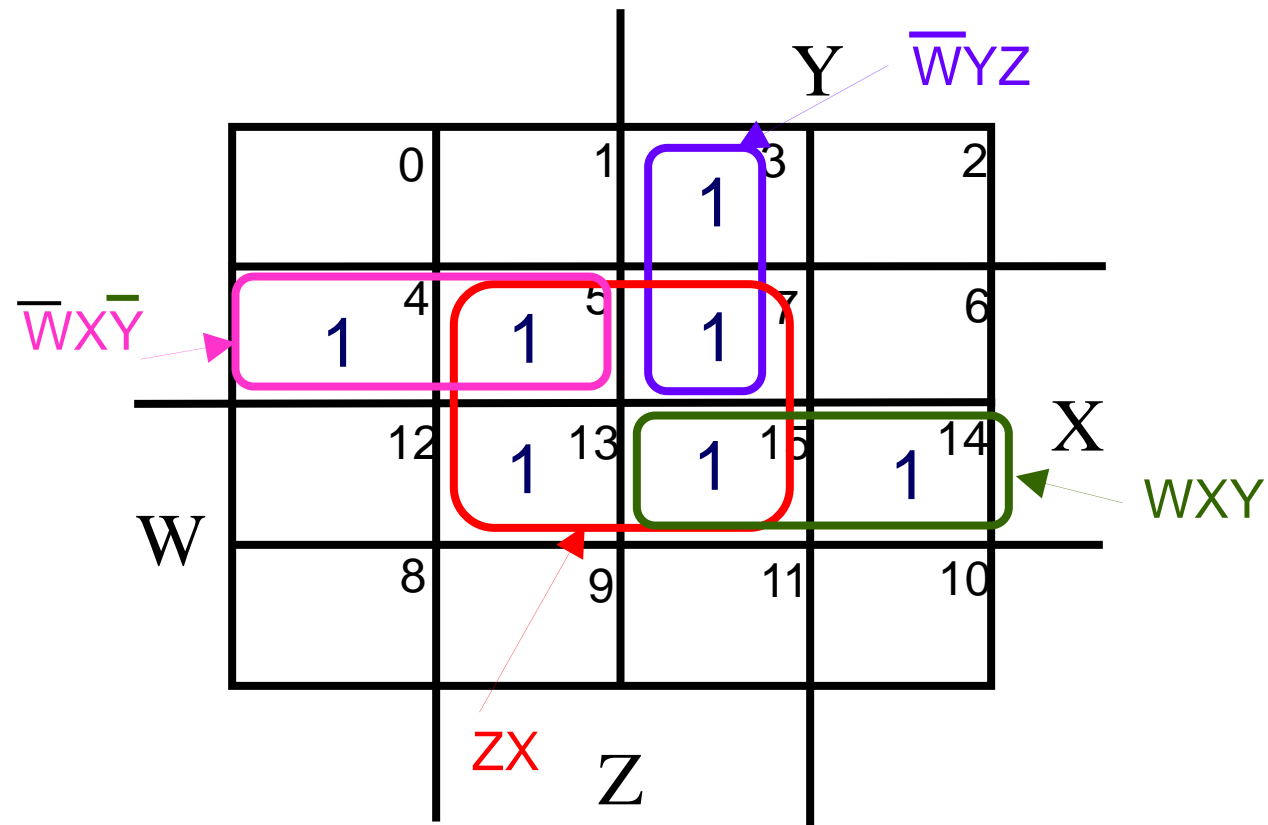**More Examples:**


$$F(W, X, Y, Z) = \sum_m(3,4,5,7,13,14,15)$$



$$F(W, X, Y, Z) = ZX + \overline{W}YZ + WXY + \overline{W}X\overline{Y}$$

 More Examples:

$$F = A'B + B'C$$

 

$$F = y' + w'z' + xz'$$






- ⊖ In choosing **adjacent** squares in a map, we must **ensure** that:
  - Ⓜ **All** minterms of the function are **covered** when we combine squares
  - Ⓜ The number of **terms** in the expression is **minimized**
  - Ⓜ **No redundant** terms
- ⊖ Sometimes there might be **two or more expressions** that **satisfy** the simplification criteria

- ⊖ The procedure for **combining** squares in the map may be made more **systematic** if we understand the meaning of the following terms.
- Ⓜ **Implicant:** is a product term of a function obtained by **valid grouping** of adjacent squares (minterms or 1's)
  - Ⓜ **Prime Implicant (PI):** is a product term obtained by combining the **maximum possible** number of adjacent squares
    - Ⓜ **Examples:**
      - ✓ **1** that is not adjacent to any other 1's.
      - ✓ **Two** adjacent 1's that are not in a group of four adjacent 1's.
      - ✓ **Four** adjacent 1's that are not in a group of eight adjacent 1's
  - Ⓜ **Essential Prime Implicant (EPI):** If a **minterm** is **covered** by **only one** prime implicant, that prime implicant is said to be **essential prime implicant**

The **simplified** expression is obtained from the **logical sum** of **all the essential prime implicants**, plus **other prime implicants that may be needed** to **cover** any remaining **minterms not covered** by the essential prime implicants.

**Example:**


Essential PI's

 

● The Minterm is **only** covered by this **PI**.

Essential prime implicants  
 $BD$  and  $B'D'$

Non Essential PI's

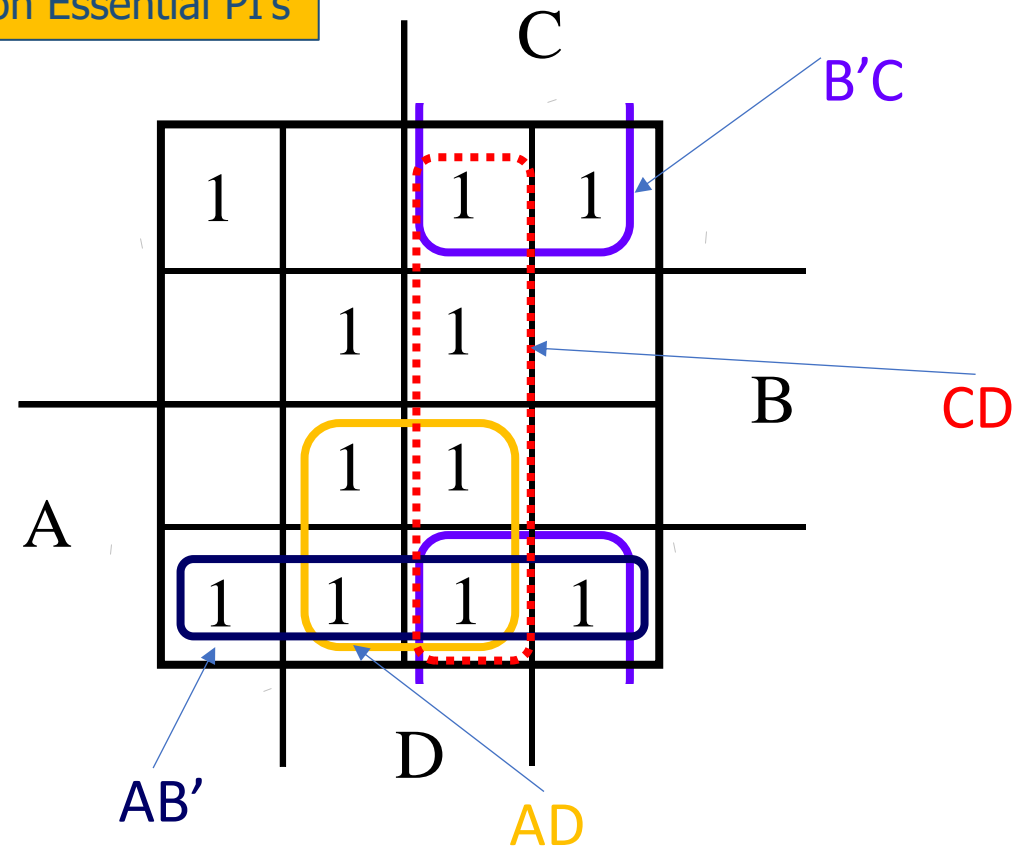

Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$

**Example Continue:**Essential prime implicants  
 $BD$  and  $B'D'$ Prime implicants  $CD$ ,  $B'C$ ,  
 $AD$ , and  $AB'$ 


The **simplified** expression is obtained from the **logical sum** of the **two essential** prime implicants and **any** two prime implicants that **cover** the **remaining** minterms (m3, m9, m11)

$$\begin{aligned} F &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$

**Extra Example :**

PI's with minimum overlap

Essential PIs

 

Avoid **Unnecessary overlap** amongst additional **selected PI's**

- ⊖ **Functions** that have **unspecified** outputs for some input combinations are called incompletely specified functions
  - Ⓜ Such situation arises in which some input variable combinations are **not allowed** OR might **never occur**
  - Ⓜ For example, in **BCD** there are six **invalid combinations**.
- ⊖ Since these **unspecified/unallowed** terms will **never** occur, they can be treated as **don't-care** terms with respect to their effect on the outputs
- ⊖ For these "**don't-care**" terms either a **1 or a 0 may** be assigned to the output
  - Ⓜ it really **does not matter** since they will **never occur**
- ⊖ For the "**don't-care**" input combinations, an **X** is placed in the corresponding square (minterm)
- ⊖ When **grouping 1's**, the **X's** can be **treated as 1's** to form **larger** groups → **simpler expression**
  - Ⓜ To get the simplified expression, we **must include all 1's** in the map, but we **may or may not include** any of the **X's**

**Example:**


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	0
0	0	0	1	X
0	0	1	0	X
0	0	1	1	X
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	X
1	0	0	0	0
1	0	0	1	X
1	0	1	0	1
1	0	1	1	X
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00		X	X	X
	01		1	X	X
	11		1	1	1
	10		X	X	1

**Example:**BCD Code :  $> 6 \rightarrow F=1$ 

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

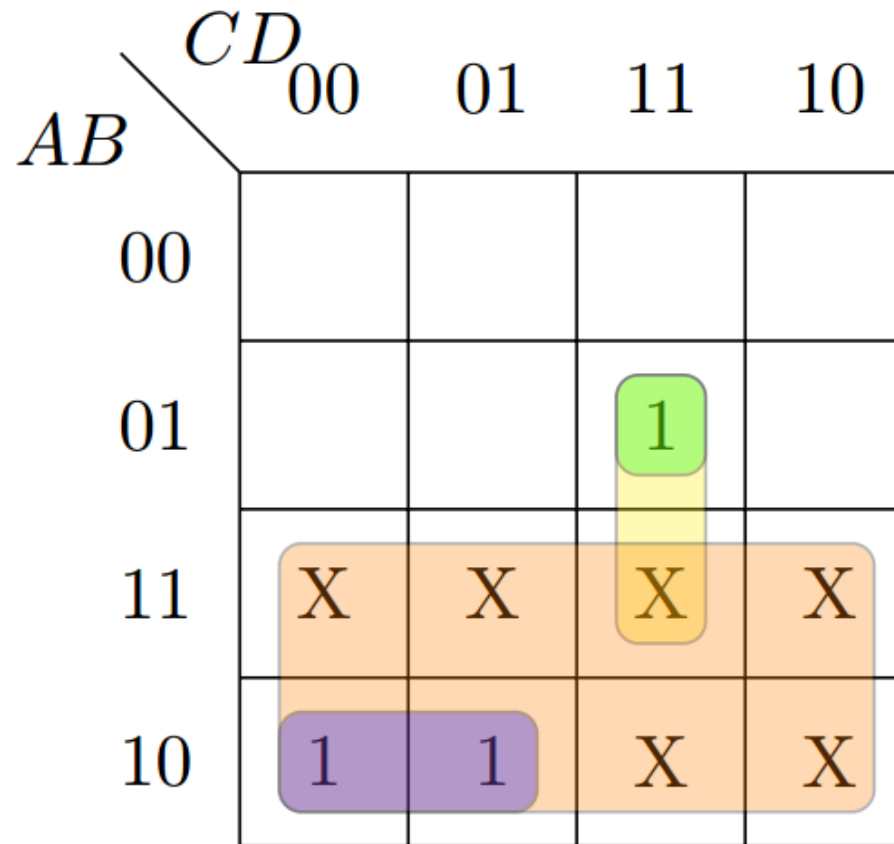


$$F = A + BCD$$



 **Extra Example:**


Simplify the function  $F(w, x, y, z) = \Sigma(1,3,7,11,15)$ , which has the don't care conditions  $d(w, x, y, z) = \Sigma(0,2,5)$



OR

$$F = yz + w'x'$$

$$F = yz + w'z$$

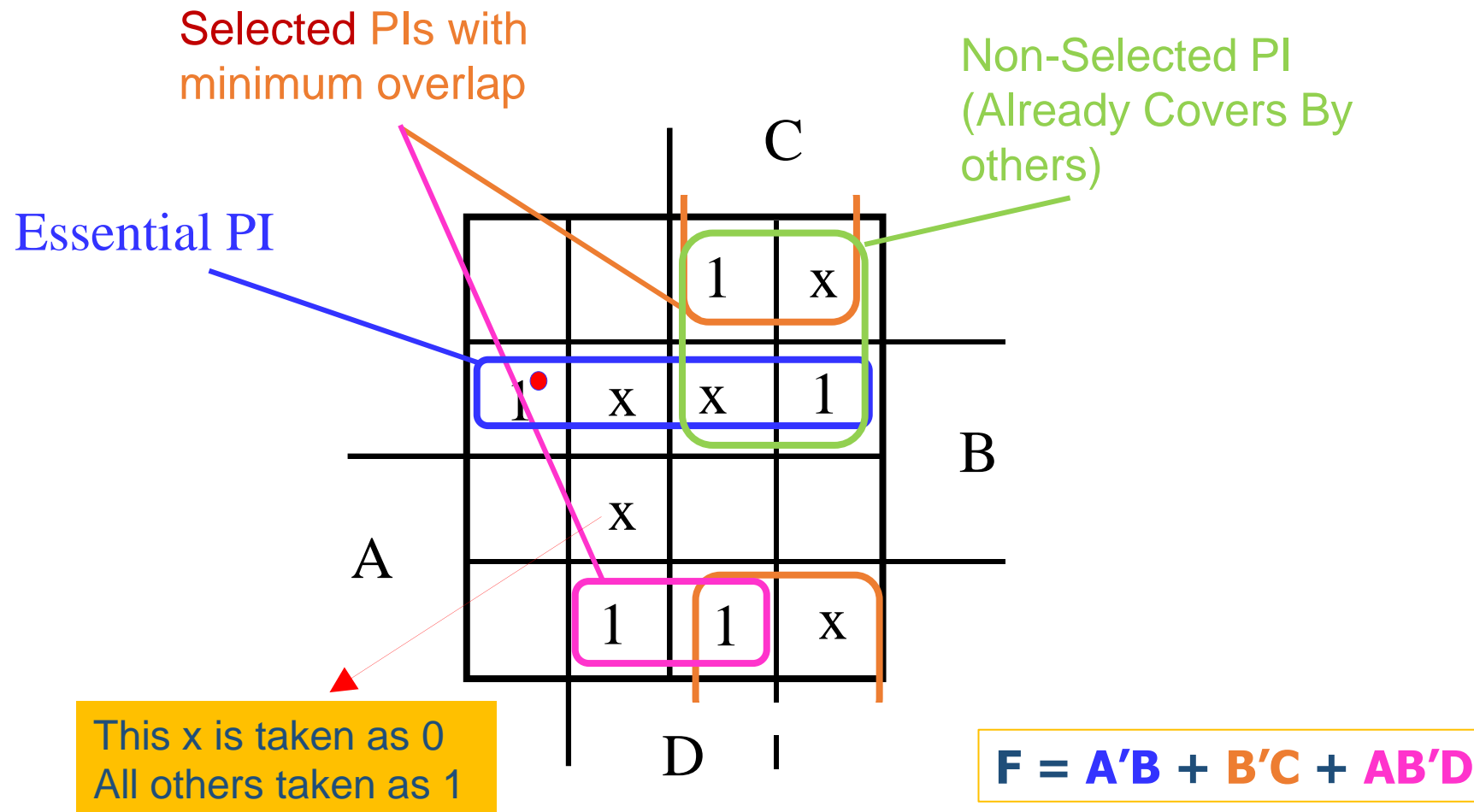**Extra Example:**

- ⊖ So far, We have been **combining minterms** ('1' squares), to get **F** as a **Sum of Products** (SOP) out of the K-Map simplification process
- ⊖ If we combine the **remaining** minterms ('0' squares), we get the **complement of F** => (**F'**)
  - ⓓ Using **DeMorgan's** Theorem we can get **F** as a **Product-of-Sums** (POS) by **complementing F'** => (**F'**)' = **F**

### Product of Sums (POS) Procedure

- 1) Combine the 0's into groups
- 2) Form a sum-of-products (SOP) expression from these groups of 0's → **F'**
- 3) Take its **complement** using DeMorgan's theorem to get **F** as **product-of-sum**

		CD			
		00	01	11	10
AB	00	0	0	X	0
	01			X	
	11	0	X	X	
	10			X	0

The following groups of 0's are formed:

- Red group:  $A'B'$
- Blue group:  $ABC'$
- Green group:  $B'C$

The expression of  $F' = A'B' + ABC' + B'C$


Use DeMorgan's theorem to find its complement in order to write an expression of  $F$

$$F = (A + B)(A' + B' + C)(B + C')$$

**Example:**

<b>x</b>	<b>y</b>	<b>z</b>	<b>F</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$F = m_1 + m_3 + m_4 + m_6$$

 

$$F = x'z + xz'$$

$$F' = xz + x'z'$$

$$(F')' = F = (x' + z')(x + z)$$


**Extra Example:**

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$

$$F' = AB + CD + BD'$$

DeMorgan's
 
$$F = (AB + CD + BD')' = (A' + B')(C' + D')(B' + D)$$




**Extra Example:**  $F(A, B, C, D) = \Sigma_m(3,9,11,12,13,14,15) + \Sigma_d(1,4,6)$

$$\bar{F} = \bar{X}\bar{Z} + \bar{W}X$$

DeMorgan's

$$F = (X+Z) \cdot (W+\bar{X})$$

 




What if the function was **given** as **product of maxterms**?

- 1) **Complement**  $F \rightarrow F'$  in **Sum-of Product** Form (SOP)
- 2) Mark  **$F'$  minterms'** squares with **0's** and the **remaining** squares with **1's**.

The map of **five** variables  $\rightarrow$  **two four** variable maps.


$F(A,B,C,D,E)$

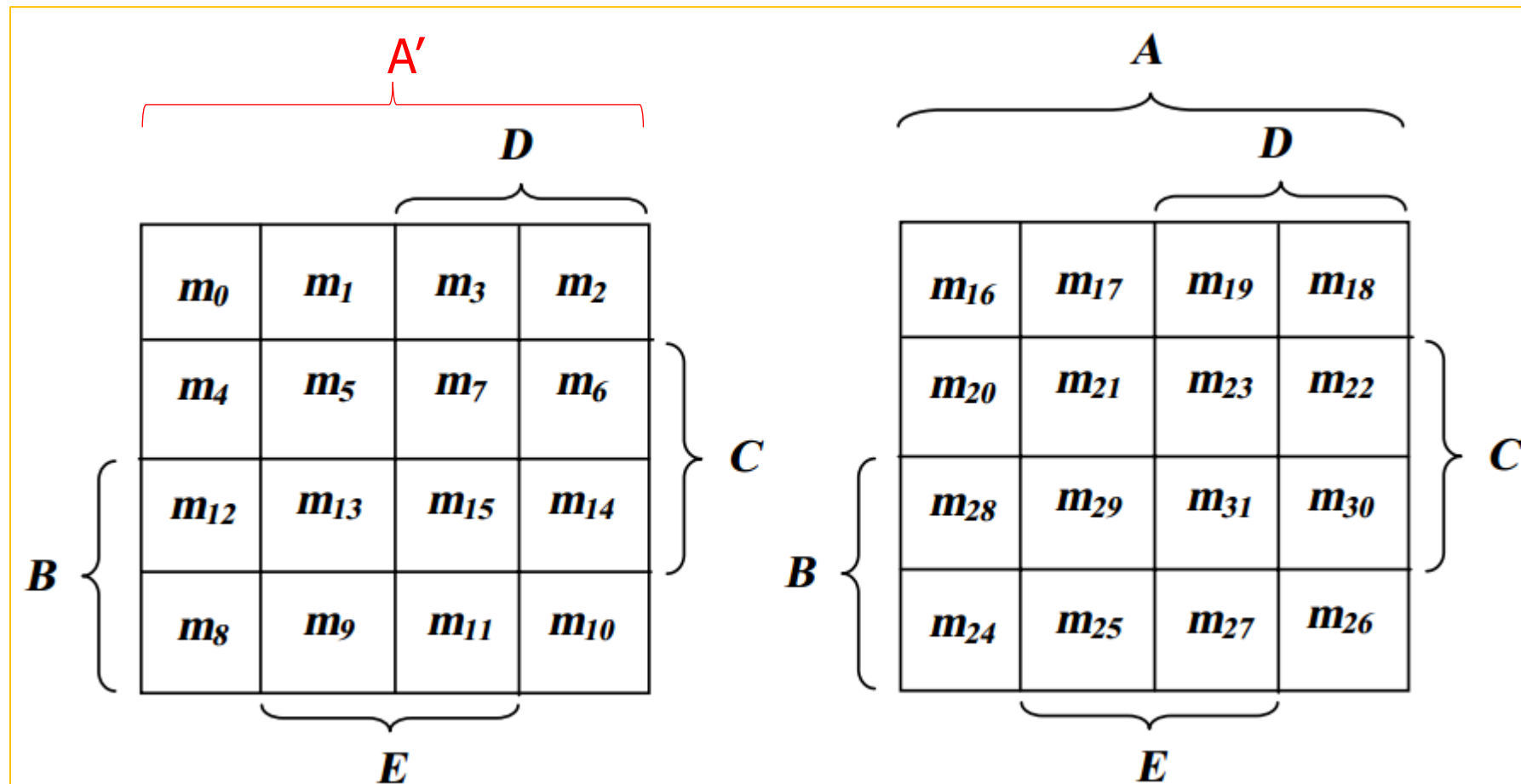



 
**Example:**

$$F(A, B, C, D, E) = \Sigma(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$



$$F(A, B, C, D, E) = A'B'E' + BD'E + ACE$$

5-Variables		
No. Cells	Literals	e.g.
1	5	ABCDE
2	4	BCDE
4	3	CDE
8	2	DE
16	1	E
32	Zero	F=1

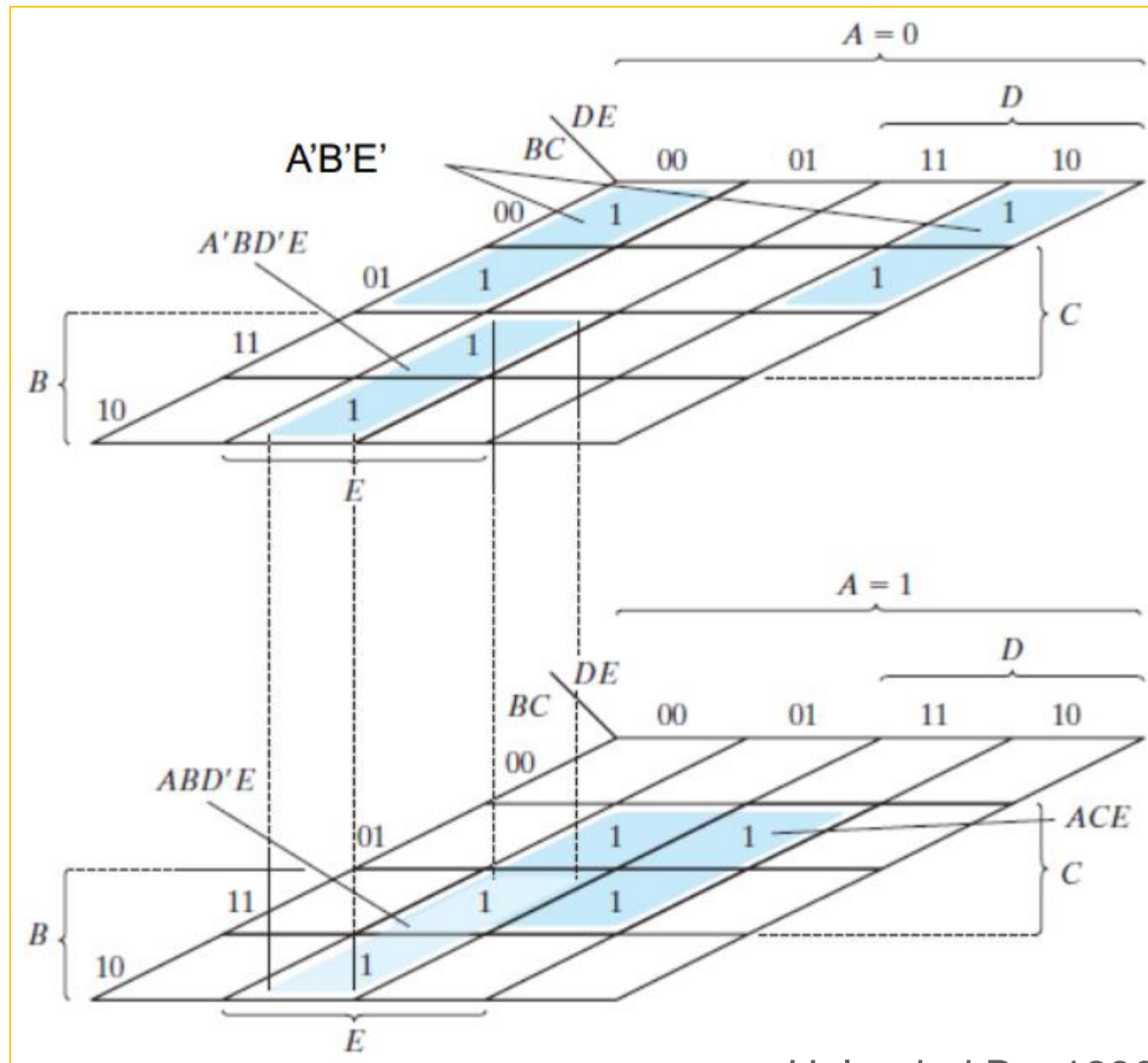
**Example:**




- ⊖ Digital circuits are frequently constructed with **NAND** or **NOR** gates rather than with AND or OR gates.
- ⊖ **NAND** and **NOR** gates are **easier to fabricate** with electronic components and are **the basic gates** used in all Integrated Circuit (IC) digital logic families.
- ⊖ NAND and NOR gates are **universal gates**
  - Ⓜ **Any** digital system can be **implemented** with **them**
- ⊖ To implement a function with **NAND** it need to be in **Sum-of Products** (SOP) form
- ⊖ To implement a function with **NOR** it need to be in **Product-of Sums** (POS) form

Rules have been developed to **convert** any logic circuit to its **equivalent** form in just **NAND gates or NOR gates**

## NAND Graphic Symbols

 

(a) AND-invert

 





(b) Invert-OR

- ⊖ **Both** Symbols are **same** because of **DeMorgan's theorem**
- ⊖ Circuits could be **drawn** using **any** of these symbols
- ⊖ When a circuit uses **both** symbols it is said to follow **mixed notation**

- ⊖ A **set** of gates is **functionally complete** if **any** Boolean expression can be **realized** with **this set** of gates
- ⊖ **AND, OR, and inverter** is functionally complete
- ⊖ **Any** set of gates which can **implement** AND, OR and inverter is also functionally complete

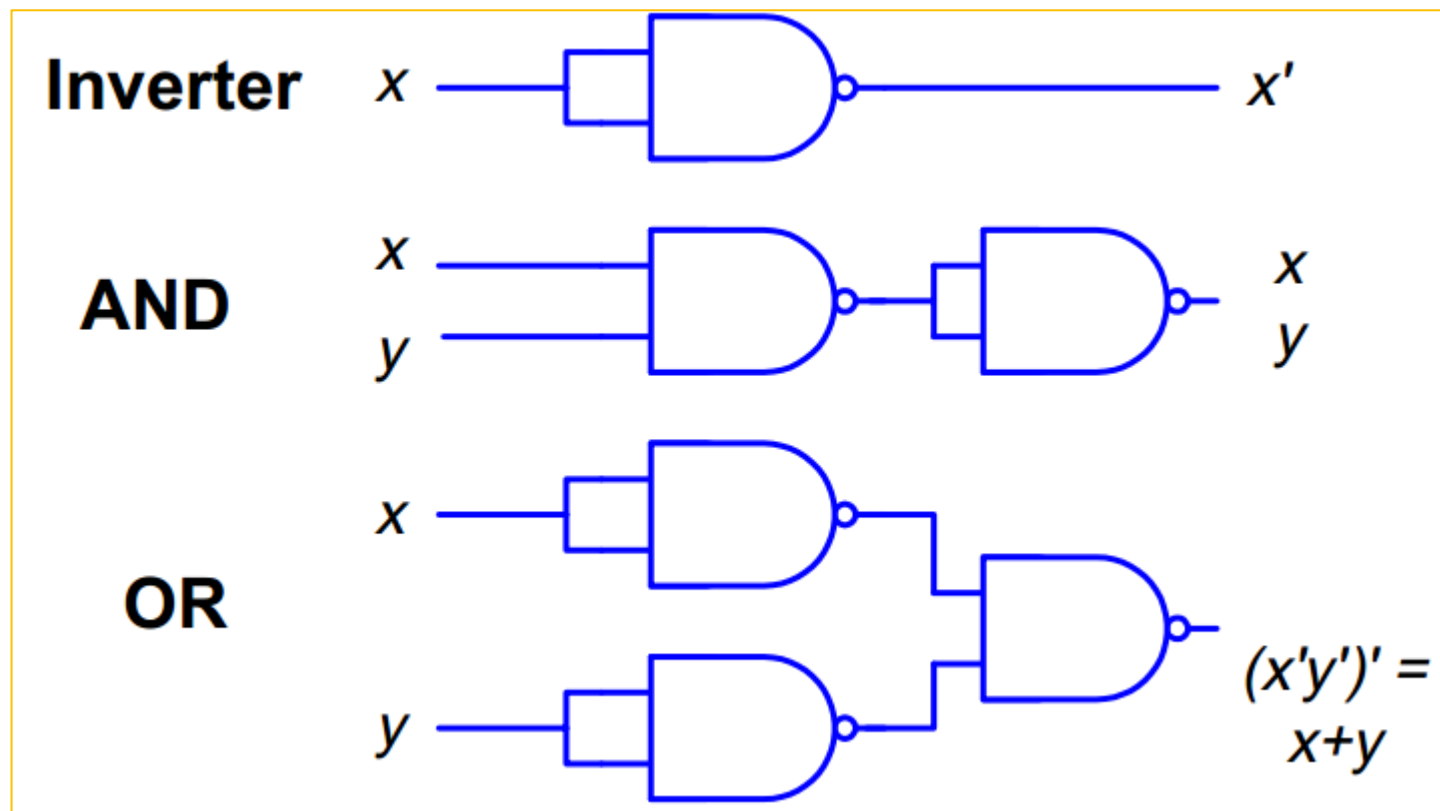**All gates can be represented using Only NAND gates → NAND is functionally complete**



  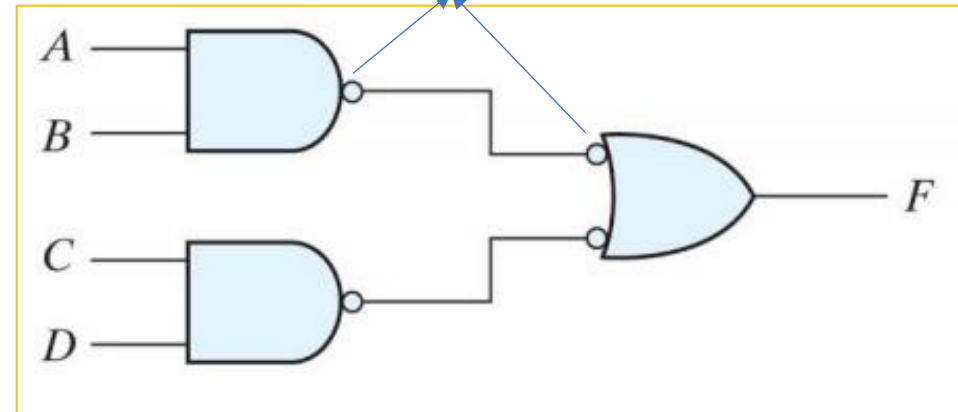**Example:**Implement  $F = AB + CD$ , using NAND gates**Inverts on same line cancel each others****Use the AND-Invert Form**






### ⊖ Two-level Implementation using NAND Gates

- 1) **Simplify** the function and express it in **sum-of-products** form.
- 2) Draw a **NAND gate** for **each product term** of the expression that has **at least two literals**. The inputs to each NAND gate are the literals of the term. This procedure produces a group of **first-level gates**.
- 3) Draw a **single gate** using the **AND-invert** or the **invert-OR** graphic symbol in the **second level**, with **inputs** coming from outputs of **first-level gates**.
- 4) A term with a **single literal** requires an inverter in the first level. However, if the single literal is **complemented**, it can be connected **directly** to an input of the **second level NAND gate**.

   **Example:**

Implement  $F(x, y, z) = (1, 2, 3, 4, 5, 7)$  with NAND gates





**Example:**


$$F(a, b, c, d) = \sum m(3, 5, 7, 9, 10, 12, 13) + \sum d(0, 1, 6, 11, 15)$$

Find SOP


		cd			
	ab	00	01	11	10
00	X	X	1		
01		1	1		X
11	1	1	X		
10		1	X	1	

$$F = d + abc' + ab'c$$

Draw Logic Gates

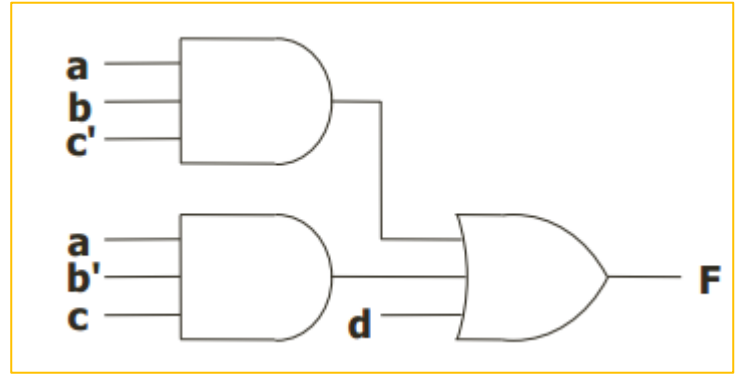

Convert to NANDs

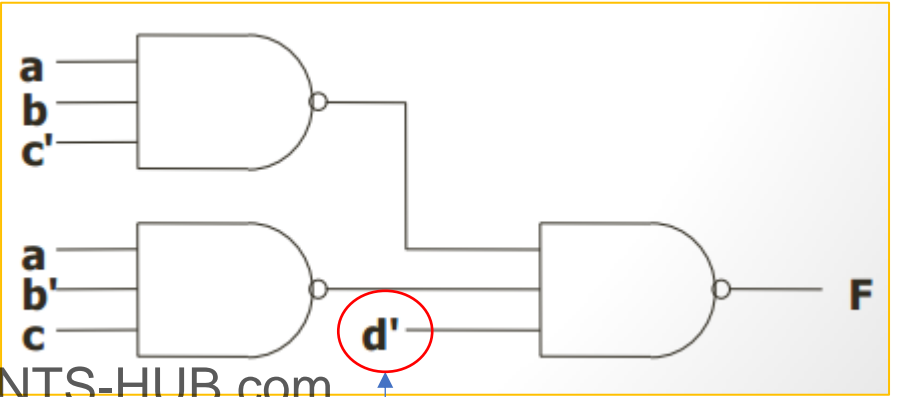

When Converting to NAND, Don't forget to **complement** the **direct** inputs (Single Literals)




⊖ The general procedure for converting a **multilevel** AND–OR diagram into an **all-NAND** diagram using **mixed notation** is as follows:


- 1) **Convert** all AND gates to NAND gates with **AND-invert** graphic symbols.
- 2) **Convert** all OR gates to NAND gates with **invert-OR** graphic symbols.
- 3) **Check** all the bubbles in the diagram. For every **bubble** that is not compensated by another **small circle (bubble)** along the same line, **insert an inverter** (a one-input NAND gate) **or complement the input literal**.

**Example:**

$$F = (AB' + A'B)(C + D')$$

 


(a) AND-OR gates

 


(b) NAND gates

The **NOR** operation is the **dual** of the **NAND** operation. Therefore, all procedures and rules for NOR logic are the **duals** of the corresponding procedures and rules developed for NAND logic

## NOR Graphic Symbols

 


(a) OR-invert

 

 (b) Invert-AND

- ⊖ **Both** Symbols are **same** because of **DeMorgan's theorem**
- ⊖ Circuits could be **drawn** using **any** of these symbols
- ⊖ When a circuit uses **both** symbols it is said to follow **mixed notation**

All gates can be **represented** using Only **NOR** gates  $\rightarrow$  NOR is **functionally complete**




Logic Operations with NOR gates

**Example:**


$$F = (A + B)(C + D)E$$

**Simplify** the function and express it in **product-of-soms** form

 **Inverts on same line cancel each others**





**Use the OR-Invert Form**

 


When Converting to NOR, Don't forget to **complement** the **direct** inputs (Single Literals)

**Extra Example:**

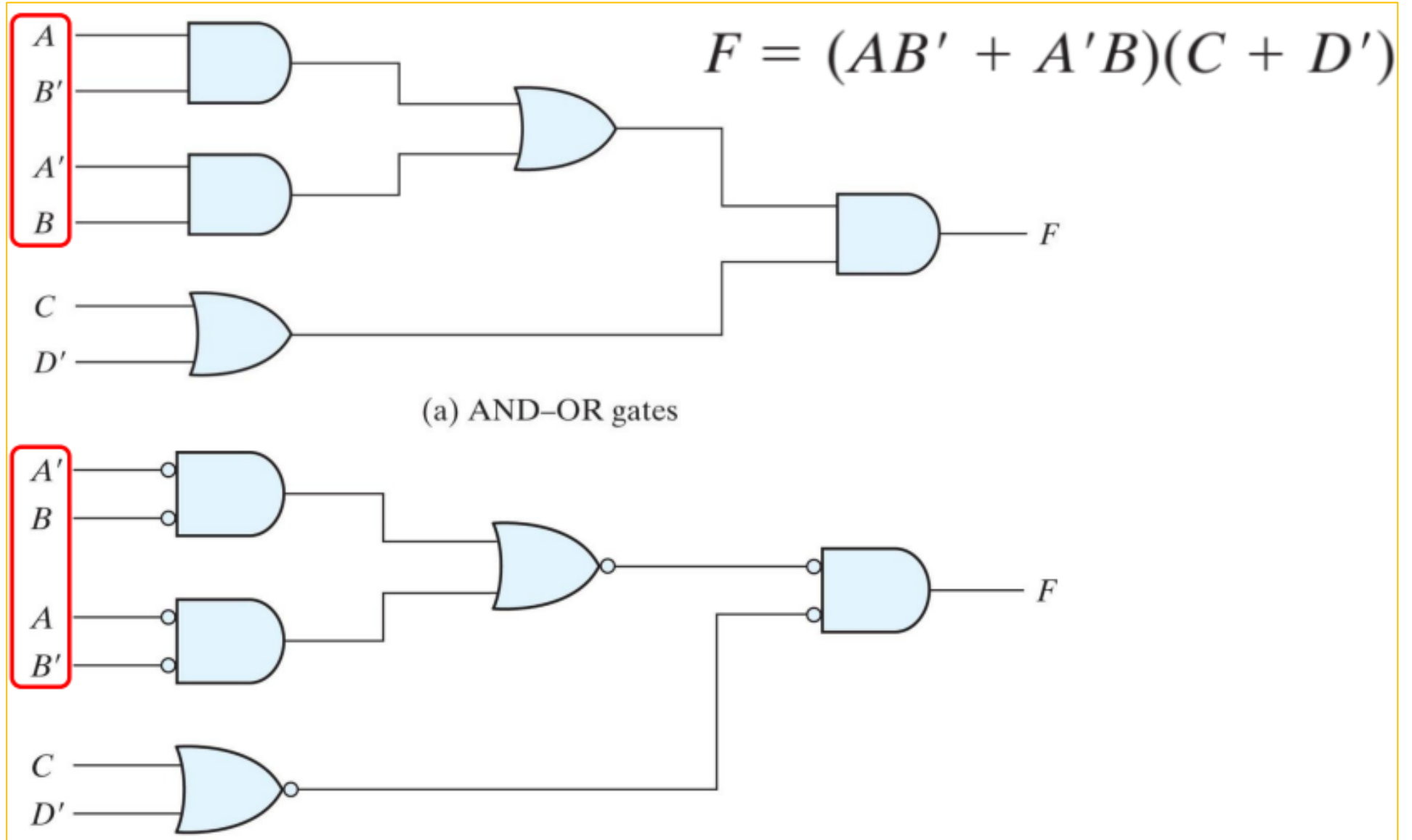

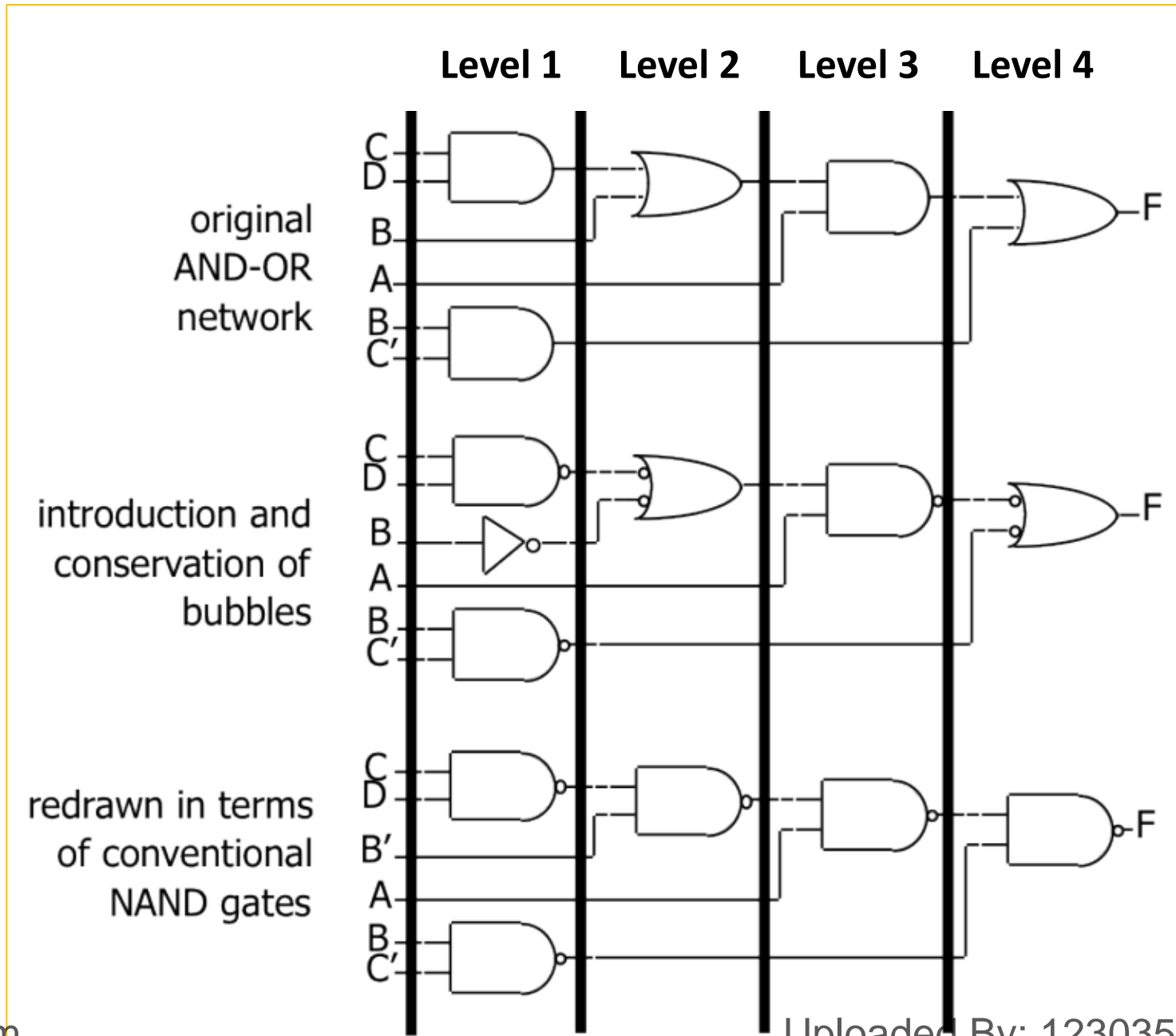



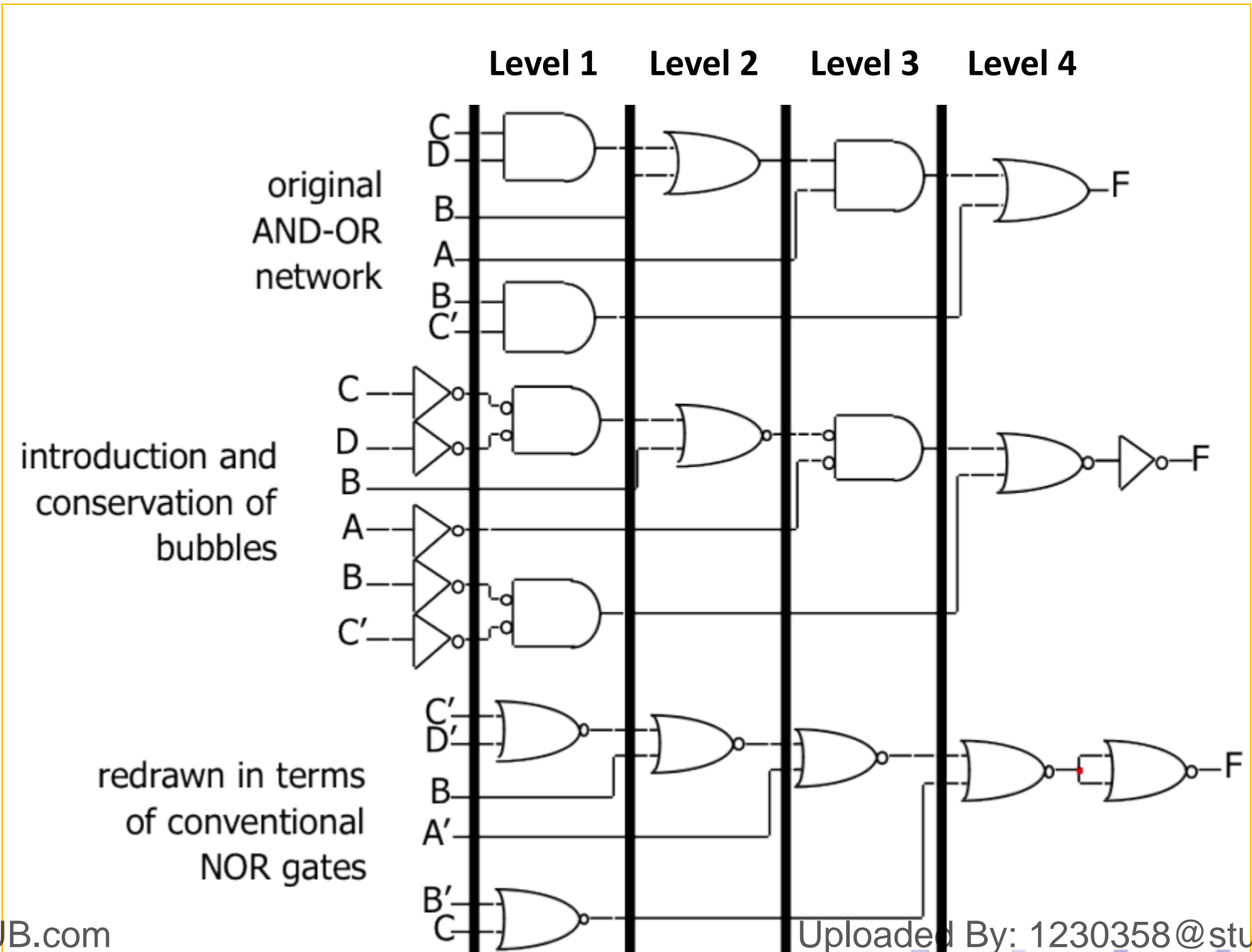



- ⊖ SOP and POS are **basic** forms of expressing functions
- ⊖ These functions can be implemented in **different** ways
- ⊖ So far, we have seen **multiple** ways of implementing the SOP and POS expressions
  - ✓ SOP can be represented as **two-level AND-OR** logic
  - ✓ SOP can be represented as **two-level NAND-NAND** logic
  - ✓ POS can be represented as **two-level OR-AND** logic
  - ✓ POS can be represented as **two-level NOR-NOR** logic

How many **two-level** logics may be formed using the **four** types of gates (AND, OR, NAND, NOR)?

**$2^4 \rightarrow 16$  Ways**



How many **two-level** logics may be formed using the **four** types of gates (AND, OR, NAND, NOR)?

**2<sup>4</sup> → 16 Ways**

- AND-AND
- AND-NAND
- OR-OR
- OR-NOR
- NAND-OR
- NAND-NOR
- NOR-AND
- NOR-NAND

**8 Degenerate**

degenerate to a **single operation** → **Straightforward**


- AND-OR
- OR-AND
- NAND-NAND
- NOR-NOR
- NAND-AND
- AND-NOR
- OR-NAND
- NOR-OR

**Already Covered**


**Covered Next**

**8 NonDegenerate**

## AND-AND

 


$$(AB)(CD) = ABCD$$

 


$$\Rightarrow \text{AND-AND} \equiv \text{AND}$$

## OR-OR

 


$$(A + B) + (C + D) = A + B + C + D$$

 


$$\Rightarrow \text{OR-OR} \equiv \text{OR}$$

## AND-NAND

 

 
$$\overline{(AB)(CD)} = \overline{ABCD}$$




$\Rightarrow$  AND-NAND  $\equiv$  NAND

## OR-NOR

 

 
$$\overline{(A + B) + (C + D)} = \overline{A + B + C + D}$$




$\Rightarrow$  OR-NOR  $\equiv$  NOR

## NOR-NAND

 

 
$$\begin{aligned} ((\overline{A+B})(\overline{C+D}))' &= \\ (\overline{A} \overline{B} \overline{C} \overline{D})' &= A+B+C+D \end{aligned}$$




⇒ NOR-NAND ≡ OR

## NAND-NOR

 

 
$$(\overline{AB} + \overline{CD})' = ABCD$$




⇒ NAND-NOR ≡ AND

## NOR-AND

 

 
$$\frac{\overline{(A + B)} \overline{(C + D)}}{\overline{(A + B) + (C + D)}} = \frac{A + B + C + D}{A + B + C + D}$$




⇒ NOR-AND ≡ NOR

## NAND-OR

 
 
$$\frac{\overline{(AB)} + \overline{(CD)}}{\overline{(AB)(CD)}} = \frac{ABCD}{ABCD}$$



⇒ NAND-OR ≡ NAND



OR-AND	AND-OR
NOR-NOR	NAND-NAND
NAND-AND	NOR-OR
AND-NOR	OR-NAND


- ⊖ The **first** gate listed in each of the forms constitutes a **first level** implementation.
- ⊖ The **second** gate listed is a single gate placed in the **second level**.
- ⊖ Note that any **two forms** listed in the same line are **duals** of each other.
- ⊖ The **green** four forms have been investigated **previously**.
- ⊖ The **red** four forms are investigated **next**.



**AND-OR-INVERT** Implementation

- ⊖ The two forms **NAND-AND** and **AND-NOR** are equivalent forms and can be treated together
- ⊖ Both perform the **AND-OR-INVERT** function
- ⊖ The **AND-OR-INVERT** implementation is similar to **AND-OR** (SOP), **except** for the **inversion**


$$F = (AB + CD + E)'$$

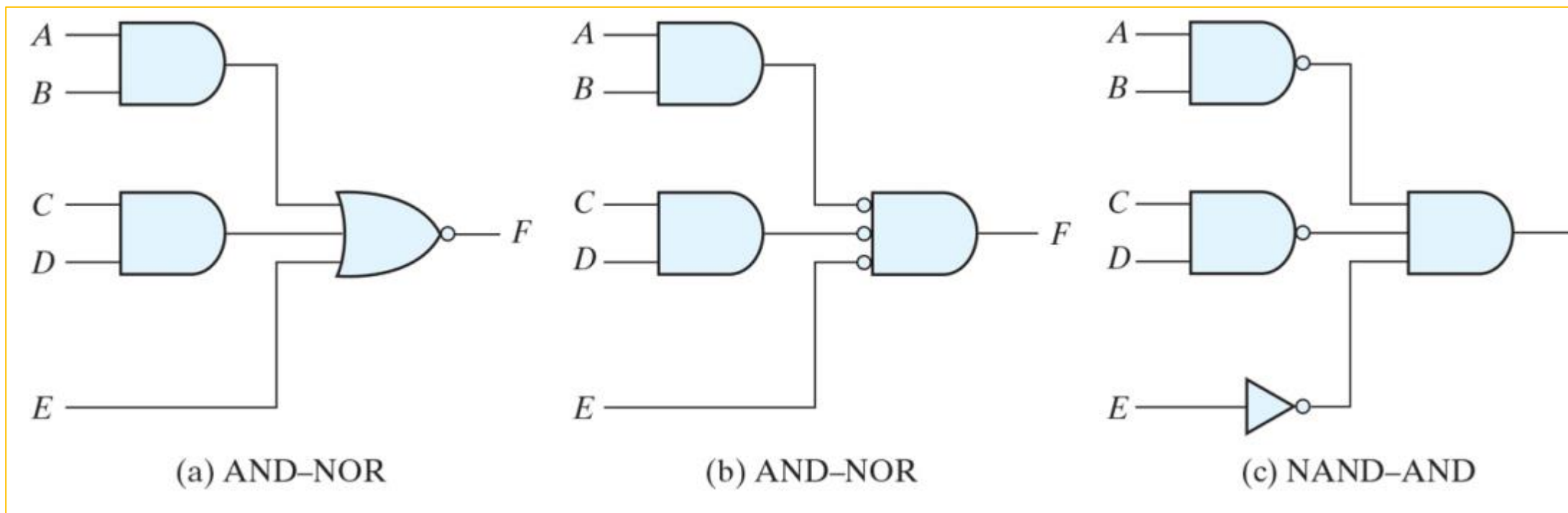

**OR-AND-INVERT** Implementation

- ⊖ The two forms **OR-NAND** and **NOR-OR** are equivalent forms and can be treated together
- ⊖ Both perform the **OR-AND-INVERT** function
- ⊖ The **OR-AND-INVERT** implementation is similar to **OR-AND** (POS), **except** for the **inversion**

$$F = [ (A+B) (C+D) E ]'$$

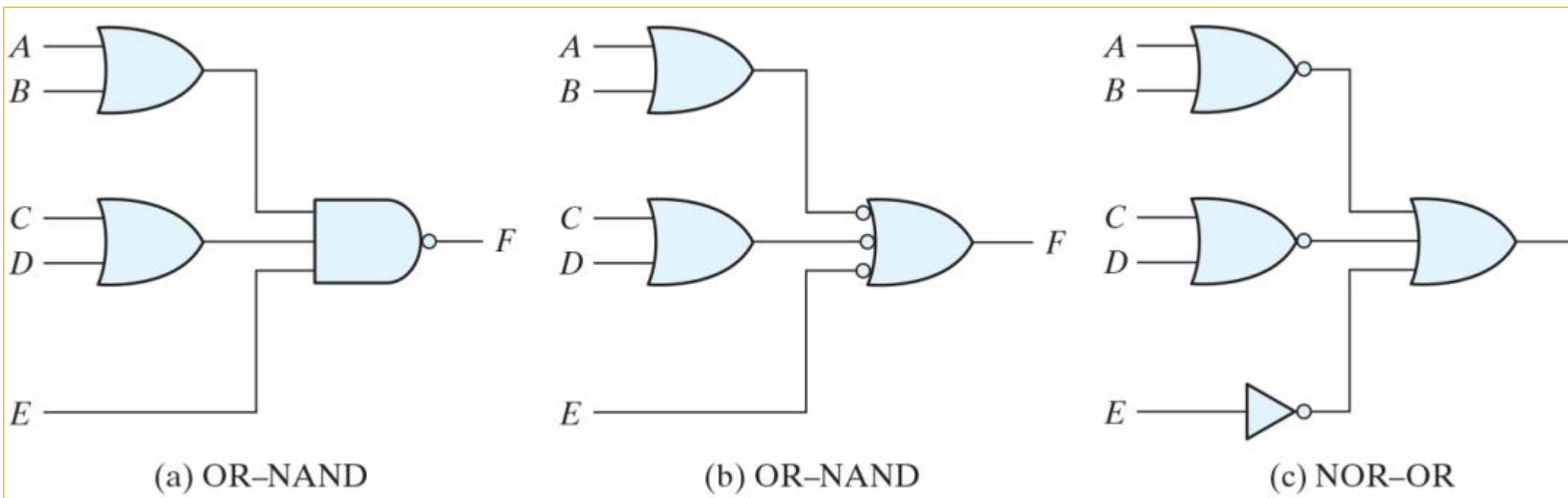

- ⊖ The following table summarizes the procedures for implementing a Boolean function in any one of the **four 2-level** forms: **NAND-AND**, **AND-NOR**, **OR-NAND** and **NOR-OR**

Equivalent Nondegenerate Implementation		Implements the Form	Simplify $F'$ into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	$F$

\*Form (b) requires an inverter for a single literal term.

- ⊖ Because of the **INVERT** part in each case, it is convenient if we find the **simplification of  $F'$**
- ⊖ When  $F'$  is implemented as an **AND-OR** or an **OR-AND** form, we can easily **get  $F$**  by simply **adding an INVERT at the end**. This will give us the circuit in one of the above-mentioned forms



Implementation With **AND-NOR** and **NAND-AND**

$$F(x, y, z) = \Sigma(0, 6)$$

- 1) Find the **simplified** form of  $F'$ 
  - ✓ Form a K-map and **group 0's**  $\rightarrow$  SOP form of  $F'$
- 2) Implement  $F'$  in a two-level **AND-OR** form
- 3) By adding a **NOT** gate at the output, we get  $F$ 
  - ✓ The resulting form is **AND-OR-INVERT** form which can be easily converted to get **AND-NOR** and **NAND-AND** forms

		$y$			
		$yz$ 00	01	11	10
$x$	0	1	0	0	0
	1	0	0	0	1

$$F' = x'y + xy' + z$$

  

Remember: We always get a **SOP** from the K-map

$$F = (x'y + xy' + z)'$$

Implementation With **OR-NAND** and **NOR-OR**

$$F(x, y, z) = \Sigma(0, 6)$$

- 1) Find the **simplified** form of **F**
  - ✓ Form a K-map and **group 1's** → SOP form of **F** → find **F'** by taking the **complement** of **F**
- 2) Implement **F'** in a two-level **OR-AND** form
- 3) By adding a **NOT** gate at the output, we get **F**
  - ✓ The resulting form is **OR-AND-INVERT** form which can be easily converted to get **OR-NAND** and **NOR-OR** forms


		y			
		00	01	11	10
x	0	$m_0$ 1	$m_1$ 0	$m_3$ 0	$m_2$ 0
	1	$m_4$ 0	$m_5$ 0	$m_7$ 0	$m_6$ 1

Labels:  $x'y'z'$  (pointing to  $m_0$ ),  $xyz'$  (pointing to  $m_6$ ),  $z$  (under  $m_0, m_1, m_4, m_5$ ),  $x$  (left of  $m_0, m_4$ )

$$F = x'y'z' + xyz'$$



$$F' = (x + y + z)(x' + y' + z)$$

 

$$F = [(x + y + z)(x' + y' + z)]'$$

Form	SOP from K-map? DeMorgan Invert?	Gate Type	Procedure
AND-OR (AO)	F No	AND-OR = NAND-NAND (SOP)	Circle <b>1's</b> in the K-Map and minimize
AND-OR-INVERT (AOI)	<b>F'</b> No	AND-NOR = NAND-AND (SOP <b>Invert</b> )	Circle <b>0's</b> in the K-Map and minimize
OR-AND (OA)	<b>F'</b> Yes	OR-AND = NOR-NOR (POS)	Circle <b>0's</b> in the K-Map and minimize SOP. Use <b>DeMorgan's</b> to transform to POS
OR-AND-INVERT (OAI)	F Yes	OR-NAND = NOR-OR (POS <b>Invert</b> )	Circle <b>1's</b> in the K-Map and minimize SOP. Use <b>DeMorgan's</b> to transform to POS.

Remember: We always get a **SOP** from the K-map




Level 1	Level 2	Equivalent	Final Form	Remarks
AND	AND	AND-AND	AND	Degenerate
AND	OR	AND-OR	<b>SOP</b>	
AND	NAND	AND-AND-NOT	AND-NOT	Degenerate
AND	NOR	AND-OR-NOT	<b>SOP-INVERT</b>	
OR	AND	OR-AND	<b>POS</b>	
OR	OR	OR-OR	OR	Degenerate
OR	NAND	OR-AND-NOT	<b>POS-INVERT</b>	
OR	NOR	OR-OR-NOT	OR-NOT	Degenerate
NAND	AND	AND-NOT-NOT-NOR	<b>SOP-INVERT</b>	
NAND	OR	NOT-OR-OR	NOT-OR	Degenerate
NAND	NAND	AND-NOT-NOT-OR	<b>SOP</b>	
NAND	NOR	AND-NOT-NOT-AND	AND	Degenerate
NOR	AND	NOT-AND-AND	NOT-AND	Degenerate
NOR	OR	OR-NOT-NOT-AND-NOT	<b>POS-INVERT</b>	
NOR	NAND	OR-NOT-NOT-OR	OR	Degenerate
NOR	NOR	OR-NOT-NOT-AND	<b>POS</b>	



 - ⊖ The **Exclusive-OR (XOR)** function is an important Boolean function used **extensively** in logic circuits.
- ⊖ Implemented **directly** as an electronic circuit (true gate) or implemented by **interconnecting other** gate types.
- ⊖ The **Exclusive-NOR (XNOR)** function, also known as **equivalence** function, is the **complement** of the **XOR** function.




**XOR**

$$z = x \oplus y$$

$$= x \bar{y} + \bar{x} y$$

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

The result is 1 only when X and Y are NOT equal (**Not equivalent**).

 **XNOR**

$$z = x \odot y$$

$$= \bar{x} \bar{y} + x y$$

x	y	$x \odot y$
0	0	1
0	1	0
1	0	0
1	1	1

$$\text{XOR: } x \oplus y = xy' + x'y$$

$$\text{XNOR: } (x \oplus y)' = xy + x'y'$$

$$x \oplus 0 = x, x \oplus 1 = x'$$



$$x \oplus x = 0, x \oplus x' = 1$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$


$$x \oplus y = y \oplus x \quad \text{Commutative}$$

$$(x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z \quad \text{Associative}$$

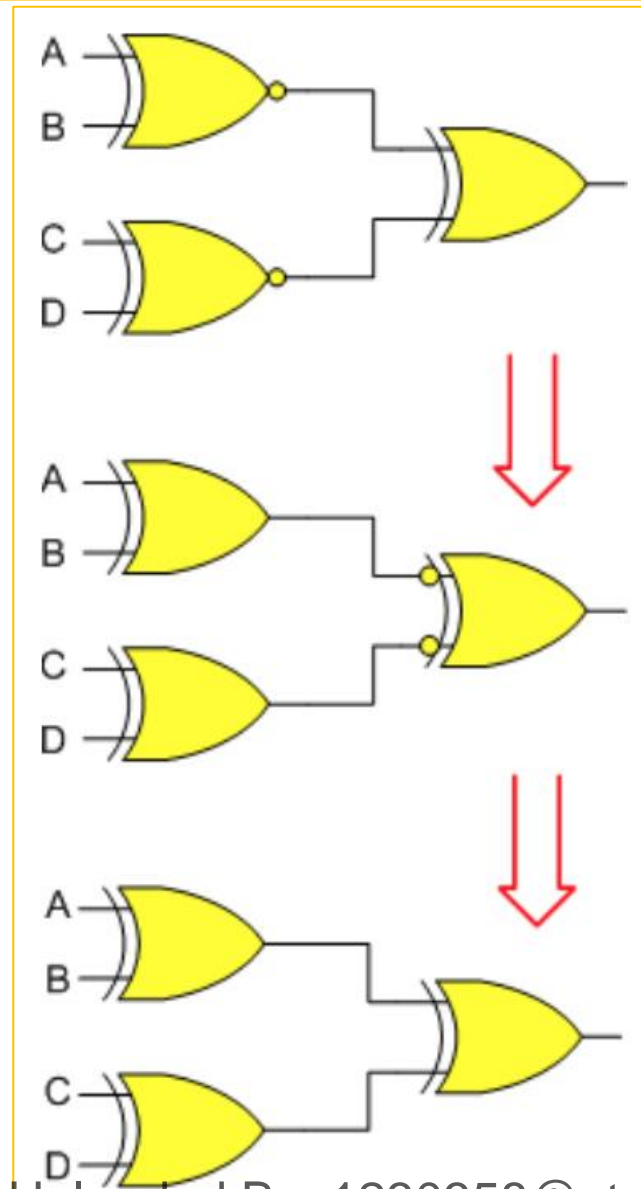 
$$(A \odot B) \oplus (C \odot D) = A \oplus B \oplus C \oplus D$$



 - ⊖ Multi-input XOR gates are **difficult** to fabricate with hardware
- ⊖ Even a two-input gate is usually **constructed** with **other** types of gates



(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

⊖ The exclusive-OR operation with three or more variables can be expressed as:

$$\begin{aligned}
 & A \oplus B \oplus C \\
 &= (AB' + A'B)C' + (AB + A'B')C \\
 &= AB'C' + A'BC' + ABC + A'B'C \\
 &= \sum(1, 2, 4, 7) \longrightarrow \left\{ \begin{array}{l} 001 \\ 010 \\ 100 \\ 111 \end{array} \right.
 \end{aligned}$$

⊖ The multiple-variable exclusive-OR operation is defined as an **odd function** ('1' when **odd** number of **variables** are equal to **1**)

$A$	$B$	$C$	$A \oplus B \oplus C$	
0	0	0	0	
0	0	1	1	Odd number of 1's
0	1	0	1	Odd number of 1's
0	1	1	0	
1	0	0	1	Odd number of 1's
1	0	1	0	
1	1	0	0	
1	1	1	1	Odd number of 1's

⊖ The complement of an **odd** function is an **even** function

$$(A \oplus B \oplus C)' = \Sigma(0, 3, 5, 6)$$

$A$	$B$	$C$	$(A \oplus B \oplus C)'$	
0	0	0	1	Even number of 1's
0	0	1	0	
0	1	0	0	
0	1	1	1	Even number of 1's
1	0	0	0	
1	0	1	1	Even number of 1's
1	1	0	1	Even number of 1's
1	1	1	0	

		$B$			
		$BC$			
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		00	01	11	10
		$C$			

(a) Odd function  $F = A \oplus B \oplus C$

		$B$			
		$BC$			
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		00	01	11	10
		$C$			



(b) Even function  $F = (A \oplus B \oplus C)'$

		$C$			
		$CD$			
$A$	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$
		00	01	11	10
		$D$			
		$B$			

(a) Odd function  $F = A \oplus B \oplus C \oplus D$


		$C$			
		$CD$			
$A$	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$
		00	01	11	10
		$D$			
		$B$			

 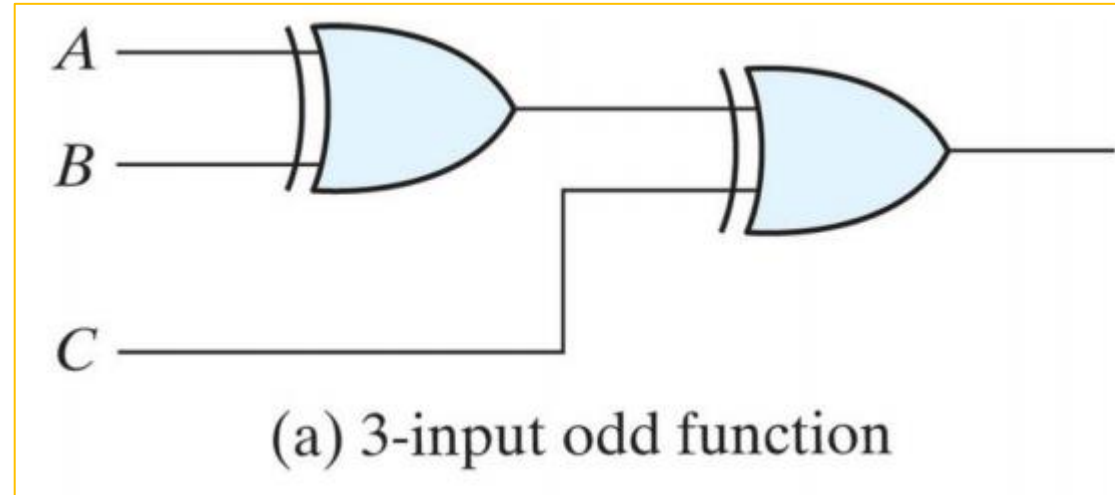(b) Even function  $F = (A \oplus B \oplus C \oplus D)'$





- ⊖ A **parity bit** is an extra bit included with a binary message to make the **number of 1's** either **odd or even**.
- ⊖ Parity bit is used for the purpose of **detecting errors** during the transmission of binary information.
- ⊖ The circuit that **generates** the parity bit in the **transmitter** is called a **parity generator**.
- ⊖ The circuit that **checks** the parity in the **receiver** is called a **parity checker**.
- ⊖ **Exclusive-OR/NOR** gates (Odd/Even Functions) are useful for **generating and checking** a parity bit

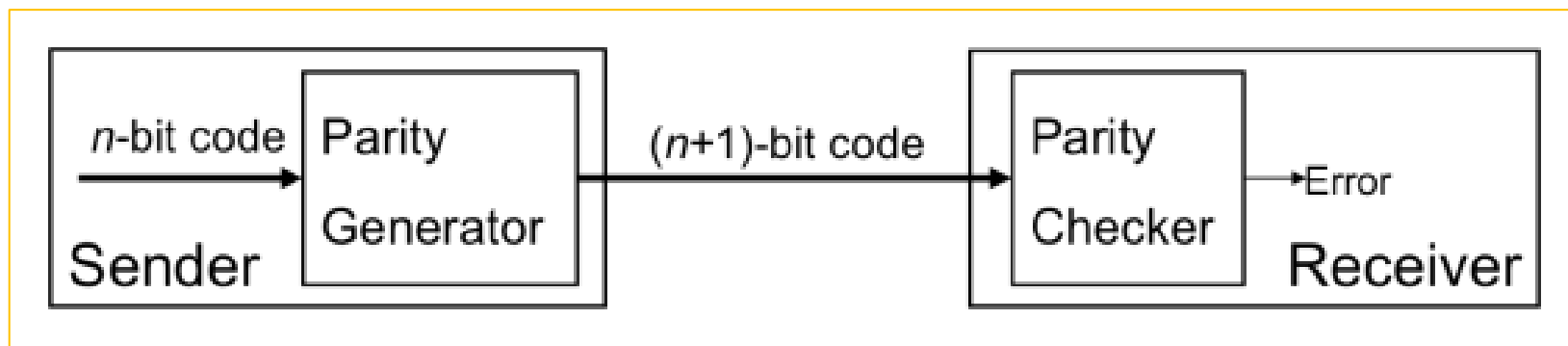


**Example:**

Transmitting a **3-bit** message with **even parity bit**. The three bits –  $x$ ,  $y$ , and  $z$  constitute the message and are the inputs to the circuit.  
The parity bit **P** is the **output**.

## Parity Generator

**P** is **Even parity** bit  $\rightarrow P = 1$  if the number of 1's in the 3-bit message is **odd**  $\rightarrow$   
**P** is an **odd function** and can be implemented using **3-Inputs XOR**

$$P = x \oplus y \oplus z$$

 


**Parity Generator**

Three-Bit Message			Parity Bit
$x$	$y$	$z$	$P$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## Parity Checker

- 1) The **three bits** in the message together with the **even** parity bit **P** are transmitted (**4 bits**)
- 2) The **receiver** at the destination checks for an **even** number of 1's in the **4-bit** message and generates an **error C** equal to 1 if the **number of 1's** in the message is **odd**
- 3) **C** (error) can be implemented using **XOR**

$$C = x \oplus y \oplus z \oplus P$$

 

Parity Checker

**C = 1 → Error**

Four Bits Received				Parity Error Check
x	y	z	P	C
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0