

Digital Systems (ENCS2340)  
 Section: 2

Instructor: Mohammed Khalil  
 SMW: 11 – 11:50

Quiz No.: (2)  
 Covered Material: (Chapter 4)


Date: December 11<sup>th</sup>, 2024  
 Pages/Questions: 2/2

Student Name	Student ID	Grade (out of 15)
ANSWER Key		


[Decoder] **Q1: Implement the following Boolean functions (Together):** {8 Mark}  
 (With **minimum** number of **inputs** in the external gates)

$$F_1(x, y, z) = \sum m(3, 5) \quad F_2(x, y, z) = \sum m(2, 4, 5, 6, 7)$$

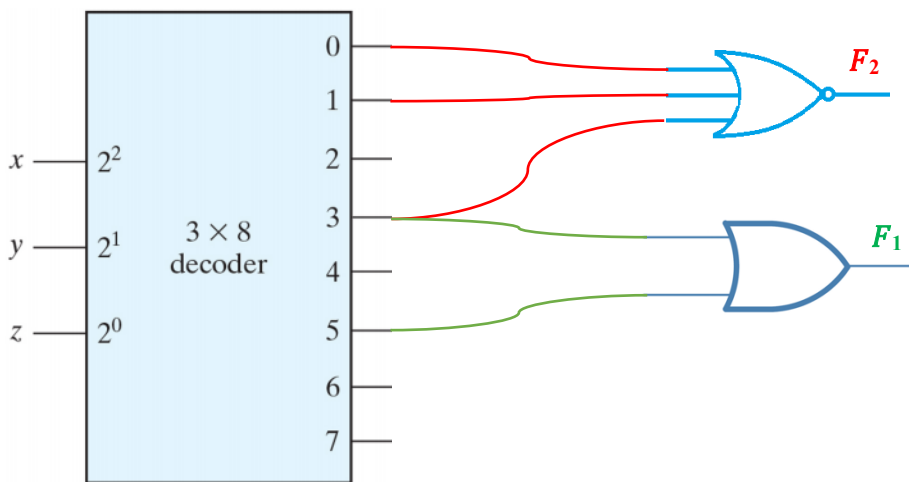[Easy] **A: Using 3x8 decoder constructed with AND gates (Active High)** {4 Mark}



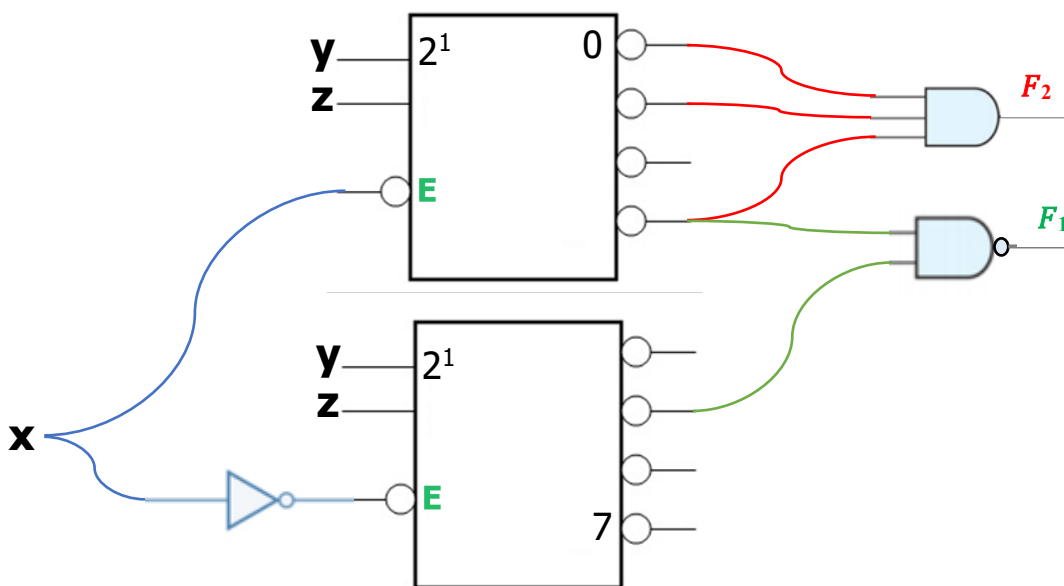
[Medium] **B: Using 2x4 decoders constructed with NAND gates (Active Low with Enable)** {4 Mark}



[MUX] Q2: Implement the following Boolean function: {7 Mark}

$$G(A, B, C) = \sum(0, 1, 3, 4)$$

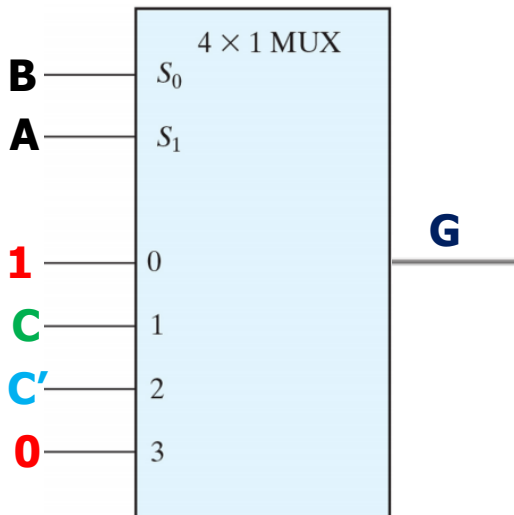[Easy] A: Using: 4-to-1 Multiplexer {4 Mark}



A	B	C	G
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

[Tricky] B: Using: 1-to-4 De-Multiplexer with one external gate {3 Mark}

Cannot be implemented as requested ( $G$  is neither 1, 0, nor any variable or its complement).