

Digital Systems

Section 2

Chapter (5)


☉ In Digital Systems, Logic circuits can be categorized as **combinational** or **sequential**

☉ **Combinational** Circuit

- ☐ Circuit made of **logic gates only** and perform an operation that can be specified logically by a set of Boolean functions.
- ☐ Circuit output at any time are determined **only by the current combination** (current state/value) of inputs.


☉ **Sequential** Circuit

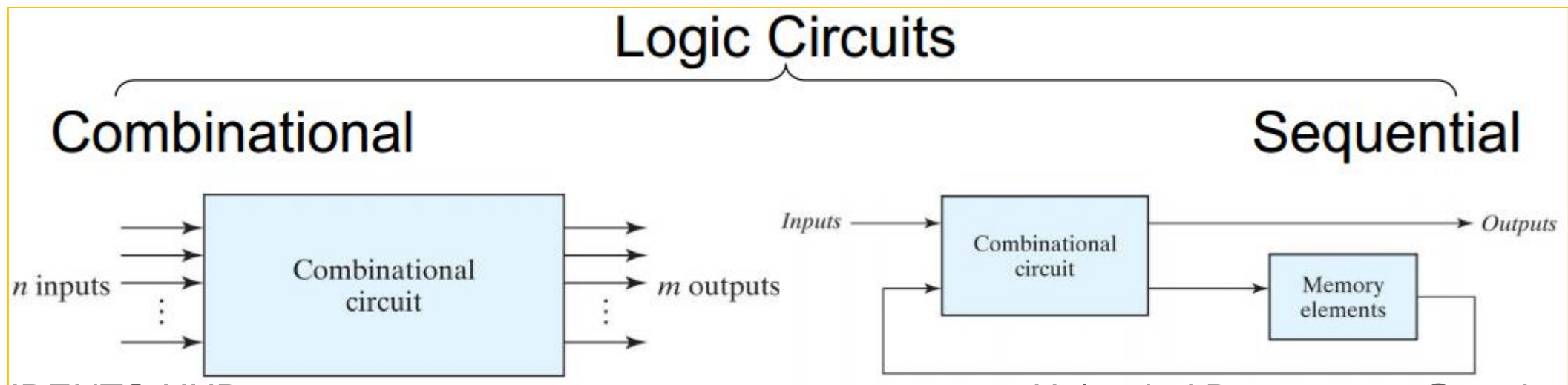- ☐ Circuit is made of **storage/memory** elements and **logic gates**.
- ☐ Circuit output depend on the current combination of inputs and **previously stored values**.




- ⊗ A **sequential** circuit consists of a **combinational** circuit to which **storage** elements are connected to form a **feedback** path.
 - Ⓜ It can **store, retain** and then **retrieve** this information
- ⊗ The **storage/memory** elements are devices capable of **storing** binary information
 - Ⓜ The **stored binary** information define the **current/present state** ($Q(t)$) of the sequential circuit at any given *time*.
- ⊗ A sequential circuit receives information from an **external inputs** as well as the **current/present state** of the **memory** elements to determine the **output** and **next state** ($Q(t+1)$).

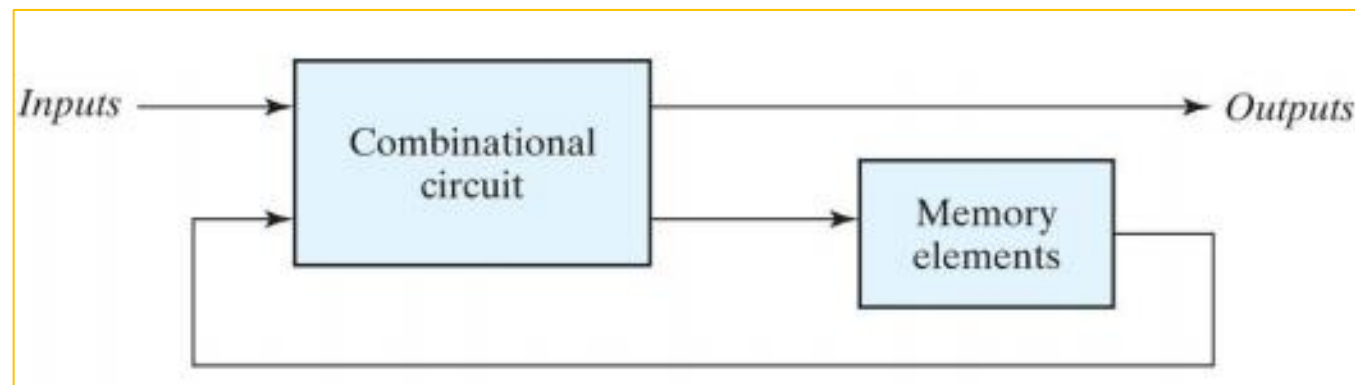
The **outputs** of the sequential circuit are **functions** of the **inputs** and the **present state** of the **memory** elements.



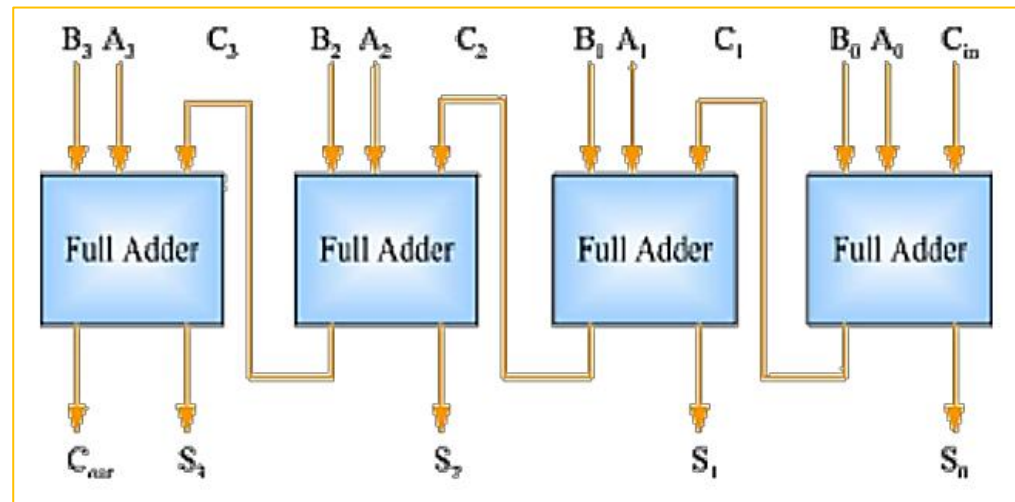🌀 The **combinational** circuit of a 4-bit binary adder comprises 4 full-adders



 🌀 The **sequential** circuit of a 4-bit binary adder comprises a full-adder and **memory**



- ⌚ A **sequential** circuit is specified by a **time sequence** of inputs, outputs, and **internal states**.
- ⌚ **Two** main **types** of sequential circuits based on the **timing** of their signals
 - ⌚ **Asynchronous** Sequential circuits: behavior depends on the **order** of **change** of **input** signals and can be affected at **any instant** of time [**Out of this Course Scope**]
 - ⌚ **Synchronous** Sequential Circuits - behavior is defined from the knowledge of signals at **discrete** instants of time.

⌚ **Synchronous** Sequential Circuit

- ⌚ Uses a **clock** signal as an additional **input**
- ⌚ Changes in the memory elements are **controlled** by the **clock**
- ⌚ Changes happen at **discrete** instances of time

⌚ **Asynchronous** Sequential Circuit


- ⌚ **No** clock signal
- ⌚ Changes in the memory elements can happen at **any** instance of time

⌚ Our focus will be on **Synchronous** Sequential Circuits

- ⌚ **Easier** to design and analyze compared to asynchronous sequential circuits


- ☉ Synchronous sequential circuits use a **clock** signal
- ☉ The clock signal is an **input** to the **memory** elements
- ☉ The clock **determines when** the **memory** should be **updated**
- ☉ The **present state** = **output** value of memory (**stored**)
- ☉ The **next state** = **input** value to memory (**NOT stored** yet)
- ☉ $Q(t) \rightarrow$ **present state**
- ☉ $Q(t+1) \rightarrow$ **next state**

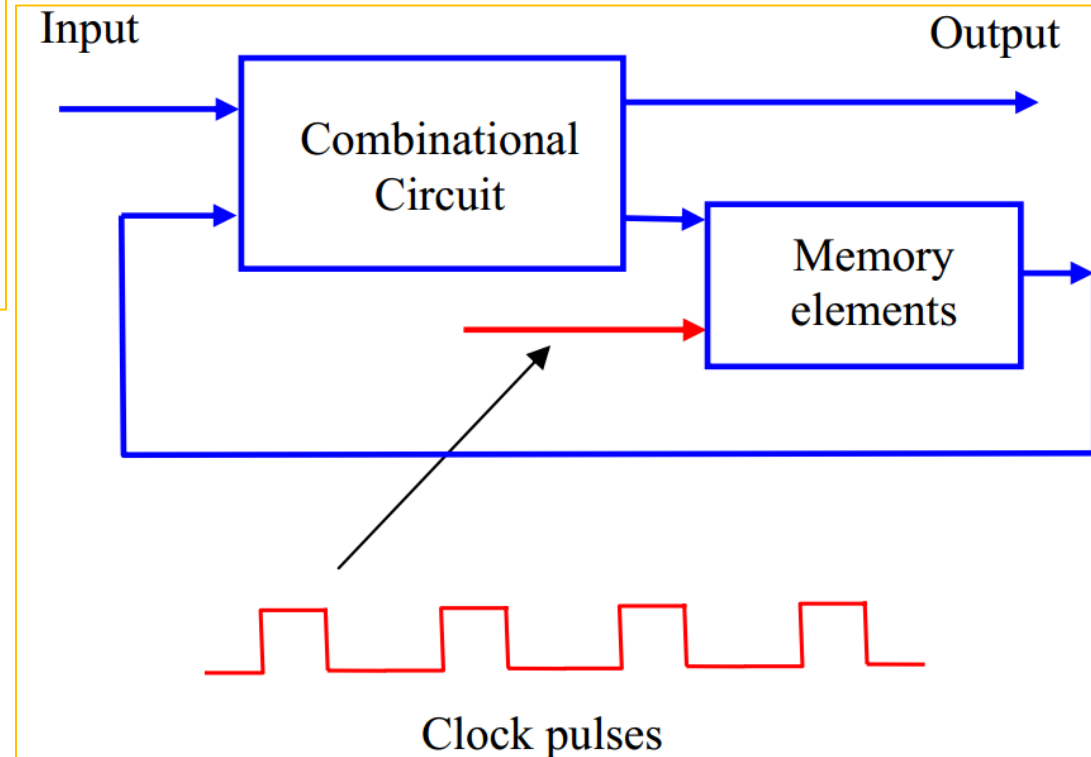Block Diagram of Synchronous Sequential Circuits





- ⌚ Clock generator provides a clock signal having the form of a **periodic** train of clock **pulses**
- ⌚ The clock determine **when computational activity will occur** in the circuit
 - ★ (Transition from $0 \rightarrow 1$, or $1 \rightarrow 0$)
- ⌚ The other signals (inputs and current state) determine **what changes** will take place affecting the **storage** elements and the **outputs**
- ⌚ **Synchronous** sequential circuits that **use clock pulses** to control storage elements are called **clocked sequential circuits**

 

🌀 T_{pos} = Time of the **positive** portion of the clock


🌀 T = **Duration** of a **complete** cycle

🌀 **Duty Cycle** = T_{pos} / T

★ 50% **duty** cycle divides the clock period into **half positive** and **half zero (negative)**

🌀 The **frequency** of the clock is $F=1/T$

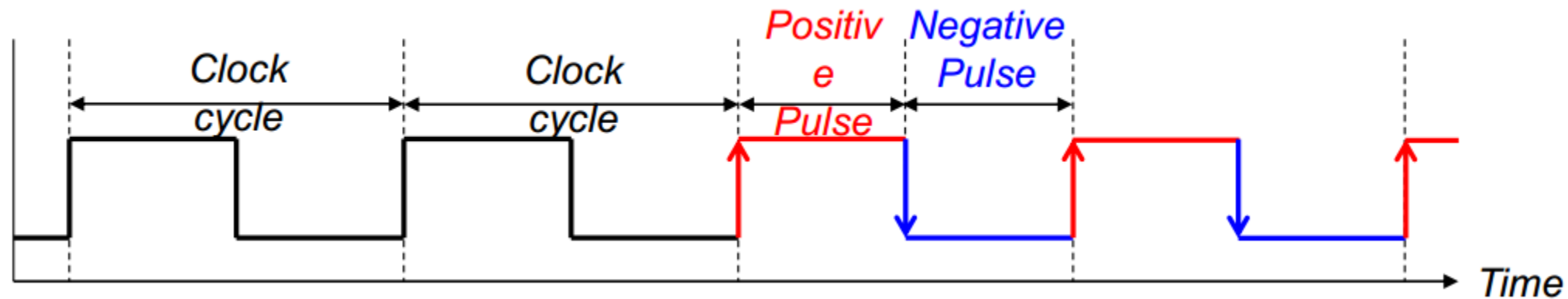★ Example: clock period (T) is **1ns** → frequency (F) is **1GHz**




- ⌚ Clock is a **periodic** signal = Train of **pulses** (1's and 0's)
 - 📌 The **same** clock **cycle repeats indefinitely** over time
- ⌚ **Positive** Pulse: when the level of the clock is **1**
- ⌚ **Negative** Pulse: when the level of the clock is **0**
- ⌚ **Rising** Edge (**Positive** Edge): when the clock **goes** from **0** to **1**
- ⌚ **Falling** Edge (**Negative** Edge): when the clock **goes** from **1** down to **0**


- Memory elements can **store and maintain** binary states (0's or 1's)
 - Until directed by an **input** signal to **change state** Or the **power** source is **lost**
- Main differences between memory elements are the **number** of **inputs** and **how** they **change** state
- Two main types:**
 - Latches** are **level-sensitive** (sensitive to the **level** of the clock)
 - Flip-Flops (FF)** are **edge-sensitive** (sensitive to the **edge** of the clock – **The Transition**)
- Flip-Flops (FF)** are the basic storage elements in **synchronous** sequential circuits
- A Flip-Flop (FF)** is made up of a **latch/latches** with **clock** control

One latch or flip-flop can **store one** bit of information

 Four main types of latches and flip-flops: **SR, D, JK, and T**



Latches

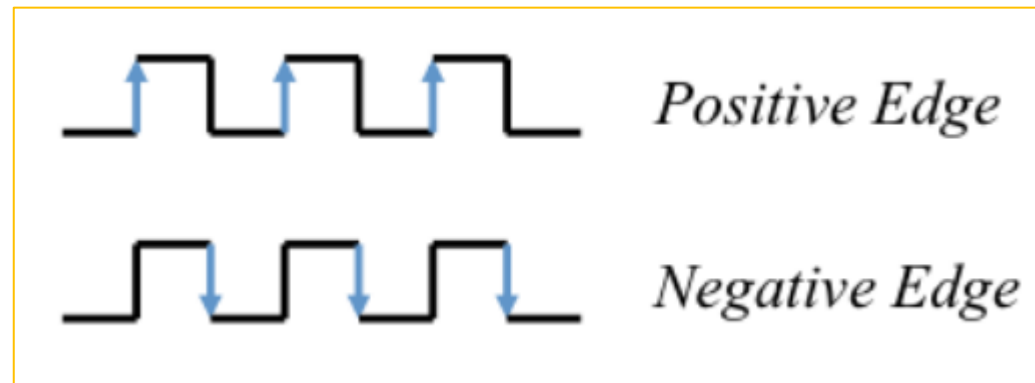

Flip Flops

- ⌚ A **latch** is a temporary binary storage element that can store 0 or 1
 - ⌚ Two **stable** states – **Bi-stable**
 - ⌚ Can “**remember**” **one** bit of information
- ⌚ **Latches** are the **basic** building blocks of more practical types of flip-flops
- ⌚ **Feedback** connection – **outputs** are **connected back** to the **inputs**
- ⌚ Easily **constructed** from a **pair** of **NOR** gates or a **pair** of **NAND** gates
- ⌚ Two types: **SR** Latch, **D** Latch

Two inputs: S (Set) and R (Reset)

Two outputs: Q and \bar{Q}

SR stands for **Set-Reset**


Two types of SR latches:

Active-**HIGH** input SR latch (two cross-coupled **NOR** gates)

Active-**LOW** input SR latch (two cross-coupled **NAND** gates)


Output of each gate is connected to an **input** of the **opposite** gate

$R \rightarrow Q$

 


NOR SR

$S \rightarrow Q$

 

NAND SR

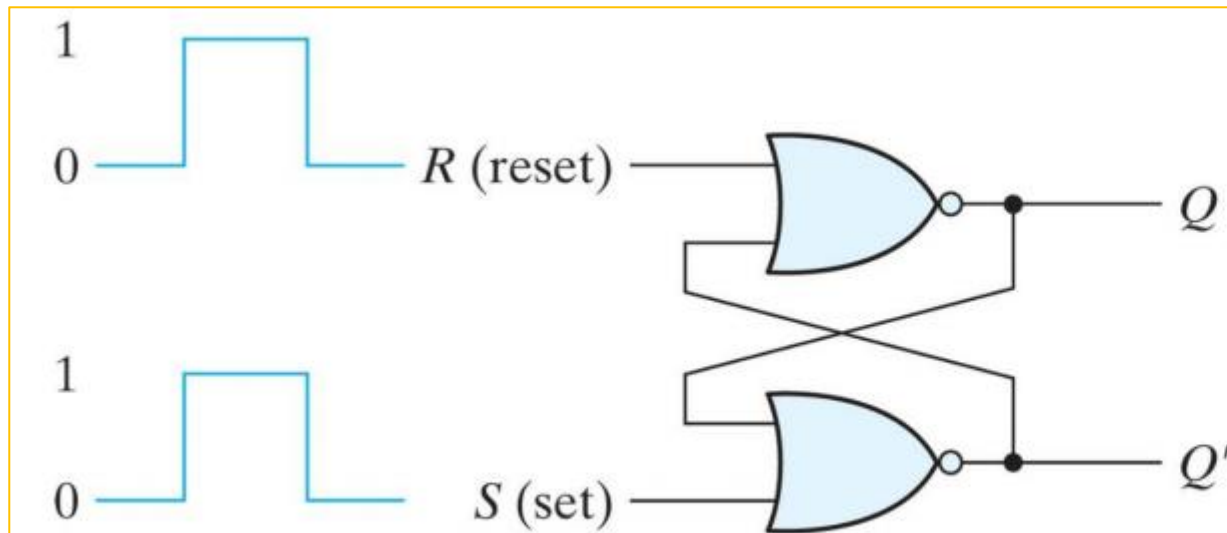

(a) Logic diagram

S	R	Q	Q'	
1	0	1	0	SET
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	RESET
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	(forbidden)

(b) Function table

If $S=1$ and $R=0$ then Set ($Q = 1, \bar{Q} = 0$)

If $S=0$ and $R=1$ then Reset ($Q = 0, \bar{Q} = 1$)

When $S = R = 0, Q$ and \bar{Q} are unchanged


The latch stores its outputs Q and \bar{Q} as long as $S=R=0$

When $S=R=1, Q$ and \bar{Q} are undefined (should never be used)

Active-High → **Set** when **S=1**
Reset when **R=1**

Set State → $Q = 1$
Reset State → $Q = 0$

 In **normal** operations, the outputs Q and Q' are always **complement** of each other



If $S = 0$ and $R = 1$ then Set ($Q = 1, \bar{Q} = 0$)

If $S = 1$ and $R = 0$ then Reset ($Q = 0, \bar{Q} = 1$)

When $S = R = 1$, Q and \bar{Q} are unchanged (remain the same)

The latch stores its outputs Q and \bar{Q} as long as $\bar{S} = \bar{R} = 1$


When $S = R = 0$, Q and \bar{Q} are undefined (should never be used)

Active-Low → **Set** when **S=0**
Reset when **R=0**


Set State → $Q = 1$
Reset State → $Q = 0$

In **normal** operations, the outputs Q and Q' are always **complement** of each other

- 🌀 An additional **Enable/Control** input signal **En** is used
- 🌀 Enable **controls when** the state of the latch can be **changed**
 - 1) $En=0 \rightarrow$ S and R inputs have **NO** effect on the latch [**Latch is Disabled**]
 - ★ The latch will remain in the same state, regardless of S and R
 - 2) $En=1 \rightarrow$ **normal** SR latch operation [**Latch is Enabled**]
- 🌀 **NOR SR** \rightarrow **AND** Gates are used with En
- 🌀 **NAND SR** \rightarrow **NAND** Gates are used with En [**Inverted Behavior**]

 

 $En = 0 \rightarrow$ Inputs to the NOR SR = 00 \rightarrow
NO Change




$En = 0 \rightarrow$ Inputs to the NAND SR (Right NAND) = 11
 \rightarrow NO Change

SR Latch with Enable Input – Gated SR Latch



 
Be Careful:
S & R is **Complemented** (Left NAND) →
Inverted Behavior for the latch



(a) Logic diagram


En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

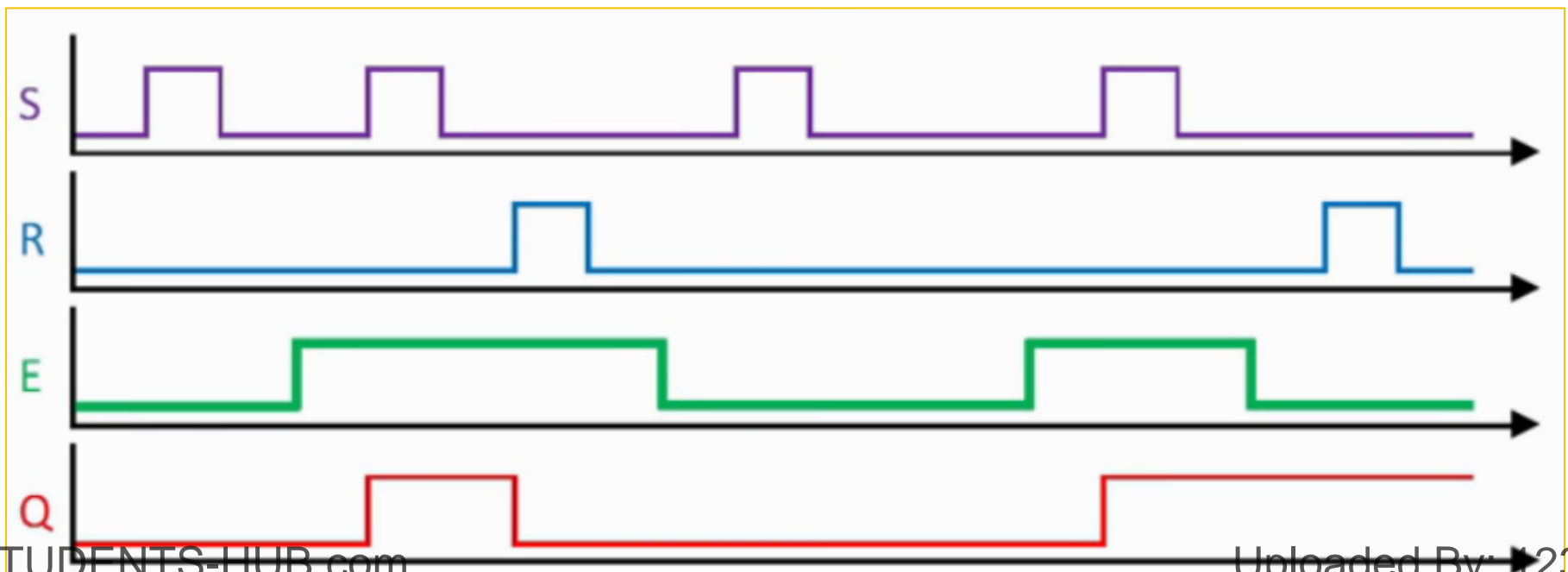

Timing Diagram Example


- ☯ All SR Latches have One Major **Issue** → Undefined/Indeterminant/Forbidden **State**
- ☯ This **undefined** state only exists when **both** inputs (S,R) are equal to 1/0 (depends on the used gates)
- ☯ A solution is to make sure that **both** inputs are **NOT** 1/0 at the **same time**, is to have a **single input only (D) → D Latch**
 - ★ Only one **data input D**
 - ★ An **inverter** is added: $S=D$ and $R=D'$
 - ★ S and R can **never** be 11/00 **simultaneously** → **No undefined state**
 - ★ When $En=0$, Q remains the same (No change in state), When $En=1$, $Q=D$ and $Q'=D'$
 - ★ It is also called a **transparent** latch because whatever appears at the D input follows at the Q output (**Q=D**)

 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

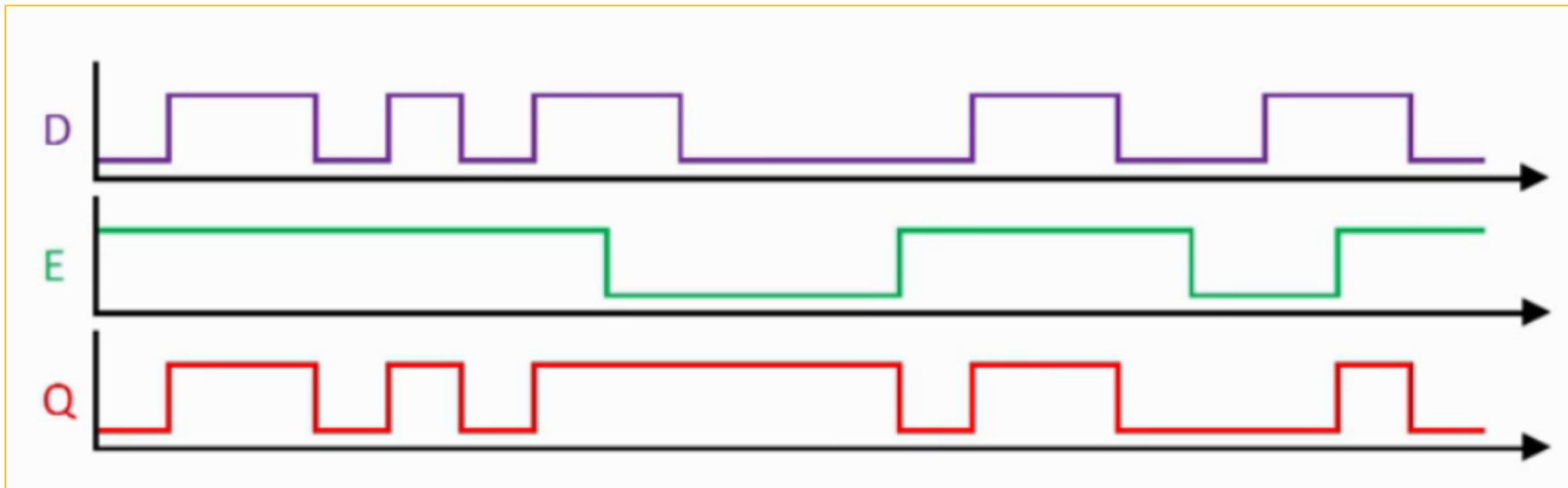

- ★ **Q follows D**
- ★ When $D = 1$, Q becomes 1 and so on
- ★ However, if the enable input E is 0, **Q will retain its state** (Q will not change, it will not follow D)
- ★ In short, if a D latch is **disabled** → it can **store/retain** one **data** bit (0 or 1)

 Active-**HIGH**Active-**Low**

Be Careful:
 Bubble @ **Output** → **Inverter** → Q'
 Bubble @ **Input** → **Active-Low**

Latches Summary

🌀 SR Latch

- 📌 SR latch with NOR gates (active **HIGH**)
- 📌 SR latch with NAND gates (active **LOW**)
- 📌 SR latch with enable/control input (**Gated** SR Latch)

🌀 D Latch (**Transparent** Latch)


- 🌀 A latch is **level-sensitive** (sensitive to the **level** of the **En**)
- 🌀 As long as the **enable** signal (control) is **high** then
 - ★ **Any change** in the value of **input D** **appears** in the **output Q**
- 🌀 Output Q **keeps changing** its **value** as long as the enable is **activated (high)**
 - ★ **Final** value of output Q is **uncertain**
- 🌀 Due to this **uncertainty**, latches are **NOT** used as memory elements in **synchronous** circuits
 - 🌀 Used mainly in **Asynchronous** circuits

- 🌀 To overcome these issues, a **synchronized** latch is needed **Flip-Flop (FF)**
 - 1) A Clock** Signal is connected to the **En** input → **Clocked** Latch (Synchronized **Level-Triggering**)
 - ★ The data might **change** while the clock is **HIGH**
 - 2) Construct** the clock in a way that **enable** the latch/FF for a **very small amount** of time
 - ★ At signal **transition only** [clock edge] → **Edge-Triggering** (**Positive** or **Negative**)
 - ★ Edge **detection** circuit is needed

Flip-Flop is a synchronized **Edge Triggered** Latch with Edge detection circuit **connected** to its Enable input




Positive (+ve) Edge Detector


 


Delay Gate

 
Due to the **Delay** of the **inverter** gate → the output is **1** for a very **small** time → **Edge detection**




- ☉ **Recall:** In **Level-Trigger** elements (latches), As long as the control (En) is **high** → output **may** change state.
- ☉ To overcome this, we use **Edge Trigger** Control → output will change **only** when a **0→1** or **1→0 transition** occurs
- ☉ To achieve **Edge Trigger** → a clock (CLK) signal is used to drive the control (enable) input of a latch
 - ★ This clock will **trigger** the flip-flop to **change** state only at the **transition**

 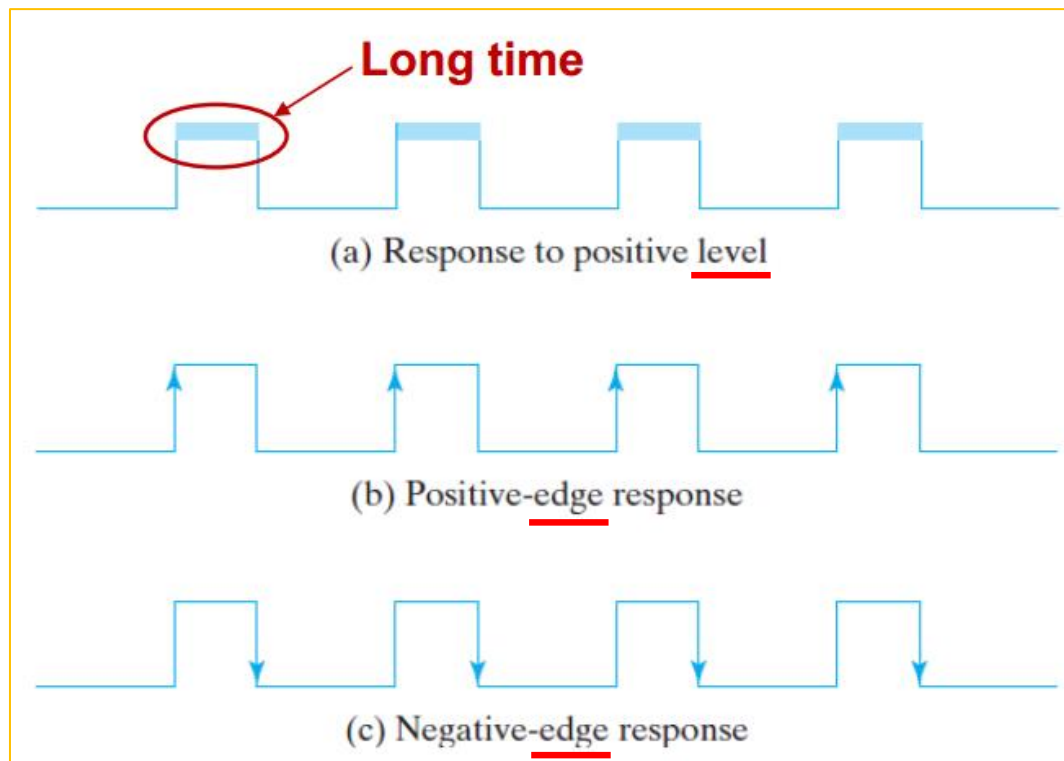

 - 🌀 We connect the **edge-detection** circuit at the **enable** input of the D latch
 - 🕒 This converts it to an **edge-triggered** D latch
 - 🕒 This new circuit is also called an Edge-Triggered **D Flip Flop (D-FF)**
- 🌀 We usually specify it as
 - 🕒 a **positive-edge** triggered flip-flop
 - 🕒 OR as a **negative-edge** triggered flip-flop



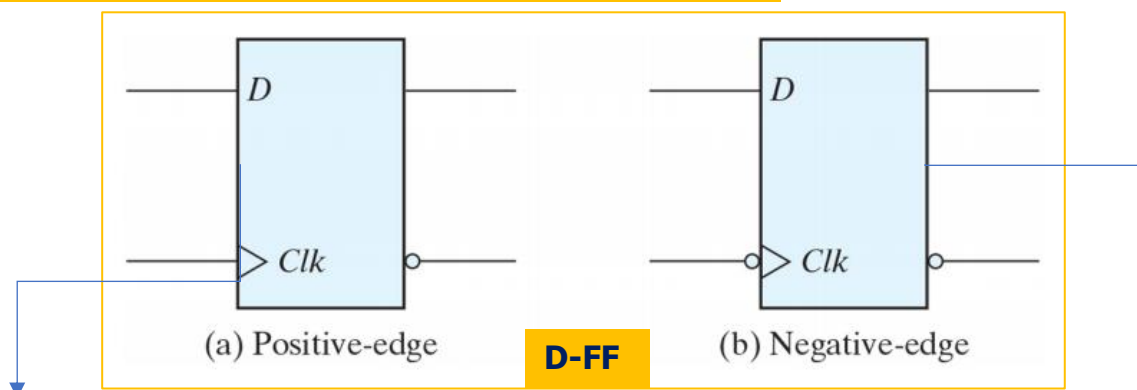
- 🌀 The **dynamic** indicator (>) denotes that flip-flop responds to the edge **transition** of the clock
- 🌀 A **bubble** adjacent to the dynamic indicator denotes that it is a **negative-edge** triggered flip-flop




- When the input **clock (Clk)** makes a **positive** transition (i.e., moves from **0 to 1**), the value of D is **transferred** to Q
- A **negative** edge of the clock does **NOT affect** the output
- The output is **NOT affected** by changes in D when the **Clk** is in the **steady logic-1 level** or the **logic-0 level**
- This type of flip-flop responds to the **transition** from **0 to 1** and **nothing else**

- When the input **clock (Clk)** makes a **negative** transition (i.e., moves from **1 to 0**), the value of D is **transferred** to Q
- A **positive** edge of the clock does **NOT affect** the output
- The output is **NOT affected** by changes in D when the **Clk** is in the **steady logic-1 level** or the **logic-0 level**
- This type of flip-flop responds to the **transition** from **1 to 0** and **nothing else**

- Common Design/Configuration of the **Negative** Edge-Triggered D Flip-Flop
- Built using **two** latches in a **master-slave** configuration
 - A **master** latch (D-type) receives **external** inputs
 - A **slave** latch (D-type) receives **inputs** from the **master** latch
- Only **ONE** latch is **enabled** at **any** given time
 - When **Clk=1**, the **master is enabled** and the D input is latched (**slave is disabled**)
 - When **Clk=0**, the **slave is enabled** to generate the outputs (**master is disabled**)

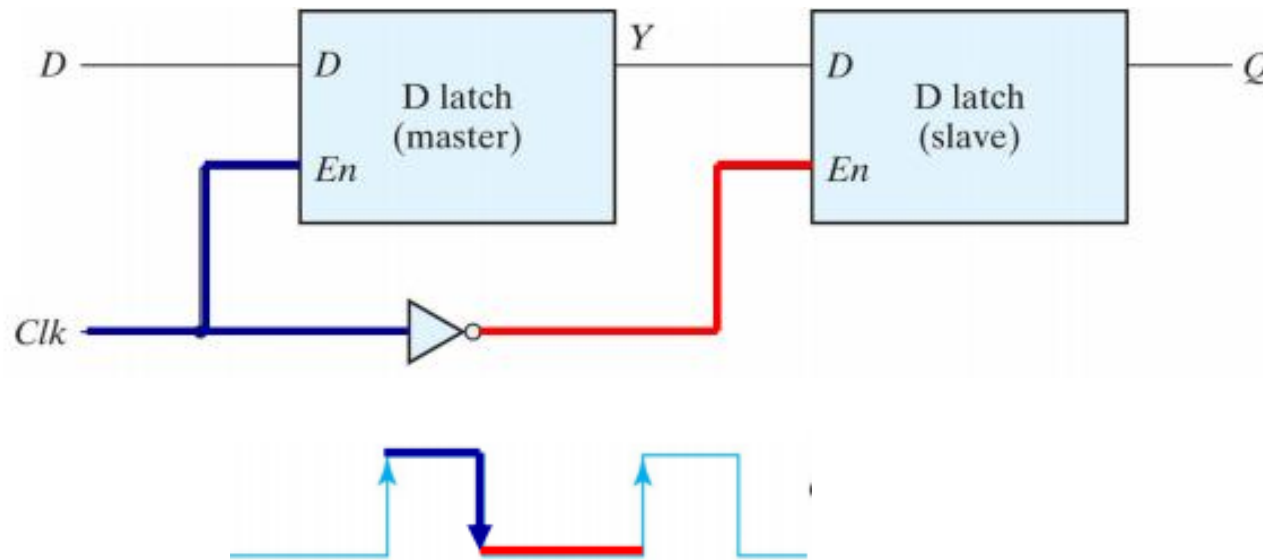

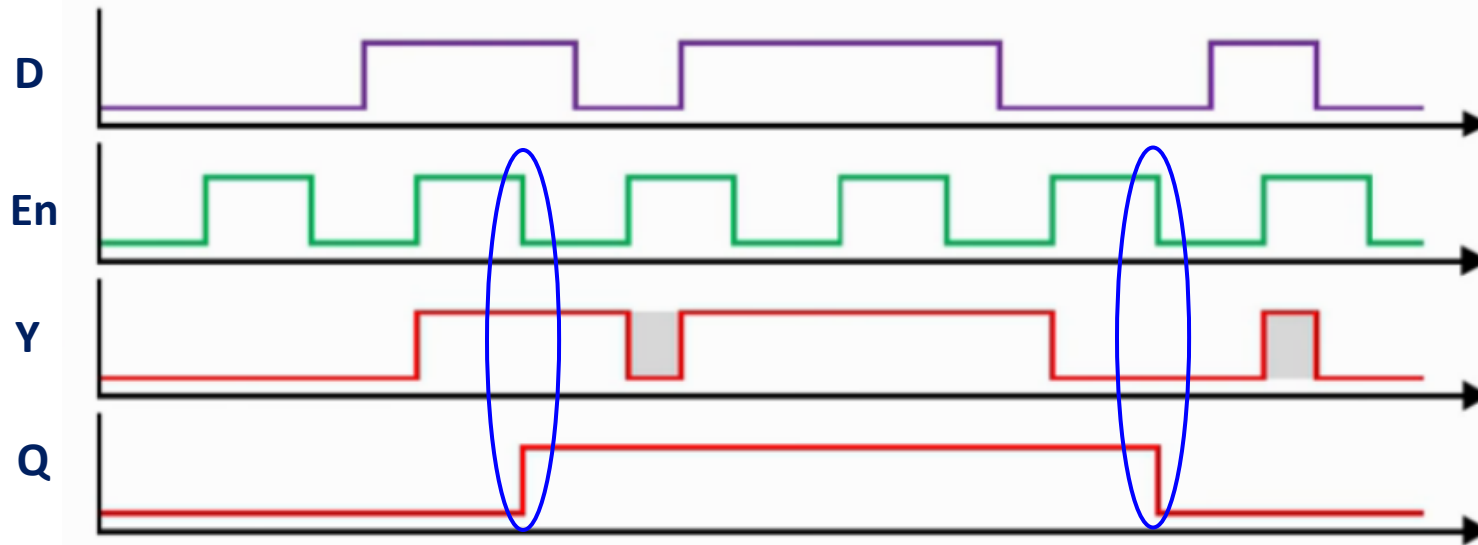
Change in the FF output can be triggered only by the transition of the clock from 1 to 0



- ✓ **Master** is enabled during **positive** CLK period.
- ✓ **Slave** is enabled during **negative** CLK period.
- ✓ D → Y during **+ ve** CLK period, while Q is NOT changed.
- ✓ Y → Q during **- ve** CLK period, while Y is NOT changed


- ☉ The behavior of the master-slave flip-flop dictates that
 - ☉ The output may change only **once**
 - ☉ A change in the output is **triggered** by the **edge** of the clock
 - ☉ The change may occur only during the clock's **negative** level
- ☉ The value that is **produced** at the **output** of the flip-flop is the value that was **stored** in the **master** stage **immediately** before the **negative** edge occurred

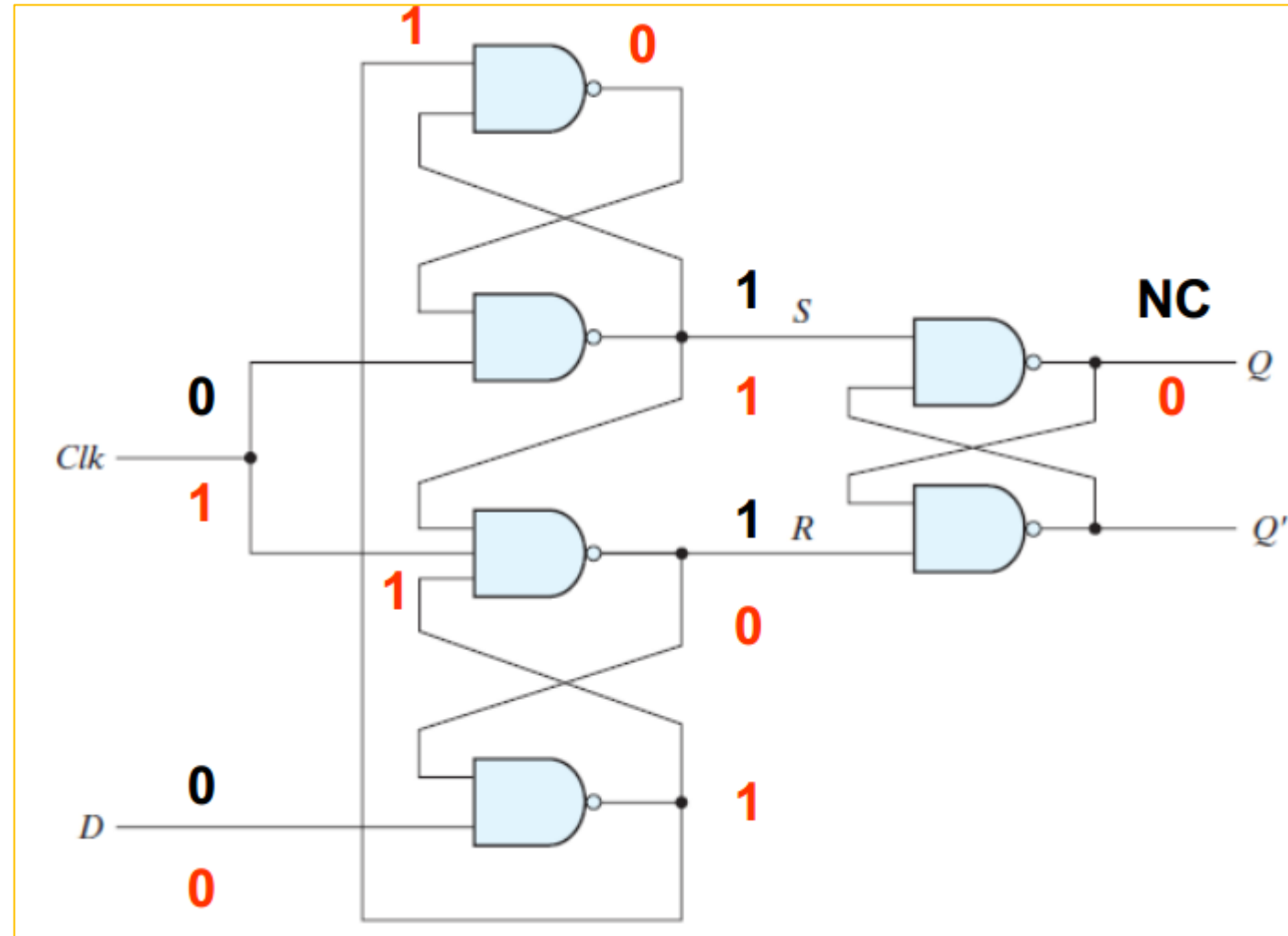- Two of the three SR latches responds to **CLK** and **D** inputs, the **third** provides **output**
- CLK=0 \rightarrow $Q(t+1)=Q(t)$ (**NC**: NO Change)
- CLK=1 & D=0 \rightarrow Q=0
- CLK=1 & D=1 \rightarrow Q=1
- If D changes after CLK becomes 1, the output is NOT changed
- Change only on CLK transition from 0 \rightarrow 1, and no other change




S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	(forbidden)

- ⌚ When $CLK=0$ and $D=0$, then the outputs of gates 1, 2, 3, and 4 are going to be 0**111**.
- ⌚ When $CLK=0$ and $D=1$, then the outputs of these gates are going to be **1110** instead.
- ⌚ In both cases, $S=R=1 \rightarrow$ No Change
- ⌚ Suppose that CLK becomes 1 while $D=0$. The output of gate **3** (which is **R**) becomes **0**. this will **reset** the output flip-flop.
- ⌚ Once R is 0, then **D can change to 1 and R remains 0**.
- ⌚ This means that **Q remains 0 while CLK is 1**. No change will occur to Q until the clock returns to 0 and then goes to 1 on the next clock pulse. This scenario shows that the flip-flop is a positive edge triggered.
- ⌚ Similar procedure occurs if $D=1$ while the clock goes from 0 to 1. In this case, $S=0$ and $Q=1$.

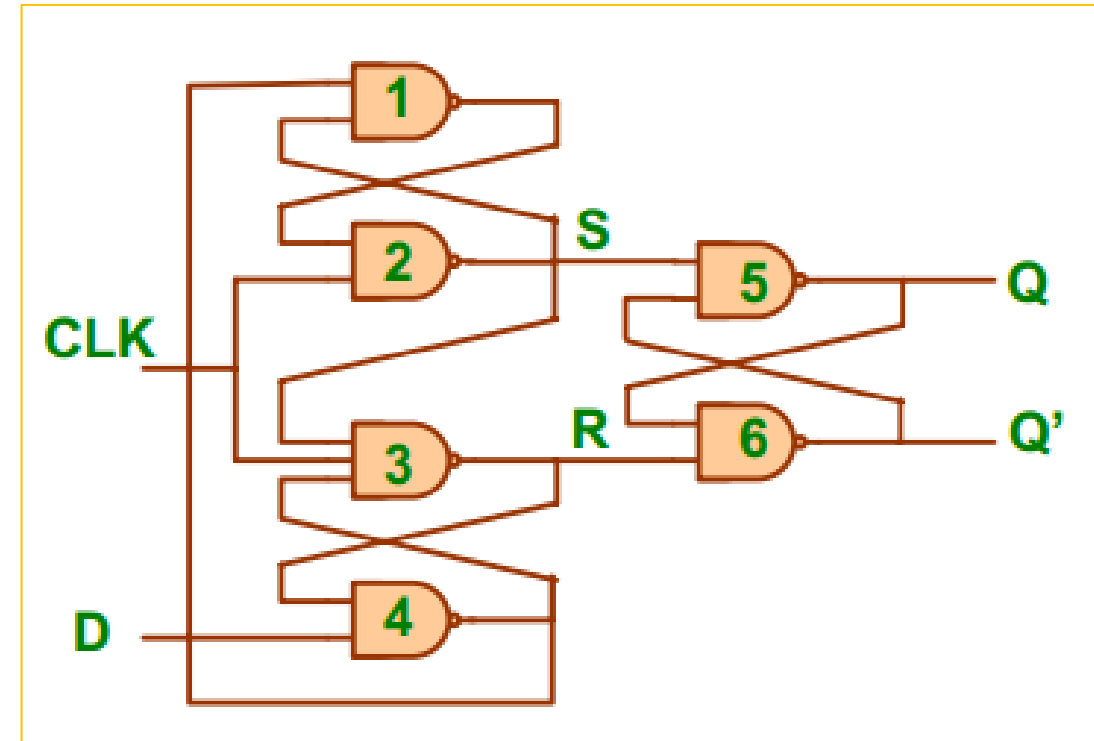

$$Q(t + 1) = D$$

Characteristic Equation

 


Graphic Symbol

D Flip-Flop		
D	Q(t + 1)	
0	0	Reset
1	1	Set


Characteristic Table

 ☯ In a **positive** edge triggered FF, output changes on CLK transition from **0 → 1**



 ☯ In a **negative** edge triggered FF, output changes on CLK transition from **1 → 0**






- 🌀 **Setup Time (T_s):** There is a **minimum** time during which the D must be **valid** and **stable before** the clock edge.
- 🌀 **Hold Time (T_h):** there is a **minimum** time during which D must **not change after** the clock edge.
- 🌀 **Propagation Delay:** the **interval** between the **trigger** edge and the **stabilization** of the **output** to a new state.

☉ If the setup and hold times are **violated**, a gate may produce an **unknown** logic signal at its output.

☉ This condition is called as **meta-stability**.

☉ In practical applications, the CLK (clock) signal, like all digital signals, requires a **finite** amount of **time** to transition between states and does **NOT** change **instantaneously**.

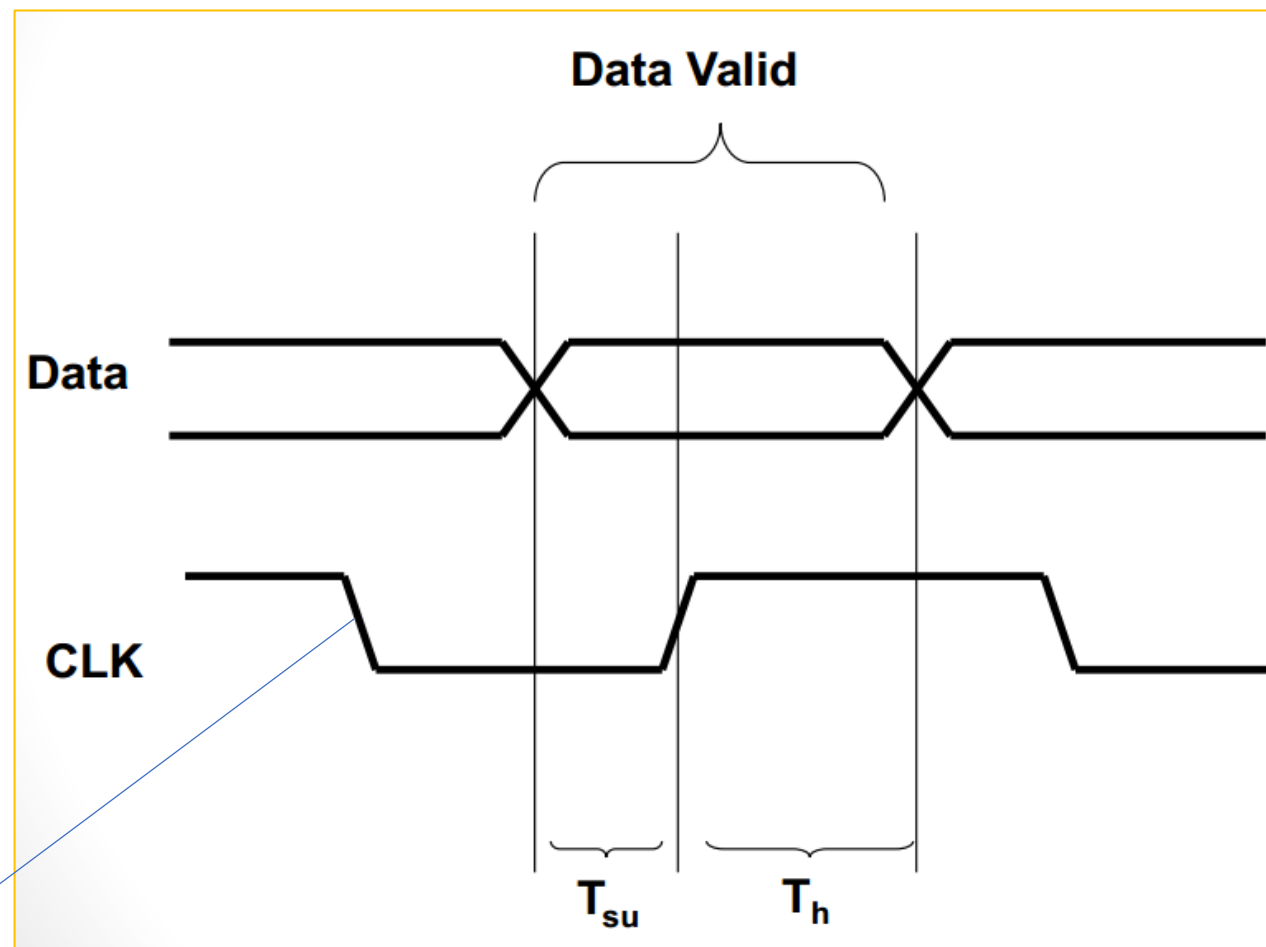☉ For simplicity in theoretical studies, we assume that the clock signal transitions instantly, **neglecting** any transition **delays**.






- 🌀 The most **economical** and **efficient** FF is **D-FF** because it requires the least number of gates
- 🌀 Other types of FF can be **constructed using** the **D-FF** and **external logic**
- 🌀 Other used flip-flops are **JK-FF** and **T-FF**


- 🌀 The JK is another type of Flip-Flop with inputs: **J**, **K**, and Clk
- 🌀 Typically constructed using the **D-FF** and **external gates**
- 🌀 **Four** operations: **set** to 1, **reset** to 0, **no change**, & **invert** output
 - 1) When JK = 10 → Set
 - 2) When JK = 01 → Reset/Clear
 - 3) When JK = 11 → Invert/Complement output
 - 4) When JK = 00 → No change
- 🌀 JK can be implemented using two Clocked SR latches and gates

Graphic Symbol

 

$$Q(t + 1) = JQ' + K'Q$$

Characteristic Equation

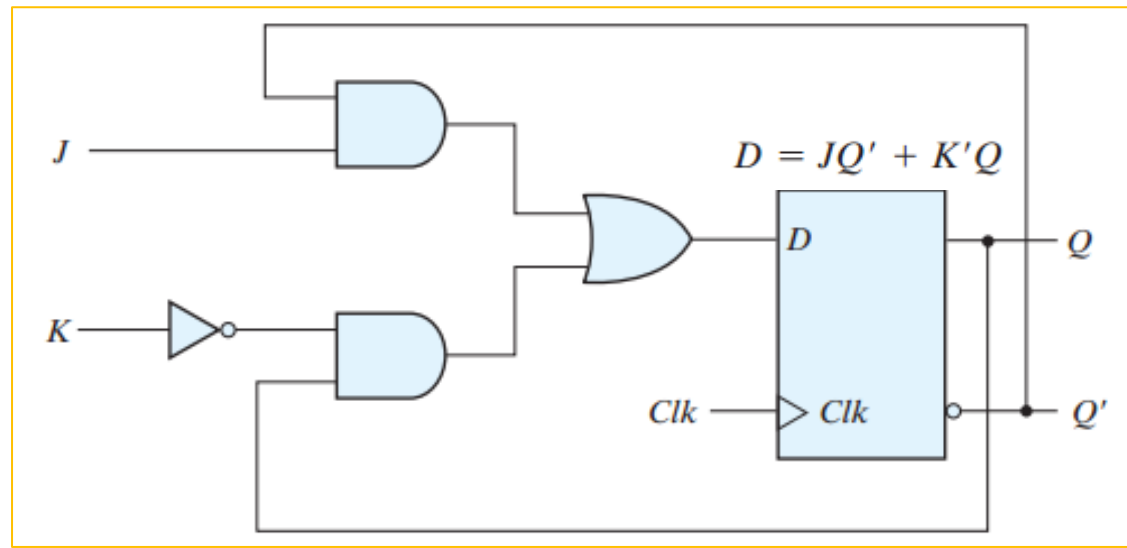

Circuit Diagram (using D-FF)


JK Flip-Flop

J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Table


- ☉ The T (**Toggle**) flip-flop has inputs: **T** and Clk
- ☉ **Two** operations: **no change** and **invert** output
 - 1) When T = 1 → Invert/Complement output
 - 2) When T = 0 → No change
- ☉ Can be implemented using
 - ☉ JK-FF
 - ☉ Or D-FF and XOR gate

Graphic Symbol

 

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

Characteristic Equation

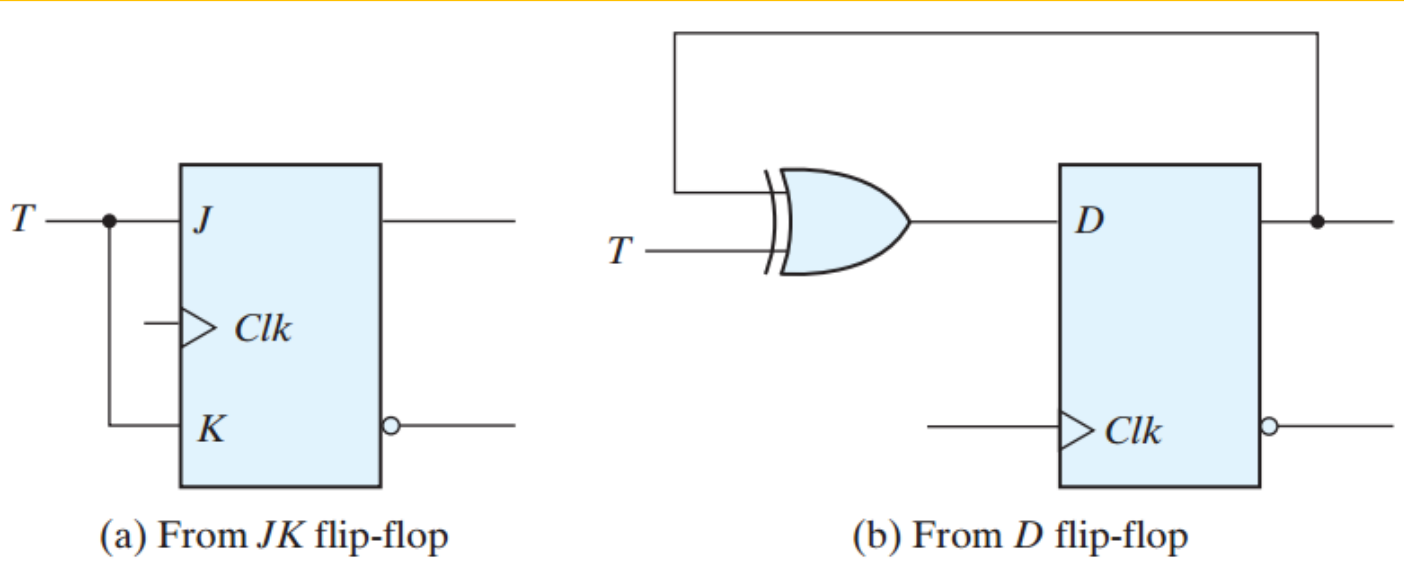

Circuit Diagram

T Flip-Flop		
T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement

Characteristic Table

- ☉ **Characteristic Tables:** Defines the **operation** of a flip-flop in a tabular form
- ☉ **Next state** is defined in terms of the **current** state and the **inputs**
- ☉ $Q(t)$ refers to current state **before** the clock edge arrives
- ☉ $Q(t+1)$ refers to **next state after** the clock edge arrives

D Flip-Flop

D	$Q(t + 1)$	
0	0	Reset
1	1	Set

T Flip-Flop

T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

JK Flip-Flop

J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

- ☉ **The characteristic equation defines the operation of a flip-flop**

D-FF

$$Q(t + 1) = D$$


T-FF

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$


JK-FF

$$Q(t + 1) = JQ' + K'Q$$

 - Direct Inputs are **Asynchronous** inputs that force the FF to a particular state regardless of the **clock**.
- The Input (**S/PR**) that sets the Flip-Flop to 1 ($Q=1$) is called **preset** or **direct set**.
- The Input (**R/CLR**) that sets the Flip-Flop to 0 ($Q=0$) is called **clear** or **direct reset**.
- When Flip-Flops are powered, their **initial** state is **unknown**




R	Clk	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0

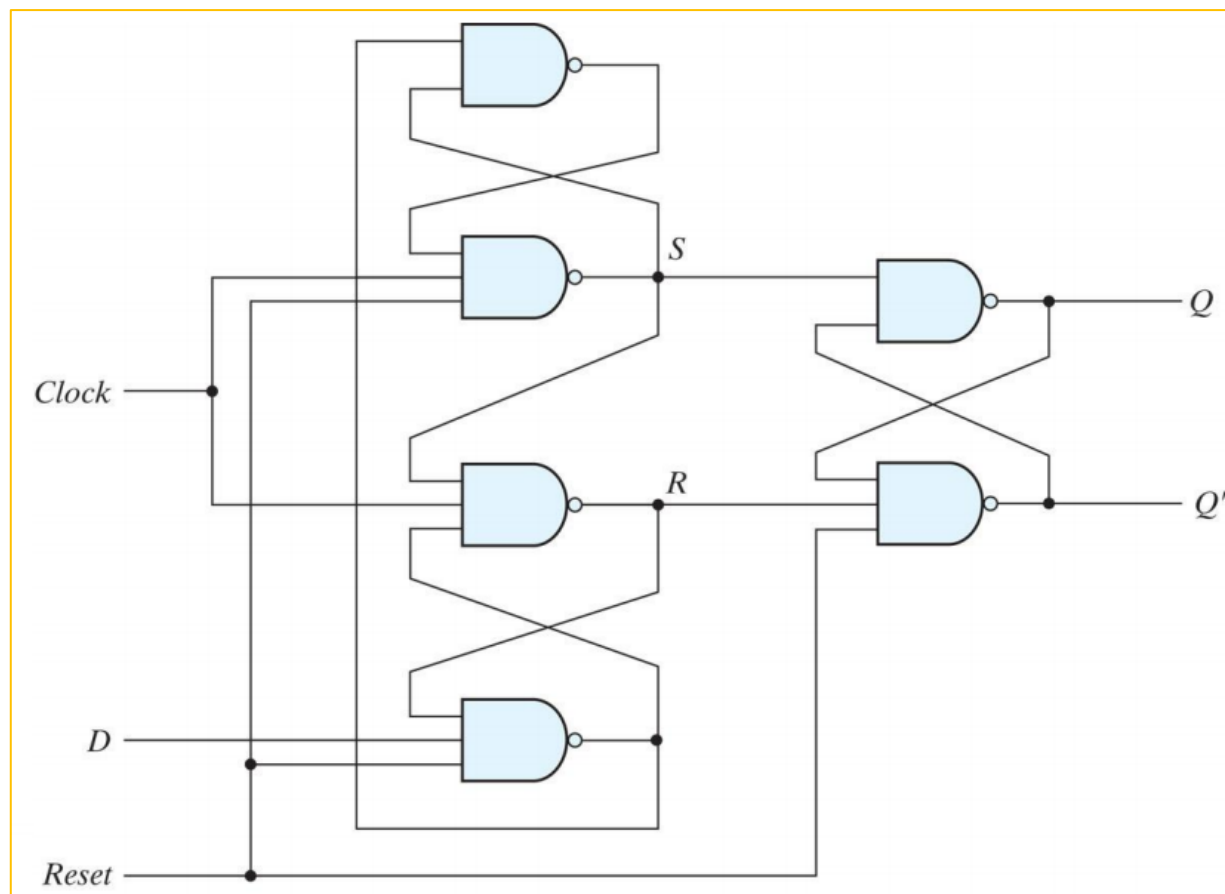

- Direct Inputs are **Asynchronous** inputs that force the FF to a particular state regardless of the **clock**.
- The Input (**S/PR**) that sets the Flip-Flop to 1 ($Q=1$) is called **preset** or **direct set**.
- The Input (**R/CLR**) that sets the Flip-Flop to 0 ($Q=0$) is called **clear** or **direct reset**.
- When Flip-Flops are powered, their **initial** state is **unknown**

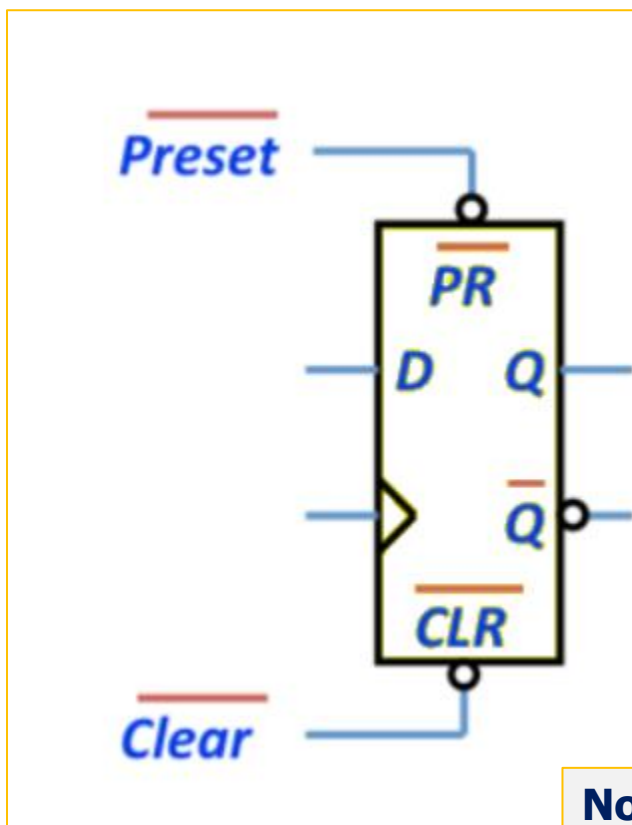Notice: As the **Bubble** Indicates Both (PR, CLR) Are **Active Low**



PR'	CLR'	D	CLK	$Q(t+1)$
1	0	x	x	0
0	1	x	x	1
1	1	0	↑	0
1	1	1	↑	1

Clear

Set

Notice: Both (PR, CLR) **Can't Be 0** (Activated) at the **same time**



- ⊙ **Recall: Analysis** is describing **what a given circuit do**
- ⊙ A logic diagram is recognized as a **clocked sequential circuit** if it includes **flip-flops with clock input**
- ⊙ The **behavior** of a clocked sequential circuit is determined from the **inputs**, the **outputs**, and the **state of its flip –flops**
- ⊙ The **outputs** and the **next state (NS)** are both a function of the **inputs** and the **present state (PS)**
- ⊙ The analysis of sequential circuits consists of:
 - 1) Determine the Circuit **Type** from the **Circuit/Logic Diagram** (**Sequential** or Combinational)
 - 2) Deriving **State Equations** for the next states of memory elements
 - 3) Obtaining a **State Table** for the time sequence of inputs, internal states and outputs of the circuit
 - 4) Obtaining a **State Diagram**

🌀 A **state equation** describes the **next state** as a function of the **present state and inputs**

🌟 Also called a **transition equation**

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = A'(t)x(t)$$



**State
Equations**

$$A(t+1) = Ax + Bx$$


$$B(t+1) = A'x$$

2 Flip-Flops → 2 State Equations

$$y(t) = [A(t) + B(t)]x'(t)$$

**Output
Expression**

$$y(t) = (A + B)x'$$

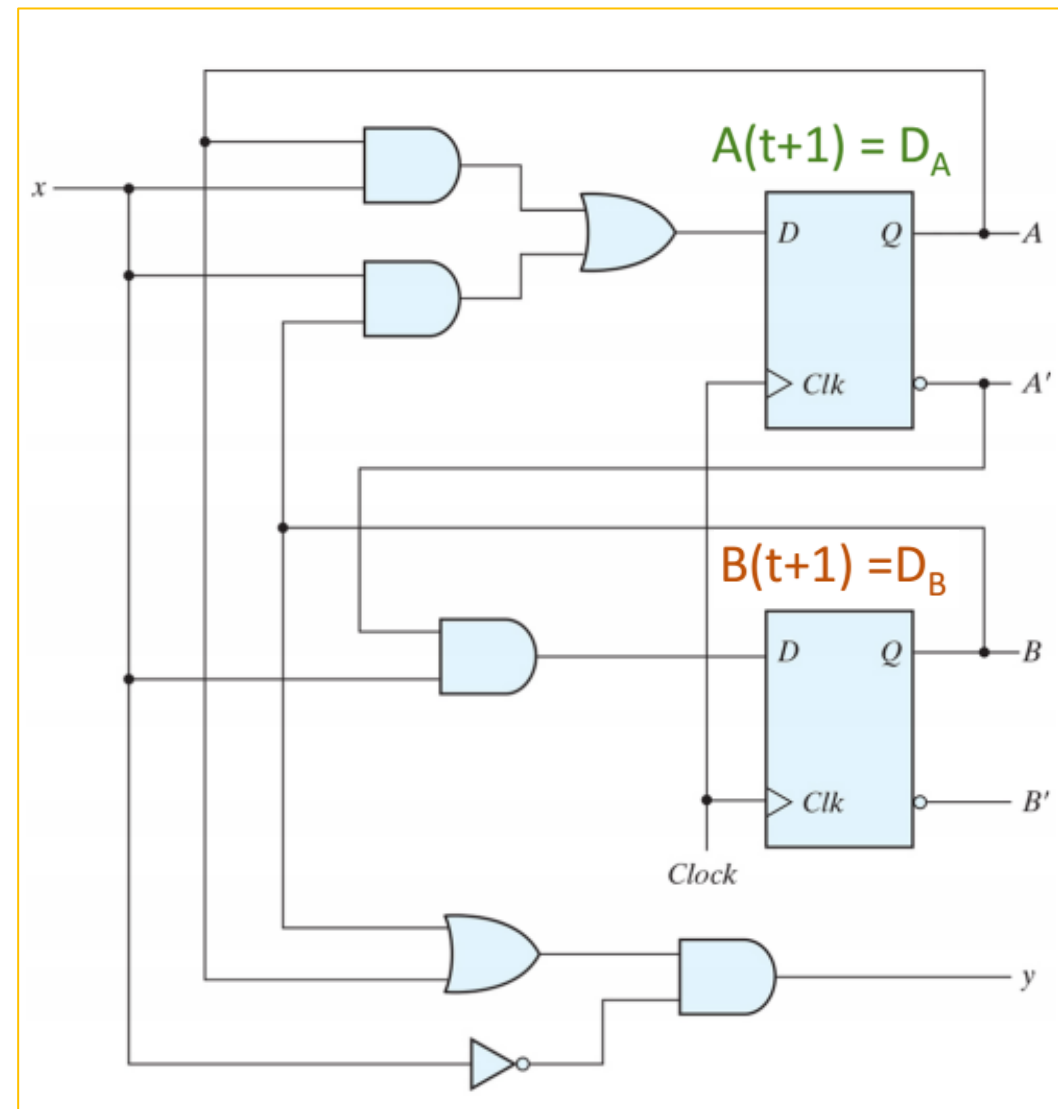



- 🌀 The time sequence of inputs, outputs and states can be described using **state tables**
- 🌀 **State tables** contain **four** sections:
Present state, Input, Next State, Output
- 🌀 Write all possible binary **combinations** for **Present** state and **Input** together
- 🌀 **Next state** values are determined from either the **logic diagram** or the **state equations**

- 🌟 A sequential circuit with **m** flipflops and **n** inputs →
 - A. **Normal** Form: 2^{m+n} rows
 - B. **Compact** Form: 2^m rows
- 🌟 The **next-state** section has **m** columns, **one** for each flip-flop
- 🌟 The **output** section has as many columns as there are **output variables**

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y(t) = (A + B)x'$$

Present State		Next State				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

Compact Form (2-D) : State Table

Present State			Input	Next State		Output
A	B	A		B	y	
0	0	0	0	0	0	
0	0	0	1	0	1	
0	1	0	0	0	1	
0	1	1	1	1	0	
1	0	0	0	0	1	
1	0	1	1	0	0	
1	1	0	0	0	1	
1	1	1	1	1	0	


Normal Form (1-D): State Table

- State diagram is a graphical way of showing the state table
 - More convenient to understand the behavior of a circuit
- In this diagram, states are represented by circles
- The transition from one state to another is represented by a line (Arrow) between the circles
- Lines/Arrows are labeled as: (Inputs / Outputs)

m flipflops → m state variables → 2^m states (circles)
 m=2 → 2² → 4 States: 00,01,10,11 (All A,B Combinations)

Present State		Next State				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

AB = 00
State

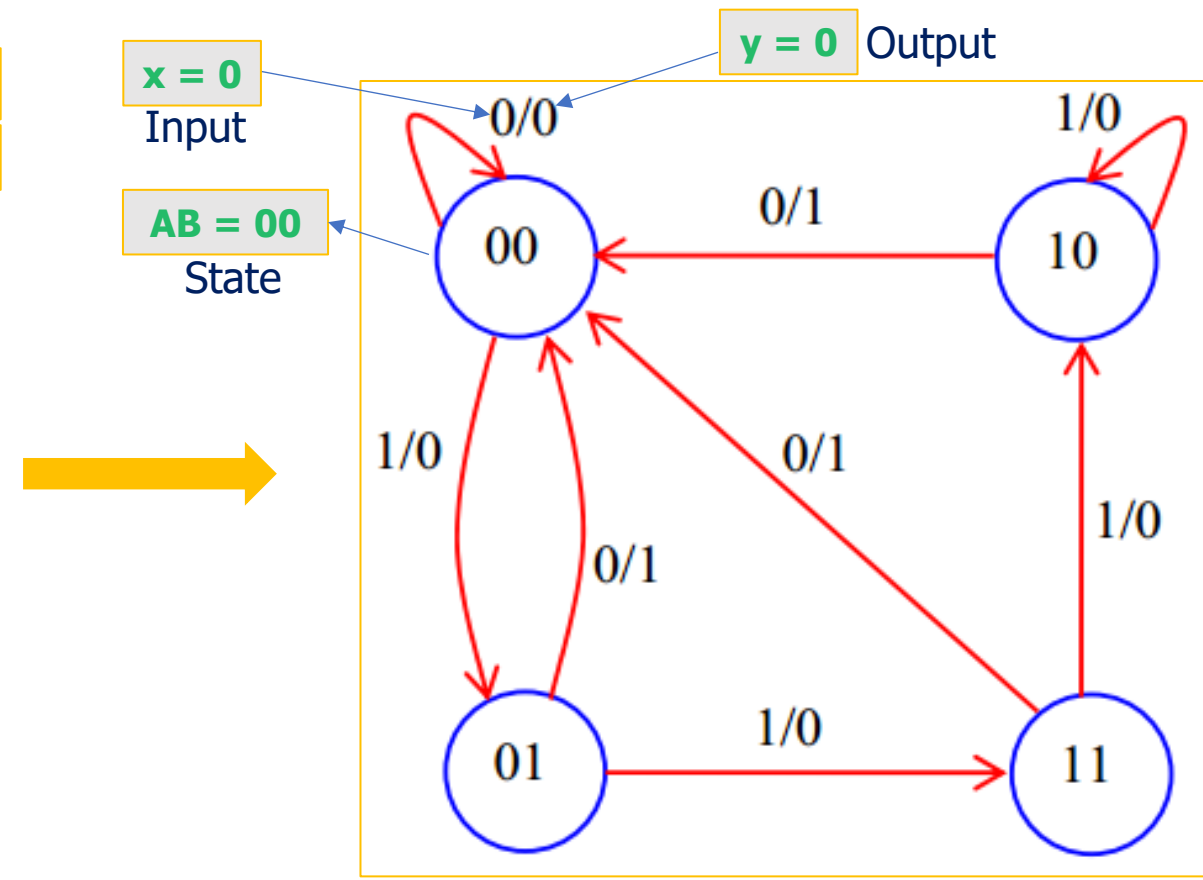

State Diagram

- ☉ Sequential circuits → combinational circuits + flip-flops
- ☉ We need **two** types of equations for drawing the logic diagram of the sequential circuit:
 - 1) Set of Boolean functions that describes algebraically the **combinational** circuit that generates **outputs**
 - ☉ **Output Equations**
 - 2) Set of Boolean functions that describes algebraically the circuit that generates the **inputs to flip-flop**
 - ☉ **Input Equations** or **Excitation Equations**

- ☉ Consider the previous example:

$$\begin{array}{l}
 D_A = A X + B X \\
 D_B = A' X \\
 y = X' (A+B)
 \end{array}
 \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} \text{input equations} \\ \text{output equations} \end{array}$$

Flip-Flops Analysis Steps (Mainly for JK & T Flip-Flops)

- 1) **Determine** the flip-flop **input equations** in terms of the **current state** and circuit **inputs**
- 2) **List** the **binary values** of each **input equation**
- 3) **Use** the flip-flop **characteristic table** to determine the **next state** values in the state table

- 🌀 **One** D flip-flop (A) → **Two** States
- 🌀 **NO** external output
- 🌀 **Two** inputs **x, y**




Input equation: $D_A = A \oplus x \oplus y$

D-FF →
Next State = D

State equation: $A(t+1) = A \oplus x \oplus y$

2

1 **Circuit Diagram**

 


Notice: When **Multiple** Input combinations → **Same** Transition : We use (,) to separate them

PS		NS	
Present state	Inputs	Next state	
A	x y	A	
0	0 0	0	
0	0 1	1	
0	1 0	1	
0	1 1	0	
1	0 0	1	
1	0 1	0	
1	1 0	0	
1	1 1	1	

Notice: Since NS = D,
No need for a column D



xy = 00
Input

 

xy = 11
Input

Notice: No External Output in this circuit →
No (/) exist over the arrow

State Diagram 4

Characteristic Equations:

$$\text{D Flip-Flop: } Q(t + 1) = D$$

$$\text{JK Flip-Flop: } Q(t + 1) = JQ' + K'Q$$

$$\text{T Flip-Flop: } Q(t + 1) = TQ' + T'Q$$

State Equations:

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

Examples

Input/Output Equations:

Input

$$D_A = Ax + Bx$$

$$D_B = A'x$$


Output

$$y = (A + B)'$$

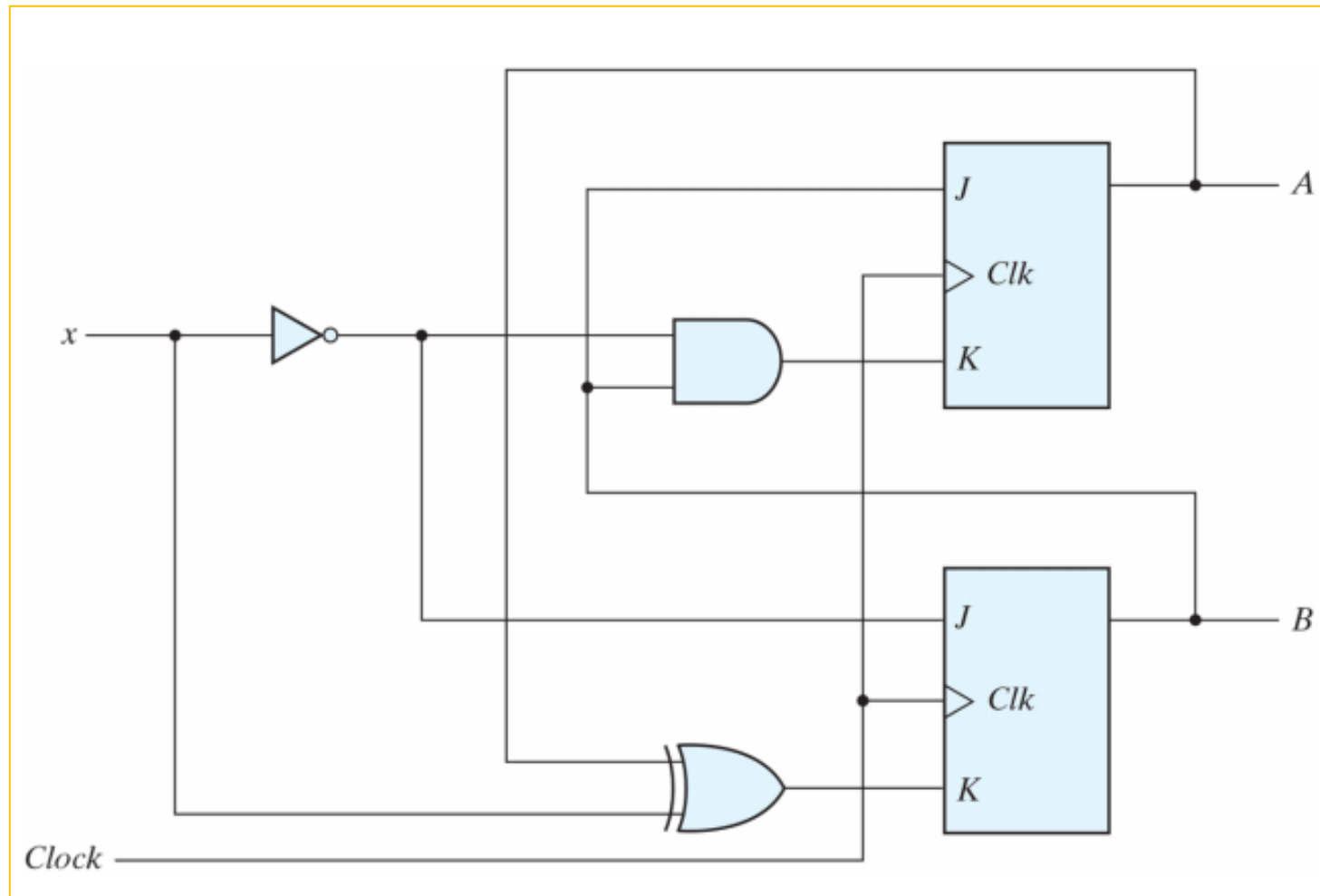Examples

- 🌀 **Two** JK flip-flops (A,B) → **Four** States
- 🌀 **NO** external output
- 🌀 **One** input **x**

Input equation: $J_A = B$, $K_A = B x'$
 $J_B = x'$, $K_B = A \oplus x$



Circuit Diagram

Input equation: $J_A = B, K_A = B x'$
 $J_B = x', K_B = A \oplus x$

J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Derive the **JK columns** by substituting **PS/Input** combinations into the **Input equations**

1

Use JK-FF **Characteristic Table** to fill the **next state columns**

2

Not part of the state table

PS Present State		Input	Flip-Flop Inputs				NS Next State	
A	B		J _A	K _A	J _B	K _B	A	B
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

Notice: No need to find the **state equations**. The **Characteristic Table** is directly used to find **NS** values in the state table

Alternative Method using Characteristic Equations

☞ The next-state values can also be obtained by **evaluating** the **state equations** from the **characteristic equation**. This is done as:

- 1) **Determine** the FF **input** equations
- 2) **Substitute** the **input** equations into the FF **characteristic equation** to get the **state equation**
- 3) **Use** corresponding **state** equations to determine **next state** values in the state table

$$\text{JK-Characteristic equation: } Q(t + 1) = JQ' + K'Q$$

$$\text{Characteristic equation: } \begin{aligned} A(t + 1) &= J_A A' + K'_A A \\ B(t + 1) &= J_B B' + K'_B B \end{aligned}$$

$$\text{Input equation: } \begin{aligned} J_A &= B, & K_A &= B x' \\ J_B &= x', & K_B &= A \oplus x \end{aligned}$$

Substitute


$$\begin{aligned} A(t + 1) &= (B)A' + (Bx')'A \\ &= A'B + AB' + Ax \end{aligned}$$

$$\begin{aligned} B(t + 1) &= (x')B' + (A \oplus x)'B \\ &= B'x' + ABx + A'Bx' \end{aligned}$$

State equations

Construct the **State table** directly from the **State equations**

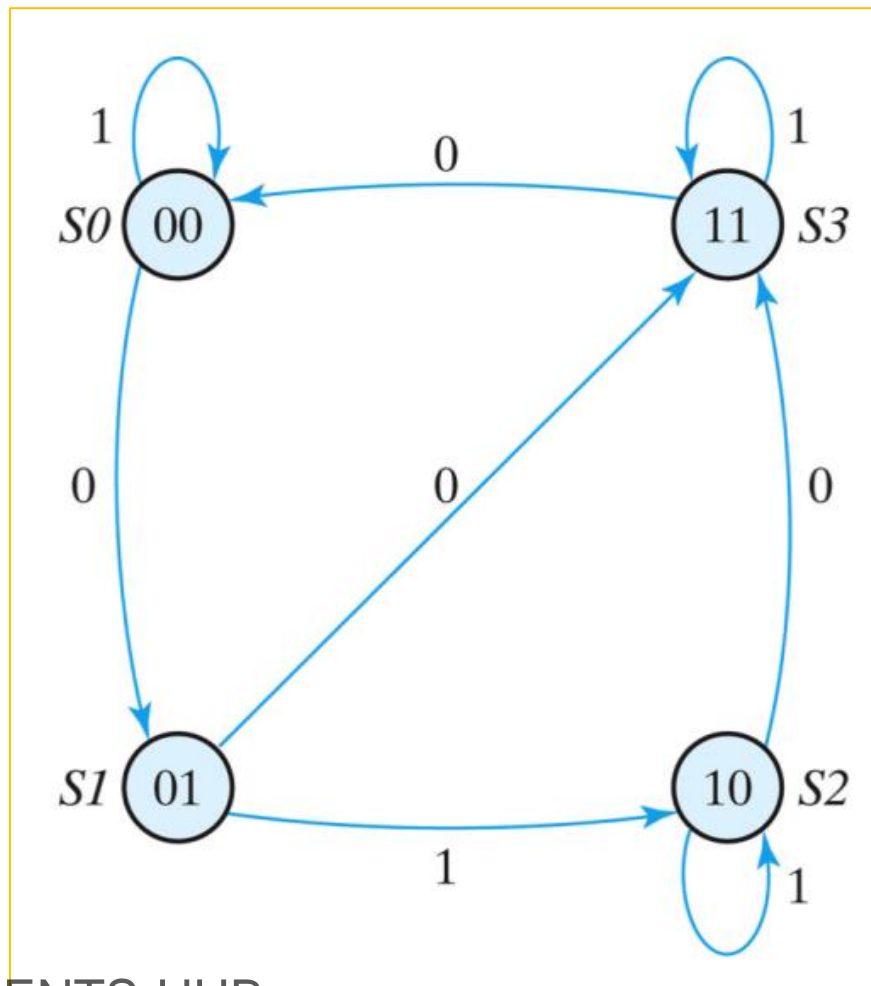Notice: It is common practice to label the states with **alphanumeric labels** such as S0, S1.. Where the numeric value is the **decimal equivalence** of the state



State equations

$$A(t + 1) = A'B + AB' + Ax$$

$$B(t + 1) = B'x' + ABx + A'Bx'$$

Present State		Input x	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

- 🌀 **Two** T flip-flops (A,B) → **Four** States
- 🌀 **One** external output
- 🌀 **One** input **x**

Output equation: $y = AB$

Input equation: $T_A = Bx$
 $T_B = x$ **Substitute**


$Q(t + 1) = T \oplus Q = TQ' + T'Q$

T-FF - Characteristic equation

$A(t+1) = (xB)'A + xBA' = x'A + AB' + xA'B$

$B(t+1) = x'B + xB'$

State equations

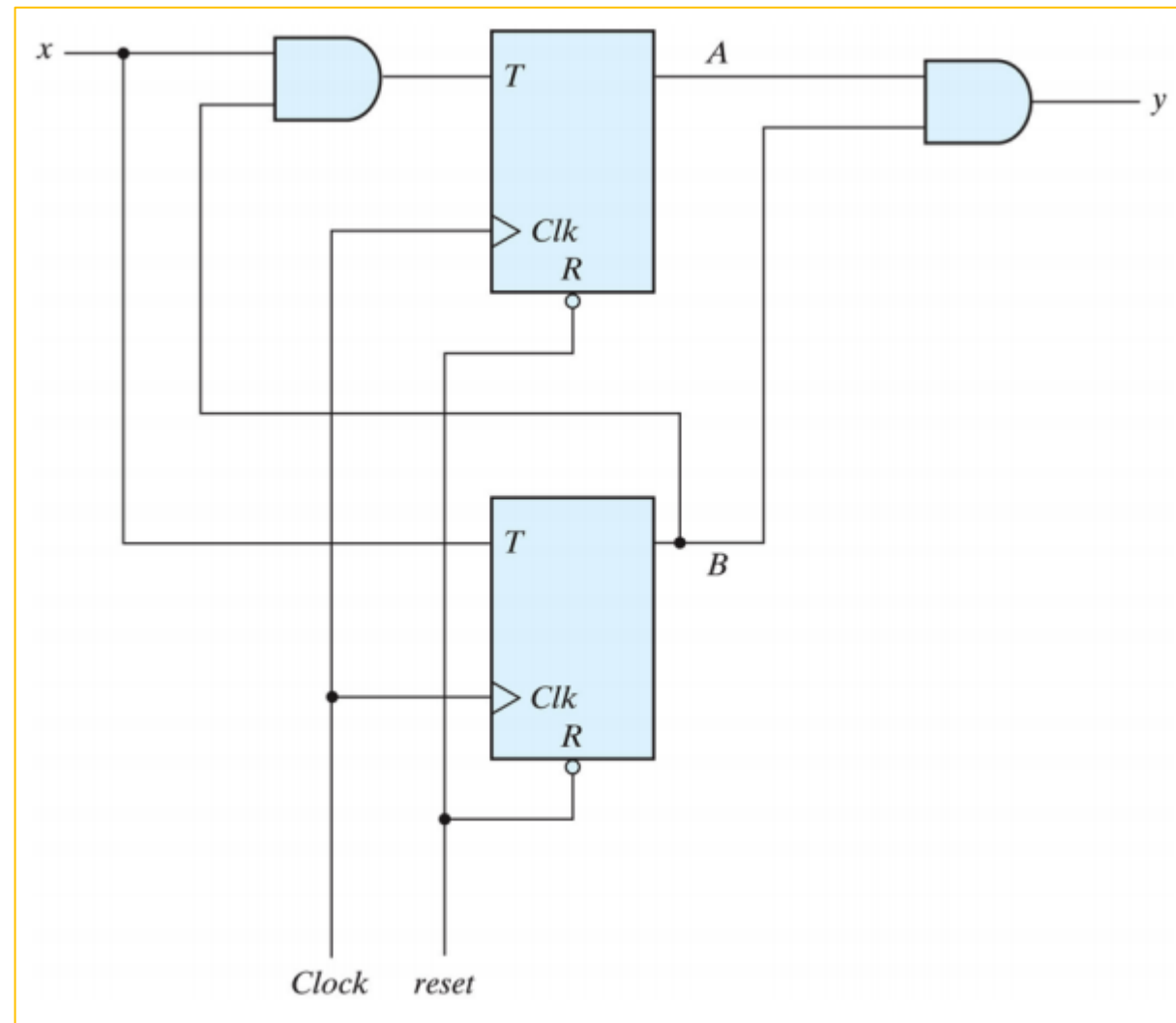

Circuit Diagram

Input equation: $T_A = Bx$
 $T_B = x$

T Flip-Flop

T	Q(t + 1)
0	Q(t) No change
1	Q'(t) Complement

Derive the **T columns** by substituting **PS/Input** combinations into the **Input equations** **1**

Use T-FF **Characteristic** Table to fill the **next state columns** **2**

Output equation: $y = AB$

Output Column always constructed from the **Output Equation**

Notice: No need to find the **state equations**. The **Characteristic** Table is directly used to find **NS** values in the state table

PS Present State		Input x	T		NS Next State		Output y
A	B		T _A	T _B	A	B	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	1	0
0	1	1	1	1	1	0	0
1	0	0	0	0	1	0	0
1	0	1	0	1	1	1	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	1

Construct the **State table** directly from the **State equations**

State equations


$$A(t+1) = (xB)'A + xBA' = x'A + AB' + xA'B$$

$$B(t+1) = x'B + xB'$$

Output Column always constructed from the **Output Equation**



Notice: We put the **output inside** the state circle because it does **Not depend** on the Input

$y = AB$

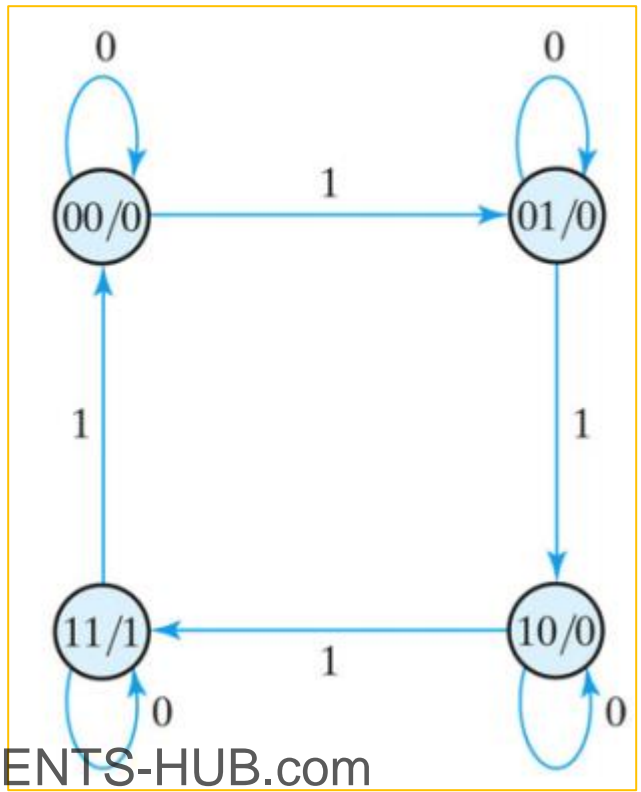


Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1


- There are **two** ways to design a clocked sequential circuit (differ only in the way **output is generated**)
 - Mealy FSM:** **Outputs** depend on **present state and inputs**
 - Moore FSM:** Outputs depend on **present state only**
- A circuit may have **both** types of **outputs**

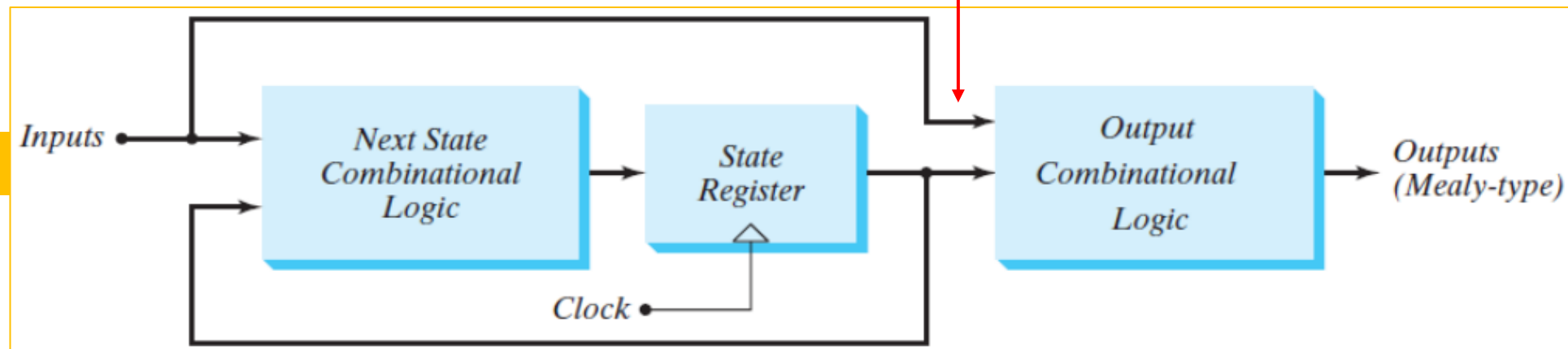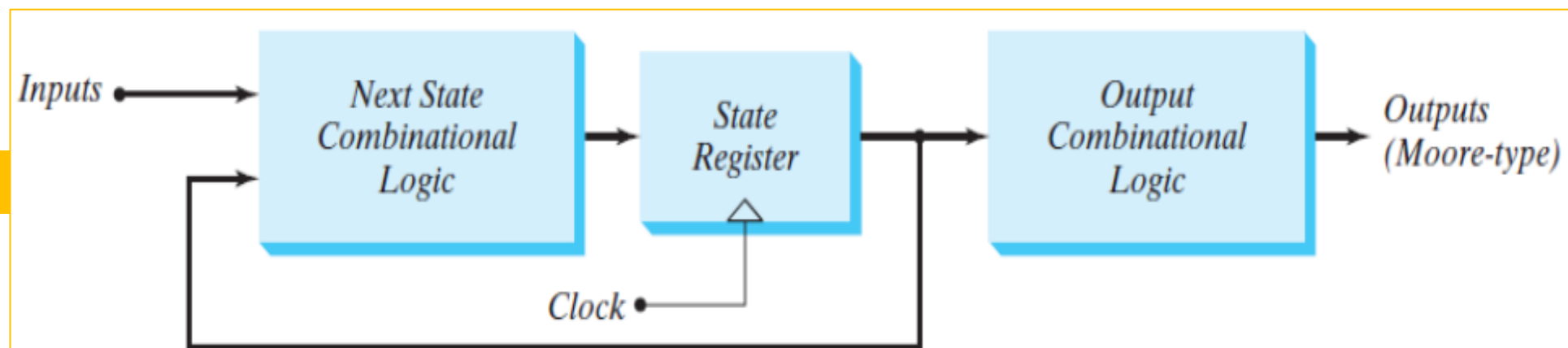Mealy FSM**Moore FSM**

Moore FSM

 


Mealy FSM

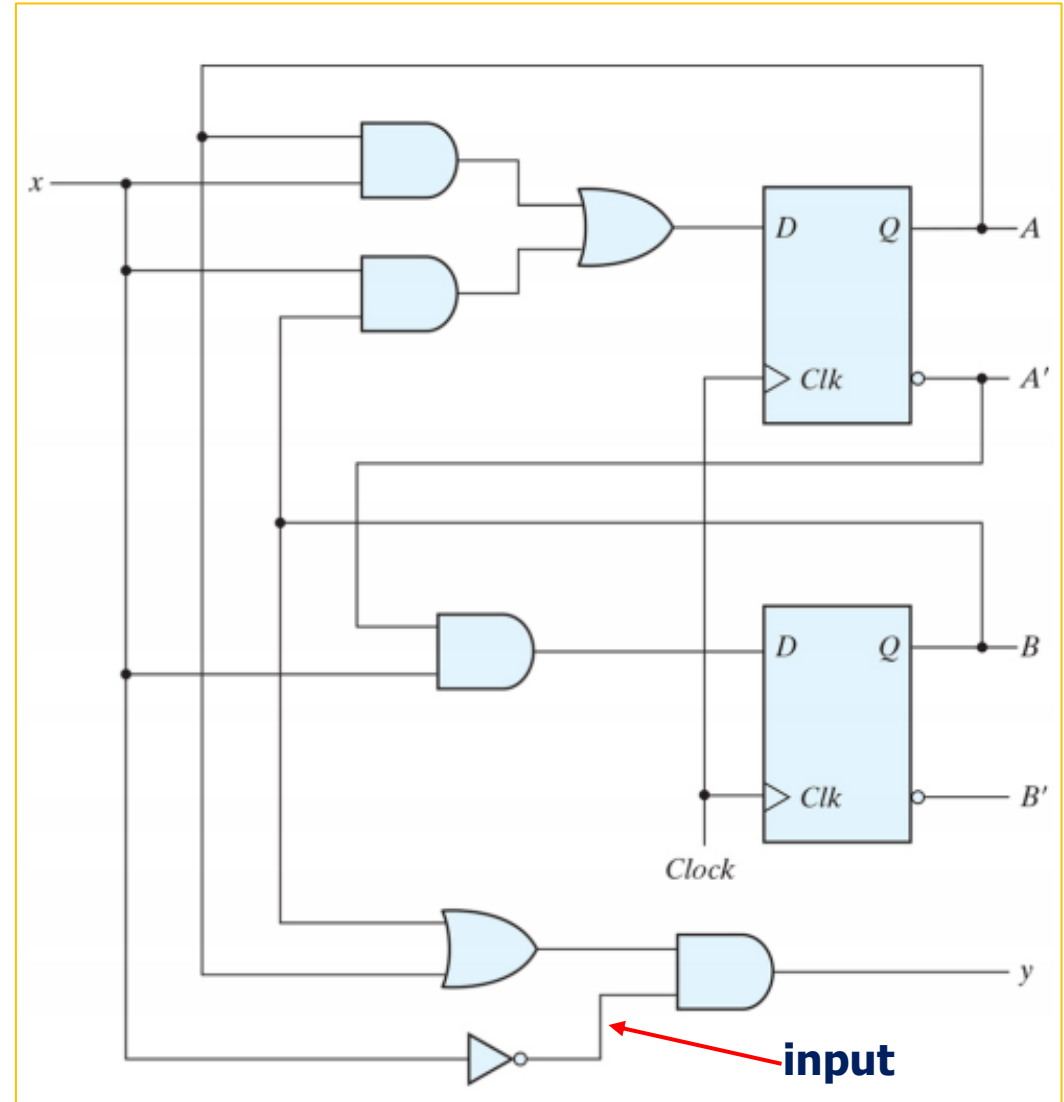

- ☞ The **outputs** are a function of the **present state and Inputs**
- ☞ The **outputs** are **NOT synchronized** with the clock
- ☞ The **outputs** may **change** if inputs change **during** the clock cycle
- ☞ The **outputs** may have momentary **false values** (called **glitches**)
- ☞ The **correct outputs** are present **just before** the **edge** of the clock



- ☞ Each line/arrow is **labeled** with: **Input / Output**
- ☞ The **output** is shown on the line/arrow of the state diagram

 Notice: We indicate the **output over the line/arrow** because it **depend** on the **Input**



Mealy FSM

Cycle	0	1	2	3	4	5	6	7	8
Input x	0	1	1	0	1	1	1	1	0
Present State A B	?	0	0	1	0	0	1	1	1
Output z	0	0	0	0	0	0	1	1	0

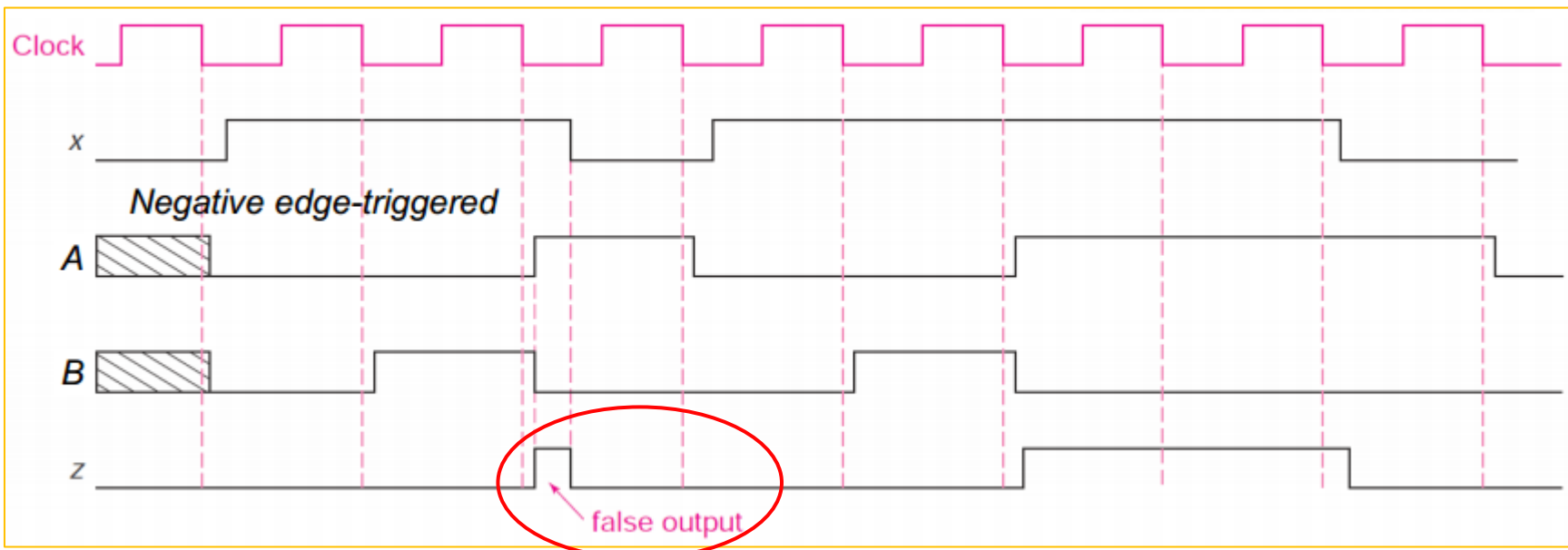 


- When the circuit is **powered**, the initial state (AB) is **unknown**
- Even though the initial state is unknown, the **input x = 0** forces a **transition to state AB = 00**, regardless of the present state
- Sometimes, a **reset input** is used to initialize the state to 00

- ☞ The **outputs** are a function of the **Flip-Flop** outputs **only**
- ☞ The **outputs** depend on the **current state only**
- ☞ The **outputs** are **synchronized** with the clock
- ☞ **Glitches cannot** appear in the outputs (even if inputs change)


- ☞ Each line/arrow is **labeled** with **Input** only
- ☞ The **output** is shown **inside** the state: (**State / Output**)
 - ✓ The output depends on the current state only

A given design might **mix** between Mealy and Moore

 
Notice: We indicate the **output inside the state circle** because it **depend** on the **state only**



Cycle	0	1	2	3	4	5	6	7	8
Input x	0	1	1	0	1	1	1	1	0
Present State A B	?	0	0	1	0	0	1	1	1
State A B	?	0	1	0	0	1	0	1	1
Output z	?	0	0	0	0	0	0	1	1

 

 - When the circuit is **powered**, the initial state (AB) and output are **unknown**
- Input x = 0** resets the state AB to 00. Can also be done with a reset signal.



The output is **synchronized** with the clock. **No false** output (or **glitch**) may appear.



- ☉ **Recall:** The **number of states** in the system determines the **number of FFs** needed
 - ★ 2^m **states** → **m FF**
- ☉ Two sequential circuits may have **same input-output** behavior but **different number of internal** states
- ☉ Certain properties of sequential circuits allow us to **reduce their number of states**
- ☉ **State-Reduction** is referred to the reduction of the **number of states** in a sequential circuit to **reduce the number of FFs** (Less FFs → Cost reduction)
 - ☉ **Reducing** the **number of states** while **preserving** the input/output relationship

State **Reduction** \equiv State Minimization \equiv Eliminate **Redundant** States


Notice: Reduction of states does **NOT** always result in reduction of flip-flops

Sometimes, reduction in flip-flops result in a **bigger combinational circuit** to realize the next state and the outputs

Example: Consider the input sequence: **01010110100** starting from the **initial** state **a**

State	a	a	b	c	d	e	f	f	g	f	g	a
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	


Pattern

 

Only interested in **input-output relationship**, states are of secondary importance

There are an **infinite** number of input sequences that may be applied to the circuit; each results in a **unique** output sequence

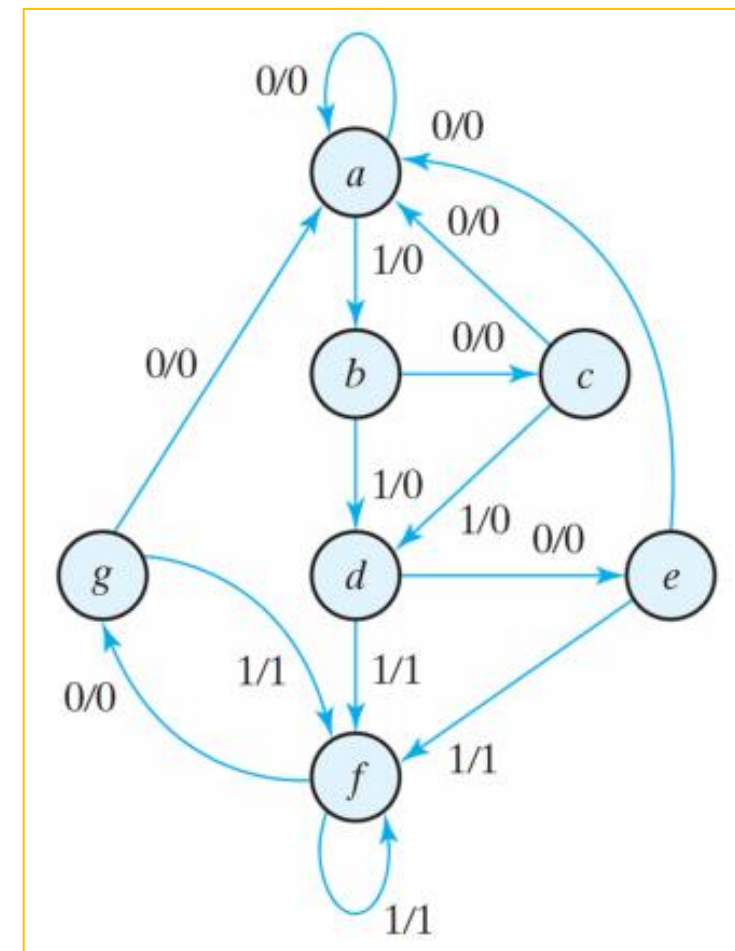
Only **input-output sequences are important**, the internal states are used to provide required sequences



- Two circuits are said to be **identical** if the **same** applied **input sequence** gives the **same output sequence**
- The challenge with state-reduction is to find ways to reduce the number of states **without affecting** the input-output relationships

Two states are said to be **equivalent**, if, for each set of inputs, they **give exactly** the **same output** and **send** the circuit to the **same state** or to an **equivalent state**

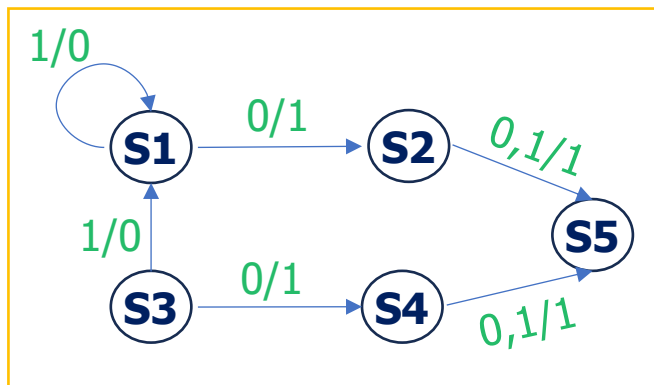When two states are **equivalent**, one of them can be **removed** without **altering** the input-output relationships



S2 & S4 are **equivalent**




S1 & S3 are **equivalent**

It is easier to work with **state tables**

- ☉ **Systematically** determines which **states** can be considered **equivalent**
- ☉ **Steps** (Let **n** = Number of States in the original Diagram/Table)

- 1) Start with the **state** table
- 2) Construct the Implication table
 - a) **Stair Case** Structure
 - b) Shall contains a **square** for each **pair** of states
 - c) Rows (2 to n) | Columns (1 to n-1)
- 3) For every square, compare each pair of rows in the state table:
 - a) If any of the **outputs** for the rows being compared **differ**, place an **X** in the square.
 - b) If the **outputs** are the **same**, list the **implied pairs** in the square.
 - ☉ Any implied pair that is **identical** or the states **themselves** is **omitted**.
 - c) If the **outputs** are the **same** and if both the **implied pairs** are **identical** and/or the states **themselves**, then place a ✓ in the square.
- 4) For **all** squares in the table with **implied pairs**, examine the square of each implied pair. If **any** of the implied pair squares **has an X**, then put an **X** in this square
- 5) Repeat the step 4 until **NO** more **Xs** are added.
- 6) Upon completion of the previous step, squares **without X's** indicate **equivalent states**.
- 7) **Remove redundant** states, and **replace** them with **equivalent** states.

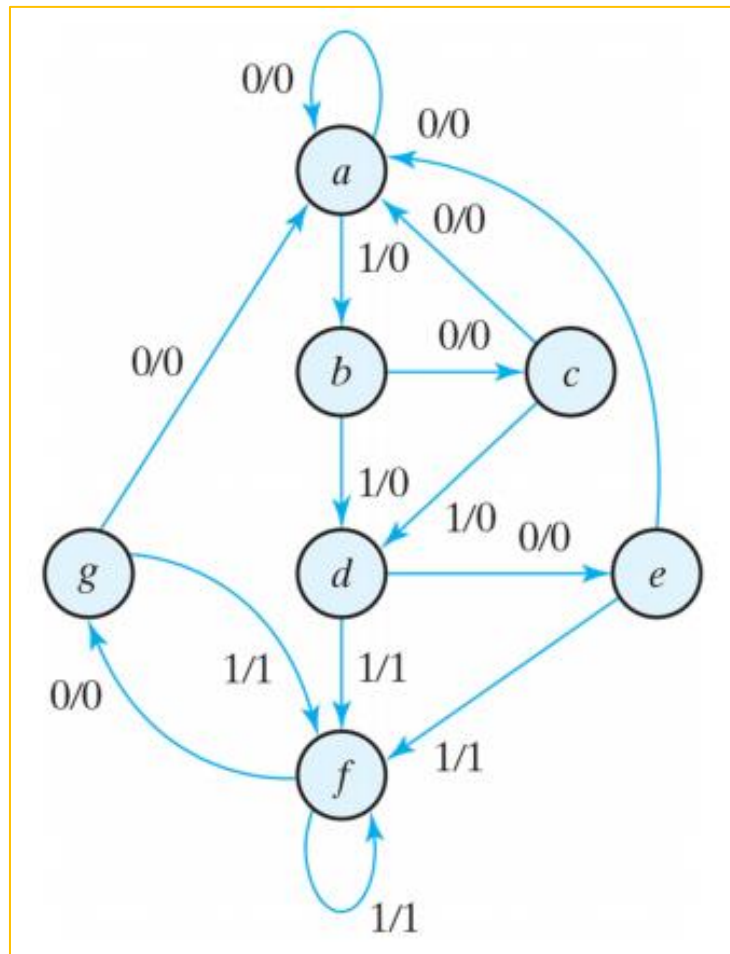Example:


Step 1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Example:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Step 2

 

$n = 7 \rightarrow 6 \times 6$ Table

Example:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Step 3

b	(a=c) (b=d)					
c	(b=d)	(a=c)				
d	X	X	X			
e	X	X	X	(a=e)		
f	X	X	X	(e=g)	(a=g)	
g	X	X	X	(a=e)	✓	(a=g)
	a	b	c	d	e	f



$n = 7 \rightarrow 6 \times 6$ Table

Example:

Steps 4-5

b	(a,c) (b,d)					
c	(b,d)	(a,c)				
d	X	X	X			
e	X	X	X	(a,e)		
f	X	X	X	(e,g)	(a,g)	
g	X	X	X	(a,e)	✓	(a,g)
	a	b	c	d	e	f

b	(a=c) (b=d) X					
c	(b=d) X	(a=c) X				
d	X	X	X			
e	X	X	X	X		
f	X	X	X	✓	X	
g	X	X	X	X	✓	X
	a	b	c	d	e	f



Steps 6

- State e ≡ State g
- State d ≡ State f

Example:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Steps 7

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1


State e \equiv *State g***e** and **g** are equivalent \rightarrow

- 1) **Remove g** row
- 2) **Replace g** with **e** whenever it occurs as next State

State d \equiv *State f***d** and **f** are equivalent \rightarrow

- 1) **Remove f** row
- 2) **Replace f** with **d** whenever it occurs as next State

Example:

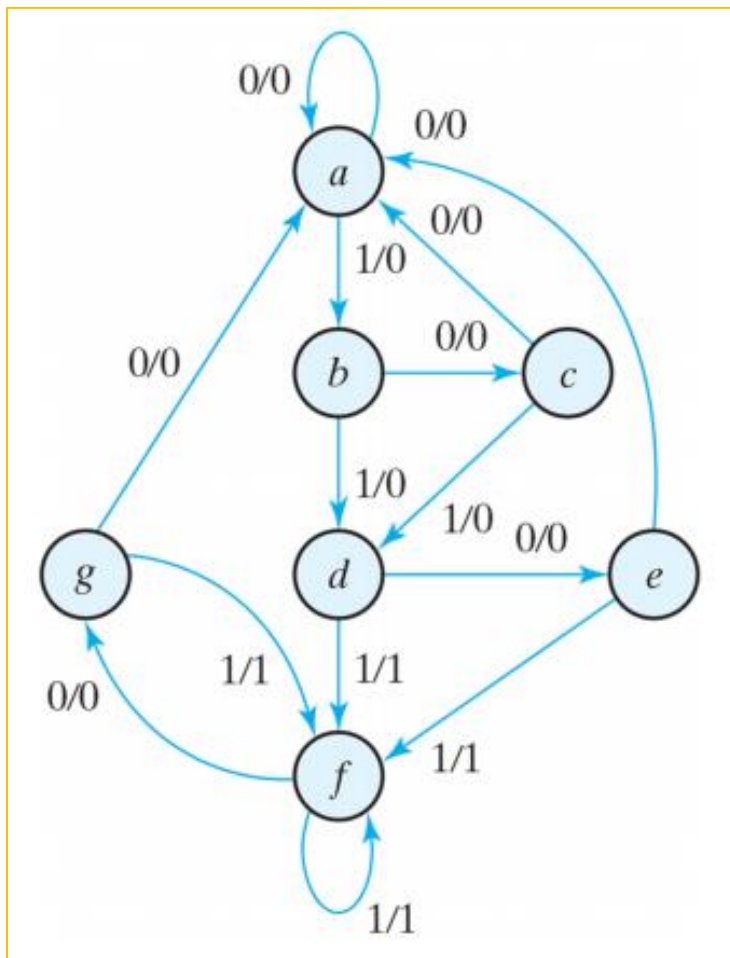

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1


State e ≡ State g

- e and g are equivalent →
- 1) **Remove g** row
 - 2) **Replace g** with e whenever it occurs as next State



Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Example:

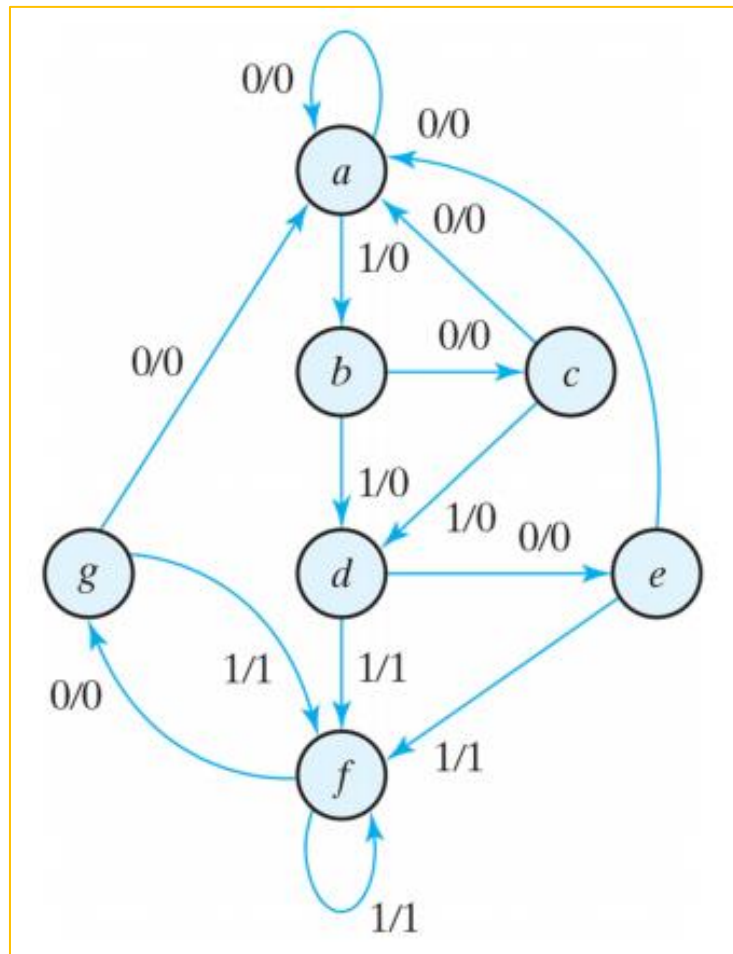

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1




Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

State d ≡ State f

- d** and **f** are equivalent →
- 1) **Remove f** row
 - 2) **Replace f** with **d** whenever it occurs as next State

Example:

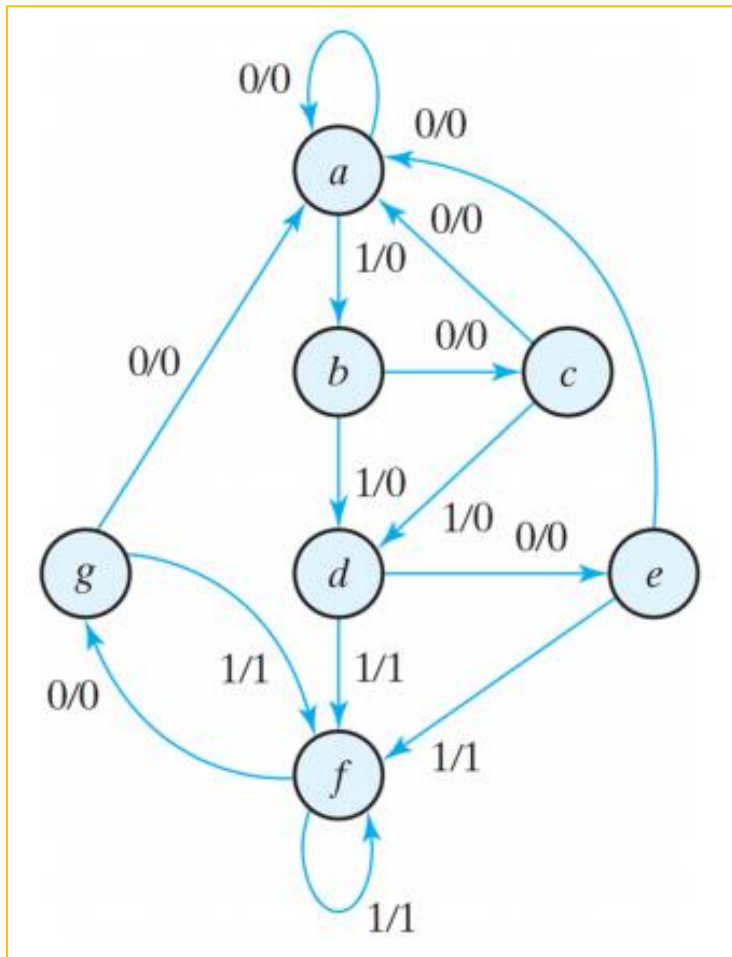


Reduced from **7** – **5** states



To cover 7 states → 3 FFs is needed
To cover 5 states → 3 FFs is needed

Notice: No. FFs (m) ≥ $\lceil \log_2(\text{No. States}) \rceil$


Ceiling Function

 


We did **NOT** save any **FF** in this design, but we have **more Unused states** that we can substitute for as **don't cares during design**, thus **simplifying** some combinational design logic.

Notice:
No. **Unused** Sates = **Max No. States** – No. **Used States**
= $2^3 - 5 = 3$

Example: *Verify Reduction*

 

State	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>	<i>a</i>
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	

 

State	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>d</i>	<i>d</i>	<i>e</i>	<i>d</i>	<i>e</i>	<i>a</i>
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	

Identical Output Sequence

Extra Example: (Moore FSM)

n = 8 → 7x7 Table

Present State	Next State		Present Output
	X=0	X=1	
a	g	c	0
b	f	h	0
c	e	d	1
d	a	c	0
e	c	a	1
f	f	b	1
g	a	c	0
h	c	g	1



b	(g=f) (c=h) ✗						
c	X	X					
d	(g=a) ✓	(f=a) ✗ (h=c)	X				
e	X	X	(d=a) ✓	X			
f	X	X	(e=f) (d=b) ✗	X	(c=f) (a=b) ✗		
g	✓	(f=a) ✗ (h=c)	X	✓	X	X	
h	X	X	(e=c) ✓ (d=g) ✓	X	(a=g) ✓	(f=c) (b=g) ✗	X
	a	b	c	d	e	f	g

State a ≡ State d ≡ State g
State c ≡ State e ≡ State h



Four States (a, b, c, f)



8 states → 4 states
3 FFs → 2 FFs

- ☉ it is necessary to assign **unique** coded **binary values** to the **states**
- ☉ For a circuit with **m** states, the codes must contain at least **n** bits, where $2^n \geq m$
 - ★ This may generate $(2^n - m)$ **unused** states

State Assignment Methods

☉ A **different** assignment will result in a state table with different binary values for the states.

☉ The **complexity** of the combinational circuit **depends** on the binary state **assignment chosen**.

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

Notice: One-hot requires extra FFS, but usually leads to **simpler** logic for the next state and output

🌀 A **state table** with a **binary assignment** is called a **Transition table**

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

Notice: 101, 110, 111 → Unused States

Transition Table



- 🌀 **Recall: Design** goal is to specify the **hardware/circuit** that will **implement** a desired behavior
 - 🌟 **Starts** from a **set of specifications** and **conclude** with a **logic diagram**
- 🌀 **Recall:** Sequential circuits are made up of flip-flops and combinational logic that may influence the flip-flops inputs and/or the circuit outputs
- 🌀 Once the type and number of flip-flops are determined, the design problem turns to a combinational circuit design problem
- 🌀 The **D-FF** is the **basic** storage element from which all others are derived using additional combinational logic
- 🌀 **Remember**, number of **FF depends** on number of **states**



Derive a State Diagram from the Verbal Description

State Diagram

Decide on Moore or Mealy FSM



Construct the State Table from the State Diagram

State Table

Use 2D or 1D Form



Reduce States (if necessary)

Optimal State Table

Use Implication Table Method



Assign Binary Codes for States

Binary State Table

Use Suitable State Assignment Method



Obtain Binary Coded State Table

Choose Flip-Flop Type

Derive Simplified Flip-Flop Input Equations

Boolean Equations




Derive Simplified Output Equations

Draw Logic Circuit Diagram

Circuit Diagram

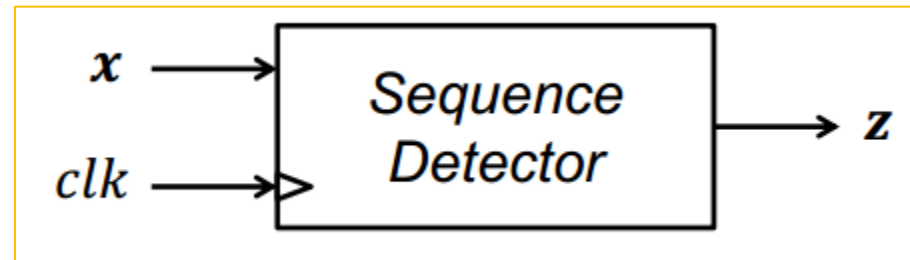Example: Sequence Detector


- ☉ This kind of sequential circuits is commonly known as A **sequence detector**
- ☉ It **Detects** a specific **sequence of bits** in the **input**
- ☉ The input is a serial bit stream: **One** input bit **x** is fed to the sequence detector **each cycle**
- ☉ The output is also a bit stream: **One** output bit **z** each cycle **indicates** whether a given sequence is **detected or NOT**



Example: Design a **sequence detector** that will **detect three or more consecutive 1's**. When the three **consecutive 1's (111)** are detected, the **output is set to 1 for one clock cycle**. If any **further consecutive 1** is detected the **output remains to be 1**. If a **zero** occurs in between the 1's, the **output become 0** and the detector goes to its **initial state** and starts all over again.

State Diagram

 - 1) Begin in an **initial** state: call it **S_0**
- 2) **S_0** indicates that a **1** is **NOT detected** yet
- 3) As long as the input x is 0, remain in the initial state **S_0**
- 4) Add a state (call it **S_1**) that detects the **first "1"** in the input
- 5) Add a state (call it **S_2**) that detects the input sequence **"11"**
- 6) Add a state (call it **S_3**) that detects the input sequence **"111"**




Example:

Sequence Detector

State Diagram

Complete the State Diagram

 
- When the **input** is **0**: Add transitions from S_1 , S_2 , and S_3 **back to S_0**
- When the **input** is **1**: Add transition from S_3 **to itself** to detect sequences longer than **three 1's**



Consider Moore FSM

Assign Output to States

 - The output in S_0 , S_1 , and S_2 should be **0**
- The output in S_3 should be **1**



State Reduction is NOT necessary

State Table


Present State	Next State		Output z
	$x = 0$	$x = 1$	
S_0	S_0	S_1	0
S_1	S_0	S_2	0
S_2	S_0	S_3	0
S_3	S_0	S_3	1

Example:**Sequence Detector****State Assignment**Recall: for m states

The minimum number of state bits: $n = \lceil \log_2 m \rceil$
 $\lceil x \rceil$ is the smallest integer $\geq x$ (ceiling function)

- Ⓜ **Each state** must be assigned a **unique** binary code
- Ⓜ In this example:
 - ★ **Four** states: $S_0, S_1, S_2,$ and S_3 ($m=4$) → Minimum number of state bits (FFs) is ($n=2$)
- Ⓜ State assignment: **$S_0 = 00, S_1 = 01, S_2 = 10,$ and $S_3 = 11$**
- Ⓜ **Recall:** If n bits are **used**, the number of unused states = $(2^n - m)$
 - Ⓜ In this example, there are **NO unused** states

Example: Sequence Detector

 


State Assignment
 $S_0 = 00, S_1 = 01$
 $S_2 = 10, S_3 = 11$

Binary-Coded State Table

Present State	Next State		Output z
	x = 0	x = 1	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

Recall: Moore FSM Structure

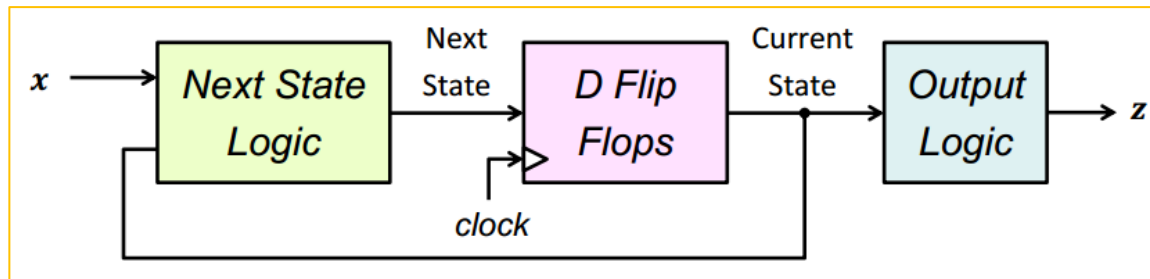

In this Design, Only **D-FF** will be used

Example: **Sequence Detector** **Boolean Equations (D-FF)**

Present State	Next State		Output Z
	x = 0	x = 1	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

2 State Bits → 2 Flip-Flops
 Label: State Bits (FFs) → **A,B**



1-D form is easier to derive Equations

Present State		Input x	Next State		Output Z
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Recall: When Using **D-FF**

Next State = Flip-Flop Inputs D_1 and D_0

Example: Sequence Detector **Boolean Equations (D-FF)**


Present State		Input <i>x</i>	Next State		Output <i>Z</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

$$A(t+1) = D_A(A,B,x) = \Sigma(3, 5, 7)$$

$$B(t+1) = D_B(A,B,x) = \Sigma(1, 5, 7)$$

$$Z(A,B,x) = \Sigma(6,7)$$


FF-Inputs/Output Simplification

 

$$D_A = A\bar{B} + Bx$$

$$D_B = Ax + B'x$$

$$Z = AB$$

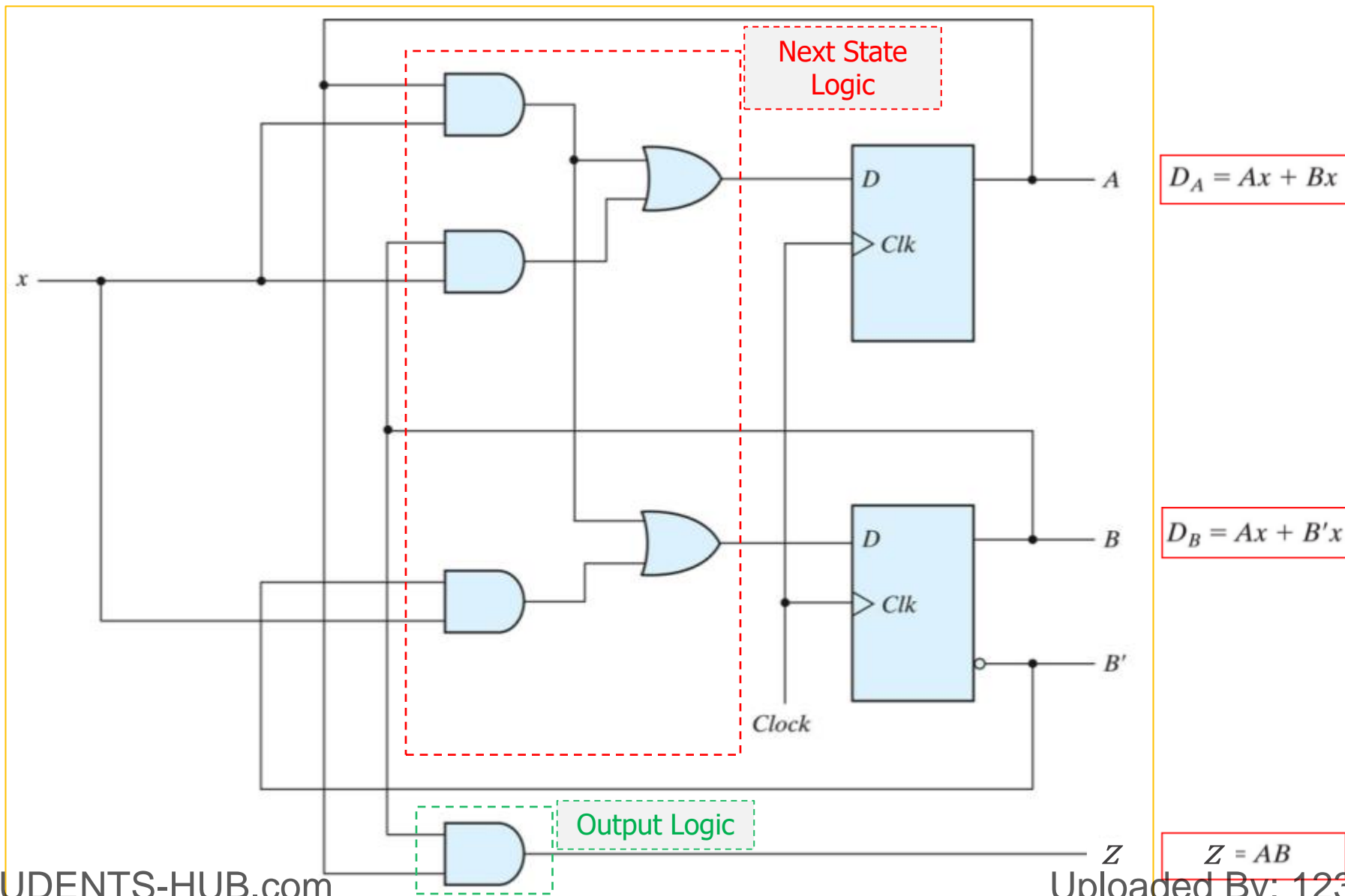Example:**Sequence Detector****Logic Circuit Diagram**


Example: Sequence Detector – Mealy FSM

Recall: in **Mealy** FSM

Change in State Diagram

At **S₂**, when the next **input** is **1** → the **output** should be **1**
 Make a **transition** from **S₂** **back to itself** labeled **1 / 1**
 No need for state **S₃**, because output is on the line/arrow

 Each line/arrow is **labeled** with: **Input / Output**
 The **output** is shown on the line/arrow of the state diagram



State Diagram

Mealy FSM typically use **less states** than Moore FSM

Binary-Coded State Table

Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₀	S ₂	0	0
S ₂	S ₀	S ₂	0	1

State Assignment
S₀ = 00, S₁ = 01
S₂ = 10
State 11 → Unused

Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	0
01	00	10	0	0
10	00	10	0	1

Example: Sequence Detector – Mealy FSM


Binary-Coded State Table

Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	0
01	00	10	0	0
10	00	10	0	1
11	XX	XX	X	X

2 State Bits → 2 Flip-Flops

Label: State Bits (FFs) → Q_1, Q_0

 
Unused States → **Don't Care Conditions in Next States & Output**



Boolean Equations (D-FF)

Example: Sequence Detector – Mealy FSM

Logic Circuit Diagram

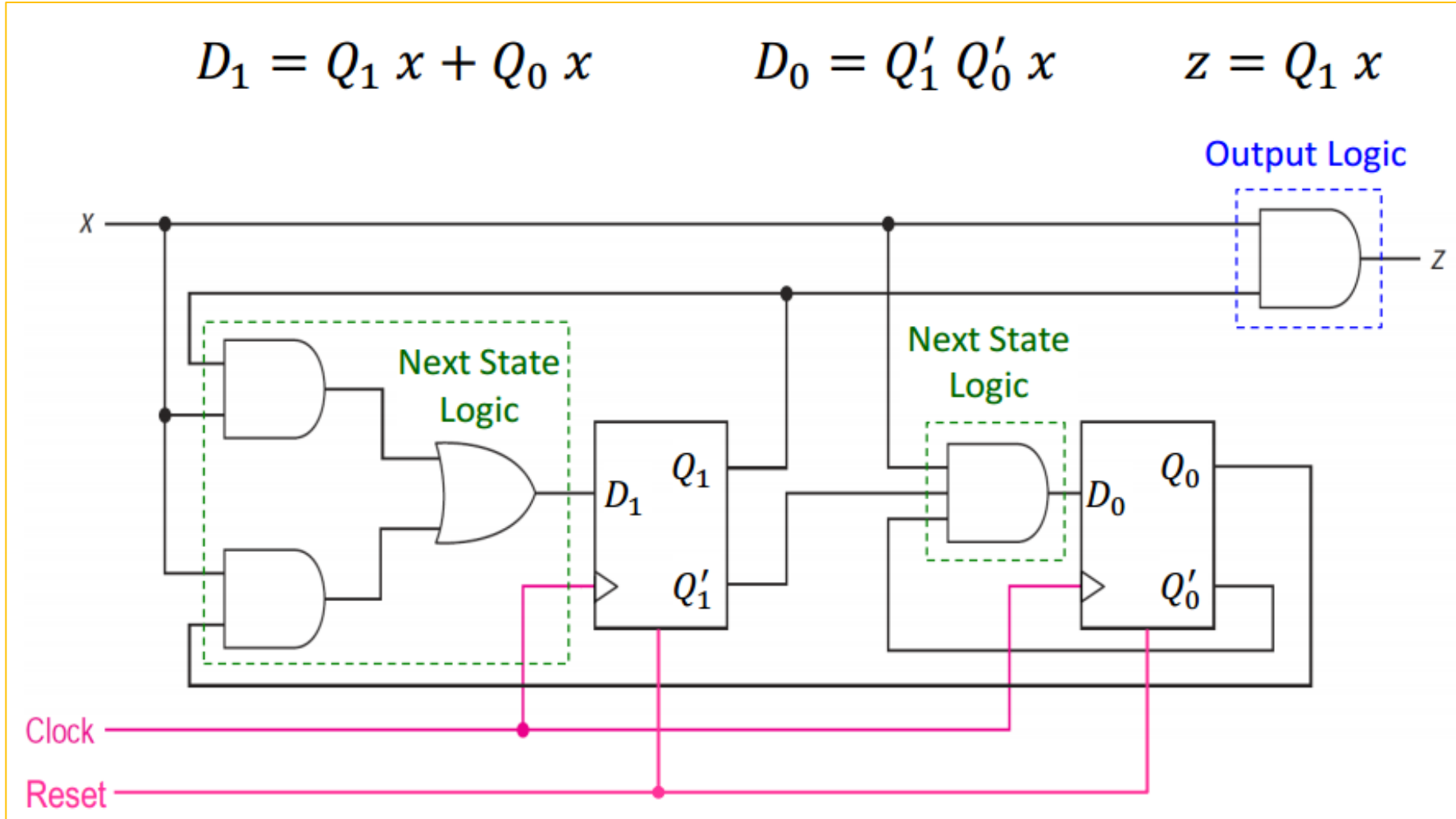



Design/Circuit Verification


- Sequential circuits should be **verified** by showing that the circuit **produces** the **original** state diagram
- Verification can be done **manually**, or with the help of a **simulation** program
- All** possible input **combinations** are applied at **each** state and the **state variables and outputs** are **observed**
- A **reset** input is used to **reset** the circuit to its **initial** state
- Apply a **sequence** of **inputs** to **test all the state-input combinations**, i.e., **all transitions** in the state diagram
- Observe** the **output and the next state** that appears **after each clock edge** in the timing diagram

Input Test Sequence


- Required to **verify the correct operation** of a sequential circuit
- It should **test each state transition** of the state diagram
- Test sequences can be **produced from the state diagram**
- Consider the **Mealy** sequence detector, starting at S_0 (reset), we can use the following input test sequence to verify all state transitions:

Input test sequence: **reset** then $x = 0, 1, 0, 1, 1, 0, 1, 1, 1, 1$

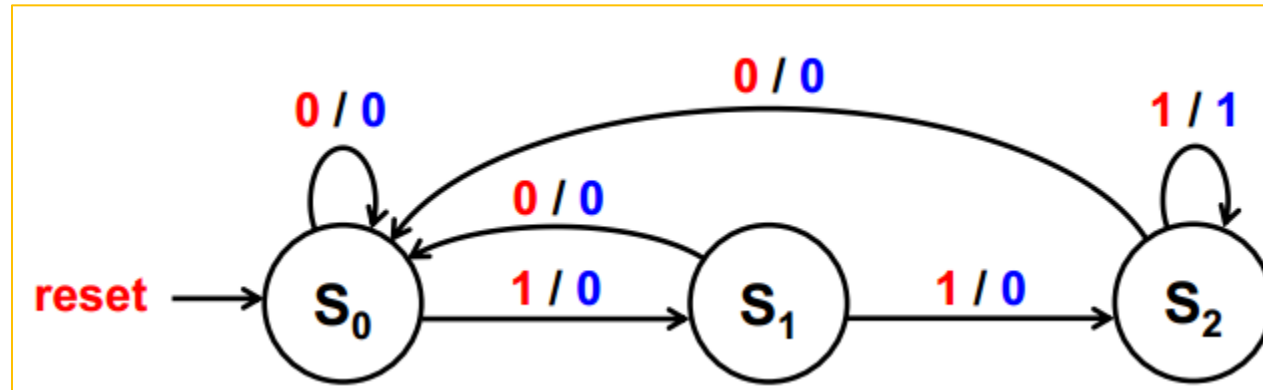
Reset input
forces initial
state to be S_0



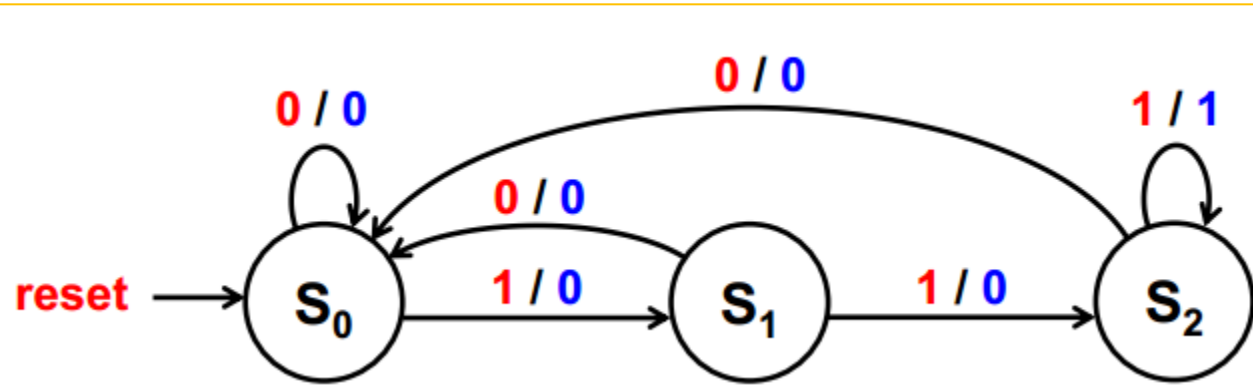Sequence Detector – Mealy FSM Timing Diagram



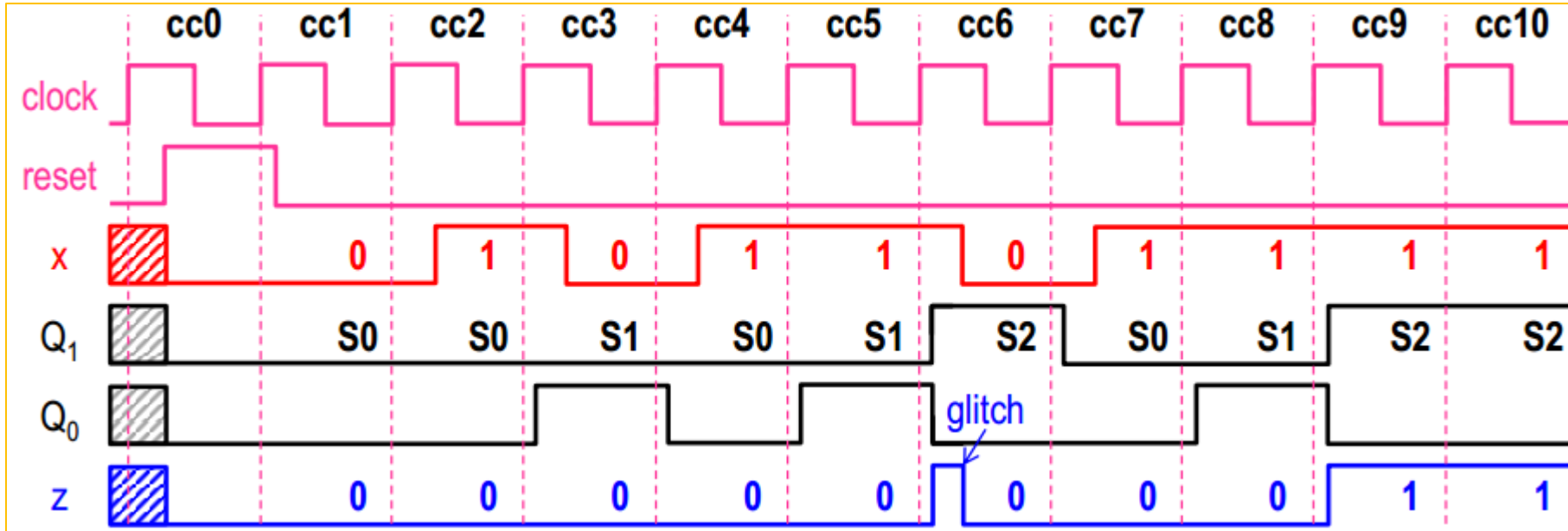Input test sequence: **reset** then $x = 0, 1, 0, 1, 1, 0, 1, 1, 1, 1$



Recall: The drawback of Mealy is that **glitches** can appear in the output if the input is not synchronized with the clock

- ☉ **Recall:** In the design of clocked sequential circuits, we **know** the **present** state and **next** state of the flip-flops
- ☉ We need to find the flip-flop **input functions/equations** and the **output functions /equations** in order to design the combinational circuit part of the circuit
- ☉ These **functions/equations** can be easily obtained using the **flip flop excitation table**
- ☉ **Excitation Tables** give us the **required inputs** that will **achieve** a given **transition** from preset state (PS) to next state (NS) [i.e. Q_t to Q_{t+1}]

Flip-Flop Excitation Tables

$Q(t)$	$Q(t = 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a) *JK* Flip-Flop

$Q(t)$	$Q(t = 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) *T* Flip-Flop

What about
D Flip-Flop
Excitation
Table?

List the inputs that will **cause** the **state change** in the **state table**

J	K	$Q(t + 1)$		$Q(t)$	$Q(t = 1)$	J	K
0	0	$Q(t)$	No change	0	0	0	X
0	1	0	Reset	0	1	1	X
1	0	1	Set	1	0	X	1
1	1	$Q'(t)$	Complement	1	1	X	0

Characteristic Table
Excitation Table

Recall: If **present** state is **0**, and **next** state is **1**, then you either had a **Toggle** ($J=1, K=1$) or you had a **set** ($J=1, K=0$)

Recall: If **present** state is **0**, and **next** state is **0**, then you either had a **NC** ($J=0, K=0$) or you had a **reset** ($J=0, K=1$)

Side Note: **Synthesis** is a design procedure that follows some **predefined** steps.

Sequence Detector – Using JK-FF

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

From **State transitions**, and using the **excitation table** of a JK-FF, derive the JK-FF inputs

Sequence Detector – Using JK-FF

Boolean Equations (JK-FF)

		B			
		Bx	00	01	11
A	0	m_0	m_1	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 X	m_6 X
		x			
		$J_A = Bx'$			


		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3 X	m_2 X
	1	m_4	m_5	m_7 1	m_6
		x			
		$K_A = Bx$			

		B			
		Bx	00	01	11
A	0	m_0	m_1 1	m_3 X	m_2 X
	1	m_4	m_5 1	m_7 X	m_6 X
		x			
		$J_B = x$			

		B			
		Bx	00	01	11
A	0	m_0 X	m_1 X	m_3	m_2 1
	1	m_4 X	m_5 X	m_7 1	m_6
		x			
		$K_B = (A \oplus x)'$			

Sequence Detector – Using JK-FF

Circuit Diagram (JK-FF)

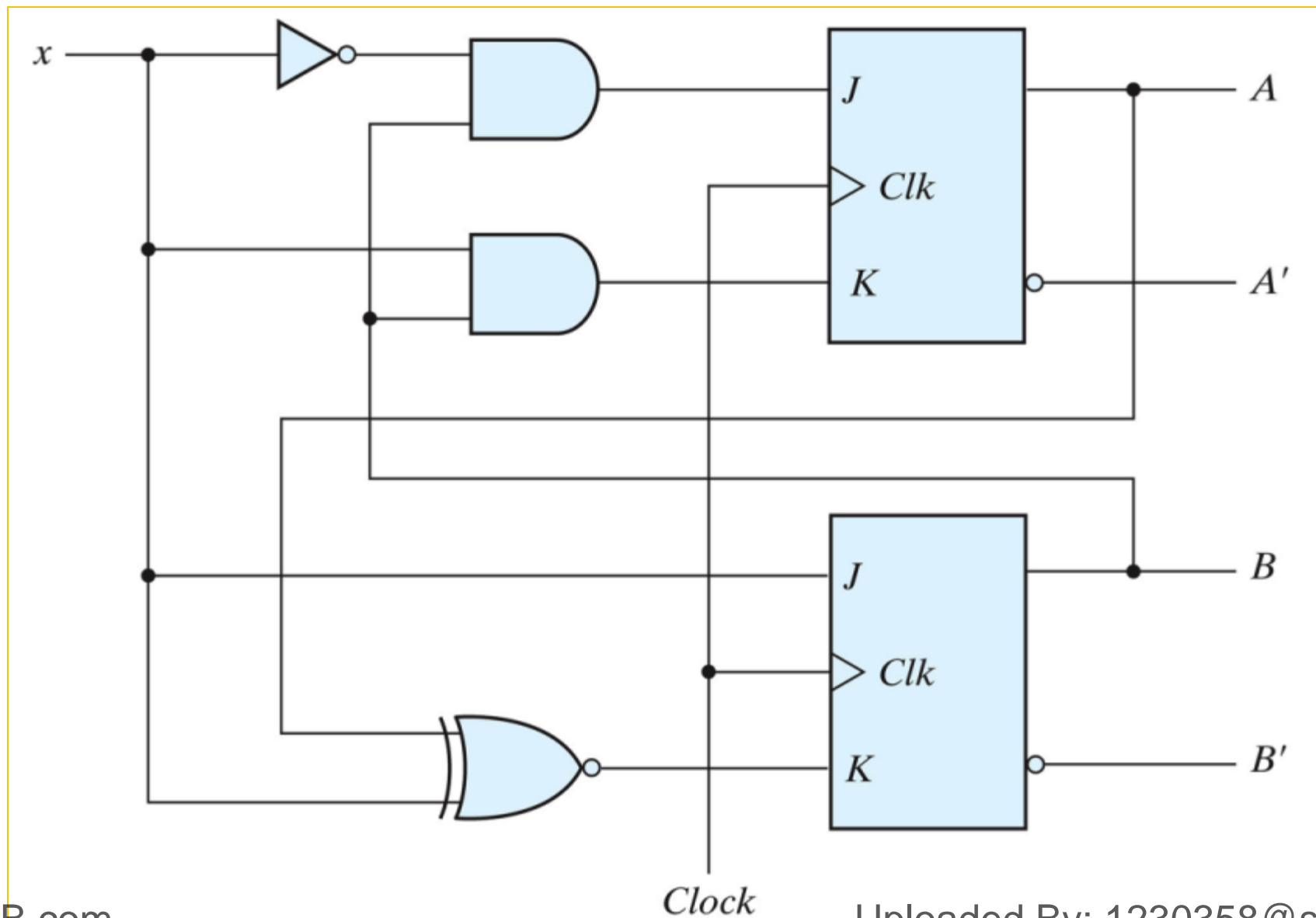

T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Characteristic Table

$Q(t)$	$Q(t = 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table

Recall: If **present** state and **next** state are **different** \rightarrow **Toggle** ($T=1$)

Recall: If **present** state and **next** state are **same** \rightarrow **NC** ($T=0$)

**Example:**

Design a circuit that **counts up** from **0 to 7 then back to 0**

- ✓ When reaching **7**, the counter **goes back** to **0** then **repeat**
- ✓ There is **no input** to the circuit
- ✓ The counter is **incremented each cycle**
- ✓ The **output** of the circuit is the **present** state (count value)
- ✓ The circuit should be designed using **T-type** Flip-Flops


State Diagram

- 1) **Eight** states are needed to store the count values 0 to 7
- 2) **No input**, state **transition** happens at the **edge** of each cycle

State Assignment

- 1) **Eight** states \rightarrow 3 State Bits \rightarrow **3** FFs
- 2) **State Assignment (000 – 111)**

State Reduction is NOT necessary

 Example: Up Counter**State Diagram**


3 State Bits → 3 Flip-Flops

Label: State Bits (FFs) →
 A_2, A_1, A_0


Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

From **State transitions**, and using the **excitation table** of a T-FF, derive the T-FFs inputs

Example: Up Counter

 


Boolean Equations (T-FF)

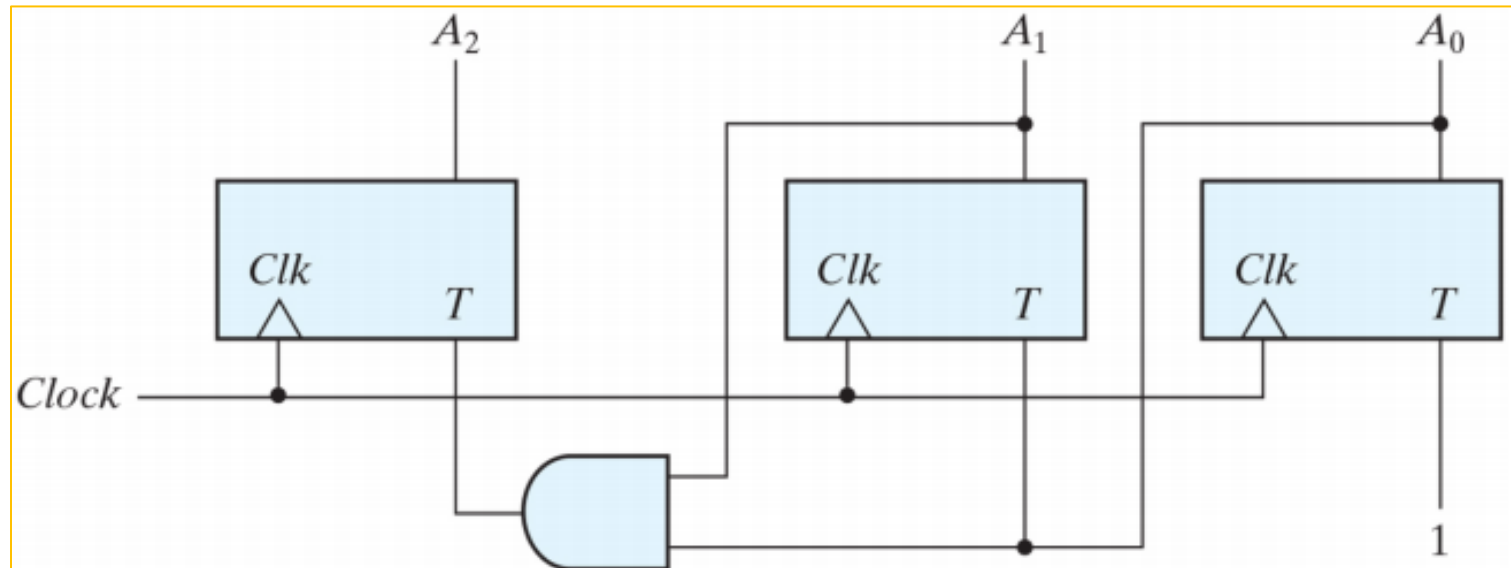

Circuit Diagram

Practice Problem:

 Design a one-input(x), one-output(y) serial 2's complement with asynchronous reset



Present state	Input	Next state	Output
A	x	A	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

