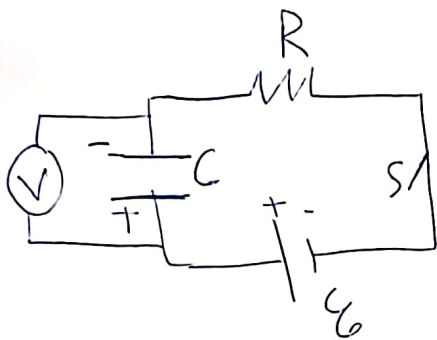


Exp 9 : RC - Circuit

The aim: is to find the time constant τ of an RC circuit and the value of its capacitor.

Theory



initially the capacitor is uncharged

$$\therefore Q_0 = 0 \text{ at } t = 0$$

when the switch is closed charge will start accumulating on the capacitor.

$$V_c = \frac{Q}{C}$$

Part A:

charging

by Kirchhoff's second rule.

$$\sum V_j = 0$$

$$\therefore \mathcal{E} - IR - \frac{Q}{C} = 0$$

$$I = \frac{dQ}{dt}$$

$$\mathcal{E} - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$\frac{dQ}{dt} = \frac{\mathcal{E}C - Q}{RC}$$

$$\int_0^Q \frac{dQ}{\mathcal{E}C - Q} = \int_0^t \frac{1}{RC} dt$$

let $u = \mathcal{E}C - Q$

$du = -dQ$

$$-\int \frac{du}{u} = \frac{1}{RC} \int_0^t dt$$

$$\ln \left[\frac{\mathcal{E}C - Q}{\mathcal{E}C} \right] = -t/RC$$

$$\therefore \frac{Q(t)}{C} = \frac{C\mathcal{E}}{C} \left(1 - e^{-t/RC} \right)$$

Changing

$$V(t) = \mathcal{E} \left(1 - e^{-t/RC} \right)$$

$$\tau = RC$$

time constant.




$$V(\tau) = \mathcal{E} (1 - e^{-1}) = 0.63\mathcal{E}$$

\therefore time constant : is the time needed for the potential difference on the capacitor $V(t)$ to reach 0.63 of the max voltage \mathcal{E}

Part B : Discharging

The capacitor has an initial potential difference ϵ and initial $Q = C\epsilon$

By removing $\frac{||}{\epsilon}$ \Rightarrow

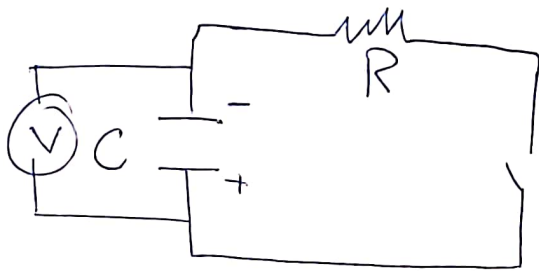

$$\sum V = 0$$

$$-I \cdot R - \frac{Q}{C} = 0 \Rightarrow I = \frac{dQ}{dt}$$

$$-\frac{dQ}{dt} R - \frac{Q}{C} = 0$$

divide by RQ

$$\int_{Q_0}^{Q(t)} \frac{dQ}{Q} = \int_0^t \frac{-dt}{RC}$$

$$Q(t) = Q_0 e^{-t/RC} = \epsilon C e^{-t/RC}$$


$$V(t) = \frac{Q(t)}{C} = \mathcal{E} e^{-t/RC}$$

time constant $t = \tau = RC$

$$V(\tau) = \mathcal{E} e^{-1}$$

$$V(\tau) = 0.37 \mathcal{E}$$

Calculation

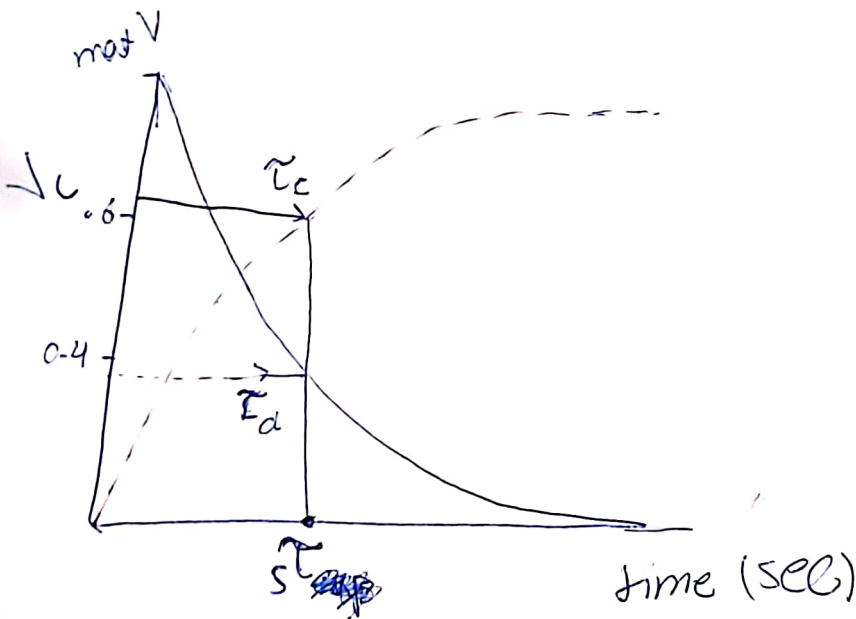

semi-log graph papers

page 33

$$\tau_{exp} = \frac{\tau_d + \tau_c + \tau_s}{3}$$

$$\tau_{theo} = RC$$

time	V charging	V discharging
0		
5		
10		
15		
⋮		
60		
70		
80		
⋮		
120		
140		

$$\textcircled{1} \quad C = \frac{\bar{I}}{R_{\text{exp}}}$$

R color code

$$\frac{\Delta C}{C} = \frac{\Delta \bar{I}}{\bar{I}} + \frac{\Delta R}{R}$$

$\Delta \bar{I} = \delta_m(\bar{I})$ for the three values.

$\textcircled{2}$ to find the slope of the line using this relation

$$\text{slope} = m = \frac{E_m(V_2) - E_m(V_1)}{E_2 - E_1}$$