

# ENEE2304

## Circuit Analysis


### Chapter 3 Analysis of Simple Resistive Circuits

1

**Reading Assignment:** Chapter 3 in *Electric Circuits, 10<sup>th</sup> Edition* by Nilsson
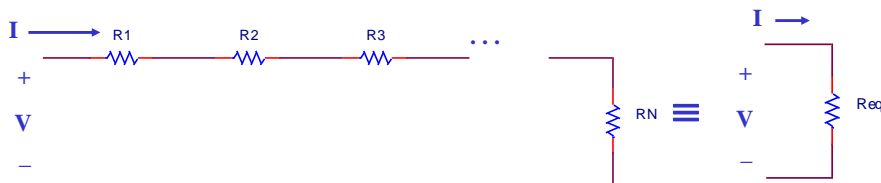
#### Series Resistance

Two or more resistors in series can be replaced by a single equivalent resistance,  $R_{eq}$ , as shown below.



We use KVL to show that:


$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_N$$

$$V = IR_1 + IR_2 + IR_3 + \dots + IR_N$$

$$V = I(R_1 + R_2 + R_3 + \dots + R_N)$$

$$V = I(R_{eq}); \text{ where } R_{eq} = R_1 + R_2 + R_3 + \dots + R_N$$


## Resistors in series

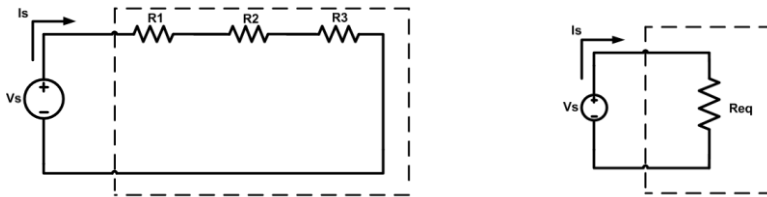

$$R_{eq} = R_1 + R_2 + R_3$$
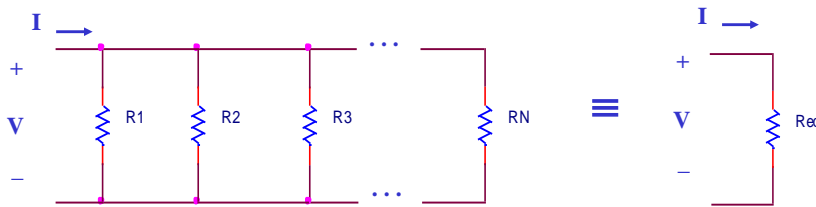
### Parallel Resistance

Two or more resistors in parallel can be replaced by a single equivalent resistance,  $R_{eq}$ , as shown below.




Use KCL to show that:

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots + \frac{V}{R_N}$$

$$I = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N} \right) \quad \therefore R_{eq} = \frac{V}{I} = \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N} \right)}$$

## Resistors in parallel

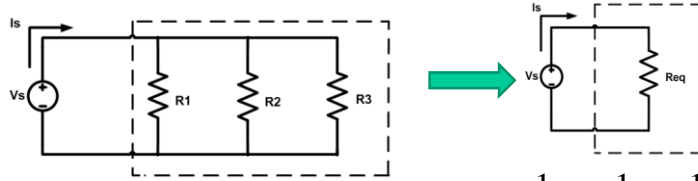

Two Resistors in parallel :

$$R_1 // R_2 = R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


$$= \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 // R_2 < \min(R_1, R_2)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

6

## Find $V_x$ ?

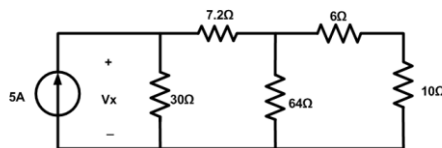


$$16 // 64 = \frac{(16)(64)}{16 + 64}$$

$$= 12.8 \Omega$$

$$12.8 + 7.2 = 20 \Omega$$

$$20 // 30 = \frac{(20)(30)}{20 + 30}$$



$$= 12 \Omega$$

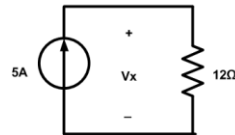

$$V_x = (5) (12) = 60 \text{ V}$$

7

## Find I?

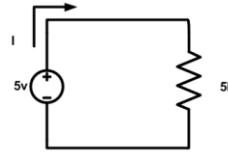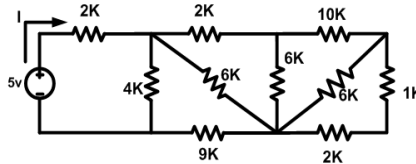

Start at the Right

$$(1 + 2) // 6 = \frac{(3)(6)}{3 + 6} = 2k\Omega$$

$$(2 + 10) // 6 = \frac{(12)(6)}{12 + 6} = 4k\Omega$$

$$(2 + 4) // 6 = 3k\Omega$$



$$(3 + 9) // 4 = 3k\Omega$$

$$\therefore R_{eq} = (3 + 2) = 5k\Omega$$

$$I = \frac{5v}{5k} = 1mA$$

8

## Voltage divider Rule

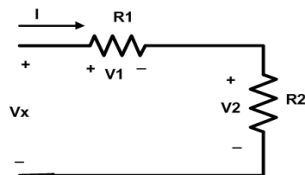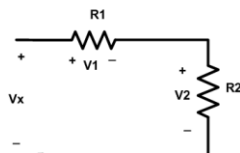

$$V_1 = \frac{R_1}{R_1 + R_2} V_x$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_x$$

$$V_x = V_1 + V_2$$


$$= I R_1 + I R_2$$

$$\therefore I = \frac{V_x}{R_1 + R_2}$$

$$V_1 = R_1 I = V_x \frac{R_1}{R_1 + R_2}$$

$$V_2 = R_2 I = V_x \frac{R_2}{R_1 + R_2}$$

## Find $V_x$ ?

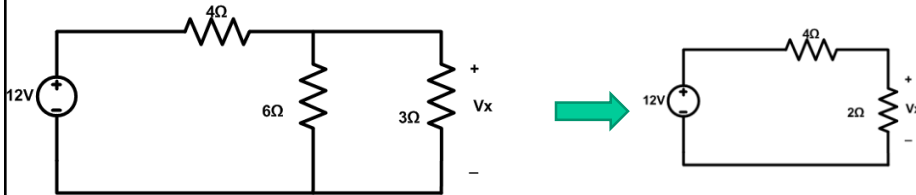


$$3\Omega // 6\Omega = 2\Omega$$

$$V_x = 12 \frac{2}{2+4} = 4V$$

10

## Current Divider Rule

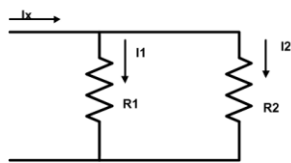


$$I_1 = \frac{R_2}{R_1 + R_2} I_x$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_x$$


$$I_x = I_1 + I_2$$
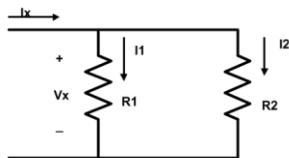
$$I_x = \frac{V_x}{R_1} + \frac{V_x}{R_2}$$



11

## Proof

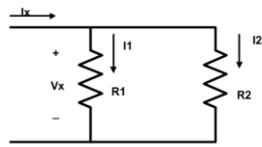


$$V_x = \frac{R_1 R_2}{R_1 + R_2} I_x$$

$$I_1 = \frac{V_x}{R_1} = \frac{R_2}{R_1 + R_2} I_x$$

$$I_2 = \frac{V_x}{R_2} = \frac{R_1}{R_1 + R_2} I_x$$

12


## Find I3?

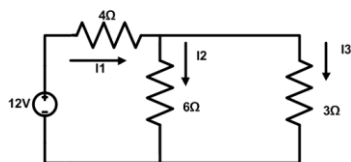

$$I_3 = \frac{6}{6+3} I_1$$


$$I_1 = \frac{12 \text{ V}}{(4+2)\Omega} = 2 \text{ A}$$
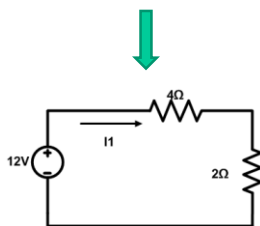
$$I_3 = \frac{6}{6+3} 2 = 1.33 \text{ A}$$



13

## Find $V_o$ ?

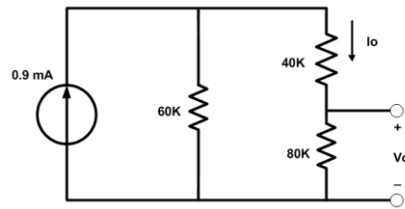

$$V_o = I_o \cdot (80 \text{ k}\Omega)$$


$$I_o = \frac{60 \text{ k}\Omega}{60 \text{ k}\Omega + (80 \text{ k}\Omega + 40 \text{ k}\Omega)} 0.9 \text{ mA}$$

$$I_o = 0.3 \text{ mA}$$


$$V_o = I_o \cdot (80 \text{ k}\Omega) = 24 \text{ V}$$

14

## Find $I_o$ ?

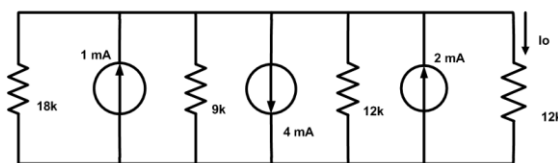
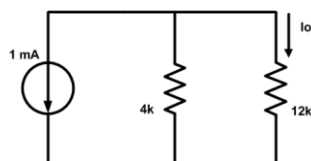
$$18\text{k} \parallel 9\text{k} \parallel 12\text{k} = 4\text{k}$$




$$I_o = -\frac{4\text{k}}{4\text{k} + 12\text{k}} 1\text{mA}$$

$$I_o = -0.25\text{mA}$$

15

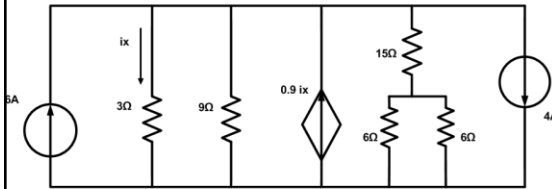Find the power supplied by the  $0.9 i_x$  source?



- The 6A and 4A sources are combined into one source pointing up
- The two  $6\ \Omega$  resistors are in parallel, and result is in series with  $15\ \Omega$
- The resulting  $18\ \Omega$  is in parallel with  $9\ \Omega$  yielding  $6\ \Omega$

Find the power supplied by the  $0.9 i_x$  source?

KCL :

$$2 + 0.9i_x = i_x + \frac{V_x}{6}$$


$$i_x = \frac{V_x}{3}$$

$$2 + 0.9i_x = i_x + \frac{3i_x}{6}$$

$$2 = 0.6i_x$$

$$i_x = \frac{2}{0.6} = \frac{10}{3} = 3.33\text{ A}$$

$$V_x = 3i_x = 10\text{ V}$$

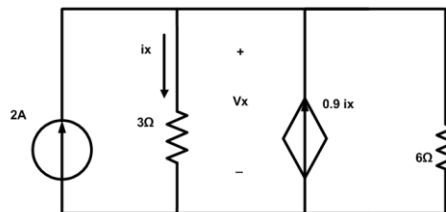

$$P_{(0.9i_x)} = -(0.9i_x)(V_x)$$


$$= -\left(0.9\left(\frac{10}{3}\right)\right)(10)$$

$$= -30\text{ W supplying}$$




**Bridge Circuits**

One type of resistive circuit that cannot be simplified through series and/or parallel combinations is the “bridge circuit.” A bridge circuit is shown below (drawn twice). Study the circuit to verify that there are no series resistors and no parallel resistors.

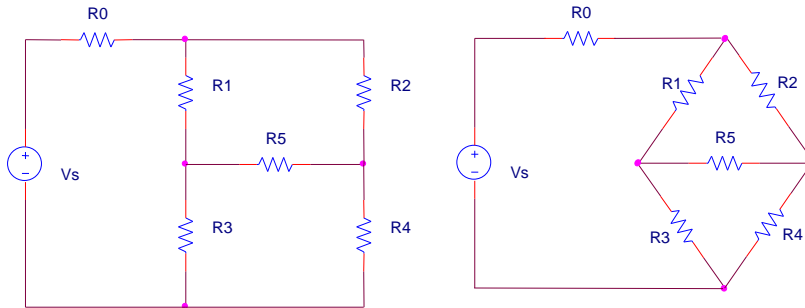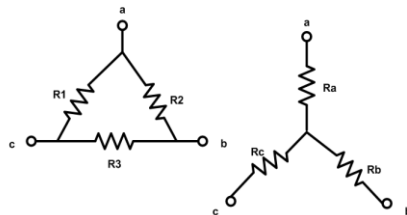**Delta-to-Wye ( $\Delta$ -Y) and Wye-to-Delta (Y- $\Delta$ ) Transformations**

Bridge circuits contain resistors that are connected in delta ( $\Delta$ ) and wye (Y) configurations. One way to analyze this circuit is to use a  $\Delta$ -Y or a Y- $\Delta$  transformation.

Y and  $\Delta$  connections of resistors are shown below:




If the wye and delta circuits to be equivalent, then they should provide the same resistance between each pair of terminals (a-b, b-c, and c-a).

**Development:** Determine the resistance seen at each set of terminals and equate them as follows:

$$R_{a-b} (\text{Delta}) = R_{a-b} (\text{Wye})$$

$$R_{b-c} (\text{Delta}) = R_{b-c} (\text{Wye})$$
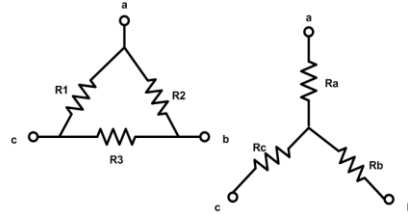
$$R_{c-a} (\text{Delta}) = R_{c-a} (\text{Wye})$$



$$R_{ab} = R_a + R_b = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{bc} = R_b + R_c = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{ca} = R_c + R_a = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

Solving this set of equations



Solving the equations on the previous page yields the following relationships:

*Y – Δ transformation*

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$


$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

*Δ – Y*

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$
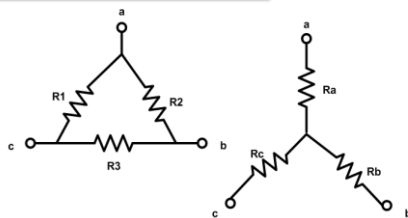
$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$



**Note:** The equations above must be used along with the circuit diagrams shown. The labeling of the resistors and nodes in the diagrams is critical.

### Solving the Equations

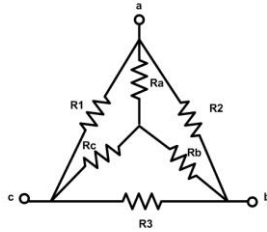

- For a balanced case where:

$$R_a = R_b = R_c = R_y$$

$$R_1 = R_2 = R_3 = R_\Delta$$

$$R_\Delta = 3 R_y$$

$$R_y = \frac{1}{3} R_\Delta$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$



$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$


### Find Req?

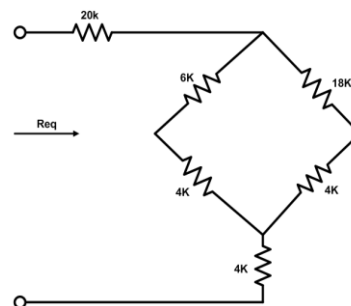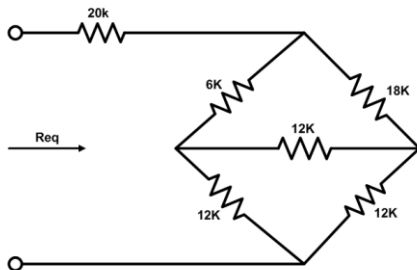

$$R_{eq} = 20k + 4k + (6k + 4k) \parallel (18k + 4k)$$

$$R_{eq} = 30.88k$$
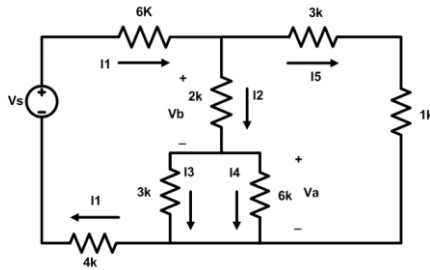
## Design: given $I_4 = 0.5\text{mA}$ , find $V_s$



$$V_a = (6k\Omega)(0.5\text{mA}) = 3V$$

$$I_3 = \frac{V_a}{3k} = 1\text{mA}$$

$$I_2 = I_3 + I_4 = 1.5\text{mA}$$

$$V_b = (2k\Omega)(1.5\text{mA}) = 3\text{V}$$

$$I_5 = \frac{V_a + V_b}{4k} = 1.5\text{mA}$$

$$I_1 = I_2 + I_5 = 3\text{mA}$$

$$V_s = (10k\Omega)I_1 + V_b + V_a = 36\text{V} \quad 24$$

## Measuring Voltage and current

- Ammeter: designed to measure current
- Voltmeter : designed to measure voltage

