


Exp 4: DC circuits

Part A: DC circuit with one resistor.

The aim of this part is finding R_1 (Exp., Theo.)

* $R_{1(\text{exp})}$:

I (mA)				...
V (V)				...

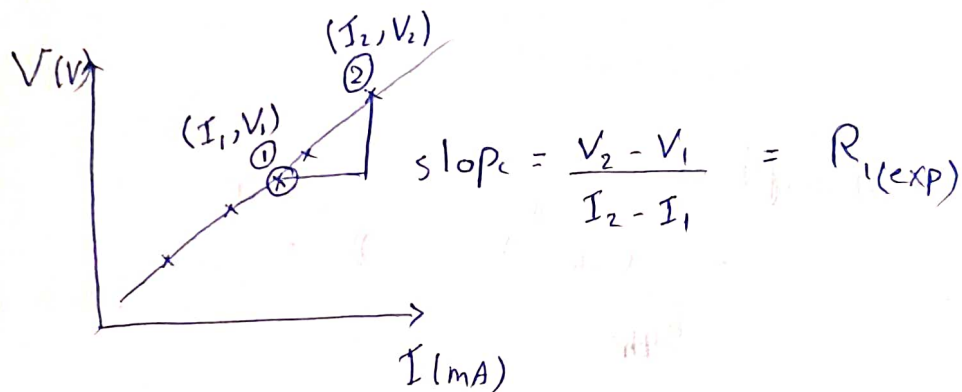


$$R = \frac{V}{I} \quad (\text{Ohm's Law})$$

$$\frac{\Delta R}{R} = \frac{\Delta V}{\bar{V}} + \frac{\Delta I}{\bar{I}}$$

ΔV , ΔI : The uncertainty in V & I from the smallest division on the scale of Voltmeter & Ammeter

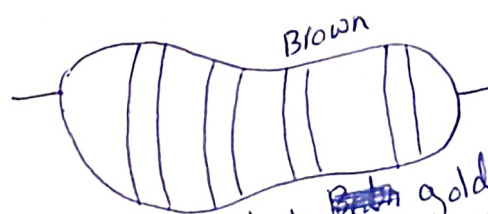$R_{1(\text{theo})}$: from the color code (page 89)



Carbonic Resistor

Brown Black ~~Black~~ gold
 $1 \quad 0 \times 10^{\pm} \quad 5\% (R)$ → ΔR_{theo}


$$R_{\text{theo}} = 100 \pm \frac{5}{100} (100) = 100 \pm 5 \Omega$$

* To test if R_1 is Accepted or not !!


Range test

$$R_{1,exp} = 105 \pm 7 \Omega \Rightarrow 98 \leq R_{exp} \leq 112$$

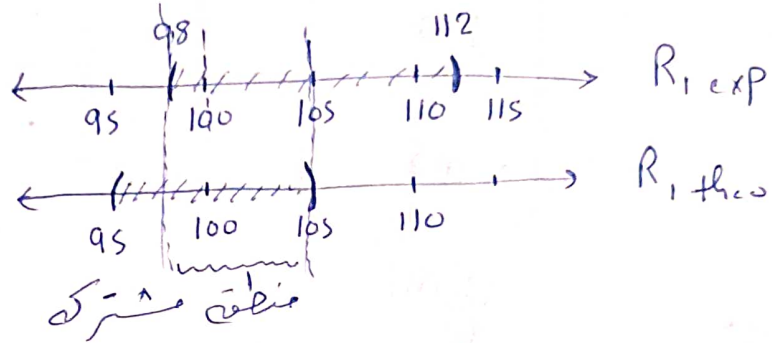
$$R_{1,theo} = 100 \pm 5 \Omega \Rightarrow 95 \leq R_{theo} \leq 105$$



⇒ Accepted

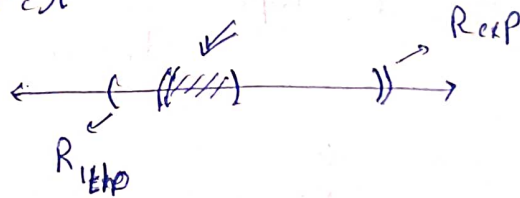

* if

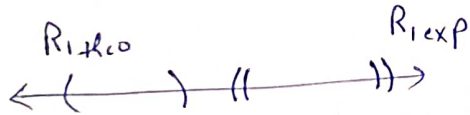


not accepted

Part B: DC circuit with Two Resistors connected
in Series
توالی

* Experimentally:

$$R_{s \text{ exp}} = \frac{V_s}{I_s}$$

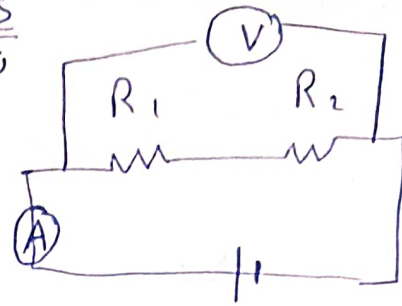

$$\frac{\Delta R_{s \text{ exp}}}{R_s} = \frac{\Delta V}{V_s} + \frac{\Delta I}{I_s}$$

$\Delta V, \Delta I$: The smallest division on the scale.

* Theoretically:

$$R_{s \text{ theo}} = R_1 + R_2$$

$$\Delta R_{s \text{ theo}} = \Delta R_1 + \Delta R_2$$


} from the color code

Part C: DC circuit with Two Resistors connected
in parallel
 على التوازي

+ EXP. :

$$R_{P(\text{exp})} = \frac{V_P}{I_P}$$
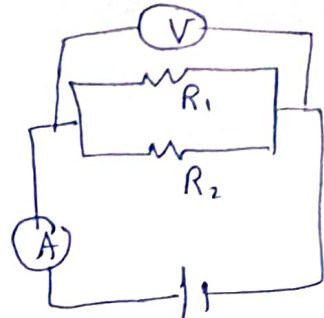
$$\frac{D R_{P(\text{exp})}}{R_{P(\text{exp})}} = \frac{D V_P}{V_P} + \frac{D I}{I_P}$$



+ Theo :

$$\frac{1}{R_{P(\text{theo})}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{P(\text{theo})} = \frac{R_1 R_2}{R_1 + R_2}$$

To find $D R_{P(\text{theo})}$:

$$\frac{D R_{P(\text{theo})}}{(R_{P(\text{theo})})^2} = \frac{D R_1}{|R_1|^2} + \frac{D R_2}{|R_2|^2}$$

$$\frac{D R_P}{R_{P(\text{theo})}^2} = \frac{D R_1}{R_1^2} + \frac{D R_2}{R_2^2}$$

from the
color code