

Experiment NO.4

Digital Circuits Implementation using Breadboard


Post Lab

Name : Mohammed Jamil Saada

ID : 1221972

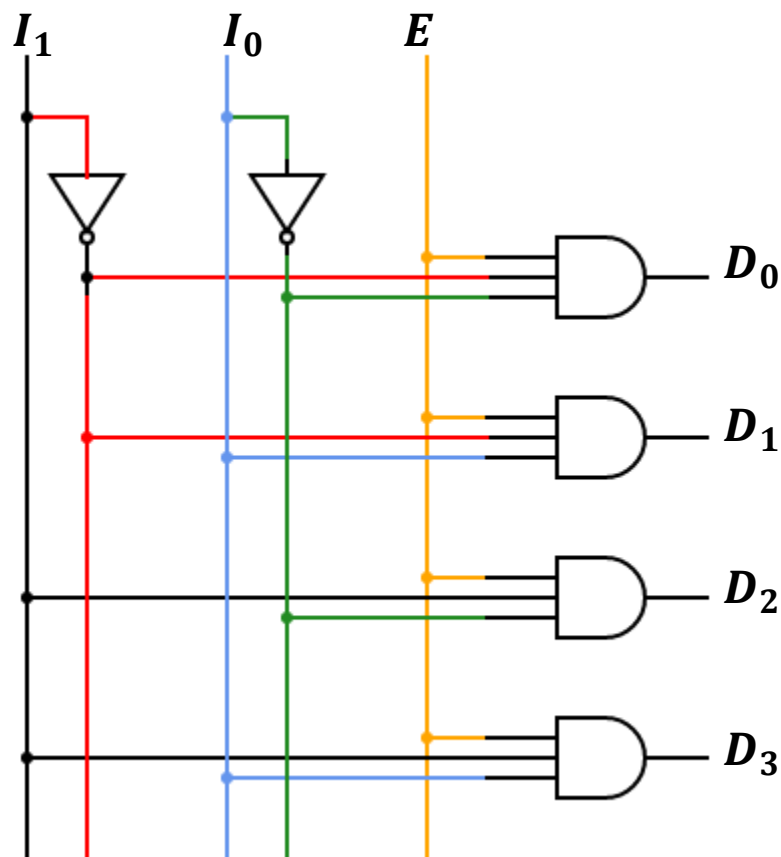
- 1) How do you go about adding an Enable (E) signal to the decoder in Figure 4.7? Modify the implementation to show that. (Design Only using chips in Figure 1).

To add an Enable to 2x4 decoder we will add a third input E to each AND gate as follow :




The truth table for this circuit as :

INPUTS			OUTPUTS			
I_1	I_0	E	D_0	D_1	D_2	D_3
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

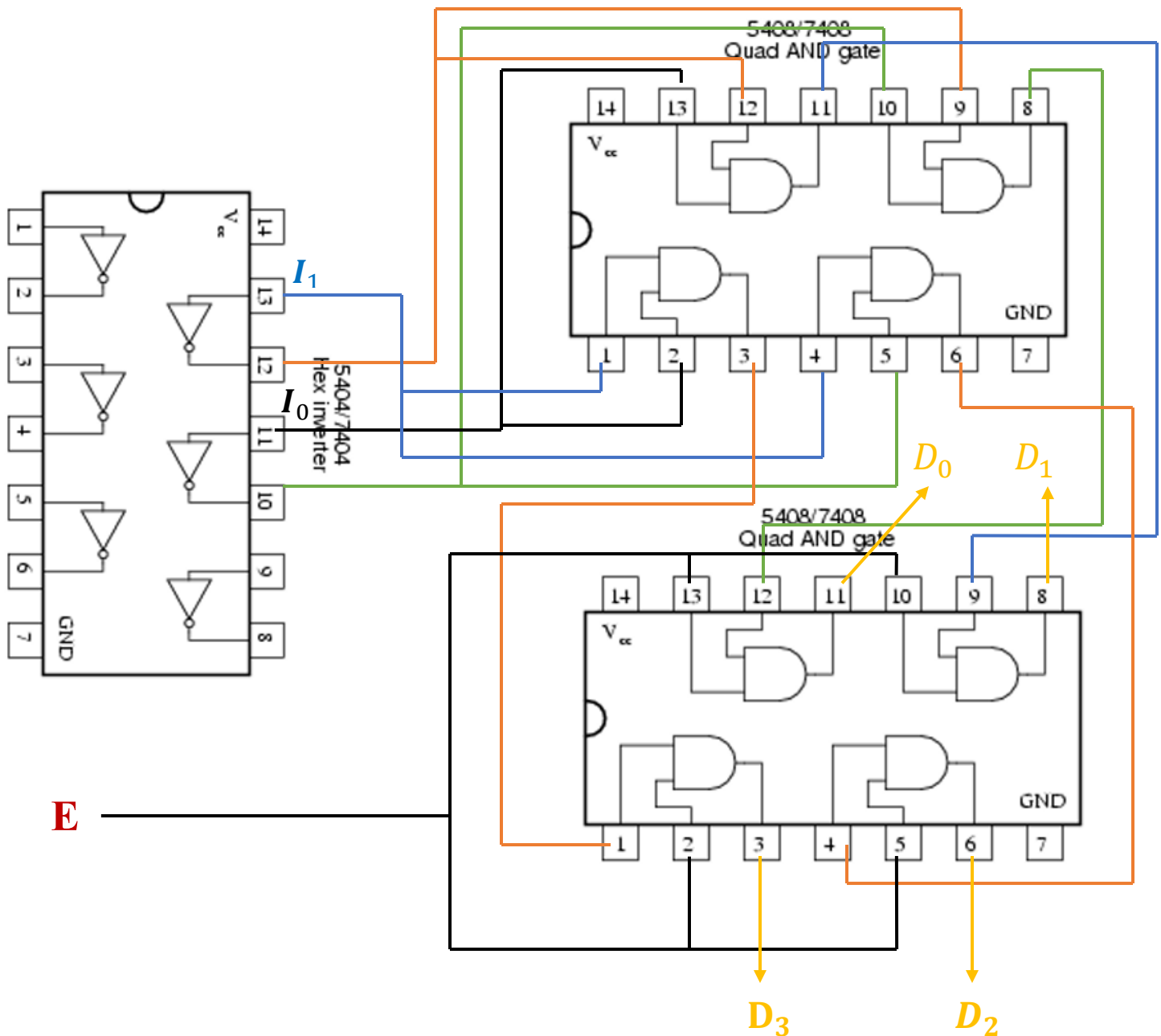


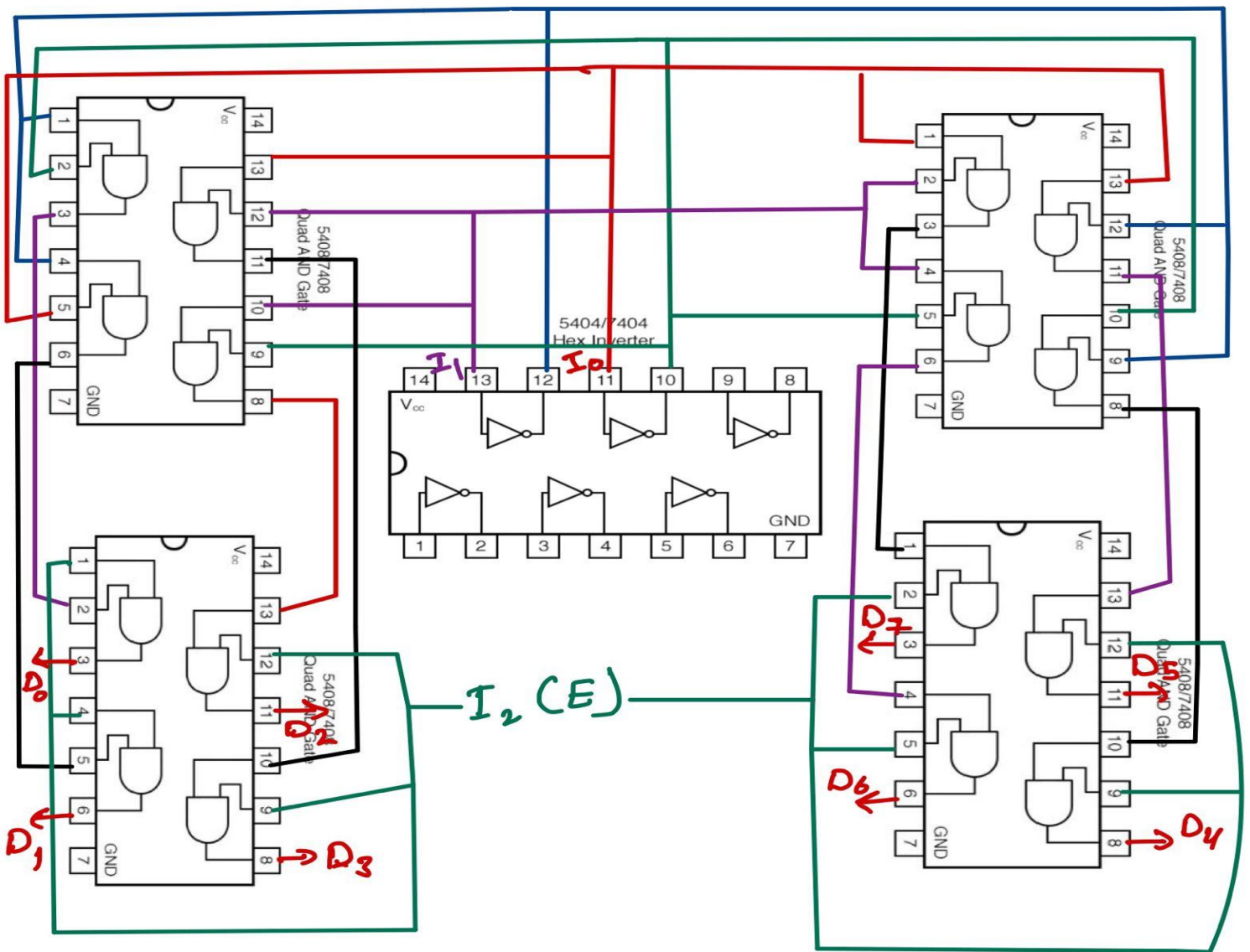
2) How to use that to implement a 3x8 decoder using chips in Figure 1.




We make I_2 the enable of both decoders, and use I_1 and I_0 as the inputs of the decoders.

- 3) Use the just constructed 4x1 multiplexer to design a three inputs network that gives 1 if the majority of its inputs are 1 and outputs a zero otherwise (Design Only using chips in Figure 1).

INPUTS			OUTPUTS	
A	B	C	F	F
0	0	0	0	0
0	0	1	0	
0	1	0	0	C
0	1	1	1	
1	0	0	0	C
1	0	1	1	
1	1	0	1	1
1	1	1	1	

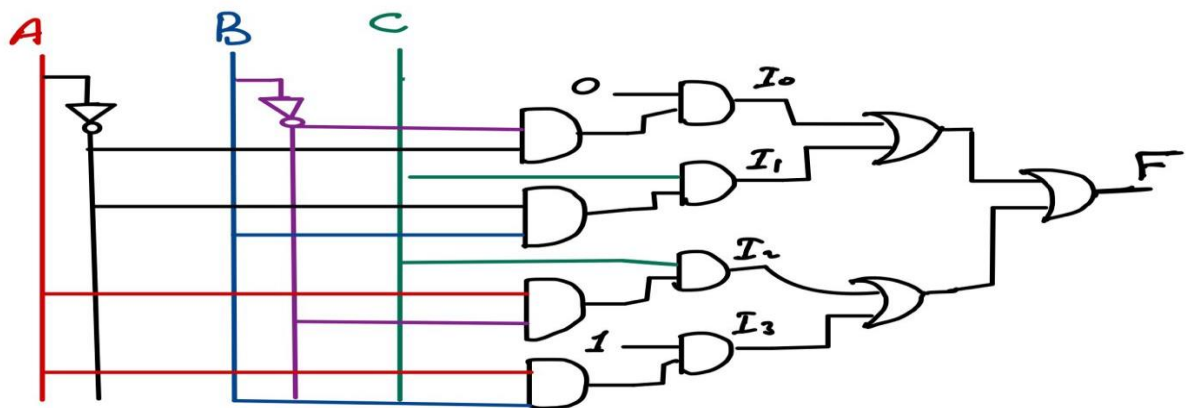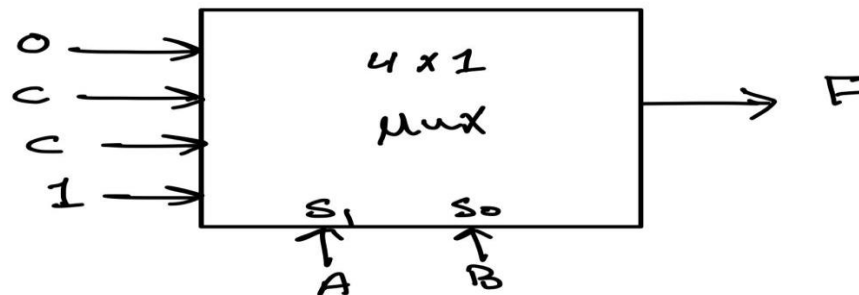

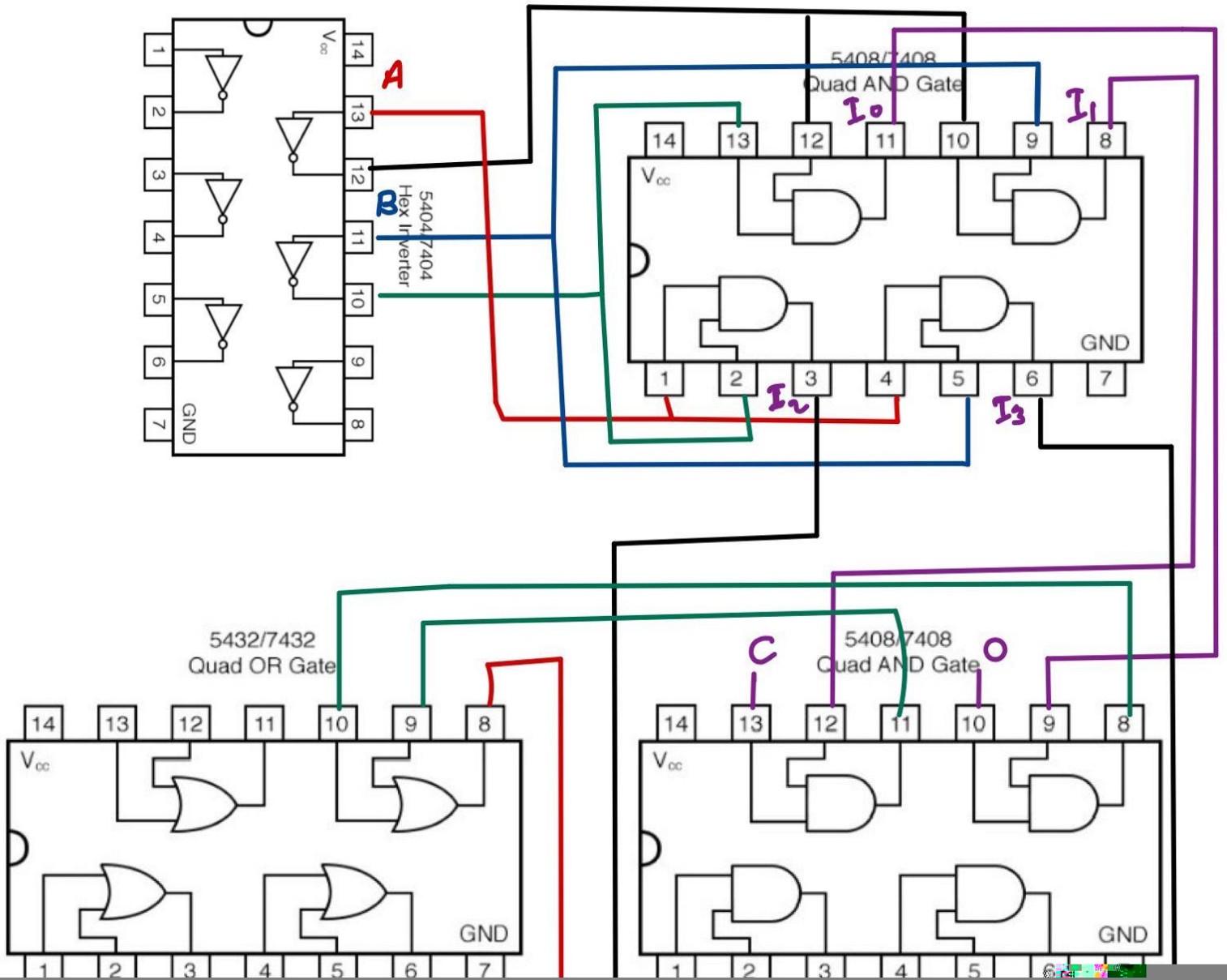

- 4) Implement $f(x, y, z) = m(0, 1, 4, 6, 7)$, using 4x1 MUX using chips in Figure 1.

$$f(x, y, z) = m(0, 1, 4, 6, 7)$$

Inputs			Outputs	
x	y	z	F	F
0	0	0	1	1
0	0	1	1	
0	1	0	0	0
0	1	1	0	
1	0	0	1	z'
1	0	1	0	
1	1	0	1	1
1	1	1	1	

