


chapter 10

$v = \frac{dw}{dq}$ w is energy in joules
 q is charge in coulombs

for DC $p = \frac{dw}{dt} = \left(\frac{dw}{dq}\right) \left(\frac{dq}{dt}\right)$

$p = vi$

supplying power

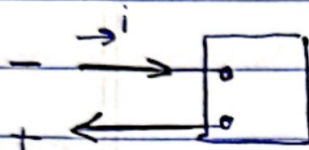

power absorbed


absorbed

$p = -vi$

supplied to : consumed
 delivered to : consumed

supplied by :
 delivered by :

circuit elements

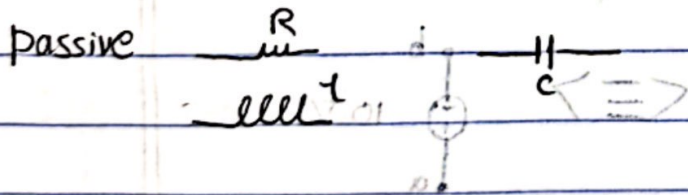

Active sources

pass or Active

البطارية في وضع discharge

Active

البطارية في وضع charge


passive

Active circuit elements

Batteries and Generators

non-electric energy → electric energy

~~non-electric energy~~

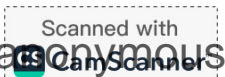

Short circuit $V=0$


Active elements

Independent Sources

Dependent Sources

1.1 Independent Sources

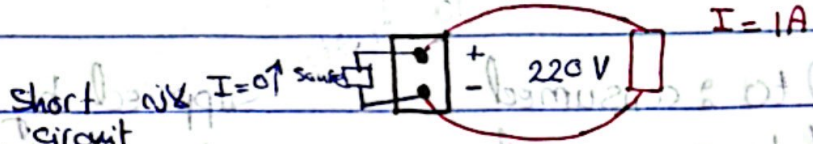
1.1.1 voltage source: It maintains a specific voltage across its terminal independent of the current that flows through it.



voltage source

جانب من طرفه في الطرف الأخرى


قيمة التيار

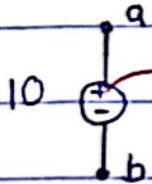


It represents the positive reference polarity

$V_{ab} = 10V$

$V_{ba} = -10V$

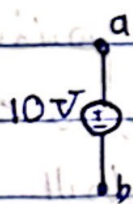


equivalent to

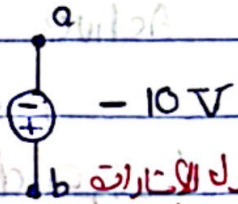

لتبديل الأقطاب


equivalent to

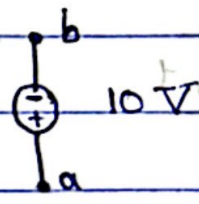


ويحافظ على Terminalين في الطرف الأخرى

Voltage sources


DC voltage source

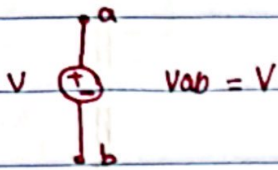




where V is constant

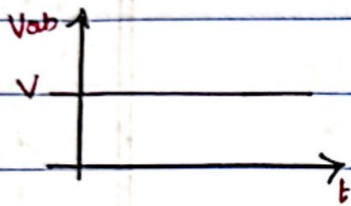


AC voltage source

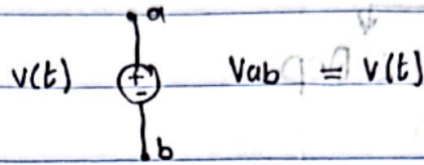


where $v(t)$ is a function of time

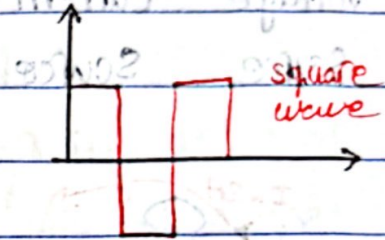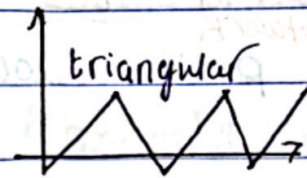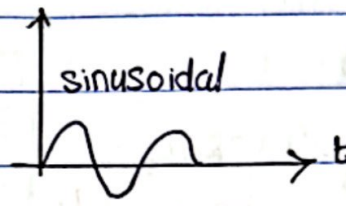

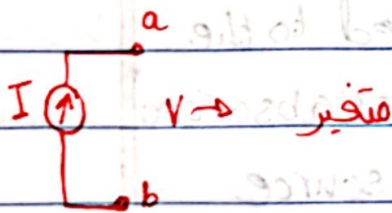
1.1.2 current source: It maintains a specific current through it independent of the voltage developed across its terminals.



DC "constant"

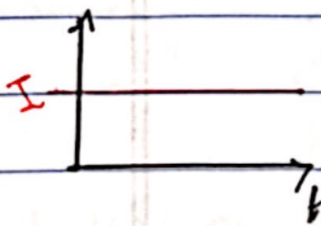

AC "Function of time"

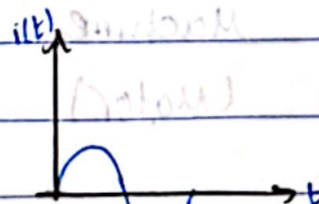

circuit Elements

① Active

② passive

1.1 Indep


1.2 Dep

1.1.1

1.1.2

Voltage Source

Current Source

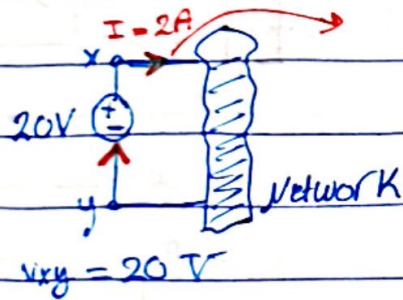

power for network


القدم داخله الى الب لوجب بوجبه

$$p = VI = 20(2) = 40W$$

delivered to the network

Machine or Battery

(generator) (Discharge mode)

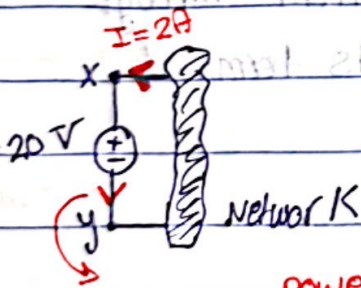

$$p = VI = 40W$$


delivered to the source or absorbed by the source

power بوجبه from network

Machine or Battery


(Motor) (Charging mode)

Ex 9

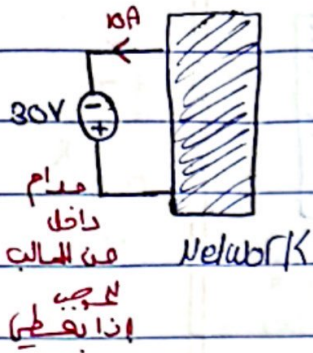

$P = 300 \text{ W}$ delivered to the network

Ex 10

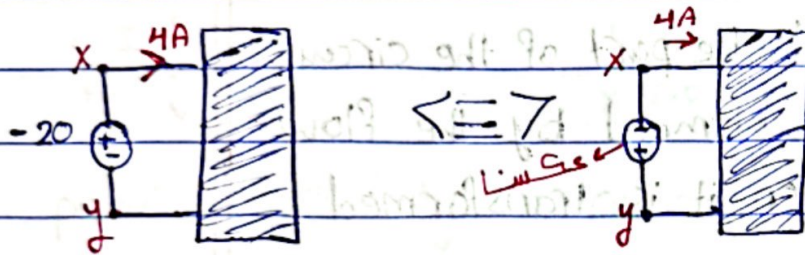

$P = 20(4) = 80 \text{ W}$ delivered to the source


1.2 Dependent sources (controlled sources):

They generate a voltage or a current that is determined by a voltage or current at a specified location in the circuit


Symbol

Examples (Transistors)

1.2.1 voltage source

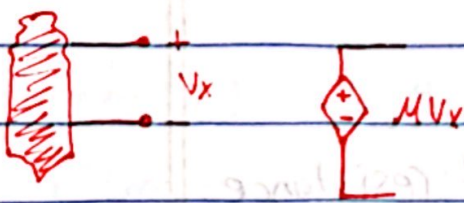

voltage controlled
voltage source

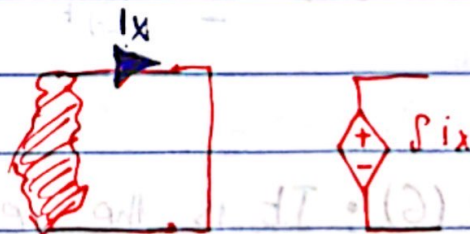


current controlled
voltage source

1.2.2 current source



current controlled current source

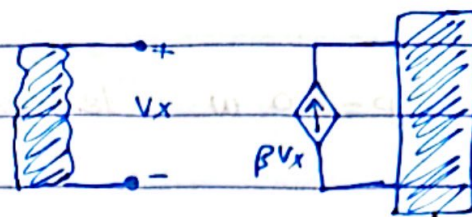


voltage controlled current source

2 passive Elements

2.1 Resistor (R): It represents the part of the circuit in which energy entering the element by the flow of current through it, and then it is transformed to heat.


The resistor is measured in ohms [Ω]

Resistor symbol


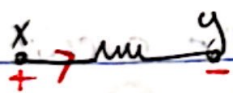


التيار يجرى من الألف إلى الألف

Exp:

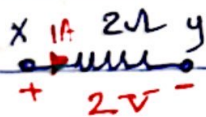

$$V = 2 \cdot 1 = 2V$$

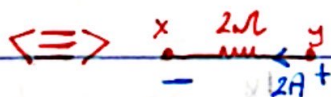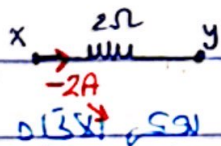


$$V = 4V$$

Conductance (G): It is the reciprocal of resistance and measured in [siemens or σ]

$$G = \frac{1}{R}$$


When $R=0 \Rightarrow V=RI$
 $=0$

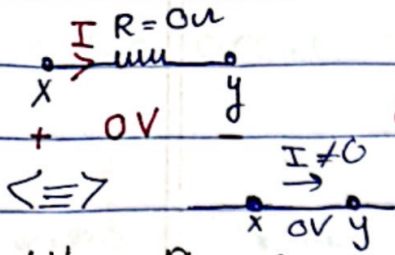

The element is called short circuit
 مرور تيار عالٍ (فوق حد) في مقاومة صفرية مع مقاومة صفرية

When $R = \infty$ open circuit

$I = \frac{V}{R} = \frac{V}{\infty} = 0$

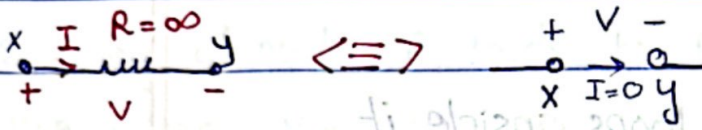

power absorbed by the resistor

$P = VI$ $P = \frac{V^2}{R}$ $P = I^2R$


Kirchhoff laws

↳ Kirchhoff's voltage law (KVL)

↳ Kirchhoff's current law (KCL)

Node: It is a point of connection of two or more circuit element.
 نقطة اتصال

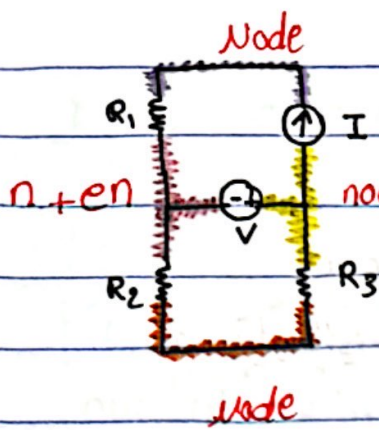
Essential node: It is a point of connection of three or more circuit elements.



2 ess
4 node

Loop: It is any closed path through the circuit such that no node is crossed more than once.

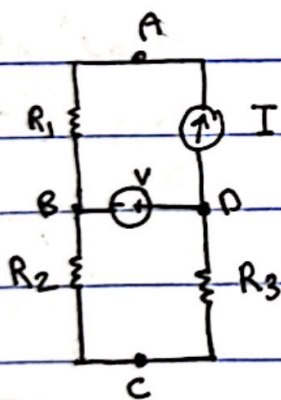Mesh: It is a loop with no loops inside it.




Loops: ABDA, BCDB, ABCDA

Meshs: ABDA, BCDB

not Mesh loops 2 loops

Kirchoff's current law (KCL)

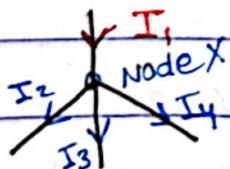The algebraic sum of all currents at any node in the circuit equals to zero.




$$I_1 = I_2 + I_3 + I_4$$

$$-I_1 + I_2 + I_3 + I_4 = 0$$

$$\sum_{i=1}^N I_i = 0$$

Kirchhoff's voltage Law (KVL)

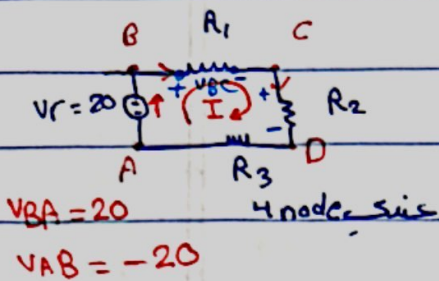The algebraic sum of all voltages around any closed path in the circuit is zero.



$V_{BA} =$
 يجب مكتوب
 في الكمية لانه
 بقدر اضع القطب
 الموجب

لما يكون بالداره بس مقاومات مستحيل المبر يكون
 motor لانه لازم مصدر فرق الجهد هو بي يوظي طاقة

Starting at node A leads to the expression

$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$

$$-V_s + R_1 I + R_2 I + R_3 I = 0 \quad \text{clockwise}$$

$$V_{AD} + V_{DC} + V_{CB} + V_{BA} = 0$$

$$-R_3 I - R_2 I - R_1 I + V_s = 0 \quad \text{counter}$$