

Q1: Two conductors are made of the same material and have the same length. Conductor A is a solid wire of radius 1.0 mm. Conductor B is a hollow tube of outside radius 2.2 mm and inside radius 1.0 mm. What is the resistance ratio R_A/R_B , measured between their ends?

$$V = IR$$

$$R = \frac{V}{I}$$


$$\frac{\rho L}{A}$$

$$A = 2\pi r$$

$$\frac{R_A}{R_B} = \frac{\frac{\rho L}{A_A}}{\frac{\rho L}{A_B}}$$

$$\frac{R_A}{R_B} = \frac{\rho L}{A_A} \cdot \frac{A_B}{\rho L}$$
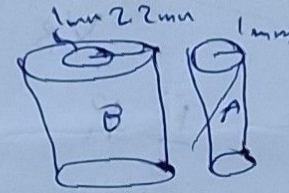
$$\frac{R_A}{R_B} = \frac{1}{2\pi(1 \times 10^{-3})^2}$$



مساحة الخارج - مساحة الداخل

$$2\pi[(2 \times 10^{-3})^2 - (1 \times 10^{-3})^2]$$

$$= \frac{(2 \times 10^{-3})^2 - (1 \times 10^{-3})^2}{(1 \times 10^{-3})^2}$$

$$= \frac{(1 \times 10^{-3})^2}{(1 \times 10^{-3})^2} = 1$$

2

Q2: Switch S in Fig.1 is closed at time $t = 0$, to begin charging an initially uncharged capacitor of capacitance $C = 49.0 \mu\text{F}$ through a resistor of resistance $R = 32.0 \Omega$. At what time is the potential across the capacitor equal to that across the resistor?

$$V_C = V_R$$

$$V_C(t) = \mathcal{E}(1 - e^{-t/RC})$$

$$V_R = IR$$

$$V_R = V_C$$

$$IR = \mathcal{E}(1 - e^{-t/RC})$$

$$\frac{\mathcal{E}}{R}(R) = \mathcal{E}(1 - e^{-t/RC})$$

$$1 = 1 - e^{-t/RC}$$

$$2 = -e^{-t/RC}$$

$$-2 = e^{-t/RC}$$

$$\ln -2 = \ln e^{-t/(32 \times 49 \times 10^{-6})}$$

$$0.69 = -t/(32 \times 49 \times 10^{-6})$$

$$t = 1.086 \text{ s}$$

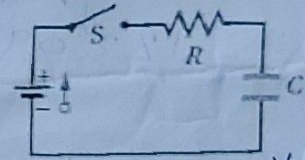


Fig.1

$$V_C(t) = \mathcal{E}(1 - e^{-t/RC})$$

$$I(t) = \frac{\mathcal{E}}{R}(1 - e^{-t/RC})$$

$$I_0 = \frac{R}{\mathcal{E}}$$

$$I(0) = \frac{R}{\mathcal{E}}$$

$$= \frac{R}{\mathcal{E}}$$

$$V(0) = \mathcal{E}C$$

$$q = \mathcal{E}C$$

$$\mathcal{E} = \frac{q}{C}$$

$$V = IR$$