

## PHYSICS 112 Homework 1

Student name \_\_\_\_\_

Student no: \_\_\_\_\_

1. For the following RLC circuit if  $L = 10\text{mH}$  and  $V_c$  is shown in the figure below. Use the information in the  $V_c$  vs. time curve to find the following quantities.


- The half-life time  $t_{1/2}$ .
- Decay constant  $\delta$ .
- The resistance  $R$ .

- Angular frequency  $\omega$ .

خلف  
الرقم  
الحل

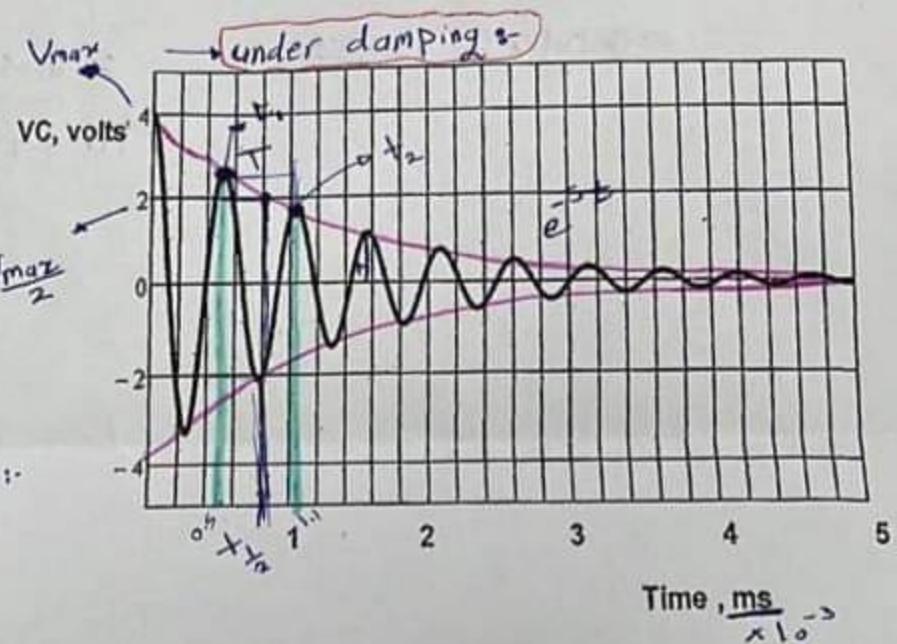a) from the graph:-

$$t_{1/2} = 0.8 \text{ ms} \\ = 0.8 \times 10^{-3} \text{ s}$$



b) Decay constant:

$$\delta = \frac{\ln 2}{t_{1/2}} = \frac{\ln 2}{0.8 \times 10^{-3}} = 866.43 \text{ sec}^{-1} \\ \boxed{\delta = 0.866 \text{ K Sec}^{-1}}$$

or

$$\delta = \frac{R}{2L} \\ = \frac{17.32}{2 \times 10 \times 10^{-3}} \\ \boxed{\delta = 866.4 \text{ sec}^{-1}}$$

c) the resistance  $R$

$$\delta = \frac{R}{2L}$$

$$R = \delta L$$

$$= 2(866.43)(10 \times 10^{-3})$$

or

$$R = \frac{2L \ln 2}{t_{1/2}} \\ = \frac{2 \times 10 \times 10^{-3} \ln(2)}{0.8 \times 10^{-3}} \\ \boxed{R = 17.32 \Omega}$$

$$\boxed{R = 17.32 \Omega}$$