

<b>Started on</b>	Thursday, 18 January 2024, 6:00 PM
<b>State</b>	Finished
<b>Completed on</b>	Thursday, 18 January 2024, 6:34 PM
<b>Time taken</b>	34 mins 3 secs
<b>Grade</b>	11.00 out of 11.00 (100%)

**Question 1**

Complete

Not graded

Given the circuit below, if  $M = 1$ ,  $A = 0000$  and  $B = 0000$ , then  $S$  is


- a. The 2's complement of A
- b. None
- c. The 1's complement of A
- d. The 2's complement of B
- e. The 1's complement of B

**Question 2**

Correct

Mark 1.00 out of 1.00

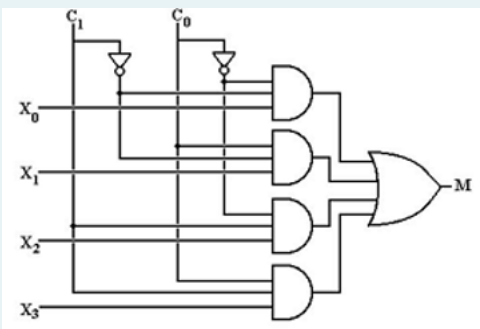In the given 4 x 1 multiplexer, if  $c_1 = 0$  and  $c_0 = 1$  then the output  $M$  is \_\_\_\_\_. Select one or more:



- a. X2
- b. X3
- c. X1 ✓
- d. X0
- e. None



Question **3**

Correct

Mark 1.00 out of 1.00

How many 3 x 8 line decoders with enable input are needed to construct a 6 x 64 line decoder?

- a. 9 ✓
- b. 7
- c. None
- d. 8
- e. 10

Question **4**

Correct

Mark 1.00 out of 1.00

The number of full and half adders required to add 32-bit numbers is \_\_\_\_\_

- a. None
- b. 8 half adders, 24 full adders
- c. 1 half adders, 31 full adders ✓
- d. 16 half adders, 16 full adders
- e. 32 half adders, 0 full adders




Question 5

Correct

Mark 1.00 out of 1.00

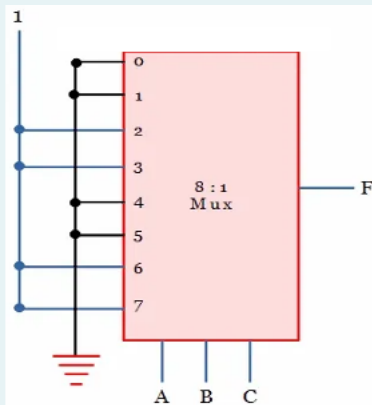The 8 x 1 multiplexer shown in the figure implements:



- a.  $F(A,B,C) = \prod (2,3,6,7)$
- b. None
- c.  $F(A,B,C) = \sum (0,1,4,5)$
- d.  $F(A,B,C) = \prod (0,1,4)$
- e.  $F(A,B,C) = \sum (2,3,6,7)$  ✓

Question 6

Correct

Mark 1.00 out of 1.00

The output **Y** of a 2 bit comparator is logic 1 whenever the 2 bit input **A** is greater than the 2 bit input **B**. The number of combinations for which the output is logic 1, is

- a. 4
- b. 6 ✓
- c. 10
- d. 8
- e. A will never be greater than B in any of the combinations




Question 7

Correct

Mark 1.00 out of 1.00

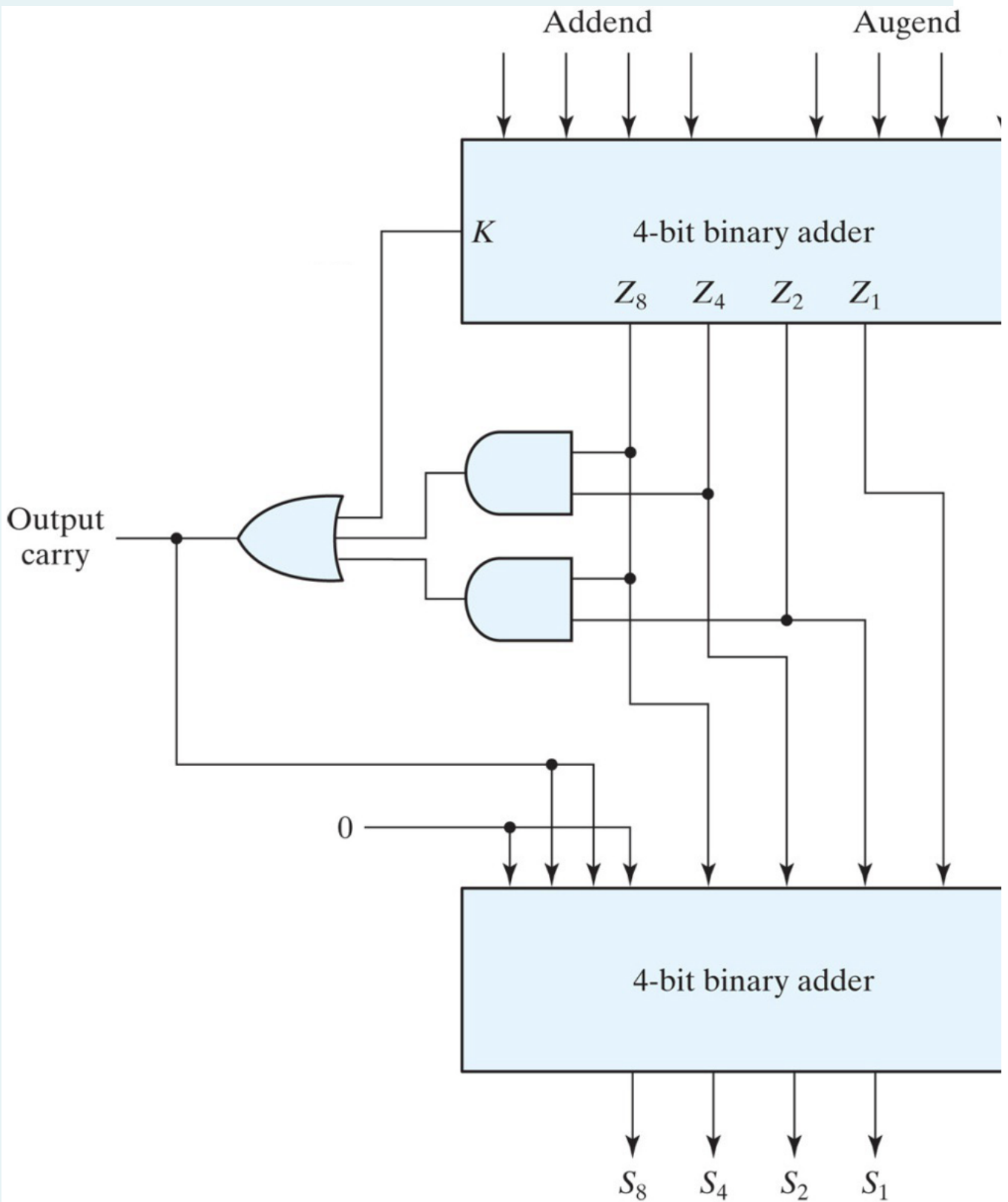In the below circuit, if the Added =  $(7)_{BCD}$  and the Augend =  $(9)_{BCD}$ , then the [Output\_carry S<sub>8</sub> S<sub>4</sub> S<sub>2</sub> S<sub>1</sub>] =



- a. None
- b. 1 0110 ✓
- c. 1 0001






Question 10

Correct

Mark 1.00 out of 1.00

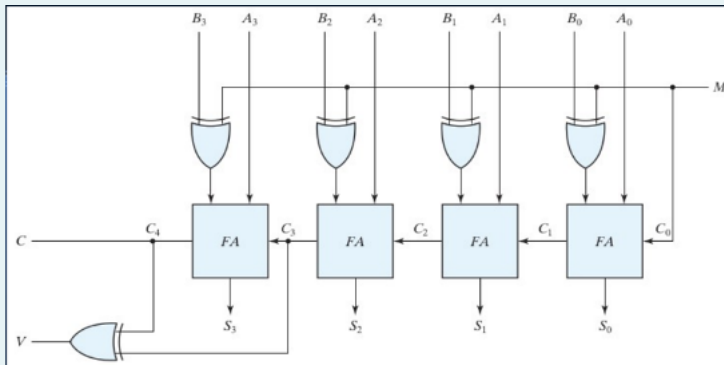Given the circuit below, when using  $M = 1$ ,  $A = 1011$  and  $B = 0111$ , then  $V$  indicates that an overflow bit is set.



- a. True ✓
- b. False




Question 11

Correct


Mark 1.00 out of 1.00

Realize the carry-out function of the full-adder, using 4\*1 MUX. Where  $F(x,y,z) = x+y+z$ .

a.

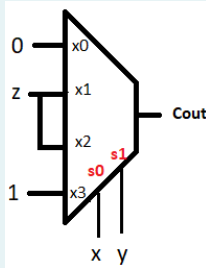


b.

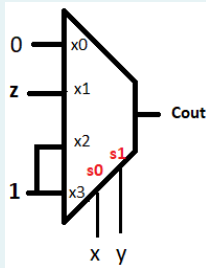


c. None

d.

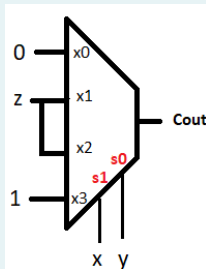

e.

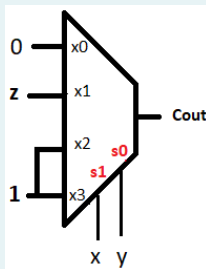

Question 12

Correct

Mark 1.00 out of 1.00

\_\_\_\_\_ converts binary coded information into unique outputs such as decimal, octal digits, etc.

- a. Full Adder
- b. Multiplexer
- c. Decoder ✓
- d. Encoder
- e. Demultiplexer



