

Verilog

Part I

Presentation Outline

- ❖ Hardware Description Language
- ❖ Logic Simulation versus Synthesis
- ❖ Verilog Module
- ❖ Gate-Level Description and Gate Delays
- ❖ Module Instantiation
- ❖ Continuous Assignment
- ❖ Writing a Simple Test Bench

Hardware Description Language

- ❖ Describes the hardware of digital systems in a textual form
- ❖ Describes the hardware structures and behavior
- ❖ Can represent logic diagrams, expressions, and complex circuits
- ❖ NOT a software programming language
- ❖ Two standard hardware description languages (HDLs)
 - 1. Verilog** (will be studied in this course)
 - 2. VHDL** (harder to learn than Verilog)

Verilog = "Verifying Logic"

- ❖ Invented as a simulation language in 1984 by Phil Moorby
- ❖ Opened to public in 1990 by Cadence Design Systems
- ❖ Became an IEEE standard in 1995 (Verilog-95)
- ❖ Revised and upgraded in 2001 (Verilog-2001)
- ❖ Revised also in 2005 (Verilog-2005)
- ❖ Verilog allows designers to describe hardware at different levels
 - ✧ Can describe anything from a single gate to a full computer system
- ❖ Verilog is supported by the majority of electronic design tools
- ❖ Verilog can be used for logic simulation and synthesis

Logic Simulation

- ❖ Logic simulator interprets the Verilog (HDL) description
- ❖ Produces **timing diagrams**
- ❖ Predicts how the hardware will behave before it is fabricated
- ❖ Simulation allows the detection of functional errors in a design
 - ✧ Without having to physically implement the circuit
- ❖ Errors detected during the simulation can be corrected
 - ✧ By modifying the appropriate statements in the Verilog description
- ❖ Simulating and verifying a design requires a **test bench**
- ❖ The test bench is also written in Verilog

Logic Synthesis

- ❖ Logic synthesis is similar to translating a program
- ❖ However, the output of logic synthesis is a digital circuit
- ❖ A digital circuit modeled in Verilog can be translated into a list of components and their interconnections, called **netlist**
- ❖ Synthesis can be used to fabricate an integrated circuit
- ❖ Synthesis can also target a Field Programmable Gate Array
 - ✧ An FPGA chip can be configured to implement a digital circuit
 - ✧ The digital circuit can also be modified by reconfiguring the FPGA
- ❖ Logic simulation and synthesis are automated
 - ✧ Using special software, called Electronic Design Automation (EDA) tools

HDL Verilog

- ❖ A module can be described in any one (or a combination) of the following modeling techniques:
 1. **Gate – level modeling** using instantiation of primitive gates and user - defined modules
 2. **Data flow modeling** using continuous assignment statements with keyword **assign**
 3. **Behavioral modeling** using procedural assignment statements with keyword **always**

Gate – Level Modeling (Structural Modeling)

- ❖ Structural Modeling is the set of interconnected components.
- ❖ It describes the structure (as in, the components that are visible in a structure).
- ❖ The visible components are instantiated in the declarative part of the architecture body while the declared components are instantiated with their respective interface ports in the statement part of the architecture body.
- ❖ Structural Modeling doesn't say anything about functionality.
- ❖ **The component instantiation statements are concurrent in nature.** Thus, the order of these statements is not important.

Basic Gates

- ❖ Basic gates: **and**, **nand**, **or**, **nor**, **xor**, **xnor**, **not**, **buf**
- ❖ Verilog define these gates as **keywords**
- ❖ Each gate has an optional name
- ❖ Each gate has an output (listed first) and one or more inputs
- ❖ The **not** and **buf** gates can have only one input
- ❖ Examples:

```
and g1(x,a,b); // 2-input and gate named g1
```

```
or g2(y,a,b,c); // 3-input or gate named g2
```

```
nor g3(z,a,b,c,d); // 4-input nor gate named g3
```

↑ ↑ ┌──────────┐
name output inputs

Verilog Module

- ❖ A digital circuit is described in Verilog as a set of modules
- ❖ A module is the design entity in Verilog
- ❖ A module is declared using the **module** keyword
- ❖ A module is terminated using the **endmodule** keyword
- ❖ A module has a name and a list of **input** and **output** ports
- ❖ A module is described by a group of statements
- ❖ The statements can describe the module structure or behavior

Verilog Syntax

❖ **Keywords:** have special meaning in Verilog

Many keywords: `module`, `input`, `output`, `wire`, `and`, `or`, etc.

Keywords cannot be used as identifiers

❖ **Identifiers:** are user-defined names for modules, ports, etc.

Verilog is **case-sensitive**: `A` and `a` are different names

❖ **Comments:** can be specified in two ways (similar to C)

✧ Single-line comments begin with `//` and terminate at end of line

✧ Multi-line comments are enclosed between `/*` and `*/`

❖ **White space:** space, tab, newline can be used freely in Verilog

❖ **Operators:** operate on variables (similar to C: `~` `&` `|` `^` `+` `-` etc.)

Verilog Four-Valued Logic

❖ Verilog Value Set consists of four basic values:

0 – represents a logic zero, or false condition

1 – represents a logic one, or true condition

X – represents an unknown logic value

Z – represents a high-impedance value


x or **X** represents an unknown or uninitialized value

z or **Z** represents the output of a disabled tri-state buffer

Structure Description in Verilog

```
module Add_half (sum, c_out, a, b);  
  input  a, b; ← Declaration of port modes  
  output sum, c_out; ← Declaration of port modes  
  wire  c_out_bar; ← Declaration of internal signal  
  
  xor Gate1 (sum, a, b); ← Instance name, Instantiation of primitive gates  
  nand (c_out_bar, a, b); ← Instantiation of primitive gates  
  not  (c_out, c_out_bar); ← Instantiation of primitive gates  
endmodule
```

Verilog keywords

 

Gate level representation example: Half Adder

A half adder adds two bits: a and b

Two output bits:

1. Carry bit: $\text{cout} = a \cdot b$

2. Sum bit: $\text{sum} = a \oplus b$

```
module Half_Adder(a, b, cout, sum);
```

```
    input a, b;
```

```
    output sum, cout;
```


```
    and (cout, a, b);
```

```
    xor (sum, a, b);
```

```
endmodule
```

Truth Table

a	b	cout	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full Adder

- ❖ Full adder adds 3 bits: **a**, **b**, and **c**
- ❖ Two output bits:
 1. Carry bit: **cout**
 2. Sum bit: **sum**
- ❖ Sum bit is 1 if the number of 1's in the input is odd (odd function)

$$\text{sum} = (a \oplus b) \oplus c$$

- ❖ Carry bit is 1 if the number of 1's in the input is 2 or 3

$$\text{cout} = a \cdot b + (a \oplus b) \cdot c$$

Truth Table

a	b	c	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder Module

```
module Full_Adder(input a, b, c, output cout, sum);
```

```
  wire w1, w2, w3;
```

```
  and (w1, a, b);
```


```
  xor (w2, a, b);
```

```
  and (w3, w2, c);
```

```
  xor (sum, w2, c);
```

```
  or (cout, w1, w3)
```

```
endmodule
```

 

Modular Design

A full adder can be designed using two half adders and one OR gate

First Half Adder: HA1

$$w1 = a \cdot b$$




$$w2 = a \oplus b$$

Second Half Adder: HA2

$$w3 = w2 \cdot c = (a \oplus b) \cdot c$$

$$\text{sum} = w2 \oplus c = (a \oplus b) \oplus c$$
  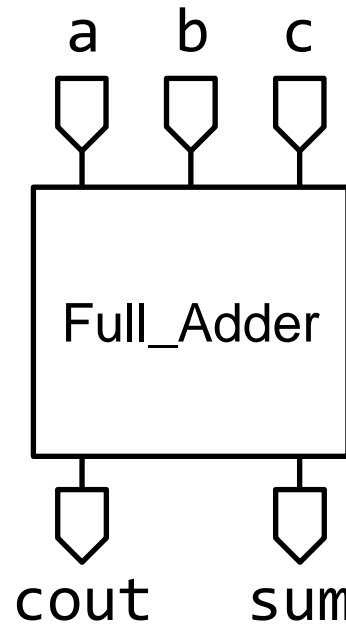
$$\text{cout} = w1 + w3 = a \cdot b + (a \oplus b) \cdot c$$




Module Instantiation

- ❖ Module declarations are like **templates**
- ❖ Module instantiation is like creating an **object**
- ❖ Modules are instantiated inside other modules at different levels
- ❖ The top-level module does not require instantiation
- ❖ Module instantiation defines the **structure** of a digital design
- ❖ It produces a **tree of module instances** at different levels
- ❖ The ports of a module instance must match those declared
- ❖ The matching of the ports can be done **by name** or **by position**

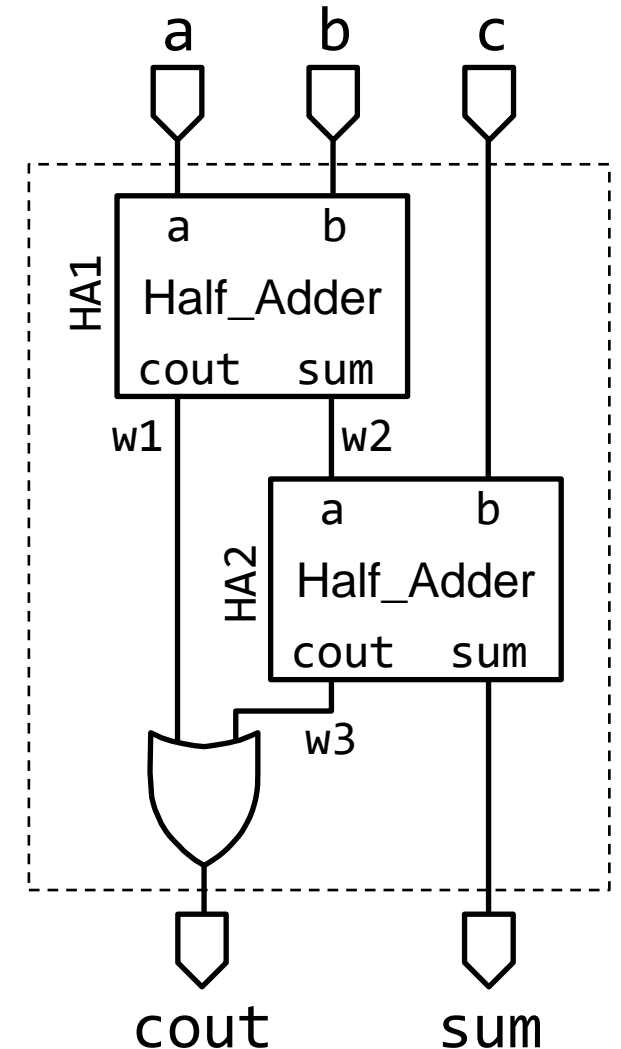Example of Module Instantiation

```
module Full_Adder (input a, b, c, output cout, sum);  
    wire w1, w2, w3;  
    // Instantiate two Half Adders: HA1, HA2  
    // The ports are matched by position  
    Half_Adder HA1 (a, b, w1, w2);  
    Half_Adder HA2 (w2, c, w3, sum);  
    or (cout, w1, w3);  
    // Can also match the ports by name  
    // Half_Adder HA2  
    // (.a(w2), .b(c), .cout(w3), .sum(sum));  
endmodule
```



Number Representation in Verilog

Numbers are represented as:

`<size>'<signed><radix>value` ("`<>`" indicates optional part)

size The number of binary bits the number is comprised of. Not the number of hex or decimal digits. Default is 32 bits.

' A separator, single quote, not a backtick

signed Indicates if the value is signed. Either `s` or `S` can be used. Not case dependent. Default is unsigned.

radix Radix of the number

'b or 'B : binary

'o or 'O : octal

'h or 'H : hex

'd or 'D : decimal

default is decimal

Bit Vectors in Verilog

- ❖ A Bit Vector is multi-bit declaration that uses a single name
- ❖ A Bit Vector is specified as a Range **[msb:lsb]**
- ❖ **msb** is *most-significant bit* and **lsb** is *least-significant bit*

❖ Examples:

```
input  [15:0] A;    // A is a 16-bit input vector
```


```
output [0:15] B;   // Bit 0 is most-significant bit
```

```
wire   [3:0] W;    // Bit 3 is most-significant bit
```

- ❖ **Bit select:** **W[1]** is bit **1** of W
- ❖ **Part select:** **A[11:8]** is a 4-bit select of A with range **[11:8]**
- ❖ The part select range must be consistent with vector declaration

4-bit Binary Adder Example

<i>Subscript i:</i>	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

 

4-bit Binary Adder Example

```
module adder4 (sum, C4, A, B, C0) ;
```

```
output [3:0] sum;
```

```
output C4;
```

```
input [3:0] A, B;
```

```
input C0;
```

```
wire C1, C2, C3; // Intermediate carries
```

```
// Instantiate chain of full adders
```


```
Add_full FA0 (sum[0], C1, A[0], B[0], C0) ;
```

```
Add_full FA1 (sum[1], C2, A[1], B[1], C1) ;
```

```
Add_full FA2 (sum[2], C3, A[2], B[2], C2) ;
```

```
Add_full FA3 (sum[3], C4, A[3], B[3], C3) ;
```

```
endmodule
```

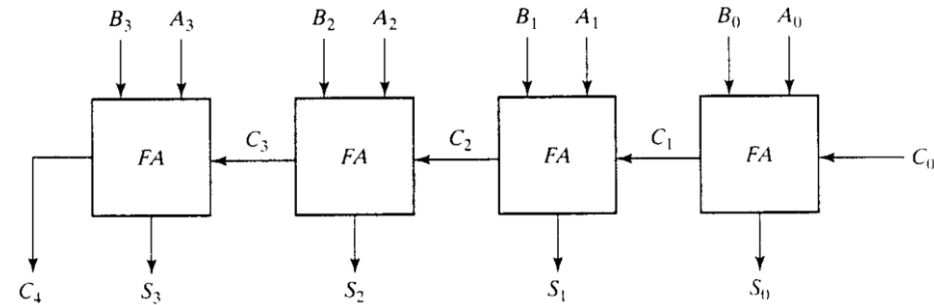

Dataflow Modeling

- ❖ Dataflow modeling provides the means of describing combinational circuits by **their function** rather than by their gate structure.
- ❖ Used mostly for describing Boolean equations and combinational logic
- ❖ Synthesis tool can map a dataflow model into a target technology
- ❖ Can describe: adders, comparators, multiplexers, etc.
- ❖ Dataflow modeling uses a number of operators that act on operands to produce desired results
- ❖ Dataflow modeling uses continuous assignments and the keyword **assign**.

Continuous Assignment

- ❖ The **assign** statement defines continuous assignment
- ❖ Syntax: **assign** *net_name* = *expression*;
- ❖ Assigns *expression* value to *net_name* (wire or output port)
- ❖ Continuous assignment statements are **concurrent**
- ❖ Can appear in any order inside a module
- ❖ Continuous assignment can model combinational circuits
- ❖ Describes the flow of data between input and output

Continuous Assignment

❖ Examples:

```
assign x = a&b | c&~d;      // x = ab + cd'  
assign y = (a|b) & ~c;     // y = (a+b)c'  
assign z = ~(a|b|c);       // z = (a+b+c)'  
assign sum = (a^b) ^ c;    // sum = (a ⊕ b) ⊕ c
```

❖ Verilog uses the bit operators: ~ (not), & (and), | (or), ^ (xor)

❖ Operator precedence: (parentheses), ~ , & , | , ^

Verilog Operators

Bitwise Operators	
<code>~a</code>	Bitwise NOT
<code>a & b</code>	Bitwise AND
<code>a b</code>	Bitwise OR
<code>a ^ b</code>	Bitwise XOR
<code>a ~^ b</code>	Bitwise XNOR
<code>a ^~ b</code>	Same as <code>~^</code>

Arithmetic Operators	
<code>a + b</code>	ADD
<code>a - b</code>	Subtract
<code>-a</code>	Negate
<code>a * b</code>	Multiply
<code>a / b</code>	Divide
<code>a % b</code>	Remainder

Relational Operators	
<code>a == b</code>	Equality
<code>a != b</code>	Inequality
<code>a < b</code>	Less than
<code>a > b</code>	Greater than
<code>a <= b</code>	Less or equal
<code>a >= b</code>	Greater or equal

Reduction Operators	
<code>&a</code>	AND all bits
<code> a</code>	OR all bits
<code>^a</code>	XOR all bits
<code>~&a</code>	NAND all bits
<code>~ a</code>	NOR all bits
<code>~^a</code>	XNOR all bits

Shift Operators	
<code>a << n</code>	Shift Left
<code>a >> n</code>	Shift Right

Miscellaneous Operators	
<code>sel?a:b</code>	Conditional
<code>{a, b}</code>	Concatenate

Reduction operators produce a 1-bit result

Relational operators produce a 1-bit result

`{a, b}` concatenates the bits of `a` and `b`

Nets and Variables

Verilog has two major data types:

1. **Net data types:** are connections between parts of a design
2. **Variable data types:** can store data values
 - ✧ The **wire** is a net data type (physical connection)
 - A wire cannot store the value of a procedural assignment
 - However, a wire can be driven by continuous assignment
 - ✧ The **reg** is a variable data type
 - Can store the value of a procedural assignment
 - However, cannot be driven by continuous assignment

Reduction Operators

```
module Reduce
```

```
( input [3:0] A, B, output X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are 1-bit outputs
```

```
// X = A[3] | A[2] | A[1] | A[0];
```

```
assign X = |A;
```

```
// Y = B[3] & B[2] & B[1] & B[0];
```

```
assign Y = &B;
```

```
// Z = X & (B[3] ^ B[2] ^ B[1] ^ B[0]);
```

```
assign Z = X & (^B);
```

```
endmodule
```

Concatenation Operator { }

```
module Concatenate
```

```
( input [7:0] A, B, output [7:0] X, Y, Z );
```

```
// A, B are input vectors, X, Y, Z are output vectors
```

```
// X = A is right-shifted 3 bits using { } operator
```

```
assign X = {3'b000, A[7:3]};
```

```
// Y = A is right-rotated 3 bits using { } operator
```

```
assign Y = {A[2:0], A[7:3]};
```

```
// Z = selecting and concatenating bits of A and B
```

```
assign Z = {A[5:4], B[6:3], A[1:0]};
```

```
endmodule
```

Modeling a 16-bit Adder

```
module Adder16
```

```
  ( input [15:0] A, B, input cin,  
    output [15:0] Sum, output cout );
```

```
// A and B are 16-bit input vectors
```

```
// Sum is a 16-bit output vector
```

```
// {cout, Sum} is a concatenated 17-bit vector
```

```
// A + B + cin is 16-bit addition + input carry
```

```
// The + operator is translated into an adder
```

```
assign {cout, Sum} = A + B + cin;
```

```
endmodule
```


Modeling a Magnitude Comparator

```
// n-bit magnitude comparator, No default value for n
module Comparator (input [1:0] A, B, output GT, EQ,
LT);

// A and B are n-bit input vectors (unsigned)
// GT, EQ, and LT are 1-bit outputs

assign GT = (A > B);
assign EQ = (A == B);
assign LT = (A < B);

endmodule
```

 

Conditional Operator

❖ Syntax:

Boolean_expr ? True_expression : False_expression

If *Boolean_expr* is true then select *True_expression*

Else select *False_Expression*

❖ Examples:

```
assign max = (a>b)? a : b; // maximum of a and b
```

```
assign min = (a>b)? b : a; // minimum of a and b
```

❖ Conditional operators can be nested

Modeling a 2-Input Multiplexer

```
// Parametric 2-input Mux, default value for n = 1
```

```
module Mux2( input [1:0] A, B, input sel,  
            output [1:0] Z);
```

```
// A and B are n-bit input vectors
```


```
// Z is the n-bit output vector
```

```
// if (sel==0) Z = A; else Z = B;
```

```
// Conditional operator used for selection
```

```
assign Z = (sel == 0)? A : B;
```

```
endmodule
```

 

Modeling a 4-Input Multiplexer

```
// Parametric 4-input Mux, default value for n = 1
```

```
module Mux4 #(parameter n = 1)
```

```
( input [n-1:0] A, B, C, D,
```

```
  input [1:0] sel,
```

```
  output [n-1:0] Z );
```

```
// sel is a 2-bit vector
```


```
// Nested conditional operators
```

```
assign Z = (sel == 'b00)? A :
```

```
          (sel == 'b01)? B :
```

```
          (sel == 'b10)? C : D;
```

```
endmodule
```

 

Dataflow and Behavioral Modeling

- ❖ Behavioral Modeling using Procedural Blocks and Statements
 - ✧ Describes what the circuit does at a functional and algorithmic level
 - ✧ Encourages designers to rapidly create a prototype
 - ✧ Can be verified easily with a simulator
 - ✧ Some procedural statements are synthesizable (Others are NOT)

Behavioral Modeling

- ❖ Uses procedural blocks and procedural statements
- ❖ There are two types of **procedural** blocks in Verilog
 1. The **initial** block
 - ✧ Executes the enclosed statement(s) one time only
 2. The **always** block
 - ✧ Executes the enclosed statement(s) repeatedly until simulation terminates
- ❖ The body of the **initial** and **always** blocks is **procedural**
 - ✧ Can enclose one or more **procedural statements**
 - ✧ Procedural statements are surrounded by **begin ... end**
- ❖ Multiple procedural blocks can appear in any order inside a module and run in parallel inside the simulator

Example of Initial and Always Blocks

```
module behave;
  reg clk; // 1-bit variable
  reg [15:0] A; // 16-bit variable
  initial begin // executed once
    clk = 0; // initialize clk
    a = 16'h1234; // initialize a
    #200 $finish
  end
  always begin // executed always
    #10 clk = ~clk; // invert clk every 10 ns
  end
  always begin // executed always
    #20 A = A + 1; // increment A every 20 ns
  end
endmodule
```

The **initial** Statement

- ❖ The **initial** statement is a procedural block of statements
- ❖ The body of the **initial** statement surrounded by **begin-end** is sequential, like a sequential block in a programming language
- ❖ Procedural assignments are used inside the **initial** block
- ❖ Procedural assignment statements are executed in sequence

Syntax: *variable = expression;*

Always Block with Sensitivity List

❖ Syntax:

```
always @(sensitivity list) begin  
    procedural statements  
end
```

❖ An **always** block can have a *sensitivity list*

❖ Sensitivity list is a list of signals: @(signal1, signal2, ...)

The sensitivity list triggers the execution of the **always** block

When there is a ***change of value in any listed signal***

Otherwise, the **always** block does nothing until another change occurs on a signal in the sensitivity list

Sensitivity List for Combinational Logic

- ❖ For combinational logic, the sensitivity list **must include**:

ALL the signals that are read inside the **always** block

Example: A, B, and sel must be in the sensitivity list below:

```
always @(A, B, sel) begin  
    if (sel == 0) Z = A;  
    else Z = B;  
end
```

A, B, and sel are
read inside the
always block

- ❖ Combinational logic can also use: **@(*)** or **@***

@(*) is automatically sensitive to all the signals that are read inside the **always** block

If Statement

- ❖ The **if** statement is procedural
- ❖ Can only be used inside a procedural block
- ❖ Syntax:

if (*expression*) *statement*

[**else** *statement*]

- ❖ The **else** part is optional

A *statement* can be simple or compound


A *compound statement* is surrounded by **begin** ... **end**

- ❖ **if** statements can be nested
- ❖ Can be nested under **if** or under **else** part

Modeling a 2-Input Multiplexer

```
// Behavioral Modeling of a Parametric 2-input Mux
module Mux2 ( input [1:0] A, B, input sel,
              output reg [1:0] Z);

 // Output Z must be of type reg
// Sensitivity list = @(A, B, sel)
always @(A, B, sel) begin
    if (sel == 0) Z = A;
    else Z = B;
end
endmodule
```



Modeling a 3x8 Decoder

```
module Decoder3x8 (input [2:0] A, output reg [7:0] D);  
    // Sensitivity list = @(A)  
    always @(A) begin  
        if (A == 0)          D = 8'b00000001;  
        else if (A == 1)    D = 8'b00000010;  
        else if (A == 2)    D = 8'b00000100;  
        else if (A == 3)    D = 8'b00001000;  
        else if (A == 4)    D = 8'b00010000;  
        else if (A == 5)    D = 8'b00100000;  
        else if (A == 6)    D = 8'b01000000;  
        else                  D = 8'b10000000;  
    end  
endmodule
```

Modeling a 4x2 Priority Encoder

```
module Priority_Encoder4x2
    (input [3:0] D, output reg V, output reg [1:0] A);
    // sensitivity list = @(D)
    always @(D) begin
        if (D[3])      {V, A} = 3'b111;
        else if (D[2]) {V, A} = 3'b110;
        else if (D[1]) {V, A} = 3'b101;
        else if (D[0]) {V, A} = 3'b100;
        else           {V, A} = 3'b000;
    end
endmodule
```

Modeling a Magnitude Comparator

```
// Behavioral Modeling of a Magnitude Comparator
```

```
module Comparator #(parameter n = 1)
```

```
(input [n-1:0] A, B, output reg GT, EQ, LT);
```

```
// Sensitivity list = @(A, B)
```

```
always @(A, B) begin
```

```
    if (A > B)
```

```
        {GT, EQ, LT} = 'b100;
```

```
    else if (A == B)
```


```
        {GT, EQ, LT} = 'b010;
```

```
    else
```

```
        {GT, EQ, LT} = 'b001;
```


```
end
```

```
endmodule
```

 

Modeling a 4-Input Multiplexer
 
```
// Behavioral Modeling of a 4-input Mux
module Mux4 #(parameter n = 1)
  ( input  [n-1:0] A, B, C, D, input [1:0] sel,
    output reg [n-1:0] Z );
  // @(*) is @(A, B, C, D, sel)
  always @(*) begin
    if (sel == 'b00) Z = A;
    else if (sel == 'b01) Z = B;
    else if (sel == 'b10) Z = C;
    else Z = D;
  end
endmodule
```



Case Statement

- ❖ The **case** statement is procedural (used inside **always** block)
- ❖ Syntax:

```
case (expression)  
    case_item1: statement  
    case_item2: statement  
    . . .  
    default:    statement  
endcase
```

The **default** case is optional

A *statement* can be simple or compound

A *compound statement* is surrounded by **begin** ... **end**

Modeling a Mux with a Case Statement

```
module Mux4( input [1:0] A, B, C, D, input [1:0]  
            sel, output reg [1:0] Z );
```

```
// @(*) is @(A, B, C, D, sel)
```

```
always @(*) begin
```

```
  case (sel)
```

```
    2'b00: Z = A;
```

```
    2'b01: Z = B;
```


```
    2'b10: Z = C;
```

```
    default: Z = D;
```

```
  endcase
```

```
end
```

```
endmodule
```

 


Modeling a Multifunction ALU

// Behavioral Modeling of an ALU

```
module ALU #(parameter n = 16)
  ( input  [n-1:0] A, B, input [1:0] F,
    output reg [n-1:0] Z, output reg Cout );
  // @(*) is @(A, B, F)
  always @(*) begin
    case (F)
      2'b00: {Cout,Z} = A+B;
      2'b01: {Cout,Z} = A-B;
      2'b10: {Cout,Z} = A&B;
      default: {Cout,Z} = A|B;
    endcase
  end
endmodule
```

ALU Symbol

 

Modeling a BCD to 7-Segment Decoder

```
module BCD_to_7Seg_Decoder
( input [3:0] BCD, output reg [6:0] Seg )
always @(BCD) begin
    case (BCD)
        0: Seg = 7'b1111110;    1: Seg = 7'b0110000;
        2: Seg = 7'b1101101;    3: Seg = 7'b1111001;
        4: Seg = 7'b0110011;    5: Seg = 7'b1011011;
        6: Seg = 7'b1011111;    7: Seg = 7'b1110000;
        8: Seg = 7'b1111111;    9: Seg = 7'b1111011;
        default: Seg = 7'b0000000;
    endcase
end
endmodule
```

