

# Experiment #9

## Pre Lab

Name : Mohammed Jamil Saada


Number : 1221972

### 1) Design 4x2 priority encoder

#### Code :

```
priority_Encoder.v | Compilation Report - Flow Summary | priority_Encoder_Wave.vwf | Simulator Tool
1 //Design 4X2 priority encoder
2 module priority_Encoder(output reg [1:0] out, input [3:0] in);
3
4 //Mohammed Jamil Saada - 1221972
5
6 always @ (in)
7 if(in[3]==1) out[1:0] = 2'b11;
8 else if(in[2]==1) out[1:0] = 2'b10;
9 else if(in[1]==1) out[1:0] = 2'b01;
10 else if(in[0]==1) out[1:0] = 2'b00;
11 else out[1:0] = 2'b00;
12 endmodule
```

#### Wave form :

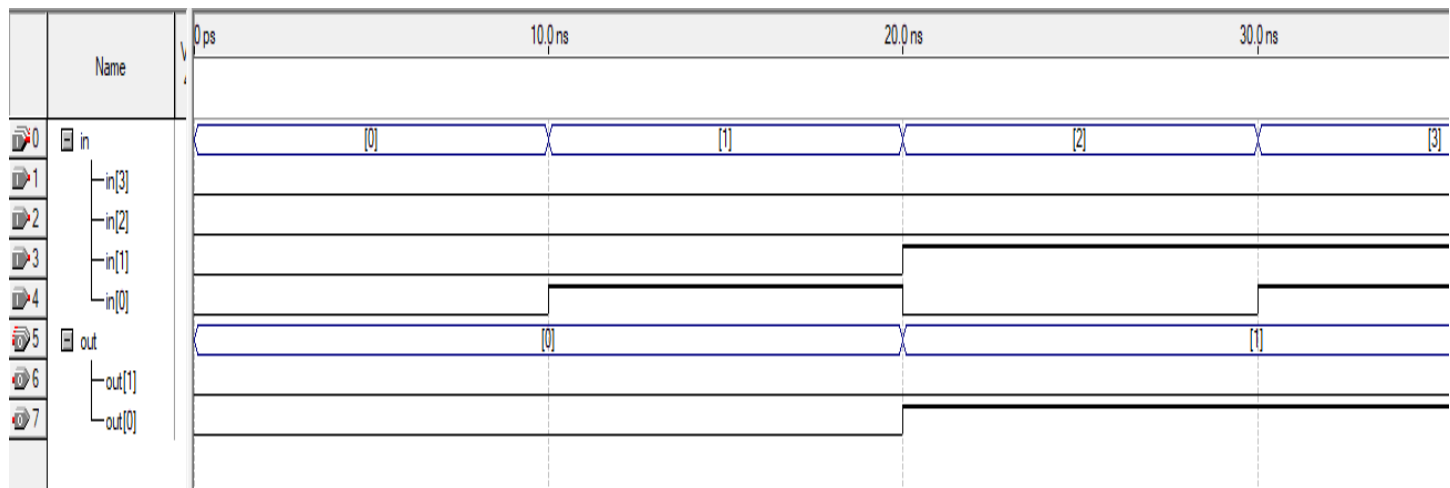


## 2) Design the 7-segment display

### Code :

```
seven_segment_display_driver.v
1 //Design the 7-segment display driver
2 module seven_segment_display_driver(output reg [6:0]out, input [1:0] in);
3
4 //Mohammed Jamil Saada - 1221972
5
6 always @(in)
7     begin
8         case(in)
9             0 : out = 7'b0000001;
10            1 : out = 7'b1001111;
11            2 : out = 7'b0010010;
12            3 : out = 7'b0000110;
13        endcase
14    end
15 endmodule
```

### Wave form :

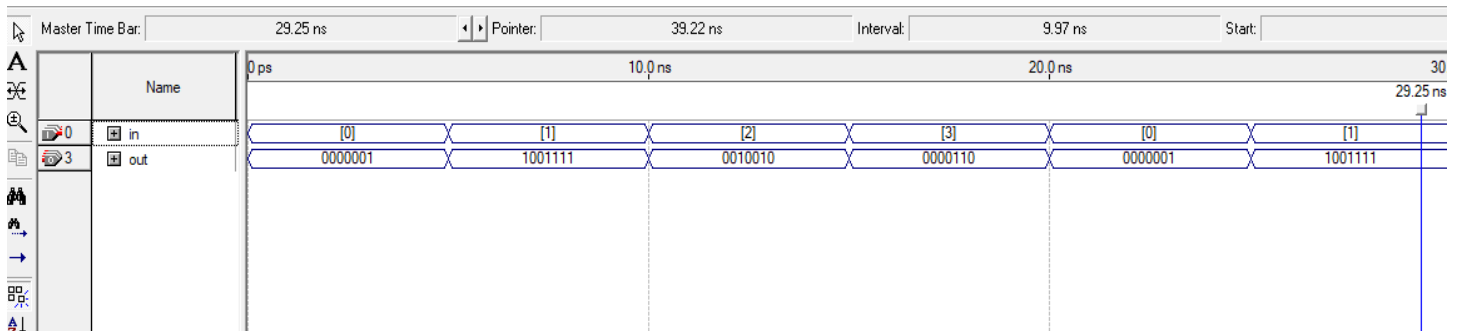


## 3) write and simulate the Verilog code of a D-Flip Flop

### Code :

```
//D-Flip Flop
1 module D_Flip_Flop(output reg Q, input D,clk);
2
3 //Mohammed Jamil Saada - 1221972
4
5 always @ (posedge clk)
6     Q <= D;
7
8 endmodule
```

## Wave form :

 

## 4) Write and simulate the Verilog code of 2x1 MUX.

### Code :

```
1 //2x1 MUX
2 module MUX_2x1(output reg m, input A, B, Sel);
3
4 //Mohammed Jamil Saada - 1221972
5
6 always @ (*)
7     if(Sel==0)
8         m = B;
9     else
10        m = A;
11 endmodule
```

## Wave form :

