

Experiment #8

Post Lab

Name : Mohammed Jamil Saada

Number : 1221972

- Verilog Codes :

• Full Adder :

```
FullDesign.bdf | Full_Adder.v
1 module Full_Adder(input A, B, C, output sum, c_out);
2
3 //Mohammed Jamil Saada - 1221972
4
5 assign sum = A^B^C;
6 assign c_out = (A&B) || (B&C) || (A&C);
7 endmodule
```

• Four Bit Adder

```
FullDesign.bdf | Full_Adder.v | FourBit_Adder.v
1 module FourBit_Adder(input [3:0]A, input [3:0]B, input c_in, output [3:0]sum, output c_out);
2
3 //Mohammed Jamil Saada - 1221972
4
5 wire [2:0] c;
6 Full_Adder FA0(A[0],B[0],c_in,sum[0],c[0]);
7 Full_Adder FA1(A[1],B[1],c[0],sum[1],c[1]);
8 Full_Adder FA2(A[2],B[2],c[1],sum[2],c[2]);
9 Full_Adder FA3(A[3],B[3],c[2],sum[3],c_out);
10
11 endmodule
```

• Four Bit AND :

```
FullDesign.bdf | Full_Adder.v | FourBit_Adder.v
1 module FourBit_AND(input [3:0]A, input [3:0]B, output [3:0]Result);
2
3 //Mohammed Jamil Saada - 1221972
4
5 assign Result[0] = A[0] & B[0];
6 assign Result[1] = A[1] & B[1];
7 assign Result[2] = A[2] & B[2];
8 assign Result[3] = A[3] & B[3];
9
10 endmodule
```


• Four Bit OR

```
FullDesign.bdf | Full_Adder.v | FourBit_Adder.v | FourBit_AND.v
1 module FourBit_OR(input [3:0]A, input [3:0]B, output [3:0]Result);
2
3 //Mohammed Jamil Saada - 1221972
4
5 or gate1(Result[0],A[0],B[0]);
6 or gate2(Result[1],A[1],B[1]);
7 or gate3(Result[2],A[2],B[2]);
8 or gate4(Result[3],A[3],B[3]);
9
10 endmodule
```

• (4-bit input) Multiplexer 2X1

```
FullDesign.bdf | Full_Adder.v | FourBit_Adder.v | FourBit_AND.v | FourBit_OR.v
1 module QuadMux_2X1(input [3:0]A, input [3:0]B, input sel, output [3:0]Result);
2
3 //Mohammed Jamil Saada - 1221972
4
5 assign Result = (sel==0) ? A : B;
6
7 endmodule
```

- Full Design :

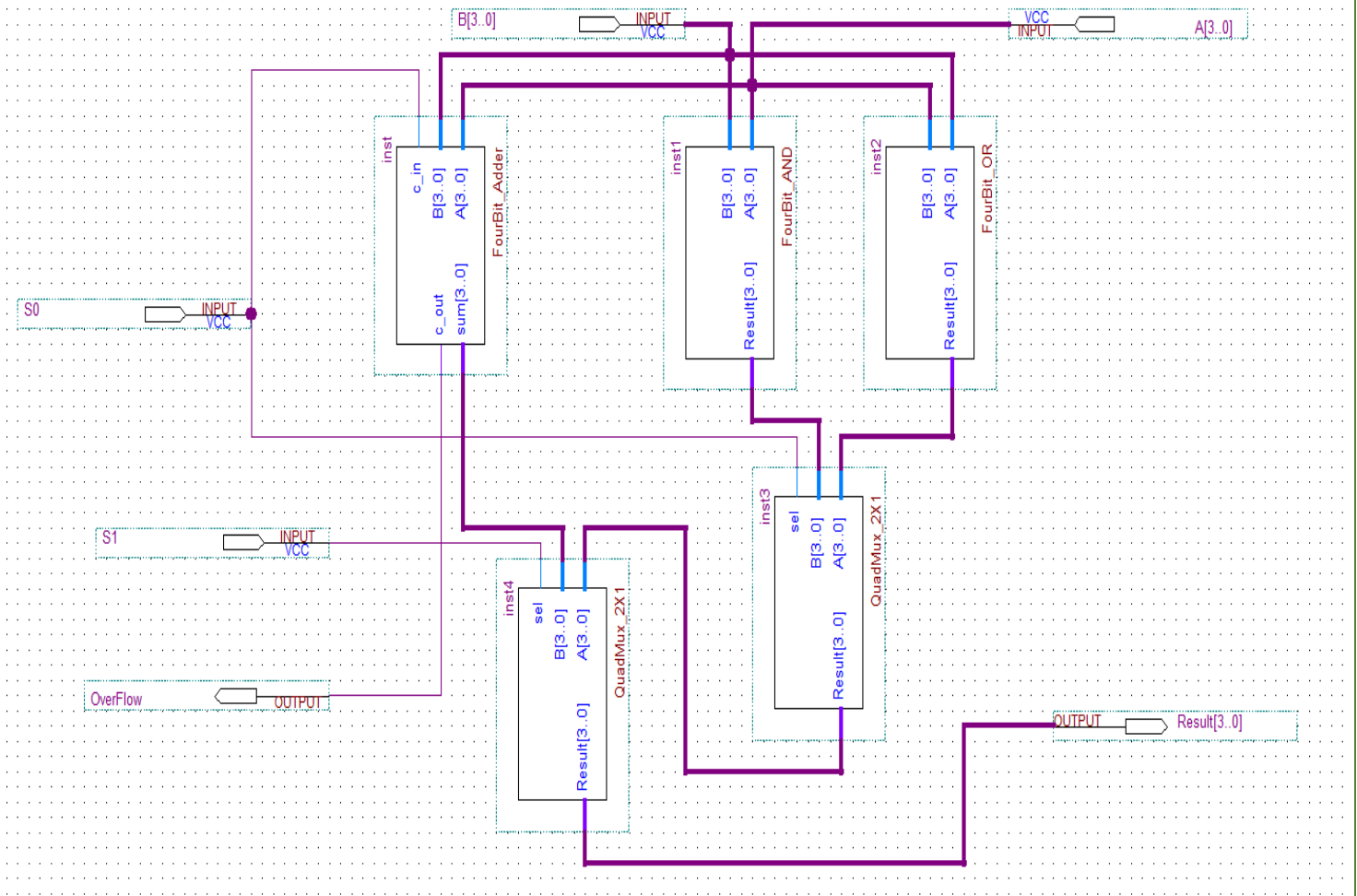

- Wave Form for Full Design :

