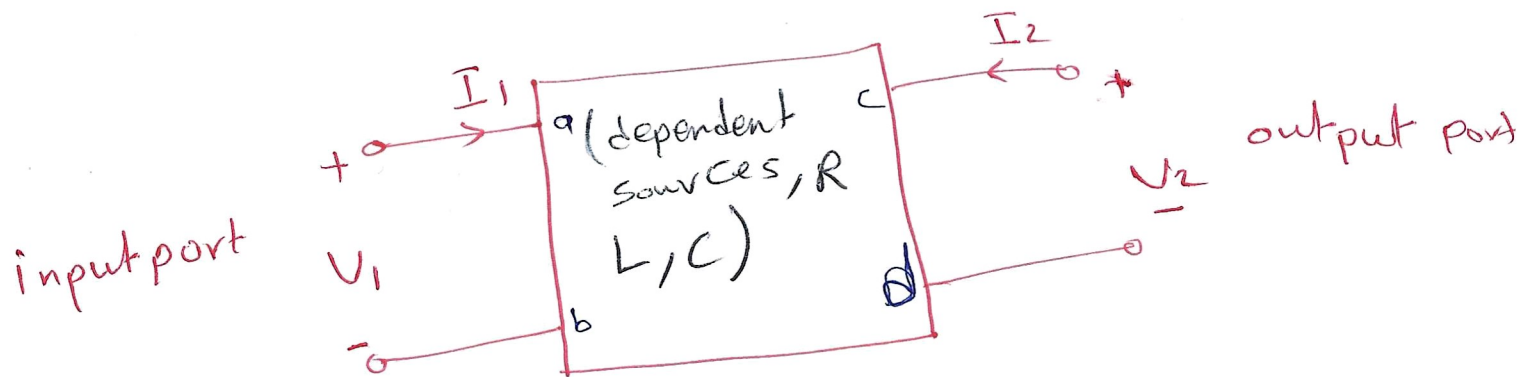


Chapter 18 $\frac{1}{2}$ Two-port Circuits



Two-port circuits can be modeled by 2×2 matrix to relate V/I variables. The matrix elements can be obtained by performing open, and short circuit tests.

There are 6 possible ways to form sets of two equations.

1- Z-parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

2- Y-parameters

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

3- A-Parameters

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \begin{bmatrix} a_{11} & -a_{12} \\ a_{21} & -a_{22} \end{bmatrix} = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

4- B-Parameters

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} \begin{bmatrix} b_{11} & -b_{12} \\ b_{21} & -b_{22} \end{bmatrix} = \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

5 - h - parameters


$$\begin{bmatrix} -I_1 \\ V_2 \end{bmatrix} \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

6 - g - parameters

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} = \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Calculating of z - parameters
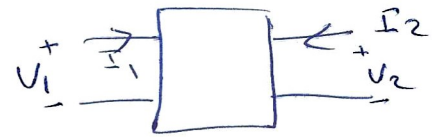
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

If $I_2 = 0 \Rightarrow$ open circuit at port II

$$V_1 = z_{11} I_1 \Rightarrow z_{11} = \frac{V_1}{I_1}$$

$$V_2 = z_{21} I_1 \Rightarrow z_{21} = \frac{V_2}{I_1}$$


If $I_1 = 0 \Rightarrow$ open circuit at port I

$$V_1 = z_{12} I_2 \Rightarrow z_{12} = \frac{V_1}{I_2}$$

$$V_2 = z_{22} I_2 \Rightarrow z_{22} = \frac{V_2}{I_2}$$

We can use Table 18.1 to convert to other parameters

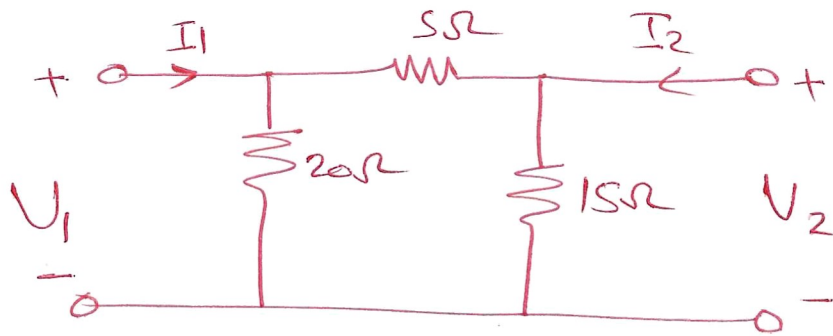Example: Determine the z-parameters using the z-parameter definitions for the network shown below



If $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 20 \parallel (s+15) = 10 \Omega \Rightarrow I_1 = \frac{V_1}{10}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_2 = \frac{V_1 (15)}{s+15} = 0.75 V_1$$

$$I_1 = \frac{V_1}{10}$$

$$\Rightarrow Z_{21} = \frac{0.75 V_1}{\frac{V_1}{10}} = 7.5 \Omega$$


If $I_1 = 0$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = (5+20) \parallel 15 = 9.375 \Omega \Rightarrow I_2 = \frac{V_2}{9.375}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$\Rightarrow Z_{12} = \frac{0.8 V_2}{\frac{V_2}{9.375}} = 7.5 \Omega$$

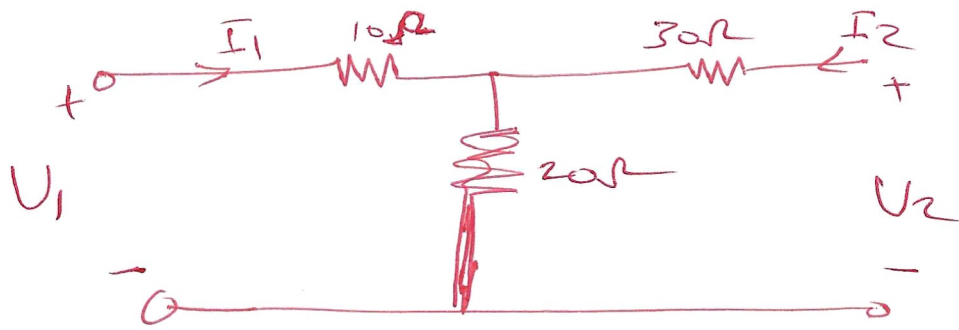Examples- Determine the Z-parameters using the Z-parameter definitions for the network shown below



for $I_2 = 0$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 10 + 20 = 30 \Omega \quad \Rightarrow \quad I_1 = \frac{V_1}{30}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad V_2 = 20 I_1$$

$$Z_{21} = \frac{20 I_1}{I_1} = 20 \Omega$$

for $I_1 = 0$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 30 + 20 = 50 \Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad V_1 = 20 I_2$$

$$Z_{12} = \frac{20 I_2}{I_2} = 20 \Omega$$

Example 8- The following measurements pertain to a two-port circuit operating in the sinusoidal steady state.

with port two open ($I_2 = 0$), a voltage equal to $150 \cos(4000t)$ V is applied to port 1. The current into port 1 is $25 \cos(4000t - 45^\circ)$ A, and the port 2 voltage is $100 \cos(4000t + 15^\circ)$ V. With port 2 short circuited ($V_2 = 0$), a voltage equals to $30 \cos(4000t)$ V is applied to port 1. The current into port 1 is $1.5 \cos(4000t + 30^\circ)$ A, and the current into port 2 is $0.25 \cos(4000t + 150^\circ)$ A. Find the parameters that can describe the sinusoidal steady state behavior of the circuit.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & -a_{12} \\ a_{21} & -a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = a_{11} V_2 - a_{12} I_2$$

$$I_1 = a_{21} V_2 - a_{22} I_2$$

for $I_2 = 0$


$$a_{11} = \frac{V_1}{V_2} = \frac{150 \angle 0^\circ}{100 \angle 15^\circ} = 1.5 \angle -15^\circ$$

$$a_{21} = \frac{I_1}{V_2} = \frac{25 \angle -45^\circ}{100 \angle 15^\circ} = 0.25 \angle -60^\circ \text{ S}$$

for $V_2 = 0$

$$a_{12} = \frac{V_1}{I_2} = \frac{-30 \angle 0^\circ}{0.25 \angle 150^\circ} = 120 \angle 30^\circ \Omega$$
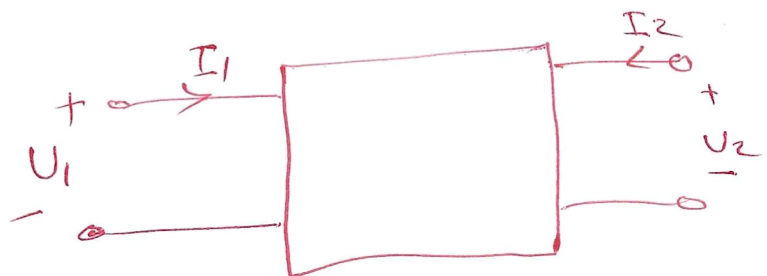
$$a_{22} = \frac{I_1}{I_2} = \frac{1.5 \angle 30^\circ}{0.25 \angle 150^\circ} = 6 \angle 60^\circ$$



for $I_2 = 0$ $V_1 = 150 \angle 0^\circ$, $V_2 = 100 \angle 15^\circ$, $I_1 = 25 \angle -45^\circ$

for $V_2 = 0$ $V_1 = 30 \angle 0^\circ$, $I_1 = 1.5 \angle 30^\circ$ A, $I_2 = 0.25 \angle 150^\circ$