

Chapter I - Circuit Variables

1.1 Electrical engineering - an overview

An electric circuit is a mathematical model that approximates the behavior of an actual electrical system

Three basic assumptions to use circuit theory

1) A lumped-parameter system of electrical effects happen instantaneously throughout a system.

If the wavelength of the signal is large compared to the physical dimensions of the system, we have a lumped-parameter system.

$$\lambda = \frac{c}{f} \quad c = 3 \times 10^8 \text{ m/s} \\ f = 50, 60 \text{ Hz}$$

If the dimension of the system is 1/10th (or smaller) of the dimension of the wavelength, we have a lumped-parameter system.

2) The net charge on every component in the system is always zero

3) There is no magnetic coupling between the components in a system.


1.2 The international system of units (SI)

Table 1.1, Table 1.2, Table 1.3

Basic and derived SI units Prefixes to signify power of 10

1.3 Circuit analysis - An overview

Analysis -

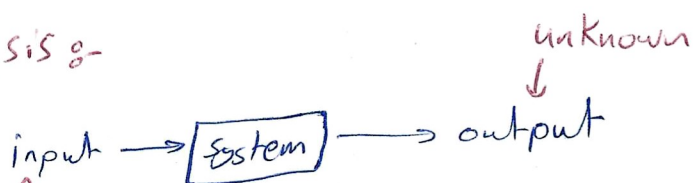

1.4 Voltage and Current

Voltage:- is the energy per unit charge created by the separation of positive and negative charge.


$$V = \frac{dw}{dq}$$

Current:- The rate of charge flow

$$i = \frac{dq}{dt}$$

1.5 Ideal and basic circuit element

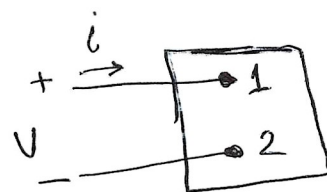- 1) has only two terminal
- 2) can be described mathematically in terms of current and voltage
- 3) can't be subdivided into other elements



ideal basic circuit element

* The passive sign convention

whenever the current in the element is in the direction of the voltage drop (from + to -),

use positive sign in any expression that relates the voltage to the current. otherwise, use negative


sign.

1.6 Power and energy

Power:- is the rate of expanding or absorbing energy

$$P = \frac{dw}{dt} = \left(\frac{dw}{dq} \right) \left(\frac{dq}{dt} \right) = Vi$$

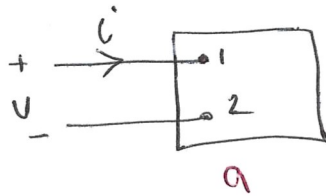
Example 9 - Suppose that we have selected the polarity reference shown in the figures below. Assume $i = 4A$ and $V = -10V$. Find the power associated with the terminal pair 1 and 2?



$$P = Vi$$

$$= (-10)(4) = -40 \text{ W}$$

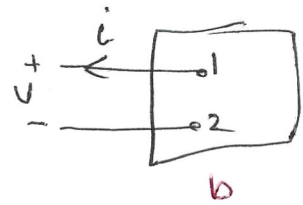
the circuit inside the box is **expanding power** Energy



$$P = -Vi$$

$$= -(-10)(4) = 40 \text{ W}$$


the circuit **absorbing power** Energy

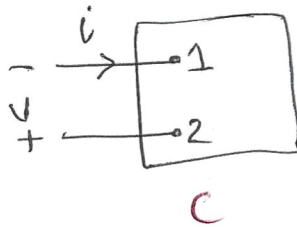

$$P = -Vi$$

$$= -(-10)(4) = 40 \text{ W}$$

Expanding Energy

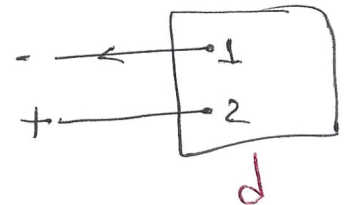

$$P = Vi$$

$$= (-10)(4) = -40 \text{ W}$$

Absorbing Energy