

# Forms on ch.3 By Rawan Alfares



A communication system for binary-coded decimal (BCD) codes uses even parity for error detection. Assume the sender wants to **send** the two numbers: 9 and 7. Then, the sender **transmits**:

(Note: In this communication system, the parity bit is padded/added for every transmitted BCD digit)

		even parity
9	→ 1001	01001
7	→ 0111	10111

- a. 0 1001 0111
- b. 01001 10111 ✓
- c. 1 1001 0111
- d. 11001 00111
- e. 1001 0111

The minimum product-of-sums (POS) expression for the Boolean function G(A, B, C, D) subject to the don't care conditions given in the following K-map is:

AB \ CD	00	01	11	10
00	X	1		
01	1	1	X	1
11	1	X	X	
10		1		X

← Kmap → SOP → min terms

$$G(A, B, C, D) = BC' + C'D + A'B$$





$$G(A, B, C, D) = (B'+C) \cdot (C+D) \cdot (A+B')$$

- a. None ✗
- b.  $G(A, B, C, D) = (B + D) \cdot (A' + C') \cdot (C' + D')$
- c.  $G(A, B, C, D) = (B' + C) \cdot (A + B') \cdot (C + D')$  ✓
- d.  $G(A, B, C, D) = (B + D) \cdot (A' + C') \cdot (B + C') \cdot (C' + D')$
- e.  $G(A, B, C, D) = (B' + D') \cdot (A + C) \cdot (B' + C)$

Consider the following K-map of the Boolean function F(W, X, Y, Z):

WX \ YZ	00	01	11	10
00	0	1	0	0
01	1	1	0	1
11	1	1	0	1
10	0	1	0	0


The gate-level implementation for the simplified complement of F expressed as sum-of-products (SOP) is:

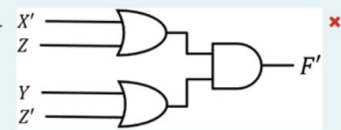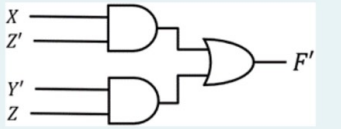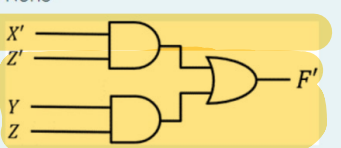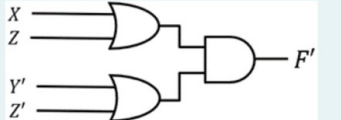- a.  ✗
- b. 
- c. None
- d.  ✓
- e. 


$$F = YZ' + XZ'$$

$$F' = (Y+Z') \cdot (X'+Z)$$

$$F' = YZ + X'Z'$$

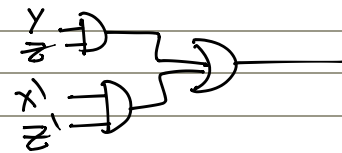


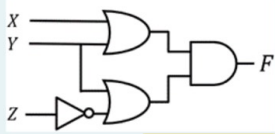Given the following circuit diagram with AND/OR/NOT gates:




The equivalent **NAND gates only** implementation of the above circuit is:

- a.
- b.
- c.
- d.
- e.

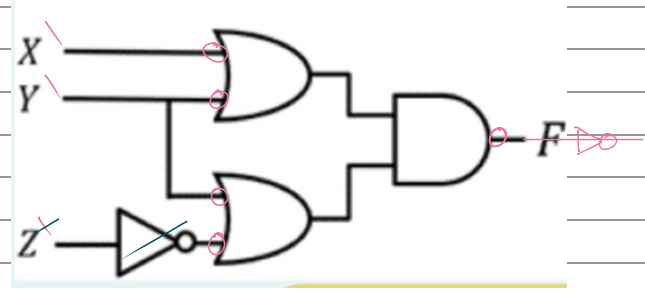

The following circuit is equivalent to:

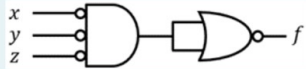

- a. 3-input **NAND** gate
- b. 3-input **AND** gate
- c. 3-input **NOR** gate
- d. 3-input **XNOR** gate
- e. 3-input **OR** gate ✓

Given the Boolean function  $F(W, X, Y, Z) = \prod(0, 1, 2, 5, 8, 9, 10)$ , which of the following is **not** a **Prime Implicant** of F?

$$= \sum(3, 4, 6, 7, 11, 12, 13, 14, 15)$$

- a.  $XZ'$
- b. None
- c.  $XY$  ✗
- d.  $YZ$
- e.  $WX$

W\YZ	00	01	11	10
00			1	
01	1		1	1
11	1	1	1	1
10			1	

$$(XZ', WX, YZ, XY) \text{ PI}$$

Which of the following expressions is **not** equivalent to  $X'$ ?

- a.  $X \text{ NOR } 1$  ✓  $(X+1)' = 0' = 1$
- b.  $X \text{ NOR } X \rightarrow (X+X)' = X'$
- c.  $X \text{ NAND } 1 \rightarrow (X \cdot 1)' = X'$
- d.  $X \text{ NAND } X \rightarrow (X \cdot X)' = X'$
- e.  $X \text{ XOR } 1 \rightarrow (X \oplus 1) = X'$



Consider the circuit with the following truth table. The circuit has three inputs; **A**, **B**, and **C**.  
The output **Z** = \_\_\_\_\_






A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

A \ BC	00	01	11	10
0	1	0	0	1
1	1	0	0	1


$$F = C'$$

- a.  $BC + B'C$
- b.  $B'C' + BC'$
- c.  $C'$  ✓
- d. None
- e.  $B'$

The implementation of Boolean function  $F(A, B, C, D) = (A + B) \cdot (C' \cdot D')$  using NOR gates only is:

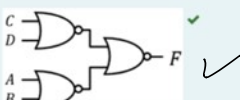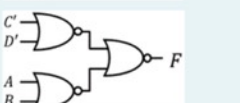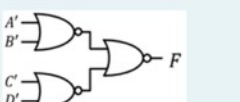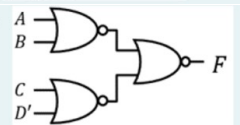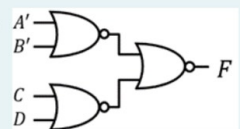- a.  ✓
- b. 
- c. 
- d. 
- e. 

$$c + D$$

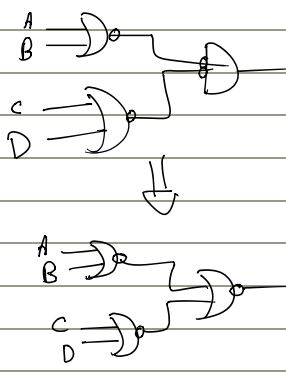

Consider the Boolean function  $F(W, X, Y, Z) = \sum(0, 1, 2, 4, 6, 10, 12)$  which has the don't care conditions  $D(W, X, Y, Z) = \sum(7, 13, 14, 15)$ , the minimum sum-of-products (SOP) expression of **F** is:

- a.  $F(W, X, Y, Z) = W'X'Y + W'Z + YZ'$
- b.  $F(W, X, Y, Z) = W'X'Y + W'Z + XZ'$
- c.  $F(W, X, Y, Z) = W'X'Y + W'Z + XZ' + YZ'$  ✗
- d.  $F(W, X, Y, Z) = W'X'Y + XZ' + YZ'$  ✓
- e.  $F(W, X, Y, Z) = W'X'Y + WX + XZ' + YZ'$

Wx \ YZ	00	01	11	10
00	1	1	0	1
01	1	0	X	1
11	1	X	X	X
10	0	0	0	1

$$w'x'y + xz' + yz'$$

The Boolean function  $F(A, B, C, D) = A \oplus B \oplus C \oplus D = 1$  means: → number of ones is odd

- a. Half of the inputs are zeros (for example:  $A = 0, B = 0, C = 1, D = 1$ )
- b. One or three of the inputs are ones ✓
- c. All inputs are zeros ( $A = 0, B = 0, C = 0, D = 0$ )
- d. One or two or three of the inputs are ones
- e. All inputs are ones ( $A = 1, B = 1, C = 1, D = 1$ )

Given the following K-map of the Boolean function  $F(W, X, Y, Z)$ :

YZ	00	01	11	10
WX	1	1	0	1
01	1	X	X	1
11	0	X	X	0
10	1	1	0	0

$w^1z^1$

$x^1y^1$

Which of the following is an **Essential Prime Implicant** of  $F$ ? (Select all that apply)

- a.  $W'Y'$
- b.  $X'Y'$  ✓
- c.  $W'Z'$  ✓
- d.  $Y'Z$
- e.  $W'X$