

Experiment #8

Pre Lab

Name : Mohammed Jamil Saada


Number : 1221972

A) Build half adder on data flow.

Code :

```
1 module Half_Adder(input A,B, output Sum, C_Out);
2
3 //Mohammed Jamil Saada - 1221972
4 //Half Adder on Data Flow
5
6 assign Sum = A^B;
7 assign C_Out = A&B;
8
9 endmodule |
```

Wave form :

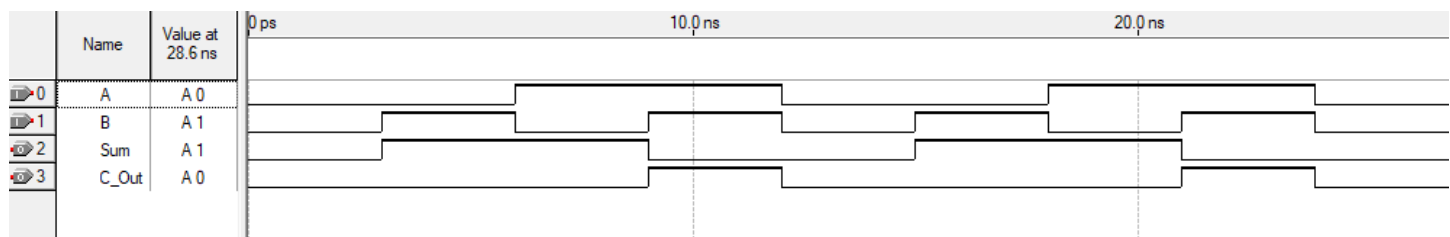


B) Build full adder using half adder structural.

Code :

```
1 module Full_Adder(input A, B, C_in, output Sum, C_out);
2
3 //Mohammed Jamil Saada - 1221972
4 //Full Adder using Half Adder Structural
5
6 wire w1, w2, w3;
7 Half_Adder(A,B,w1,w2);
8 Half_Adder(C_in,w1,Sum,w3);
9 or gate(C_out,w2,w3);
10
11 endmodule
```

Wave form :

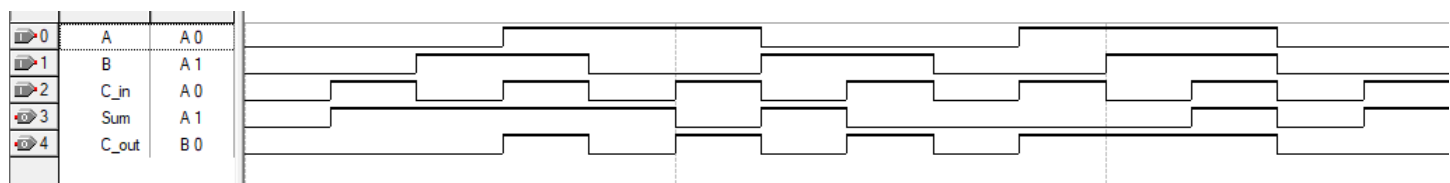


C) Build a 2-bit counter on behavioral.

Code :

```
1 module TwoBit_Counter(output reg[1:0]count, input clk, reset);
2
3 //Mohammed Jamil Saada - 1221972
4 // 2-bit counter on behavioral
5
6 always @(posedge clk, posedge reset) begin
7
8     count = 2'b00;
9
10    count = count+1;
11 end
12
13 endmodule
```

Wave form :

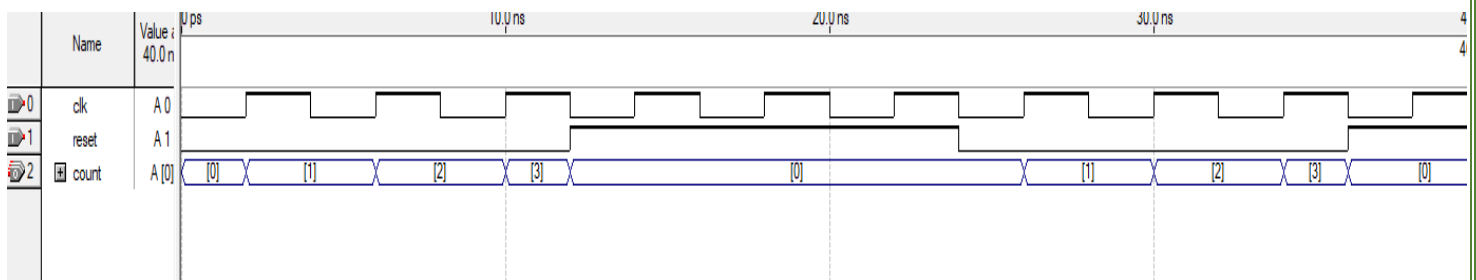


D) Build an 8x1 Multiplexer on behavioral.

Code :

```
1 module Mux_8to1(output reg F, input [7:0] I, input [2:0] selection);
2
3 //Mohammed Jamil Saada - 1221972
4 // 8x1 Multiplexer on behavioral
5
6 always @(*) begin
7     case(selection)
8         3'b000 : F = I[0];
9         3'b001 : F = I[1];
10        3'b010 : F = I[2];
11        3'b011 : F = I[3];
12        3'b100 : F = I[4];
13        3'b101 : F = I[5];
14        3'b110 : F = I[6];
15        3'b111 : F = I[7];
16    endcase
17 end
18 endmodule
```

Wave form :

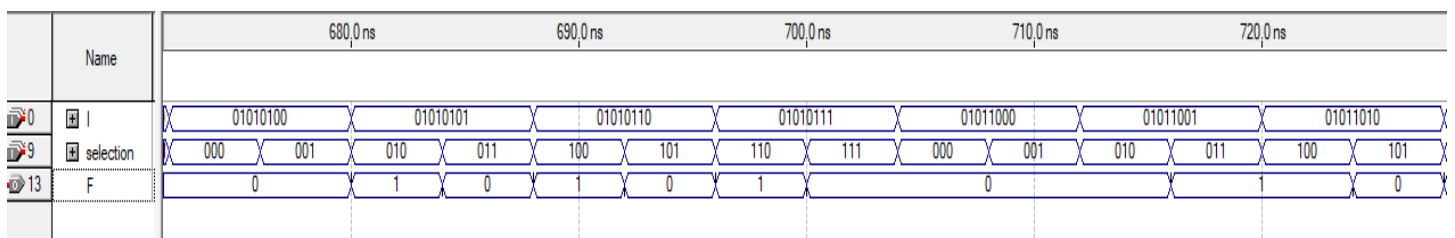


E) Build a 2x4 Decoder using basic gates (structural).

Code :

```
1 module Decoder_2to4(output D0, D1, D2, D3, input I0, I1);
2
3 //Mohammed Jamil Saada - 1221972
4 //2x4 Decoder using basic gates (stuctural)
5
6 wire i0, i1;
7 not gate1(i0,I0);
8 not gate2(i1,I1);
9 //i0 = I0' ,, i1 = I1'
10 and gate3(D0,i0,i1);
11 and gate4(D1,I0,i1);
12 and gate5(D2,i0,I1);
13 and gate6(D3,I0,I1);
14
15 endmodule |
```

Wave form:

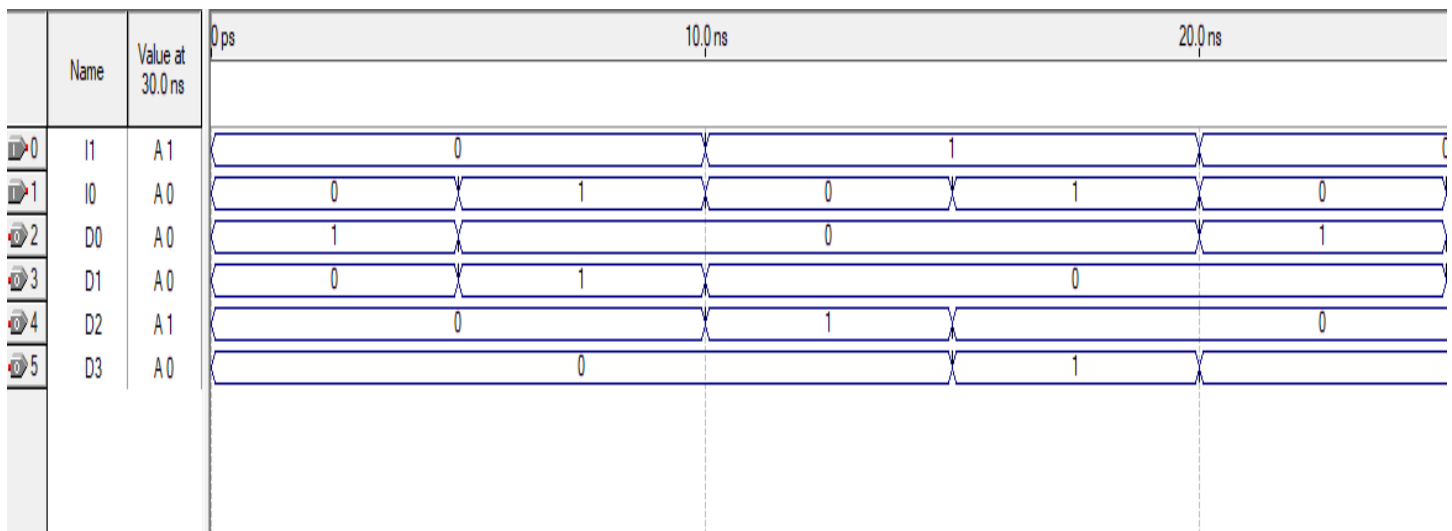

F) Show the wave form for above parts.

I have attached the wave form for each part above.